

## Chapter 3.


### — Gate level Minimization. —

- How to make cost Reduction for any digital circuit.
- The complexity of digital logic gates is directly proportional to the boolean expression from which the Function implemented.

ex  $F = x \cdot y + x \cdot y'$

$$F = x(y + y')$$

More simplify  $F = X$ .

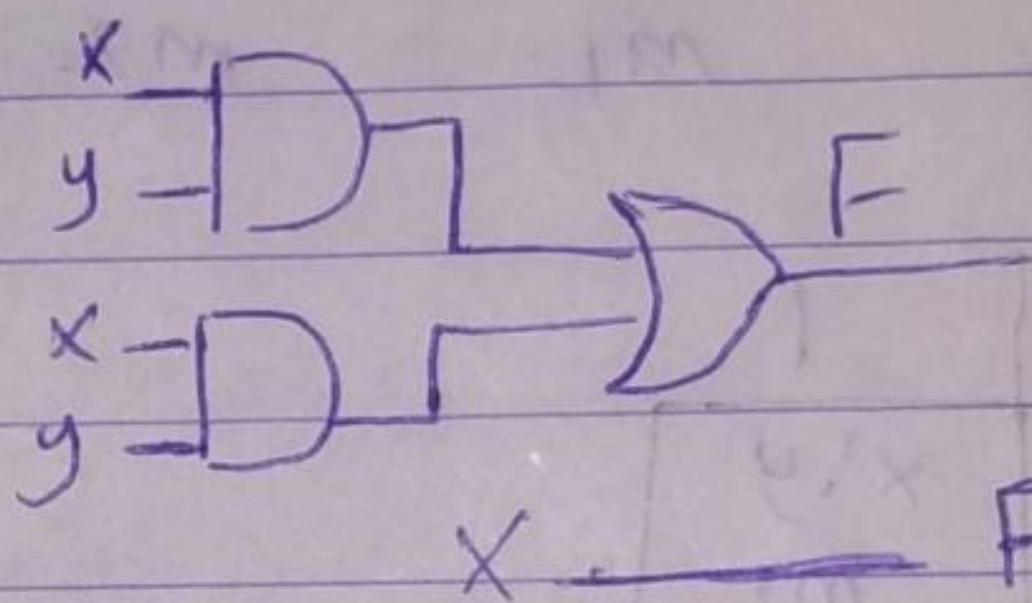

"Boolean Algebra".

ch 2.

غير مباشر

\* Minimize the Function using algebra is a keyword approach, so we need another way for minimization.

الطريقة البسيطة هي اقرب الى المباشرة

\* Map Method for Minimization.

Note :- Truth table is unique.

$$F = x \cdot y + x \cdot y' \equiv F = X$$

$$X = 0$$

$$F = 0$$

$$X = 1$$

$$F = 1$$

Mathematical expression

is not unique.

X	Y	F
0	0	0.0.0 + 0.0.1
0	1	0.0.1 + 0.1.1
1	0	1.0.0 + 1.0.1
1	1	1.1.1 + 1.1.0



K-map method for minimization.

Diagram made of squares, each square represent one minterm.

ex Two variables maps.

2 variables  $\Rightarrow 2^2 = 4$  minterms.

$x'y'$      $x'y$      $xy'$      $xy$   
 $m_0$      $m_1$      $m_2$      $m_3$

$x \backslash y$	0	1
0	$x'y'$ $m_0$	$x'y$ $m_1$
1	$x.y'$ $m_2$	$x.y$ $m_3$

ex Minimize the Following Function.

$$F(x, y) = x'y + x.y' + x.y$$

Algebra

Sum of minterms.

$$= m_1 + m_2 + m_3 = [1, 2, 3]$$

$$F(x, y) = x'y + x(y + y')$$

$$= x'y + x = (x + x') \cdot (x + y)$$

$$= x + y$$

$x \backslash y$	0	1
0	0	1
1	1	1

one variable



ex  $F(x, y) = \overset{m_0}{x' \cdot y'} + \overset{m_1}{x' \cdot y} + \overset{m_3}{x \cdot y}$

$= x' (y' + y) + x \cdot y$

$= x' + x \cdot y$

$= (x' + x) \cdot (x' + y) = x' + y$

Algebra.

K-map :-

y		0	1
x	0	0	1
	1	0	1

ال  $y$  تغيرت  
وال  $x$  ثابتة على 0

ال  $x$  تغيرت  
وال  $y$  ثابتة على 1

ex  $F = x' \cdot y' + x \cdot y$

$= m_0 + m_3$

$F = x' \cdot y' + x \cdot y$

y		0	1
x	0	0	1
	1	1	1



# \* Three Variable maps:

3 variable  $\Rightarrow$  max & minterm.  
= 8 squares.

$\begin{matrix} yz \\ x \end{matrix}$	00	01	11	10
0	$x'y'z'$ m0	$x'y'z$ m1	$x'yz$ m3	$x'yz'$ m2
1	$xy'z'$ m4	$xy'z$ m5	$xyz$ m7	$xyz'$ m6

ex Minimize the following function using k-maps  
 $F(x, y, z) = \sum (0, 1, 3, 7)$

$\begin{matrix} yz \\ x \end{matrix}$	00	01	11	10
0	1	1	1	
1			1	

$x \cdot y'$  (grouping the first row)  
 $y \cdot z$  (grouping the third column)

$$x \cdot y' + y \cdot z$$



ex  $F(A, B, C) = \sum (0, 1, 2, 3)$

A \ BC	00	01	11	10
0	1	1	1	1
1				

$A'$

ex  $F(A, B, C) = \sum (0, 1, 2, 3, 4, 6)$

A \ BC	00	01	11	10
0	1	1	1	1
1	1			1

$A'$

$A' + C'$

ex  $F(A, B, C) = \sum (0, 2, 4, 5, 6, 7)$

A \ BC	00	01	11	10
0	1			1
1	1	1	1	1

$A + C'$

$(1 \text{ is } A)$



ex  $F(A, B, C) = \sum 3, 5, 6, 7$

BC \ A	00	01	11	10
0	0	1	1	0
1	1	1	1	1

$AC$  (orange box around cells (1,01), (1,11))  
 $B \cdot C$  (purple oval around cells (0,11), (1,11))  
 $A \cdot B$  (purple box around cells (1,01), (1,11), (1,10))

$AC + BC + AB$

\* Four variables maps :-

$F(A, B, C, D) = 4 \text{ variables}$

16 minterms = 16 squares

CD \ AB	00	01	11	10
00	$A'B'C'D'$ m0	$A'B'CD'$ m1	$A'BCD'$ m3	$A'B'CD$ m2
01	$A'B'CD$ m4	$AB'C'D'$ m5	$A'BCD$ m7	$AB'CD'$ m6
11	$ABCD'$ m12	$AB'CD$ m13	$ABCD$ m15	$AB'CD'$ m14
10	$AB'CD$ m8	$AB'C'D$ m9	$AB'CD$ m11	$AB'CD'$ m10



ex Minimize using K-map.

$$F(A, B, C, D) = \sum (0, 1, 4, 5, 7)$$

AB \ CD	00	01	11	10
00	1	1		
01	1	1	1	
11				
10				

$$\bar{A}\bar{C} + \bar{A}BD$$

ex Minimize using K-map.

$$F(A, B, C, D) = \sum 0, 2, 4, 6, 8, 10.$$

AB \ CD	00	01	11	10
00	1			1
01	1			1
11				
10	1			1

$$\bar{A}\bar{D} + \bar{B}\bar{D}$$



ex  $F(A, B, C, D) = \sum(0, 1, 2, 3, 5, 7, 13, 15, 9, 11)$

AB \ CD	00	01	11	10
00	1	1	1	1
01		1	1	
11		1	1	
10		1	1	

$\bar{A}\bar{B}$  (points to the first row)  
 $D + \bar{A}\bar{B}$  (points to the first column)  
 $D$  (points to the first column)

ex  $F(A, B, C, D) = \sum(0, 2, 4, 6, 8, 10, 12, 14)$

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	1			1
10	1			1

$\bar{D}$  (points to the first and fourth columns)



\* Five variables maps = 32 minterms.

Note :-  $F(A, B, C) = \sum 0, 2, 4, 6$ .

A = 0				A = 1					
A	B	C	F	B	C	F	B	C	F
0	0	0	1	0	0	1	0	0	1
0	0	1	0	0	1	0	0	1	0
0	1	0	1	1	0	1	1	0	1
0	1	1	0	1	1	0	1	1	0
1	0	0	1	1	0	1	1	0	1
1	0	1	0	1	1	0	1	1	0
1	1	0	1	1	1	0	1	1	0
1	1	1	0	1	1	1	1	1	1

AB	
00	
01	1
10	0
11	

AB = 01	
C	F
0	1
1	0

AB = 10	
C	F
0	1
1	0

AB = 11	
C	F
0	1
1	0



ex Minimize  $F(A, B, C, D, E) = \{6, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31\}$

$A = 0$

$A = 1$

BC \ DE	00	01	11	10
00	AB $\bar{C}\bar{D}\bar{E}$ m0	m1	m3	AB $\bar{C}\bar{D}E$ m2
01	m4	m5	m7	m6
11	m12	m13	AB $\bar{C}DE$ m5	m14
10	m8	m9	m11	m10

BC \ DE	00	01	11	10
00	m16	m17	m19	m18
01	m20	m21	m23	m22
11	m28	m29	m31	m30
10	m24	m25	m27	m26

BC \ DE	00	01	11	10
00	1			1
01	1			1
11		1		
10		1		

BC \ DE	00	01	11	10
00				
01		1	1	
11		1	1	
10		1		

ACE

$B\bar{D}E$

$$\bar{A}\bar{B}\bar{E} + A\bar{D}E + ACE$$



\* 6 variable maps. (مخطط 6 متغيرات)


$$F(A, B, C, D, E, G) = \sum$$

$$\underline{AB = 00}$$

$$\underline{AB = 01}$$

$$\underline{AB = 11}$$

$$\underline{AB = 10}$$

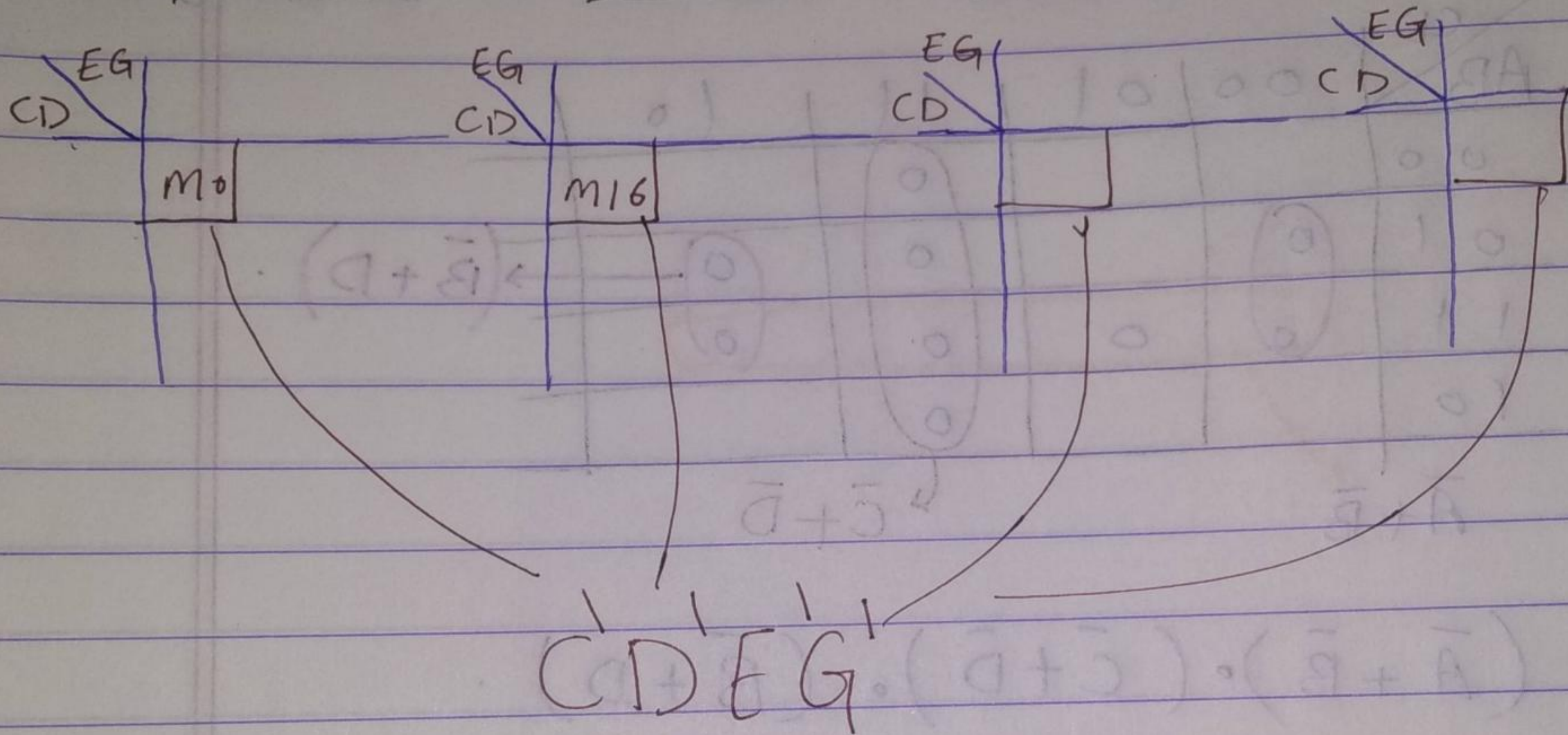



\* product of maxterm :-

Simplify the following Function.

$$F(A, B, C, D) = \prod(3, 4, 6, 7, 11, 12, 13, 14, 15)$$

AB \ CD	00	01	11	10
00			0	
01	0		0	0
11	0	0	0	0
10			0	

$\bar{A} + \bar{B}$        $\bar{C} + \bar{D}$        $(\bar{B} + D)$

$$(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) \cdot (\bar{B} + D)$$



## \* Don't Care Condition \*

Function that have unspecified outputs for some inputs.

The unspecified minterm of a function are don't care condition denoted by  $x$ .

ex Simplify the boolean function.

$$F(w, x, y, z) = \sum (1, 3, 7, 11, 15)$$

that has don't care condition.

$$d(w, x, y, z) = \sum (0, 2, 5)$$

w	x	y	z	F
0	0	0	0	X
0	0	0	1	1
0	0	1	0	X
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	1

w \ x \ yz	yz			
	00	01	11	10
00	X	1	1	X
01		1*	1	
11			1	
10			1	

$$w'z + yz$$

\* أو بتقدير نعمل الصف الأول والحدان  
ونؤخذ الصف الأول بتعريفه  
 $yz + w'x'$



# \* Prime Implicant (PI)

ex  $F(A, B, C, D) = \sum (0, 2, 5, 7, 8, 10, 13, 15)$

CD \ AB	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1

$B'D'$  [essential PI]  $\rightarrow$  0, 2, 8, 10  
 [ = term ]  
 $BD$  [term essential]  $\rightarrow$  5, 7, 13, 15  
 [essential PI]

$F(A, B, C, D) = \sum (0, 2, 5, 7, 8, 10, 13, 14, 15)$

CD \ AB	00	01	11	10
00	1			1
01		1	1	1
11		1	1	1
10	1			1

$B'D'$  [EPI]  $\rightarrow$  0, 2, 8, 10  
 $BC$  [PI]  $\rightarrow$  5, 7, 13, 14, 15  
 $CD'$  [PI]  $\rightarrow$  5, 7, 13, 14, 15  
 $BD$  [EPI]  $\rightarrow$  5, 7, 13, 14, 15

not essential  
 (لا يُعتبر، لأنه لا يغطي جميع الحالات)

(1) -  $BD + B'D' + CD'$

(2) -  $BD + B'D' + BC$



ex  $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 9, 10, 11, 13, 15)$

AB \ CD	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1	1	1	1

$B'D' [EPI]$  (0, 2)  
 ما نكتبه لا بمرحلة واحدة.  
 $BD [EPI]$   
 $AB'$   
 $AD$

$$F = B'D' + BD + AD$$

$$= BD' + BD + AB'$$


ex  $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 9, 10, 11, 13, 14, 15, 6)$

AB \ CD	00	01	11	10
00	1			1
01		1	1	1
11		1	1	1
10	1	1	1	1

$B'D' [EPI]$   
 $BC [PT]$   
 $AD [PT]$   
 $BD [EPI]$





XOR

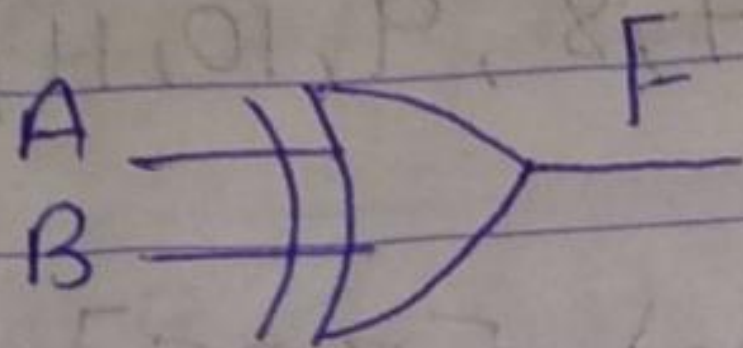


A	B	F
0	0	0
0	1	1 ← A'B
1	0	1 ← AB'
1	1	0

$$F = m_1 + m_2$$

$$= A'B + AB'$$

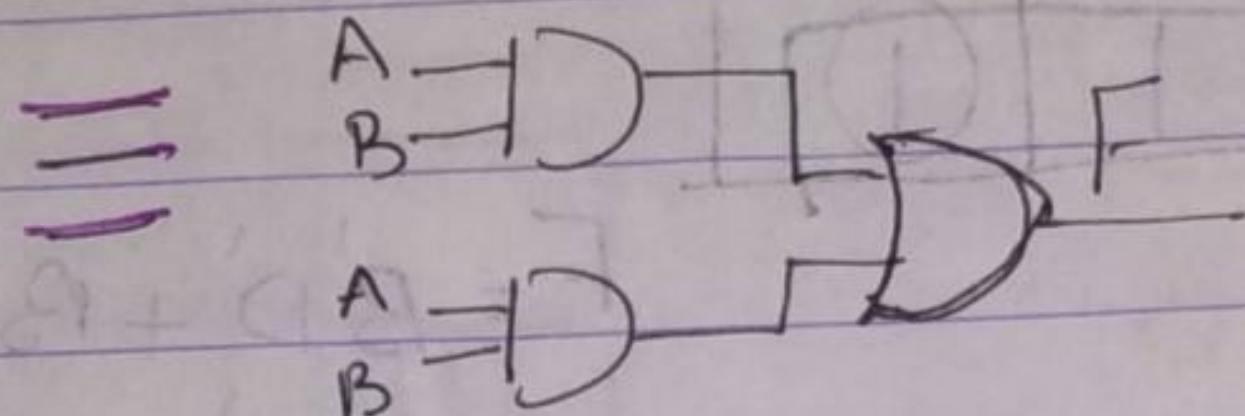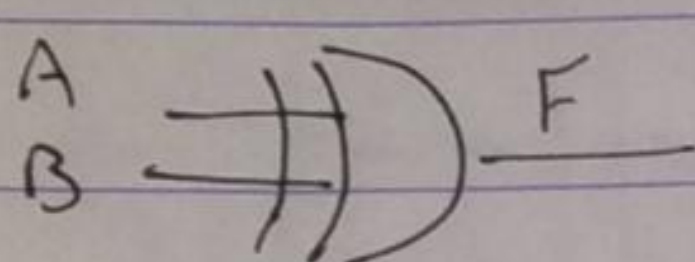

XNOR

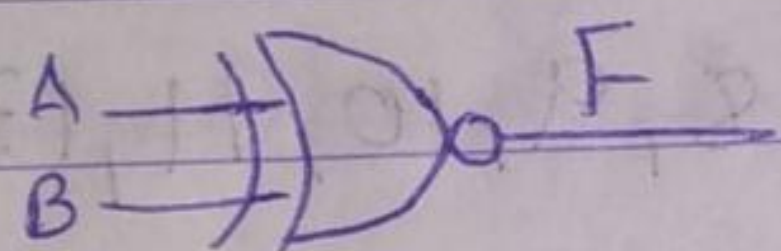

A	B	F
0	0	1 ← A'B'
0	1	0
1	0	0
1	1	1 ← AB

$$F = \overline{A \oplus B}$$

$$F = m_0 + m_3$$

$$= A'B' + AB$$

$$(A'B' + AB)' \equiv A'B + AB'$$

$$XNOR = (A \oplus B)' = [A'B + AB']'$$

$$= (A'B)' \cdot (AB)'$$

$$= (A + B') \cdot (A' + B)$$

$$= \cancel{AA'} + AB + A'B' + \cancel{B'B}$$

$$= AB + A'B'$$






Note All gates are associated except


NAND

NOR

$$(A + B + C) \oplus R = (A + B) + C$$

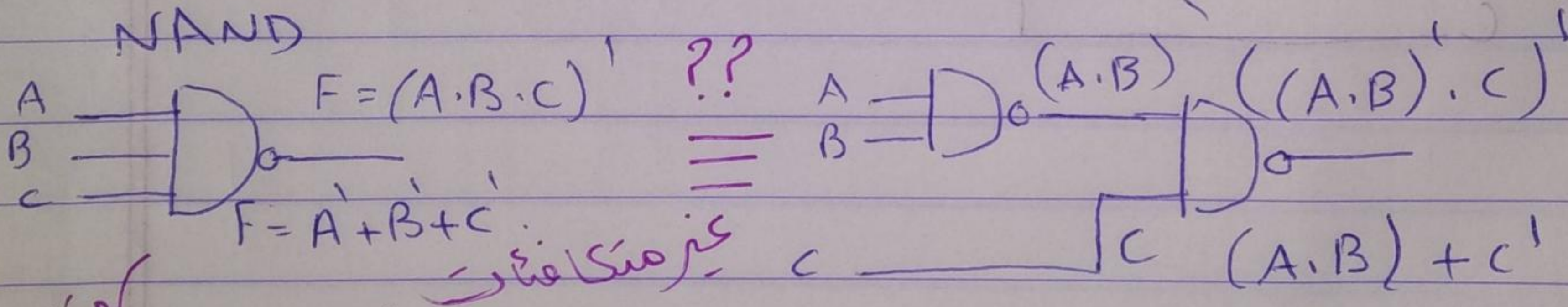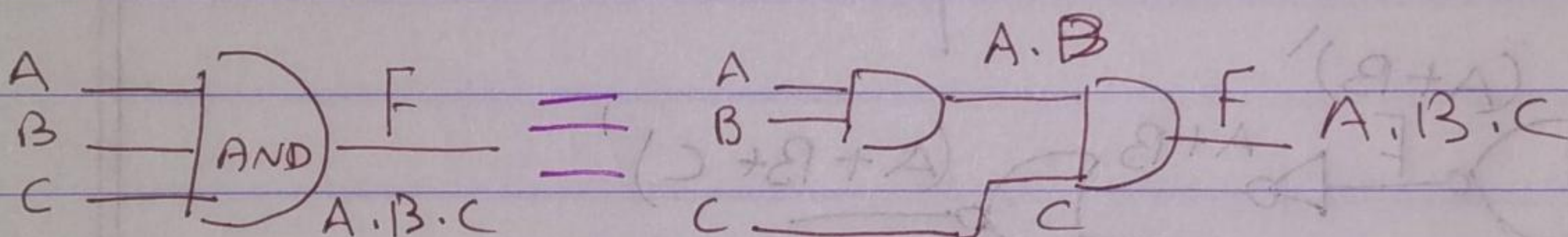
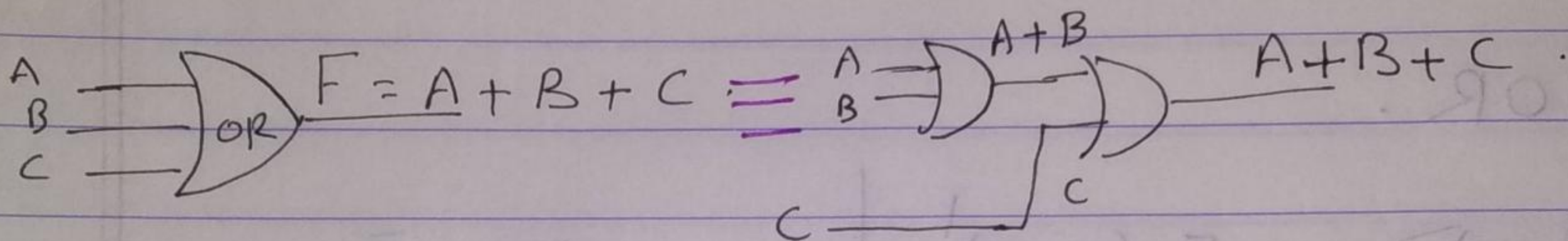


مسافین

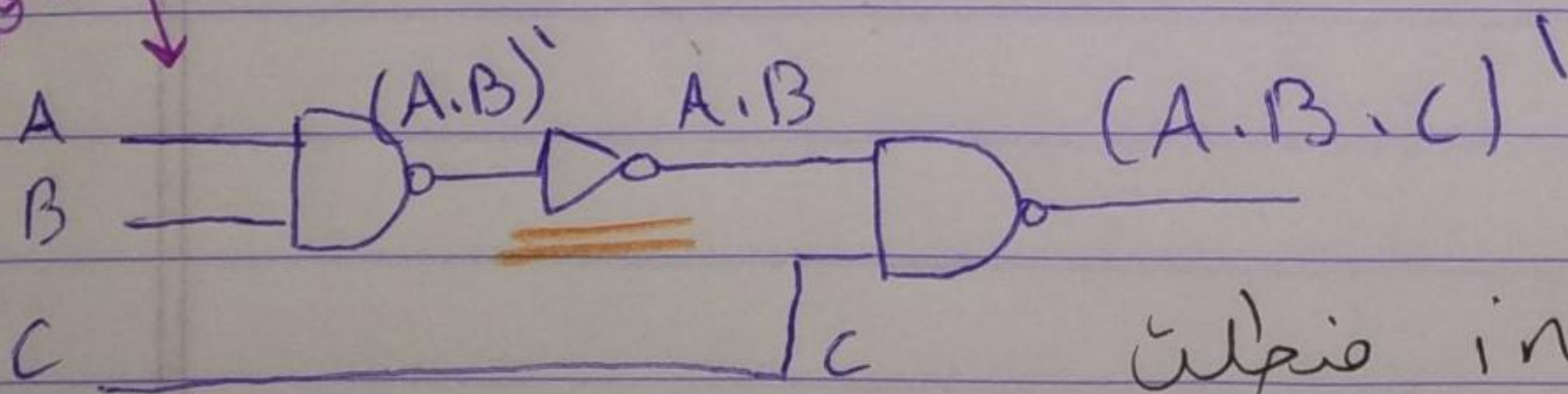



inverter lies associated.



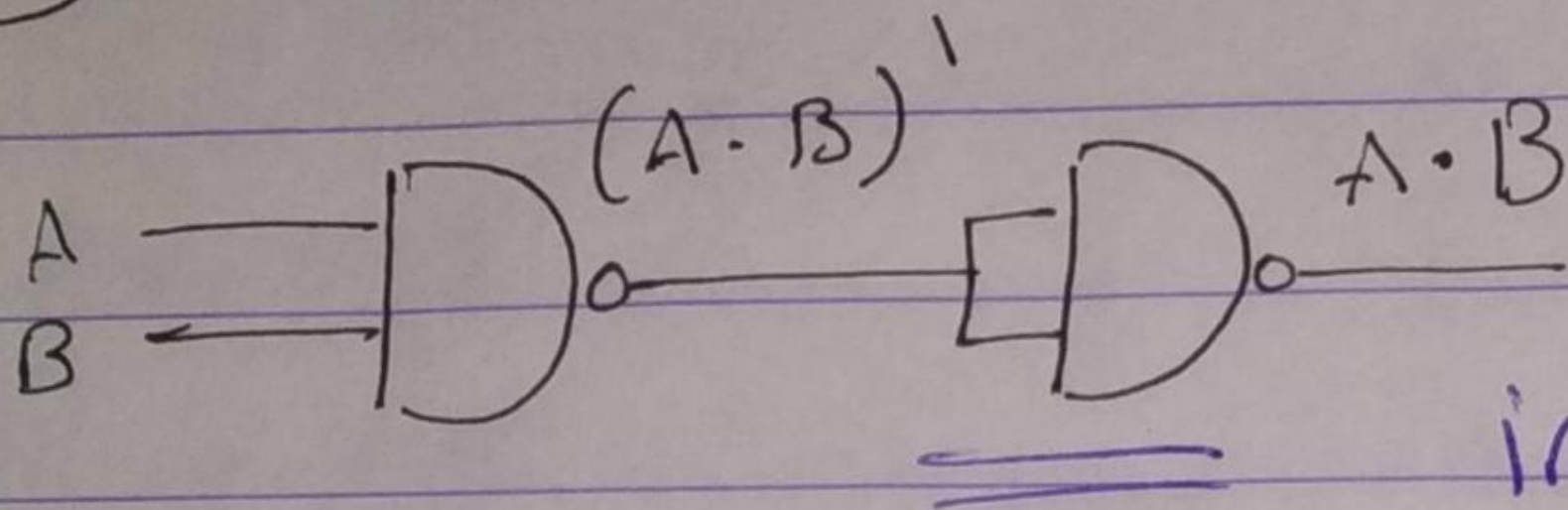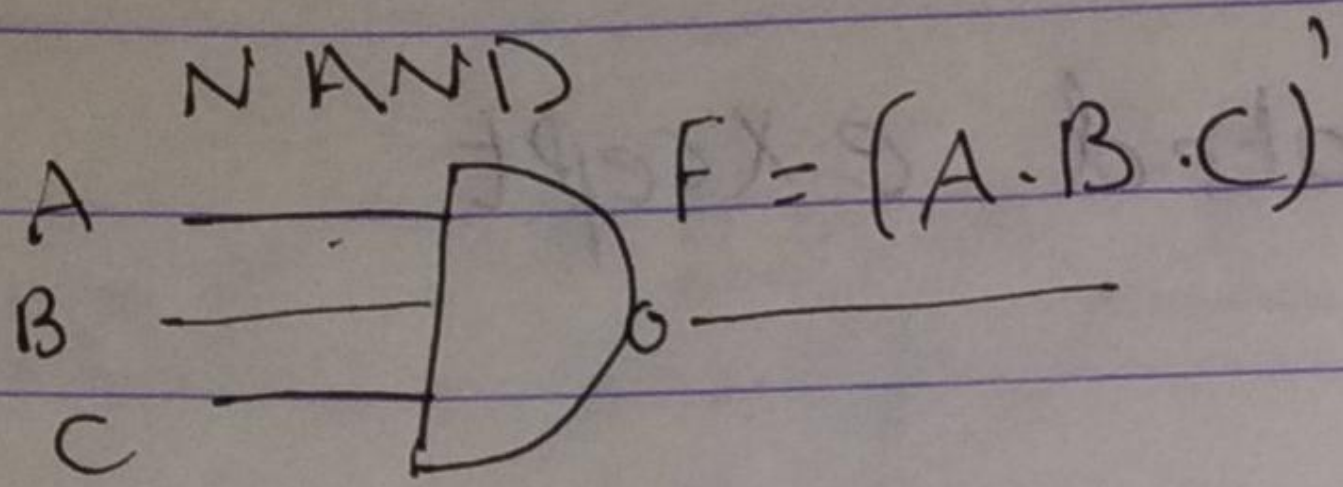

inverter \*

NOR

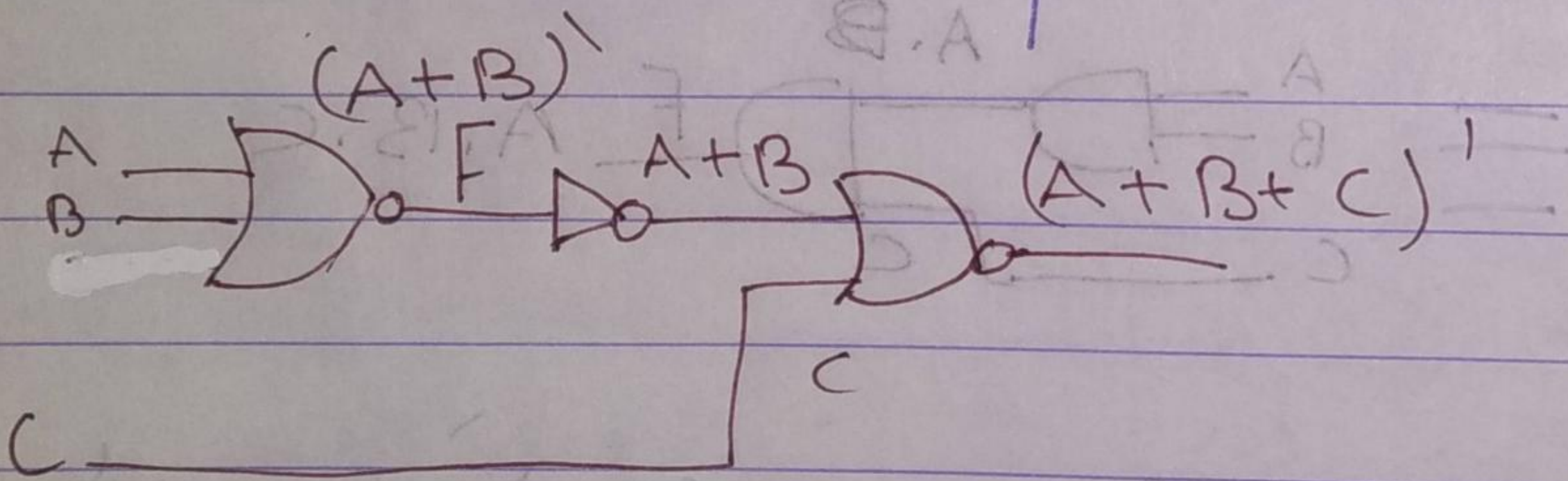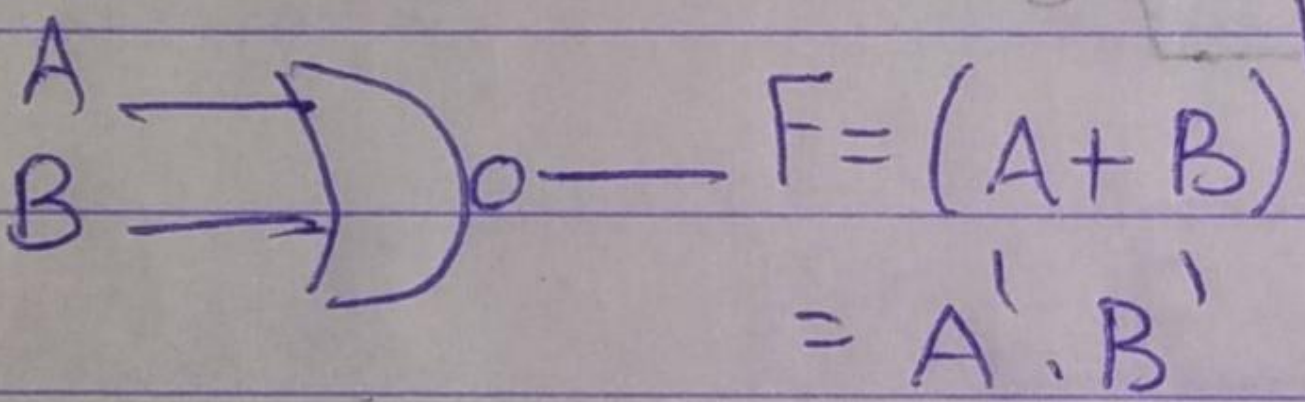




# NAND & NOR Implementation.

Digital circuits are more frequently constructed with NAND/NOR than and/or.

① NAND/NOR use fewer number of transistors.



so ① it's cheaper. ② less delay.

③ NAND/NOR universal gates.

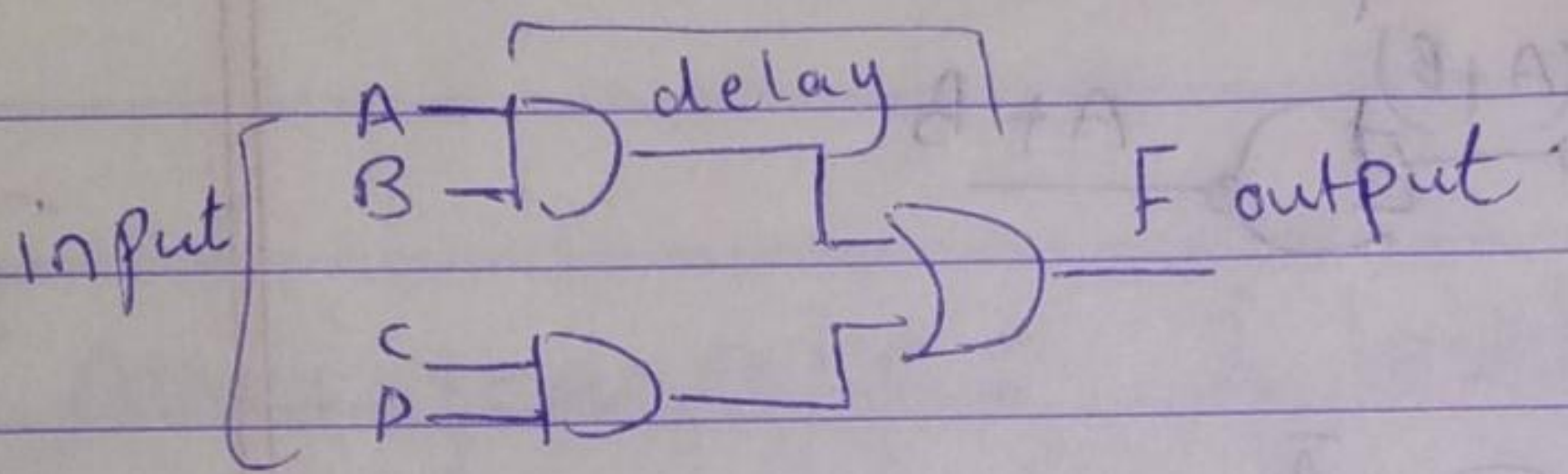


$$A \text{ --- } B \text{ --- } F = (A \cdot B)' = A' + B'$$


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

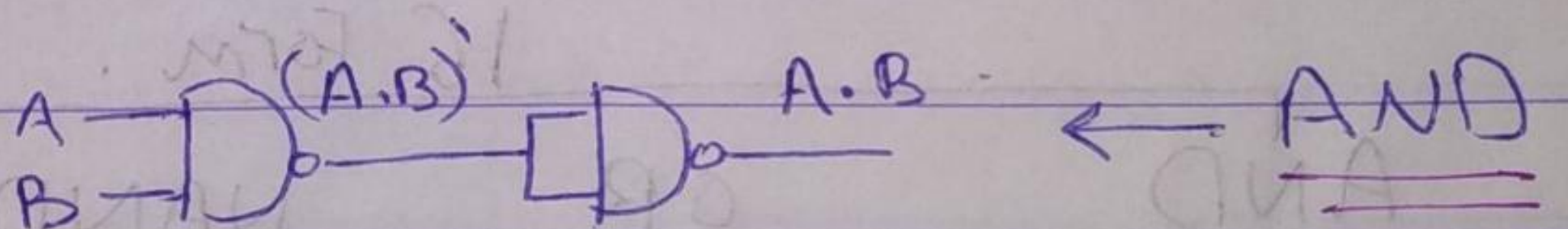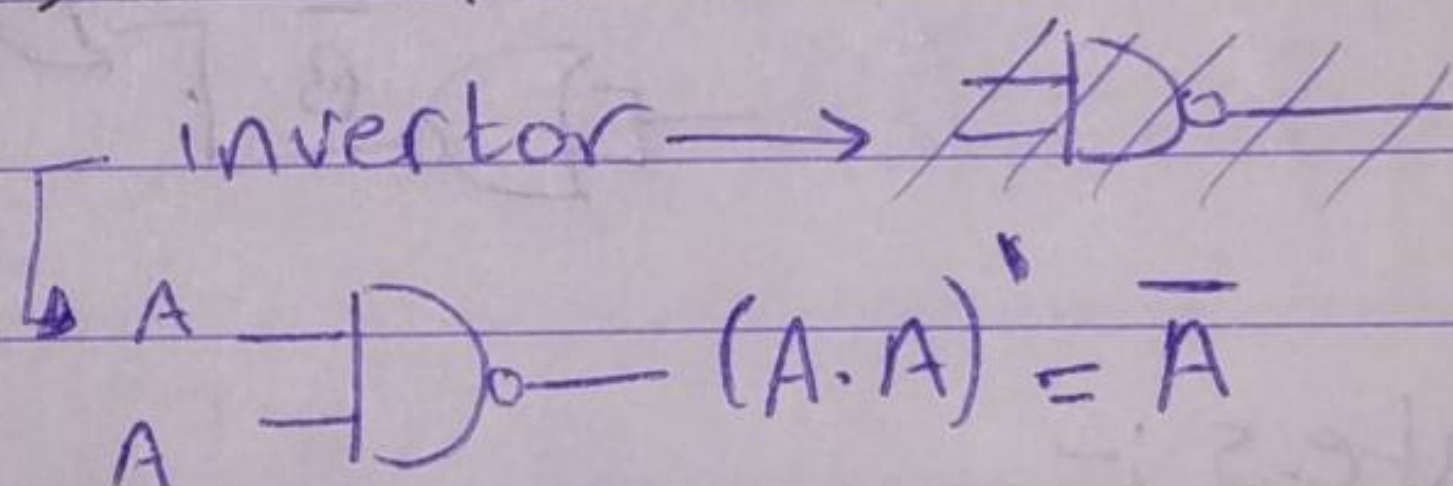

③ OR

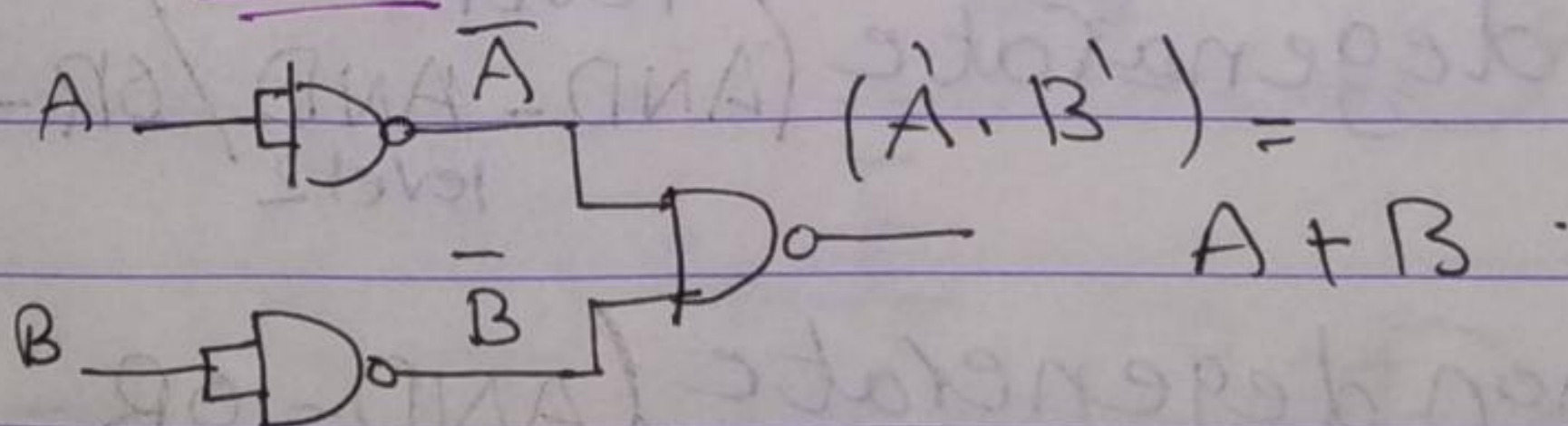


Transistor is an Electronic Device

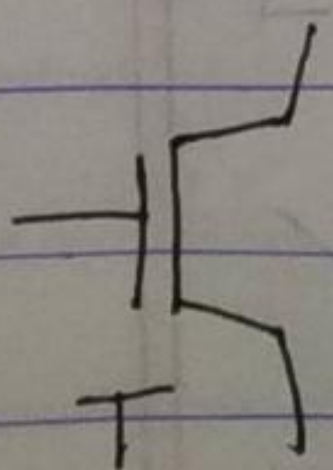

لا يوصل (نقل) ، (نقل) ، (نقل) open circuit




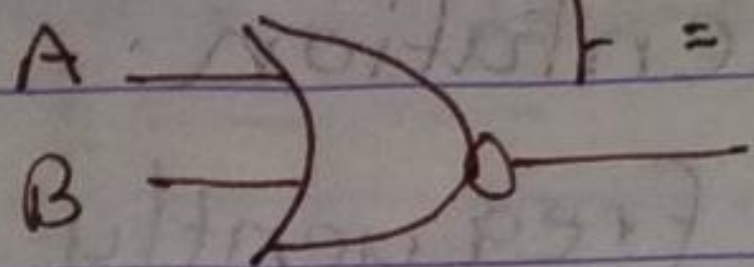NOR .  $F = (A+B)' = \bar{A} \cdot \bar{B}$




A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


(1) Inverter

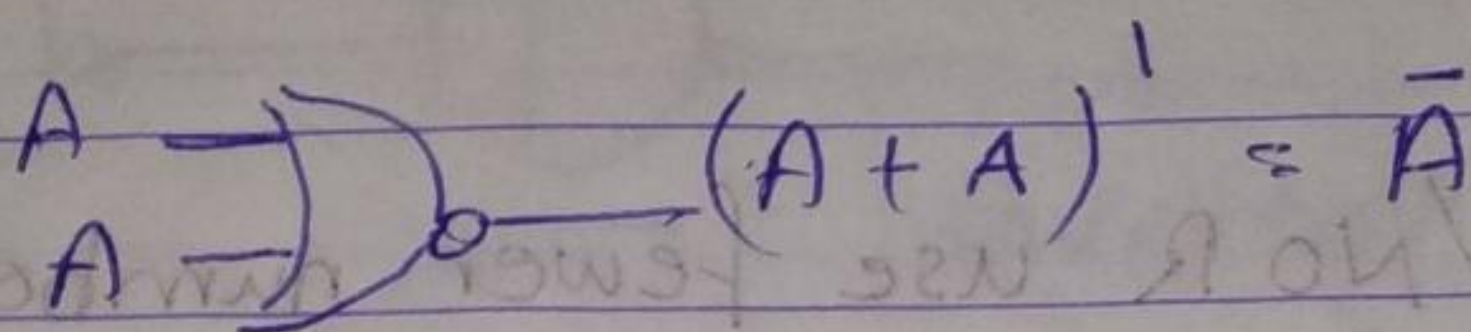

(2)

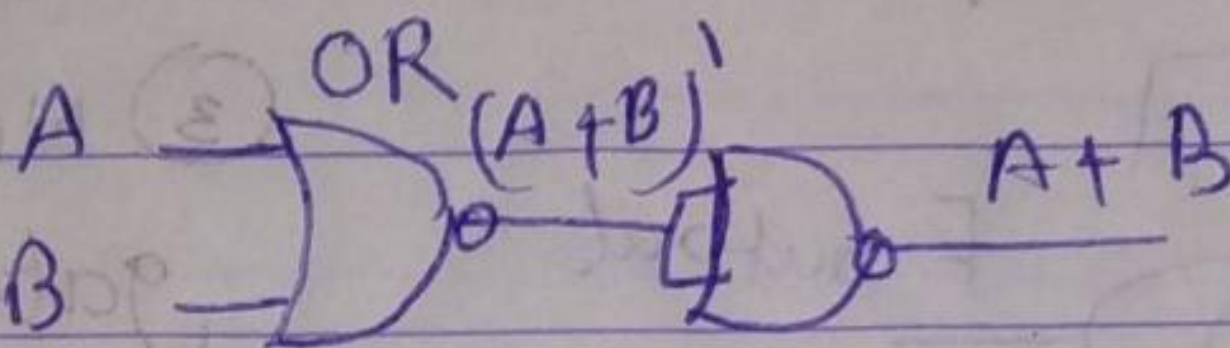

(3) AND

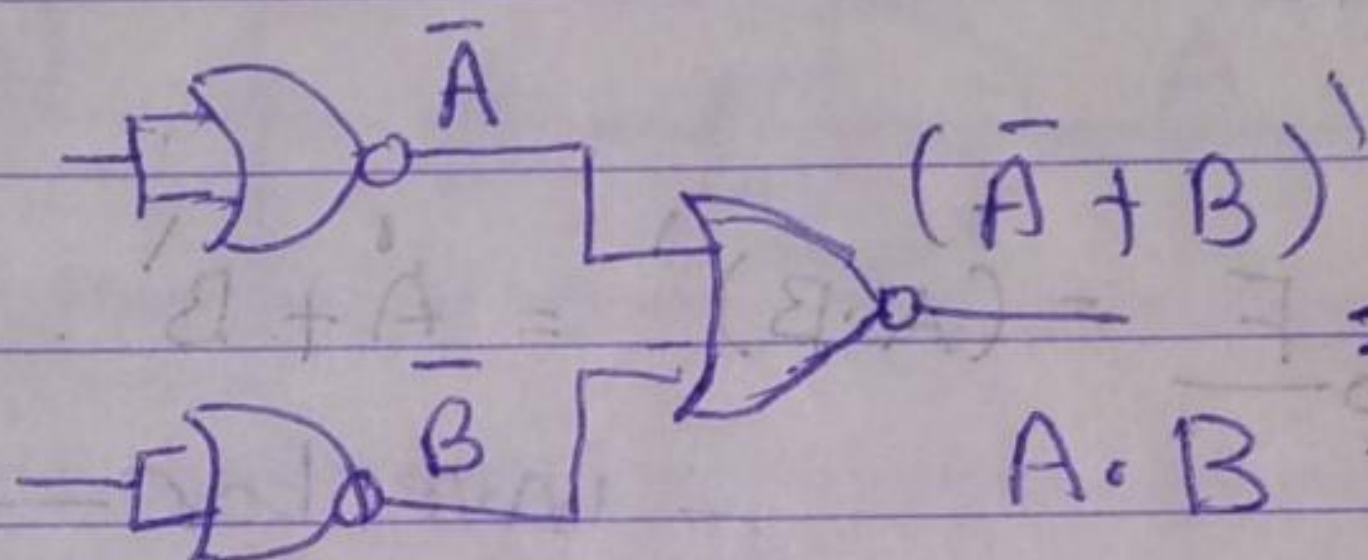

Basic Gates :-

16 Form .

AND

OR

NAND

NOR.


8 Form / degenerate (AND-AND/OR-OR) <sup>level 1</sup> <sub>level 2</sub>

8 form / non degenerate (AND-OR, NAND-NAND, NOR-OR, OR-NAND) <sup>miniterms</sup> <sub>maxterms</sub>

(OR-AND, NOR-NOR, NAND-AND, AND-NOR) <sub>maxterms</sub>



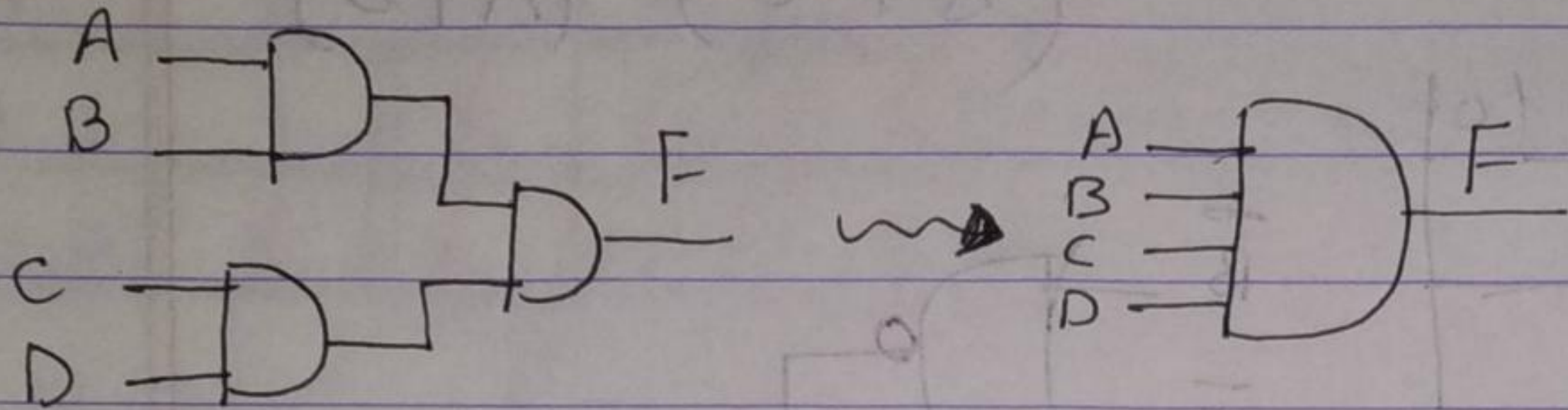انزو بنقد و نخل ال 2 level و 1 level Degenerate :-




مثال :-

ما بنقد و نخل ال 2 level و 1 level nondegenerate :-



ex  $F(A, B, C) = \sum 0, 1, 2, 6$  ← minterm.

$$= \bar{A}\bar{B} + B\bar{C}$$

BC \ A	00	01	11	10
0	1	1		1
1				1

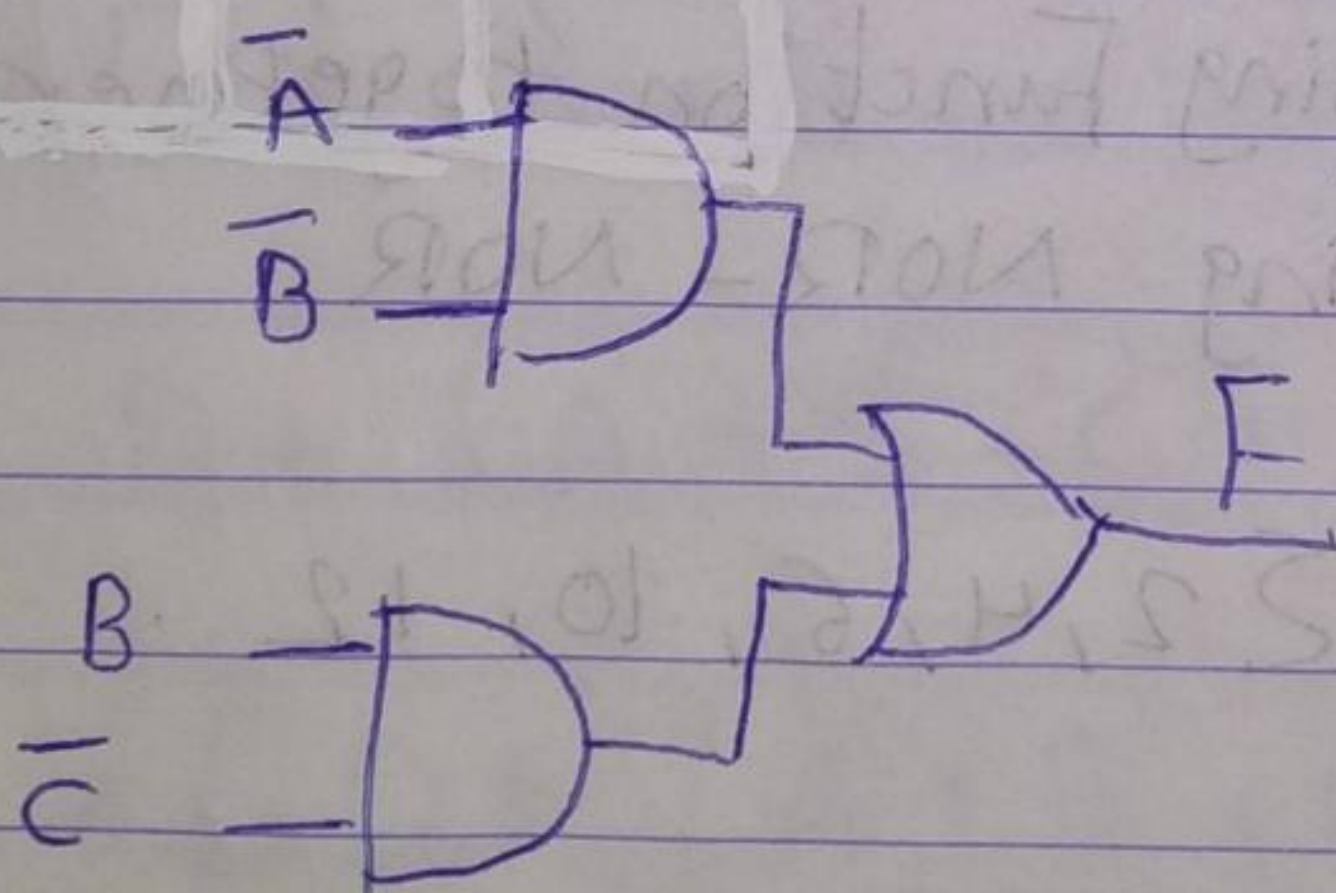

AND - OR : NAND - NAND

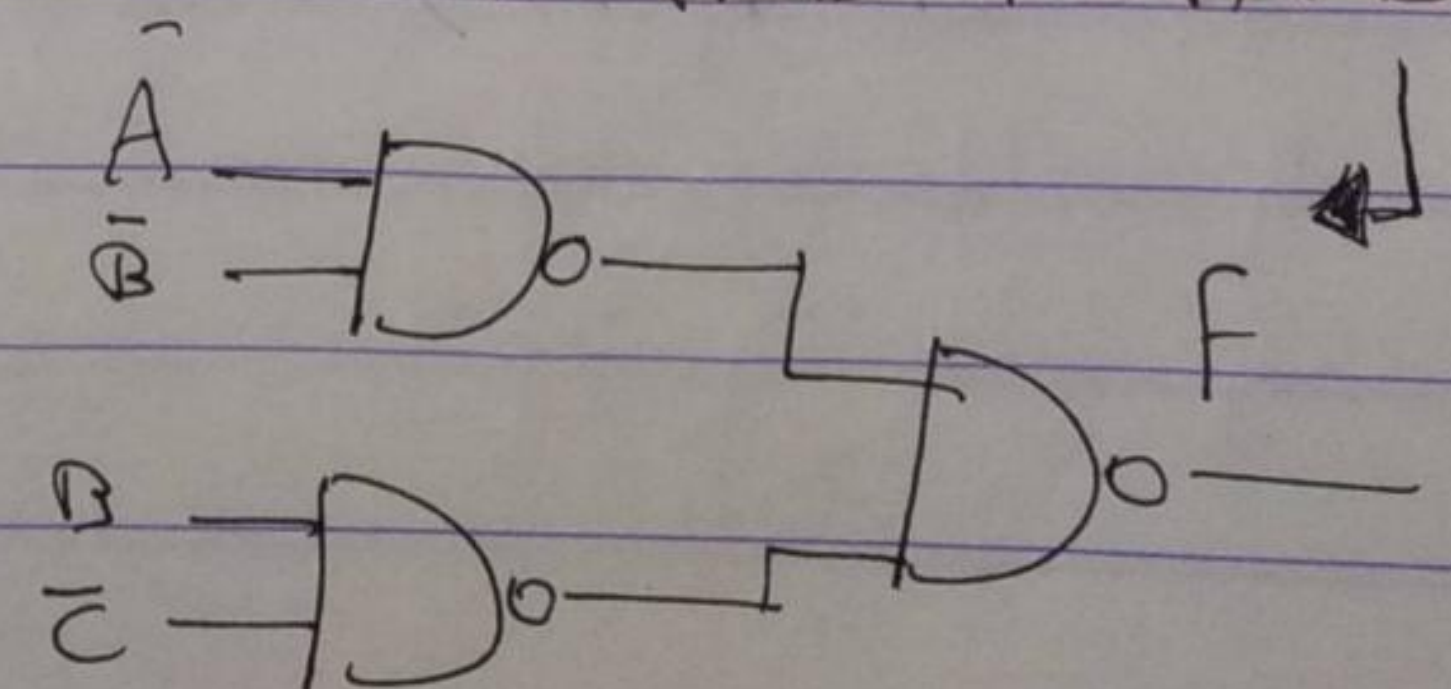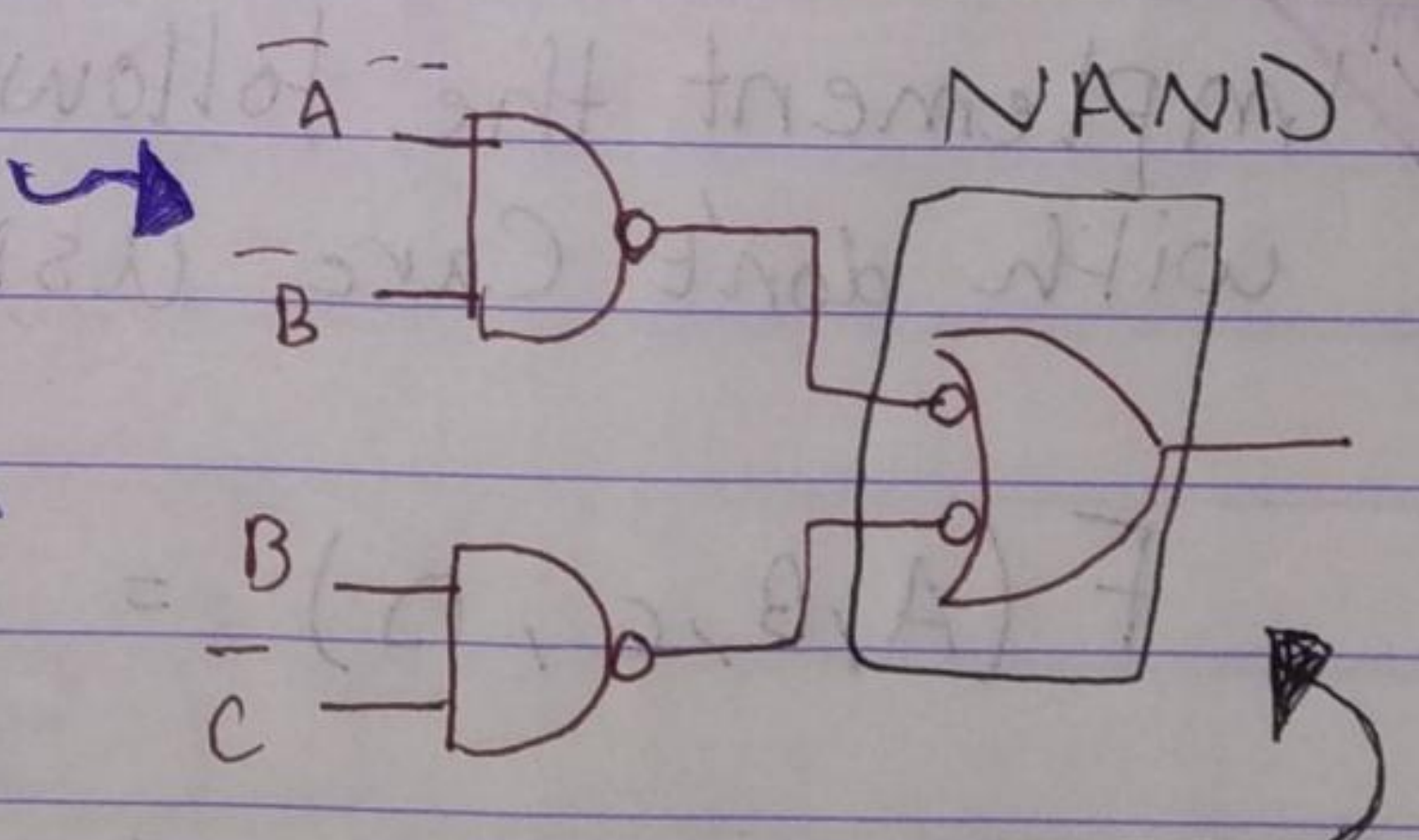



ex  $F(A, B, C) = \prod(3, 4, 5, 7)$ .




NOR - NOR.

$$= (\bar{B} + \bar{C}) \cdot (\bar{A} + B)$$

A \ B	00	01	11	10
0			0	
1	0	0	0	

$\bar{A} + B$  (circled in row 1)

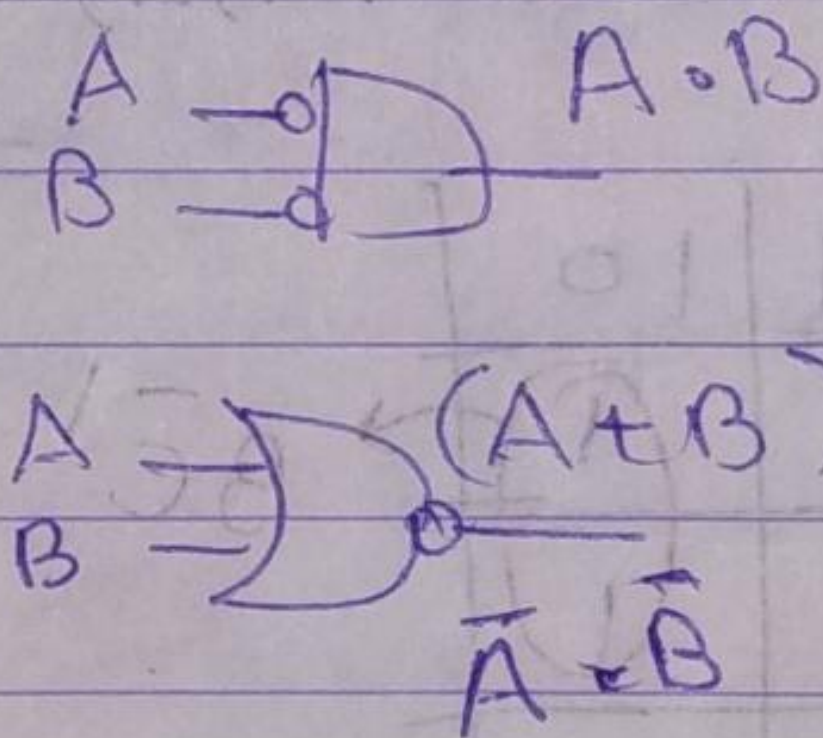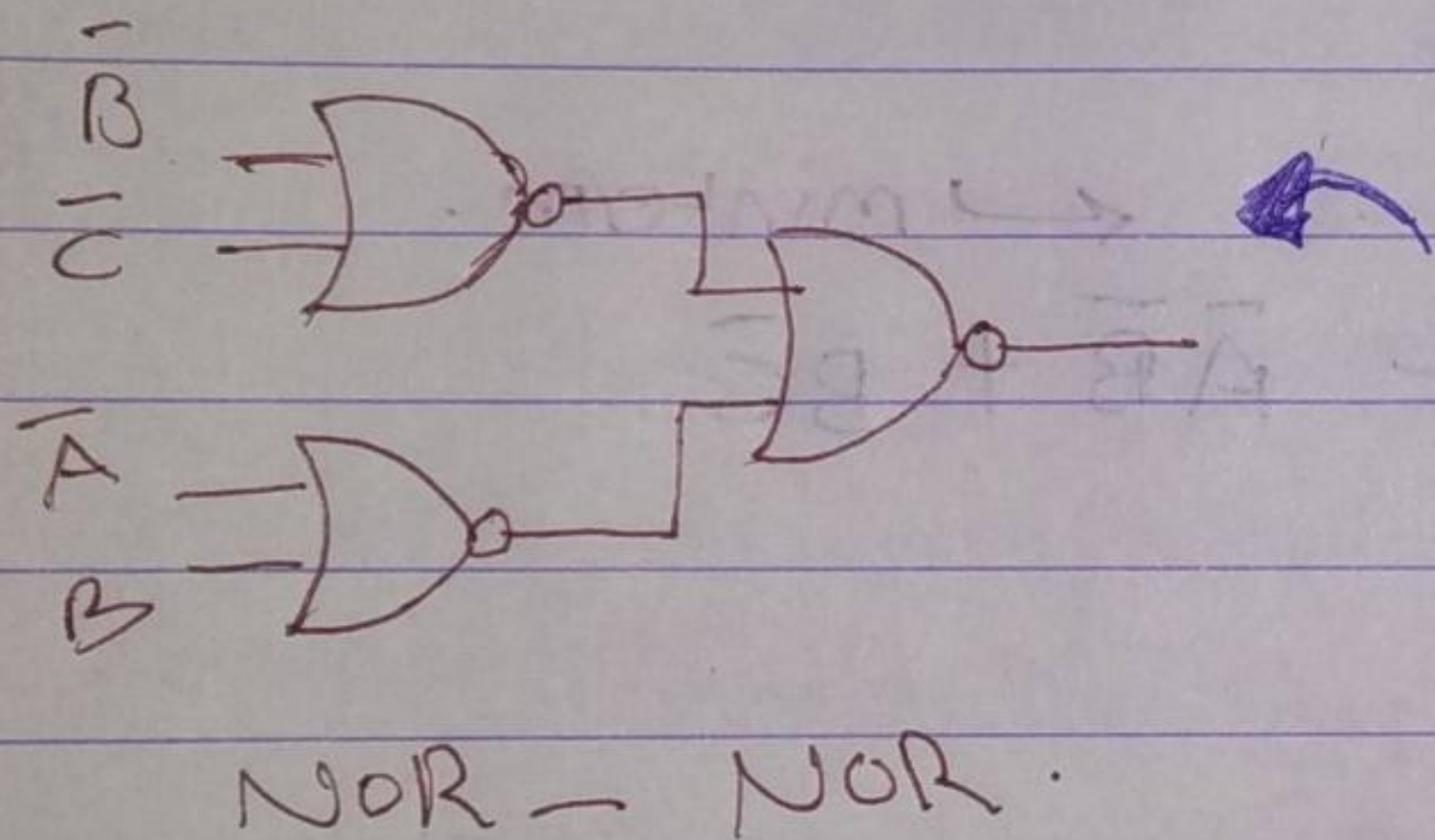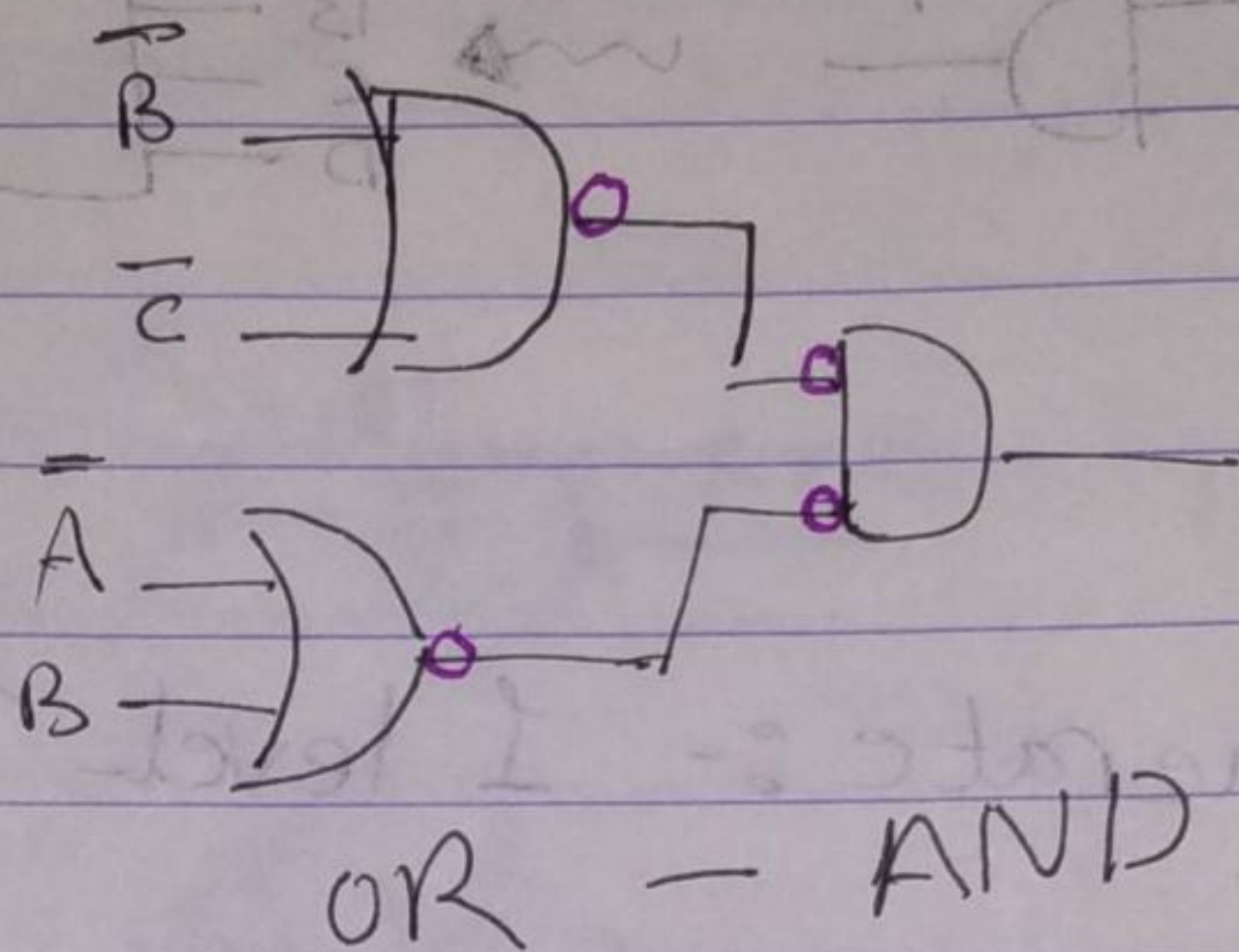
$\bar{B} + \bar{C}$  (circled in column 1)



ex Implement the following Function together with don't Care using NOR - NOR.

$$F(A, B, C, D) = \sum 2, 4, 6, 10, 12$$

$$d(A, B, C, D) = \sum 0, 8, 9, 13$$


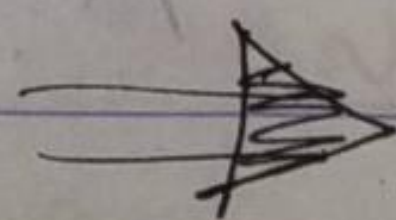




AB \ CD	00	01	11	10
00	X	0	0	1
01	1	0	0	1
11	1	X	0	0
10	X	X	0	1

$$(\bar{A} + \bar{B} + \bar{C})$$

$$D' \quad F = D' \cdot (A' + B' + C')$$

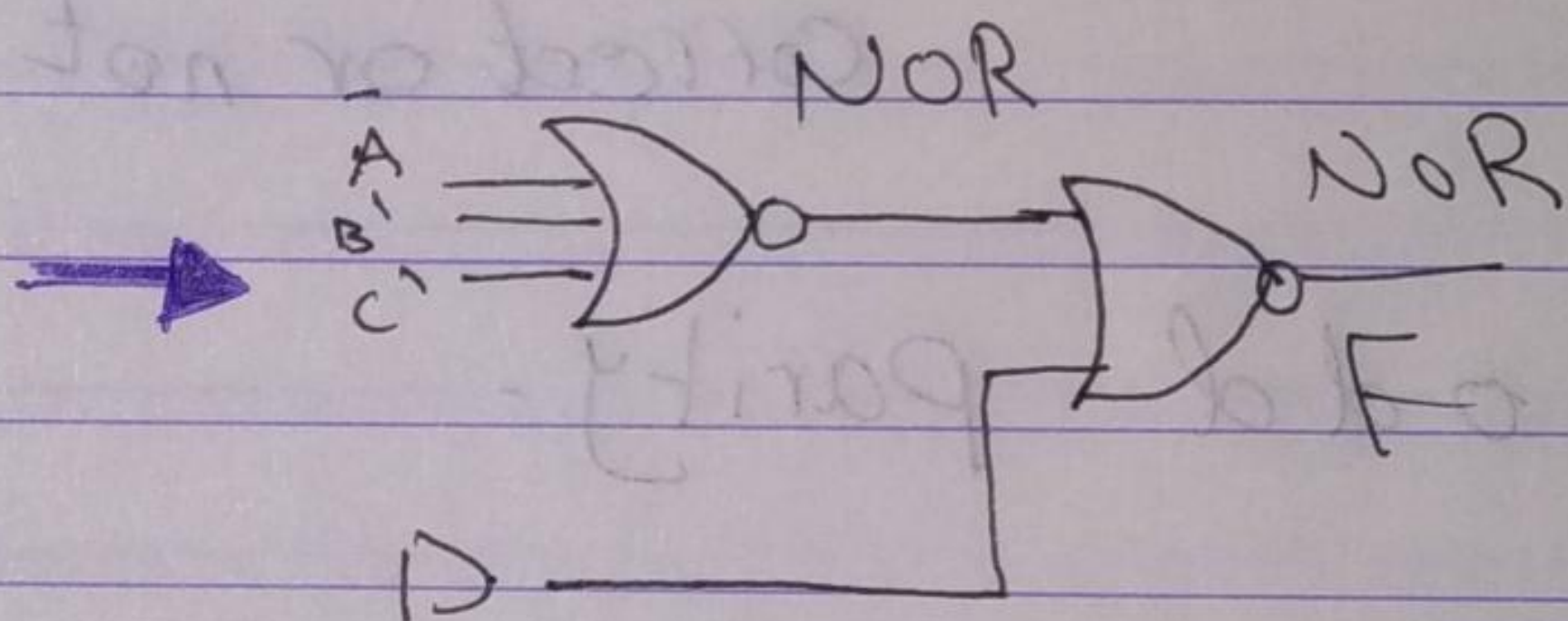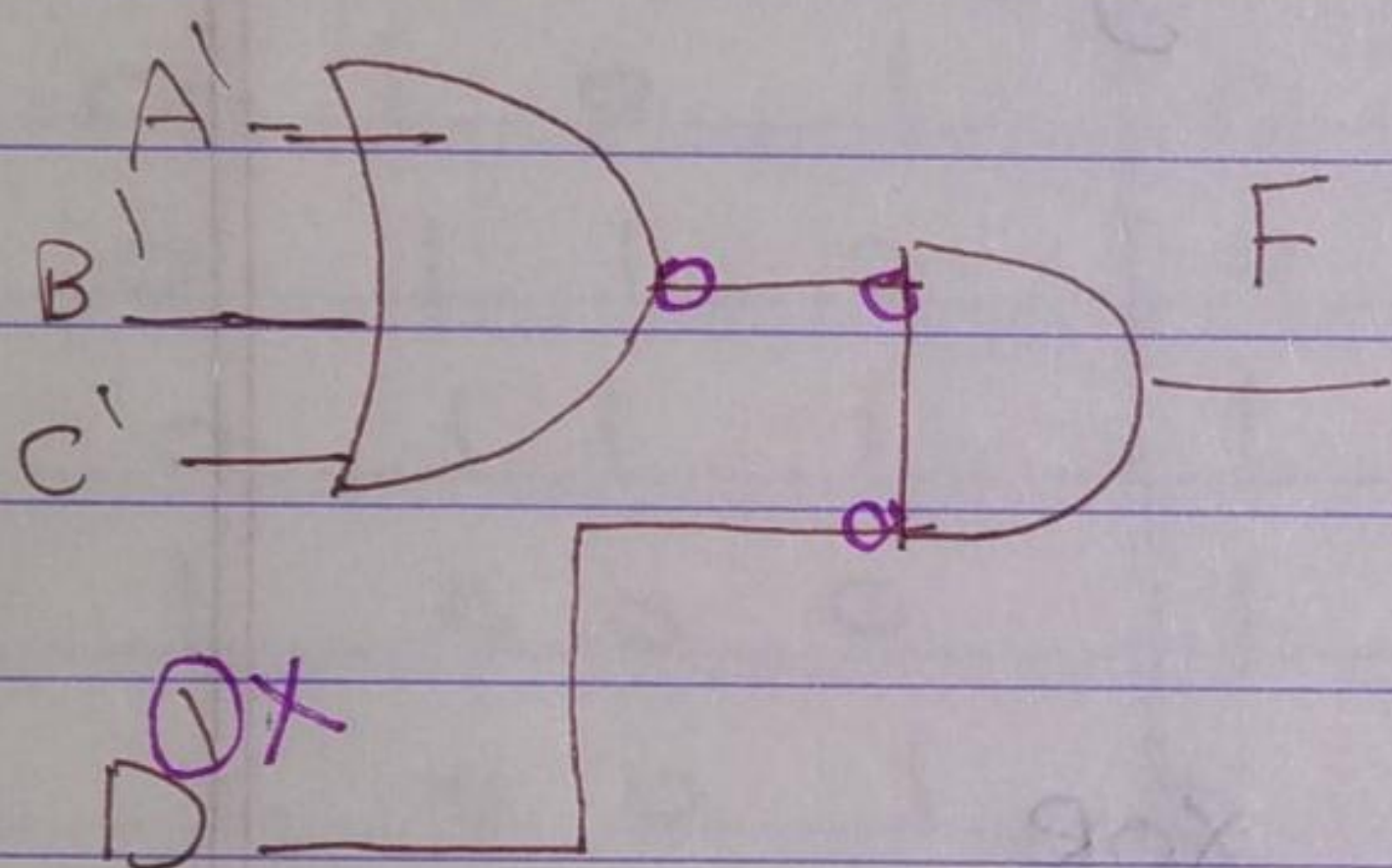

$$F = D' \cdot (A' + B' + C')$$


$$F' = [D' \cdot (A' + B' + C')]$$

$$F' = D + (A' + B' + C')$$

$$F'' = F = \underbrace{[D + (A' + B' + C')]}_{\text{NOR}}$$



# Parity Generator :-

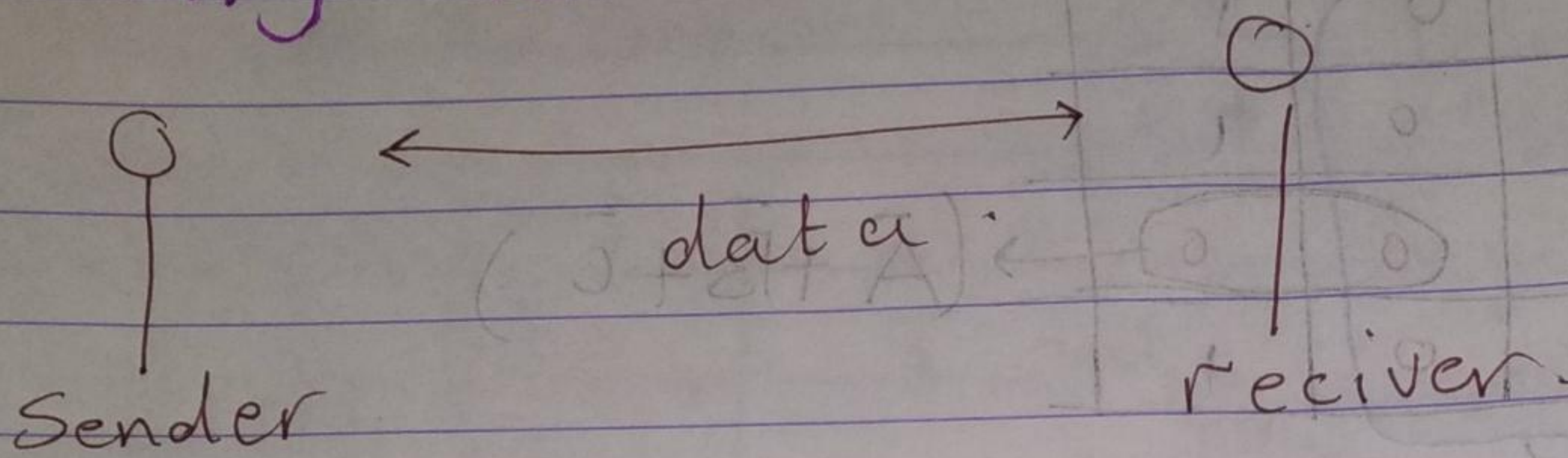

Parity :- Extra bit added by sender  
To check if the message is  
correct or not.

① odd parity.

② even parity.

ex Sender

A	B	C	P (even)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

عشانه نقل  
عدد الواحدات زوجي

اذا كان odd


XNOR



# Receiver

A	B	C	D	Check
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0

1 is 0 9

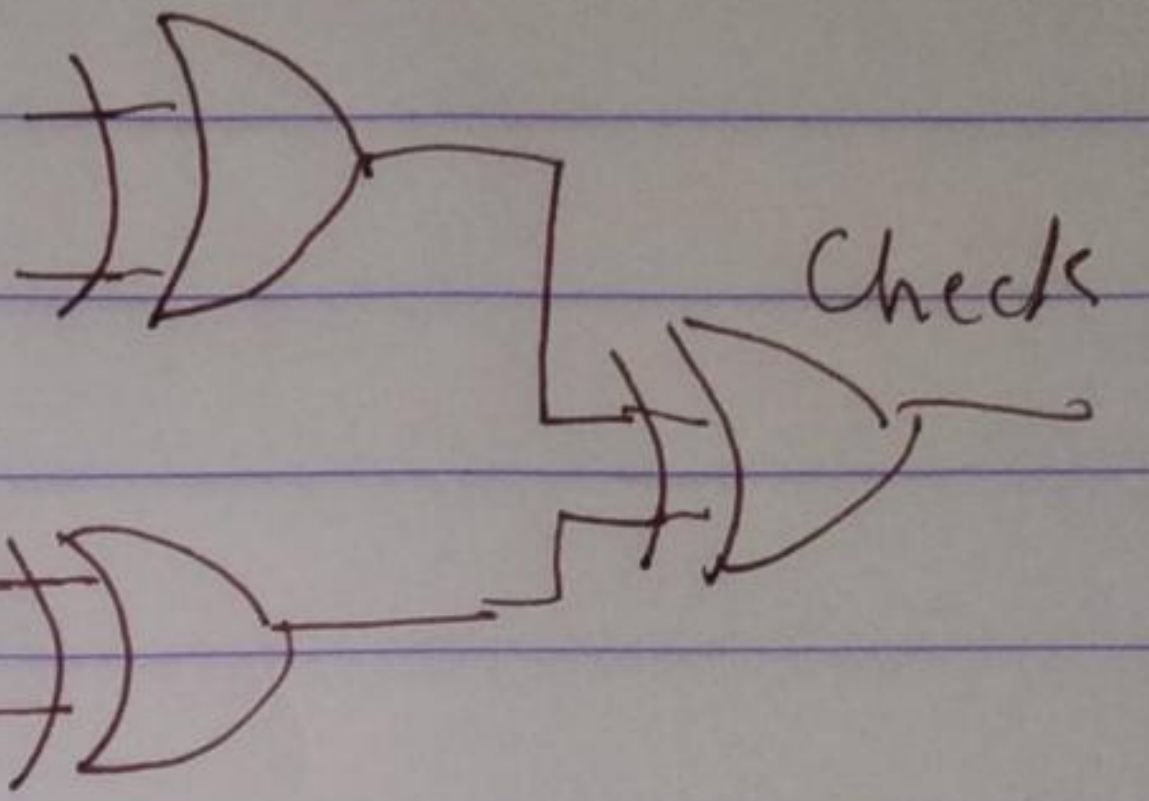

parity (odd).

x	y	z	p
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

x \ yz	00	01	11	10
0	1		1	
1		1		1

$$\begin{aligned}
 p &= x'y'z' + x'yz' + xy'z + xyz' \\
 p &= x'(y'z' + yz) + x(y'z + yz') \\
 &= x'(y \oplus z)' + x(y \oplus z) \\
 &= x'w' + xw \\
 &= (x \oplus w)' = (x \oplus y \oplus z)'
 \end{aligned}$$

