

مراجعة مسابقة  
تحليل الدوائر الكهربائية  
Circuit Analysis  
ENEE2304

First Exam  
Summer Semester  
2024 / 2025

By :

Mohammed Saada.

# Chapter 1 — Chapter 3

$$V = \frac{dW}{dq} \text{ Volt.}$$

$$I = \frac{dq}{dt} \text{ A.}$$

$$P = \frac{dW}{dt} = IV = I^2 R = \frac{V^2}{R} \text{ watt.}$$

$$G \text{ (conductance)} = \frac{1}{R} \text{ } \Omega$$

$$\text{Ohm's Law } V = IR$$

**Kirchhoff's Voltage Law (KVL):** The algebraic sum of all the voltages around any closed path (loop) in a circuit equals zero.


**Kirchhoff's Current Law (KCL):** The algebraic sum of the currents at any node in a circuit equals zero.

**Resistors in Series:**  $R_{eq} = R_1 + R_2 + \dots + R_n$

**Resistors in Parallel:**  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$

**2 Resistors in parallel:**  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

## Voltage divider rule :

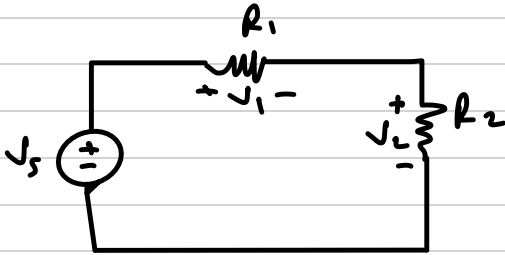


$$V_1 = \frac{V_s R_1}{R_1 + R_2}$$
$$V_2 = \frac{V_s R_2}{R_1 + R_2}$$
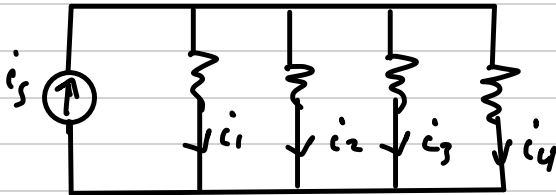
## Current divider rule :




$$i_1 = \frac{i_s R_2}{R_1 + R_2}$$
$$i_2 = \frac{i_s R_1}{R_1 + R_2}$$




$$i_j = \frac{i_s R_{eq}}{R_j}$$

## $\Delta - Y$ Transformation :

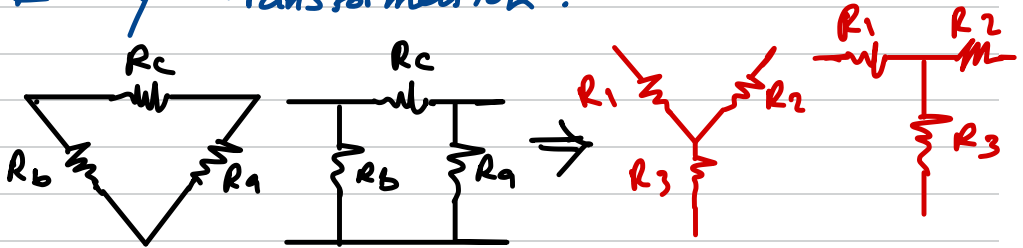

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_a R_c}{R_a + R_b + R_c}, \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

## $Y - \Delta$ Transformation :

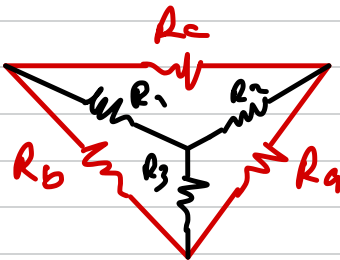

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

For the Balance Case where

$$R_a = R_b = R_c = R_0, \quad R_1 = R_2 = R_3 = R_y$$

$$R_0 = 3R_y, \quad R_y = \frac{1}{3} R_0$$

## Chapter 4 : Techniques of circuit analysis

\* Node-Voltage method.

\* Mesh - Current method.

\* Source Transformation.

\* Super position.

\* Thevenin and Norton.

\* Maximum Power Transfer.

$R_L$  will receive a maximum power, when  
 $R_L = R_{th}$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

# Chapter 9: Sinusoidal Steady-state Analysis

$$f = \frac{1}{T} \text{ Hz}, \quad \omega = 2\pi f \text{ rad/s}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}, \quad I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$\cos(\alpha) = \sin(\alpha + 90^\circ)$$

$$\sin(\alpha) = -\cos(\alpha + 90^\circ)$$

$$\sin(A \pm B) = \sin(A)\cos(B) \pm \cos(A)\sin(B)$$

$$\cos(A \pm B) = \cos(A)\cos(B) \mp \sin(A)\sin(B)$$

$$\sin(\omega t \pm 180^\circ) = -\sin(\omega t)$$

$$\cos(\omega t \pm 180^\circ) = -\cos(\omega t)$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos(\omega t)$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin(\omega t)$$

## Impedance

$$Z_R = R = R + j0$$

$$Z_L = j\omega L = 0 + j\omega L$$

$$Z_C = \frac{-j}{\omega C} = 0 + j\frac{-1}{\omega C}$$

$$X_R = 0, \quad X_L = \omega L, \quad X_C = \frac{-1}{\omega C}$$


$$\text{Admittance } Y = \frac{1}{Z}$$

$$Z = a + jb$$

a: Resistive

b: Reactance (X)

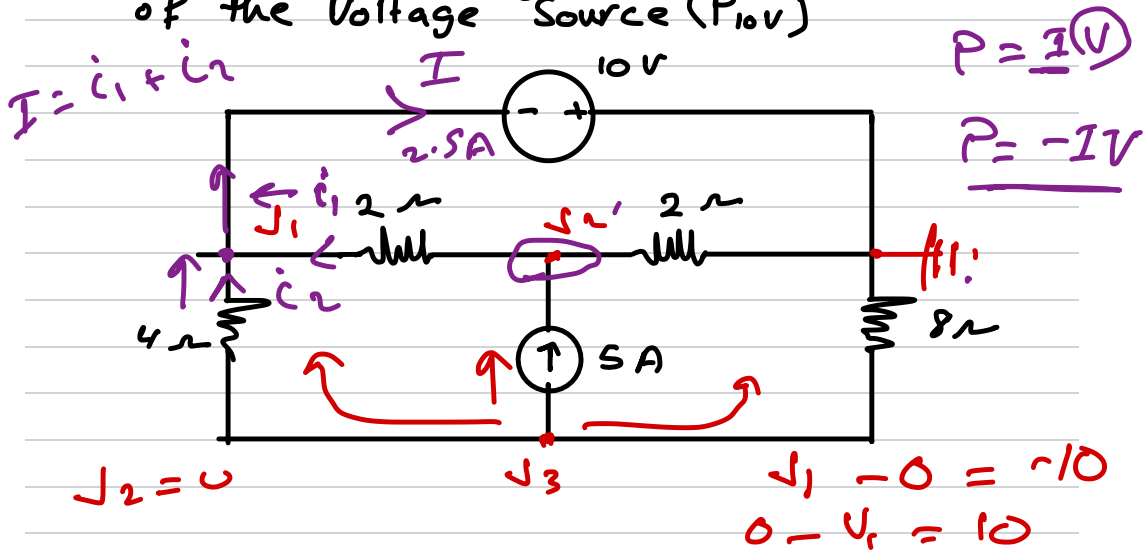Q1: Use nodal analysis to find the power of the Voltage Source ( $P_{10V}$ )



for  $V_1 - V_2$ :

$$\frac{V_1}{4} + \frac{V_1 - V_2}{2} + \frac{V_3 - V_2}{2} + \frac{V_3}{8} = 0$$

$$2V_1 + 4V_1 - 4V_2 + 4V_3 - 4V_2 + V_3 = 0$$

$$6V_1 - 8V_2 + 5V_3 = 0$$

$$6V_1 - 8V_2 + 5(10 + V_1) = 0$$

$$6V_1 - 8V_2 + 50 + 5V_1 = 0$$

$$11V_1 - 8V_2 = -50 \quad \text{--- (1)}$$

$$V_1 = -10 \text{ Volt}$$

$$V_2 = 0 \text{ Volt}$$

$$\frac{V_3 - V_1}{4} + \frac{V_3}{8} + 5 = 0$$

$$2V_3 - 2V_1 + V_3 + 40 = 0$$

$$3V_3 - 2V_1 = -40$$

$$3V_3 + 20 = -40$$

$$3V_3 = -60$$

$$V_3 = -20 \text{ Volt}$$

$$I = i_1 + i_2$$

$$= \frac{V_2 - V_1}{2} + \frac{V_3 - V_1}{4}$$

$$= \frac{10}{2} + \frac{-20 - (-10)}{4}$$

$$= 5 + -2.5$$

$$= 2.5 \text{ A}$$

$$P = -IV = (-2.5)(10) = -25 \text{ Watt}$$

For  $V_2$

$$\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2} - 5 = 0$$

$$V_2 - V_1 + V_2 - V_3 = 10$$

$$-V_1 + 2V_2 - V_3 = 10 \quad \underline{V_3 = 10 + V_1}$$

$$-V_1 + 2V_2 - (10 + V_1) = 10$$

$$-V_1 + 2V_2 - 10 - \underline{V_1} = 10$$

$$\boxed{-2V_1 + 2V_2 = 20} \quad \text{--- (2)}$$

---

$$+ \quad 11V_1 - 8V_2 = -50$$

$$+ \quad 4(-2V_1 + 2V_2 = 20)$$

$$\underline{3V_1 = 30}$$

$$\boxed{V_1 = 10 \text{ Volt}}$$

$$-2(10) + 2V_2 = 20 \rightarrow 2V_2 = 40$$

$$\boxed{V_2 = 20 \text{ Volt}}$$

$$V_3 = 10 + V_1 \Rightarrow$$

$$\boxed{V_3 = 20 \text{ Volt}}$$

$$I = i_1 + i_2$$

$$= \frac{V_3 - V_2}{2} + \frac{V_3}{8}$$

$$= \frac{20 - 20}{2} + \frac{20}{8} = \underline{2.5 \text{ A}}$$

$$P = -I V$$



$$= (-2.5)(10)$$

$$= -25 \text{ Watt. Supplied power}$$

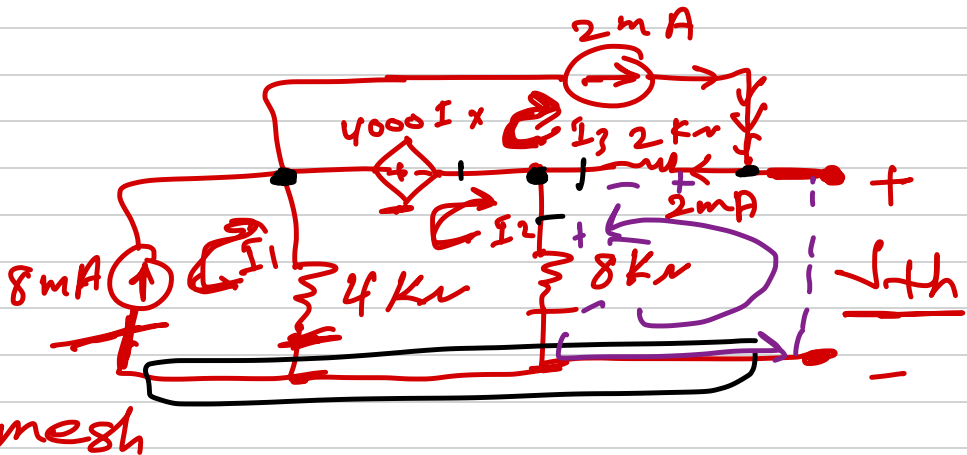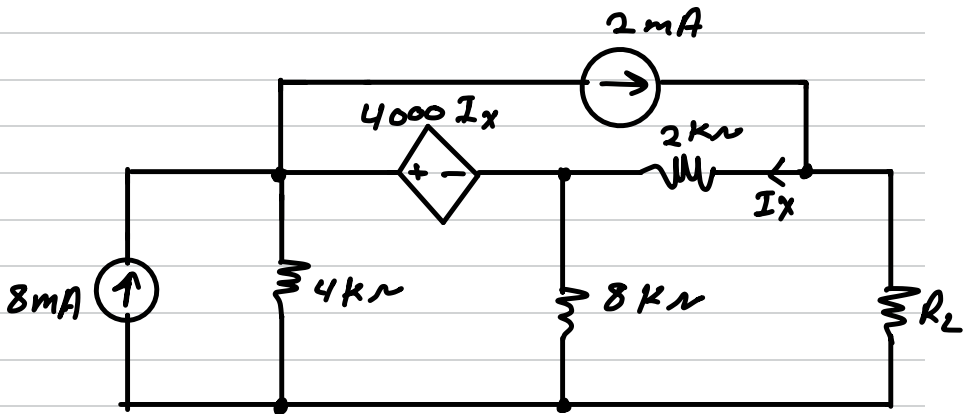Q2. For the following circuit :

→ (a) Find the Value of  $R_L$  For max Power transfer.

→ (b) Calculate the maximum power transferred to  $R_L$



$$I_1 = 8 \text{ mA} \quad , \quad I_3 = 2 \text{ mA}$$

For mesh (2)

$$(4 + 8) I_2 - 4 I_1 + 4000 I_x = 0$$

$$\text{but } (I_x = 2 \text{ mA})$$

$$12 I_2 - 4(8) + 4 \times 10^3 \times 2 \times 10^{-3} = 0$$

$$12 I_2 - 32 + 8 = 0$$


$$12 I_2 = 24$$

$$I_2 = 2 \text{ mA}$$

KVL

$$-V_{th} + 4 + 16 = 0$$

$$V_{th} = 20 \text{ Volt}$$

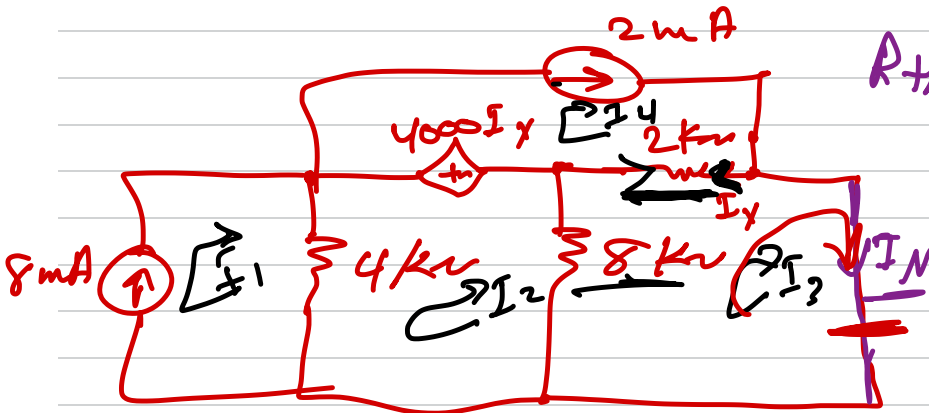

$$I_N = I_3$$

$$R_{th} = \frac{V_{th}}{I_N}$$

$$I_1 = 8 \text{ mA} , \quad I_4 = 2 \text{ mA}$$

For mesh (2)

$$(4+8)I_2 - 4I_1 - 8I_3 + 4I_x = 0$$
$$(I_x = I_4 - I_3)$$

$$12I_2 - 4I_1 - 8I_3 + 4(I_4 - I_3) = 0$$

$$12I_2 - 4I_1 - 8I_3 + 4I_4 - 4I_3 = 0$$

$$12I_2 - 4(8) - 12I_3 + 4(2) = 0$$

$$12I_2 - 12I_3 = 24 \quad \text{--- (1)}$$

For mesh (3)

$$(8+2)I_3 - 8I_2 - 2I_4 = 0$$

$$10I_3 - 8I_2 - 2(2) = 0$$

$$-8I_2 + 10I_3 = 4 \quad \text{--- (2)}$$

$$\textcircled{1} \div 3 \quad / \quad \textcircled{2} \div 2$$

$$~~4~~I_2 - 4I_3 = 8$$

$$+ ~~-4~~I_2 + 5I_3 = 2$$

---

$$I_3 = 10 \text{ mA}$$

$$I_N = I_3 = 10 \text{ mA}$$

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{20}{\underline{10}} = \boxed{2 \text{ K}\Omega}$$

For max power transfer

$$\boxed{R_L = R_{Th} = 2 \text{ K}\Omega}$$


$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(20)^2}{4(2) \times 10^3}$$

$$= 50 \times 10^{-3}$$


$$= 50 \text{ mWatt.}$$

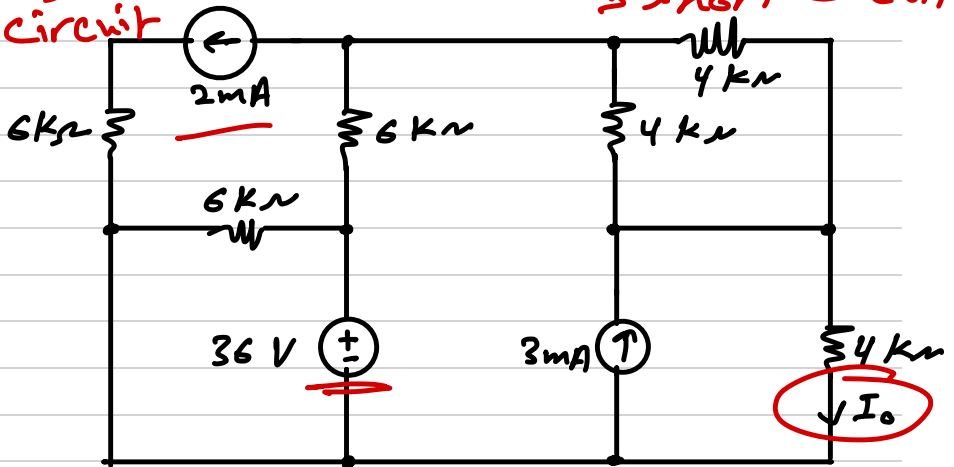Q3. Use the Superposition theorem to find the output current  $I_o$


Voltage Source  $\Rightarrow$  Short circuit  
 Current Source  $\Rightarrow$  open circuit



For source 2mA :

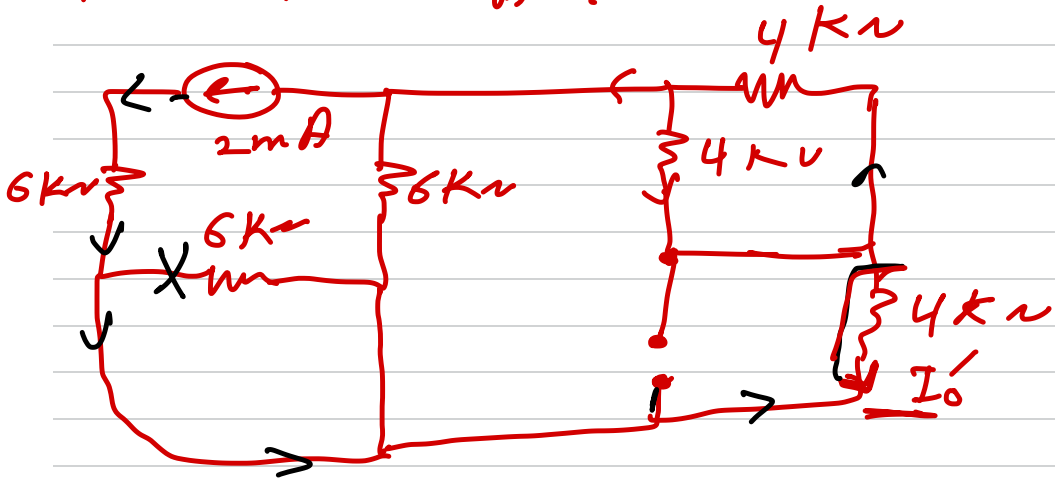

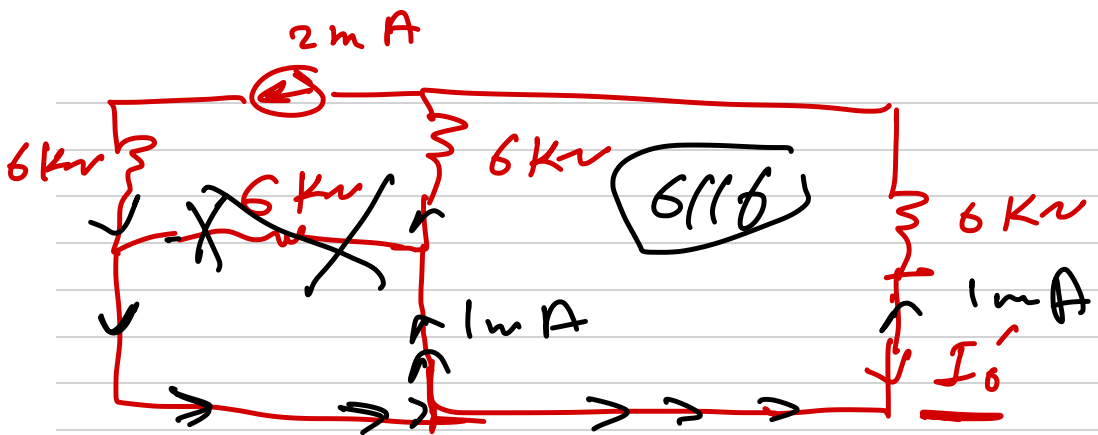
$$\begin{aligned}
 (4 // 4) + 4 &= \\
 2 + 4 &= 6 \text{ k}\Omega
 \end{aligned}$$




$$I_o' = -1\text{mA}$$

For source ( $3\text{mA}$ )


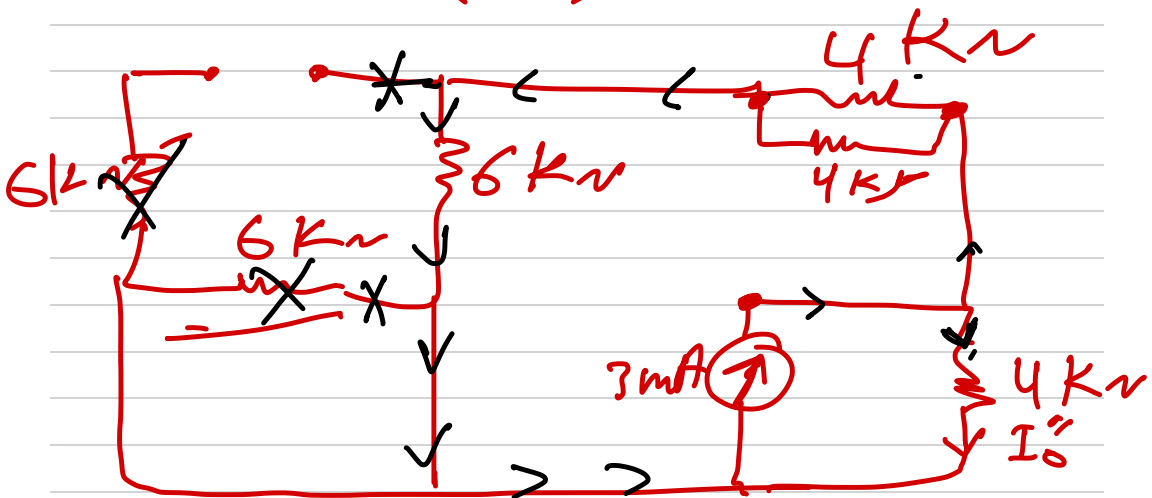

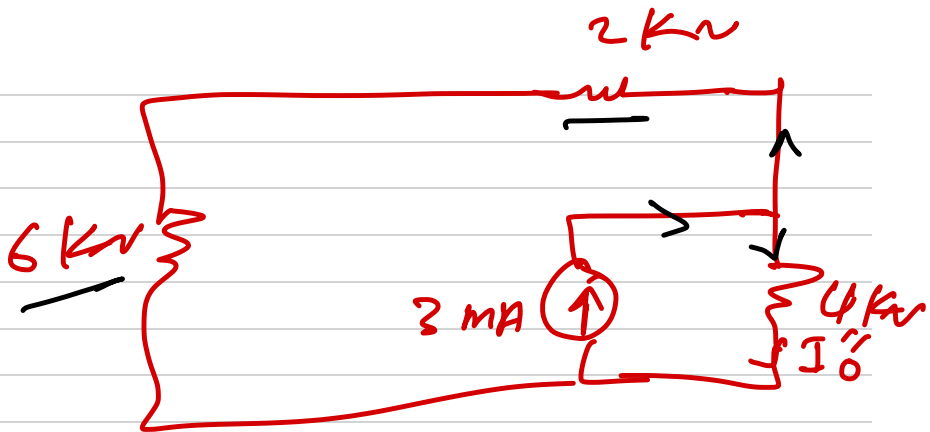
$$(4/4) \rightarrow R = 2\text{K}\Omega$$



$$I''_O = \frac{3(8)}{8 + 4} = \frac{24}{12}$$

$$I''_O = 2\text{ mA}$$

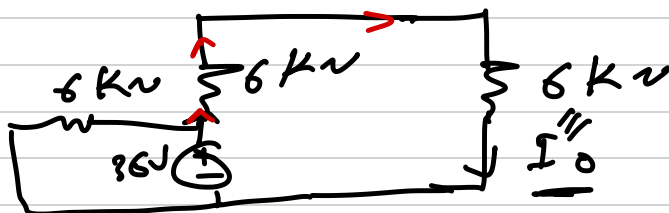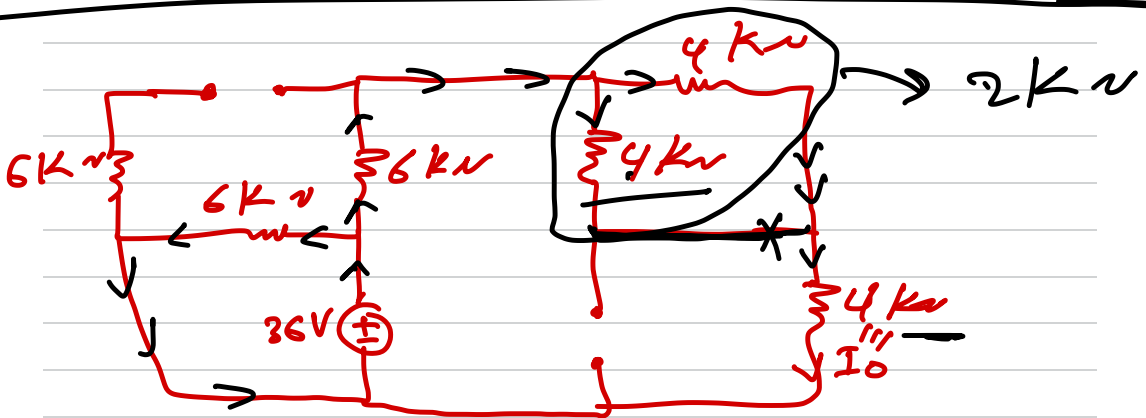



$$V_{12k\Omega} = 36V$$

$$IR = 36V$$

$$I_o'' (12k) = 36V$$


$$I_o'' = 3mA$$

$$I_o = I_o' + I_o'' + I_o'''$$

$$= -1 + 2 + 3$$

$$= 4mA$$

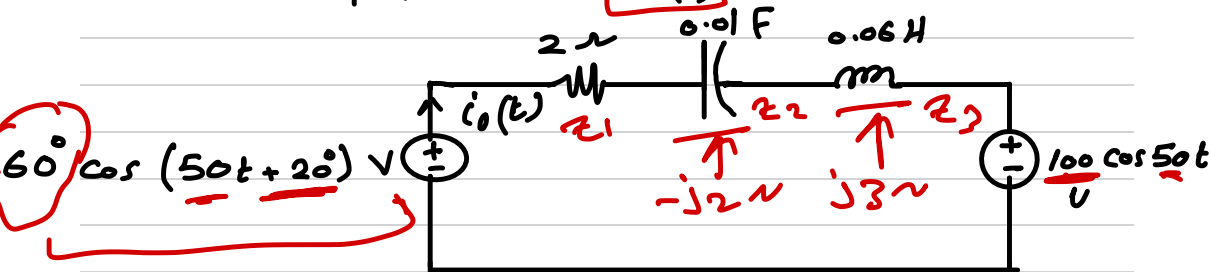
Q4. For the following circuit, Find the steady state output current  $I_o(t)$



$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(50)(0.01)} = -j2 \Omega$$

$$Z_L = j\omega L = j(50)(0.06) = j3 \Omega$$
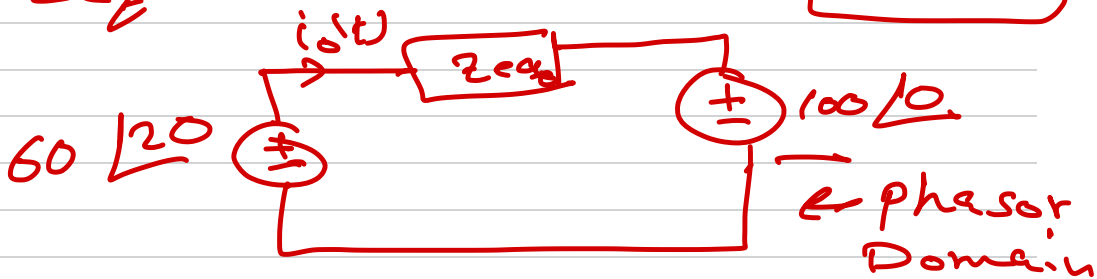
$$Z_{eq} = 2 + -j2 + j3 = 2 + j1 \Omega$$



$$i_o(t) = \frac{60 \angle 20^\circ - 100 \angle 0^\circ}{2 + j1} \leftarrow \begin{matrix} \text{Polar} \\ \text{Rect} \end{matrix}$$

$$\left. \begin{aligned} 60 \angle 20^\circ &= 56.38 + j20.52 \\ -100 \angle 0^\circ &= 100 + j0 \end{aligned} \right\}$$

$$= -43.62 + j20.52$$

$$\dot{I}_0(t) = \frac{-43.62 + j20.52}{2 + j}$$



$$= \frac{48.2 \angle 154.8^\circ}{2.236 \angle 26.56^\circ}$$

$$\dot{I}_0(t) = 21.55 \angle 128.24^\circ \text{ A}$$

Phasor Domain

$$I_0(t) = 21.55 \cos(50t + 128.24^\circ) \text{ A}$$

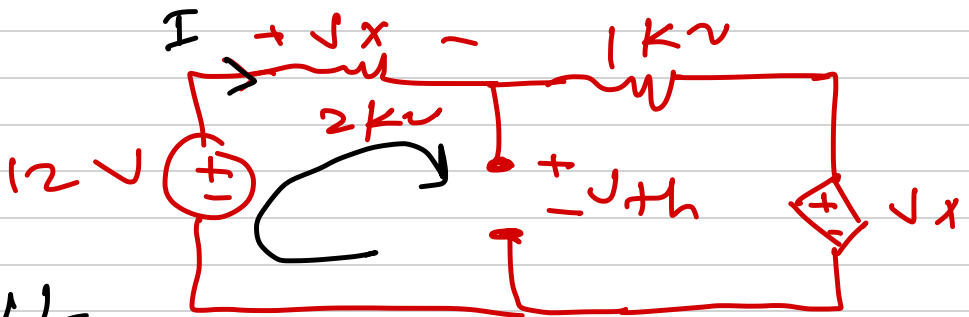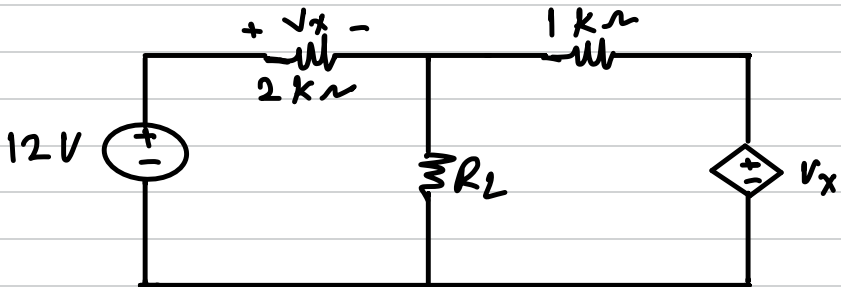Q5. For the circuit shown, Find the maximum power that can be delivered to the load  $R_L$



KVL

$$-12 + v_x + I + v_x = 0$$

$$-12 + 2v_x + I = 0$$


$$-12 + 4I + I = 0 \quad \boxed{v_x = 2I}$$

$$5I = 12 \rightarrow I = \frac{12}{5} \text{ mA}$$

$$= 2.4 \text{ mA}$$

$$-12 + 2I + V_{th} = 0$$
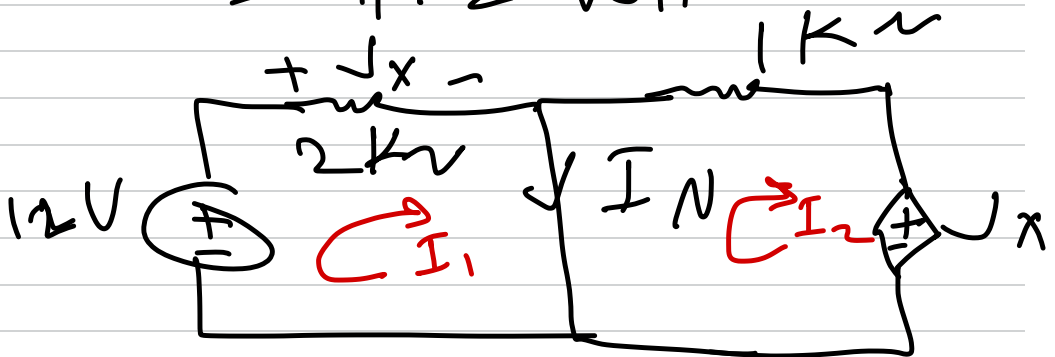
$$\begin{aligned} V_{th} &= 12 - 2(2.4) \\ &= 7.2 \text{ Volt.} \end{aligned}$$



mesh ①:

$$-12 + 2I_1 = 0$$

$$2I_1 = 12 \rightarrow I_1 = 6 \text{ mA}$$

mesh ②:

$$V_x + I_2 = 0 \quad V_x = 2I_1$$

$$12 + I_2 = 0 \quad = 12$$

$$I_2 = -12 \text{ mA}$$

$$I_N = I_1 - I_2 = 6 - (-12) = 18 \text{ mA}$$

$$R_{th} = \frac{V_{th}}{I_N} = \frac{7.2}{18 \text{ mA}}$$

$= 0.4 \text{ k}\Omega$

$$P_{max} \leq \frac{V_{th}^2}{4R_{th}}$$

$$= \frac{(7.2)^2}{(4)(0.4) \times 10^3}$$

$$= 32.4 \times 10^{-3}$$

$= 32.4 \text{ mWatt.}$