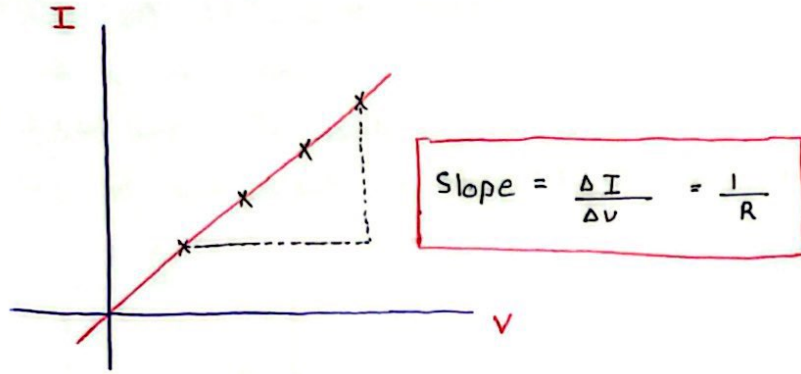


1 linear & non linear elements


$$R = \frac{V}{I}$$

i) for linear elements



example: carbon Resistor
Light bulb




ii) for non linear elements

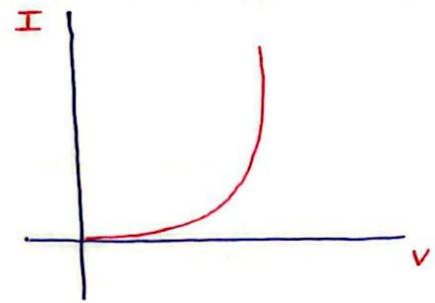

example: Diode


2 Internal Resistance & Impedance Matching

$$\text{power} = I^2 R_L$$

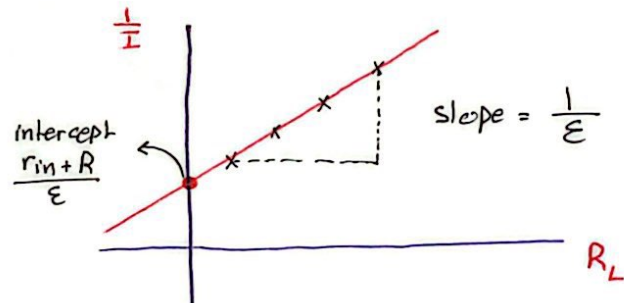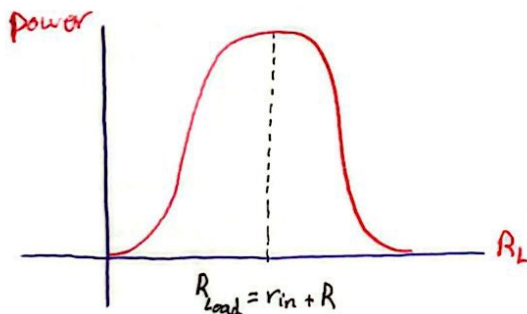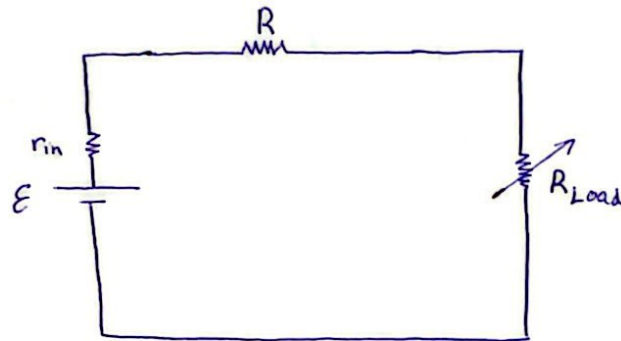

3

i) Kirchhoff

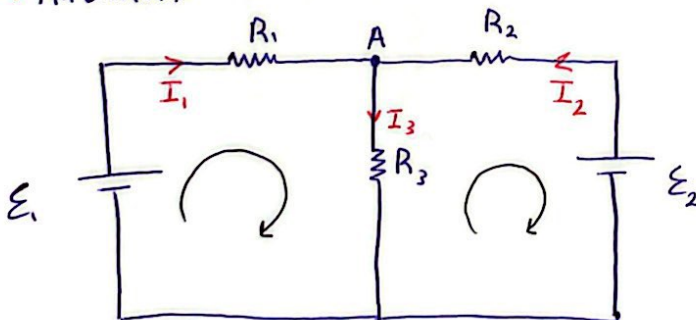

by $\sum V = 0 \rightarrow$ we get 2 & 3

& by $\sum I_{\text{in}} = \sum I_{\text{out}} \rightarrow$ we get 1

$$\textcircled{1} \quad I_1 + I_2 = I_3$$

$$\textcircled{2} \quad \epsilon_1 - I_1 R_1 - I_3 R_3 = 0$$


$$\textcircled{3} \quad \epsilon_2 - I_2 R_2 - I_3 R_3 = 0$$

(1)

i) Superposition (spp)

* Steps:-

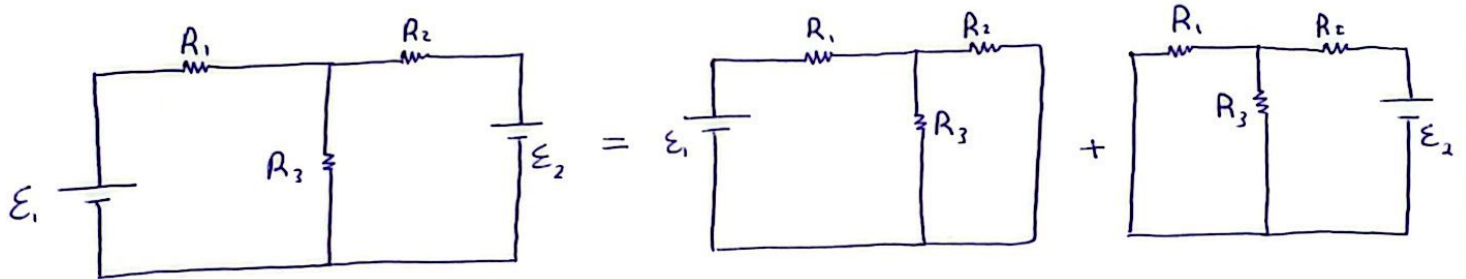
- 1) Turn off all sources except one source, find the output (voltage or current) due to that source
- 2) Repeat step 1 for each of the other sources
- 3) Find the total output by adding algebraically all the outputs due to each source.




4 Thevenin Equivalent Circuit

Assume we have the following circuit \rightarrow

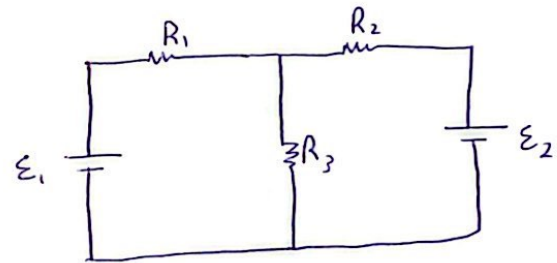
we can find the Thevenin equivalent circuit by two ways:-



i) Voltage at the open circuit

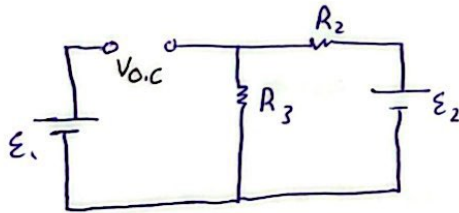


Th. circuit \rightarrow

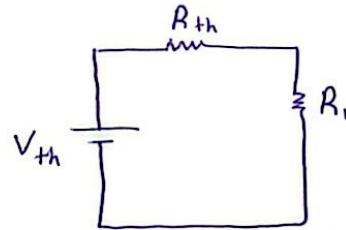


by Kirchhoff in exp 3

$$V_{th} = V_{o.c} \quad \& \quad R_{th} = R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

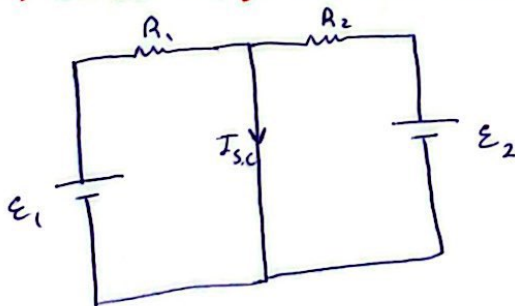ii) current through the short circuit (Norton eq. circuit)



\rightarrow

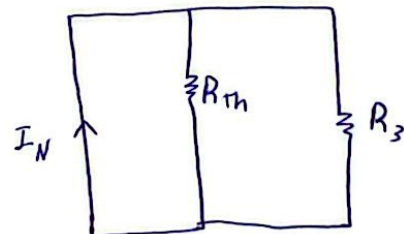




$$I_N = I_{s.c} = \frac{E_1}{R_1} + \frac{E_2}{R_2}$$

$$R_{th} = R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

(2)

5 Capacitors & Inductors


i) RC circuits → Resistor & capacitor

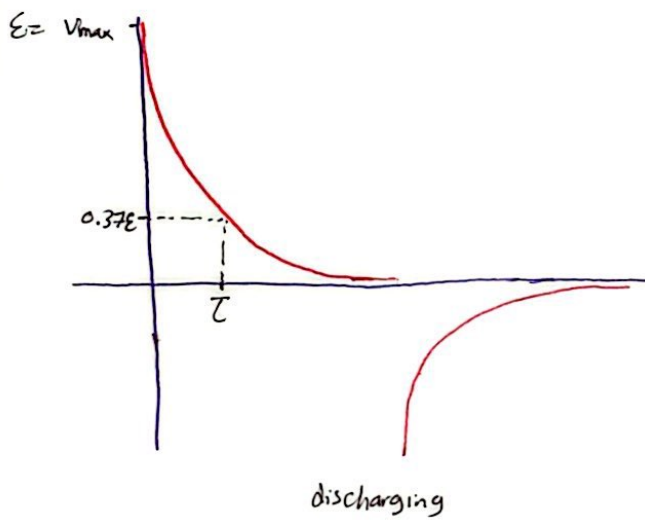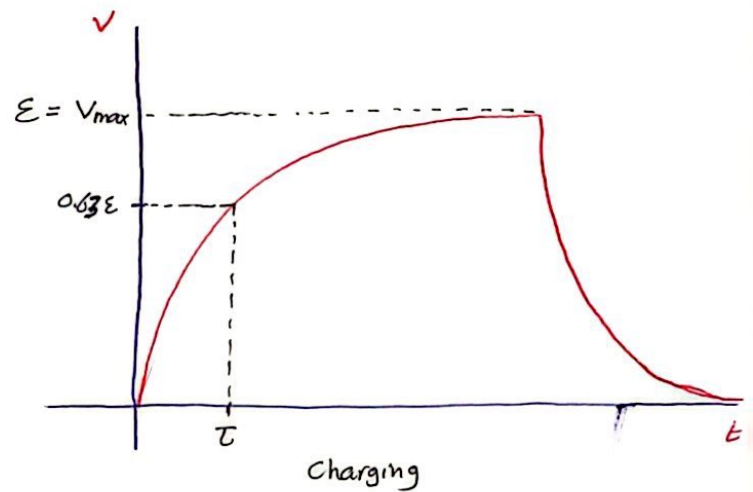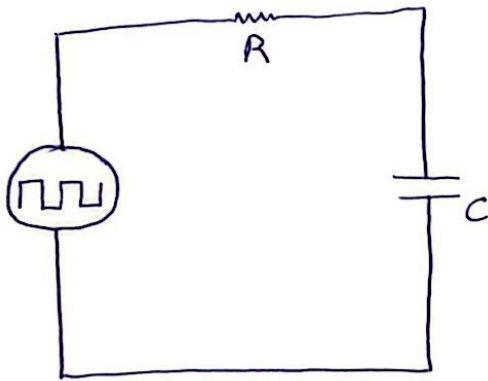


$$\tau_{theo} = RC$$

$$\tau_{exp} = \frac{\tau_{charging} + \tau_{discharging}}{2}$$

ii) RL circuits → Resistor & Inductor

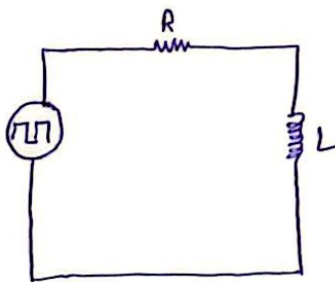


$$\tau_{theo} = \frac{L}{R}$$

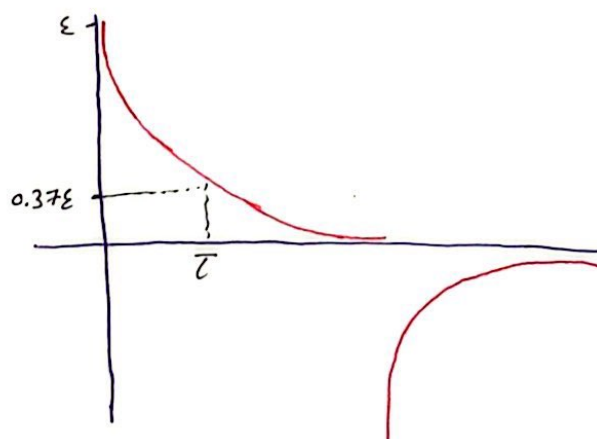

(3)

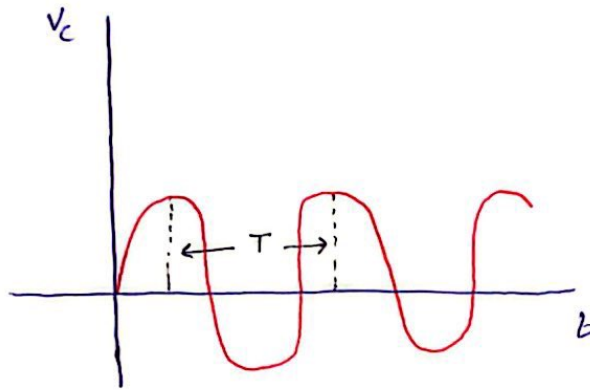
iii) LC circuits \rightarrow Inductor & capacitor




~~XXXXXXXXXXXX~~
 $\omega = 2\pi f$

$$f_{exp} = \frac{1}{T}$$

$$f_{theo} = \frac{1}{2\pi\sqrt{LC}}$$

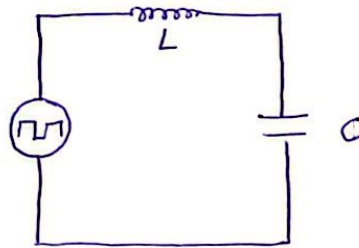


6 Damping

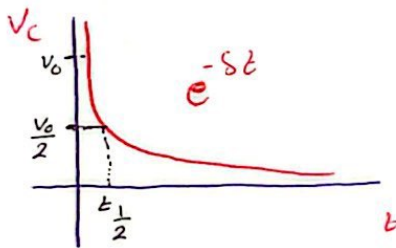


$$V_c = V_0 e^{-st}$$

$$s = \frac{\ln 2}{t_{1/2}}$$

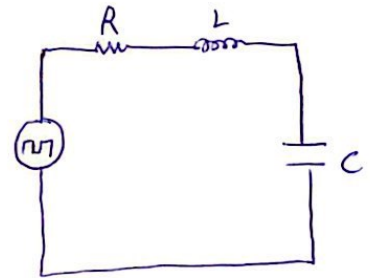


case 1)

if $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$ then it is called over-damping

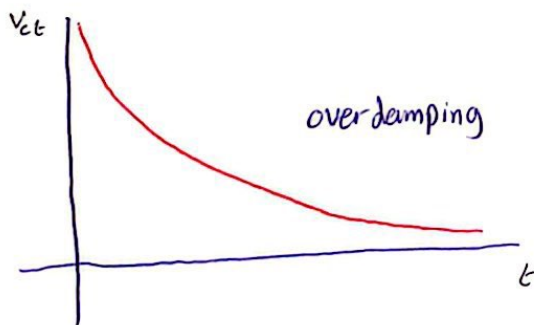

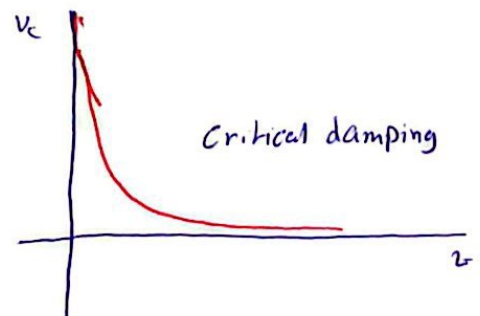case 2) if $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$ then it is a critical damping




(4)

Case 3)

if $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$

then it is underdamping

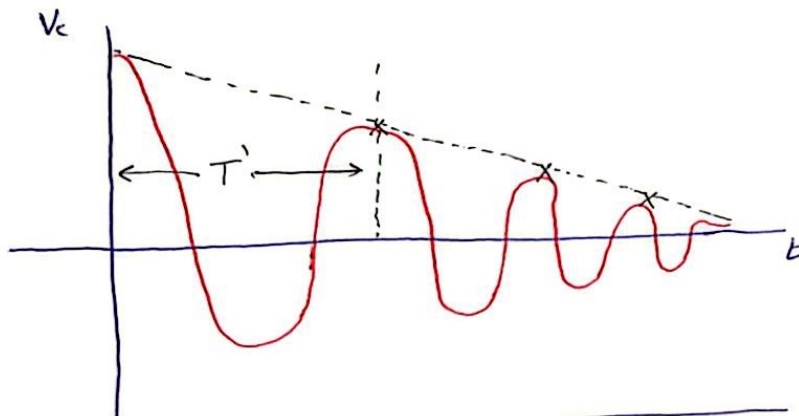

$$f_{exp} = \frac{1}{T'}$$

$$f_{theo} = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

7 Impedance & Reactance

$$Z_R = R$$

$$|Z_R| = R$$


$$Z_C = \frac{-j}{\omega C}$$

$$|Z_C| = \frac{1}{\omega C}$$

$$Z_L = j\omega L$$

$$|Z_L| = \omega L$$

$$j = \sqrt{-1}$$

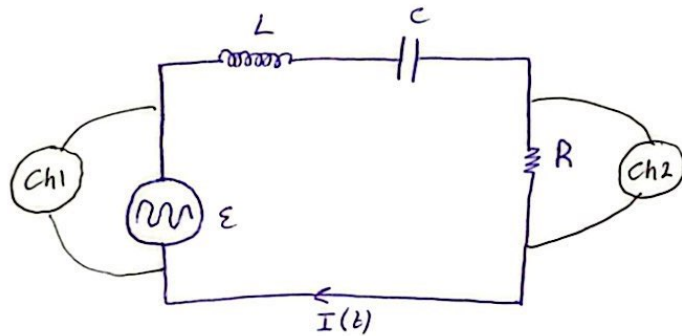


$$E(t) = E_0 \cos \omega t$$

$$I(t) = I_0 \cos(\omega t + \phi)$$

$$I_0 = \frac{E_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\omega = 2\pi f$$

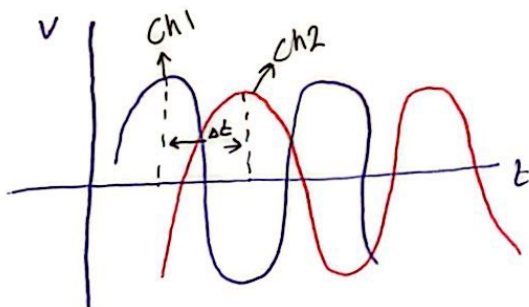

ch1 leads ch2


because it started before ch2
and we also can say that
ch2 lags ch1

Phase shift $\phi \rightarrow$ Unit is Rad

$$\phi_{exp} = \omega \Delta t$$


$$\phi_{theo} = \tan^{-1} \left(\frac{-\omega L + \frac{1}{\omega C}}{R} \right)$$

ϕ_{theo}

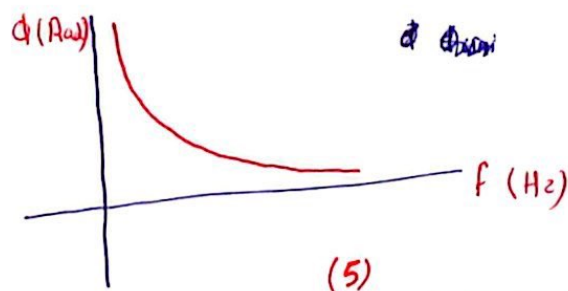

(5)

8 Resonance

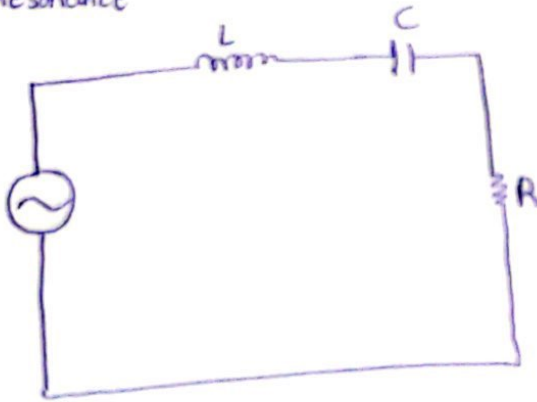


$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$I_{0\max} \text{ occurs at } \omega L = \frac{1}{\omega C}$$

$$\text{OR } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$I_{0\max} = \frac{V_0}{R}$$

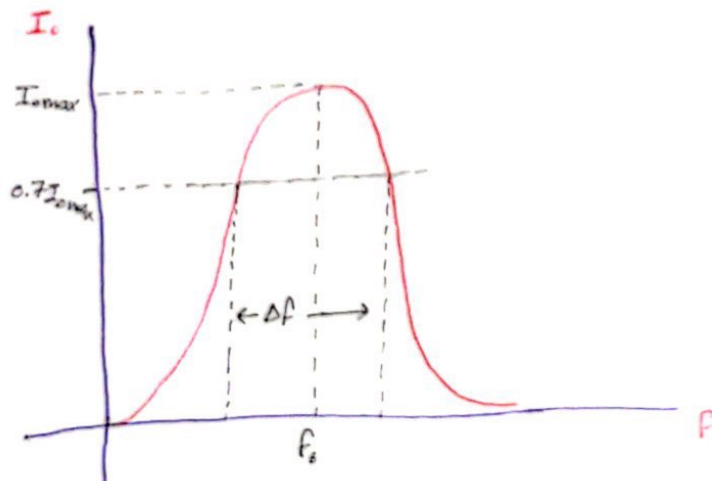

$\Delta\omega$ = bandwidth

Q = Quality factor

$$Q_{exp} = \frac{f_0}{\Delta f}$$

$$Q_{theo} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

(6)