

BIRZEIT UNIVERSITY

Faculty of Engineering and Technology

Electrical and Computer Engineering Department

Electronics LAB (ENEE3102)

Pre-LAB of Experiment #7

Power Amplifiers

Prepared by:

Name: Sara Totah

Number: 1181779

Instructor:

Mohammad Jihad Al Ju'Beh

Date:

9/10/2020

Section: #1

Table of Contents

I.	THE CLASSES OF POWER AMPLIFIER.....	2
II.	PUSH-PULL AMPLIFIER.	4
III.	<i>COMPLEMENTARY PUSH-PULL AMPLIFIER.</i>	5

I. THE CLASSES OF POWER AMPLIFIER.

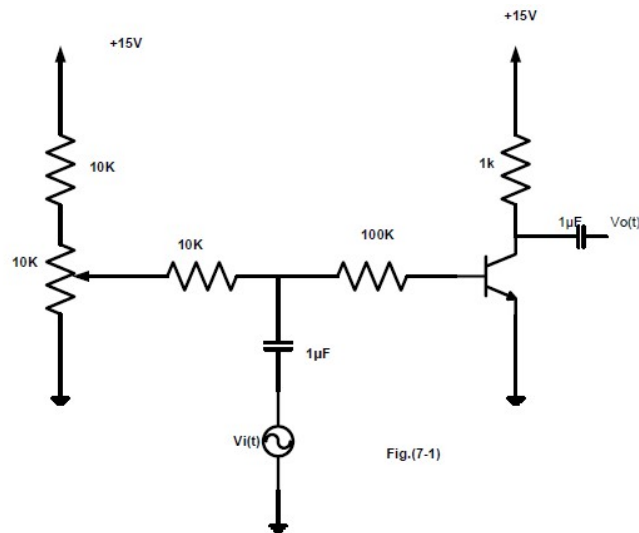


Fig.(7-1)

Figure (7-1)


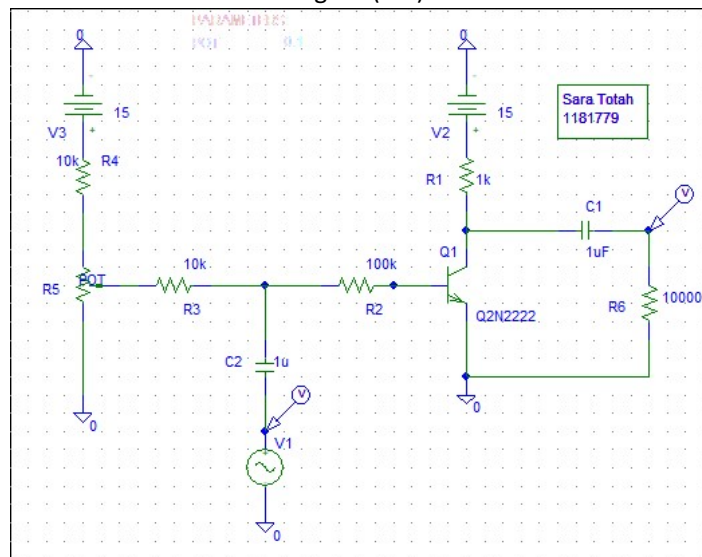



Figure (7-1): PSPICE simulation

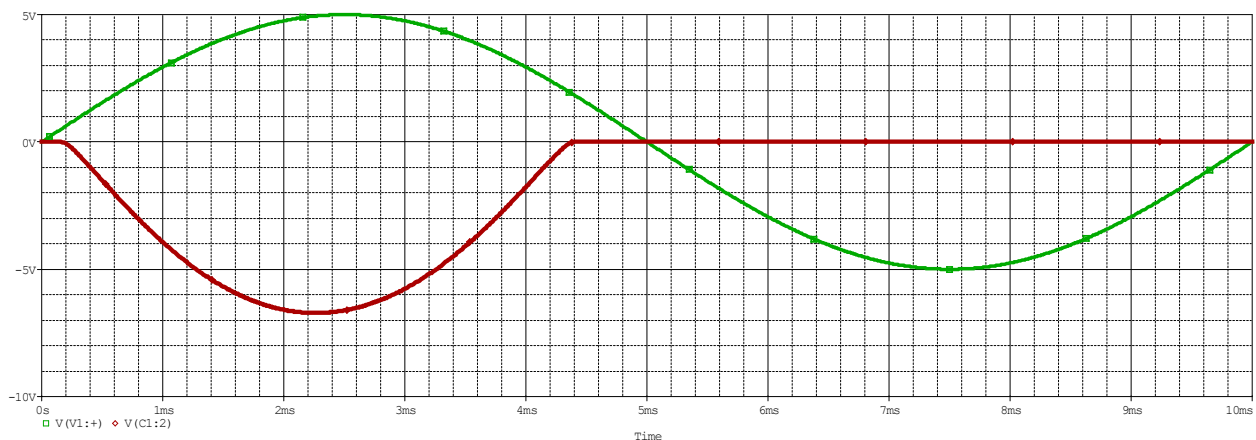1. For $V_{in} = 10\text{volts P-P}$
 - Potentiometer set = 1
 - This is a class B power amplifier.




V_{in} & V_{out} waveforms

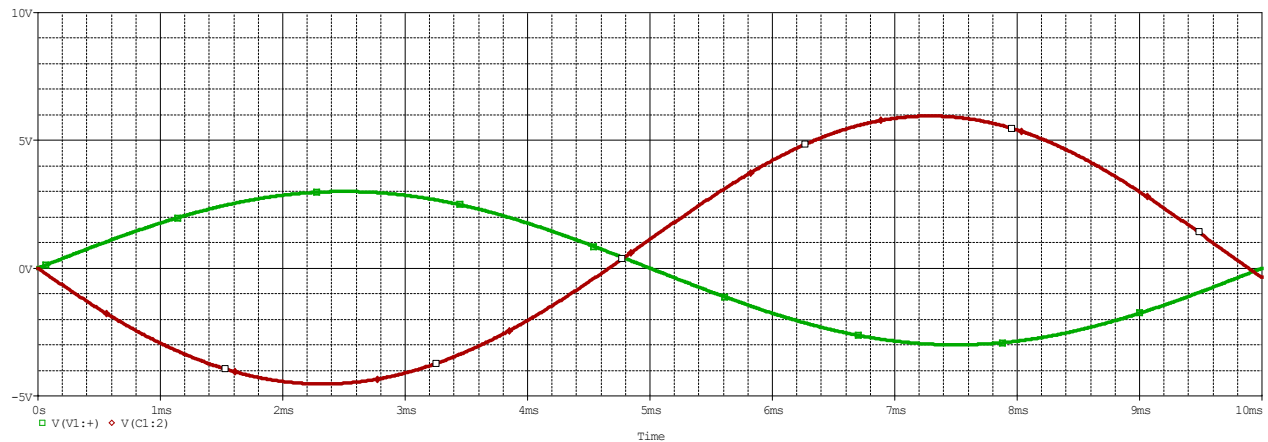2. For $V_{in} = 6\text{volts P-P}$
 - Potentiometer set = 0.3
 - This is a class B power amplifier.




V_{in} & V_{out} waveforms

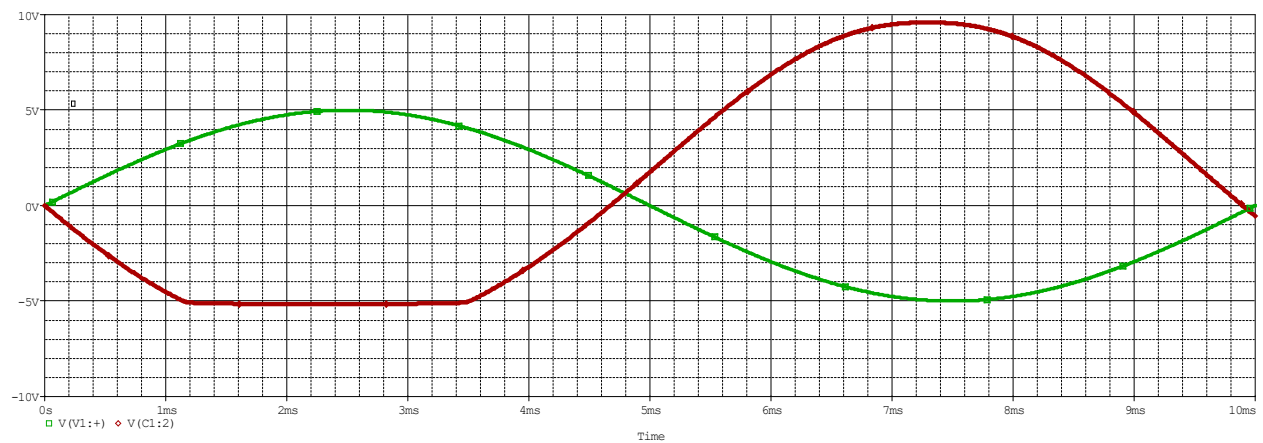3. For $V_{in} = 10\text{volts P-P}$
 - Potentiometer set = 1
 - This is a class AB power amplifier.



V_{in} & V_{out} waveforms

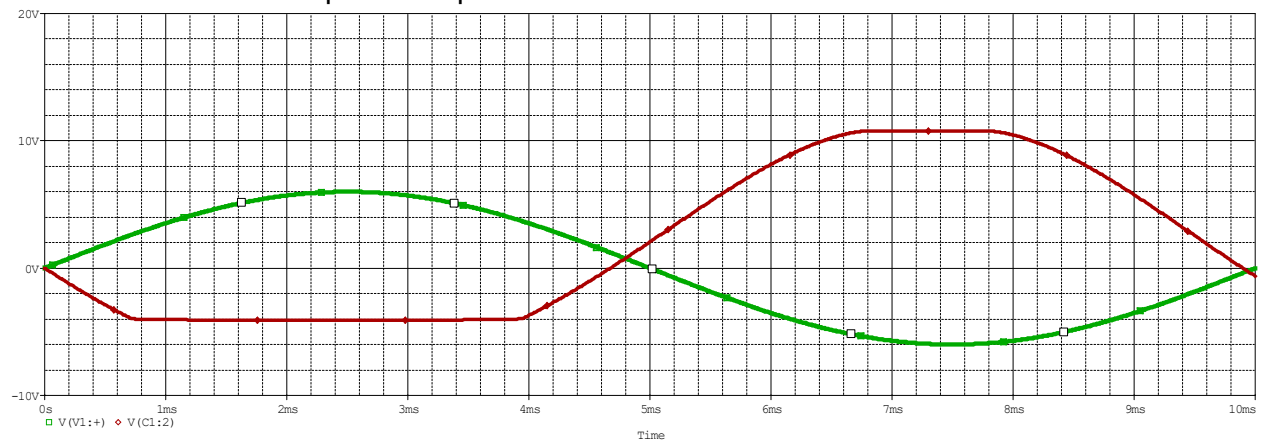4. For $V_{in} = 12\text{volts P-P}$
 - Potentiometer set = 1
 - This is a class AB power amplifier.



V_{in} & V_{out} waveforms

II. PUSH-PULL AMPLIFIER.

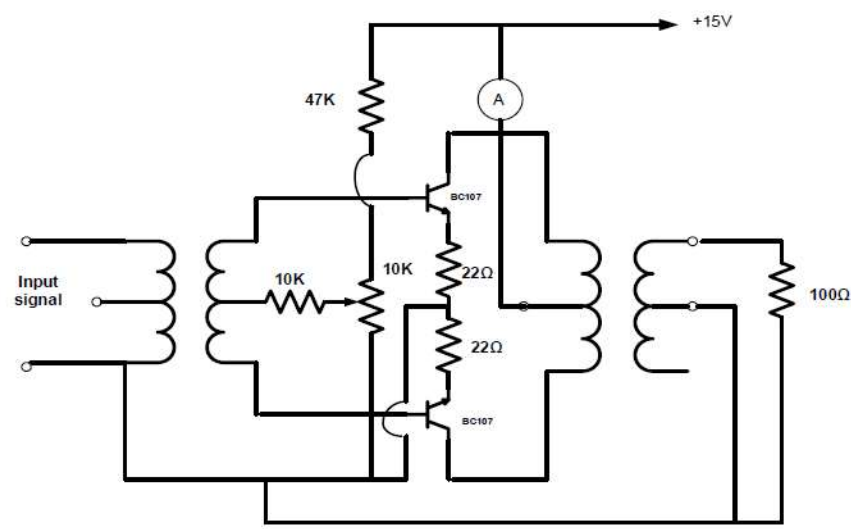


Figure (7-2)

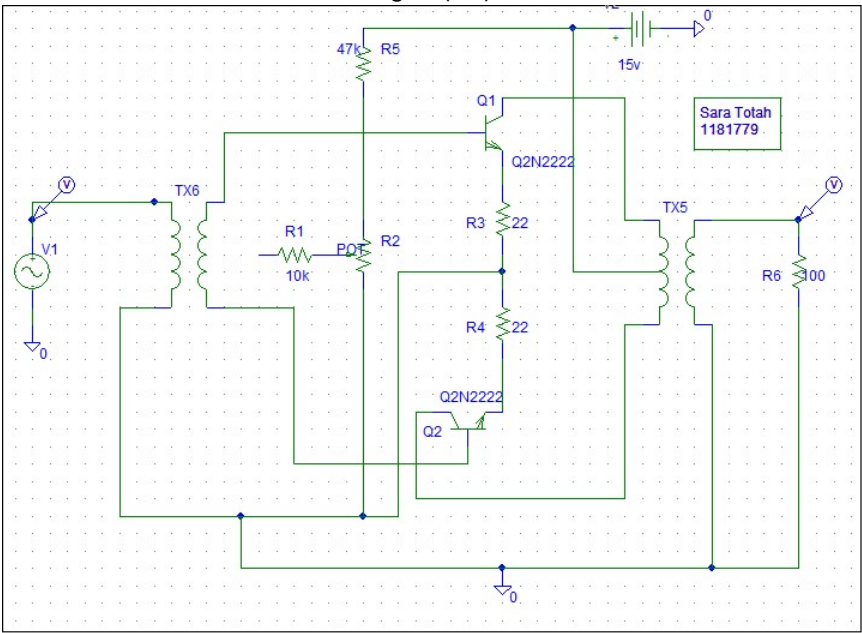


Figure (7-2): PSpice simulation

III. COMPLEMENTARY PUSH-PULL AMPLIFIER.

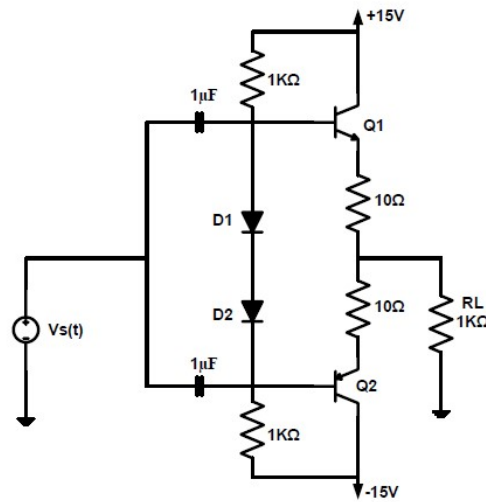


Figure (7-3)

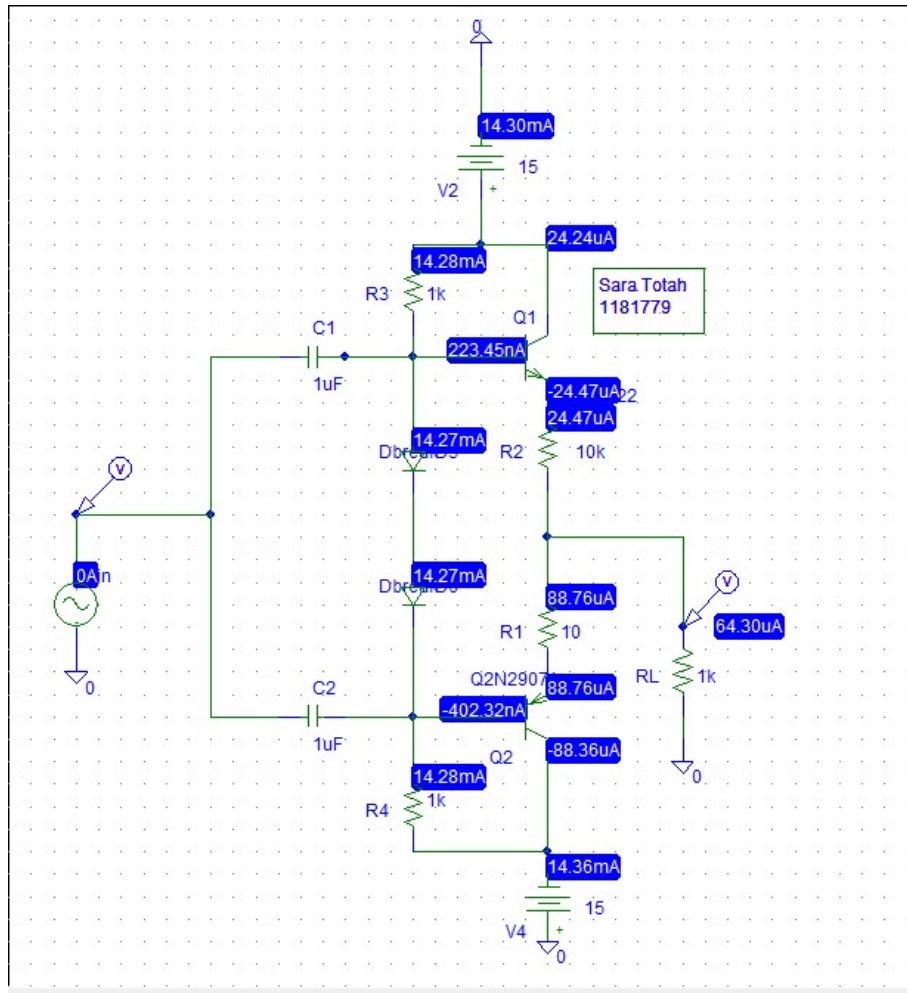


Figure (7-3): PSPICE simulation

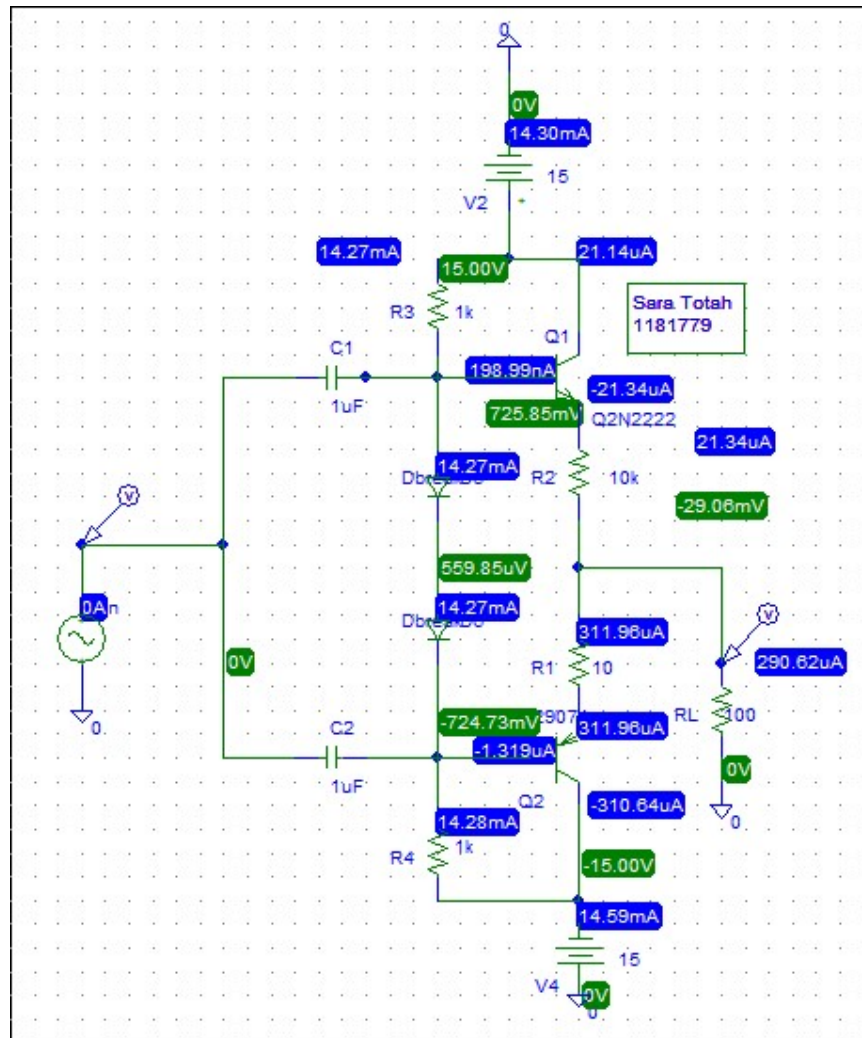


Figure (7-3): PSpice simulation
 $R_L = 100\Omega$