



**Instructor : Nasser Ismail**




**Biasing:** Applying DC voltages to a transistor in order to establish fixed level of voltage and current. For Amplifier (active/Linear) mode, the resulting dc voltage and current establish the operation point to turn it on so that it can amplify AC signals.

## DC Biasing Circuits


1. Fixed-bias circuit
2. Emitter-stabilized bias circuit
3. DC bias with voltage feedback
4. Voltage divider bias circuit

### 1) Fixed Bias Configuration

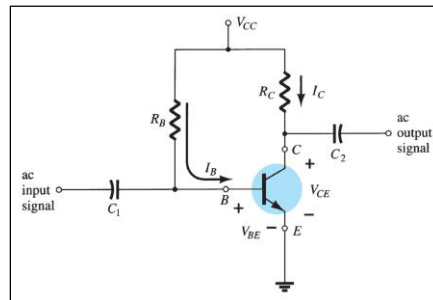

DC equivalent circuit  $\Rightarrow$  means  $f = 0$
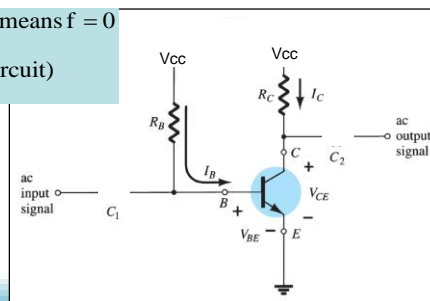
$$\Rightarrow X_C = \frac{1}{2\pi f C} \cong \infty \text{ (open circuit)}$$



## The Base-Emitter Loop


From Kirchhoff's voltage law for Input:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

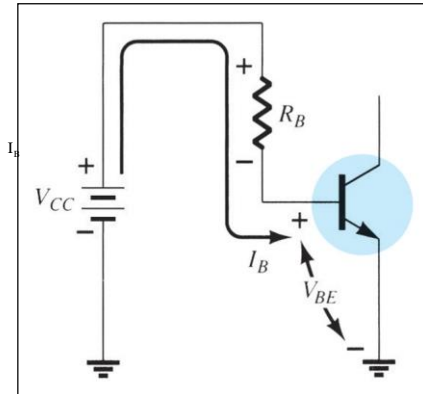Choosing  $R_B$  will establish the required level of  $I_B$



## Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$


$$\text{Since } V_E = 0 \Rightarrow \therefore V_{CE} = V_C$$

$$V_{CE} = V_{CC} - I_C R_C$$

Also

$$V_{BE} = V_B - V_E$$

$$\therefore V_{BE} = V_B$$

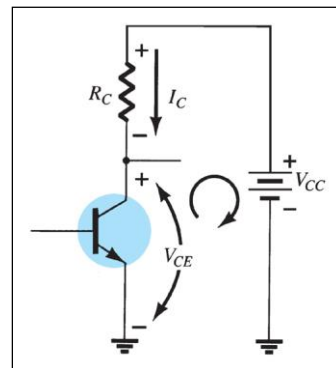

$$\begin{aligned} V_{BC} &= V_B - V_C \\ V_{BE} - V_{CE} - V_{BC} &= 0 \\ \therefore V_{BC} &= V_{BE} - V_{CE} \end{aligned}$$

## Design of Fixed Bias Circuit

Assume  $V_{CC} = 10V$ ,  $\beta_{\text{nominal}} = 100$ ,  $\beta_{\text{min}} = 50$ ,  $\beta_{\text{max}} = 150$

Design for Q - point :  $V_{CEQ} = 5V$ ,  $I_{CQ} = 1mA$  (i.e find unknown component values  $R_B$  and  $R_C$ )

*Solution*

$$I_{BQ} = \frac{I_{CQ}}{\beta_{\text{nominal}}} = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{10 - 0.7}{10 \mu\text{A}} = 930 \text{ k}\Omega$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 5 = 10 - I_C R_C$$
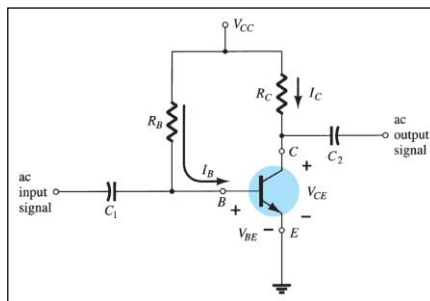
$$\therefore R_C = \frac{5}{1 \text{ mA}} = 5 \text{ k}\Omega$$



## Fixed bias Stability

Assume  $V_{CC} = 10V$ ,  $\beta_{\text{nominal}} = 100$ ,  $\beta_{\text{min}} = 50$ ,  $\beta_{\text{max}} = 150$

Design for Q - point :  $V_{CEQ} = 5V$ ,  $I_{CQ} = 1mA$

*Solution – continued*

If  $\beta = \beta_{\text{min}} = 50$

$$I_B = 10 \mu\text{A}$$

$$I_C = \beta I_B = (50)(10 \mu\text{A}) = 0.5 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 10 - (0.5 \text{ mA})(5 \text{ k}\Omega) = 7.5 \text{ V}$$


If  $\beta = \beta_{\text{max}} = 150$

$$I_B = 10 \mu\text{A}$$

$$I_C = \beta I_B = (150)(10 \mu\text{A}) = 1.5 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C$$
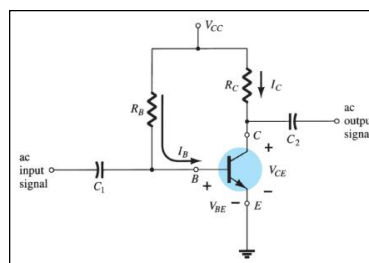
$$V_{CEQ} = 10 - (1.5 \text{ mA})(5 \text{ k}\Omega) = 2.5 \text{ V}$$



for

$$50 \leq \beta \leq 150$$

$$I_B = 10 \mu\text{A} \text{ fixed}$$


$$0.5 \text{ mA} \leq I_C \leq 1.5 \text{ mA}$$

$$7.5 \text{ V} \geq V_{CE} \geq 2.5 \text{ V}$$

$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.5 \text{ mA}}{0.5 \text{ mA}} = 3 \quad \text{Not very stable}$$
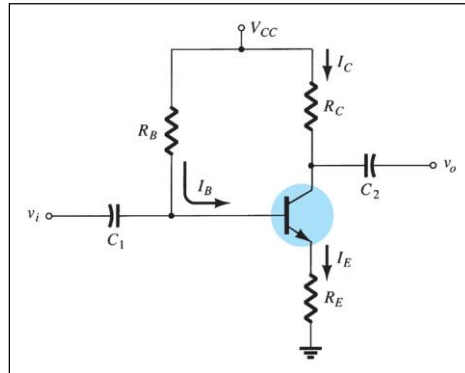
## 2) Emitter-Stabilized Bias Circuit

Adding a resistor ( $R_E$ ) to the emitter circuit stabilizes the bias circuit.



## Base-Emitter Loop

From Kirchhoff's voltage law:

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$


Since  $I_E = (\beta + 1)I_B$ :

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

Solving for  $I_B$ :

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

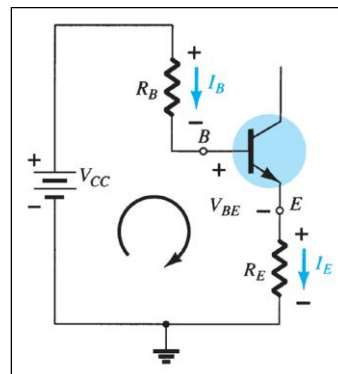$(\beta + 1)R_E$  ← is the emitter resistor as it appears in the base emitter loop



## Base-Emitter Loop


Solving for  $I_E$ :

$$I_E = \frac{V_{CC} - V_{BE}}{\frac{R_B}{(\beta + 1)} + R_E}$$

In order to get  $I_E$  almost independent of  $\beta$  we choose:

$$R_E \gg \frac{R_B}{(\beta + 1)}$$
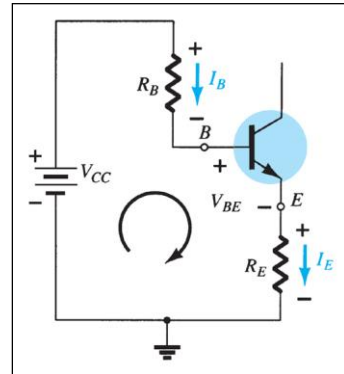
$$\Rightarrow I_E \cong \frac{V_{CC} - V_{BE}}{R_E}$$



Also, in order to guarantee operation in linear mode we choose  $0.1 V_{CC} \leq V_E < 0.2 V_{CC}$

## Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since  $I_E \cong I_C$ :


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

Also:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
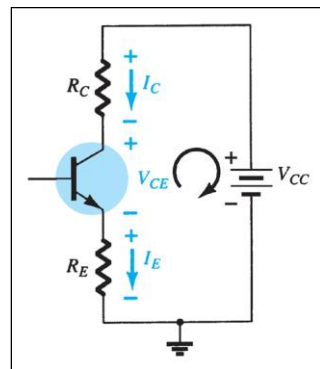
$$V_B = V_{CC} - I_B R_B = V_{BE} + V_E$$



## Design: Emitter Stabilization bias

Assume  $V_{CC} = 10\text{V}$ ,  $\beta_{\text{nominal}} = 100$ ,  $\beta_{\text{min}} = 50$ ,  $\beta_{\text{max}} = 150$

Design for Q - point :  $V_{CEQ} = 5\text{V}$ ,  $I_{CQ} = 1\text{mA}$

*Solution*


– let  $V_E = 0.1 V_{CC}$

$$V_E = 1\text{V}$$

$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1\text{V}}{1.01\text{mA}} \cong 1\text{k}\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \Rightarrow$$
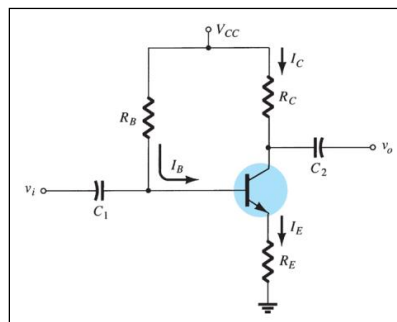
$$R_B I_B + I_B (\beta + 1) R_E = V_{CC} - V_{BE}$$



$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 5 = 10 - 1 - I_C R_C$$

$$\therefore R_C = \frac{4}{1\text{mA}} = 4\text{k}\Omega$$

## Emitter bias Stability

If  $\beta = \beta_{\text{min}} = 50$

$$I_B = \frac{9.3}{829\text{k}\Omega + 51\text{k}\Omega} = 10.56\mu\text{A}$$

$$I_C = \beta I_B = (50)(10.56\mu\text{A}) = 0.528\text{mA}$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 10 - (0.528\text{mA})(4\text{k}\Omega) - 1 = 6.89\text{V}$$


If  $\beta = \beta_{\text{max}} = 150$

$$I_B = \frac{9.3}{829\text{k}\Omega + 151\text{k}\Omega} = 9.489\mu\text{A}$$

$$I_C = \beta I_B = (150)(9.489\mu\text{A}) = 1.423\text{mA}$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$
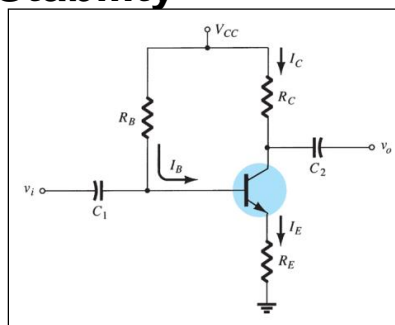
$$V_{CEQ} = 10 - (1.423\text{mA})(4\text{k}\Omega) - 1 = 3.31\text{V}$$



for

$$50 \leq \beta \leq 150$$

$$10.56\mu\text{A} \geq I_B \geq 9.489\mu\text{A}$$


$$0.528\text{mA} \leq I_C \leq 1.423\text{mA}$$

$$6.89\text{V} \geq V_{CE} \geq 3.31\text{V}$$


$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.423\text{mA}}{0.528\text{mA}} \cong 2.7$$

Improved,  
but not  
very  
stable

### Fixed bias

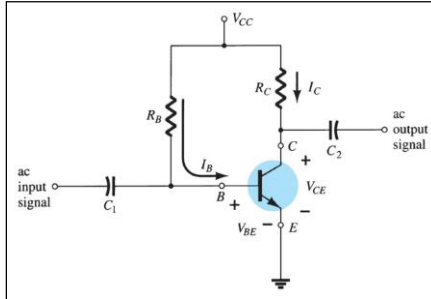


### Emitter Stabilization bias

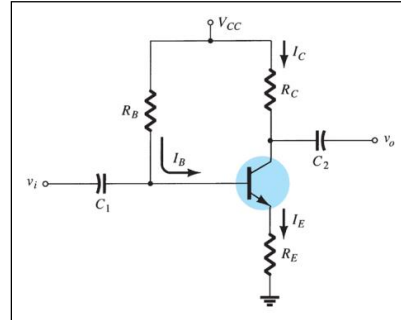
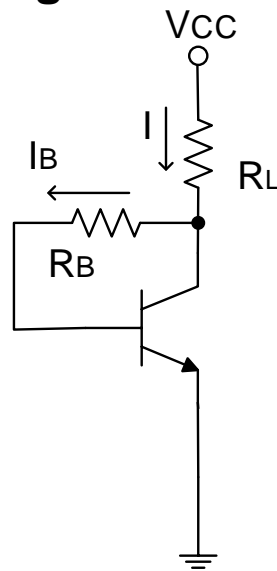
## 3) DC Bias With Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.

In this bias circuit the Q-point is only slightly dependent on the transistor beta,  $\beta$ .





## Base-Emitter Loop

From Kirchhoff's voltage law:

$$V_{CC} - I R_L - I_B R_B - V_{BE} = 0$$

$$I = I_C + I_B$$

$$I_C = \beta I_B$$

Solving for  $I_B$ :


$$I_B = \frac{V_{CC} - V_{BE}}{R_L(\beta + 1) + R_B}$$

$$V_{CC} = I R_L + V_{CE}$$

$$I = I_C + I_B$$

$$V_{CE} = V_{CC} - (I_C + I_B) R_L$$

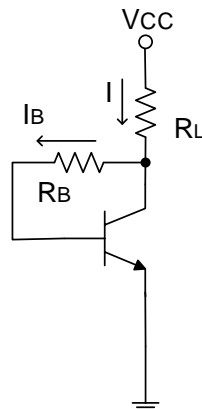suppose  $\beta \uparrow, I_B \downarrow, I_C = \uparrow \beta \cdot I_B \downarrow \cong \text{const}$   
there is some kind of compensation effect



## Design: Voltage feedback bias

Assume  $V_{CC} = 10V, \beta_{\text{nominal}} = 100, \beta_{\text{min}} = 50, \beta_{\text{max}} = 150$

Design for Q - point :  $V_{CEQ} = 5V, I_{CQ} = 1mA$

*Solution*

$$R_L = \frac{V_{CC} - V_{CE}}{I_C + I_B} = \frac{10 - 5}{1mA + \frac{1mA}{100}} = 4.95 \text{ k}\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_L(\beta + 1) + R_B}$$

$$\therefore R_B = 430 \text{ k}\Omega$$

If  $\beta = \beta_{\text{min}} = 50$

$$I_B = 0.013627 \text{ mA}$$

$$I_C = 0.68 \text{ mA}$$

If  $\beta = \beta_{\text{max}} = 150$

$$I_B = 0.00793 \text{ mA}$$

$$I_C = 1.19 \text{ mA}$$


for

$$50 \leq \beta \leq 150$$

$$0.68 \text{ mA} \leq I_C \leq 1.19 \text{ mA}$$

$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.19 \text{ mA}}{0.68 \text{ mA}} \cong 1.75$$


Better  
Q-point  
stability

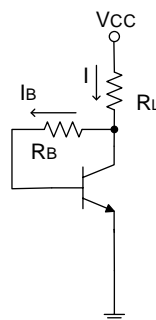
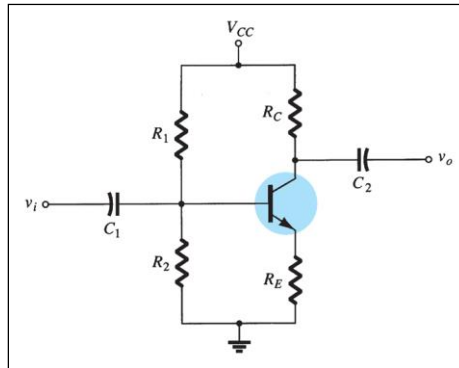
## 4) Voltage Divider Bias

*This is a very stable bias circuit.*

The currents and voltages are nearly independent of any variations in  $\beta$  if the circuit is designed properly



## Approximate Analysis

Where  $I_B \ll I_1$  and  $I_1 \cong I_2$ :

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$

$$I_{E(\text{approximate})} = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E}$$


From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

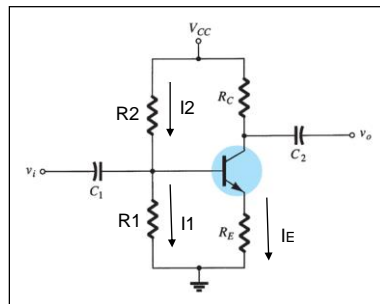Here we got  $I_C$  independent of  $\beta$  which provides good Q-point stability



## Exact Analysis

We must try to make  $I_B$  as close as possible to zero

Thevenin Equivalent circuit for the circuit left of the base is done


$$V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2}$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$\text{but } I_B = \frac{I_E}{\beta + 1}$$
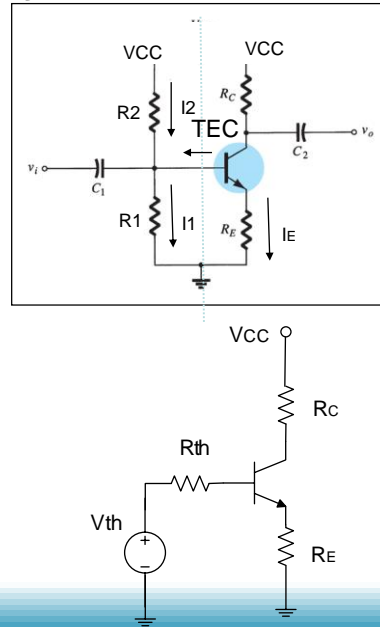
$$\therefore I_{E(\text{exact})} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$



## Exact Analysis

$$\therefore I_{E(\text{exact})} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$

if we compare to approximate solution

$$I_{E(\text{approximate})} = \frac{V_B - V_{BE}}{R_E}$$

$\Rightarrow$  we must make the quantity  $\frac{R_{th}}{\beta + 1} \ll R_E$


Here we got  $I_C$  independent of  $\beta$

$$\therefore R_{th} \ll (\beta + 1) R_E$$

$$\text{as a rule let } R_{th} \ll \frac{(\beta + 1) R_E}{10}$$

or

$$R_{th} \ll \frac{\beta R_E}{10}$$

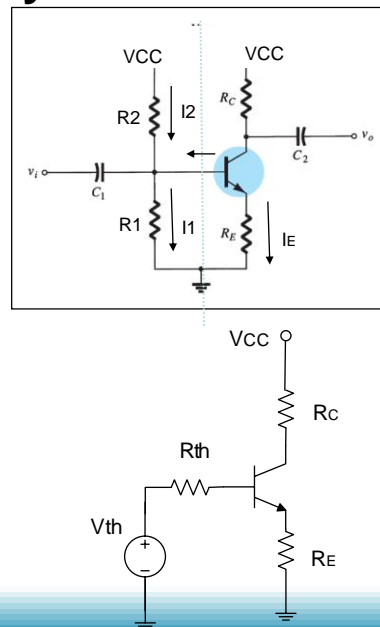

## Design: Voltage Divider bias

Assume  $V_{CC} = 10V$ ,  $\beta_{\text{nominal}} = 100$ ,  $\beta_{\text{min}} = 50$ ,  $\beta_{\text{max}} = 150$

Design for Q - point :  $V_{CEQ} = 5V$ ,  $I_{CQ} = 1mA$

*Solution*

1) let  $V_E = 0.1 V_{CC}$

$$V_E = 1V$$


$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1V}{1.01mA} \cong 1k\Omega$$

2) let  $R_{th} = \frac{R_E \cdot \beta_{\text{nominal}}}{50} = \frac{1k\Omega \cdot 100}{50} = 2k\Omega$

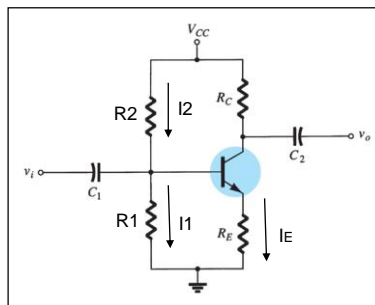3)  $V_{CC} = R_C I_C + I_E R_E + V_{CE}$

$$V_{CEQ} = 5$$

$$\therefore R_C = \frac{V_{CC} - V_{CE} - V_E}{1mA} = \frac{10 - 5 - 1}{1mA} = 4k\Omega$$



## Design: Voltage Divider bias

Assume  $V_{CC} = 10V$ ,  $\beta_{\text{nominal}} = 100$ ,  $\beta_{\text{min}} = 50$ ,  $\beta_{\text{max}} = 150$

Design for Q - point :  $V_{CEQ} = 5V$ ,  $I_{CQ} = 1mA$

*Solution - continued*

4)  $I_E = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$


$$\therefore V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2} = I_E \left( \frac{R_{th}}{\beta + 1} + R_E \right) + V_{BE} = 1.72V \dots (1)$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} = 2k\Omega \dots \dots \dots (2)$$

solving (1) & (2) yields:

$$R_1 = 2.42k\Omega$$

$$R_2 = 11.64k\Omega$$

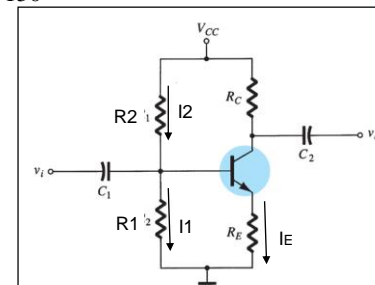

## Voltage Divider bias Stability

If  $\beta = \beta_{\min} = 50$

$I_C = 0.982 \text{ mA}$

If  $\beta = \beta_{\max} = 150$

$I_C = 1.0069 \text{ mA}$

for

$50 \leq \beta \leq 150$

$0.982 \text{ mA} \leq I_C \leq 1.0067 \text{ mA}$

$$\therefore \frac{I_{C(\max)}}{I_{C(\min)}} = \frac{1.0067 \text{ mA}}{0.982 \text{ mA}} \cong 1.0254$$

Very good  
Q-point  
stability


## PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *nnp* transistor circuits. The only difference is that the currents are flowing in the opposite direction.

## Circuit using pnp transistor:
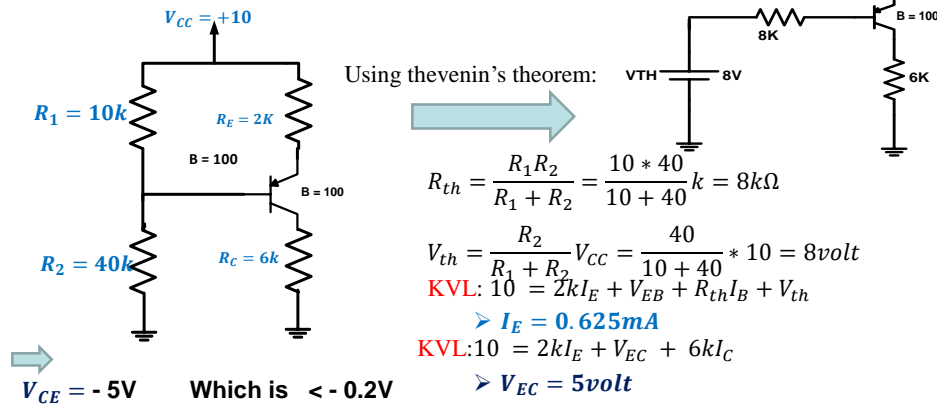
### Example:


Find  $I_E$ ,  $V_{EC}$ , for the circuit below: **solution**



### Example:

Find  $I_{E1}$ ,  $I_{E2}$

### Solution



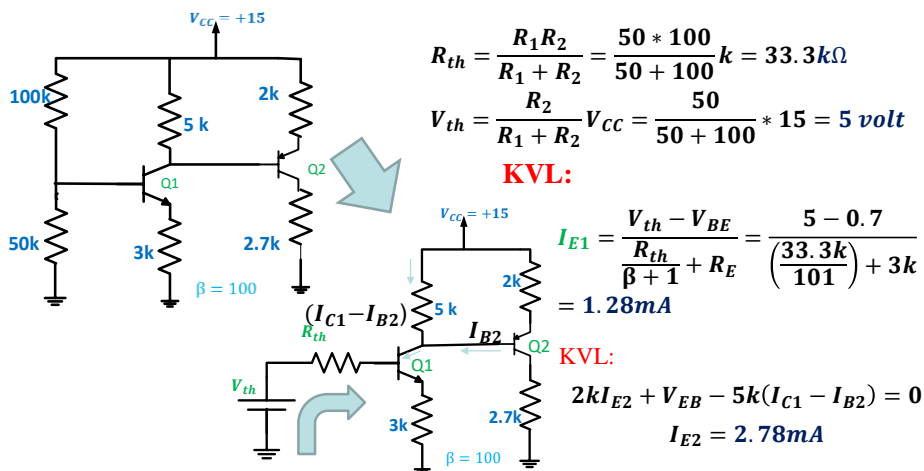


## BJT Ac-Small signal analysis using Graphical method:

Graphical method:

**KVL:**  $V_{CC} = R_C I_C + V_{CE}$
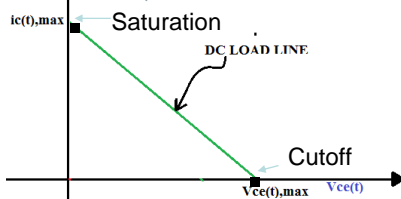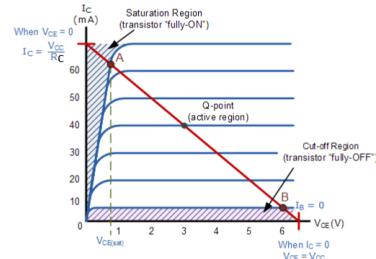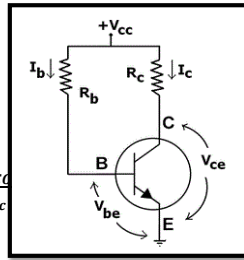
$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C}$$



$$i_{C(t),max} = \frac{V_{CC}}{R_C} \quad \text{Saturation}$$

$$V_{CE(t),max} = V_{CC} \quad \text{Cutoff}$$


## BJT Amplifier

Using superposition

$$V_{BE}(t) = V_{BE} + v_{be}$$

$$i_C(t) = I_{CQ} + i_c$$

$$V_{CE}(t) = V_{CEQ} + v_{ce}$$

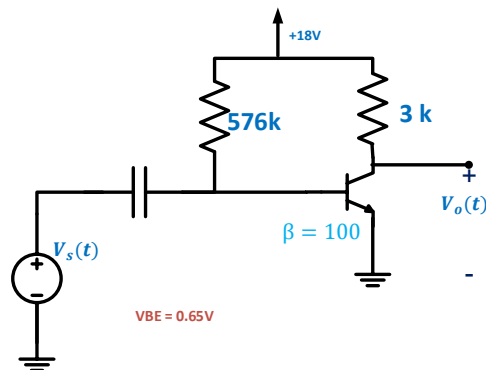

## DC Load Lines

Assume  $V_{CC} = 18V$ ,  $\beta = 100$

$R_B = 576 k\Omega$ ;  $R_C = 3k\Omega$ ;  $V_{BE} = 0.7 V$

FIRST: DC ANALYSIS

$$V_{CC} = V_{CE} + I_C R_C$$

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C} \Leftarrow I_C = f(V_{CE})$$


This is a straight line equation

$$Y = mX + b$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{18 - 0.7}{576 k\Omega} = 30 \mu A$$

$$I_C = \beta I_B = 3 mA$$
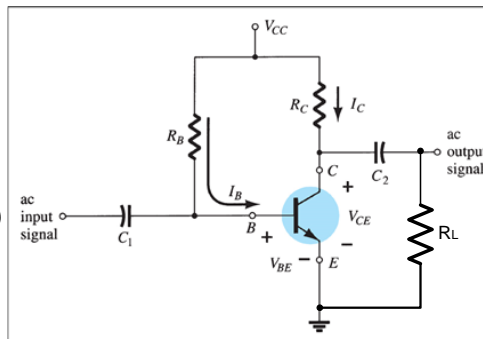
$$V_{CE} = V_{CC} - I_C R_C = 18 - (3mA)(3k\Omega) = 9 V$$



## DC Load Line

$I_{Csat}$


$$I_{Csat} = \frac{V_{CC}}{R_C}$$

$$V_{CE} = V_{CE(sat)} \cong 0 V$$

$V_{CEcutoff}$

$$V_{CE(cutoff)} = V_{CC}$$

$$I_C = 0 mA$$


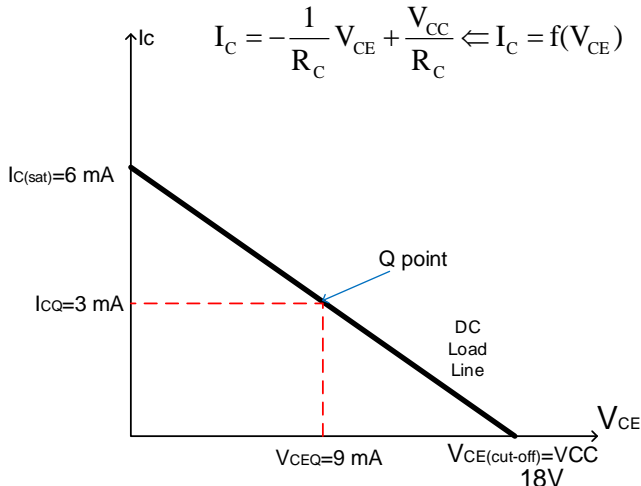




## Basic BJT Amplifiers Circuits (for info only)
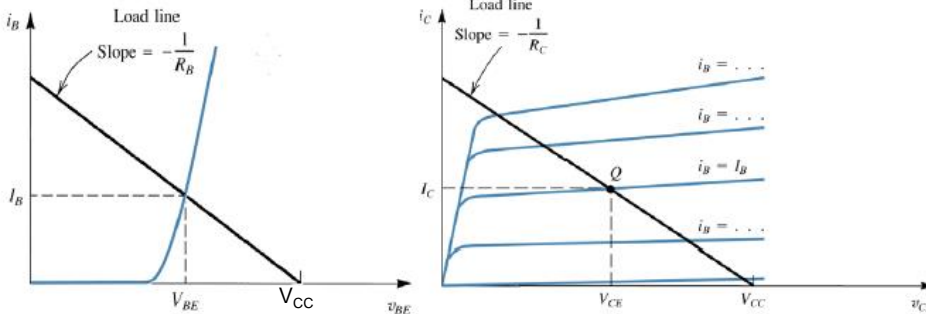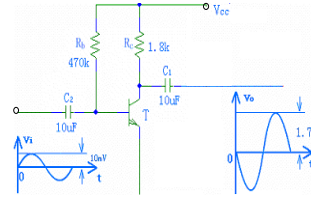
### Graphical Analysis

- Can be useful to understand the operation of BJT circuits.
- First, establish DC conditions by finding  $I_B$  (or  $V_{BE}$ )
- Second, figure out the DC operating point for  $I_C$





Can get a feel for whether the BJT will stay in active region of operation  
– What happens if  $R_C$  is larger or smaller?



## Basic BJT Amplifiers Circuits

(for info only)

### Graphical Analysis

Q-point is centered on the ac load line:

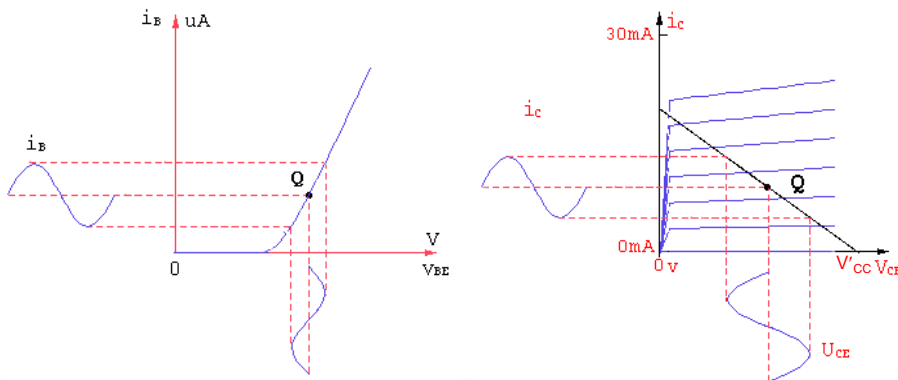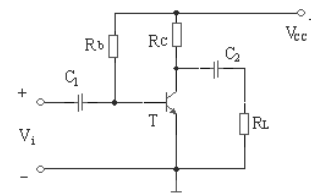

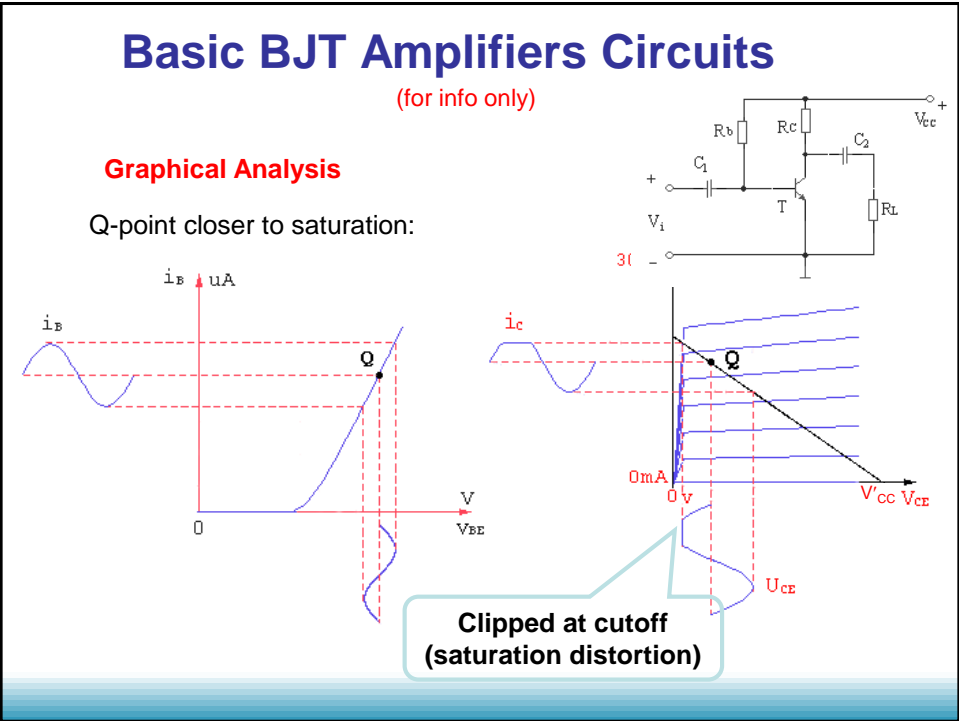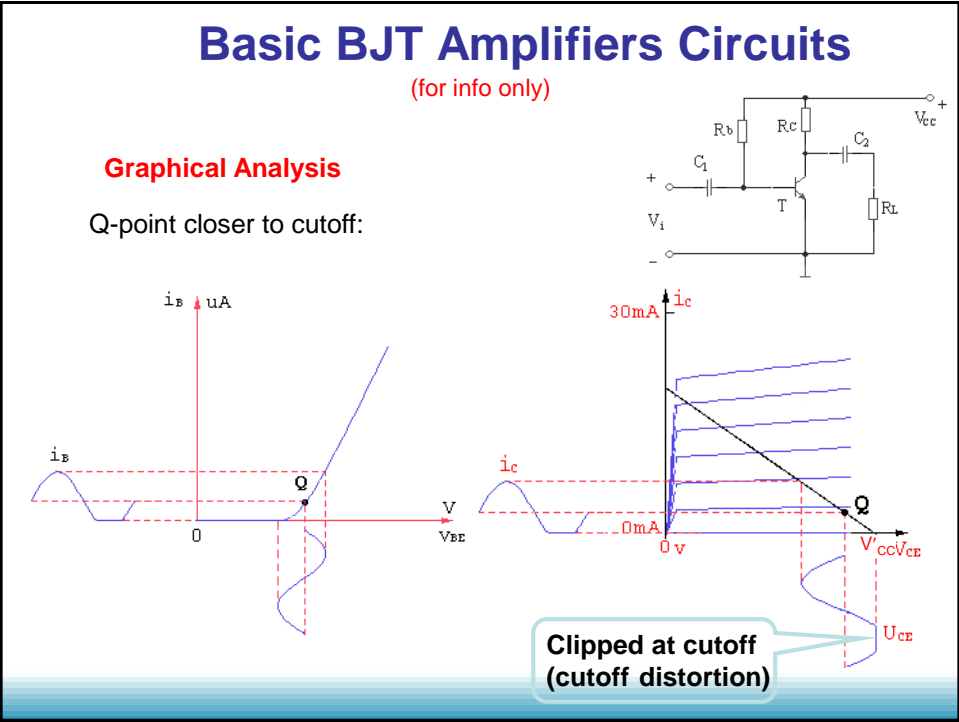

# Basic BJT Amplifiers Circuits

(for info only)

## Graphical Analysis

