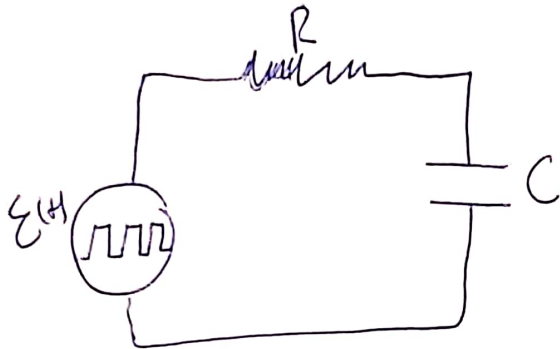


Exp 6: Capacitors and Inductors

Theory: RC Circuit



1. Charging:-

$$Q(t) = C\mathcal{E}(1 - e^{-t/RC})$$

$$V_C = \frac{Q}{C}$$

$$V_C = \mathcal{E}(1 - e^{-t/RC})$$

$RC = \tau$ $\rightarrow$ time constant :- is measure how ~~the~~ fast the voltage across the capacitor rises

$$\rightarrow \text{at } t = \tau \quad V_C = 0.63\mathcal{E}$$

which means that the voltage across the capacitor rises to 0.63 of its max value at $t = \tau$

$$I(t) = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

Current passing through the circuit

$$V_R = I(t)R = \mathcal{E} e^{-t/RC}$$

Voltage across the resistor.

charging

$$Q(t) = C \mathcal{E} e^{-t/RC}$$


$$V_C = \mathcal{E} e^{-t/RC}$$

$\boxed{T = RC}$ time constant: which means here [measure of how fast the voltage across the capacitor plates decreases]


at $t = T$ $V_C = 0.37 \mathcal{E} \rightarrow$ the voltage across the capacitor plates decay to 0.37 of the max value within a time T

$$I(t) = \frac{dQ}{dt} = -\frac{\mathcal{E}}{R} e^{-t/RC}$$


current passing through the circuit

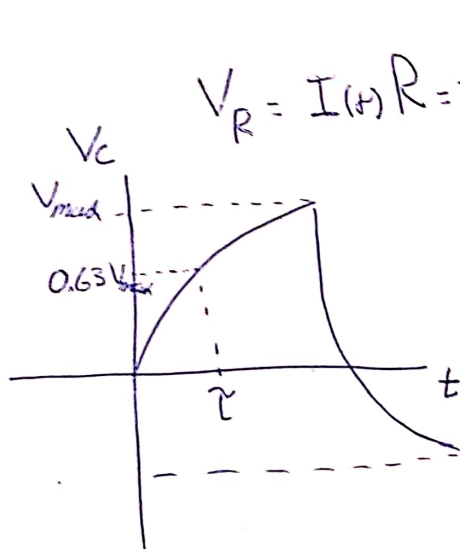

$$V_R = I(t)R = -\mathcal{E} e^{-t/RC}$$

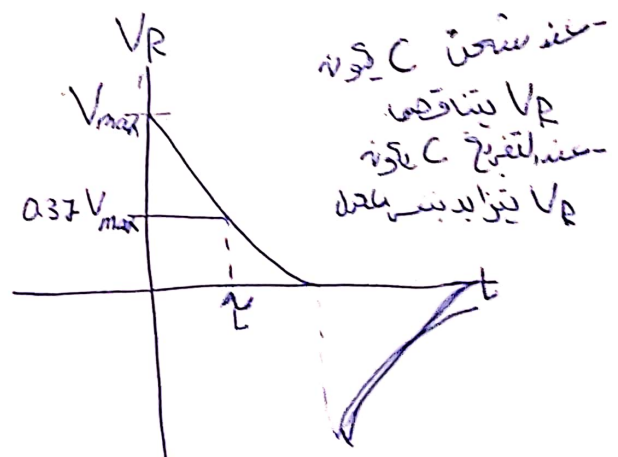

RL Circuit:

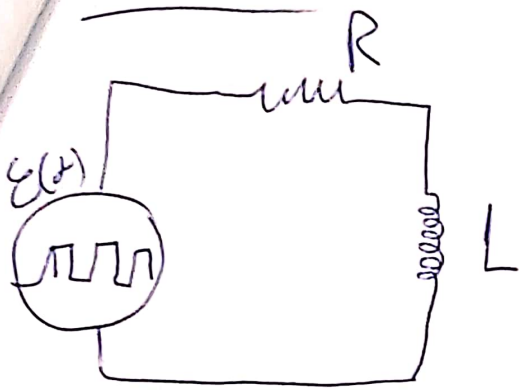

$$I(t) = \frac{\mathcal{E}}{R} \left(1 - e^{-\frac{Rt}{L}} \right)$$

- Current passing through

$$V_R = IR = \mathcal{E} \left(1 - e^{-Rt/L} \right)$$



- Voltage across the resistor

$$V_L = I \frac{dL}{dt} = \mathcal{E} e^{-Rt/L}$$


$\frac{L}{R}$ = time constant = measure how fast the current rises in the circuit.

at $t = \tau$ $V_R = 0.63 \mathcal{E}$

$V_L = 0.37 \mathcal{E}$

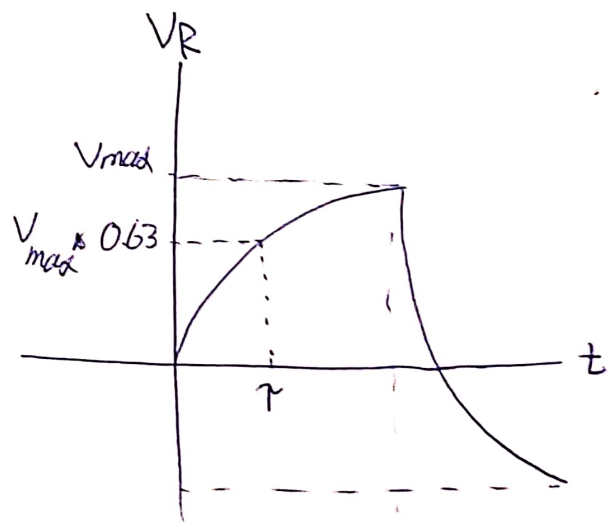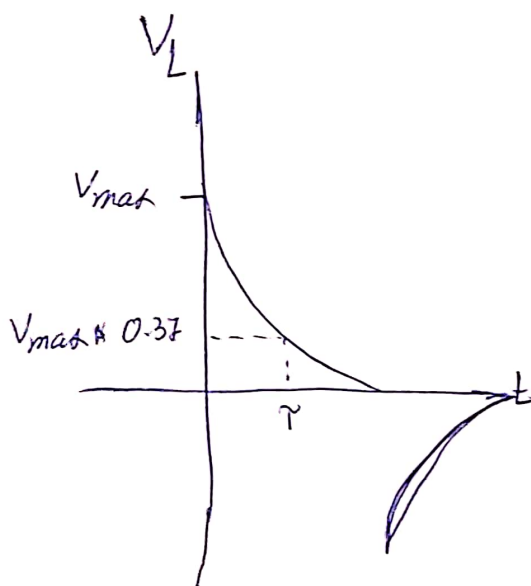

L C Circuit

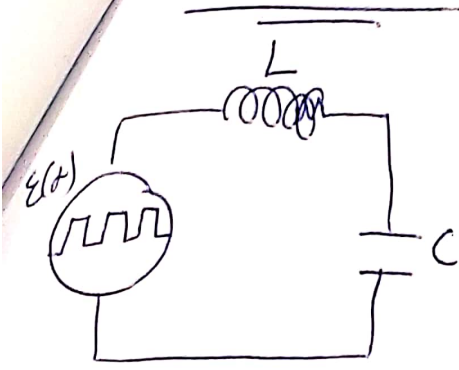


in this circuit the voltage across the capacitor

$$V_C = V_{C0} \cos(\omega t + \phi)$$

V_{C0} : the amplitude [const]


$$\omega = \frac{1}{\sqrt{LC}}$$

angular freq

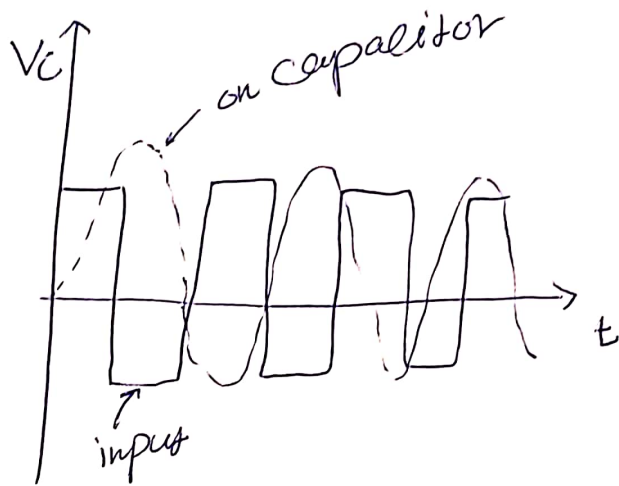

RC - Circuit :


1. Connect the following circuit.

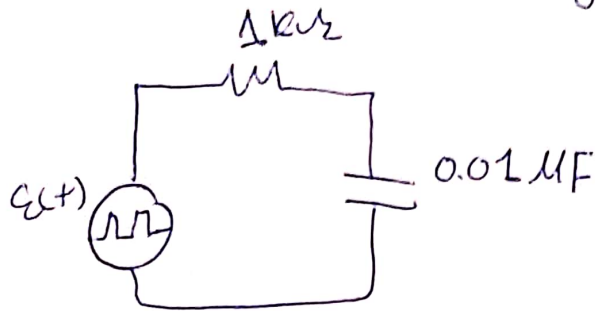

2. Use square wave from the ~~signal~~ signal generator.
 3. Display V_C on the oscilloscope screen.
Measure τ for both charging and discharging.
 4. Display V_R on Oscill ... Measure τ for both charging and discharging.
- You have to ~~exchange~~ exchange the places of R and C why?!

RL Circuit:


1. Connect the following circuit.

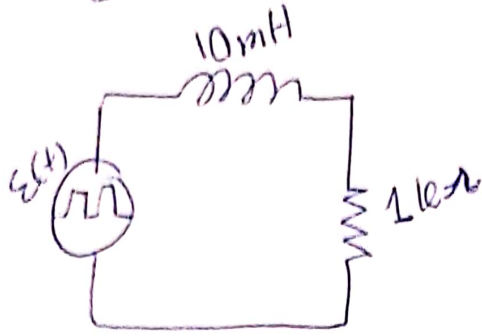

2. Display V_R and V_L on the oscilloscope screen, measure τ in Both Cases.

LC Circuit:

1. Connect the following circuit.

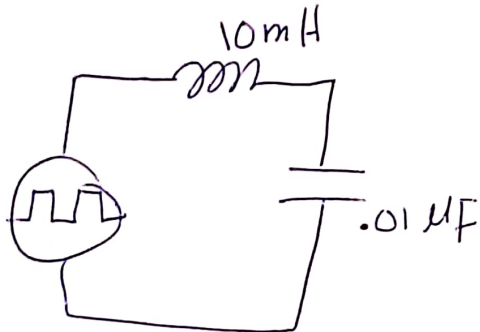

2. Display V_C on the oscilloscope screen, measure the amplitude A and the angular freq ω