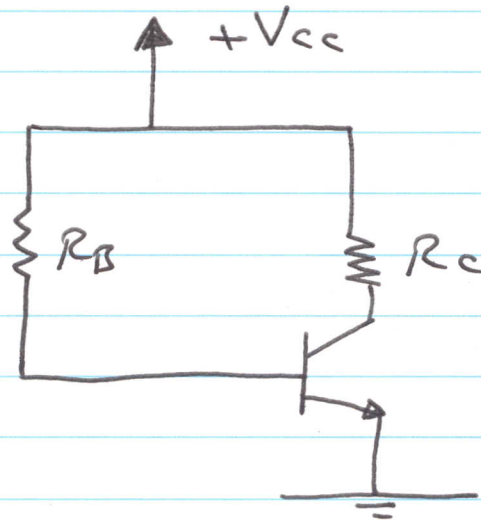


Transistor biasing Circuits

1) Fixed current bias Circuit



$$\text{KVL : } V_{CC} = R_B I_B + V_{BE}$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$\text{KVL : } V_{CC} = R_C I_C + V_{CE}$$

$$\therefore V_{CE} = V_{CC} - R_C I_C$$

Design a fixed current bias circuit using a Silicon transistor having

$$\beta(\min) = 25, \quad \beta(\max) = 75$$

Such that $I_C = 1\text{mA}$, and $V_{CE} = 5\text{V}$

$$\text{given } V_{CC} = 10\text{V}$$

$$I_B = \frac{V_{CC} - 0.7}{R_B} \quad \text{--- (1)}$$

$$V_{CE} = V_{CC} - R_C I_C \quad \text{--- (2)}$$

using equation (2)

$$5 = 10 - R_C (1 \text{ mA})$$

$$\therefore R_C = 5 \text{ k}$$

$$I_B = \frac{I_C}{\beta}$$

$$\text{Let } \beta = \frac{75 + 25}{2} = 50$$

$$\therefore I_B = \frac{1 \text{ mA}}{50} = 20 \mu\text{A}$$

using equation (1)

$$I_B = \frac{10 - 0.7}{R_B} = 20 \mu\text{A}$$

$$\therefore R_B = 465 \text{ k}$$

* If $\beta = 50$, $R_c = 5k$, and $R_B = 465k$

$$I_c = 1mA, \text{ and } V_{CE} = 5V$$

BUT

1) When $\beta = \beta(\min) = 25$

$$I_B = 20\mu A$$

$$I_c = 0.5mA$$

$$V_{CE} = 7.5V$$

2) When $\beta = \beta(\max) = 75$

$$I_B = 20\mu A$$

$$I_c = 1.5mA$$

$$V_{CE} = 2.5V$$


\therefore For

$$75 \geq \beta \geq 25$$

$$1.5mA \geq I_c \geq 0.5mA$$

\therefore The fixed current bias circuit is not a very satisfactory circuit of obtaining good bias point stability.

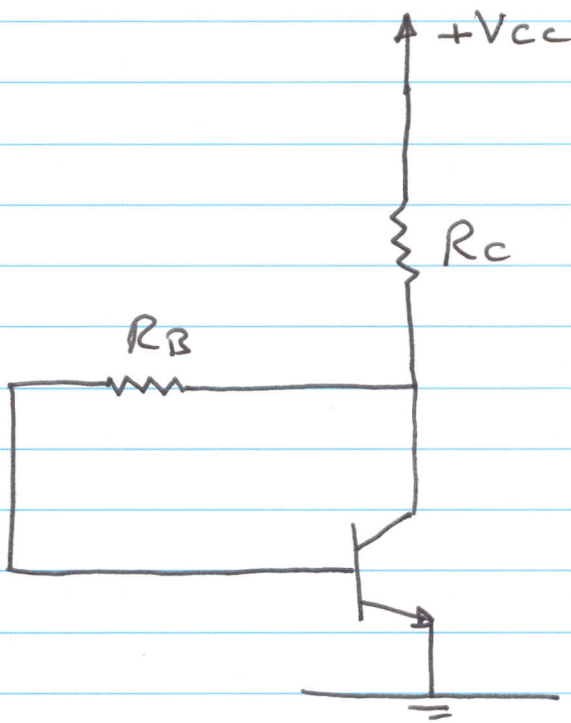2) Collector-to-base feedback bias circuit



$$\text{KVL : } V_{CC} = R_C I + R_B I_B + V_{BE}$$
$$I = I_C + I_B$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_C} \quad \text{--- (1)}$$

$$I_C = \beta I_B$$

$$\text{KVL : } V_{CC} = R_C (I_C + I_B) + V_{CE}$$

$$\therefore V_{CE} = V_{CC} - R_C (I_C + I_B) \quad \text{--- (2)}$$

Design :

$$\text{Let } \beta = \beta(\text{typical}) = 50$$

$$\therefore I_B = \frac{I_C}{\beta} = 20 \mu A$$

using equation ②

$$V_{CC} = V_{CE} + R_C (I_C + I_B)$$

$$\therefore R_C \approx 4.9 K$$

using equation ①

$$I_B = \frac{V_{CC} - 0.7}{R_B + R_C (\beta + 1)}$$

$$\therefore R_B = 215 K$$


Proof that

$$75 \geq \beta \geq 25$$

$$1.19 \text{ mA} \geq I_C \geq 0.68 \text{ mA}$$

\therefore There is an improvement over the fixed current bias circuit

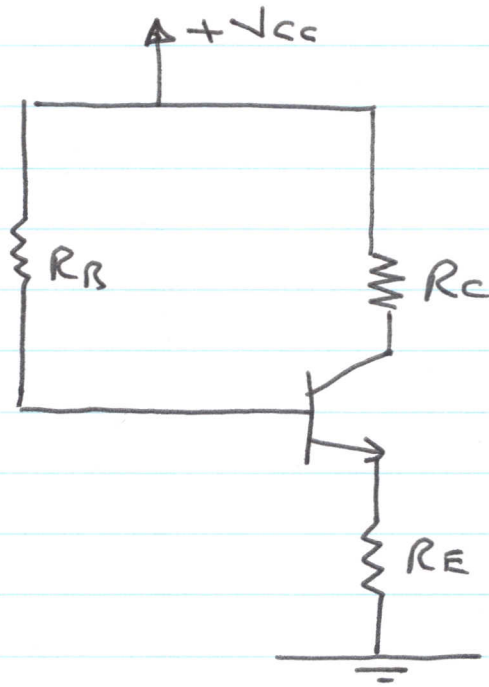3) Biasing Circuit with Stabilization resistance [R_E]



$$\text{KVL : } V_{CC} = R_B I_B + V_{BE} + R_E I_E$$

$$I_E = (\beta + 1) I_B$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} \quad \text{--- (1)}$$

$$I_C = \beta I_B$$

$$\text{KVL : } V_{CC} = R_C I_C + V_{CE} + R_E I_E$$

$$\therefore V_{CE} = V_{CC} - R_C I_C - R_E I_E \quad \text{--- (2)}$$

Design :

In this Circuit we have 3 unknowns
(R_B , R_C , and R_E) .

We have two equations

\therefore We must make a new assumption

$$\frac{V_{CC}}{5} \geq V_{RE} \geq \frac{V_{CC}}{10}$$

and $\beta = \beta(\text{typical}) = 50$

$$\therefore \text{Let } V_{RE} = \frac{V_{CC}}{5} = 2V$$

$$\therefore R_E = \frac{V_{RE}}{I_E} \approx \frac{2V}{1mA} = 2K$$

using equation (2)

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E$$

$$\therefore R_C = 3K$$

using equation (1)

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} = 20\mu A$$

$$\therefore R_B = 365 \text{ k}$$


Proof

$$75 \geq \beta \geq 25$$

$$1.349 \text{ mA} \geq I_C \geq 0.55755 \text{ mA}$$

\therefore There is an improvement over the fixed current bias circuit

4) Voltage Divider Bias Circuit

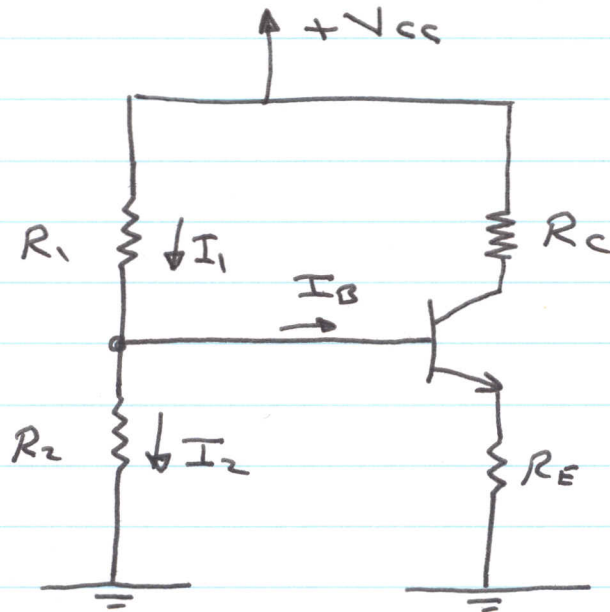

a) Approximate method

I_B very small $\rightarrow I_B \approx 0$

$$\therefore I_2 = I_1$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$


$$V_E = V_B - V_{BE}$$

$$I_{E1} = \frac{V_E}{R_E}$$

$$I_C = \alpha I_E \approx I_E$$

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E$$

b) Exact method

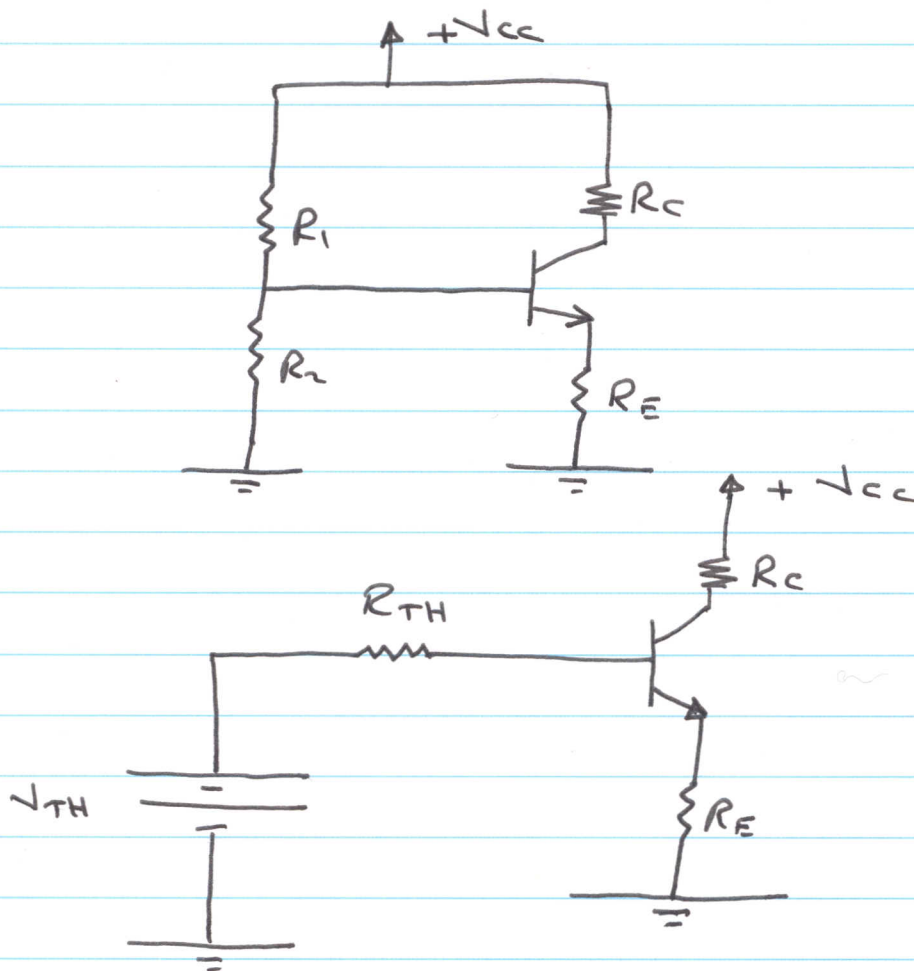

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

KVL : $V_{TH} = R_{TH} I_B + V_{BE} + R_E I_E$

$$I_E = (\beta + 1) I_B$$

$$\therefore I_{E2} = \frac{V_{TH} - V_{BE}}{\frac{R_{TH}}{\beta + 1} + R_E}$$

using the approximate method, we get

$$I_{E1} = \frac{V_B - V_{BE}}{R_E}$$

$$\text{where } V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

using the exact method, we get

$$I_{E2} = \frac{V_{TH} - V_{BE}}{\frac{R_{TH}}{\beta + 1} + R_E}$$

$$\text{where } V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

To make $I_{E2} \approx I_E$

$$\frac{R_{TH}}{\beta + 1} + R_E \approx R_E$$

$$\frac{R_{TH}}{\beta + 1} \ll R_E$$

$$R_{TH} \ll (\beta + 1) R_E$$

\therefore let

$$R_{TH} = \frac{(\beta + 1) R_E}{10, 20, 30, \dots}$$

Design :

$$\text{Let } V_{RE} = \frac{V_{CC}}{10} = 1 \text{ V}$$

$$\therefore R_E = \frac{V_{RE}}{I_E} \approx 1 \text{ K}$$

$$\text{Let } R_{TH} = \frac{\beta R_E}{50} = 1 \text{ K} ; \beta = 50$$

$$\text{KVL: } V_{CC} = R_C I_C + V_{CE} + R_E I_E$$

$$10 = R_C (1 \text{ mA}) + 5 \text{ V} + (1 \text{ K})(1.02 \text{ mA})$$

$$\therefore R_C = 4 \text{ K}$$

To find R_1 and R_2 , we need to find

R_{TH} , and V_{TH}

$$\text{using } I_E = \frac{V_{TH} - 0.7}{\frac{R_{TH}}{\beta + 1} + R_E}$$

$$\text{We get } V_{TH} = 1.72 \text{ V}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$\therefore R_1 = 5.8 \text{ K}, \text{ and } R_2 = 1.2 \text{ K}$$

If $R_1 = 5.8k$, $R_2 = 1.2k$, $R_C = 4k$, and

$$R_E = 1k, \beta = 50$$

$$I_{CQ} = 1mA, \text{ and } V_{CE} = 5V$$

But

$$75 \geq \beta \geq 25$$

$$1.0067mA \geq I_C \geq 0.982mA$$