The Use of Diode Model

STUDENTS-HUB.com

3) The use of models

A piece wise linear models is an electrical equivalent circuit of a nonlinear electronic device

It is composed of linear circuit elements arranged to approximate the characteristics of the electronic device.

STUDENTS-HUB.com



• When $V_s \ge 0$; the Diode is on, and replaced with short circuit

► When V_s<0; the Diode is off, and replaced with open STUDE KAGE HUB.com



STUDENTS-HUB.com

b) Knee Voltage model

▶ When V_s ≥ V_k; the Diode is on, and replaced with a constant voltage source



Κ

loaded By: anonymous

• When $V_s < V_k$; the Diode is off, and replaced with open circuit

K

 V_k

STUDENTS-HUB.com

Α

K



- ▶ When $V_s \ge V_o$; the Diode is on, and replaced with a constant voltage source V_o and resistance R_o
- When V_s < V_o; the Diode is off, and replaced with open circuit

STUDENTS-HUB.com



► When $V_s < V_o$; the Diode is off, and replaced with open STU**CiEGUTS**-HUB.com



Find the Q point (I_{DQ}, V_{DQ}) using

 a) ideal diode model
 b) knee voltage model



STUDENTS-HUB.com



since $V_S \ge 0$, the diode is on and replaced with short circuit.

 $\therefore I_{DQ} = \frac{2}{100} = 20 \, mA$

 $\therefore V_{DQ} = 0 V$

STUDENTS-HUB.com



b) Using knee voltage model

 $R_s = 100 \Omega$ since $V_S \ge 0.7$, the diode is on and replaced with + $V_k = 0.7$. $V_{\rm s} = 2 V_{-}$ V_{DQ} I_{DQ} $\therefore I_{DQ} = \frac{2-0.7}{100} = 13 \, mA$ $R_s = 100 \Omega$ + $\therefore V_{DO} = 0.7 V$ $V_{\rm s} = 2 V_{\rm s}$ V_D I_{D0}

STUDENTS-HUB.com

c) using nonlinear mathematic

$$I_{DQ} = 12.137 mA$$

 $V_{DQ} = 0.7863 V$

Taking the knee voltage into a count

▶ If $V_S \ge 10 V_k$, we could use ideal diode model.

If $V_S < 10 V_k$, we must use knee voltage model.

STUDENTS-HUB.com