

ENEE2360 CH9 Homework Problems

15. For the network of Fig. 9.81:

- Determine h_{ie}
- Find $A_{v_{mid}} = V_o/V_i$.
- Calculate Z_i .
- Determine f_{L_s} , f_{C_1} , f_{C_2} , f_{C_E} ($\omega_{C_1}, \omega_{C_2}, \omega_{C_E}$)
- Determine the low cutoff frequency. $\rightarrow f_L$ (ω_L)

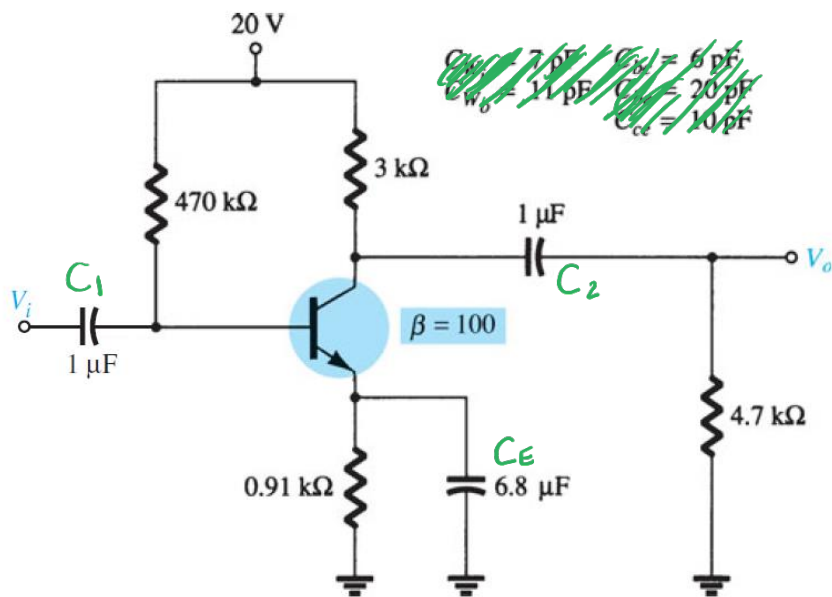


FIG. 9.81

*27. For the network of Fig. 9.81 with R_s and V_s of Fig. 9.84:
Determine f_{H_i} and f_{H_o} .

23. For the network of Fig. 9.88:
- Determine V_{GS_Q} and I_{D_Q} .
 - Find g_{m0} and g_m .
 - Calculate the midband gain of $A_v = V_o/V_i$.
 - Determine Z_i .
 - Calculate $A_{v_s} = V_o/V_s$.
 - Determine f_{L_G} , f_{L_C} , and f_{L_S} .
 - Determine the low-cutoff frequency.

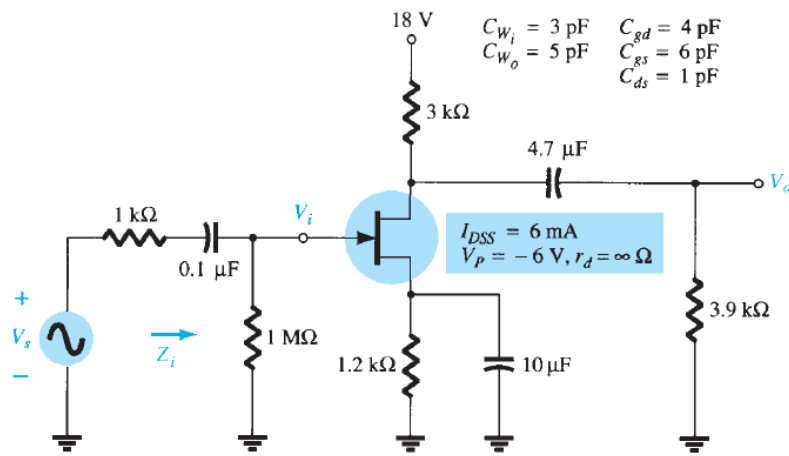


FIG. 9.88

31. For the network of Fig. 9.88:
- Determine g_{m0} and g_m .
 - Find A_v and A_{v_s} in the mid-frequency range.
 - Determine f_{H_i} and f_{H_o} .