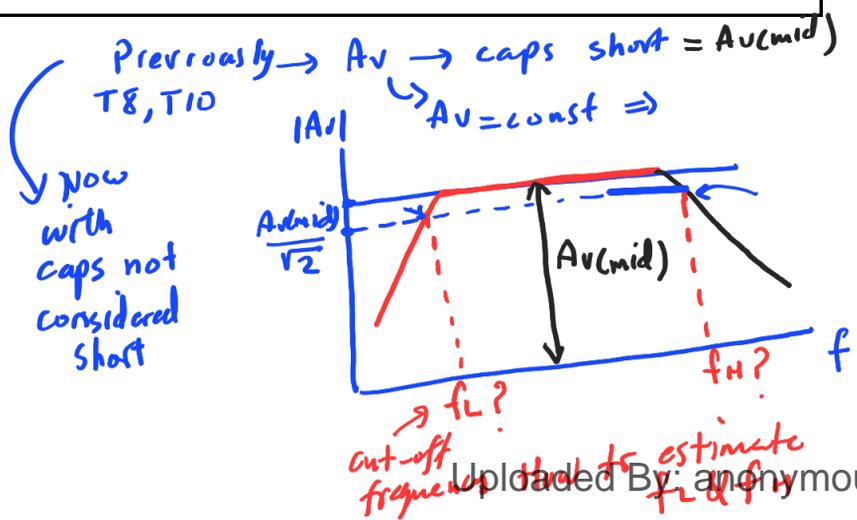


ENEE2360 Analog Electronics

T12: Amplifier Frequency Response




Instructor : Nasser Ismail



Amplifier Frequency Response ?

- Audio frequency signals such as speech and music are combination of many different sine waves, occurring simultaneously with different amplitude and frequency in the following range (20Hz-20kHz (audible noise) , other types of signals have their own range.
- In order for the output to be an amplified version of the input, the amplifier must amplify each and every component in the signal by the same amount
- The Bandwidth must cover the entire range of frequency components if considered amplification is to be achieved

Amplifier Frequency Response

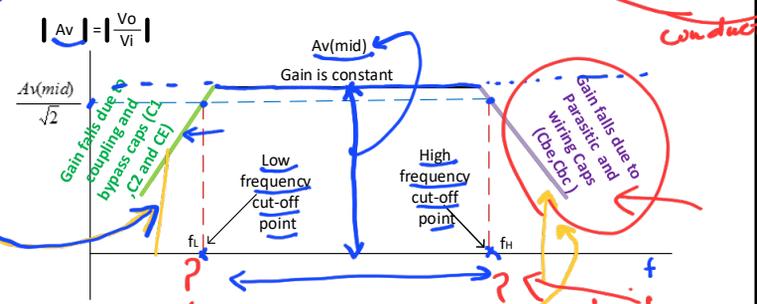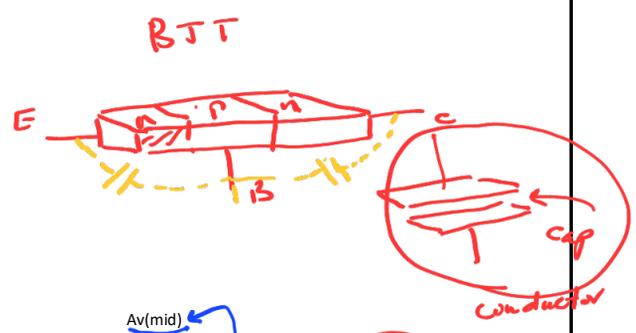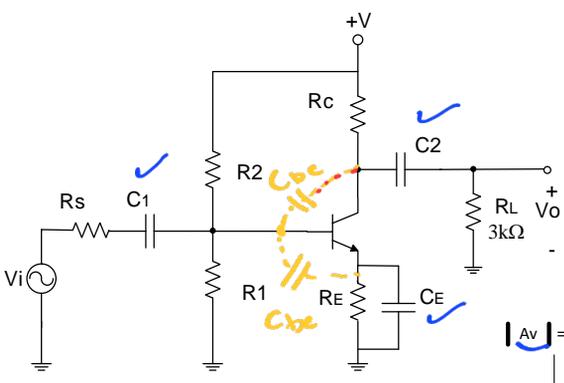


✓ C_1, C_2, C_E ← real (physical) caps

← C_{be}, C_{bc}
 C_{gs}, C_{gd} ← hidden (parasitic or stray) cap

Gain falls due to parasitic and wiring caps (C_{be}, C_{bc})

high frequency

Impedance of a cap

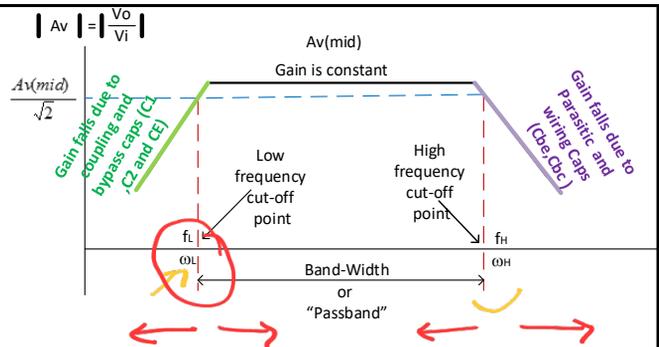

- The impedance of a cap is

$$X_c = \frac{1}{2\pi f C}$$

when $f < f_L$ the coupling caps C_1 and C_2 , and the bypass cap C_E cannot be considered as short circuit since their impedance is not small enough

when $f > f_H$ the internal caps C_{bc} and C_{be} for a BJT (or C_{gs} and C_{gd}), cannot be considered as open circuit since their impedance is not high enough

Corner Frequency

we define the corner (break and cut - off) frequency as :


$$|A(j\omega_L)| = \frac{Av(mid)}{\sqrt{2}}$$

$$|A(j\omega_H)| = \frac{Av(mid)}{\sqrt{2}}$$


$$\omega_H - \omega_L = BW - \text{Bandwidth}$$

$$\text{Midrange} = \text{midband} \cong 10\omega_L - 0.1\omega_H$$

definition

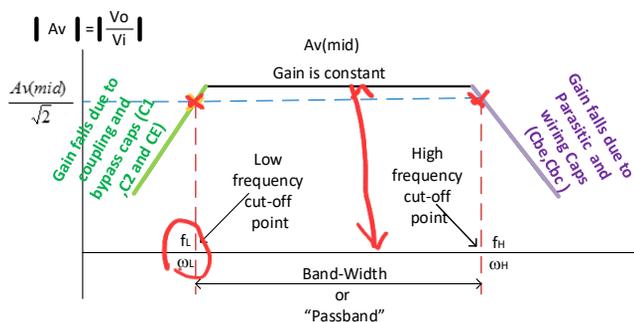

Corner Frequency

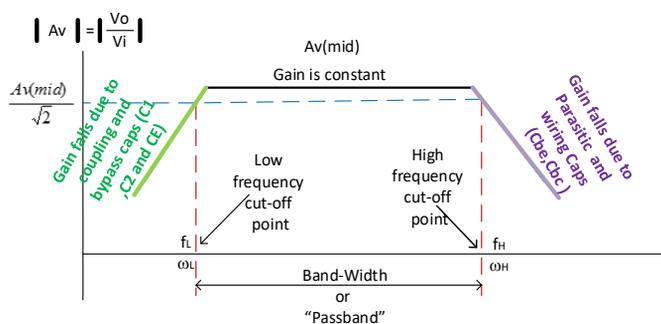

$$\text{Midrange} = \text{midband} \cong 10\omega_L - 0.1\omega_H$$


- This is the range for which the capacitors (C1, C2 and CE) are considered short circuit while the parasitic caps are considered open circuit (this is the range we have considered so far in previous chapters)

End of L26

L27 24-8-2021


x $\left\{ \begin{array}{l} f \rightarrow \omega = 2\pi f \\ \log f, \log \omega \leftarrow [\text{decade}] \end{array} \right.$

y $\left\{ \begin{array}{l} A_v(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} \\ |A(j\omega)| \\ 20 \log |A(j\omega)| \Rightarrow \text{in decibels [dB]} \end{array} \right.$

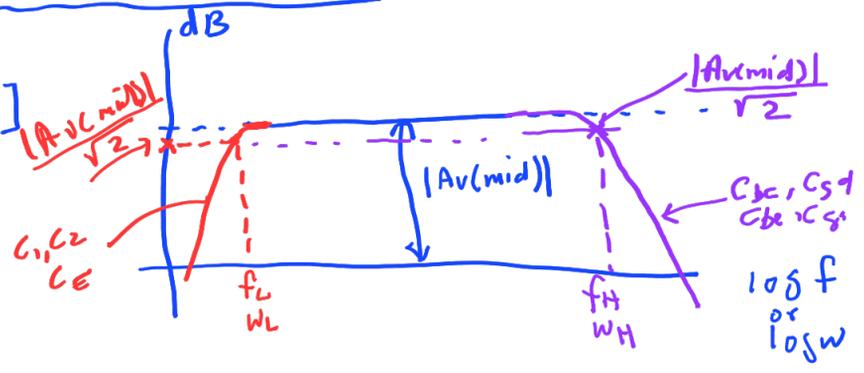

Series Capacitance and low frequency response

consider C1 only

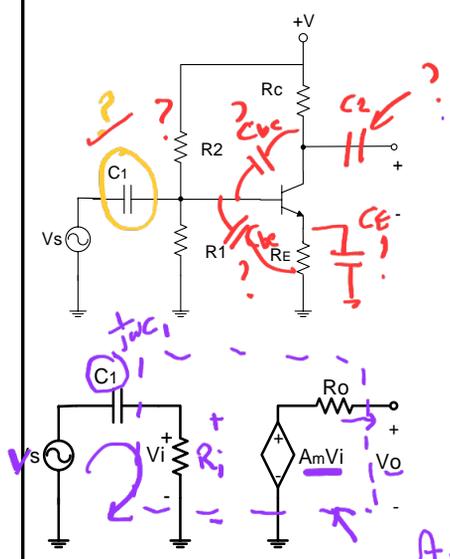

$$V_o = A_m V_i$$


$$V_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} V_s \rightarrow V_o = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}} V_s$$

$$\frac{V_o}{V_s} = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}} = A(j\omega)$$


$$\rightarrow |A(j\omega)| = \frac{A_m R_i}{\sqrt{(R_i)^2 + \left(\frac{1}{\omega C_1}\right)^2}}$$

$A_m = A_v(\text{mid})$

$\frac{V_o}{V_s} = ?$

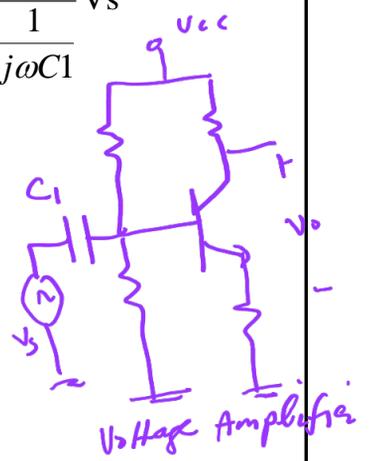

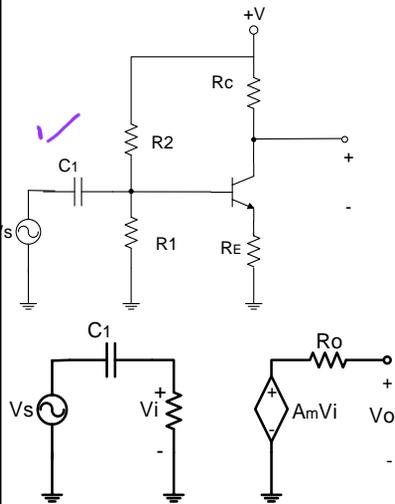Series Capacitance and low frequency response



$$|A(j\omega)| = \frac{A_m R_i}{\sqrt{(R_i)^2 + \left(\frac{1}{\omega C_1}\right)^2}}$$

$$= \frac{A_m}{\sqrt{1 + \left(\frac{\omega_{c1}}{\omega}\right)^2}}$$

where $\omega_{c1} = \frac{1}{R_i C_1}$ is the break frequency due to C1

For $A_m = 1$

for $\omega = \omega_{c1} \rightarrow 20 \log |A(j\omega)| = 20 \log A_m - 20 \log 0.707 = -3 \text{ dB}$

for $\omega = 0.1 \omega_{c1} \rightarrow 20 \log |A(j\omega)| = -20 \log 10 = -20 \text{ dB} \leftarrow \text{High pass filter}$

Handwritten notes:
 $A_m = 1$
 $\omega = 10 \omega_{c1}$ (marked with a checkmark)
 $= \frac{1}{\sqrt{1 + \left(\frac{1}{10}\right)^2}} = \frac{1}{\sqrt{1.01}} \approx 1 = \frac{V_o}{V_i}$
 $\omega = 0.1 \omega_{c1}$
 $= \frac{1}{\sqrt{1 + 10^2}} = \frac{1}{10} = \left(\frac{V_o}{V_i}\right)$
 HPF (High Pass Filter) graph showing a curve that rises from a low value at low frequencies to a high value at high frequencies.



Series Capacitance and low frequency response

$$C_1 \rightarrow \omega_{c1} \rightarrow \left(\frac{A_m}{1 + \frac{\omega_{c1}}{j\omega}} \right) = A(j\omega)$$

Note:

1) If there is only one cap, we find $\omega_{c1} = \frac{1}{R_{th1} \cdot C1}$ and $\omega_L = \omega_{c1}$

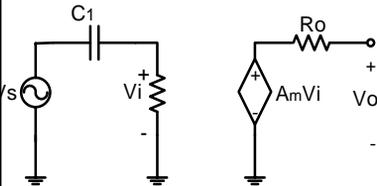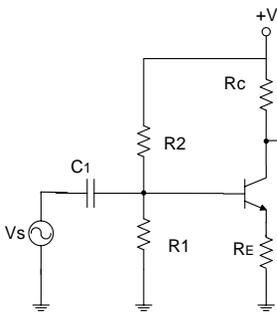
2) If there is two caps $C1$ and $C2$ with ω_{c1} and ω_{c2} then




$$A(j\omega) = A_m \left(\frac{1}{1 + \left(\frac{\omega_{c1}}{j\omega} \right)} \right) \left(\frac{1}{1 + \left(\frac{\omega_{c2}}{j\omega} \right)} \right)$$

ω_L ?

$$|A(j\omega_L)| = \frac{A_m}{\sqrt{2}}$$

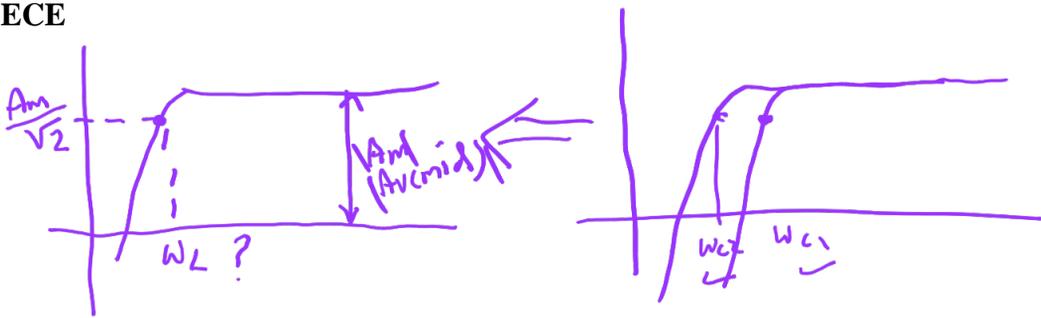

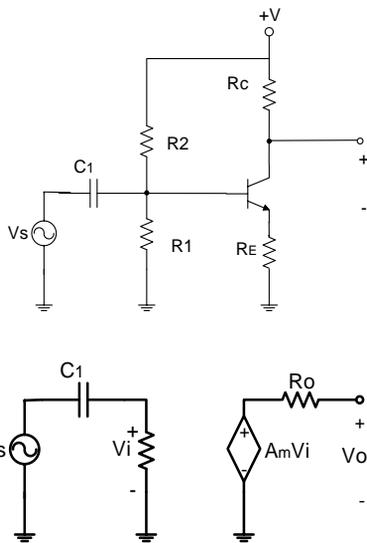Series Capacitance and low frequency response



in order to find ω_L , we find magnitude of the gain at ω_L

$$|A(j\omega_L)| = \frac{A_m}{\sqrt{2}} \rightarrow \omega_L ?$$

solving yields

$$\omega_L^2 = \frac{\omega_{C1}^2 + \omega_{C2}^2}{2} + \frac{\sqrt{\omega_{C1}^4 + 6\omega_{C1}^2\omega_{C2}^2 + \omega_{C2}^4}}{2}$$

Series Capacitance and low frequency response

1) let $\omega_{c1} = 616$ rad/sec and $\omega_{c2} = 17.86$ rad/sec

here $\omega_{c1} \gg \omega_{c2}$

$\omega_L = 616.5$ rad/sec

2) let $\omega_{c1} = 200$ rad/sec and $\omega_{c2} = 750$ rad/sec

here $\omega_{c2} \gg \omega_{c1}$

$\omega_L = 798$ rad/sec

$$\omega_L^2 = \frac{\omega_{c1}^2 + \omega_{c2}^2}{2} + \frac{\sqrt{\omega_{c1}^4 + 6\omega_{c1}^2\omega_{c2}^2 + \omega_{c2}^4}}{2}$$

In both cases and in general

if $\omega_{c1} \gg \omega_{c2}$



$$\omega_{c1} < \omega_L < \omega_{c1} + \omega_{c2}$$

Biggest $\omega_{c_i} < \omega_L < \text{sum of all } \omega_{c_i}'s$


$$\max(\omega_i) < \omega_L < \text{sum}(\omega_i) \quad ***$$

Low Frequency Response Example

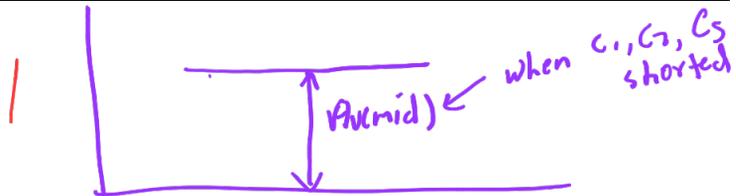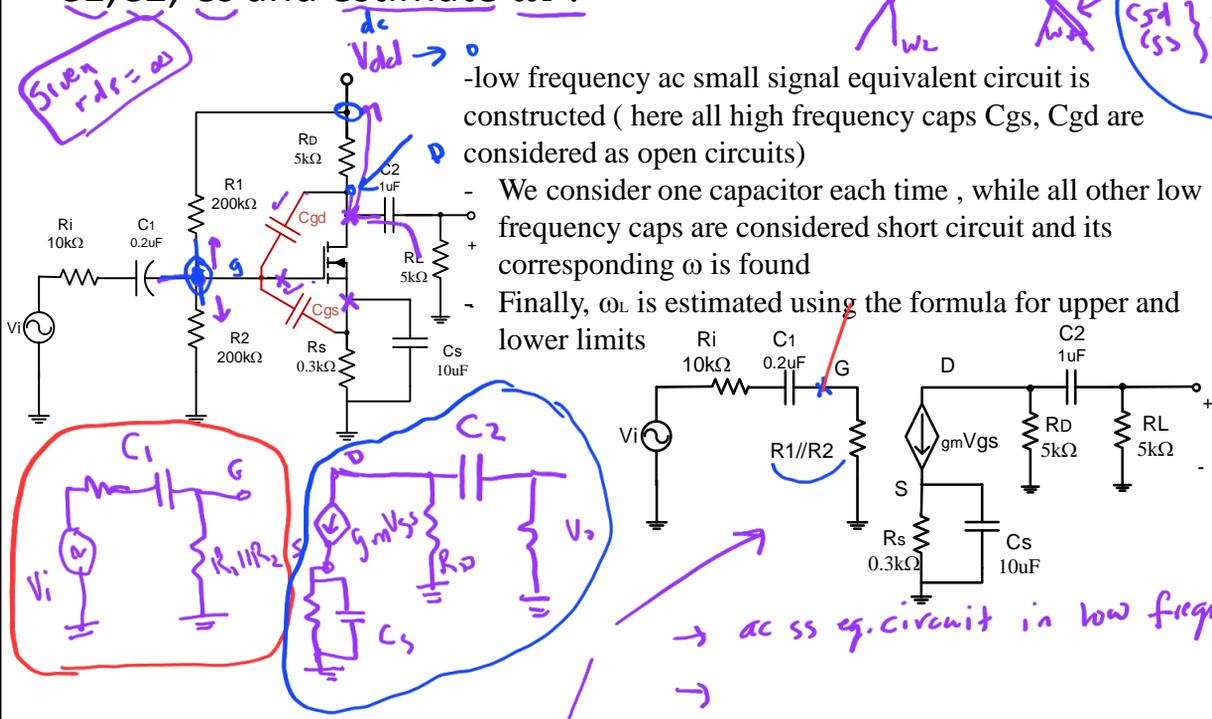- Calculate the low frequency corner frequencies due to C_1, C_2, C_s and estimate ω_L ?




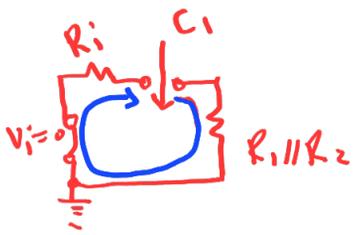Action plan: 1) take C_1 (while C_2 & C_3 shorted)
and find $\omega_{C1} = \frac{1}{C_1 R_{th1}}$



$R_{th1} \text{ seen by } C_1 = (R_1 || R_2) + R_i$

2) take C_2 (while C_1, C_3 shorted)

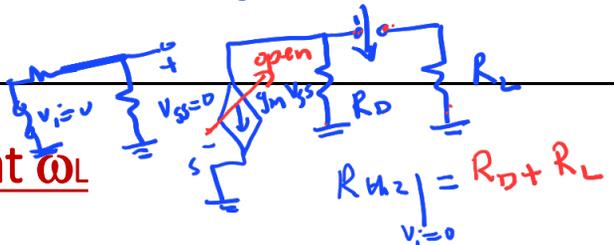

$R_{th2} = R_D + R_L$

Effect of each Capacitor at ω_L

- We Calculate the low frequency corner frequencies due to each cap acting alone while all others are considered as short circuit

1) consider C_1 (while C_2 and C_3 are shorted)

$\omega_{C1} = \frac{1}{C_1 R_{th1}} = 45.45 \text{ rad/sec}$

R_{th1} is the thevenin impedance seen by C_1 while all independant sources are set to zero


$R_{th1} = R_i + (R_1 || R_2)$

2) consider C_2 (while C_1 and C_3 are shorted)


$\omega_{C2} = \frac{1}{C_2 R_{th2}} = 100 \text{ rad/sec}$

R_{th1} is the thevenin impedance seen by C_1


$R_{th2} = R_D + R_L$

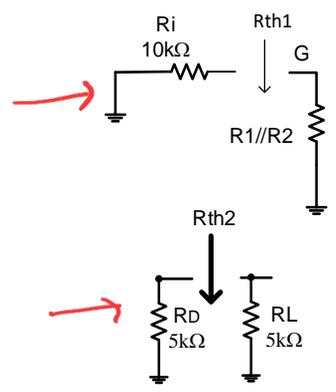


3) consider C_3 (while C_1, C_2 shorted)

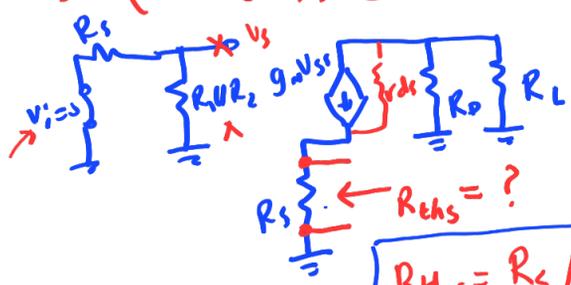

$R_{th3} = R_s || \frac{1}{g_m}$

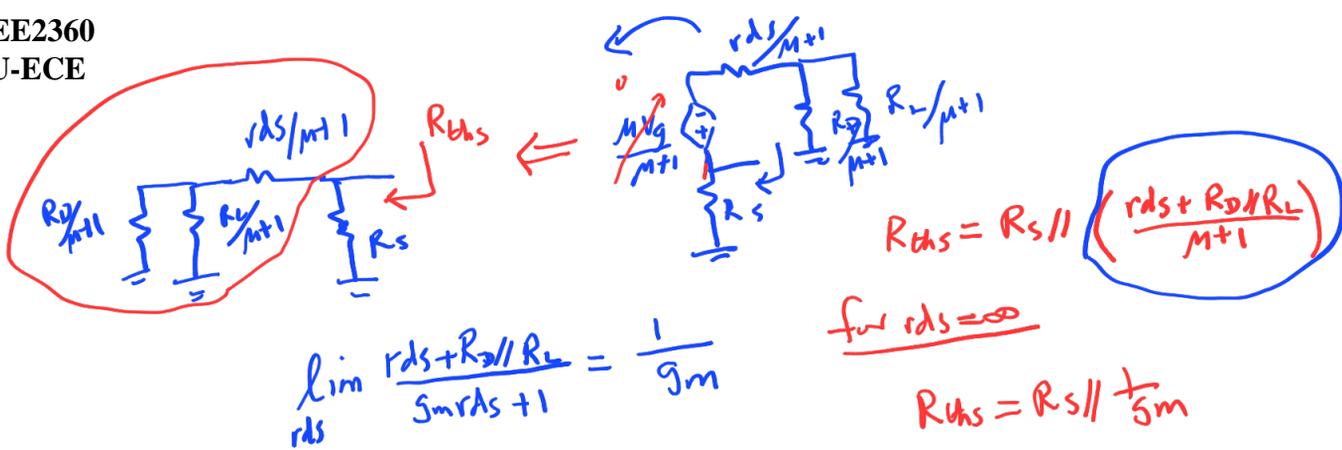

Effect of each Capacitor & ω_L

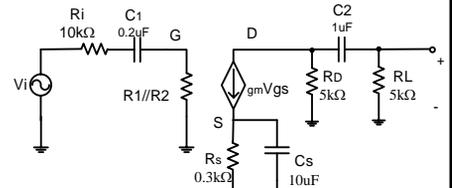

- We Calculate the low frequency corner frequencies due to cap acting alone while all others are considered as short circuit
- 3) consider C_s (while C_1 and C_2 are shorted)


$$\omega_{c3} = \frac{1}{C_s \cdot R_{th3}} = 1050 \text{ rad/sec};$$

R_{th3} is the thevenin impedance seen by C_s
remember $r_{ds} = \infty$

$$R_{th3} = R_S \parallel \frac{1}{g_m}$$

4) estimation of the ω_L

$$1050 < \omega_L < 1195.5$$

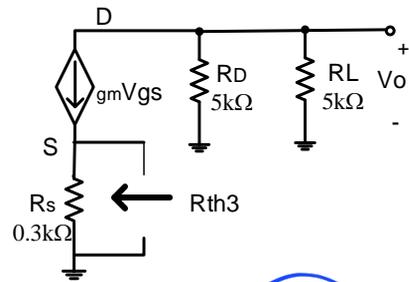

1050
100
45.4 ω_L 's



Given the following Amplifier, find the unknown Capacitors &/or resistors in order to have $\omega_L = 1000 \text{ rad/sec}$


? $\omega_L \leq \omega_{C1} + \omega_{C2} + \omega_{C3}$

Design Criteria

assume $\omega_{C3} = (0.7 - 0.8)\omega_L$

$\omega_{C1} = \omega_{C2} = (0.1 - 0.15)\omega_L$

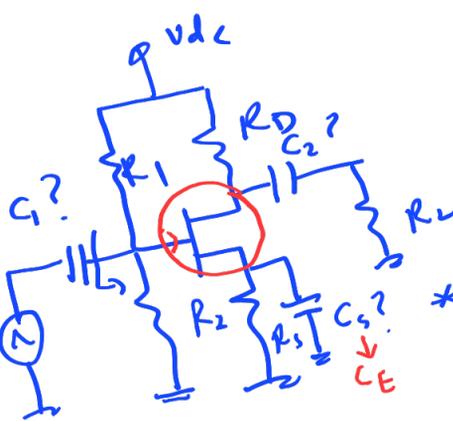always check $\omega_L = \omega_{C1} + \omega_{C2} + \omega_{C3}$



**** always ****
 $\omega_{C3} > \omega_{C1}$
 $\omega_{C3} > \omega_{C2}$

Design of ω_L

$\omega_{C3} = 700 \text{ rad/sec}, \omega_{C1} = \omega_{C2} = 150$
 $\omega_{C3} = \frac{1}{R_{th} C_3} = 700 \Rightarrow C_3 =$

- Previous method explained how to estimate value of ω_L in an analysis problem where all capacitor values are given, but what happens if it was desired to design an amplifier with certain ω_L and the task was to find capacitor values?
- Design criteria to be used is:

$\omega_{CE} = (0.7 - 0.8)\omega_L$

$\omega_{C1} = \omega_{C2} = (0.1 - 0.15)\omega_L$

C1, C2 are input and output coupling capacitors

C_E is bypass capacitor // to R_E emitter stabilizing resistor or R_s source resistor

make sure that $\omega_{CE} + \omega_{C1} + \omega_{C3} = \omega_L$

|

parallel
high frequency caps } FET | BJT } in }
Cgd | Cbc }
Cgs | Cbe }
10⁻¹² f

Shunt Capacitance and High frequency response


$$V_o = A_m V_i$$

$$V_i = \frac{R_i // \frac{1}{j\omega C_A}}{\left(R_i // \frac{1}{j\omega C_A}\right) + R_s} V_s \rightarrow \frac{V_o}{V_s} = A(j\omega)$$

$$A(j\omega) = A_m \frac{R_i // \frac{1}{j\omega C_A}}{\left(R_i // \frac{1}{j\omega C_A}\right) + R_s}$$

$$= A_m \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{1}{1 + j\omega C_A (R_s // R_i)} \right)$$

$$\rightarrow |A(j\omega)| = A_m \frac{R_i}{R_i + R_s} \cdot \frac{1}{\sqrt{1 + [\omega C_A (R_s // R_i)]^2}}$$

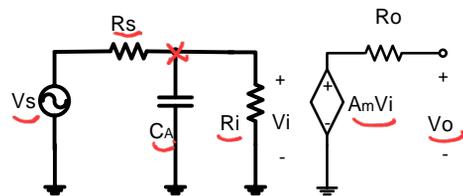

$$\rightarrow |A(j\omega)| = A_v(\text{mid}) \frac{1}{\sqrt{1 + [\omega C_A (R_s // R_i)]^2}}$$

$$\rightarrow |A(j\omega)| = A_v(\text{mid}) \frac{1}{\sqrt{1 + \left[\frac{\omega}{\omega_{CA}}\right]^2}} \leftarrow \text{LPF}$$


$$\rightarrow \text{at } \omega = \omega_H = \omega_{CA}$$

$$\therefore |A(j\omega_H)| = A_v(\text{mid}) \frac{1}{\sqrt{2}}$$

$$\rightarrow \omega_H C_A (R_s // R_i) = 1$$

End of L27

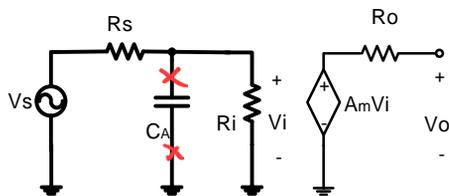
Shunt Capacitance and High frequency response



$$\rightarrow \omega_H C_A (R_s // R_i) = 1$$

$$\therefore \omega_H = \frac{1}{C_A (R_s // R_i)}$$

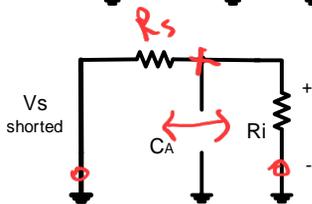
where R_{th_A} is thevenin impedance seen by capacitor C_A




For $A_v(\text{mid}) = 1$

for $\omega = \omega_{CA} \rightarrow 20 \log |A(j\omega)| = 20 \log A_v(\text{mid}) - 20 \log 0.707 = -3 \text{ dB}$

for $\omega = 10\omega_{CA} \rightarrow 20 \log |A(j\omega)| = -20 \log 10 = -20 \text{ dB} \leftarrow \text{low pass filter}$

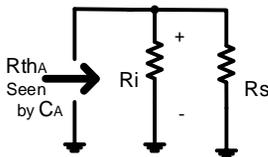

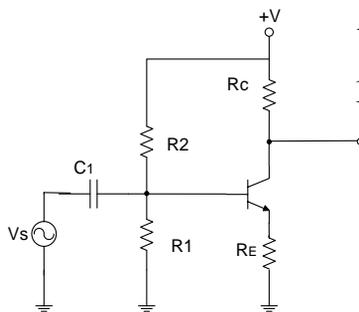Shunt Capacitance and High frequency response



Note :


1) If there is only one cap, we find $\omega_{CA} = \frac{1}{R_{thA} \cdot C1}$ and $\omega_H = \omega_{CA}$

2) If there is two caps C_A and C_B with ω_{CA} and ω_{CB} , then

$$A(j\omega) = Av(mid) \frac{1}{1 + \left(\frac{j\omega}{\omega_{CA}}\right)} \frac{1}{1 + \left(\frac{j\omega}{\omega_{CB}}\right)}$$

in order to find ω_H , we find magnitude of the gain at ω_H

$$|A(j\omega_H)| = \frac{Av(mid)}{\sqrt{2}} = \frac{Av(mid)}{\left[\left(1 + \left(\frac{j\omega}{\omega_{CA}}\right)\right) \left(1 + \left(\frac{j\omega}{\omega_{CB}}\right)\right) \right]}$$

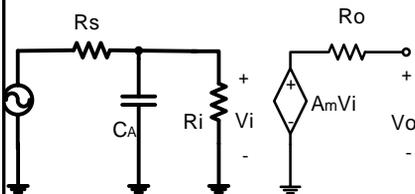

Shunt Capacitance and High frequency response

By solving for the magnitude of the gain $A(j\omega)$ at $\omega = \omega_H$ yields for an approximation for the lower and upper limit to estimate ω_H for $\omega_{CA} \gg \omega_{CB}$

$$\longrightarrow \frac{1}{\frac{1}{\omega_{CA}} + \frac{1}{\omega_{CB}}} < \omega_H < \omega_{CB}$$

$$\frac{\omega_{CA} \cdot \omega_{CB}}{\omega_{CA} + \omega_{CB}} < \omega_H < \omega_{CB}$$



lower limit $< \omega_H < \text{Smallest } \omega$

High Frequency Response Example

- Calculate the high frequency corner frequencies due to C_{gs} , C_{gd} and estimate ω_H ?

-High frequency ac small signal equivalent circuit is constructed (here all low frequency caps C_1 , C_2 and C_3 are considered as short circuits)

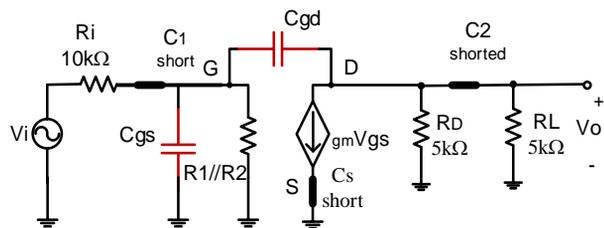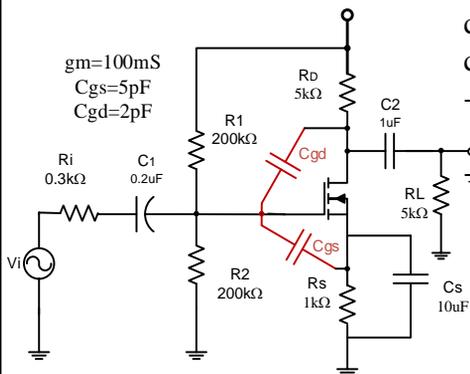- We consider one capacitor each time , while all others are considered open circuit and its corresponding ω is found Finally, ω_H is estimated using the formula for upper and lower limits



Effect of each Capacitor & ω_H

- We Calculate the high frequency corner frequencies due to each high frequency cap acting alone while all others are considered as open circuit


1) Consider C_{gs} (while C_{gs} is open , C_1, C_2 & C_s are shorted)

$$\omega_{C_{gs}} = \frac{1}{C_{gs} \cdot R_{gs}}$$

R_{gs} is the thevenin impedance seen by C_{gs}

$$R_{gs} = R_1 // R_2 // R_i$$

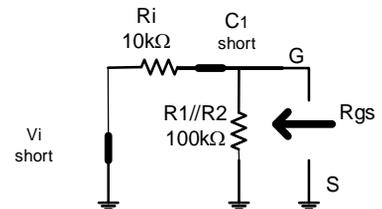
$$\omega_{C_{gs}} = 668.45 \text{ Mrad/sec;}$$



Effect of each Capacitor & ω_H


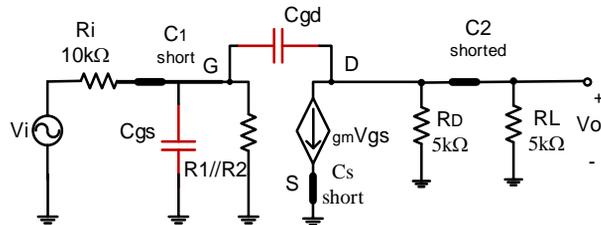
2) Consider C_{gd} (while C_{gs} is open , C_1, C_2 & C_s are shorted)

$$\omega_{C_{gd}} = \frac{1}{C_{gd} \cdot R_{gd}}$$



Effect of Capacitor Cgd

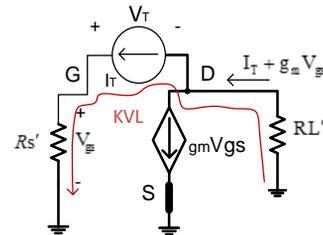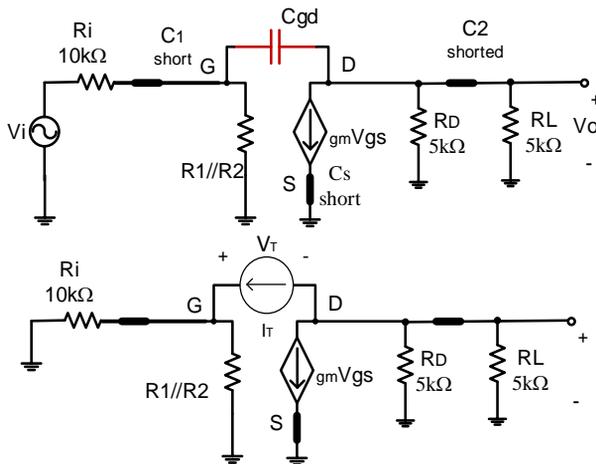- Calculation of Rgd is done through test current /voltage method



KVL :

$$RL'(I_T + g_m V_{gs}) + I_T R_{s'} = V_T$$

$$\text{but } V_{gs} = V_g - V_s = R_{s'} I_T$$

substituting yeilds

$$RL'(I_T + g_m R_{s'} I_T) + I_T R_{s'} = V_T$$

$$R_{gd} = \frac{V_T}{I_T} = RL' + R_{s'} + g_m RL' R_{s'}$$

$$RL' = R_D // R_L \quad \text{and} \quad R_{s'} = R_i // R_1 // R_2$$

Effect of each Capacitor & ω_H

Now

$$\omega_{Cgd} = \frac{1}{Cgd.Rgd} = 48.54 \text{ Mrad/sec;}$$





3) Estimation of the ω_H

$$\frac{(\omega_{gd} \bullet \omega_{gs})}{(\omega_{gd} + \omega_{gs})} < \omega_H < 48.45$$

$$45.25 < \omega_H < 48.45$$

Effect of each Capacitor & ω_H

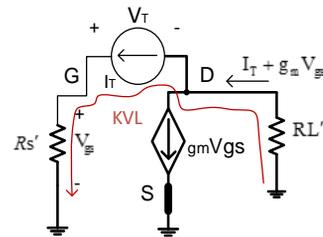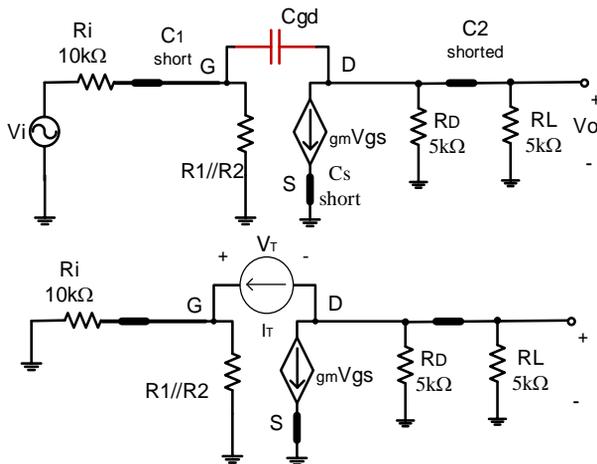- Calculation of R_{gd} is done through
- test current /voltage method



$$\text{KVL : } RL'(I_T + g_m V_{gs}) + I_T R_{s'} = V_T$$

$$\text{but } V_{gs} = V_g - V_s = R_{s'} I_T$$

substituting yeilds


$$RL'(I_T + g_m R_{s'} I_T) + I_T R_{s'} = V_T$$

$$R_{gd} = \frac{V_T}{I_T} = RL' + R_{s'} + g_m RL' R_{s'}$$


$$RL' = R_D // R_L \quad \text{and} \quad R_{s'} = R_i // R_1 // R_2$$

BJT High Frequency Response

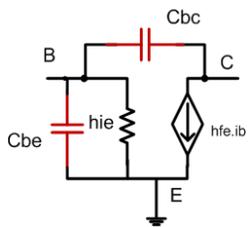
- Capacitors Cbe and Cbc
- CE and CC model



Convert to
a form
similar to
FET

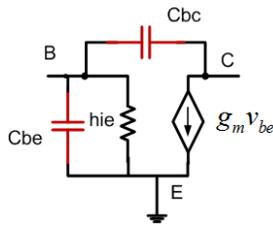

CB model

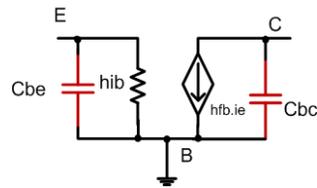

$h_{fb} = \alpha = -1$

$$h_{fe} \cdot i_b = h_{fe} \frac{v_{be}}{h_{ie}} = g_m v_{be};$$

where

$$\frac{h_{fe}}{h_{ie}} = g_m$$

CE Example:


- Estimate the high corner frequency for the following BJT amplifier

1) Effect of C_{be} (C_{bc} is considered open) High Frequency Small Signal equivalent Circuit

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{be}};$$

where R_{be} is the thevenin impedance seen by C_{be}
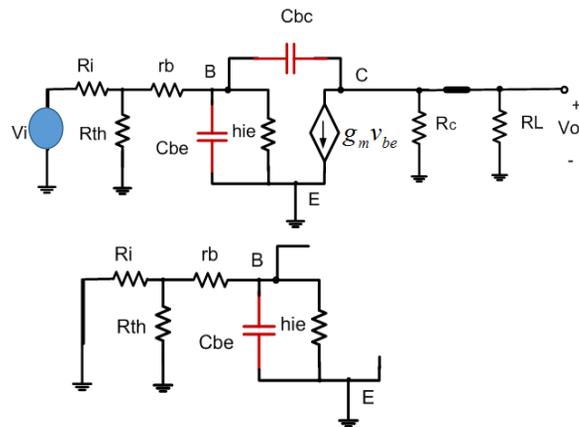
$$R_{be} = ((R_i // R_{th}) + r_b) // h_{ie}$$





CE Example:

2) Effect of C_{bc} (C_{be} is considered open)

$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}};$$

where R_{bc} is the thevenin

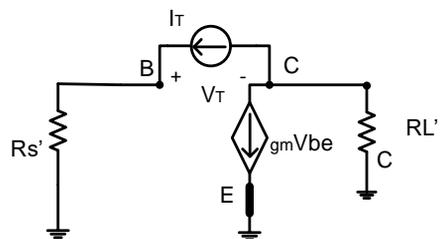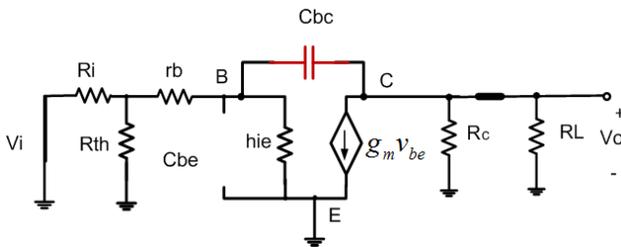impedance seen by C_{bc} and it is found by V_T/I_T method



$$RL'(I_T + g_m V_{be}) + I_T R_s' = V_T$$

$$\text{but } V_{be} = V_b - V_e = R_s' I_T$$

substituting yields

$$RL'(I_T + g_m R_s' I_T) + I_T R_s' = V_T$$

$$R_{bc} = \frac{V_T}{I_T} = RL' + R_s' + g_m RL' R_s'$$

$$R_s' = (R_i / R_{th} + r_b) // h_{ie}$$

CE Example:

- Given the following values in previous example

$$g_m = 33.5 \text{ mS}$$

$$h_{ie} = 8.77 \text{ k}\Omega$$

$$h_{fe} = 294$$

$$R_s = 1 \text{ k}\Omega, R_1 // R_2 = 16.67 \text{ k}\Omega$$

$$r_b = 20 \Omega; C_{bc} = 1.8 \text{ pF}; C_{be} = 17.25 \text{ pF}$$

$$R_c = 5 \text{ k}\Omega; R_L = 2 \text{ k}\Omega$$

calculate :

$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}} = 66.7 \text{ Mrad/sec}$$

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{bc}} = 12.67 \text{ Mrad/sec}$$

Estimate ω_H

$$\frac{(\omega_{be} \cdot \omega_{bc})}{(\omega_{be} + \omega_{bc})} < \omega_H < \omega_{be}$$

$$10.65 < \omega_H < 12.67$$

CB Example :

- Estimate the high corner frequency ω_H for the following BJT amplifier

1) Effect of C_{be} (C_{bc} is considered open)

$$\omega_{be} = \frac{1}{C_{be} \cdot R_{be}}; \text{ where } R_{be} \text{ is the thevenin}$$


impedance seen by C_{be}

$$R_{be} = ((R_s // R_E)) // h_{ib}$$

2) Effect of C_{bc}


$$\omega_{bc} = \frac{1}{C_{bc} \cdot R_{bc}};$$

$$\text{where } R_{bc} = R_L // R_C$$

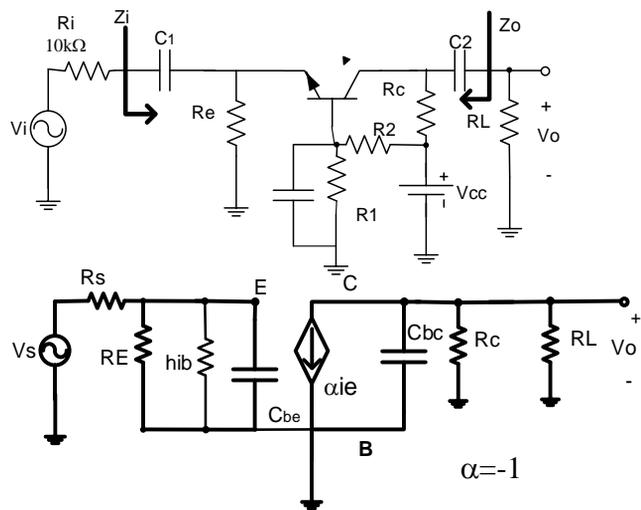



Practice Question : Amplifier Frequency Response

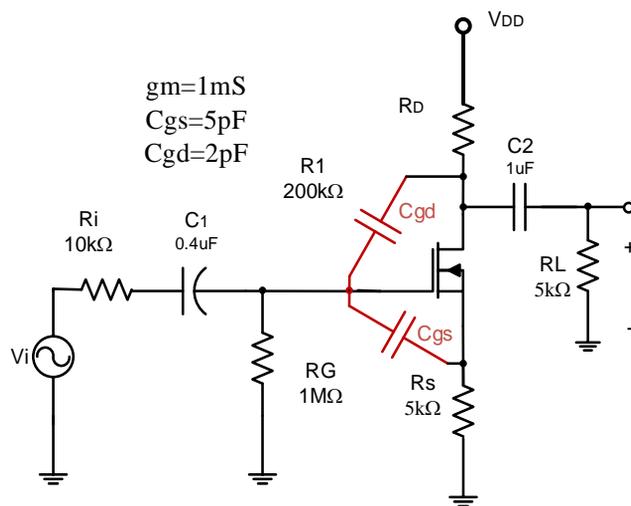- Estimate the value of **low** and **high** frequency corner frequencies and calculate the mid-range voltage gain of the following amplifier



Miller Theorem (another method to solve previous example)

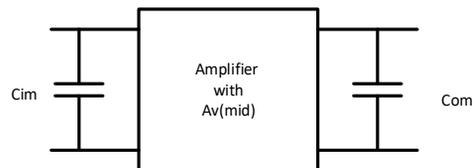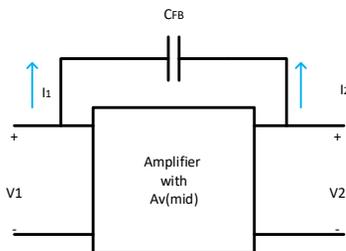- Miller theorem is used to simplify the analysis of inverting amplifiers only at high frequencies
- The feedback capacitor C_{bc} or C_{gd} is decomposed into two capacitors, one at the input C_{im} and one at the output C_{om} , whose values are found using the following formulas:



Input Miller Capacitance

$$C_{IM} = C_{FB} \left[1 - A_v(mid) \right]$$

Output Miller Capacitance

$$C_{OM} = C_{FB} \left[1 - \frac{1}{A_v(mid)} \right]$$

CE Example using Miller Theorem:

- Estimate the high corner frequency for the following BJT amplifier using miller theorem

- Calculate $A_v(\text{mid}) = \frac{V_y}{V_x}$

- Calculate $C_{IM} = C_{FB} [1 - A_v(\text{mid})]$;

$C_{FB} = C_{BC}$

- Calculate $C_{OM} = C_{FB} \left[1 - \frac{1}{A_v(\text{mid})} \right]$

- Calculate $\omega_{IM} = \frac{1}{(C_{IM} + C_{be})R_{be}}$

- Calculate $\omega_{OM} = \frac{1}{C_{OM}R_{ce}}$

- Estimate ω_L

