




DEPARTMENT OF COMPUTER SYSTEM ENGINEERING

Digital Integrated Circuits - ENCS333

Dr. Khader Mohammad
Lecture #13 Adders

Integrated-Circuit Devices and Modeling

A Generic Digital Processor

 

Building Blocks for Digital Architectures

Arithmetic unit

- Bit-sliced datapath (adder, multiplier, shifter, comparator, etc.)

Memory

- RAM, ROM, Buffers, Shift registers


Control

- Finite state machine (PLA, random logic.)
- Counters

Interconnect


- Switches
- Arbiters
- Bus

Bit-Sliced Design

 


Tile identical processing elements

Full-Adder

 

A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

The Binary Adder

 

$$S = A \oplus B \oplus C_i$$

$$= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i$$

$$C_o = AB + BC_i + AC_i$$

Express Sum and Carry as a function of P, G, D

Define 3 new variable which ONLY depend on A, B

$$\text{Generate (G)} = AB$$

$$\text{Propagate (P)} = A \oplus B$$


$$\text{Delete} = \bar{A} \bar{B}$$

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and C_o based on D and P

The Ripple-Carry Adder

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N - 1)t_{\text{carry}} + t_{\text{sum}}$$


Goal: Make the fastest possible carry path circuit

Complimentary Static CMOS Full Adder

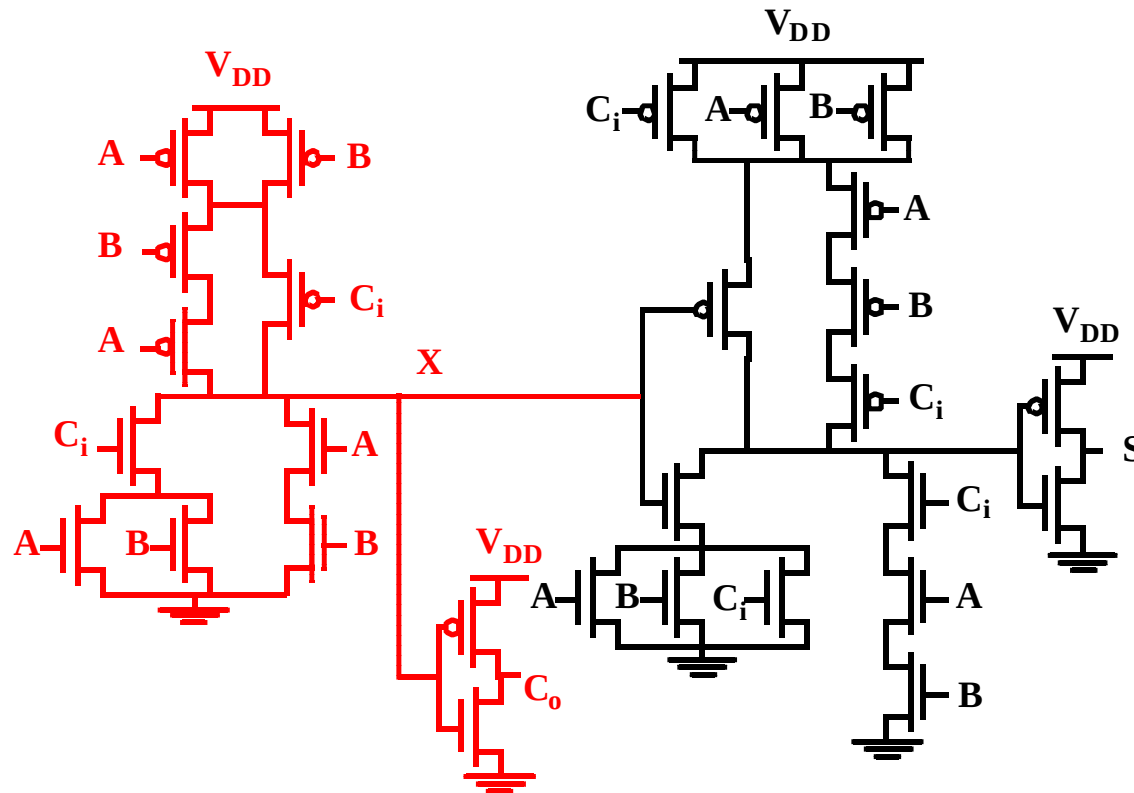

28 Transistors


Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

 
Minimize Critical Path by Reducing Inverting Stages



Exploit Inversion Property


Note: need 2 different types of cells

The better structure: the Mirror Adder

 


24 transistors


NP-CMOS Adder

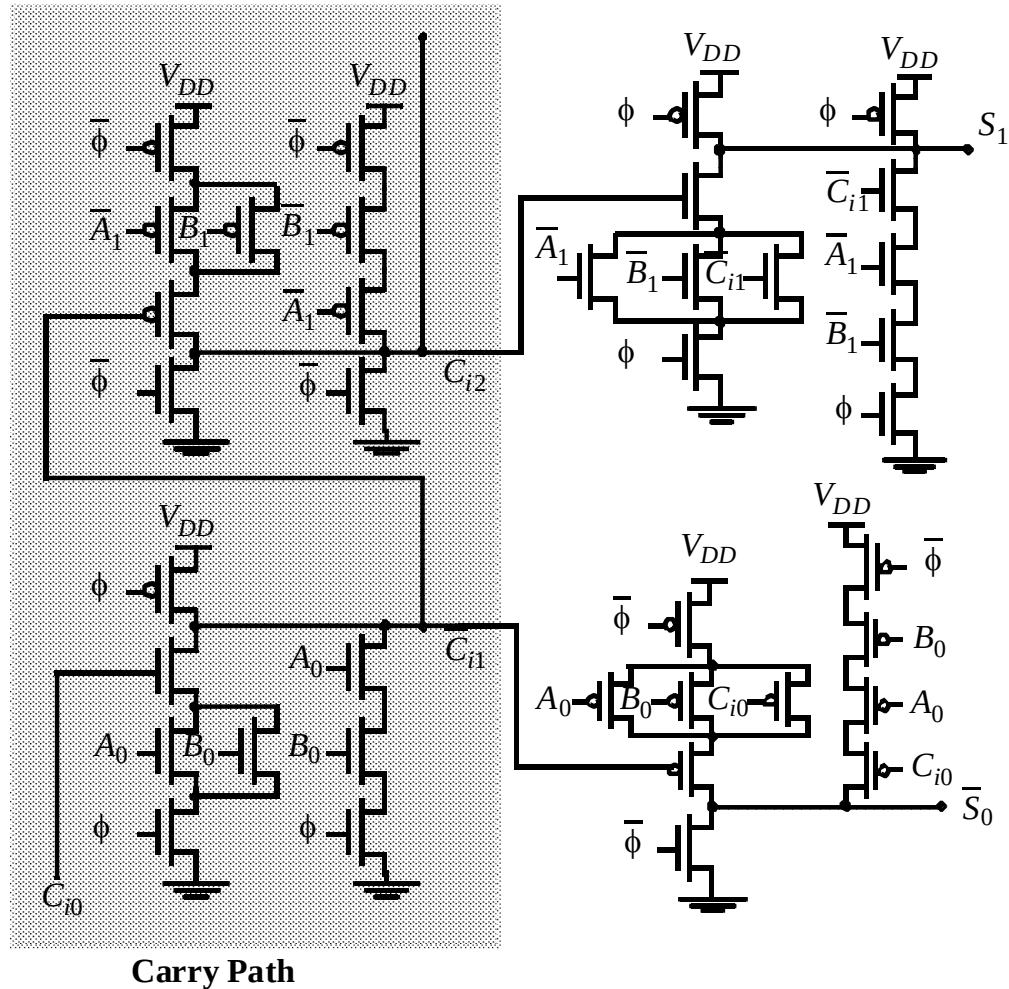


NP-CMOS Adder

 

Example: Domino Adder

 

Propagate

 

Generate

The Binary Multiplication

$$\begin{aligned} Z &= \ddot{X} \times Y = \sum_{k=0}^{M+N-1} Z_k 2^k \\ &= \left(\sum_{i=0}^{M-1} X_i 2^i \right) \left(\sum_{j=0}^{N-1} Y_j 2^j \right) \\ &= \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right) \end{aligned}$$

with

$$\begin{aligned} X &= \sum_{i=0}^{M-1} X_i 2^i \\ Y &= \sum_{j=0}^{N-1} Y_j 2^j \end{aligned}$$

The Binary Multiplication


$$\begin{array}{r} 101010 \\ \times 1011 \\ \hline 101010 \\ 101010 \\ 000000 \\ + 101010 \\ \hline 11100110 \end{array}$$

AND operation


Partial Products

The diagram illustrates the binary multiplication process. It shows the multiplication of 101010 by 1011. A horizontal line separates the multiplicand (101010) from the partial products. The partial products are shown as 101010, 101010, 000000, and 101010, which are then summed to produce the final product 11100110. An arrow points from the text 'AND operation' to the first partial product, and another arrow points from the text 'Partial Products' to the second partial product.

The Array Multiplier

 


The MxN Array Multiplier — Critical Path

 

$$t_{mult} \approx [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$




Carry-Save Multiplier

 

Vector Merging Adder


$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

Adder Cells in Array Multiplier

   


Identical Delays for Carry and Sum


Multiplier Floorplan

 

The Binary Shifter

 


Layout Strategies for Bit-Sliced Datapaths

 

Approach I —

Signal and power lines parallel

 

Approach II —

Signal and power lines perpendicular