

Diode large signal application

Example

- Find the Q point



Using thevenin's theorem , the circuit is simplified to

$$R_{th} = 10k + 10k \parallel 20k = 16.7k$$


$$V_{th} = \frac{20k}{20k+10k} * 6 = 4V$$

since $V_{th} \geq V_k$, the diode is on

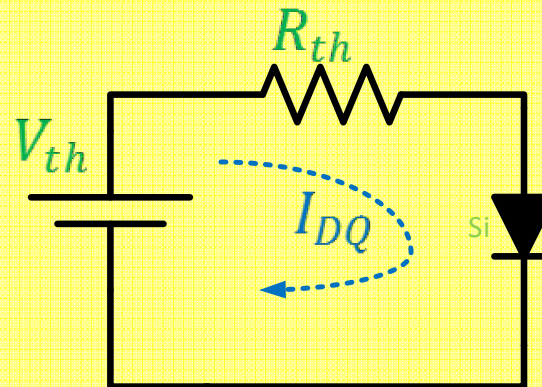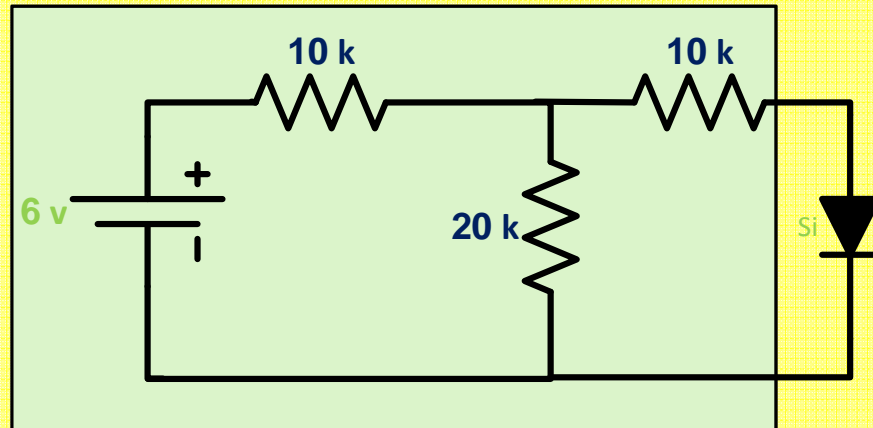since $V_{th} < 10 V_k$, we must use the knee voltage model



Knee voltage model

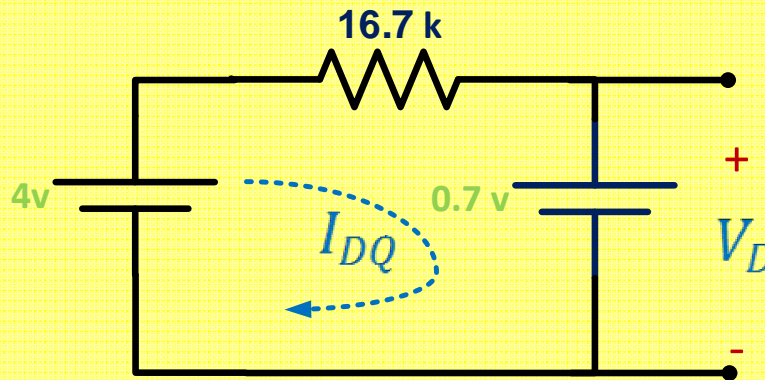


$$I_{DQ} = \frac{4 - 0.7}{16.7K} = 0.198 \text{ mA}$$

$$V_{DQ} = V_K = 0.7 \text{ V}$$

Second method

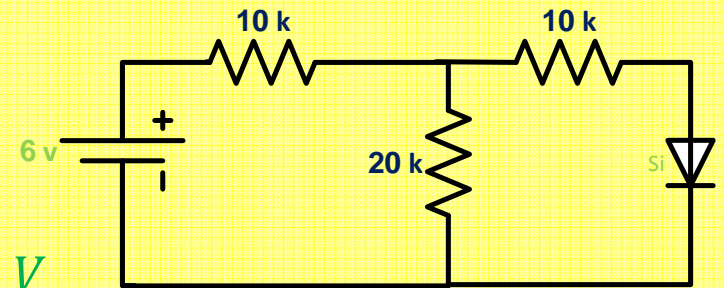assume the diode is on , replace it with $V_K = 0.7 V$



KVL:

$$6 = 30 I_1 - 20 I_2$$


$$-0.7 = -20 I_1 + 30 I_2$$

Solve for:

$$I_2 = 0.198 \text{ mA}$$

$$\therefore I_D = I_2 = 0.198 \text{ mA}$$

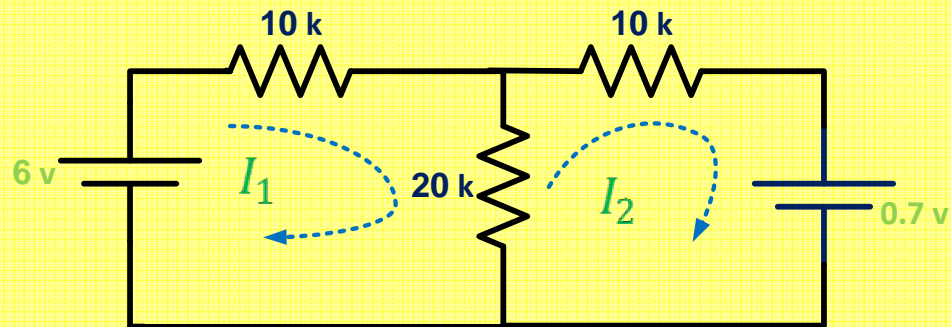
Since $I_D > 0$, \therefore our assumption is ok




Diode large - signal application

1) Diode clipper circuit

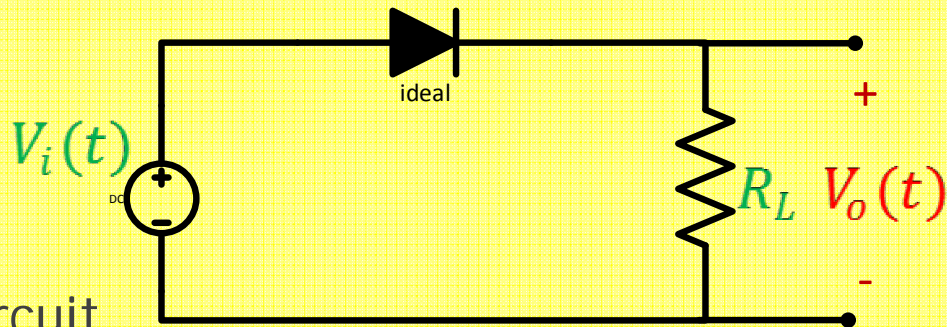a) assume the diode is on
replace it with short circuit



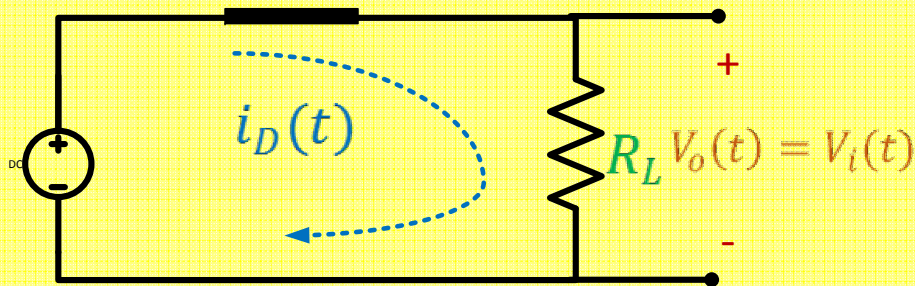
$$i_D(t) > 0$$
$$i_D(t) = \frac{V_i(t)}{R_L} > 0$$
$$\therefore V_i(t) > 0$$



\therefore when $V_i(t) > 0$, the diode is on and
 $V_o(t) = V_i(t)$

\therefore when $V_i(t) < 0$, the diode is off and $V_o(t) = 0$.

$$V_o(t) = 0.$$

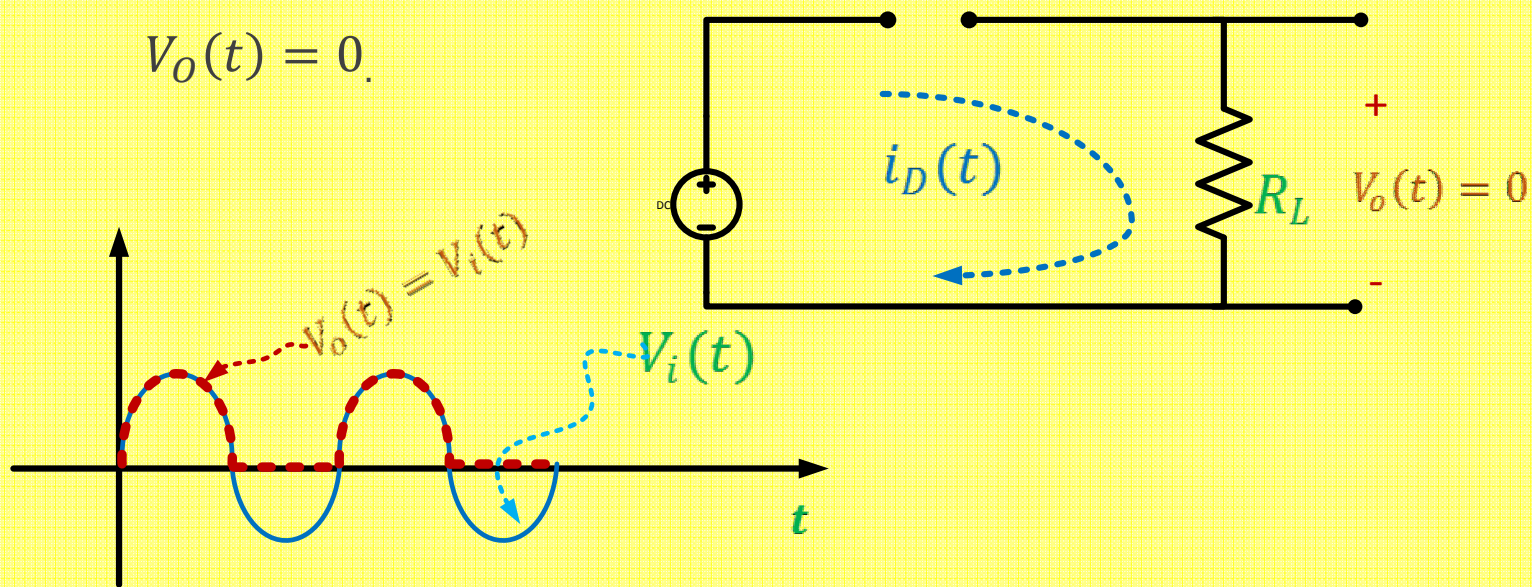


\therefore the clipper circuit used to eliminate portion of the input signal .





Example

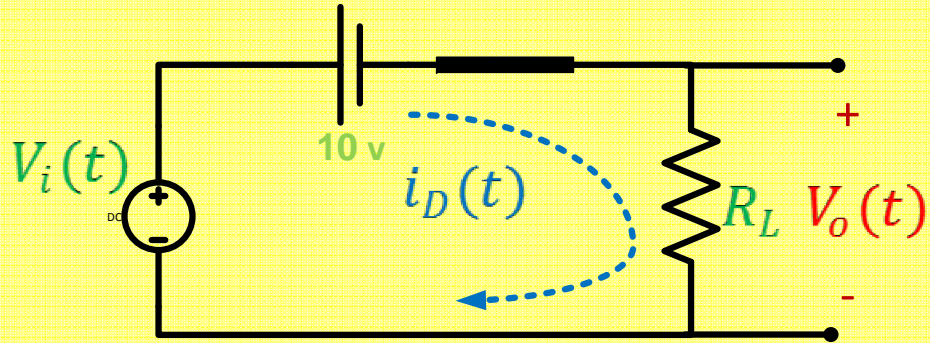- a) assume that the diode is on
- b) replace it with short circuit
- c) $i_D(t) > 0$



$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$

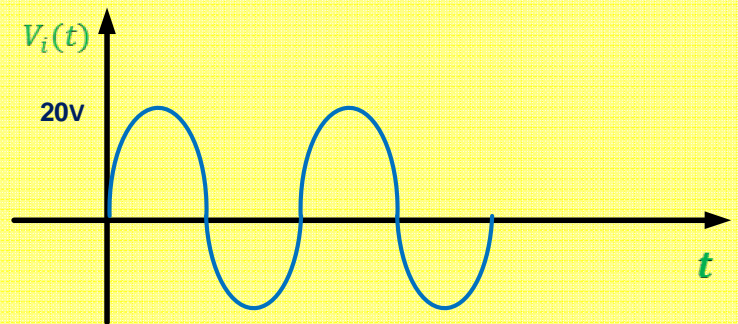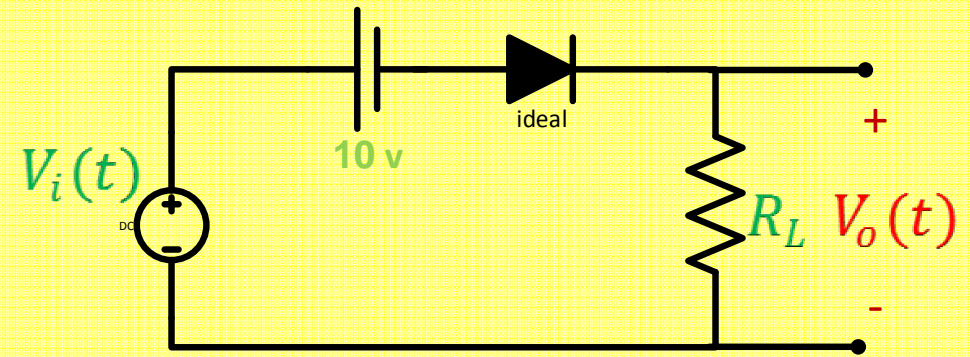

$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$


$$\therefore V_i(t) - 10 > 0$$

$$\therefore V_i(t) > 10$$


\therefore when $V_i(t) > 10 \text{ V}$, the diode is on and

$$V_o(t) = V_i - 10$$


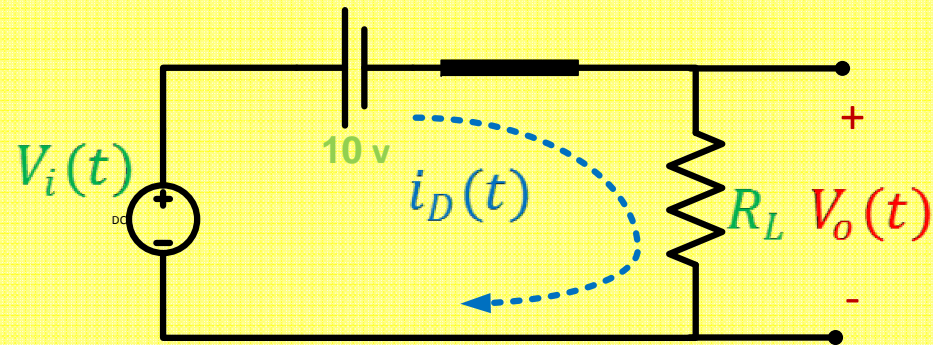
and also we can prove that when $V_i(t) < 10 \text{ V}$, the diode is off



$$\therefore V_o(t) = 0$$

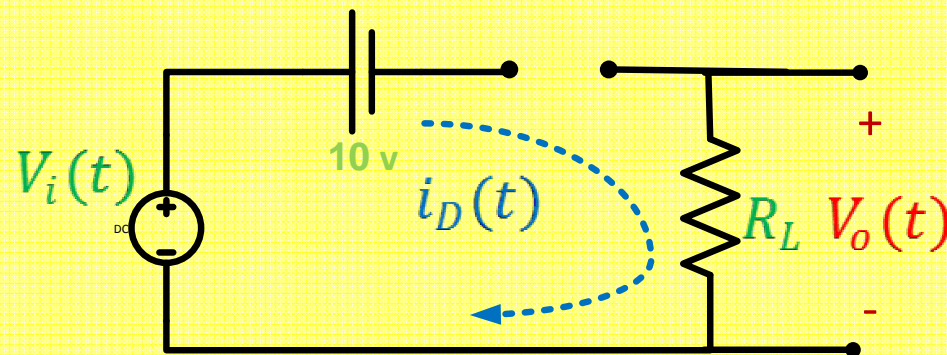

The output

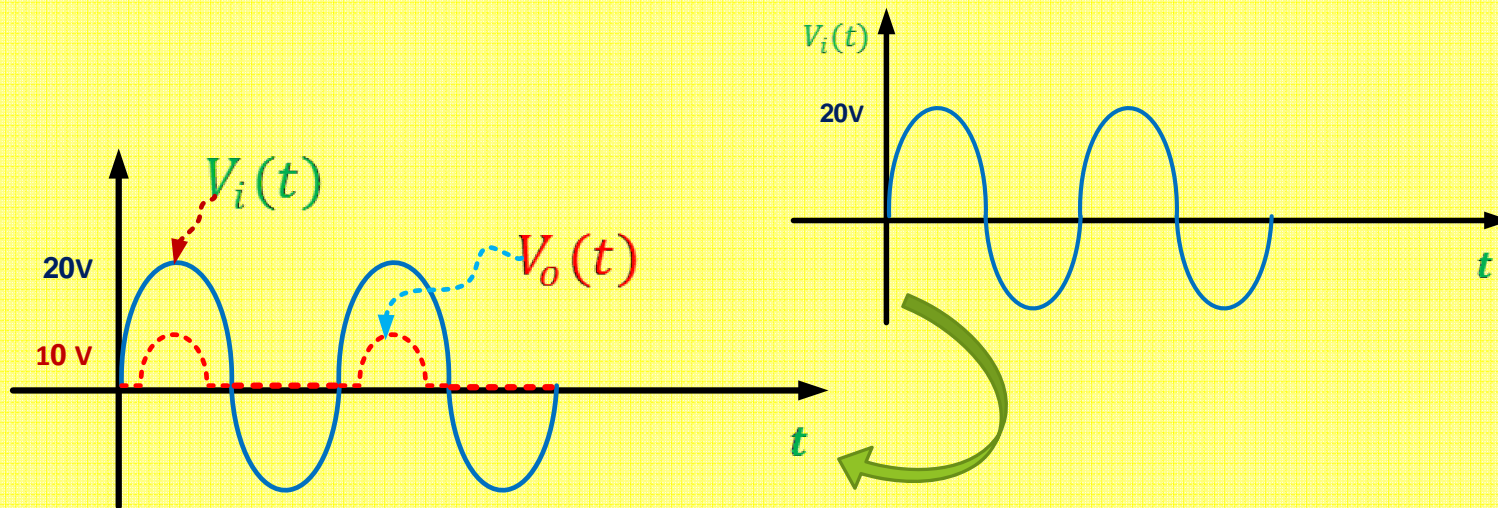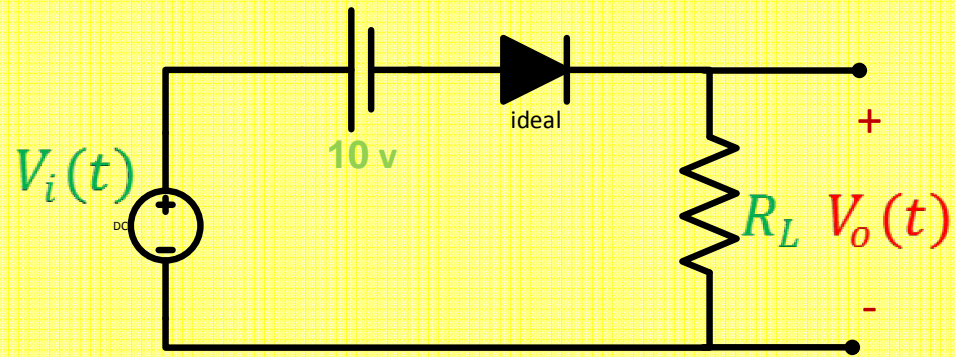


Second method

a) assume that the diode is off , b) replace it with open circuit , c) $V_D(t) < 0$.

$$V_D(t) < 0$$

$$V_D(t) = -10 + V_i$$

$$V_i(t) < 10 \text{ V}$$

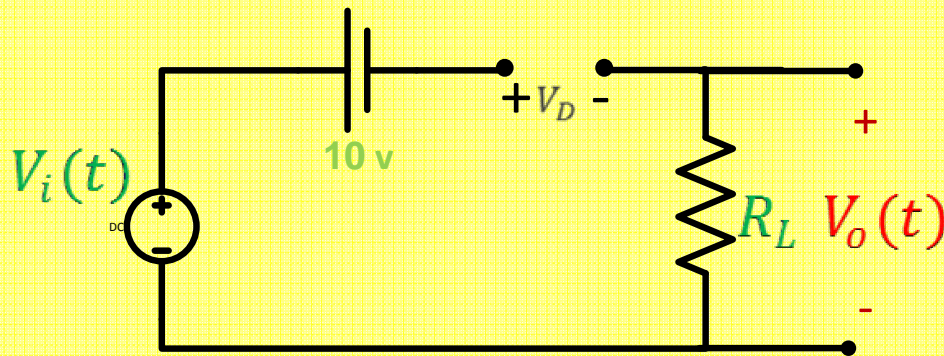

\therefore when $V_i(t) < 10 \text{ V}$, the diode is off and $V_o(t) = 0$