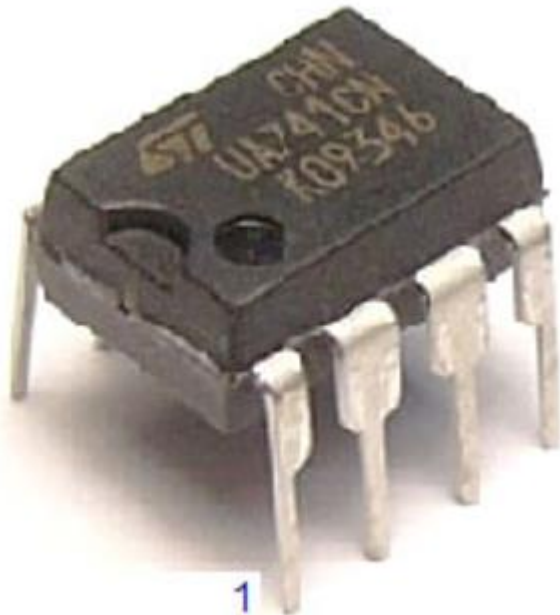


Operational Amplifiers




The Operational Amplifier

Designed to do mathematical operations such as addition , subtraction



Very high voltage gain ; 200,000

Very High input impedance ; 10M ohm


Very small output impedance ; 75ohm

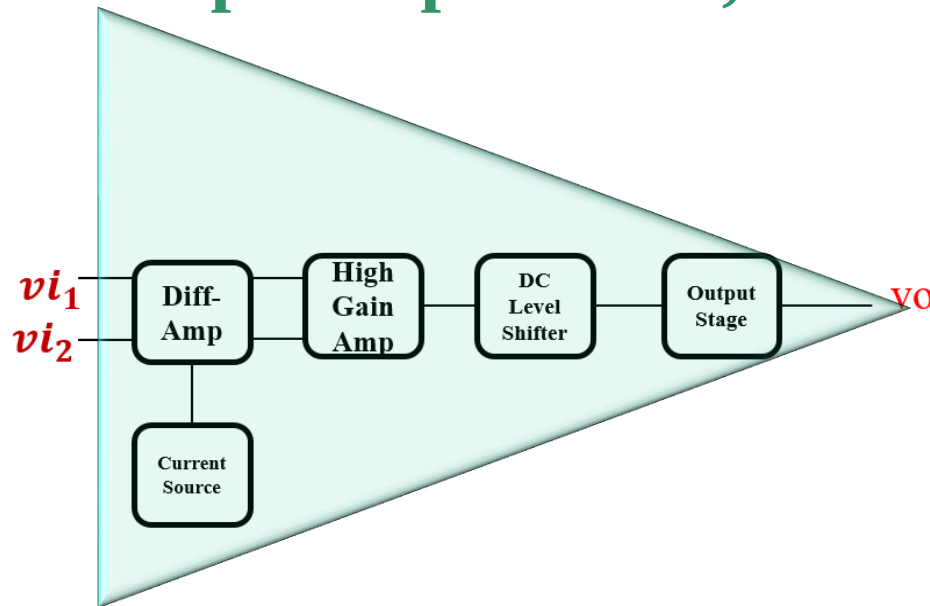

Operational Amplifiers

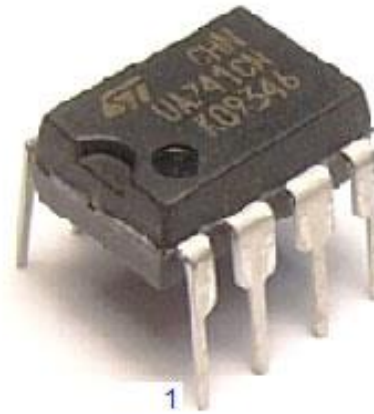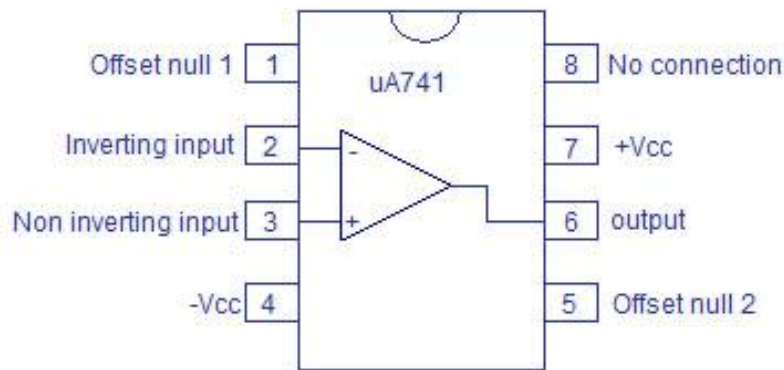

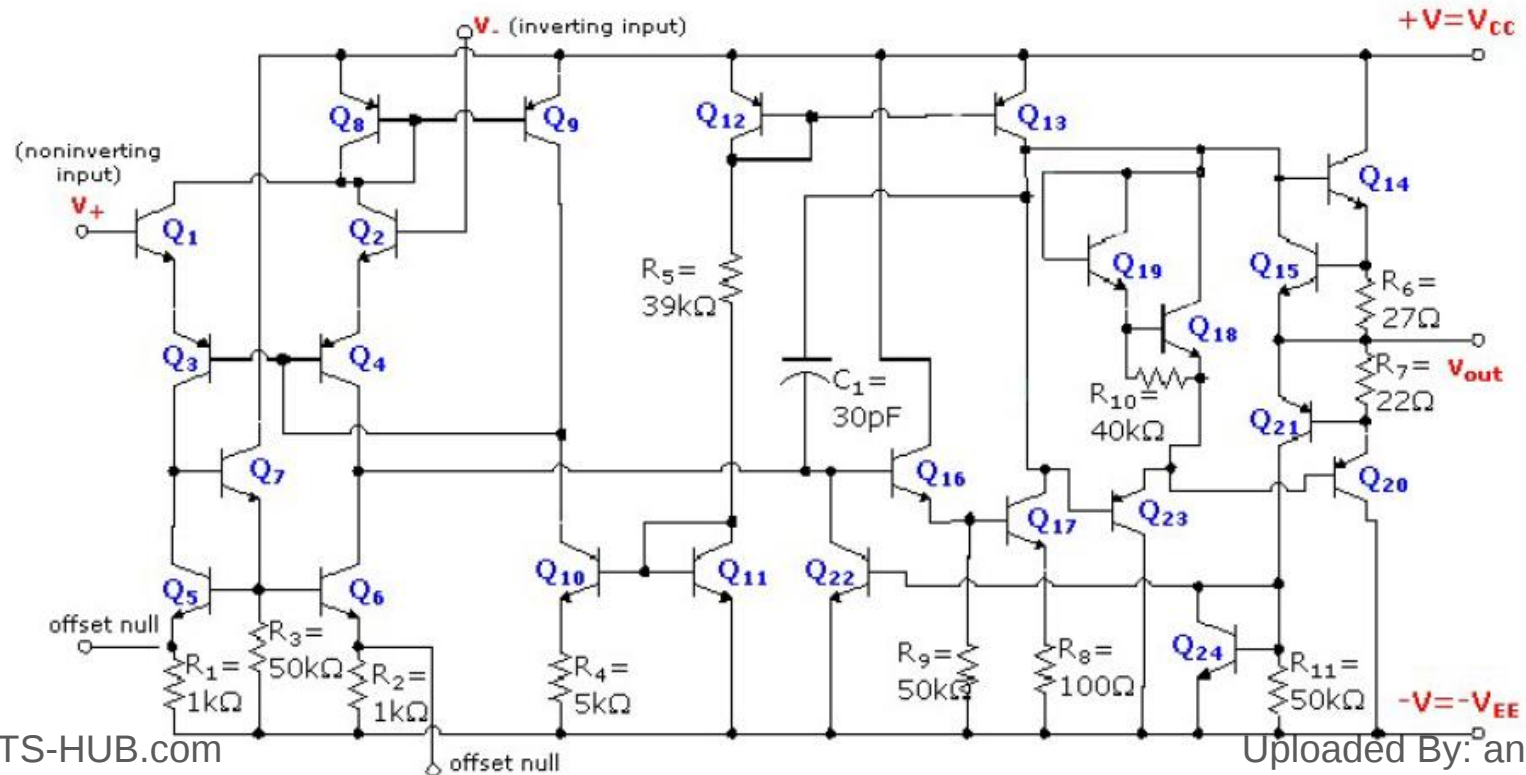
uA741 opamp Pinout and External appearance




Operational Amplifier



Transfer characteristic Curve:
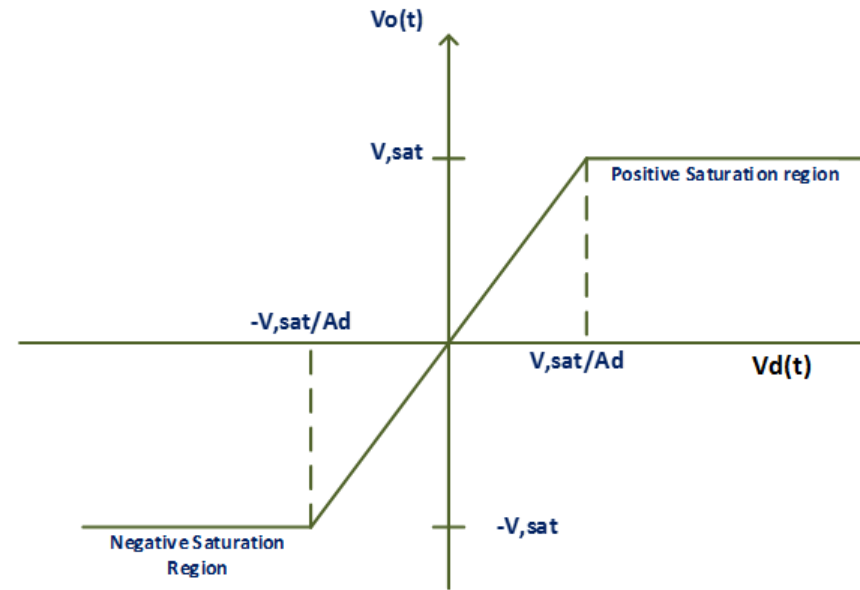
$$V_o = \begin{cases} +V_{sat} & vd > \frac{V_{sat}}{A_d} \\ A_d vd & \frac{V_{sat}}{A_d} > vd > -\frac{V_{sat}}{A_d} \\ -V_{sat} & vd < -\frac{V_{sat}}{A_d} \end{cases}$$



$$vd = V(+)-V(-)$$

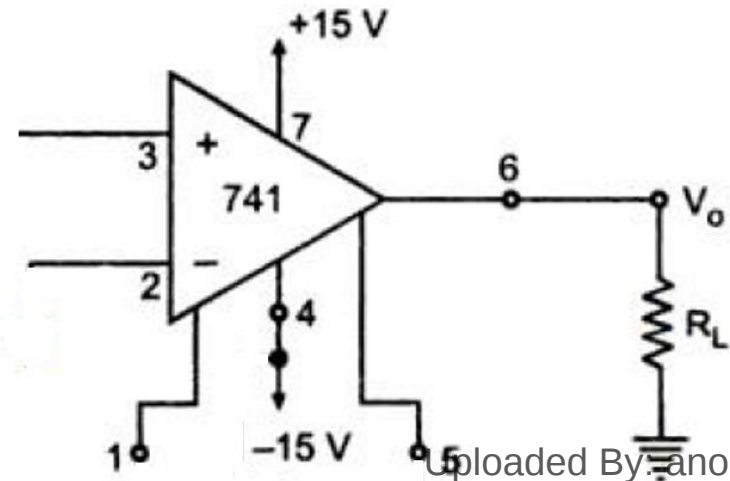

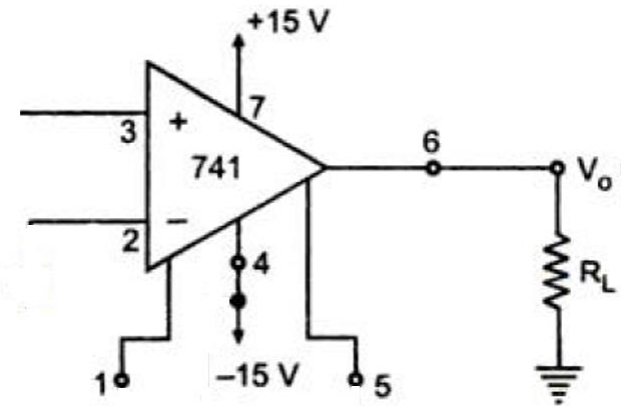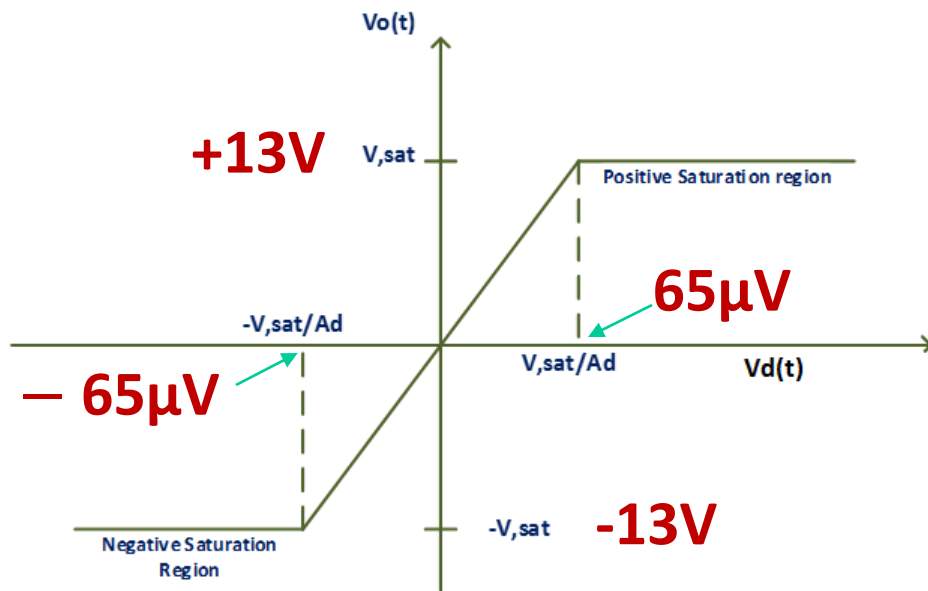

$$v_d = V(+)-V(-)$$



$$\text{Let } \pm V_{cc} = \pm 15V ; A_d = 200,000$$

$$\therefore \pm V_{sat} = \pm 13V$$

$$\therefore \text{ If } V_d > 65\mu V ; V_o = +13V$$

$$\therefore \text{ If } V_d < -65\mu V ; V_o = -13V$$

Op-amp Model in the Linear Region:

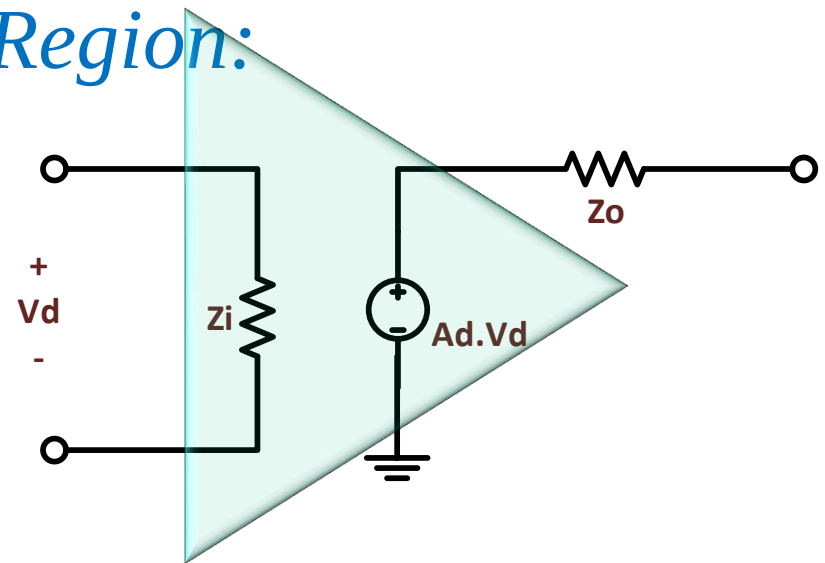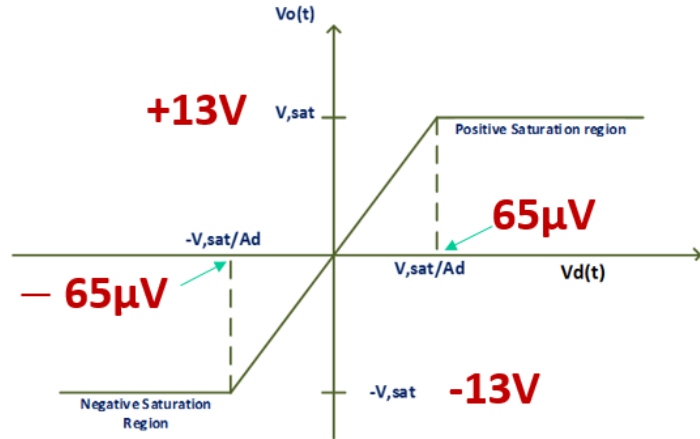


If the Op-Amp is IDEAL and in the Linear Region:

$$Z_i = \infty \Omega, Z_o = 0 \Omega, Ad = \infty$$

Two Assumptions

1) $V_d \cong 0 \Rightarrow V(+)=V(-)$

2) $i(+)=i(-)=0$

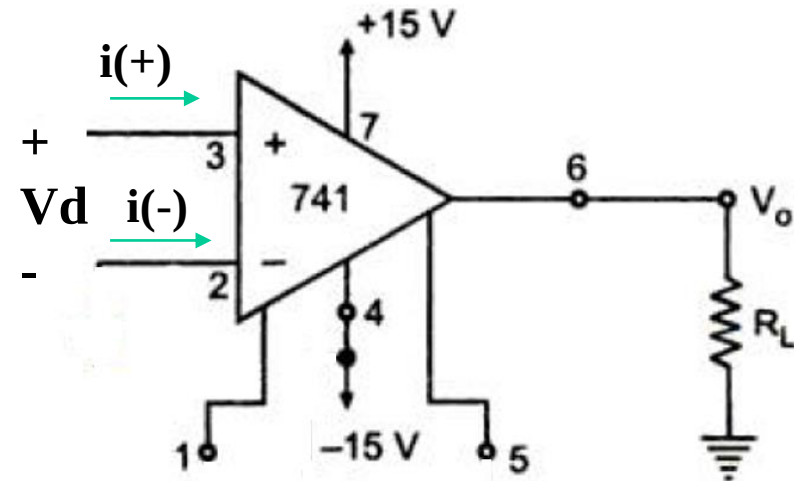

Op-amp Linear Applications:

1. Inverting Amplifier

a) Since $V(+)=0$; $\therefore V(-)=0$

And $i_s = \frac{v_s}{R_i}$ (Virtual ground)


b) Since $i(-)=0$; $\therefore i_F = i_s$

c) $V_O = -R_F i_F$

$$V_O = -R_F i_s$$

$$V_O = -\frac{R_F}{R_i} V_s$$
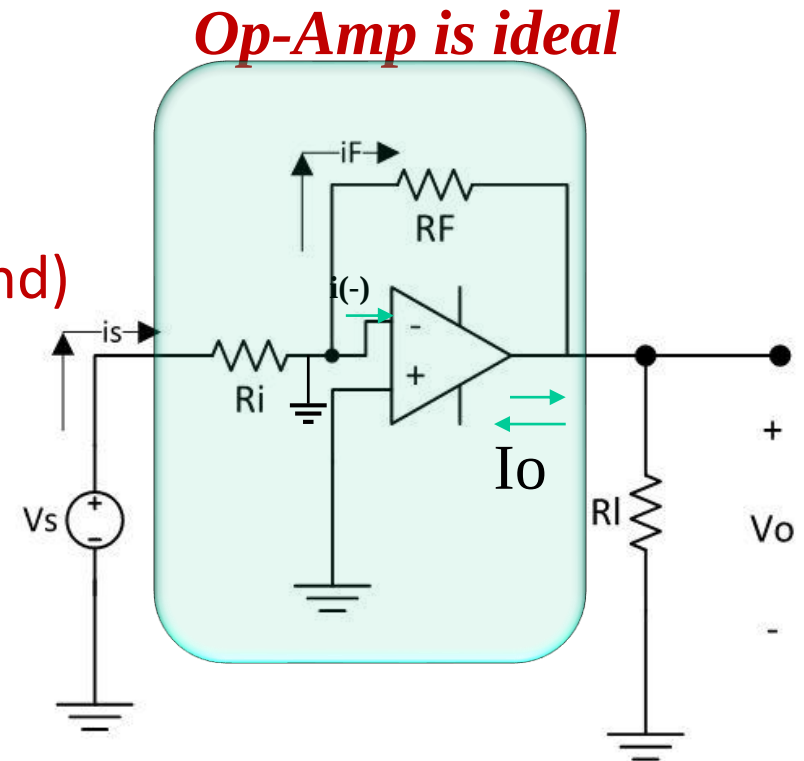
$$\therefore A_v = \frac{V_O}{V_s} = -\frac{R_F}{R_i}$$



$$+V_{sat} > V_O > -V_{sat}$$

$$I_o < I_{o,max}$$

The voltage gain does not depend on RL

Op-Amp Linear Applications:

1. Inverting Amplifier

Design an inverting amplifier to provide $A_v = -200$

Solution :


$$A_v = -\frac{R_F}{R_i} = -200$$

$$\therefore \frac{R_F}{R_i} = 200$$

Let $R_i = 20K$

$$\therefore R_F = 4000K$$

$$Z_i = R_i$$

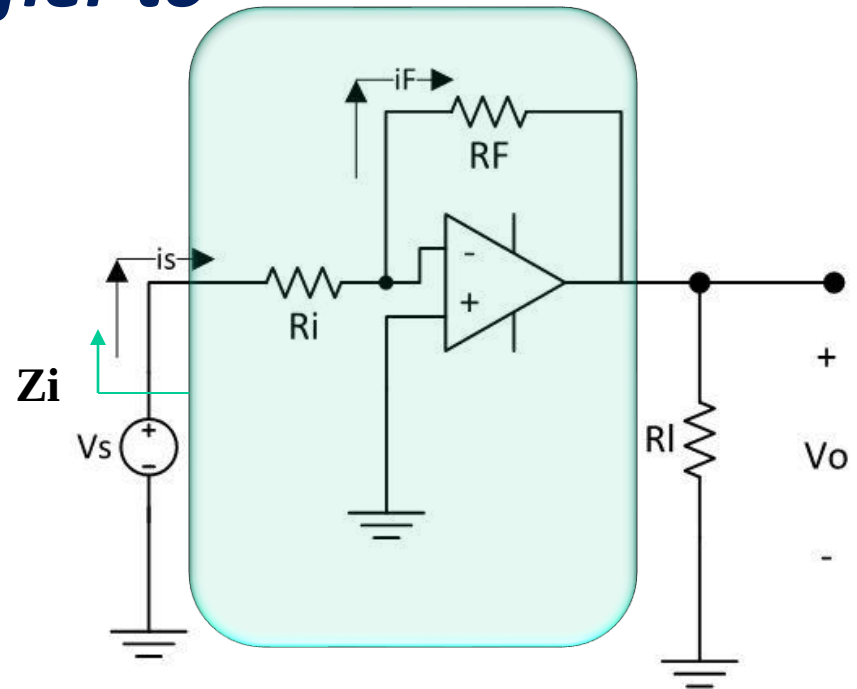

Op-amp Linear Applications:

2. Inverting Adder

1- Since $V(+) = 0$;

$\therefore V(-) = 0$


$$i_1 = \frac{v_1}{R_1} ; \quad i_2 = \frac{v_2}{R_2} ;$$

$$i_3 = \frac{v_3}{R_3}$$

$$i_s = i_1 + i_2 + i_3$$

2- Since $i(-) = 0$; $\therefore i_F = i_s$

3- $V_O = -R_F i_F$

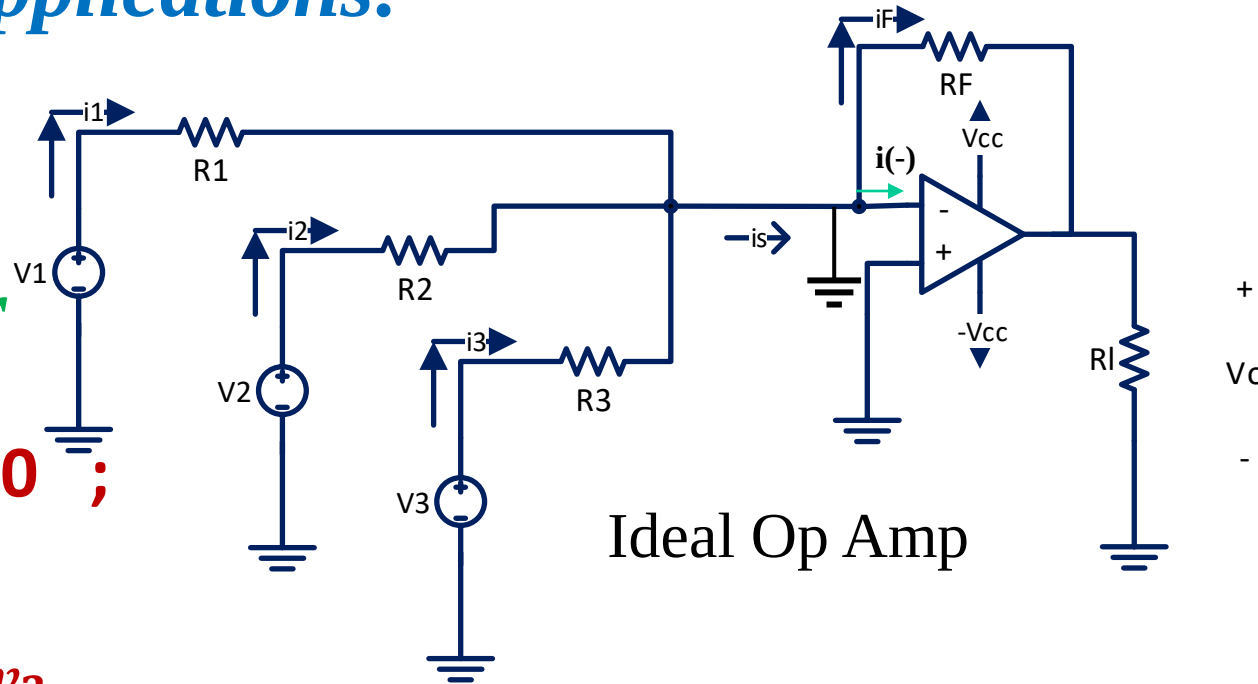


$$V_O = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$

If $R_1 = R_2 = R_3 = R_F = R$

$$V_O = - (V_1 + V_2 + V_3)$$

Op-amp Linear Applications:

2. Inverting Adder

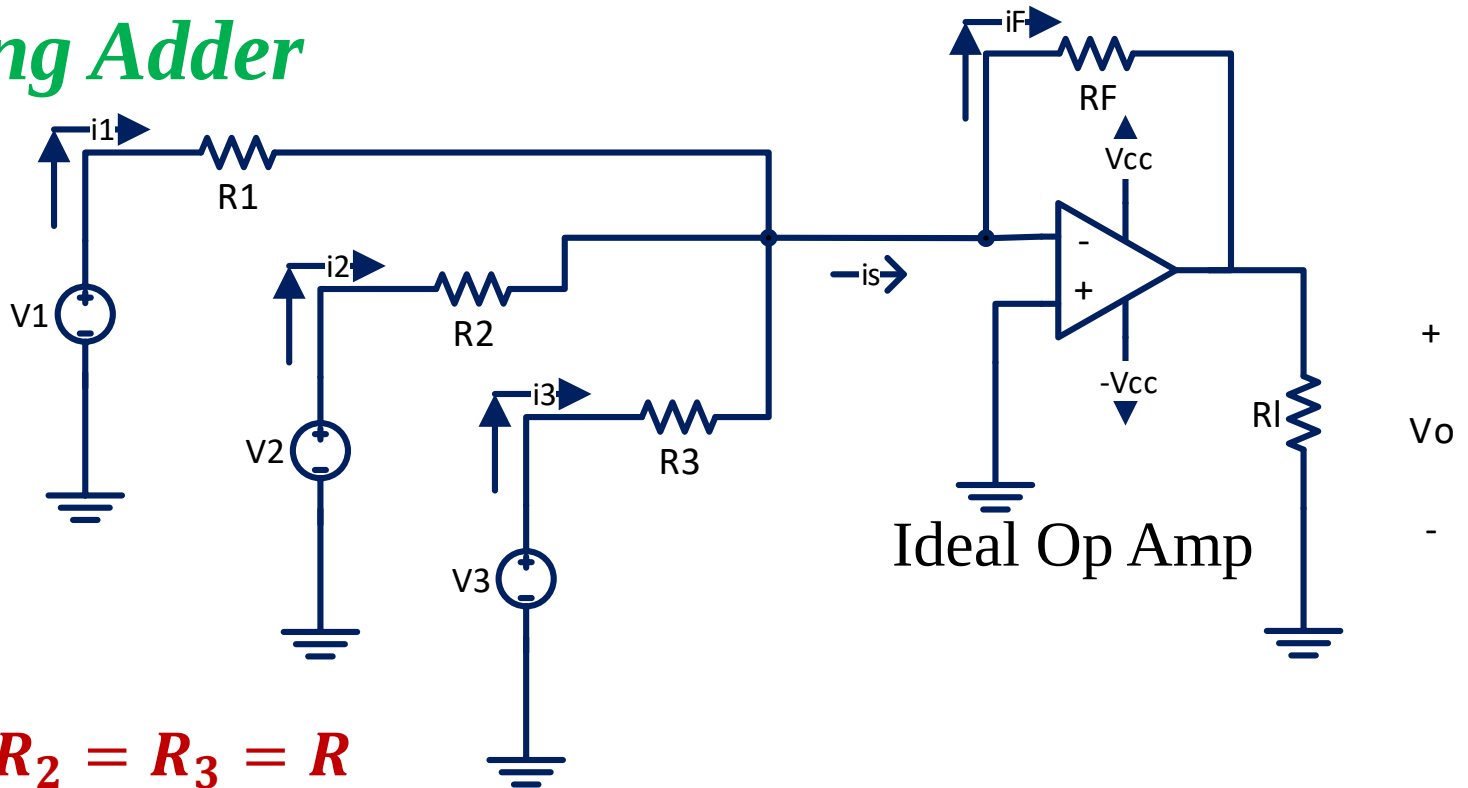

If $R_1 = R_2 = R_3 = R$

And $R_F = \frac{R}{n} = \frac{R}{3}$



Averager

$$\therefore V_O = - \left(\frac{V_1 + V_2 + V_3}{3} \right)$$

3. Non Inverting Amplifier

1- Since $V(+) = V_s$

$$\therefore V(-) = V_s$$

$$\therefore i_i = \frac{V_s}{R_i}$$


2- Since $i(-) = 0$;

$$\therefore i_F = i_i$$

$$3 - V_O = R_F i_F + R_i i_i$$

$$\Rightarrow V_O = \left(1 + \frac{R_F}{R_i}\right) V_s$$
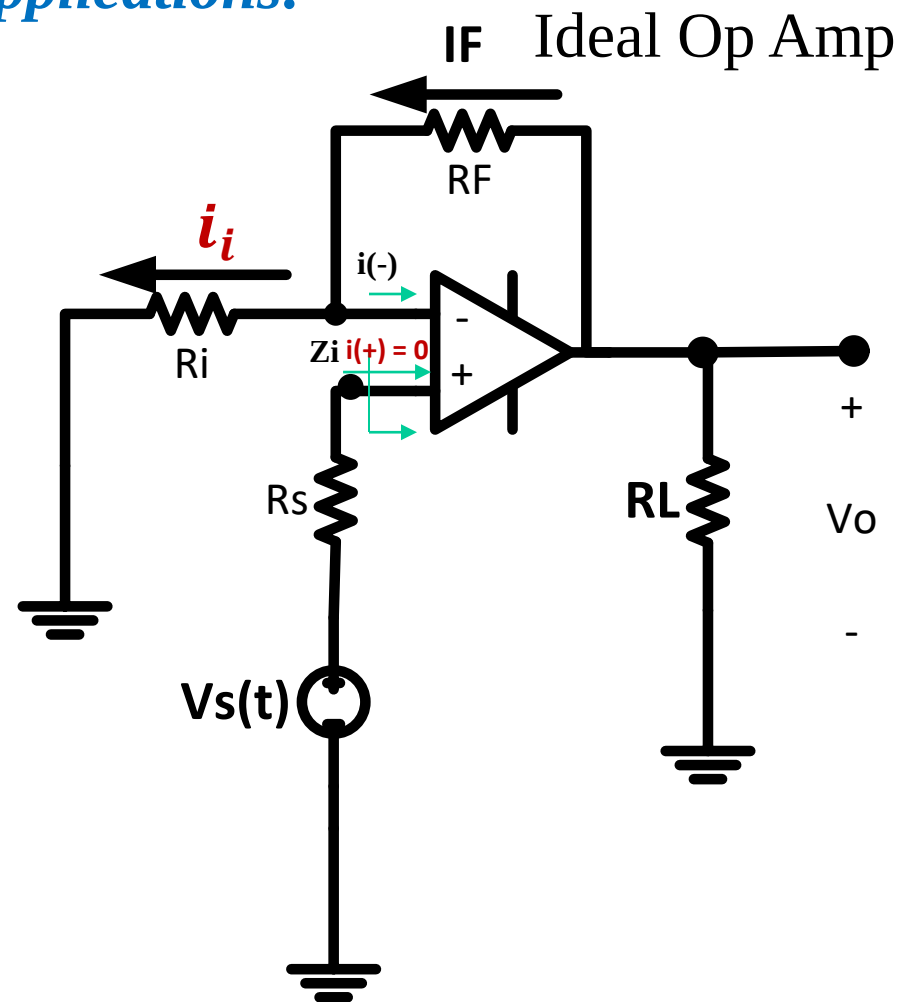
$$V_O = \left(1 + \frac{R_F}{R_i}\right) V(+)$$



$$Z_i = \infty$$

Op-amp Linear Applications:

Non Inverting Amplifier

Design a non inverting amplifier to provide $A_v = 100$


Solution :

$$A_v = 1 + \frac{R_F}{R_i} = 100$$

$$\therefore \frac{R_F}{R_i} = 99$$

$$\text{Let } R_i = 10\text{K}$$

$$\therefore R_F = 990\text{K}$$

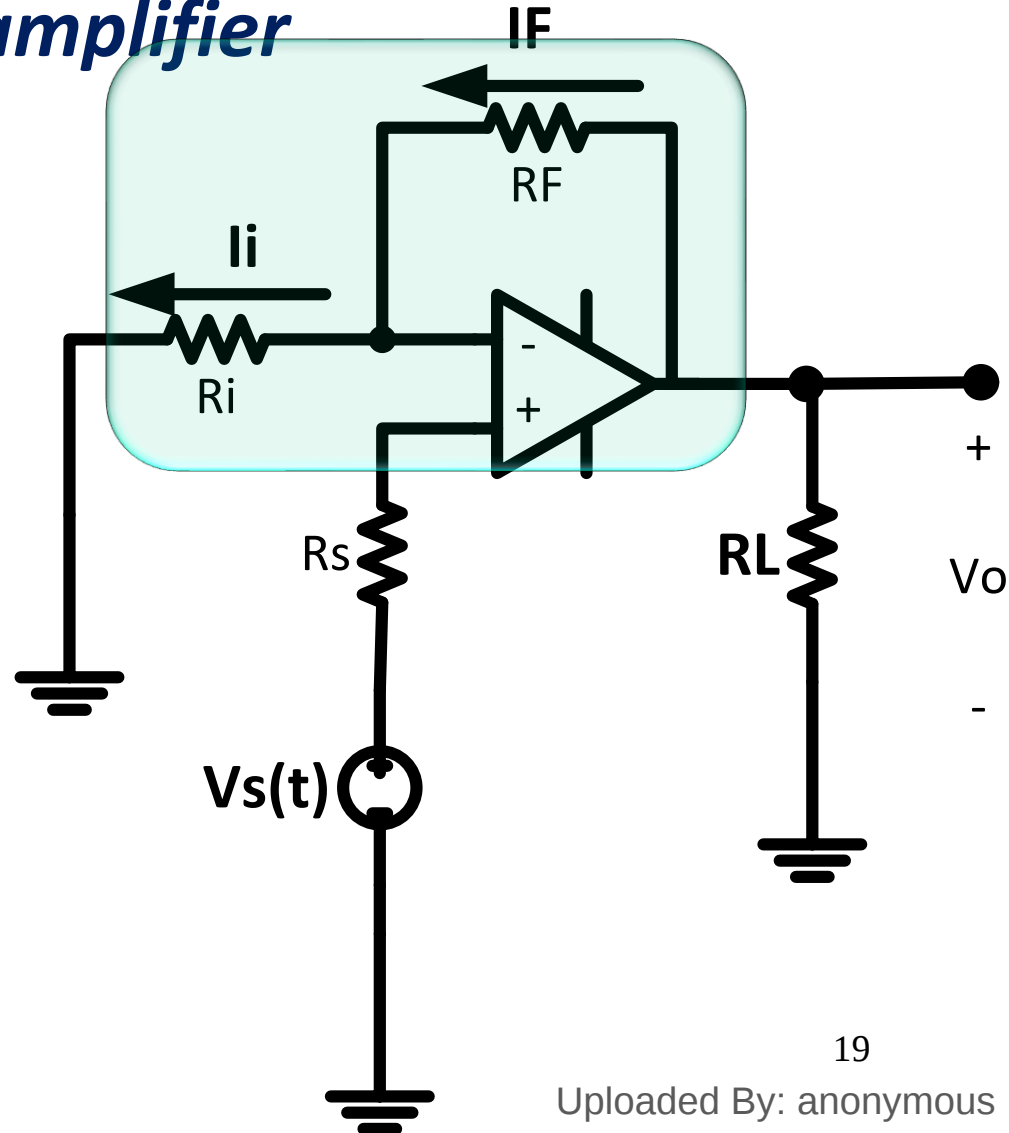

Op-amp Linear Applications:

4. Buffer , Unity Gain



1- Since $V(+)=V_s$; $\therefore V(-)=V_s$

2- $V_o = V(-) = V_s$

Buffer is a special Case of
non inverting amplifier for which:

$$R_i = \infty$$




$$R_F = 0$$

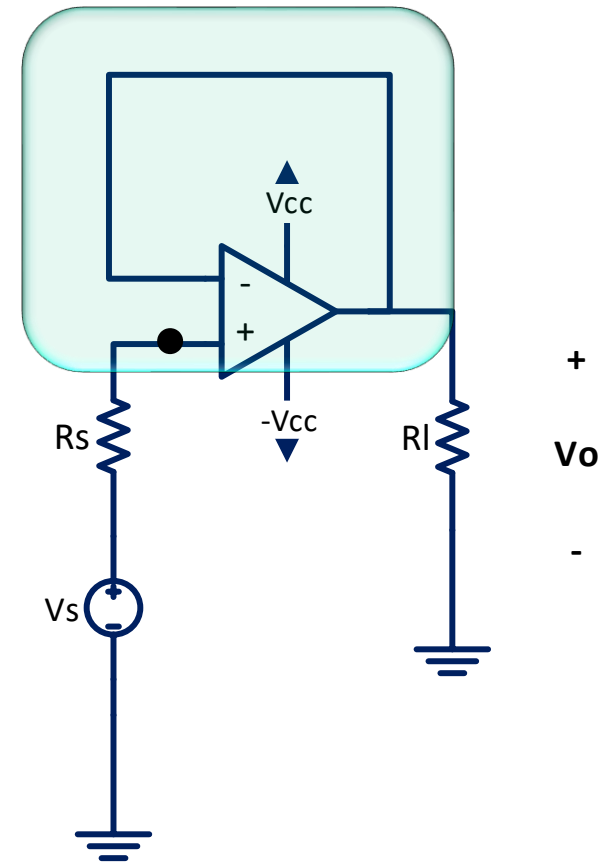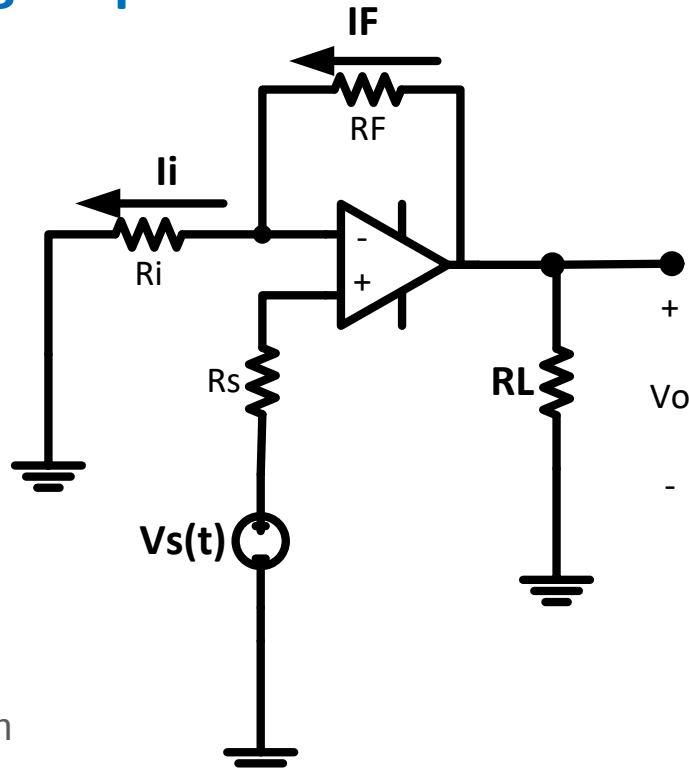

Op-Amp Buffer

$$V_{out} = V_{in}$$


Isolates loading effects

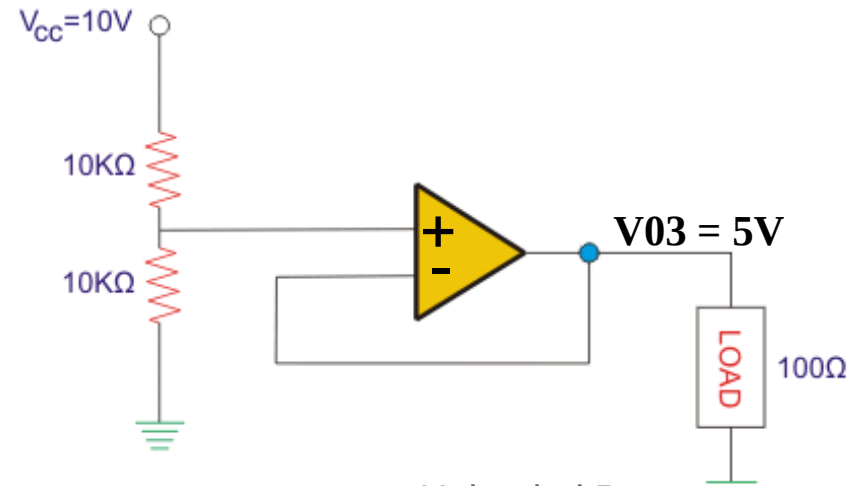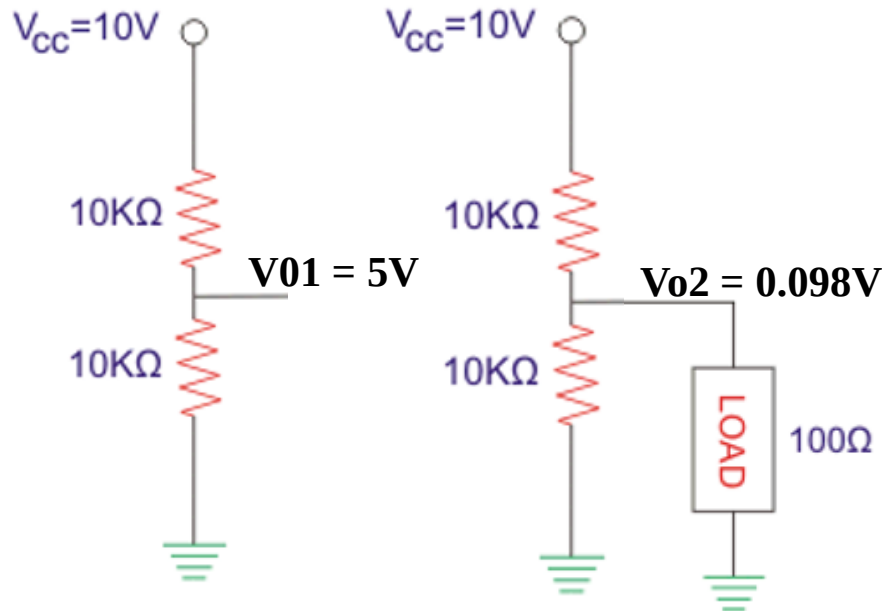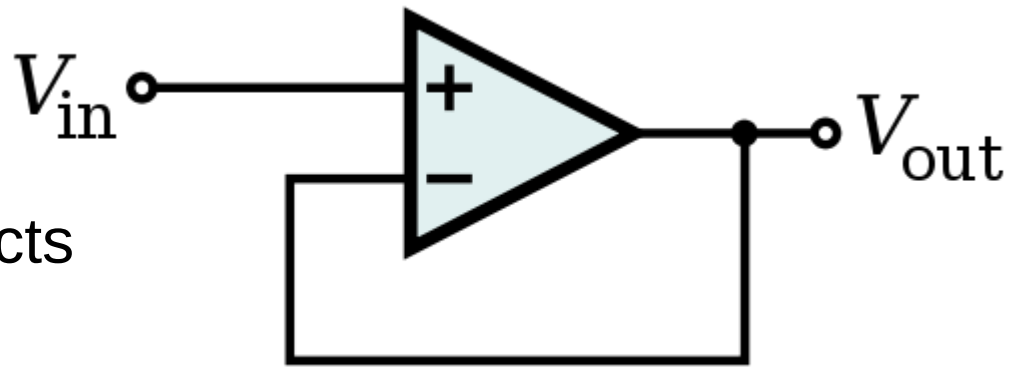

Op-amp Linear Applications:


5. Non-inverting Adder


Ideal Op Amp

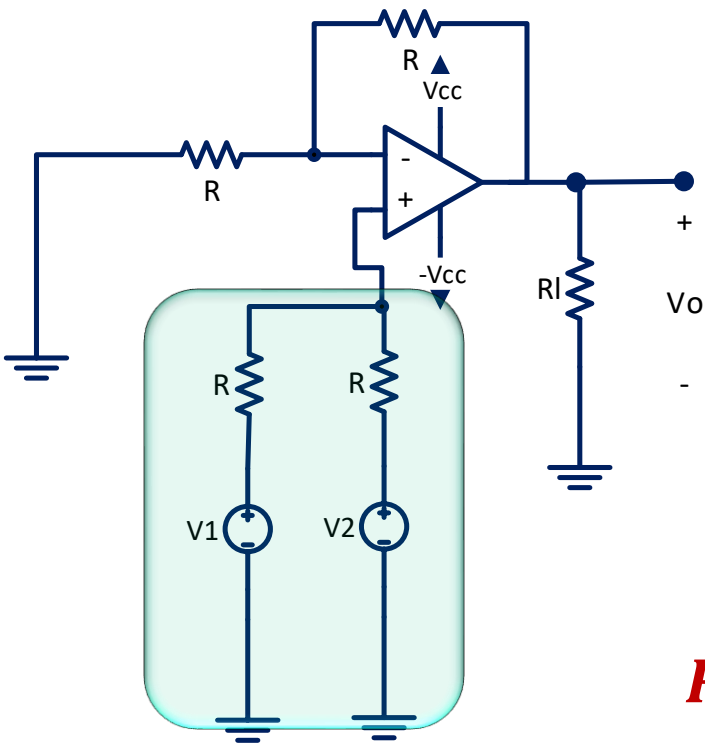

$$V_{TH} = \frac{V_1 + V_2}{2}$$

$$R_{TH} = \frac{R}{2}$$

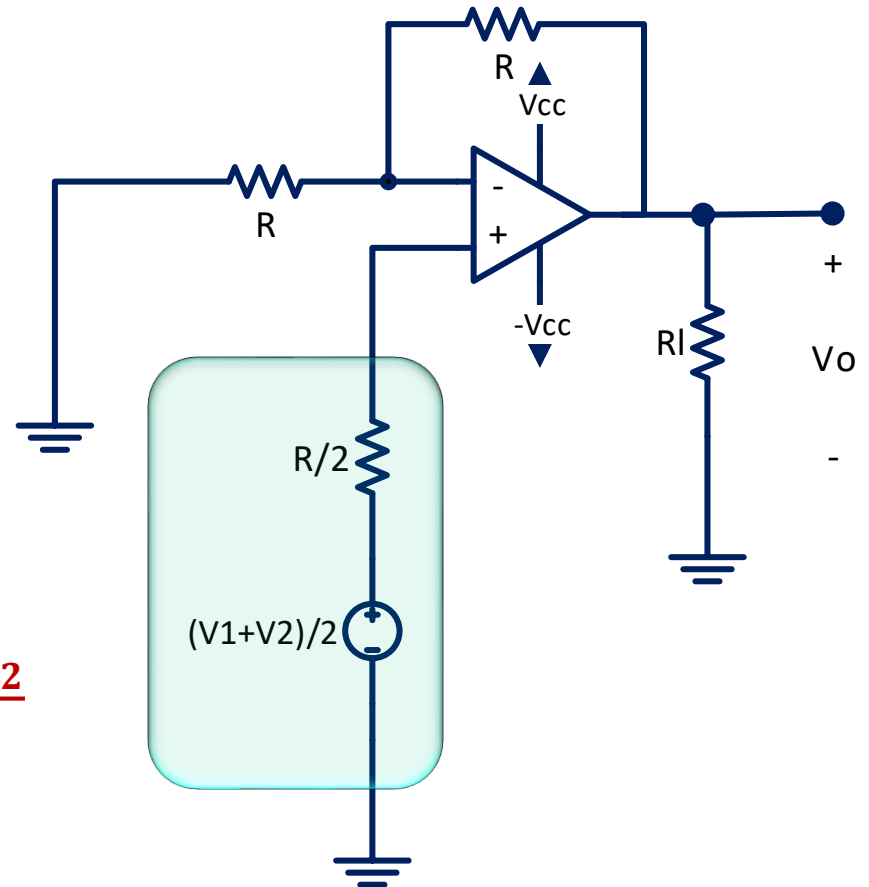

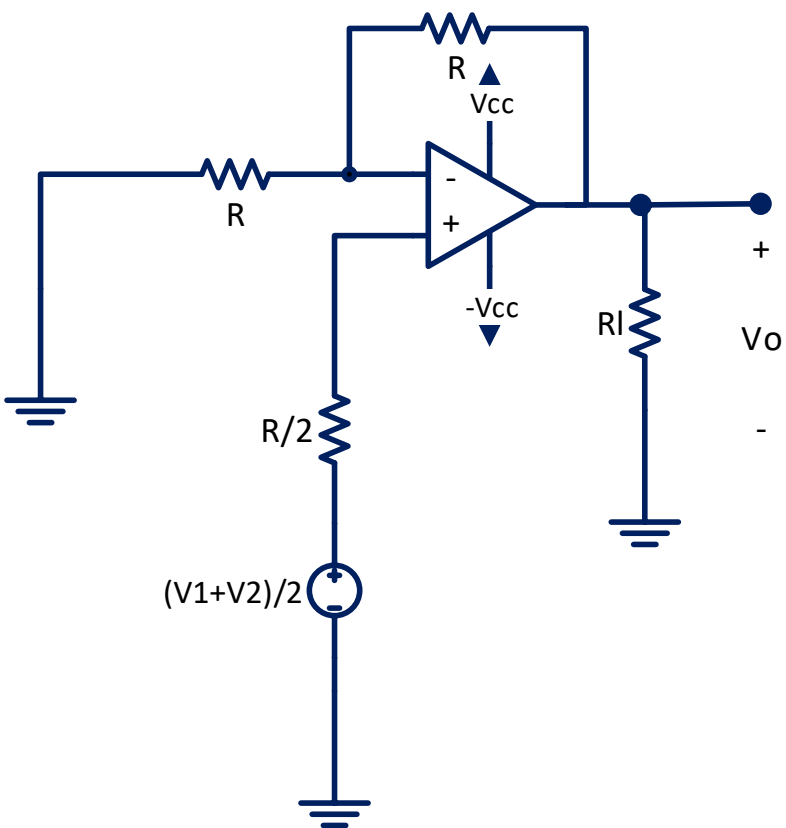

$$V_O = \left(1 + \frac{R}{R}\right) \left(\frac{V_1 + V_2}{2}\right) = V_1 + V_2$$

If we have n signal :

$$\text{let } R_F = (n-1)R$$

$$V_O = V_1 + V_2 + \dots + V_N$$

Op-amp Linear Applications:

6. Voltage Subtraction

Using superposition

a) Let $V_1 = 0$

$$\therefore V_{o1} = -\frac{R_4}{R_3} V_2 \text{ (Inverting amplifier)}$$



b) Let $V_2 = 0$


$$\therefore V_{o2} = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1$$

(non inverting amplifier)

$$\therefore V_O = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1 - \frac{R_4}{R_3} V_2$$

Ideal Op Amp

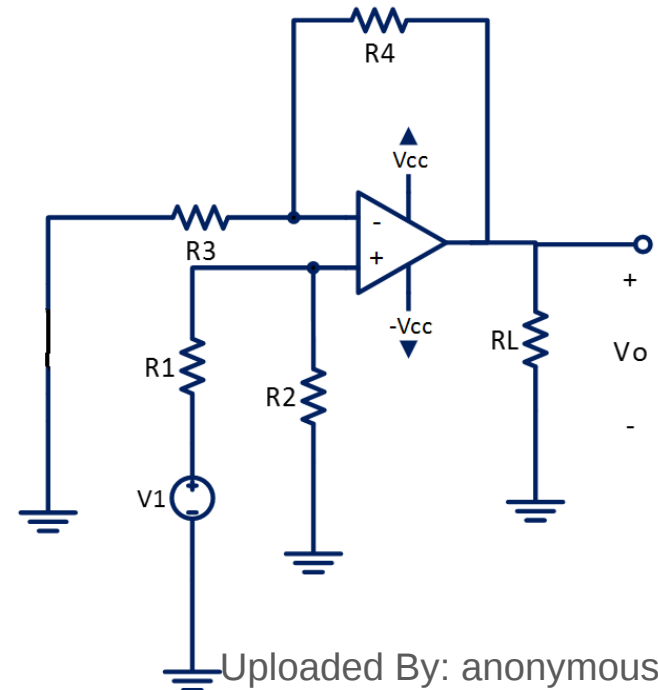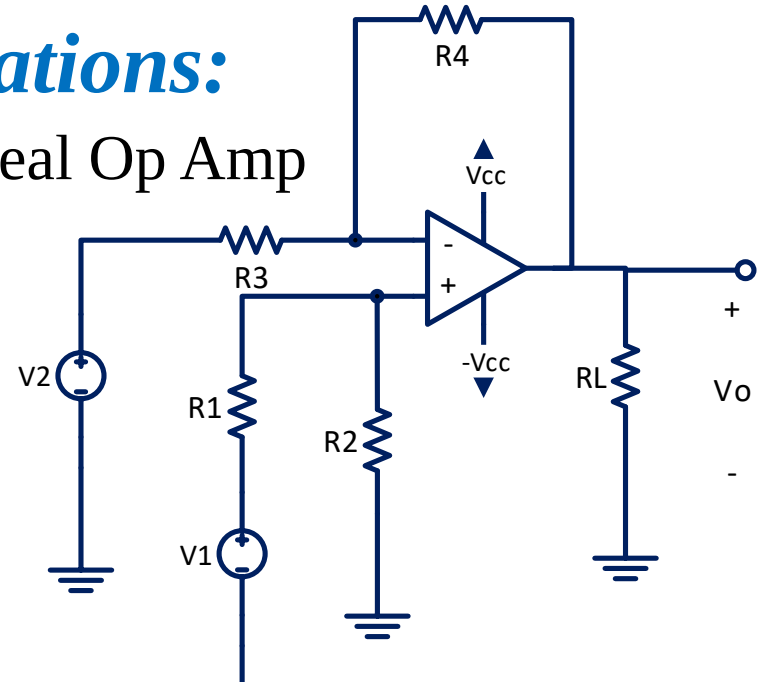

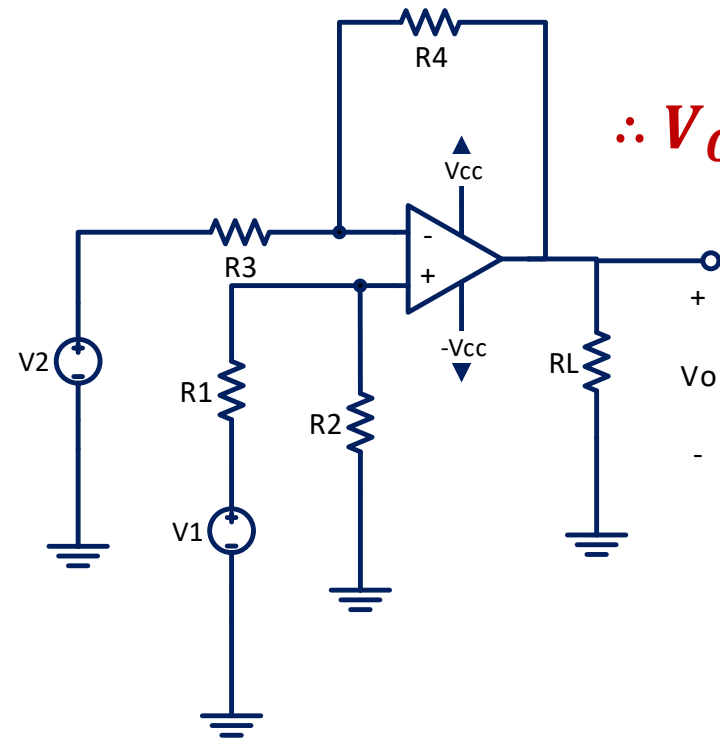

$$\therefore V_O = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1 - \frac{R_4}{R_3} V_2$$

$$V_O = aV_1 - bV_2$$

If $R_1 = R_3 = R$
and $R_2 = R_4 = mR$

$$V_O = m(V_1 - V_2)$$

Basic Difference Amplifier

Op-amp Linear Applications:

Basic Difference Amplifier


$$V_o = m(V_1 - V_2)$$


$$Z_{i1} = R + mR$$

$$Z_{i2} = R$$

*It has low input impedance

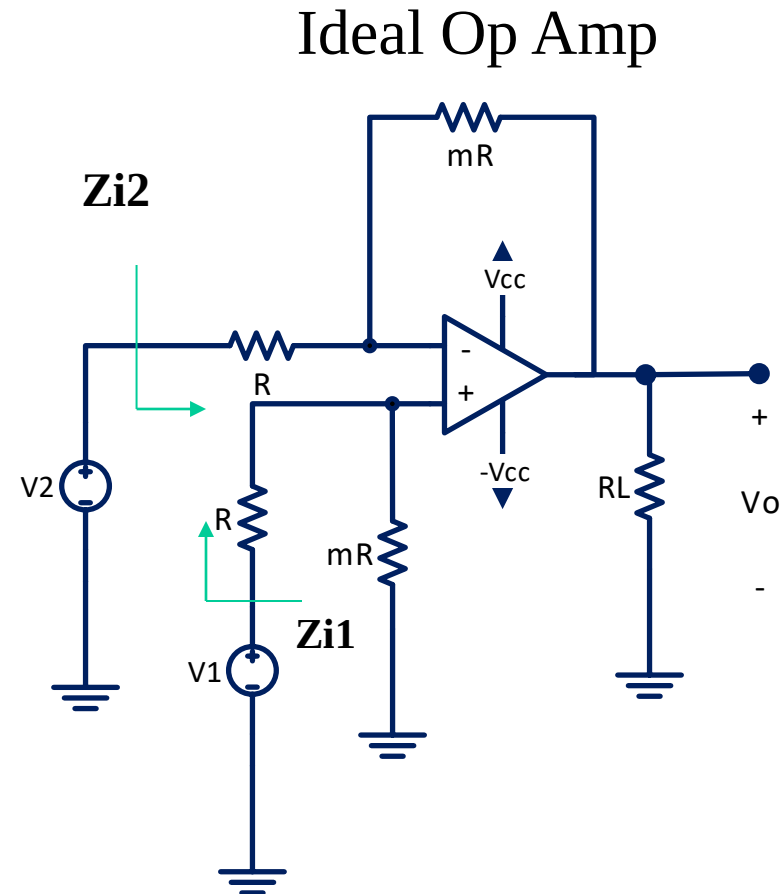*To Change the gain, we must change two resistors.



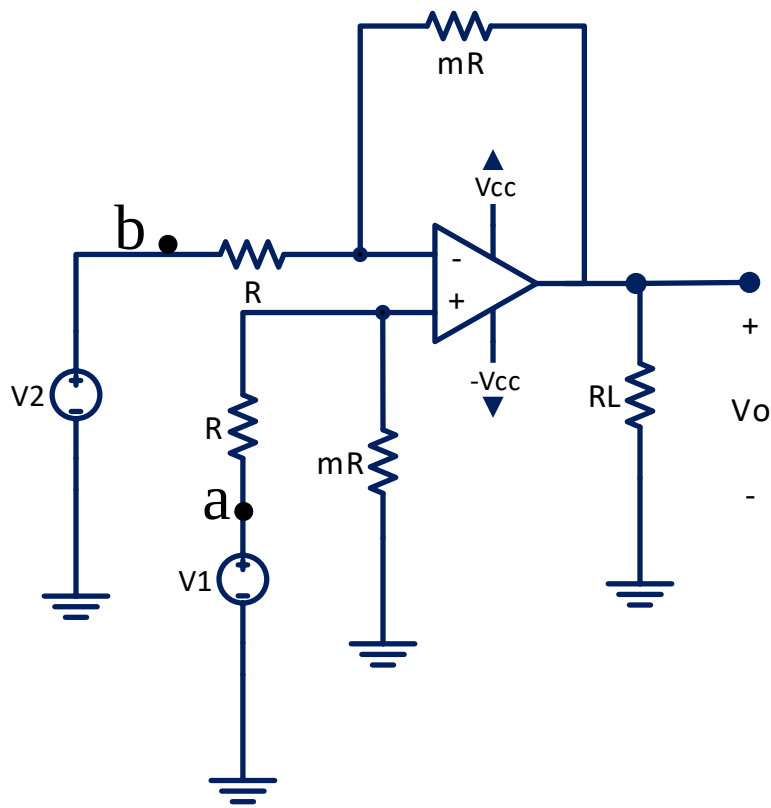


$$V_o = m(V_1 - V_2)$$

$$V_o = m V_{ab}$$

$$V_{ab} = V_1 - V_2$$

$$V_{ab} = V_s$$

$$\therefore V_o = V_s$$

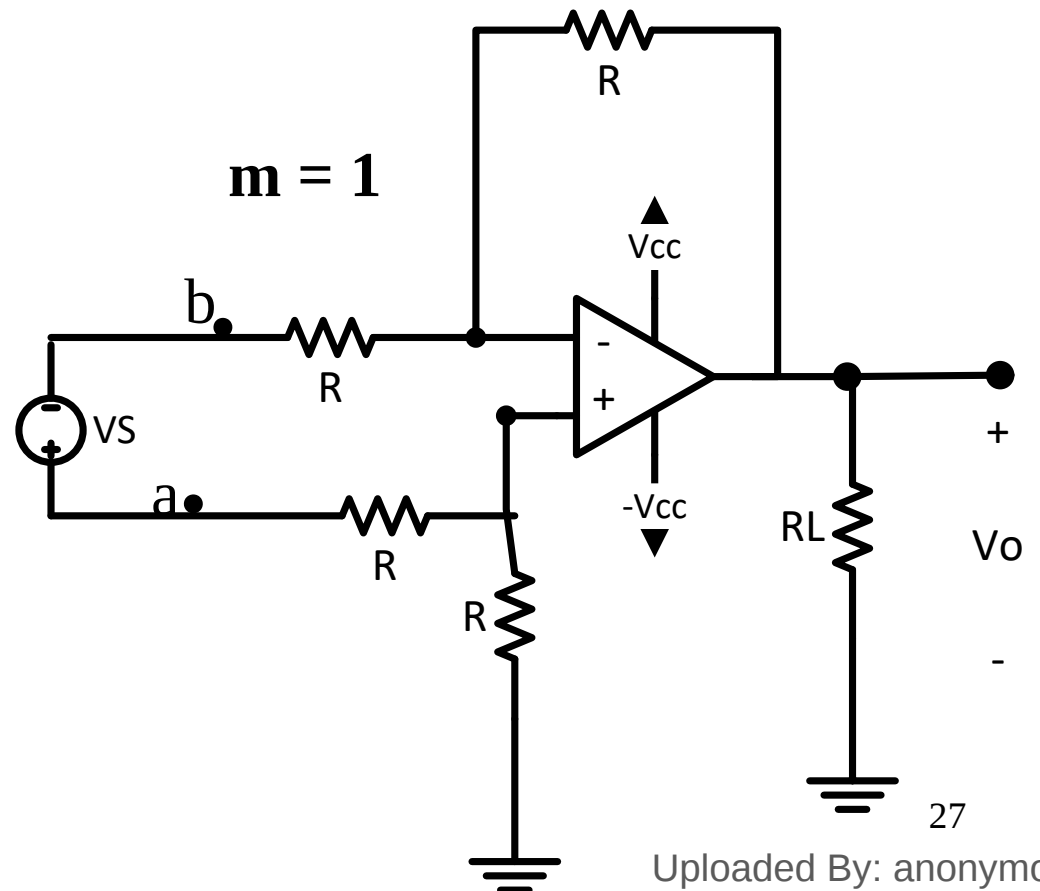

Instrumentation Amplifier:

$$I = \frac{V_1 - V_2}{aR}$$

$$V_{o1} = (R + aR + R)I$$

$$V_{o1} = \left(1 + \frac{2}{a}\right)(V_1 - V_2)$$


$$V_o = V_{o1} = \left(1 + \frac{2}{a}\right)(V_1 - V_2)$$

$$Z_{i1} = \infty$$

$$Z_{i2} = \infty$$

To change the gain →
change a

$$a \ll 1$$

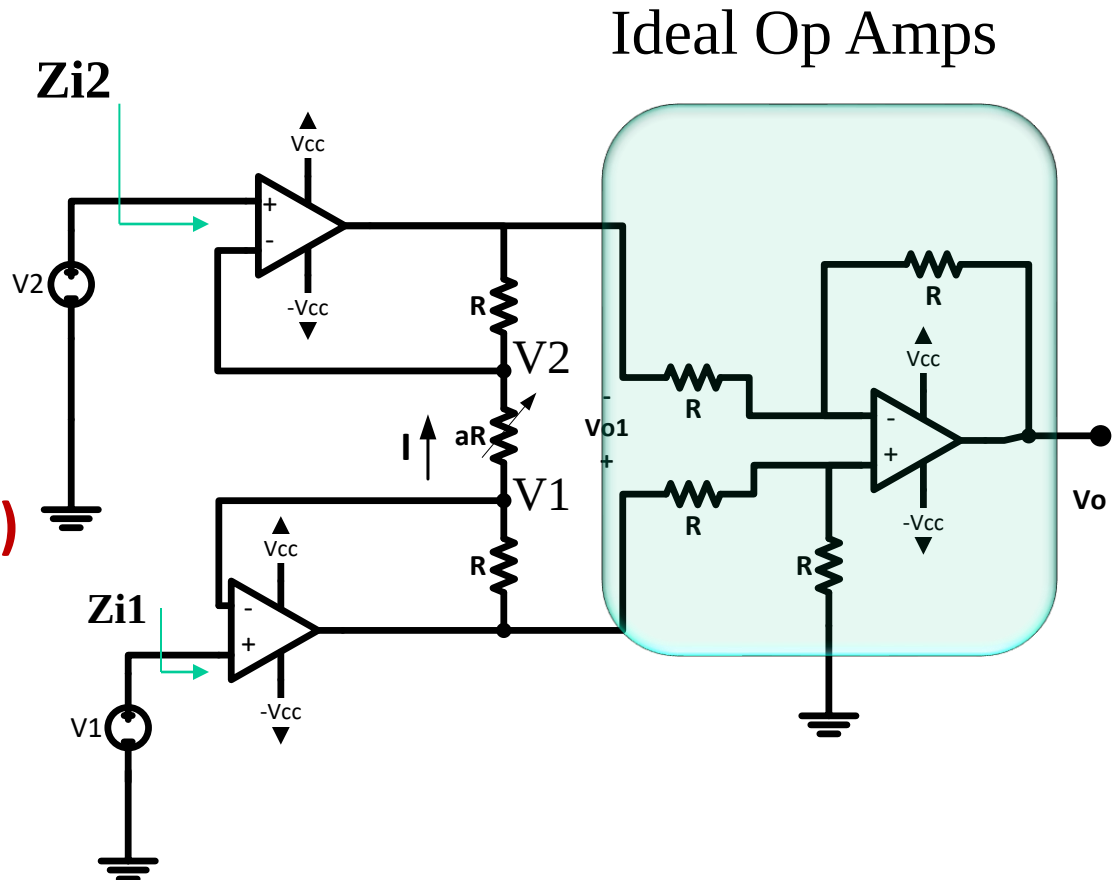

Measuring small resistance change

$$E_1 = \frac{R_1}{R_1 + R_1} E = \frac{E}{2}$$

$$E_2 = \frac{R}{R + R + \Delta R} E = \frac{R}{2R + \Delta R} E$$

$$V_o = \left(1 + \frac{2}{a}\right) (E_1 - E_2).$$

$$E_1 - E_2 = \frac{E}{2} \left(\frac{\Delta R}{2R + \Delta R} \right)$$

ΔR is very small


$$E_1 - E_2 = \frac{E}{2} \frac{\Delta R}{2R}$$

$$V_o = \left(1 + \frac{2}{a}\right) (E_1 - E_2).$$

$$\text{Let } \left(1 + \frac{2}{a}\right) = 400$$

$$V_o = (400) \left(\frac{\Delta R}{4R} \right) E$$
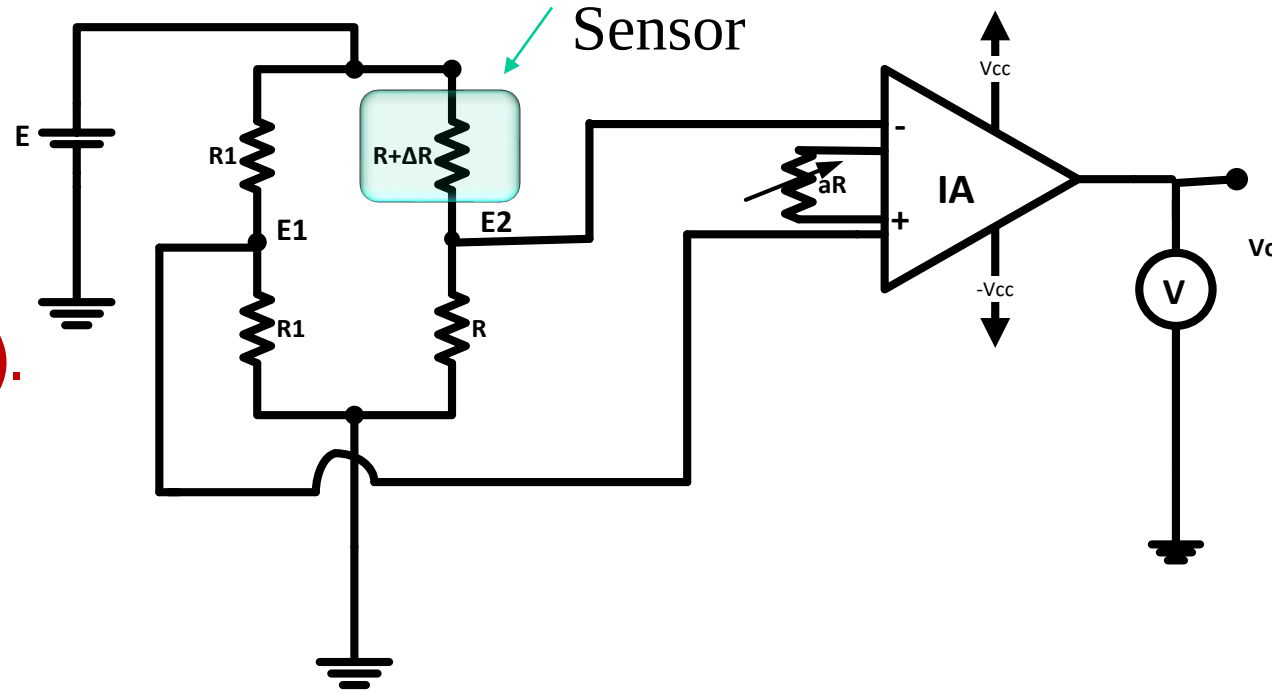
$$V_o = 100 E \left(\frac{\Delta R}{R} \right)$$



Measuring small resistance change

$$V_o = 100 E \left(\frac{\Delta R}{R} \right)$$

$$\text{If } R = 10K$$

$$\Delta R = 0.1K$$


$$E = 1V$$

$$\frac{\Delta R}{R} = 1\% \quad \text{change}$$

$$V_o = 1V$$

$$\therefore 1V \text{ per } 1\%$$

change in resistance

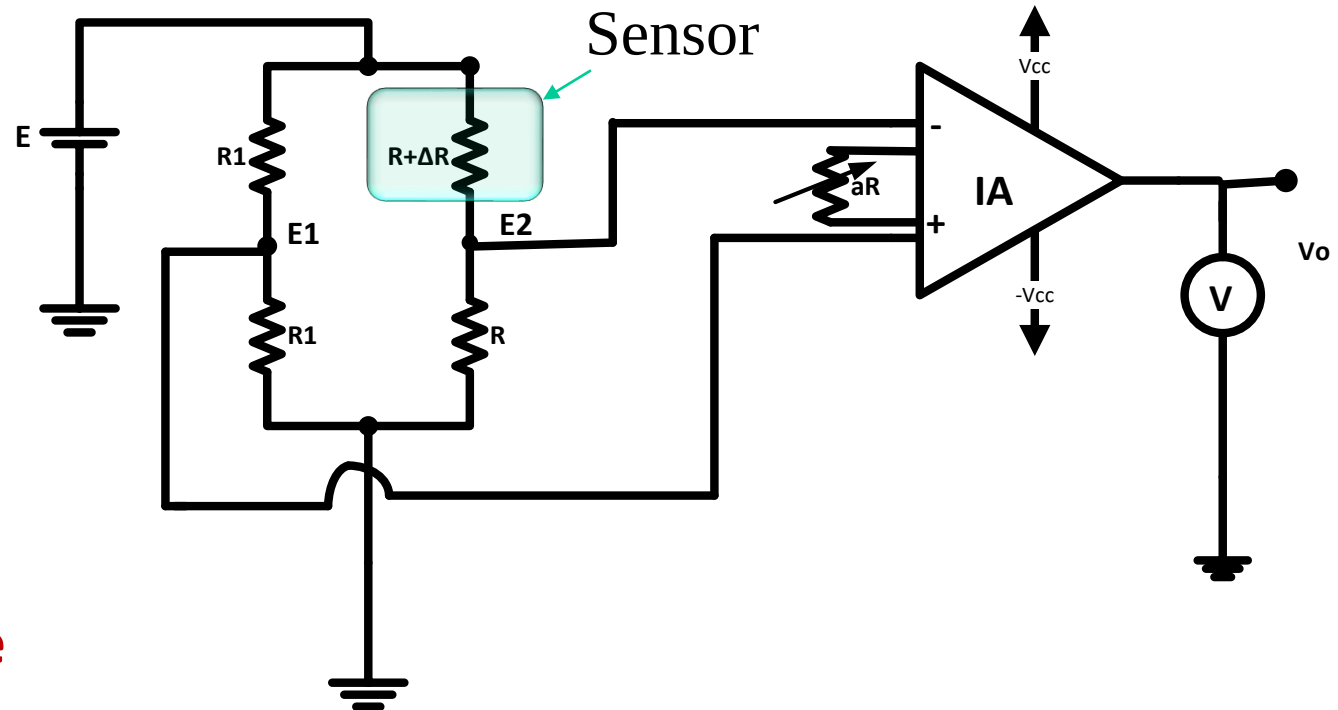

$$\text{If } V_o = 2V \quad \longrightarrow \quad \Delta R = 0.2K$$

$$\text{If } V_o = 0.1V \quad \longrightarrow \quad \Delta R = 0.01K$$

$$\text{If } V_o = 0.01V \quad \longrightarrow \quad \Delta R = 0.001K$$

$$\text{If } V_o = 1mV \quad \longrightarrow \quad \Delta R = 0.0001K$$

Voltage to current Converter


a) Floating load

Since $V(+) = V_i$

$$\therefore V(-) = V_i$$

$$I_i = \frac{V_i}{R_i}$$

$$I_L = I_i = \frac{V_i}{R_i}$$



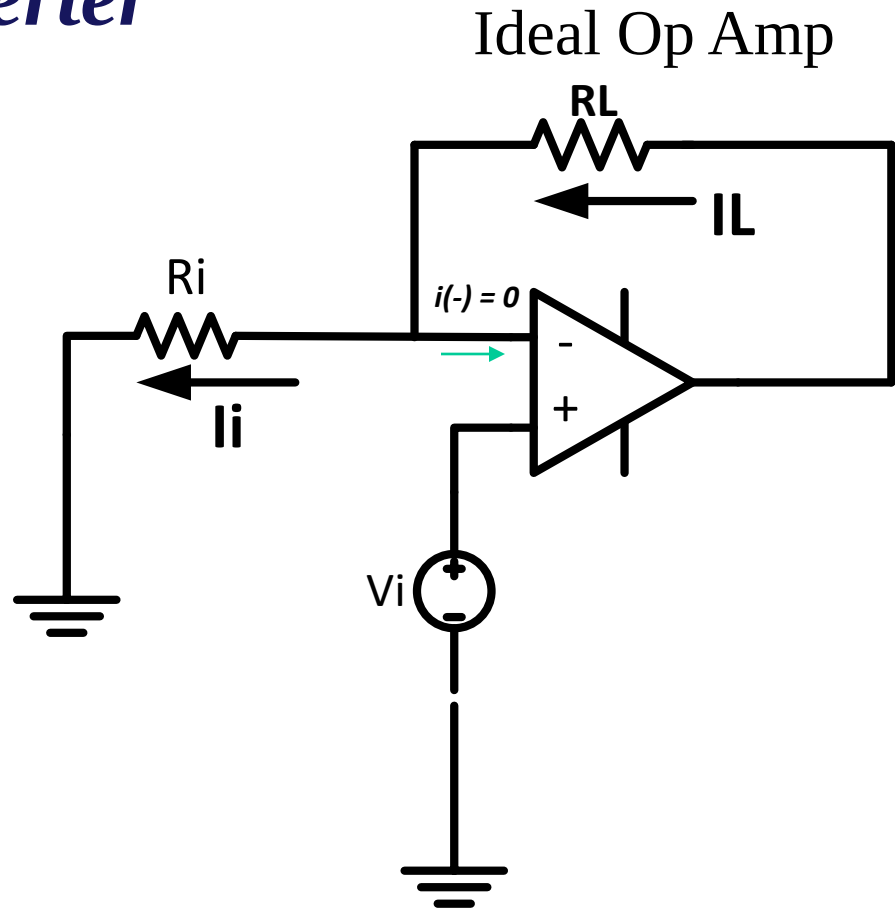



High-Resistance DC Voltmeter

$$I_m = I_i = \frac{V_i}{R_i}$$

If $V_i = +1V \rightarrow I_m = +1mA$
 $R_i = 1k$

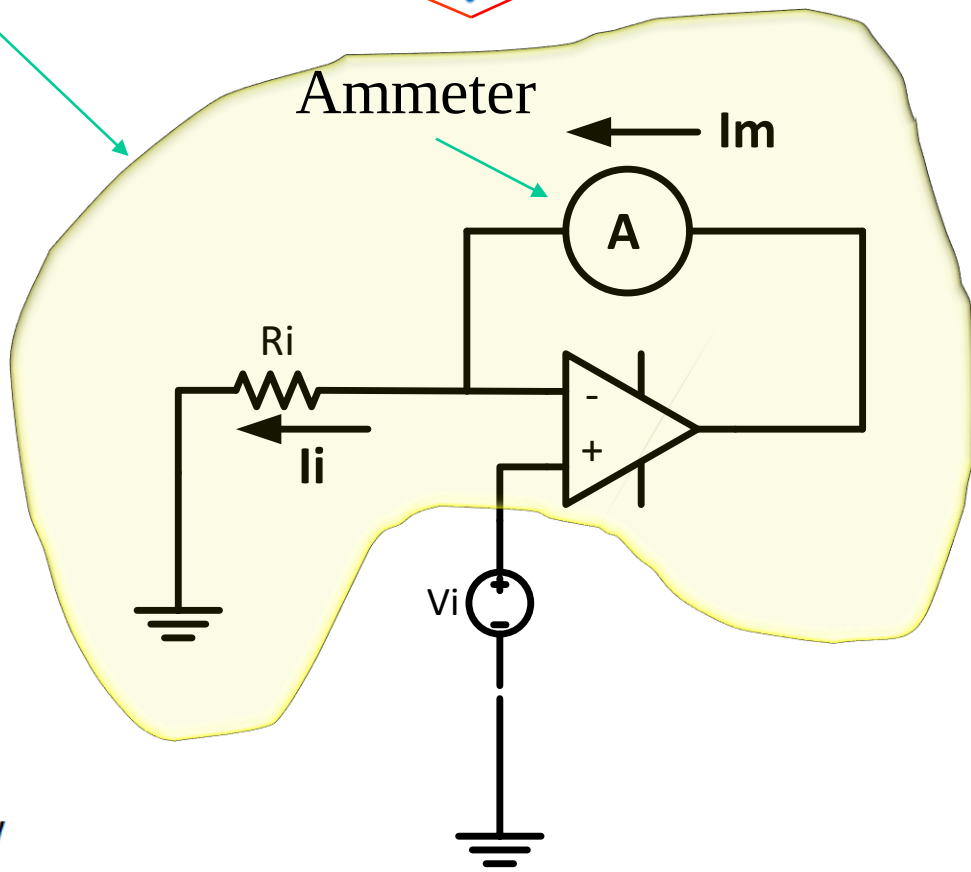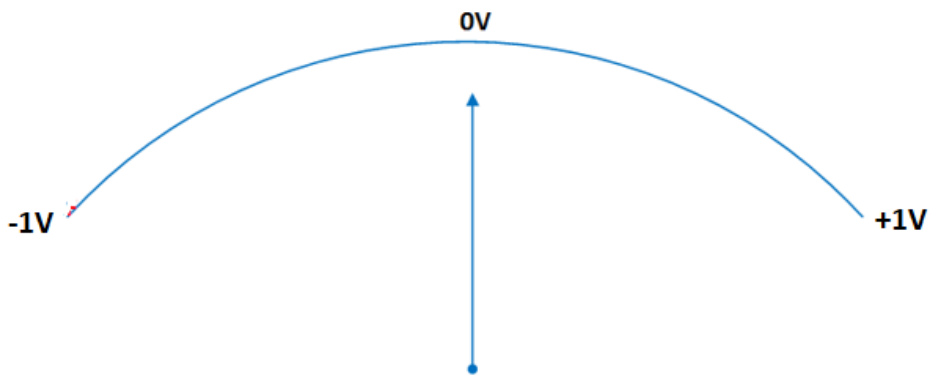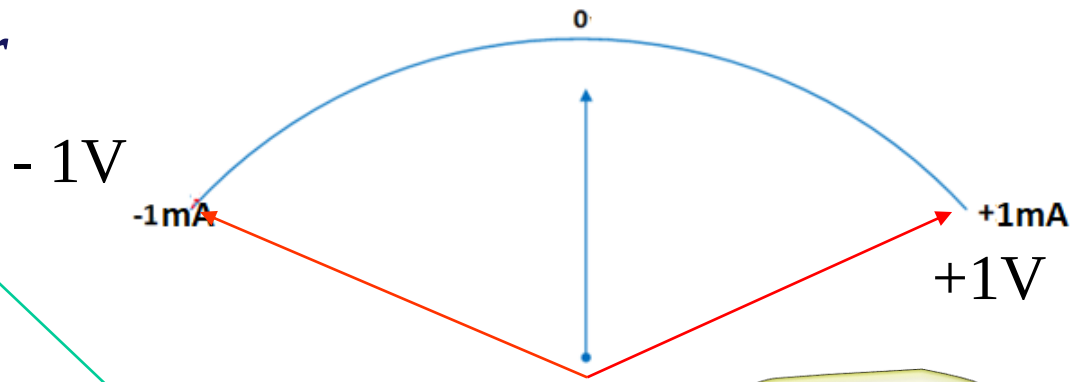If $V_i = -1V \rightarrow I_m = -1mA$
 $R_i = 1k$



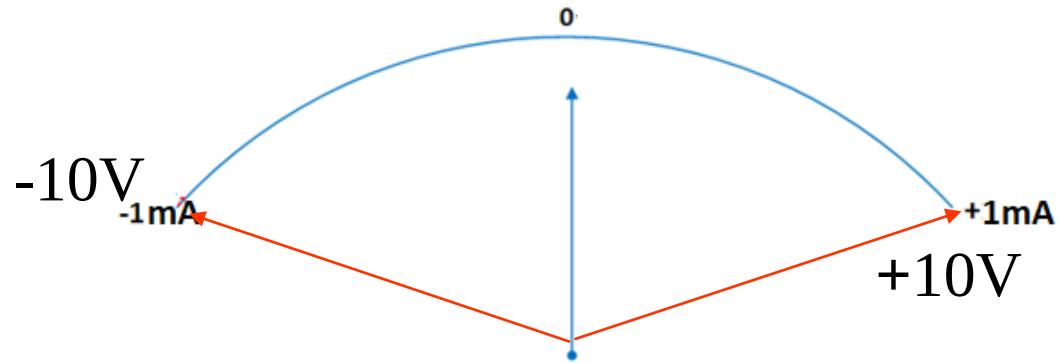




If $V_i = +10V \rightarrow I_m = +1mA$

$$R_i = 10k$$

If $V_i = -10V \rightarrow I_m = -1mA$

$$R_i = 10k$$

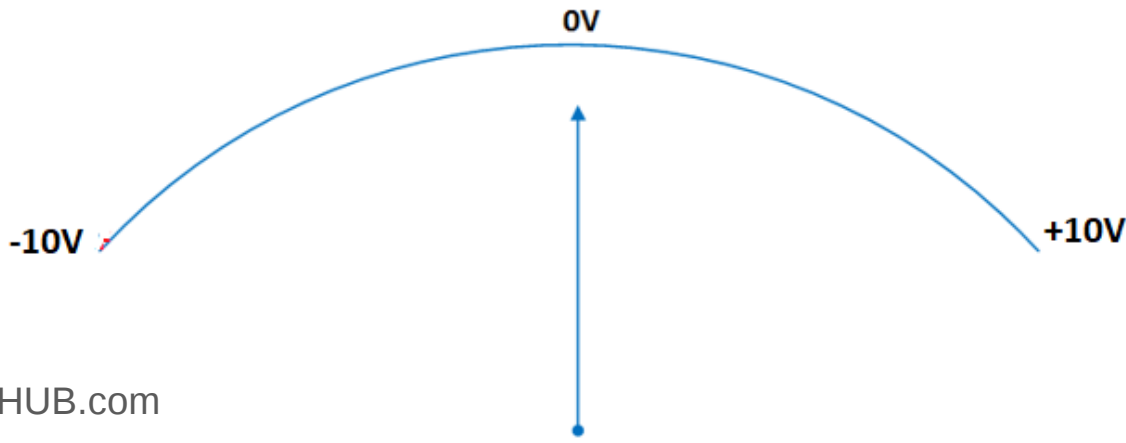

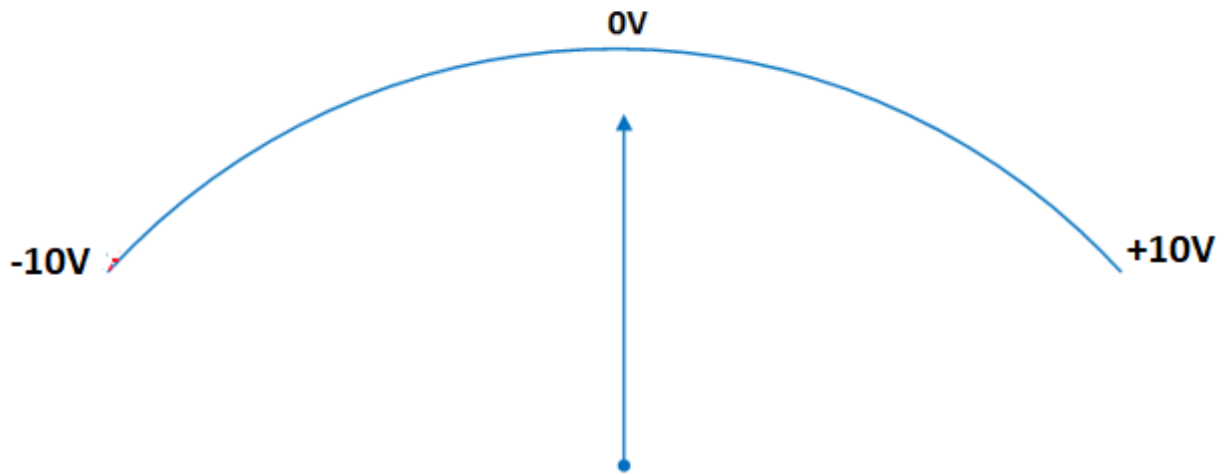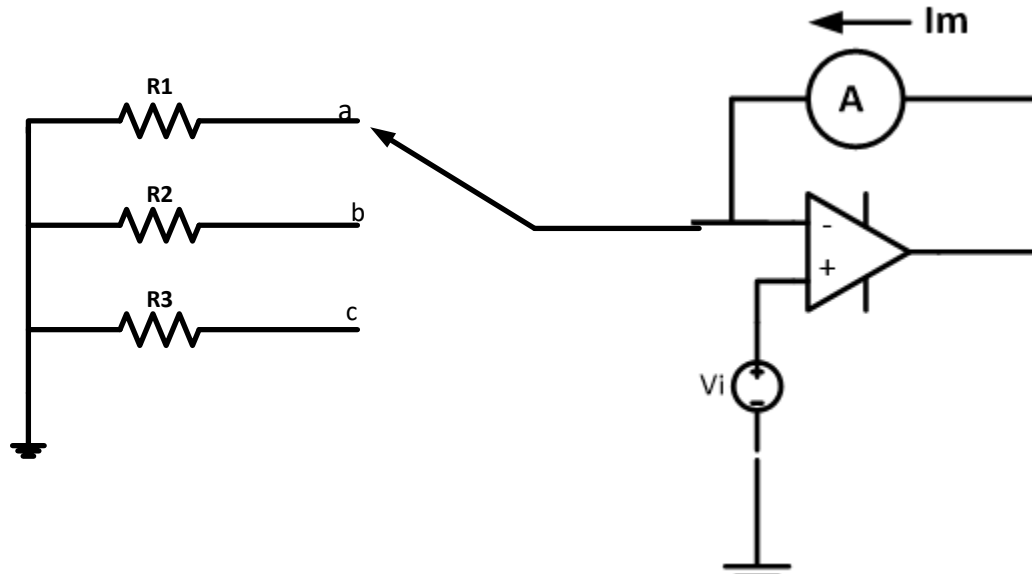

Voltage to current Converter

Ideal Op Amp


b) Grounded load

$$V_L = V(-) = \frac{1}{2} V_o$$

$$I_L = I_1 + I_2$$

$$I_L = \frac{V_o - V_L}{R} + \frac{E - V_L}{R}$$

$$\therefore I_L = \frac{E}{R}$$

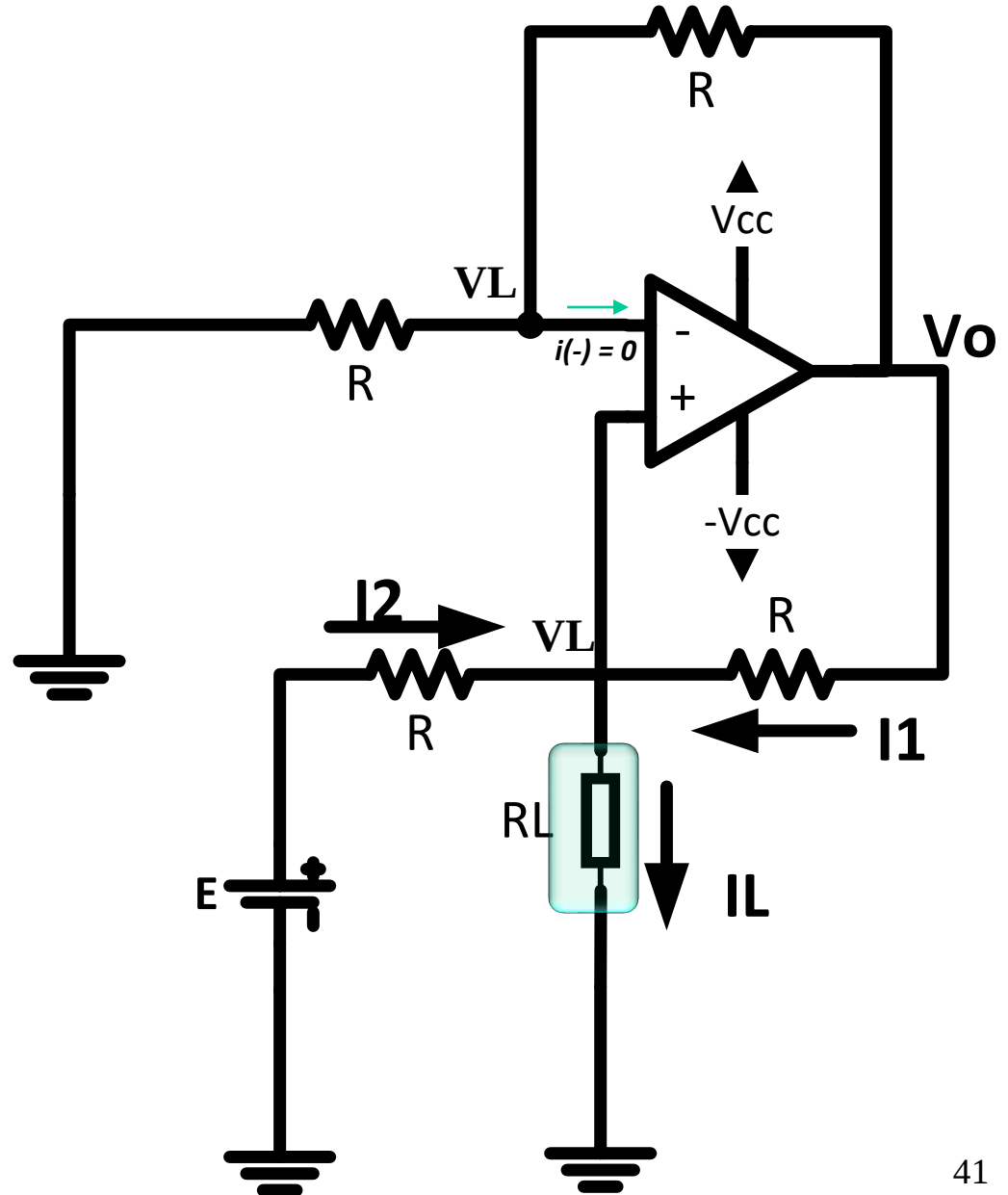

Current to Voltage Converter


$$V(+)=R I$$

$$V_o = \left(1 + \frac{R}{R}\right) V(+)$$

$$V_o = \left(1 + \frac{R}{R}\right) R I$$

$$V_o = K I$$

$$K = 2R$$

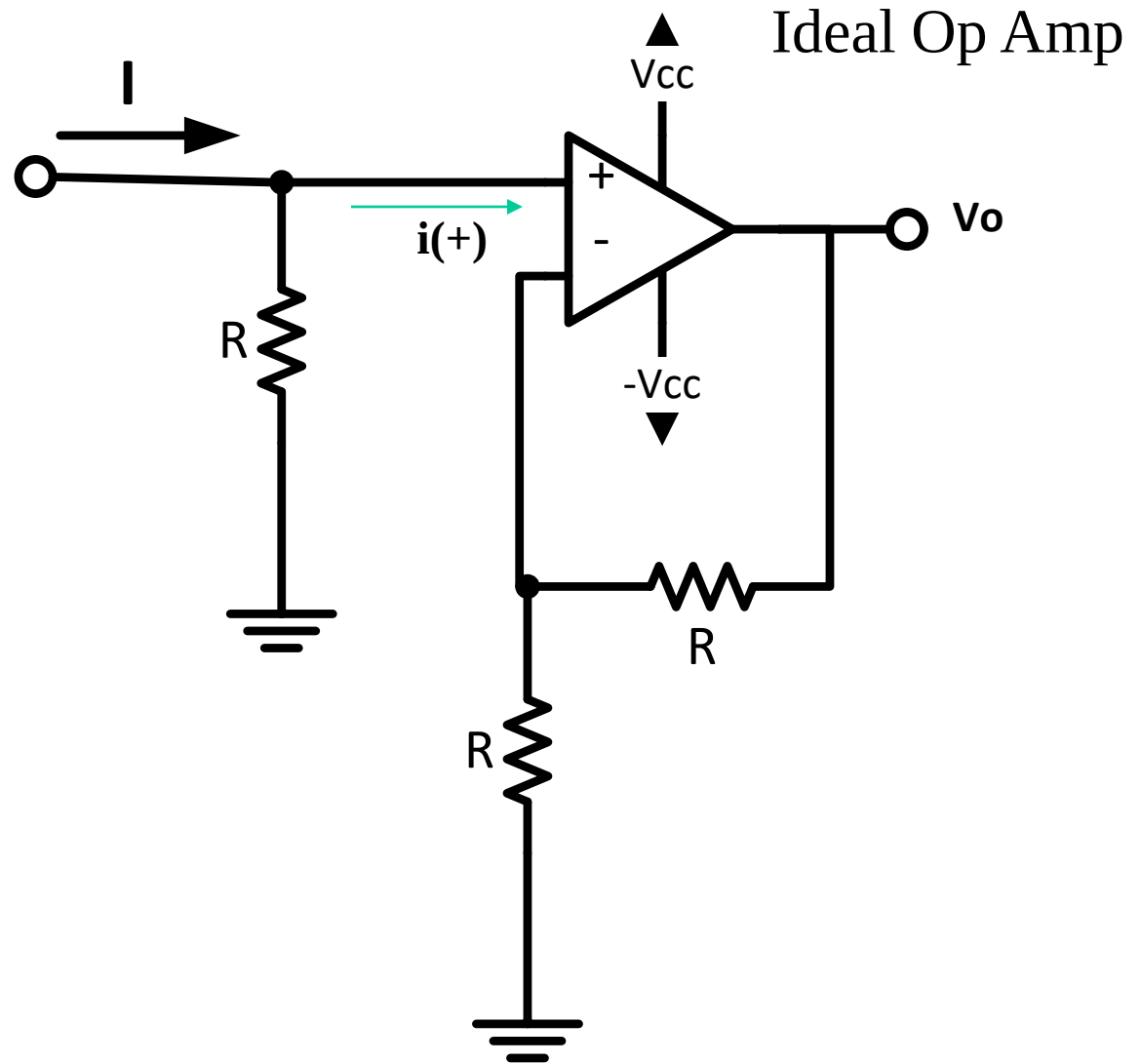

Integrator

- So far, the input and feedback components have been resistors. If the feedback component used is a capacitor, the resulting connection is called an *integrator*.

Since $V(+)=0$; $\therefore V(-)=0$

$$i_{i(t)} = \frac{V_{i(t)}}{R} \quad \text{(Virtual ground)}$$

$$i_{i(t)} = i_{f(t)} = \frac{V_{i(t)}}{R}$$


$$V_o(t) = -V_c(t)$$

$$V_c(t) = \frac{1}{C} \int_0^t i_f(t) dt + V_c(0^-)$$

$$\text{if } V_c(0^-) = 0$$

$$V_o(t) = -\frac{1}{C} \int_0^t \frac{V_i(t)}{R_i} dt$$
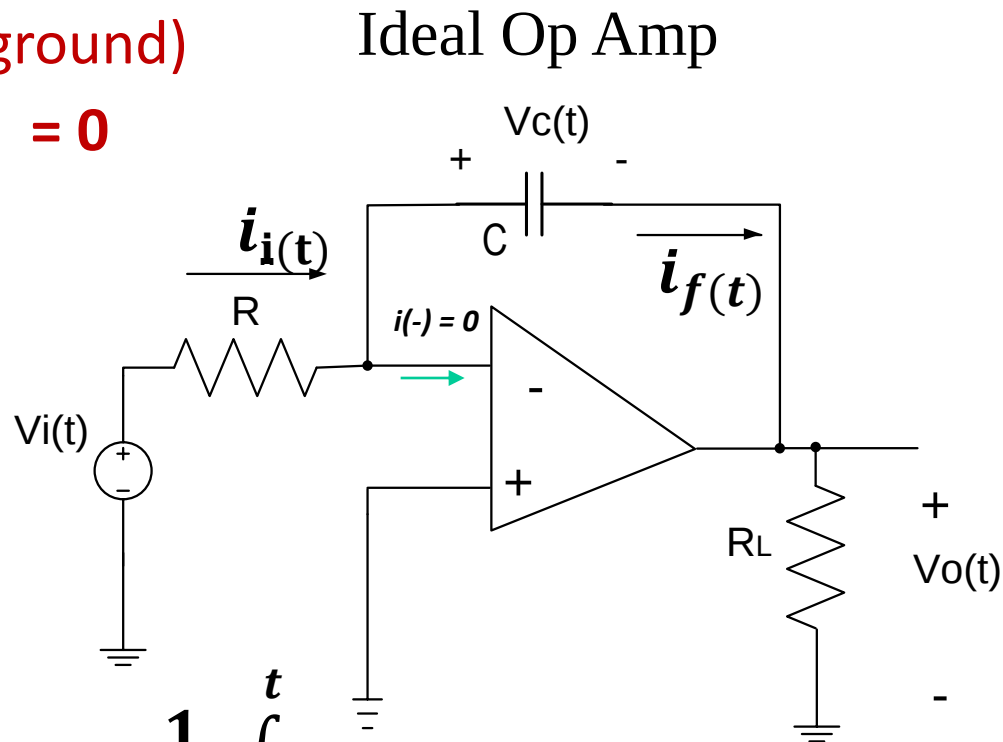
$$V_o(t) = -\frac{1}{RC} \int_0^t V_i(t) dt$$



Differentiator

Since $V(+) = 0$; $\therefore V(-) = 0$

$$i_{i(t)} = i_{C(t)} = C \frac{dV_{i(t)}}{dt}$$


Since $i(-) = 0$

$$i_{C(t)} = i_{f(t)}$$

$$V_{o(t)} = -i_{f(t)}R$$

$$V_{o(t)} = -\left(C \frac{dV_{i(t)}}{dt}\right) (R)$$

$$V_{o(t)} = -RC \frac{dV_{i(t)}}{dt}$$

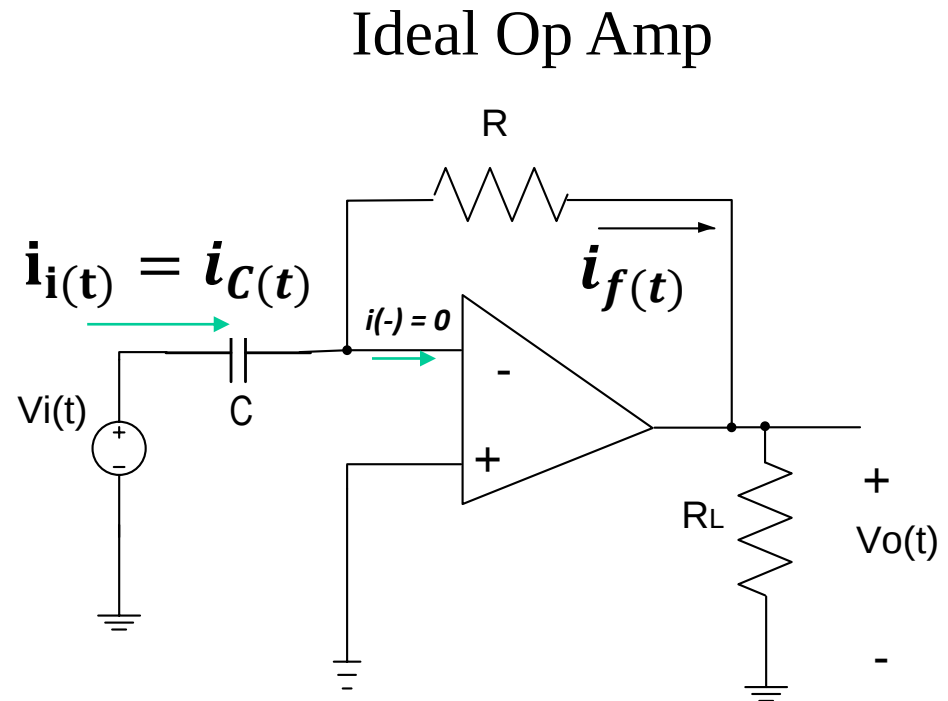

Comparator : Zero –Level detector

Exact analysis:


When $v_d > 65\mu\text{V}$; $V_O = +V_{sat}$

When $v_d < -65\mu\text{V}$; $V_O = -V_{sat}$

Approximate analysis

When $v_d > 0\text{V}$; $V_O = +V_{sat}$



When $v_d < 0\text{V}$; $V_O = -V_{sat}$

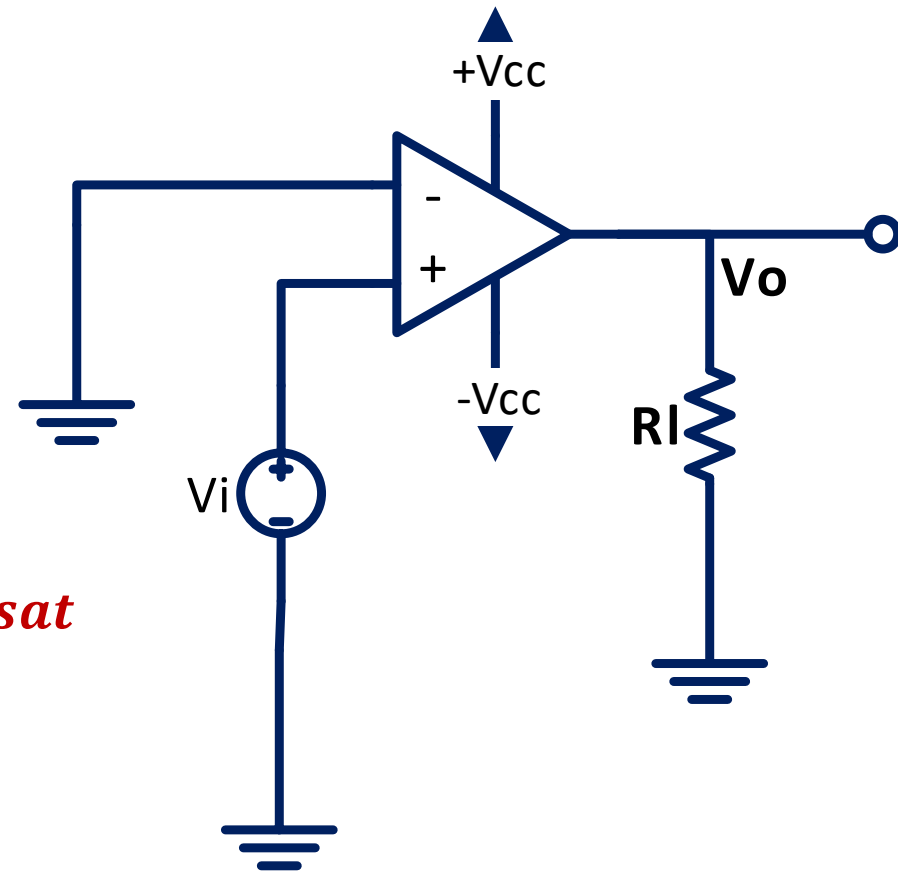

Comparator : Zero –Level detector

$$V_i(t) = 5 \sin \omega t \text{ v}$$

$$\pm V_{sat} = \pm 13 \text{ v}$$

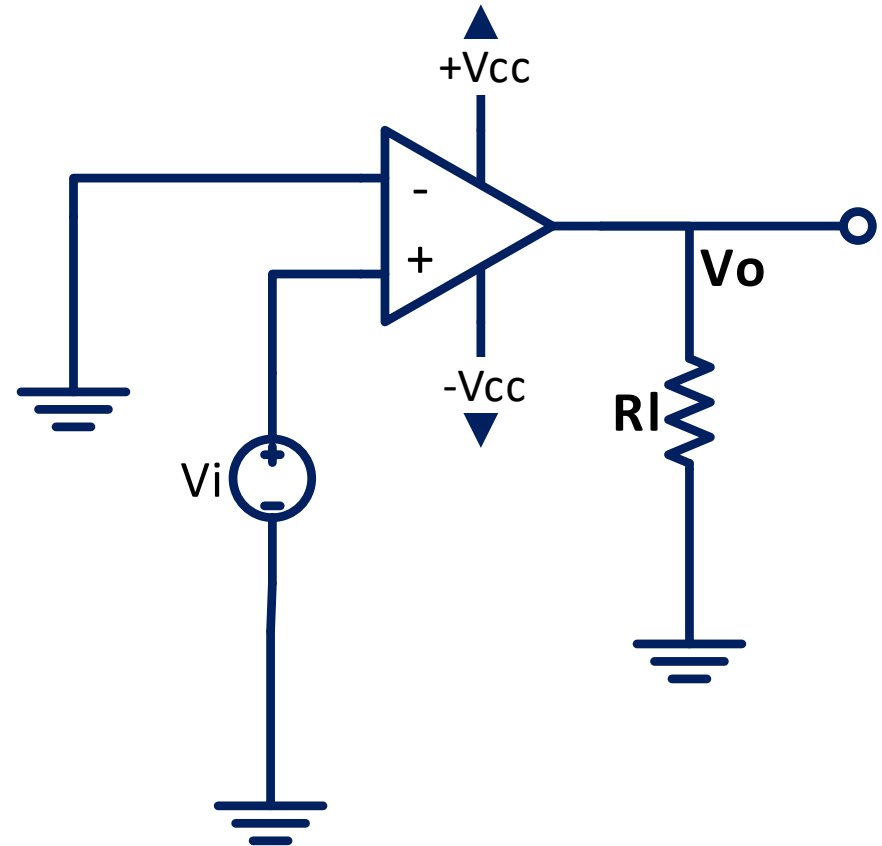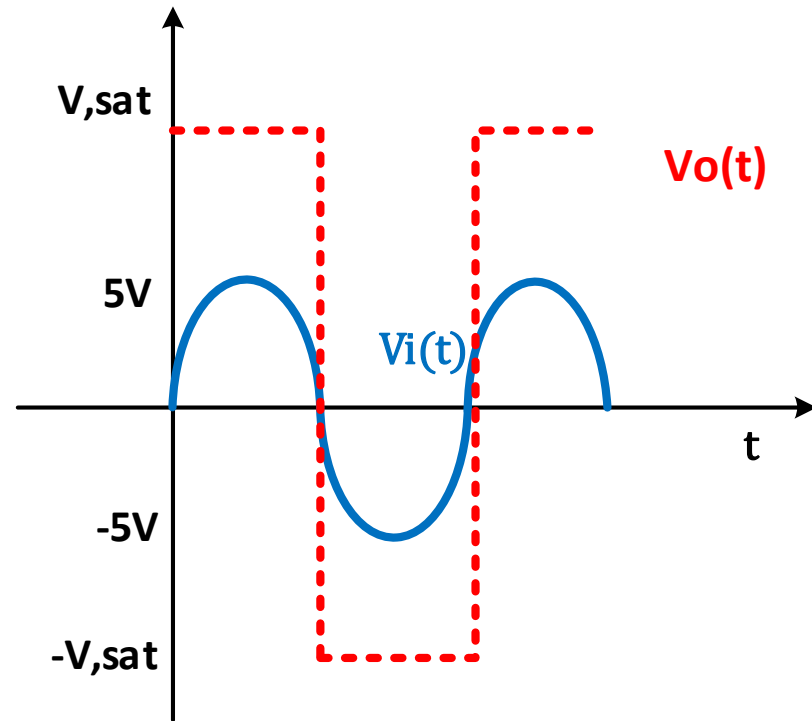

When $v_d > 0V$;

$$V_o = +V_{sat}$$

When $v_d < 0V$;

$$V_o = -V_{sat}$$

$\therefore$ When $V_i > 0V$; $V_o = +V_{sat}$

$$v_d = V_i$$

$\therefore$ When $V_i < 0V$; $V_o = -V_{sat}$



Non Zero –Level detector

$$V_i(t) = 5 \sin \omega t \text{ v}$$

$$\pm V_{sat} = \pm 13 \text{ v}$$

$$\text{When } V_i > 2\text{V} ; \quad V_O = +V_{sat}$$
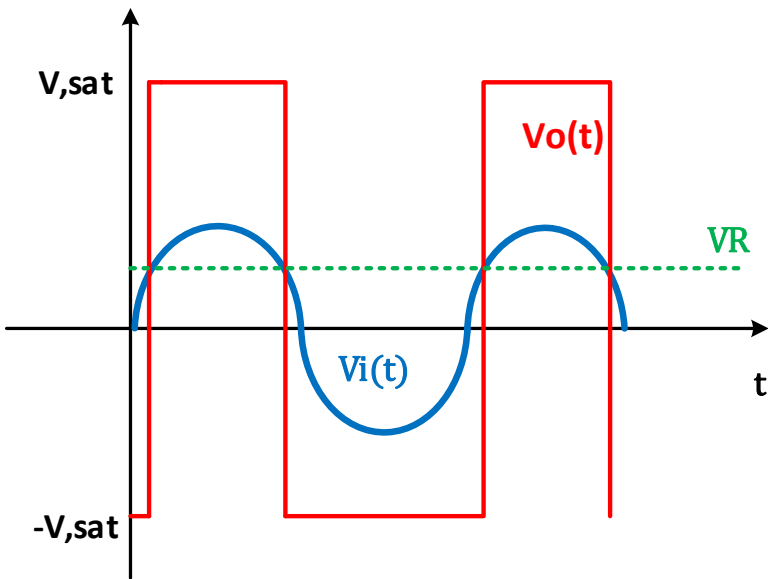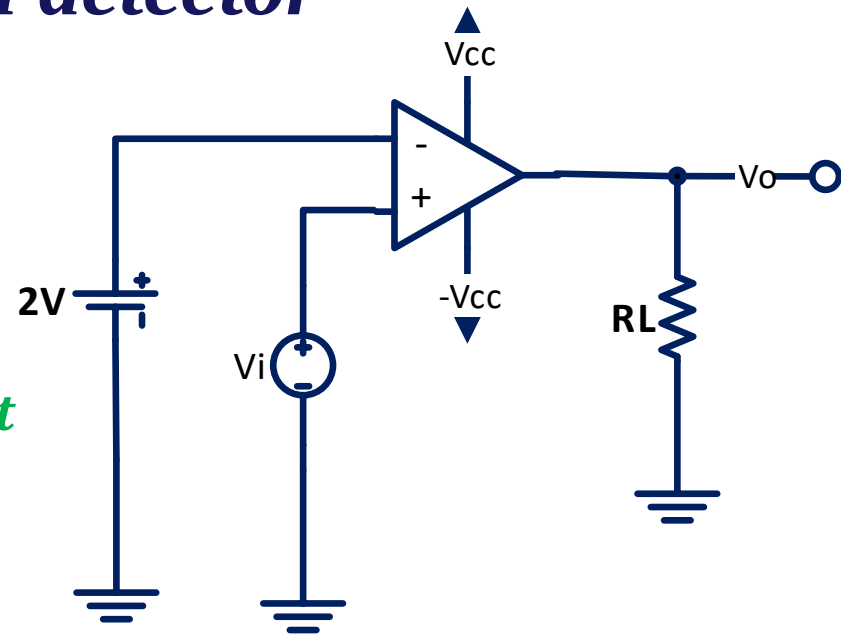
$$\text{When } V_i < 2\text{V} ; \quad V_O = -V_{sat}$$





$$\text{When } v_d > 0\text{V} ; \quad V_O = +V_{sat}$$

$$\text{When } v_d < 0\text{V} ; \quad V_O = -V_{sat}$$

$$v_d = V_i - 2$$

Practical Non Zero –Level detector

Application

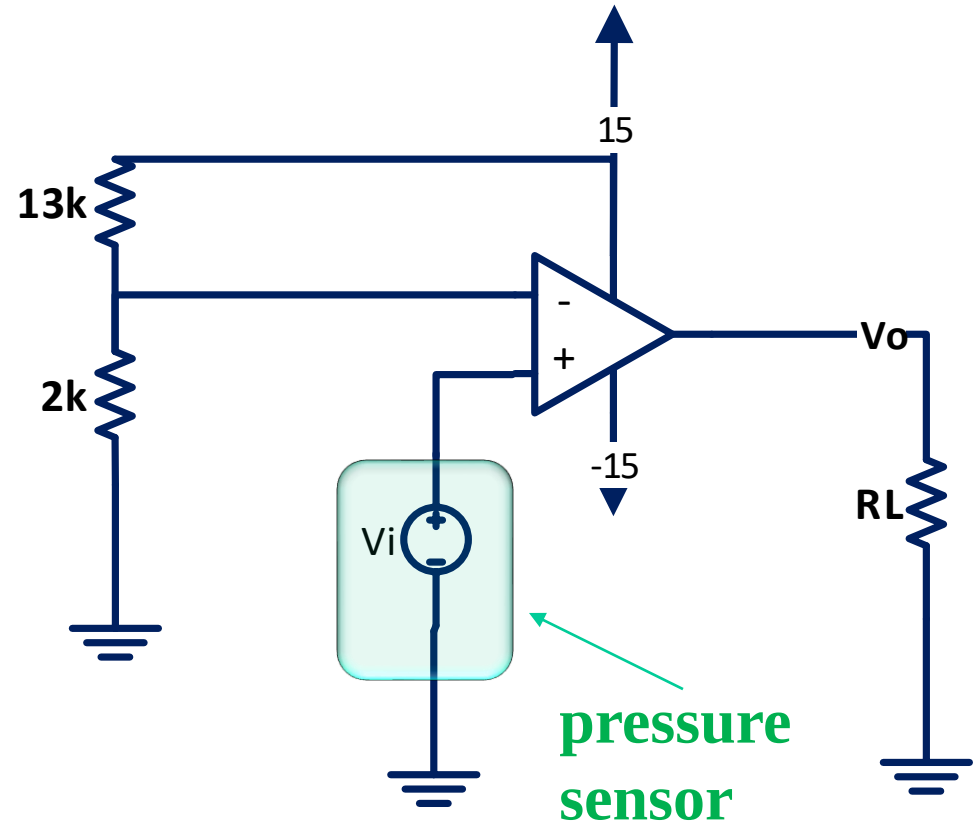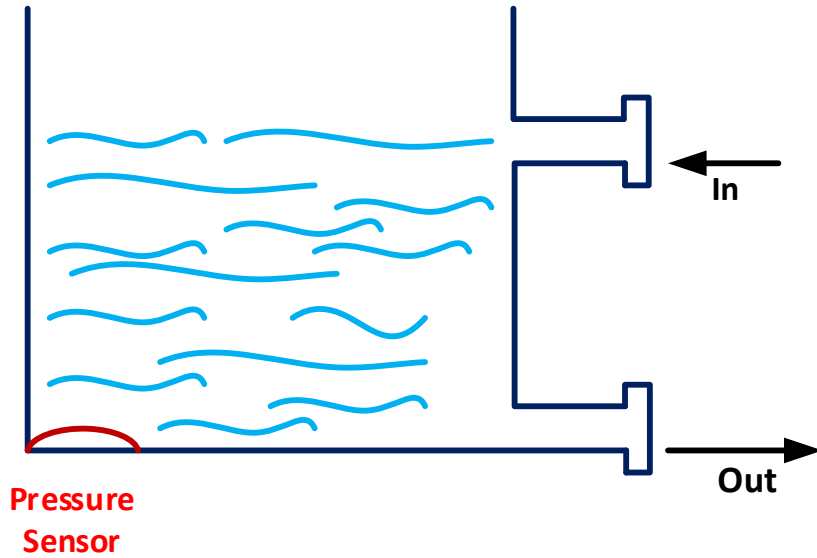

The pressure sensor generates a voltage proportional to the water level in the tank

When water level reaches the maximum allowable level

→ $V_i = 2V$

$$V(-) = 2V$$

When $V_i > 2V$; $V_o = +V_{sat}$
 When $V_i < 2V$; $V_o = -V_{sat}$

Voltage–Level detector with LEDs:

When $V_i > 2V$; $V_o = +V_{sat}$


∴ Red LED is ON

∴ green LED is OFF

When $V_i < 2V$; $V_o = -V_{sat}$

∴ green LED is ON

∴ Red LED is OFF

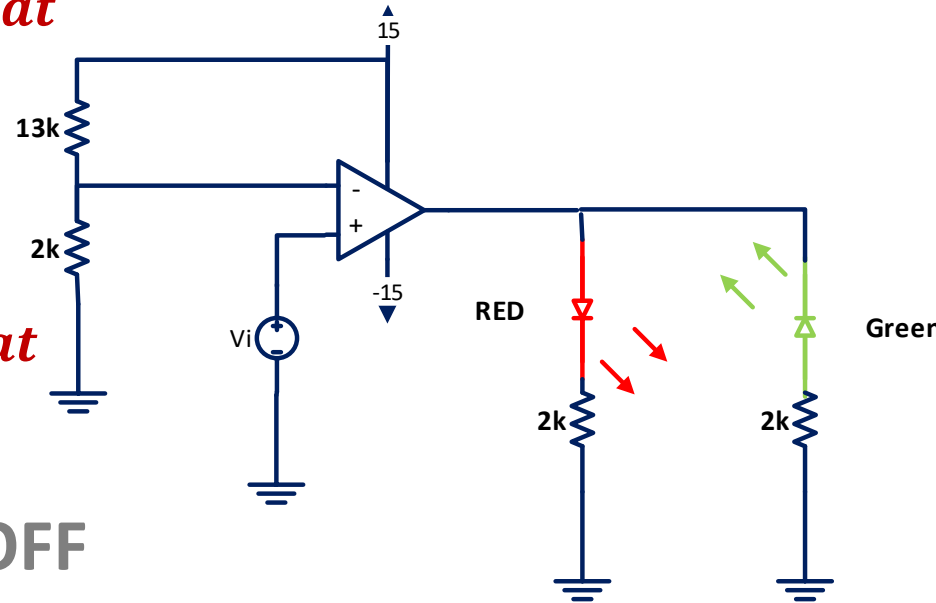

When $V_i = 2V$; $V_o = 0$

∴ green LED and the Red LED are OFF

Over Temperature sensing Circuit



$R1 \uparrow$ as $T \downarrow$

R1 = Resistance of the thermistor.

R2 is set equal to the resistance of the thermistor at the critical temp.

R = 100k

This is the thermistor

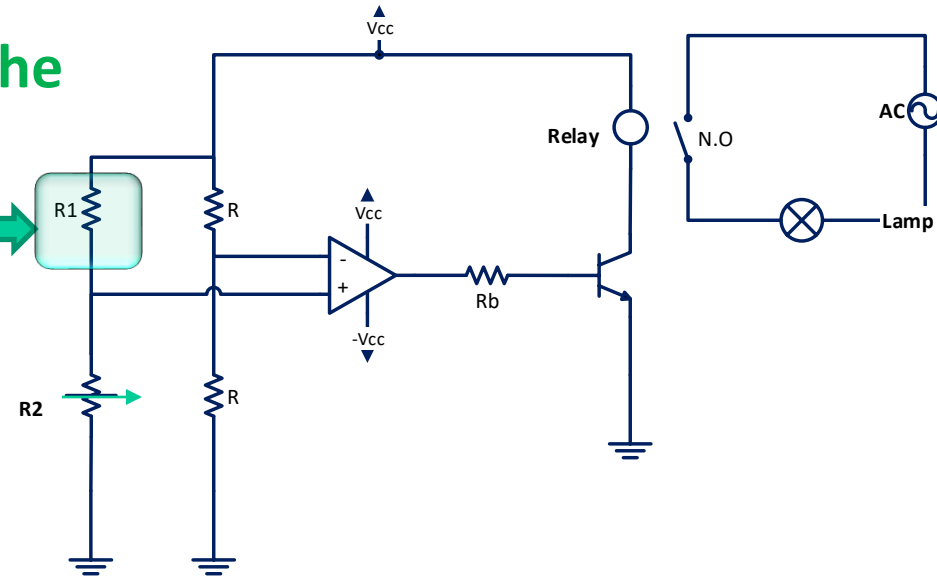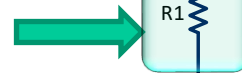

1) At Normal temperature ($T < T_c$)

$$R_1 > R_2$$

$$V(+) = \frac{R_2}{R_1 + R_2} V_{CC} < \frac{1}{2} V_{CC}$$

$$V(-) = \frac{1}{2} V_{CC}$$

$$\therefore V(-) > V(+) , \therefore V_{op} = -V_{sat}$$

$$\therefore \text{transistor is cut off} ; I_C = 0$$

$\therefore$ Relay is denenergized

$\therefore$ switch is open

$\therefore$ Lamp is OFF

Over Temperature sensing Circuit

2) When $T = T_c$

$$R_1 = R_2$$

$$V(+) = V(-) = \frac{1}{2} V_{cc}$$

$$\therefore V_{op} = 0$$


$\therefore$ transistor is in cut off ;

$$I_C = 0$$

$\therefore$ Relay is denenergized

$\therefore$ switch is open

$\therefore$ Lamp is OFF

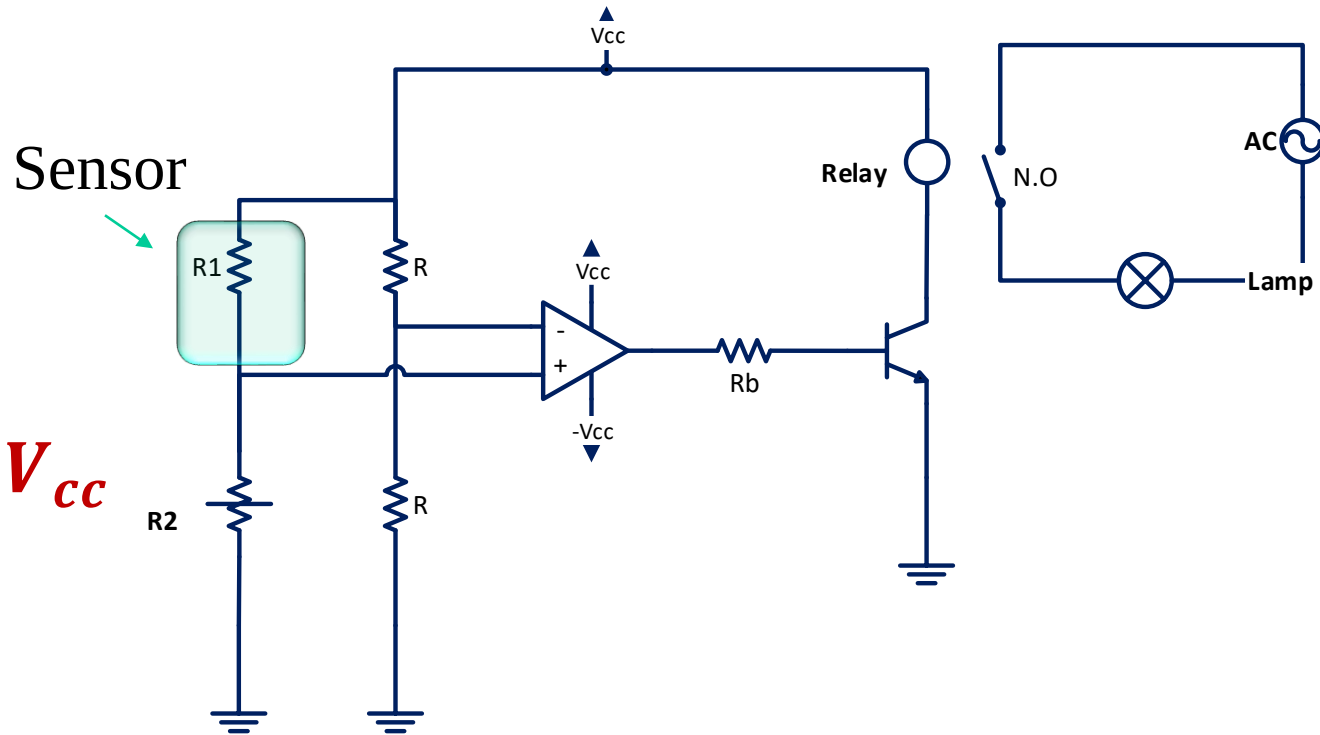

Over Temperature sensing Circuit

3- When $T > T_c$


$$R_1 < R_2$$

$$V(+) = \frac{R_2}{R_1 + R_2} V_{cc} > \frac{1}{2} V_{cc}$$

$$V(-) = \frac{1}{2} V_{cc}$$

$$\therefore V(+) > V(-)$$

$$\therefore V_{op} = +V_{sat}$$

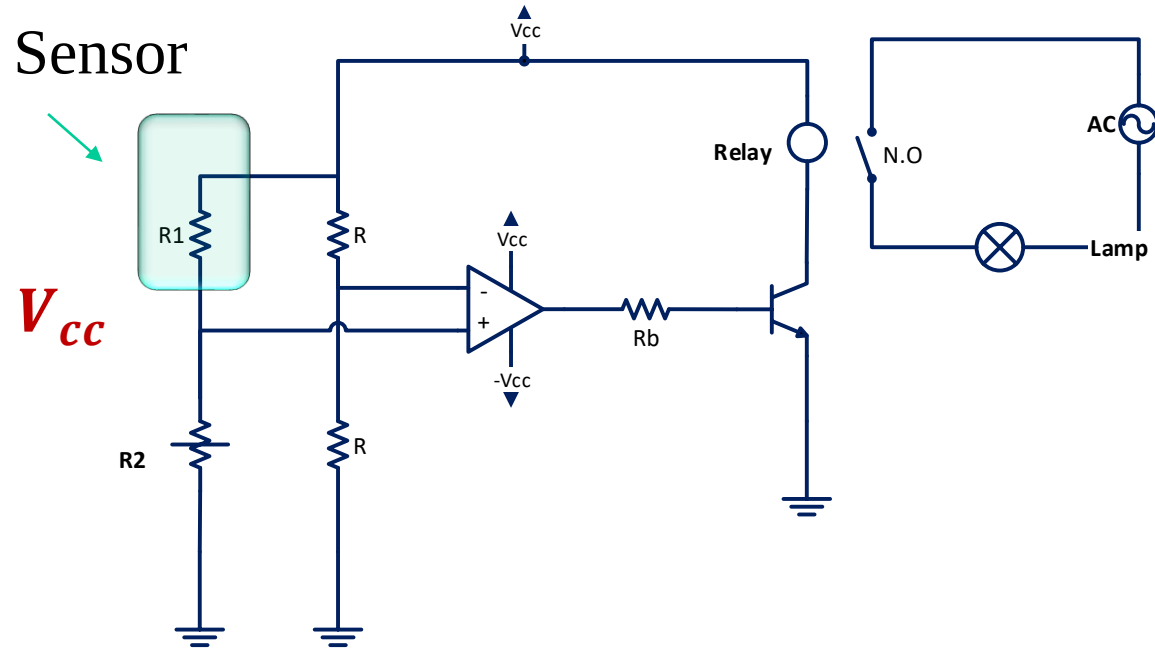

$\therefore$ transistor is conducting

$\therefore$ Relay is energized

$\therefore$ Lamp is on

Schmitt Trigger Comparator

1. Assume $V_O = +V_{sat}$

$$V(-) = V_i$$

$$V(+) = \frac{R_2}{R_1 + R_2} (+V_{sat}) = V_{UT}$$

$$v_d > 0$$

$$\frac{R_2}{R_1 + R_2} (+V_{sat}) - V_i > 0$$


$$\therefore V_i < \frac{R_2}{R_1 + R_2} (+V_{sat})$$

$$\therefore \text{as long as } V_i < \frac{R_2}{R_1 + R_2} (+V_{sat})$$


$$V_O = +V_{sat}$$

But when $V_i > \frac{R_2}{R_1 + R_2} (+V_{sat})$

$$V_O \text{ switch to } (-V_{sat})$$

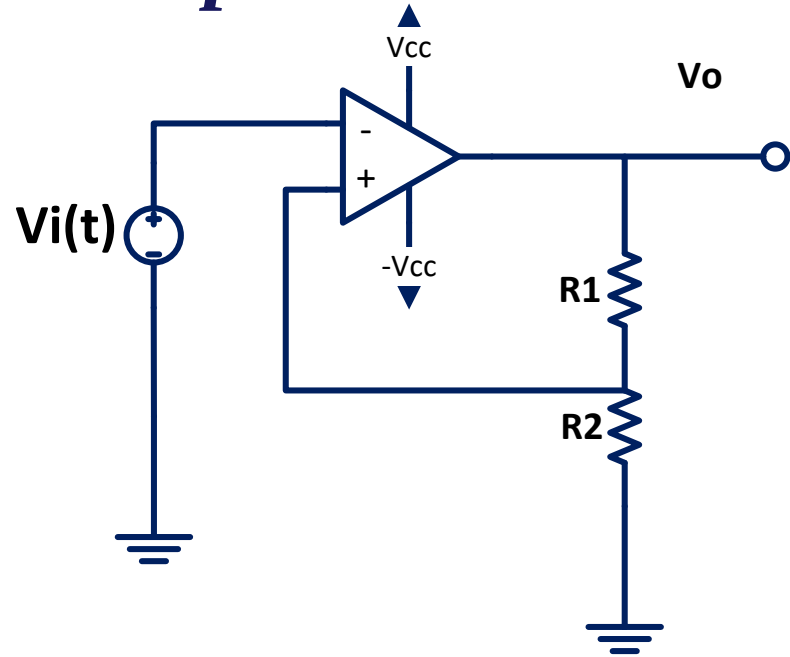

Inverting Schmitt trigger comparator

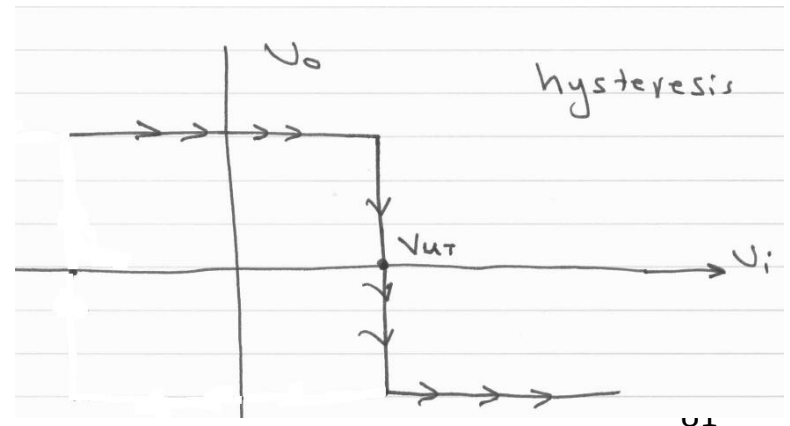

Schmitt Trigger Comparator

2. Assume $V_O = -V_{sat}$

$$V(-) = V_i$$

$$V(+) = \frac{R_2}{R_1 + R_2} (-V_{sat}) = V_{LT}$$

$$v_d < 0$$

$$\frac{R_2}{R_1 + R_2} (-V_{sat}) - V_i < 0$$



$$\therefore V_i > \frac{R_2}{R_1 + R_2} (-V_{sat})$$

$$\therefore \text{as long as } V_i > \frac{R_2}{R_1 + R_2} (-V_{sat})$$

$$V_O = -V_{sat}$$

But when $V_i < \frac{R_2}{R_1 + R_2} (-V_{sat})$

V_O switch to $(+V_{sat})$

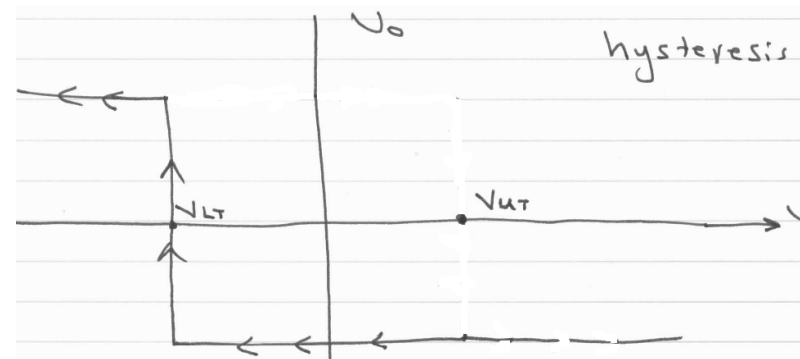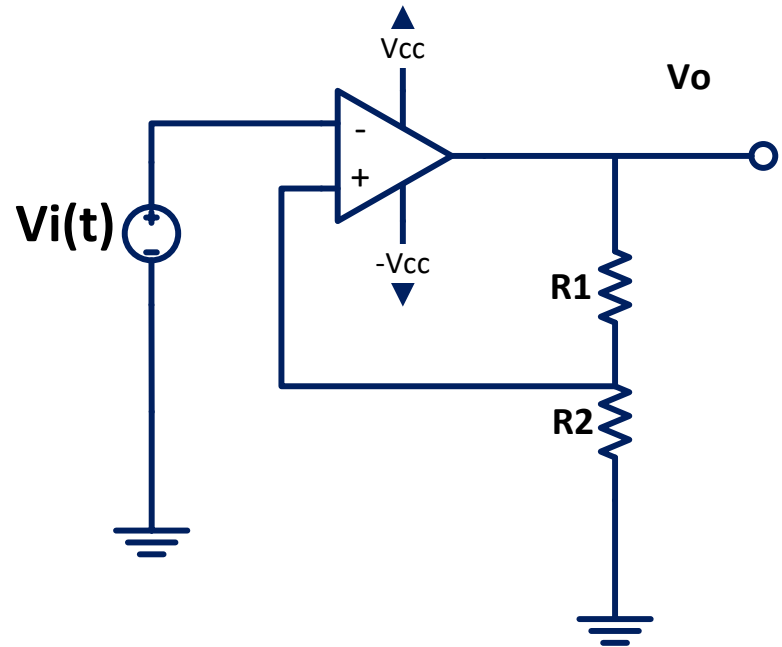

Schmitt Trigger Comparator


Hysteresis voltage $\equiv V_H = V_{UT} - V_{LT}$

$V_{UT} \equiv$ Upper Threshold voltage

$$V_{UT} = \frac{R_2}{R_1 + R_2} (+V_{sat})$$


$V_{LT} \equiv$ Lower Threshold voltage
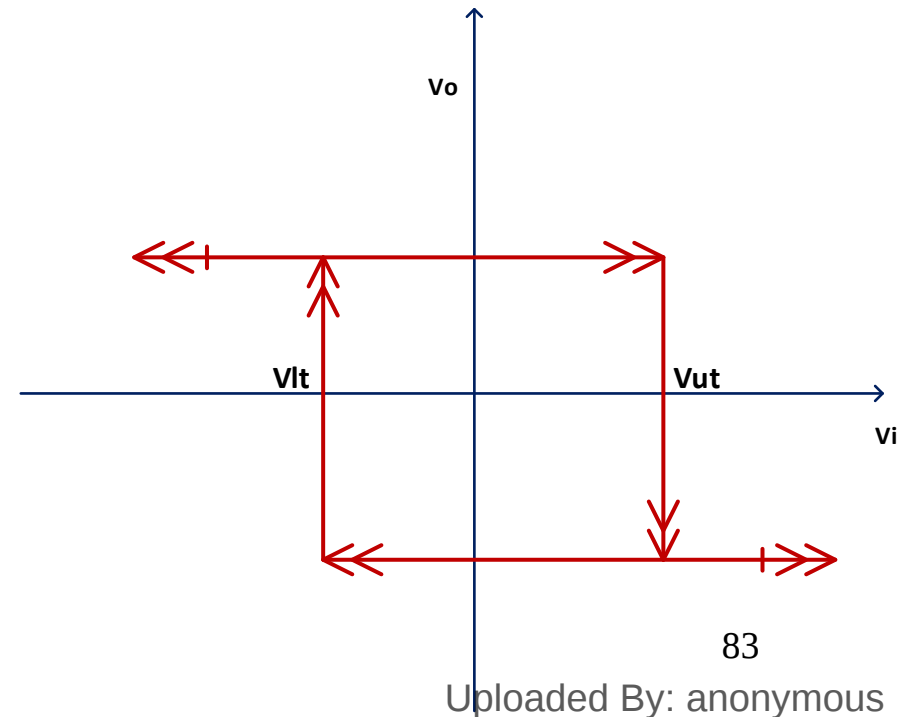
$$V_{LT} = \frac{R_2}{R_1 + R_2} (-V_{sat})$$




Schmitt Trigger Comparator

Signal Wave form

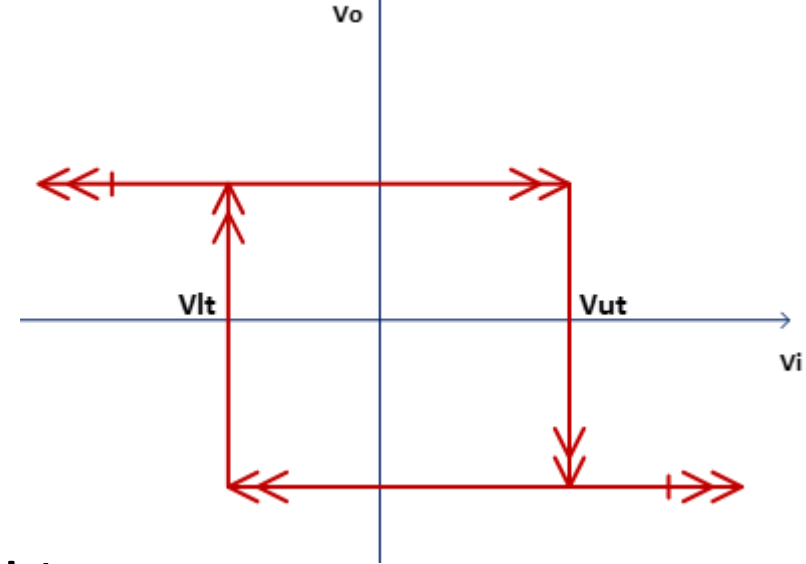


when $V_i < \frac{R_2}{R_1 + R_2} (-V_{sat})$
 V_o switch to $(+V_{sat})$

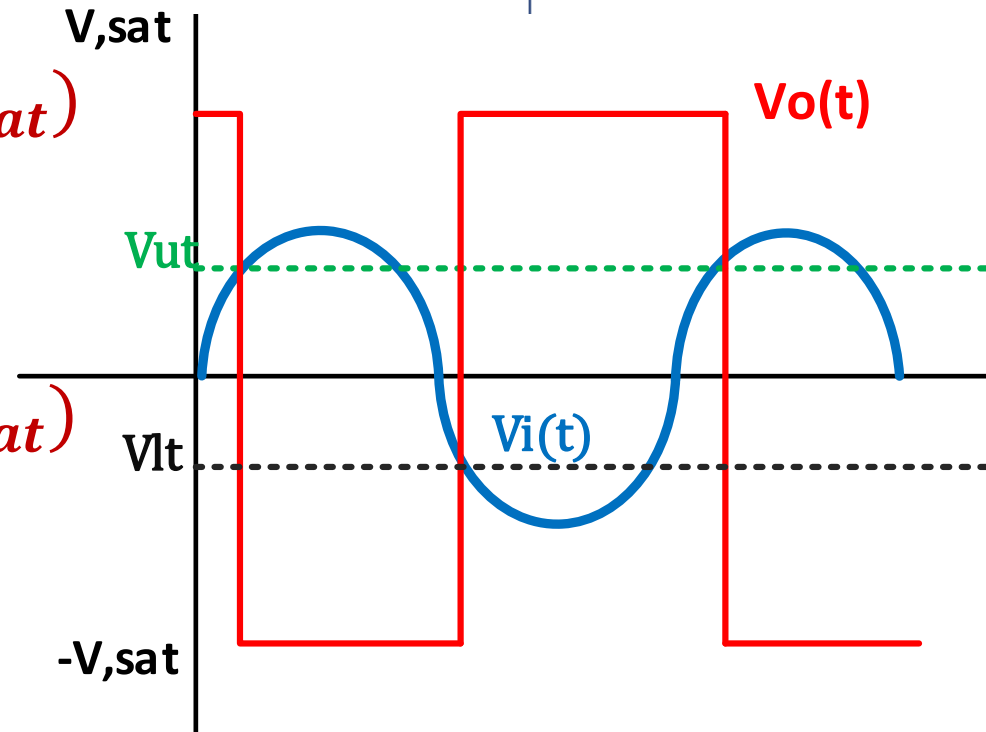
when $V_i > \frac{R_2}{R_1 + R_2} (+V_{sat})$
 V_o switch to $(-V_{sat})$



Room Thermostat

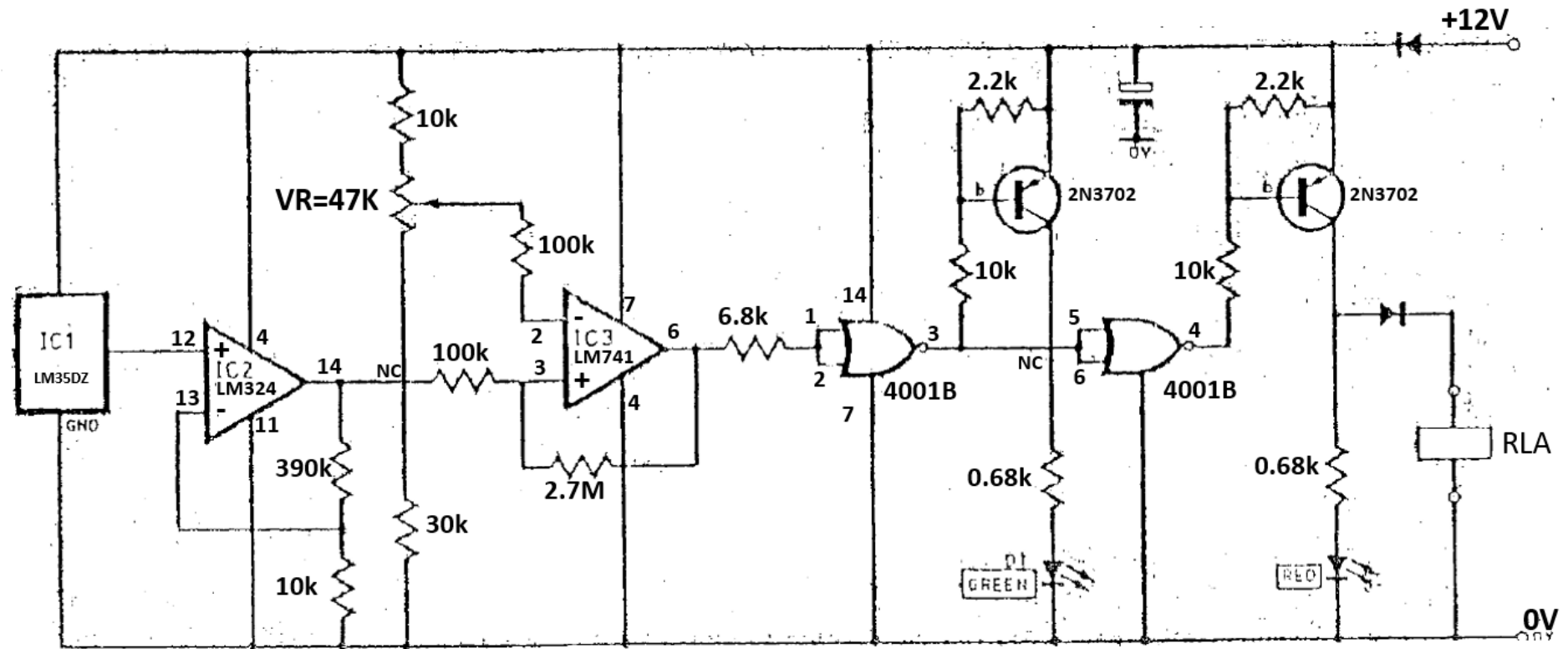


Room Thermostat

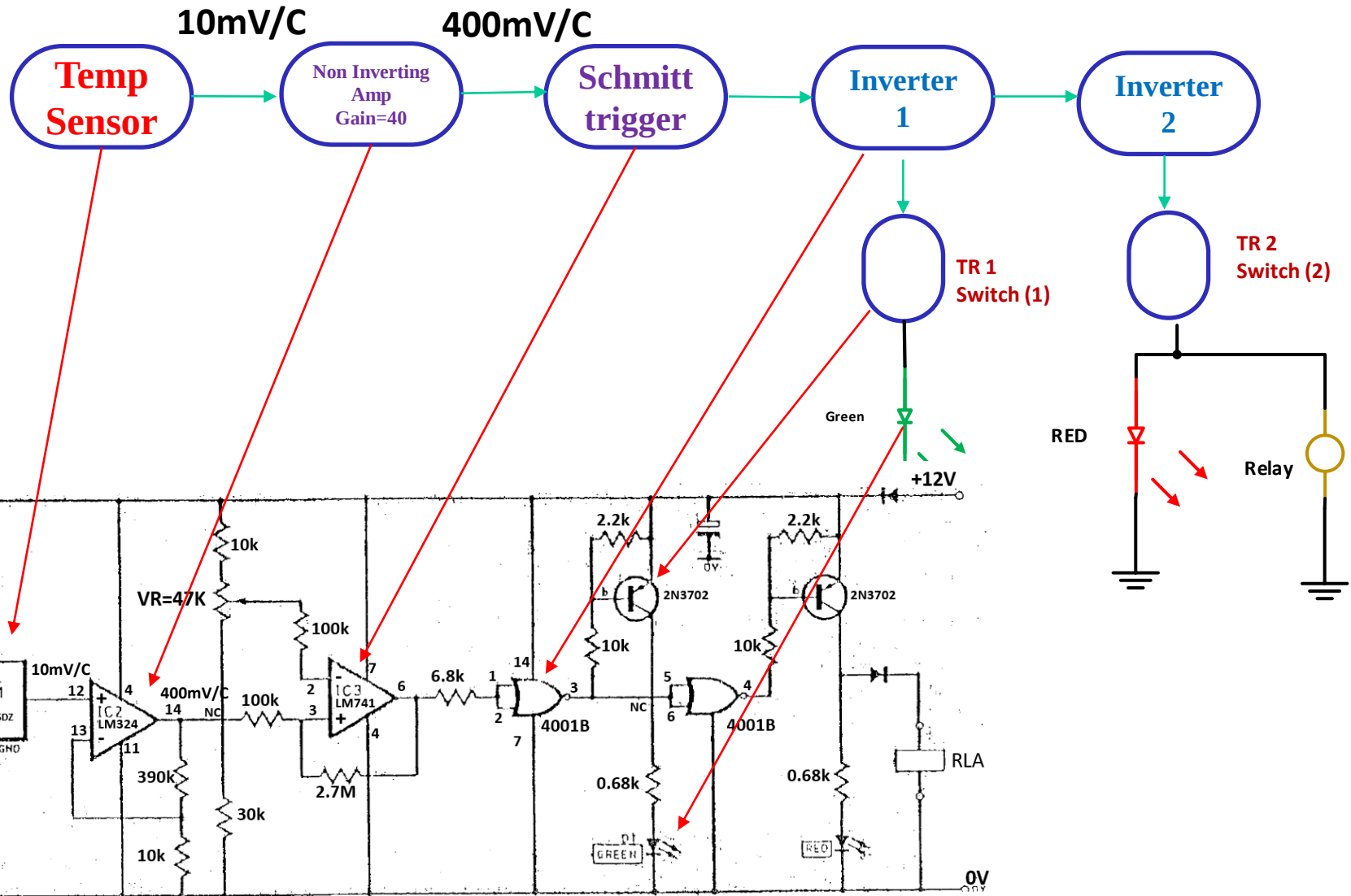

Schmitt Trigger Comparator

Room Thermostat

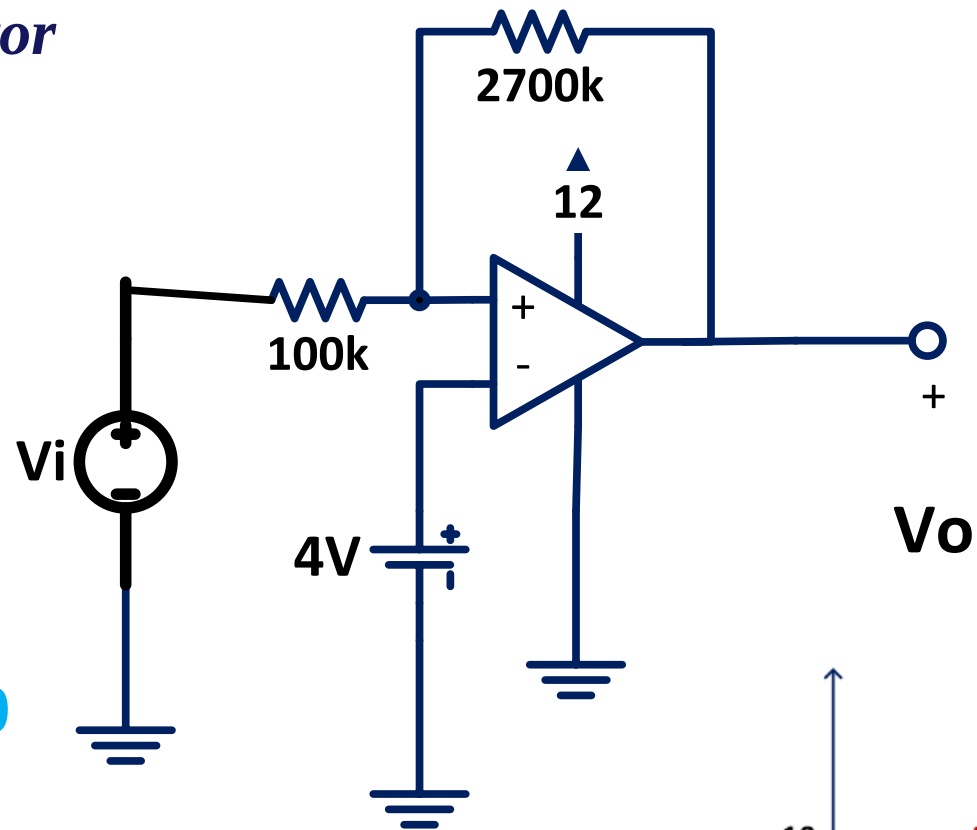

$$V_i = 400\text{mV/C}$$

$$1. \text{ Let } V_O = +V_{sat} = +10$$

$$v_d > 0$$


$$V(-) = 4\text{v}$$

$$V(+) = \frac{100K}{100K+2700K} (+V_{sat}) + \frac{2700K}{2700K+100K} V_i$$

$$\text{For } v_d > 0 ; V_i > 3.777\text{V}$$


$$\therefore \text{ As long as } V_i > 3.777\text{V} ; V_O = +V_{sat}$$
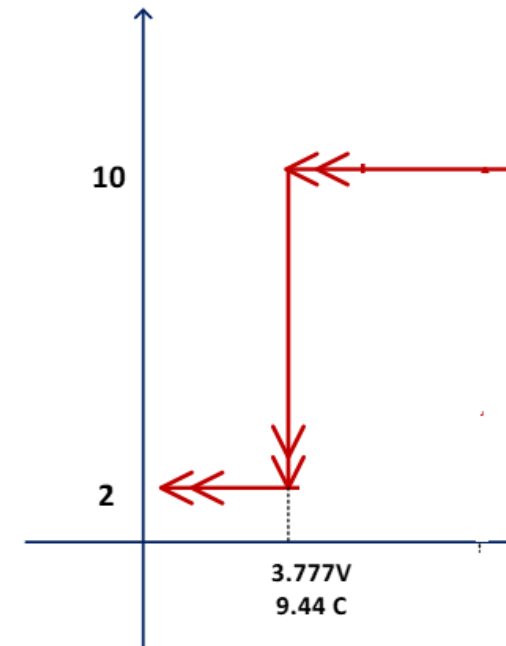
$$\text{But when } V_i < 3.777\text{V} ; V_O \text{ switch to } (-V_{sat})$$



87

Schmitt Trigger Comparator

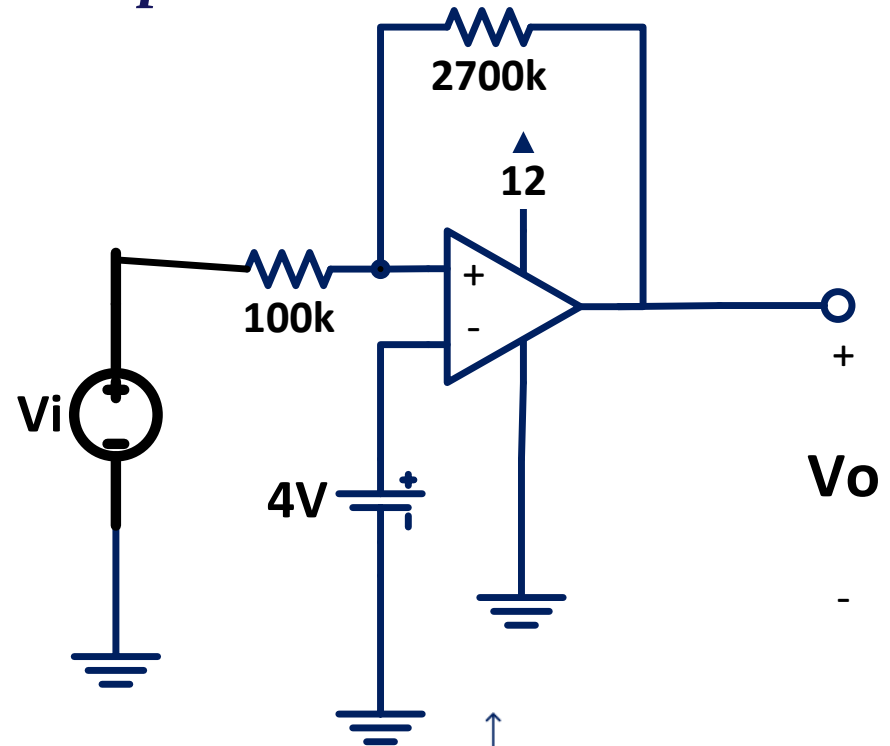

2. Let $V_O = -V_{sat} = +2$


$v_d < 0$

$V(-) = 4V$

$$V(+) = \frac{100K}{100K+2700K} (-V_{sat}) + \frac{2700K}{2700K+100K} V_i$$

For $v_d < 0$; $V_i < 4.072V$

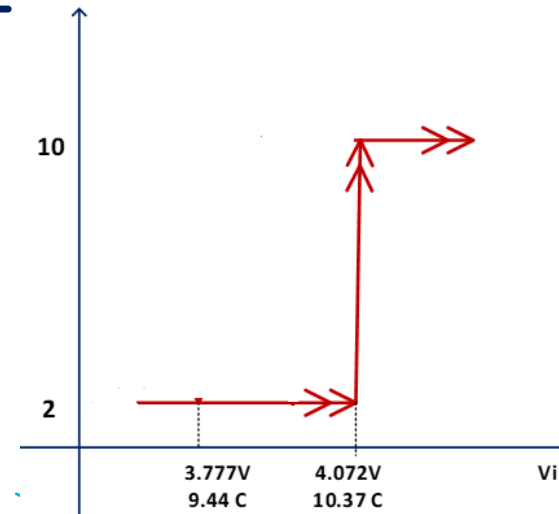$\therefore$ As long as $V_i < 4.072V$; $V_O = -V_{sat}$
 But when $V_i > 4.072V$; V_O switch to $(+V_{sat})$



Schmitt Trigger Comparator

1) When $T > 10.37^\circ\text{C}$, $V_o = +V_{sat}$
Transistor (2) is Off, Relay is
denergized and Heater is Off.

2) Then $T < 9.44^\circ\text{C}$, $V_o = -V_{sat}$
Transistor (2) is On, Relay is
energized and Heater is on.

