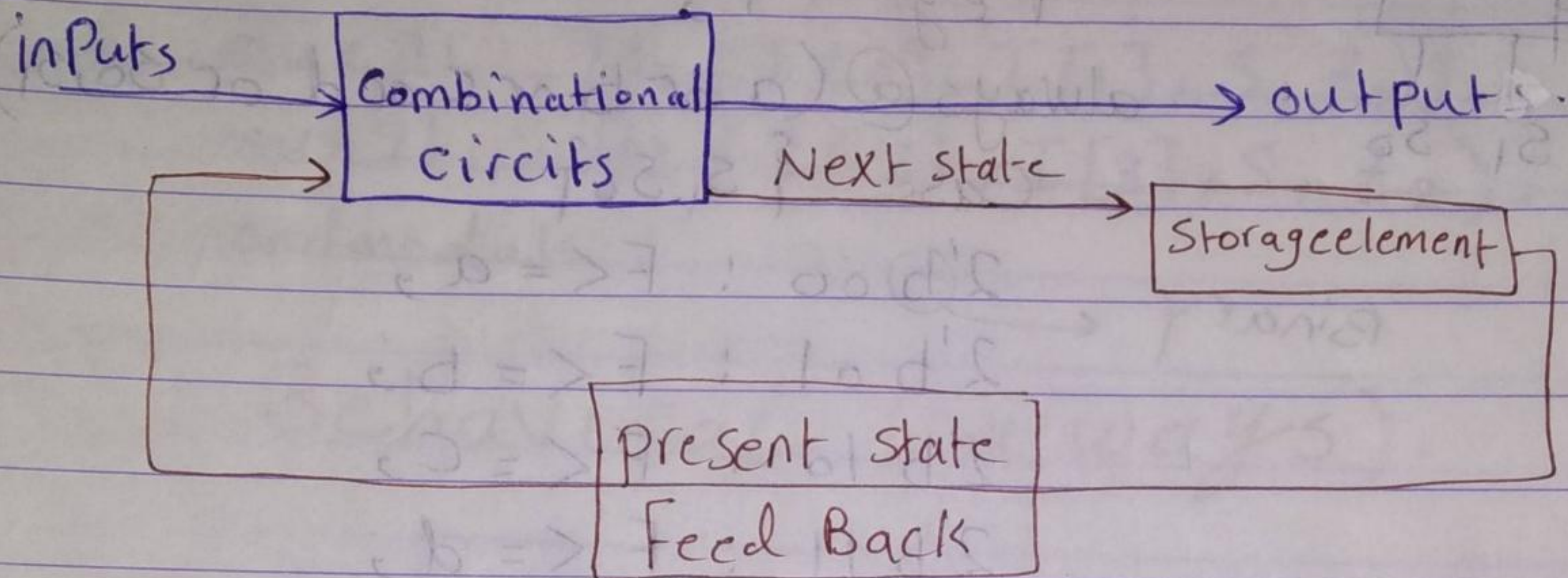



Chapter 5

مزامن Synchronous Sequential Circuits




* outputs depends on inputs and previous outputs.


Electrical circuits.

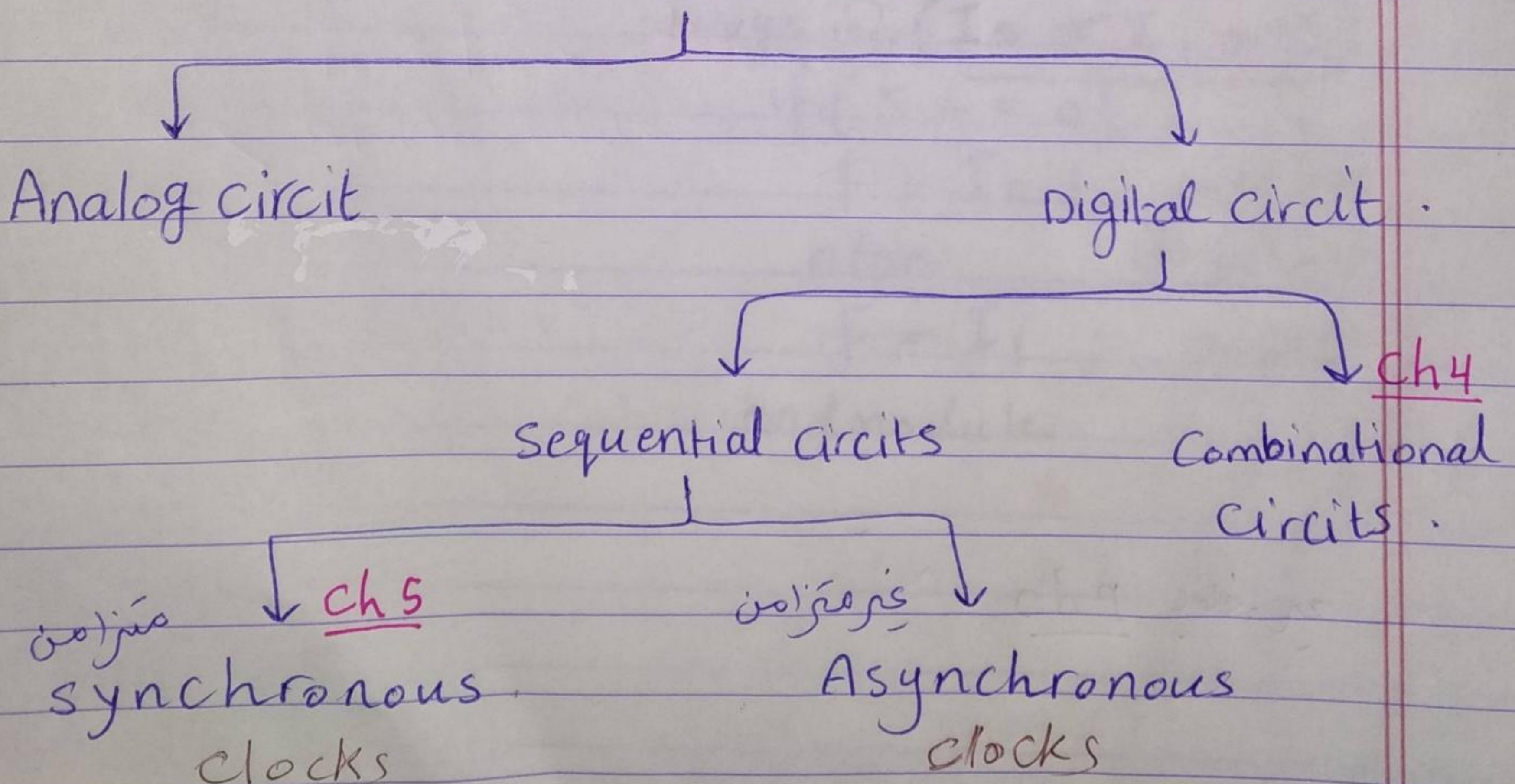

* Synchronous Sequential circuit :-

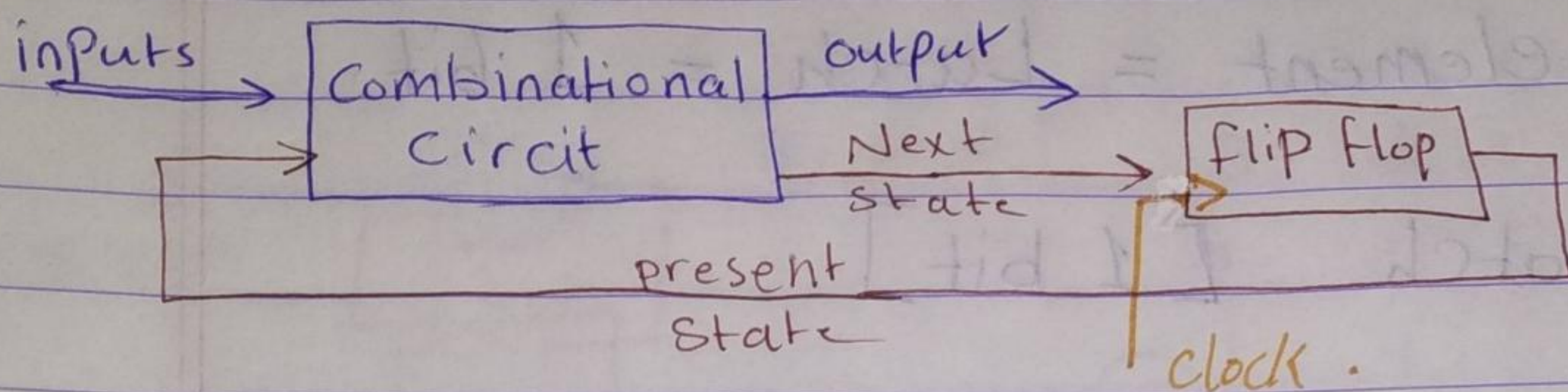

Flip flop = memory 1 bit.

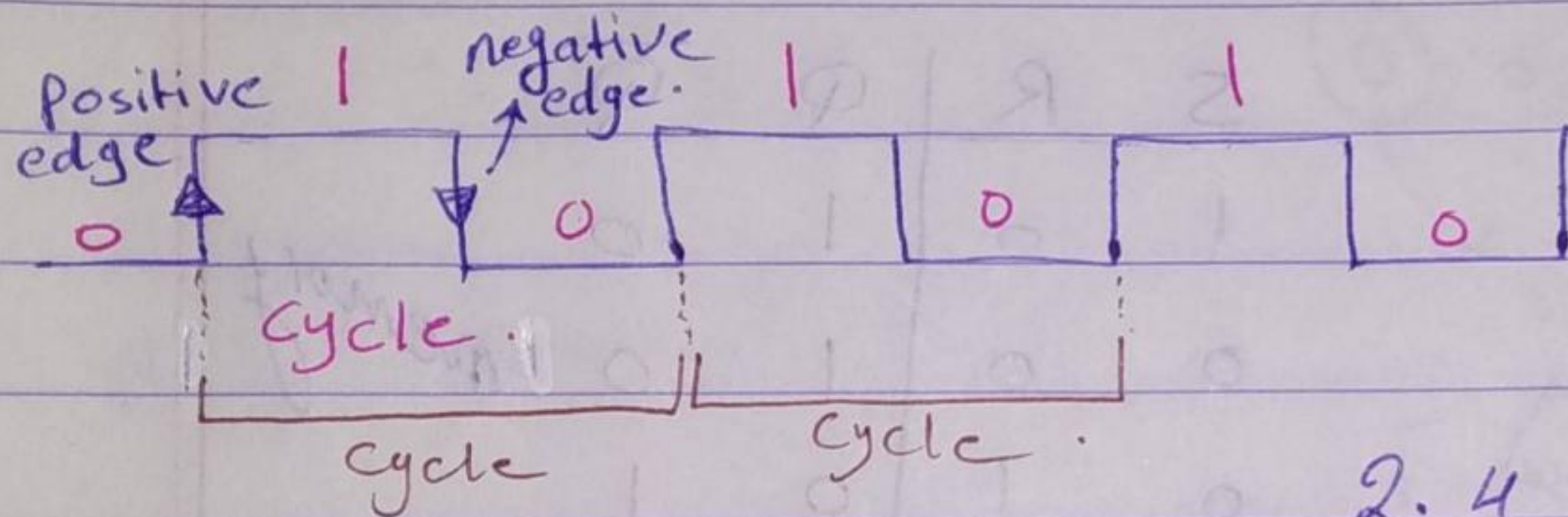



$$2.4 \text{ GHz} = 2.4 \times 10^9 \frac{1}{s}$$

$$\text{frequency} = \frac{1}{\text{Time}}$$

* positive edge :- $1 \leftarrow 0$ or $0 \leftarrow 1$

* Negative edge :- $0 \leftarrow 1$ or $1 \leftarrow 0$


* Asynchronous Circuits :-

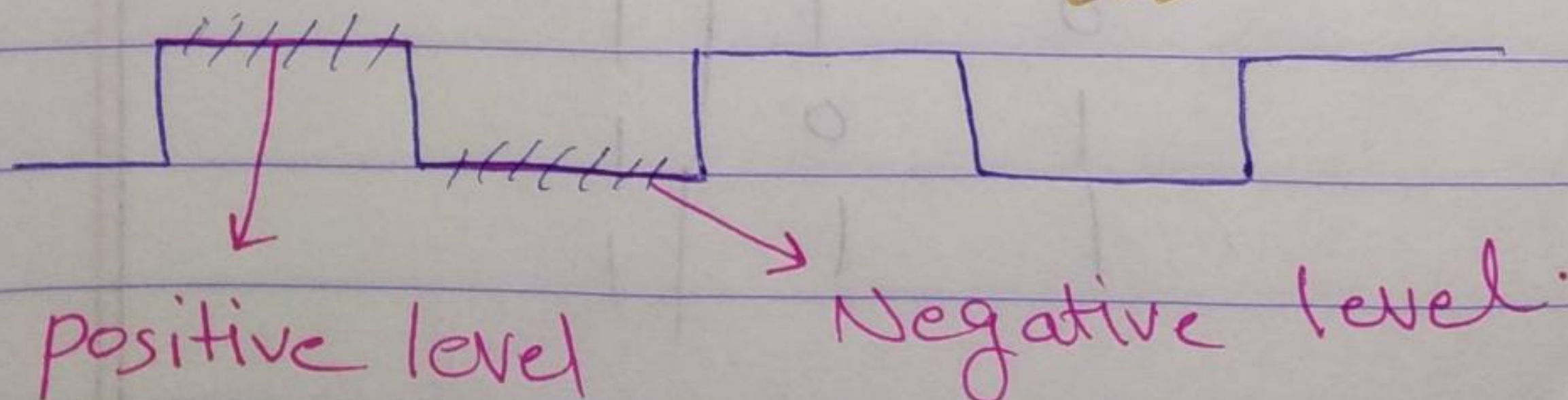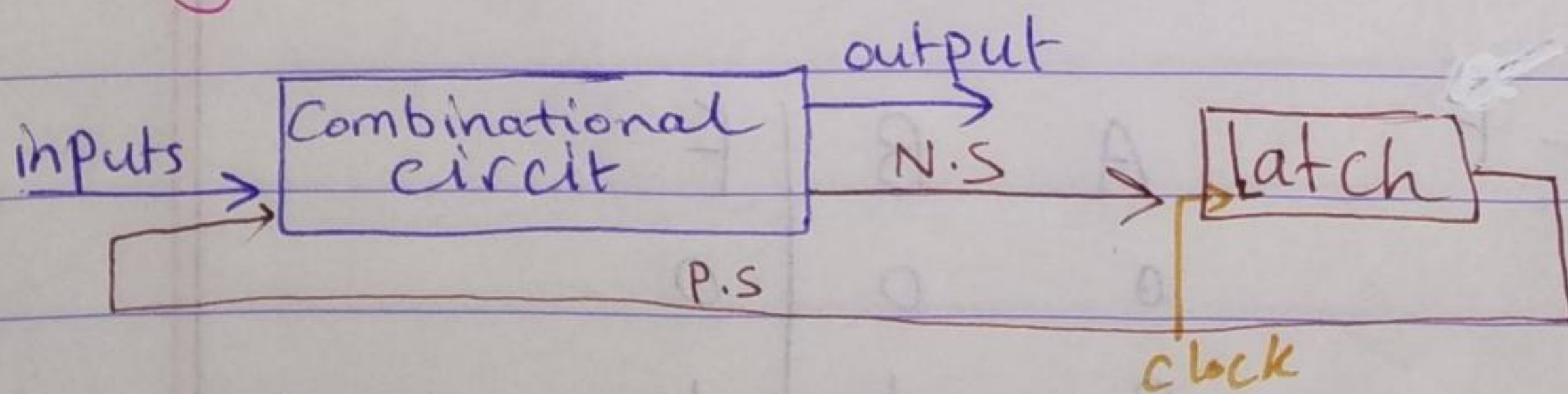

* Asynchronous Circuit :-

memory element = Latch = 1 bit.

① SR-latch [1 bit]

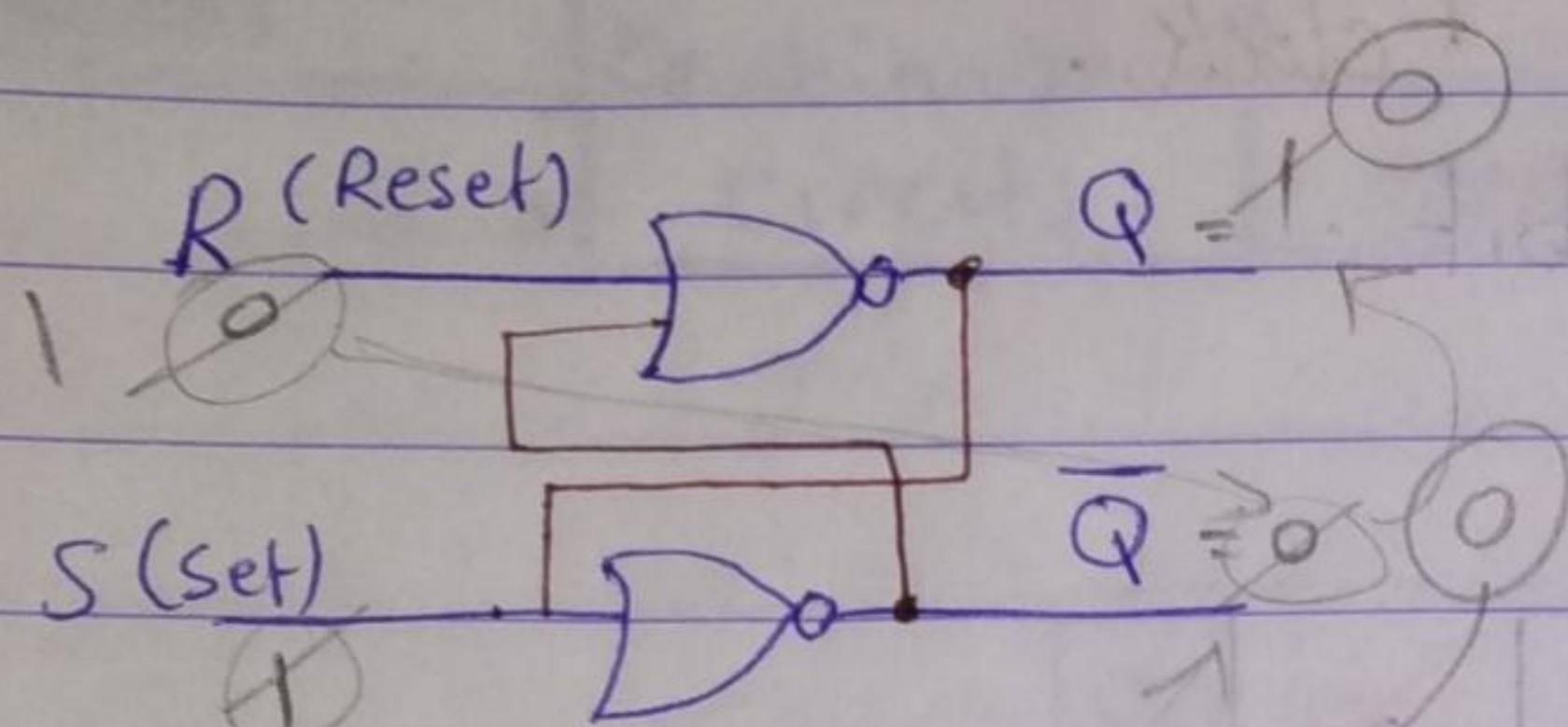

feed back \rightarrow P.S

| S | R | Q | \bar{Q} |
|---|---|---|-----------|
| 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |


memory

memory

[forbidden]


✓ Function Table

X truth table

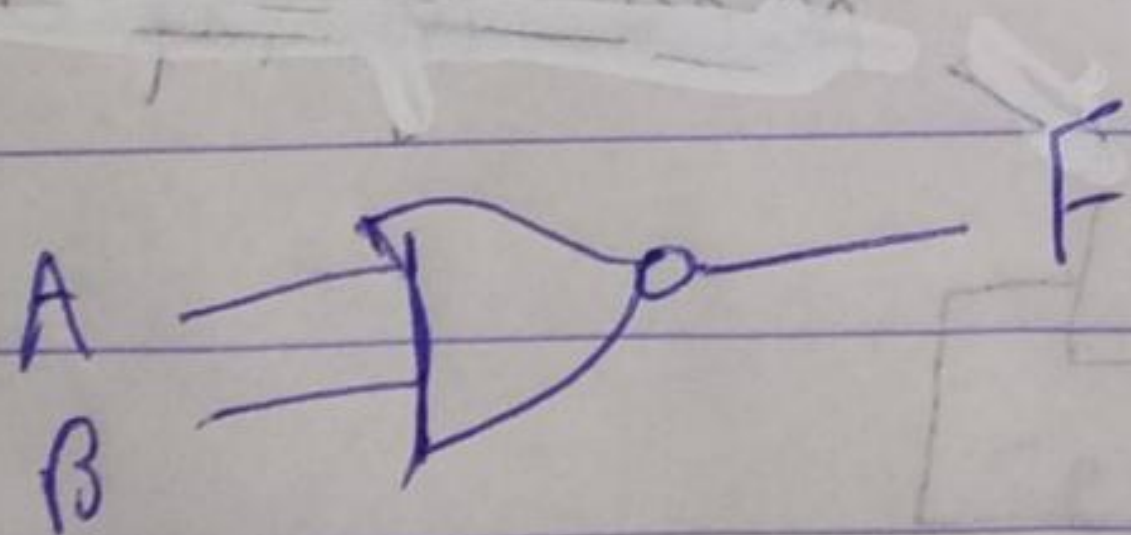


| A | B | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

② SR-Latch with NAND gate.

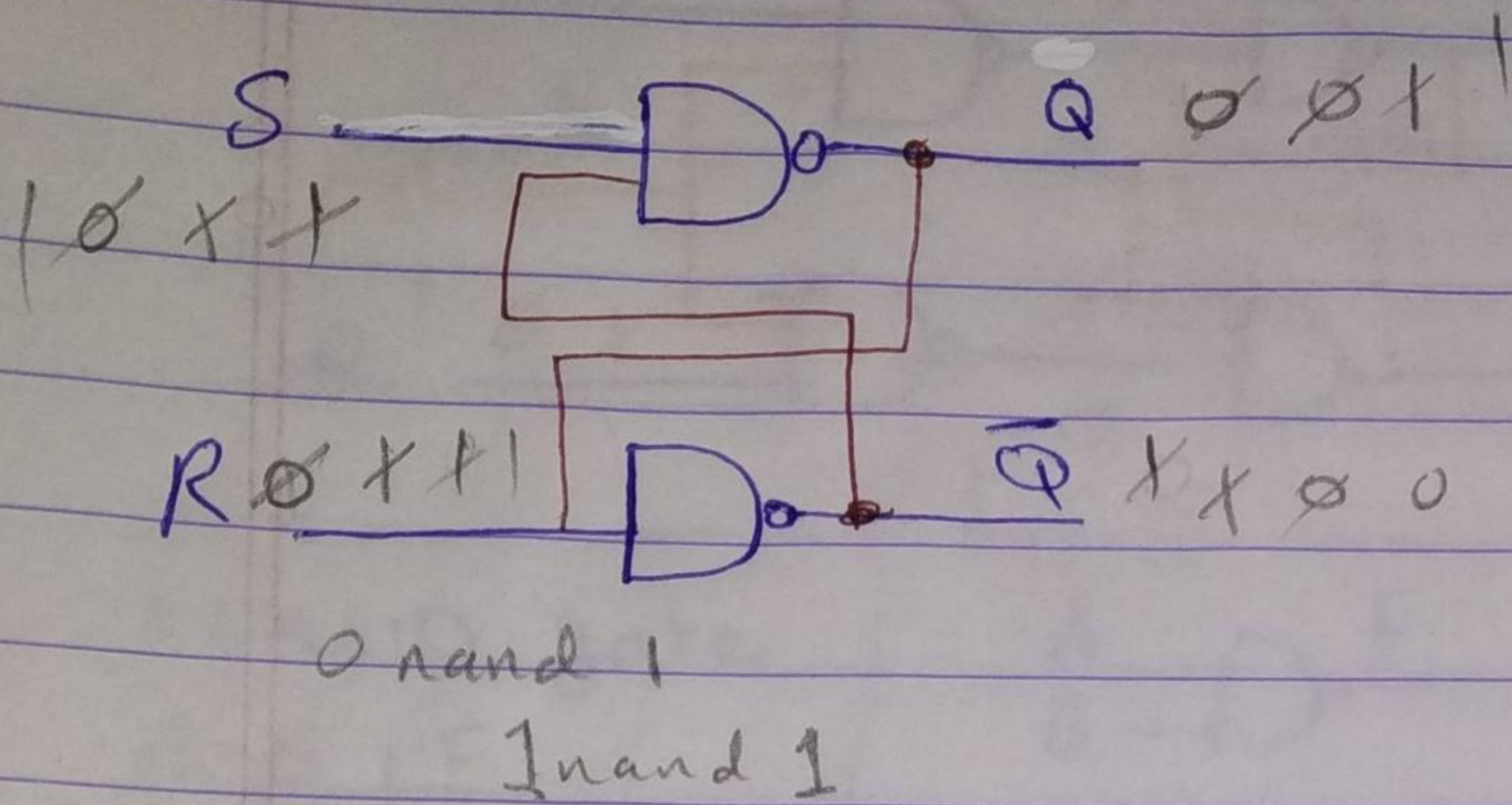

| S | R | Q | \bar{Q} |
|---|---|---|-----------|
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 |


memory
memory
[forbidden]

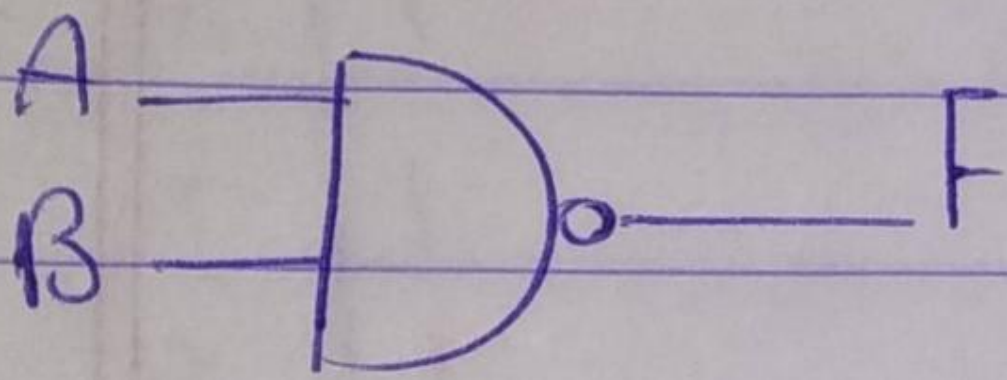

Function Table


| A | B | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

③ SR Latch with enable

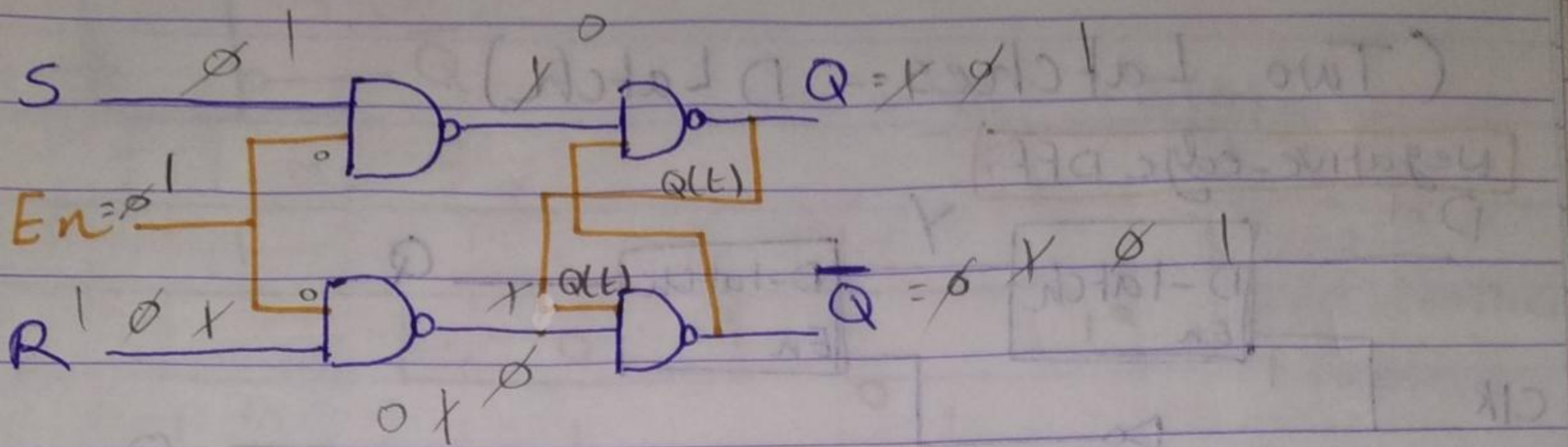


NAND gate

| A | B | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

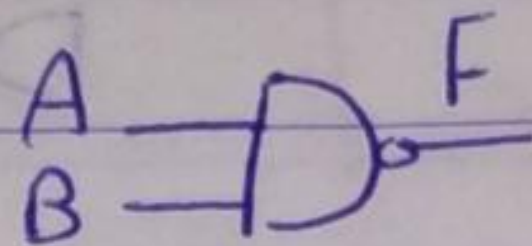

| En | S | R | memory. |
|----|---|---|---|
| 0 | x | x | No change $\rightarrow Q(t+1) = Q(t)$. |
| 1 | 0 | 0 | No change $\rightarrow Q(t+1) = Q(t)$. |
| 1 | 0 | 1 | $Q(t+1) = 0$. |
| 1 | 1 | 0 | $Q(t+1) = 1$. |
| 1 | 1 | 1 | Forbidden. |

④ D-Latch - memory element Asynchronous

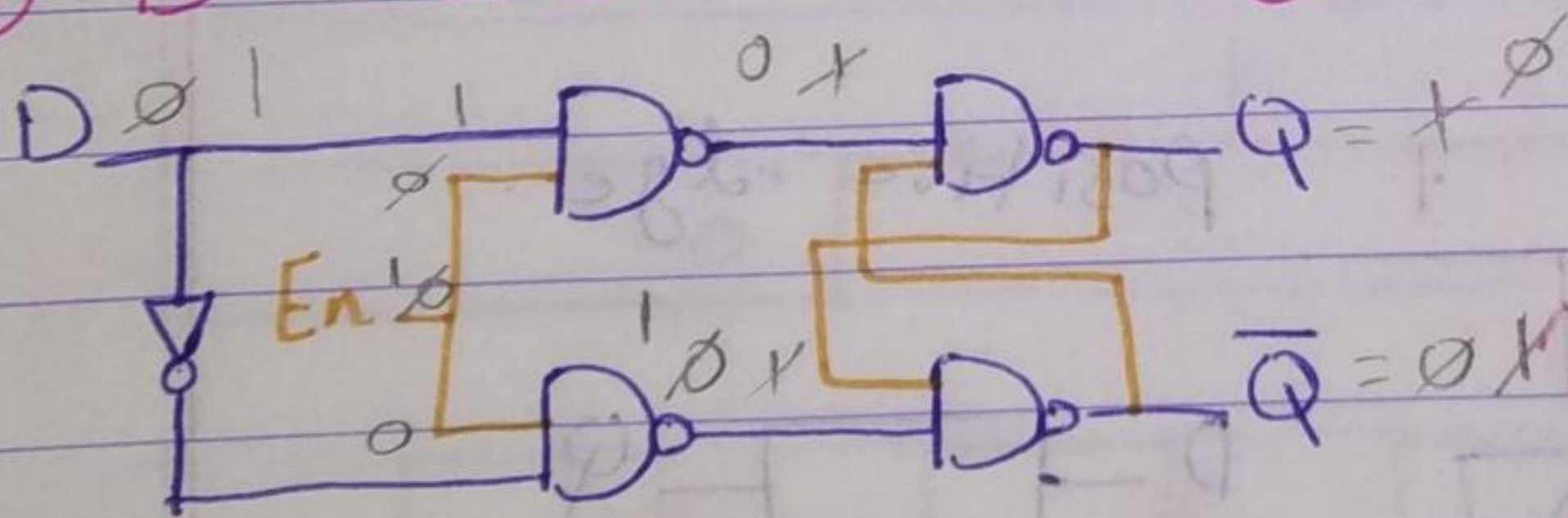

| En | D | |
|----|---|-----------------------------------|
| 0 | x | No change ($Q(t+1) = Q(t)$). |
| 1 | 0 | $Q(t+1) = 0$ |
| 1 | 1 | $Q(t+1) = 1$ |


فیش [input is forbidden]

① DFF

Edge - Triggered D-Flip Flop.

(Two Latches - D Latch)

Negative-edge DFF.

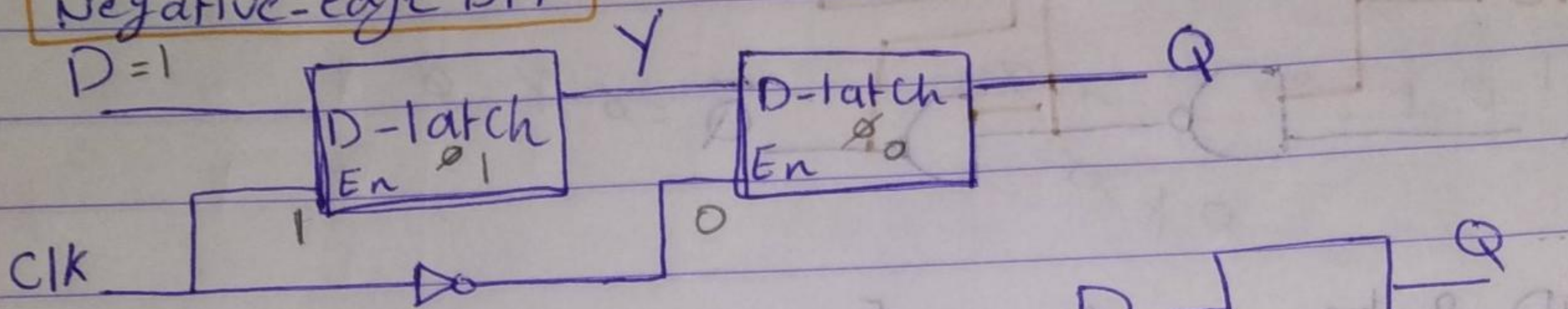


if $CLK = 1$

0 (negative edge)


$$Q(t+1) = D$$


Positive-edge DFF

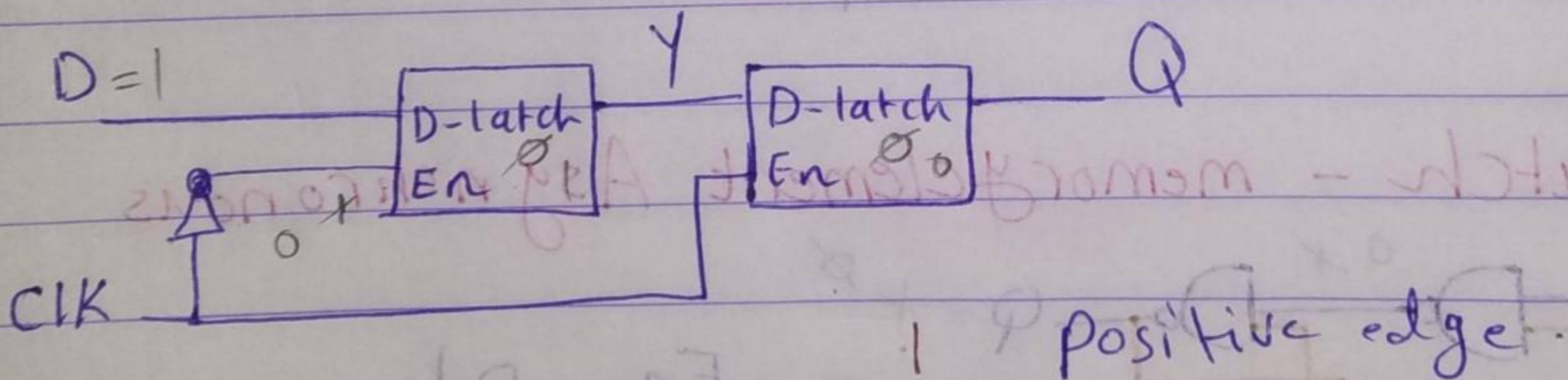

$CLK = 0$

$$Q(t+1) = D$$

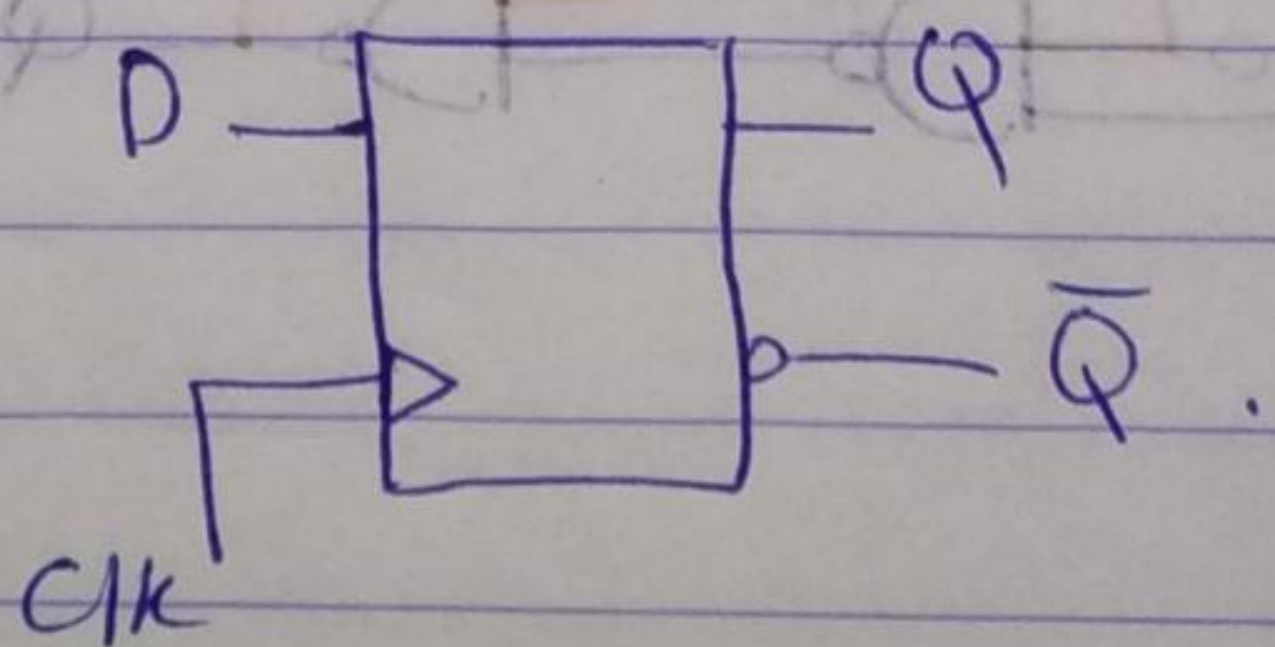


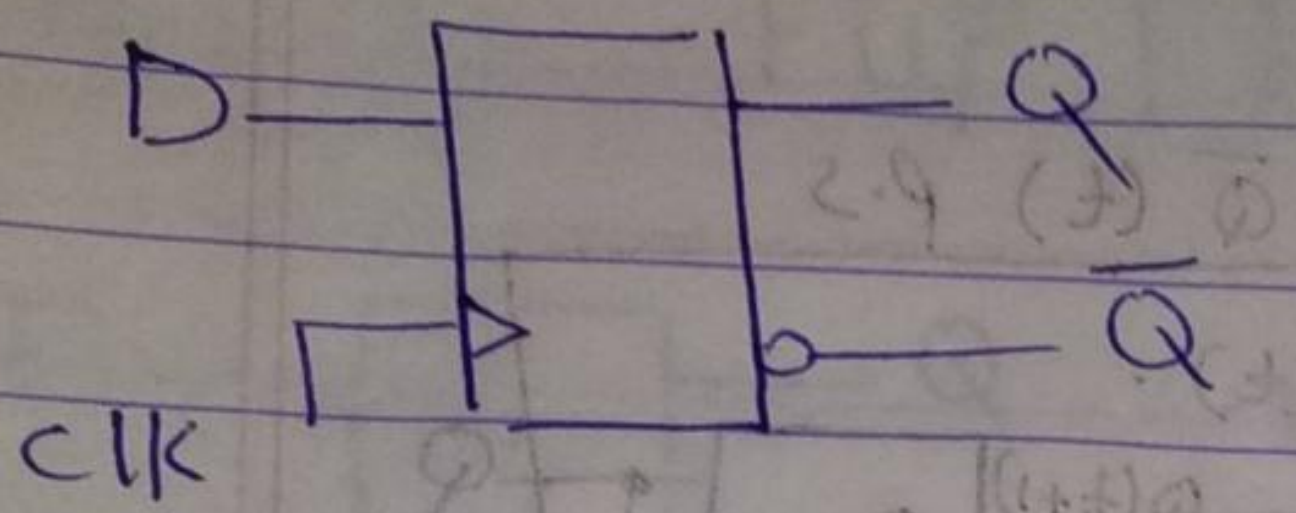

Positive edge


| D | $Q(t+1)$ |
|---|----------|
| 0 | 0 |
| 1 | 1 |

Characteristic table

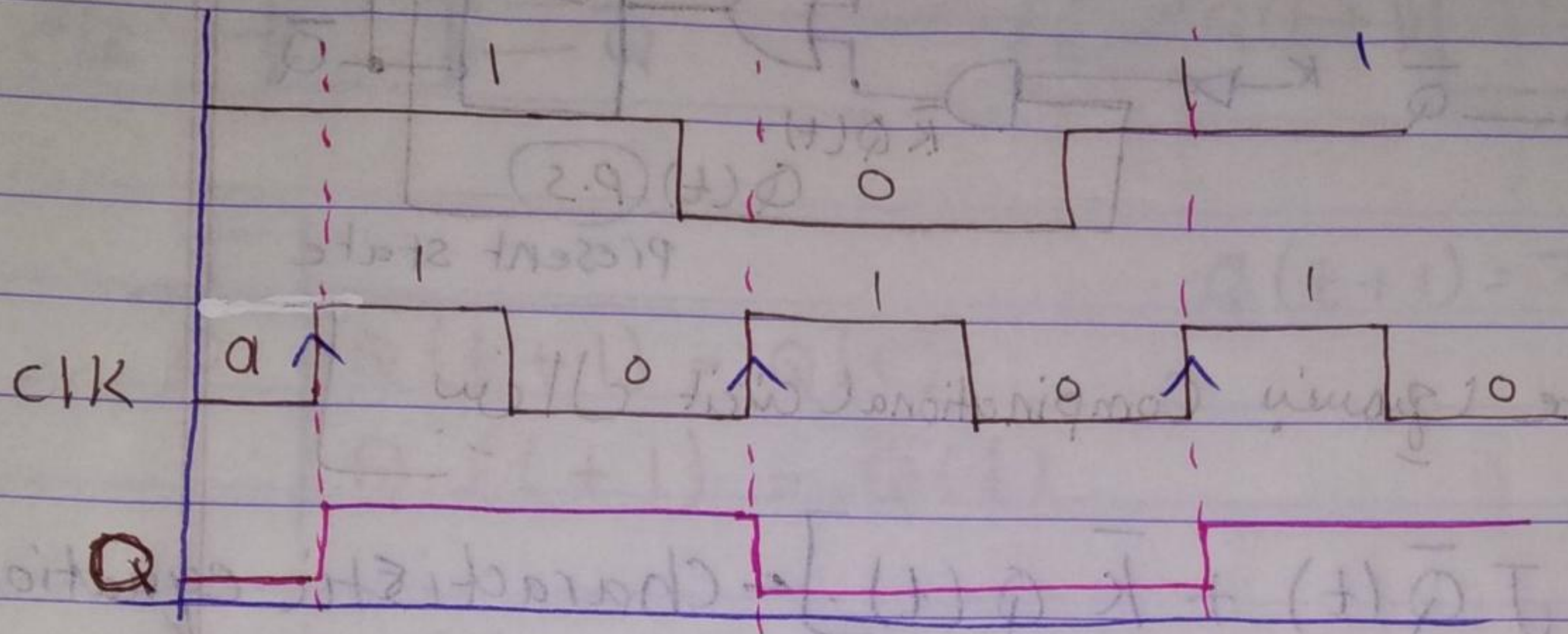


Timing Diagram -


Negative edge

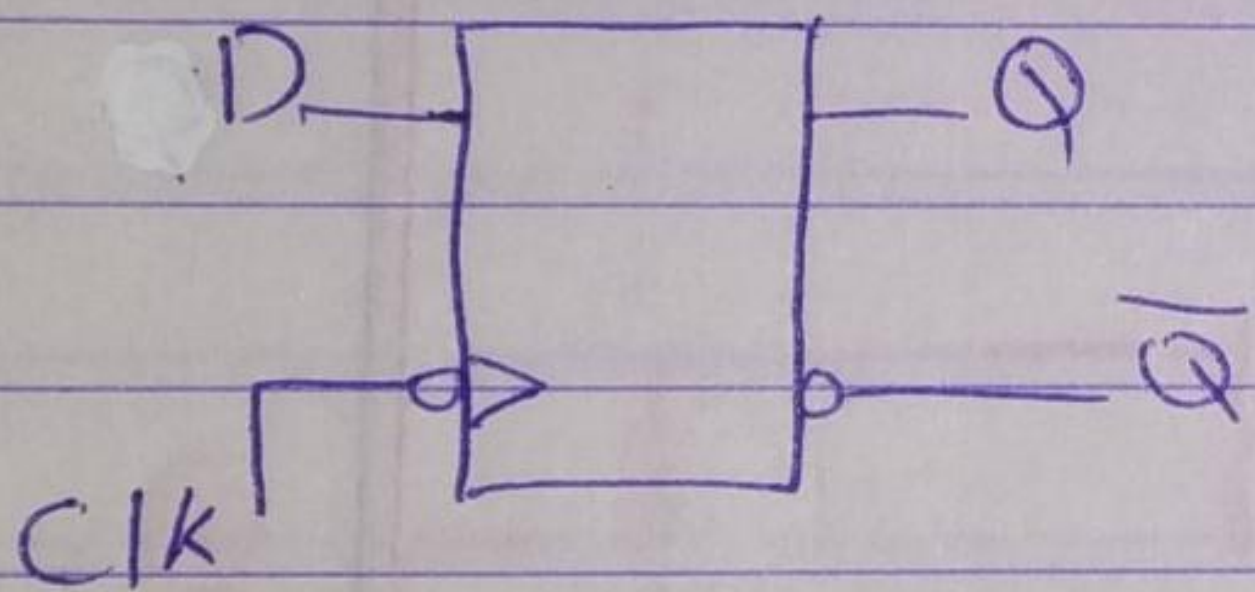

$$Q(t+1) = D$$

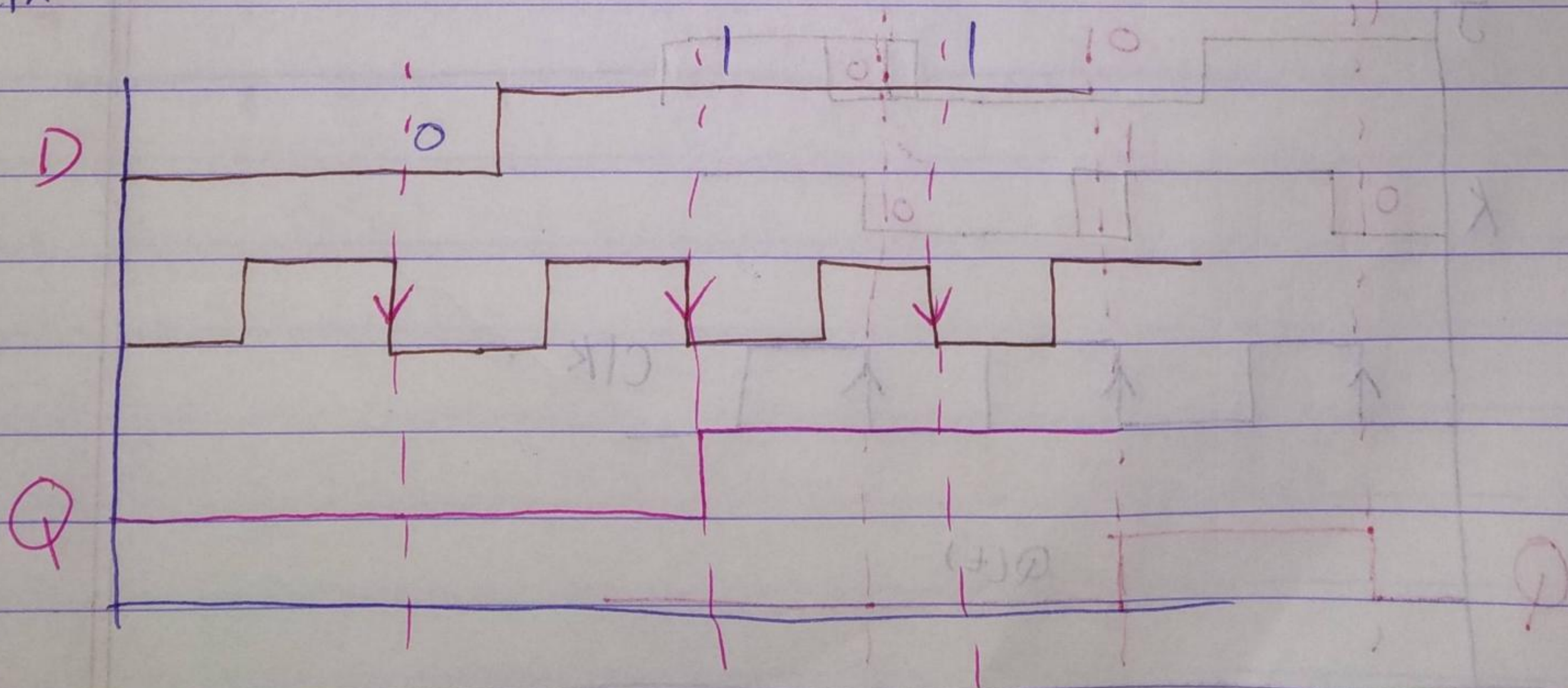


② JK Flip Flop .

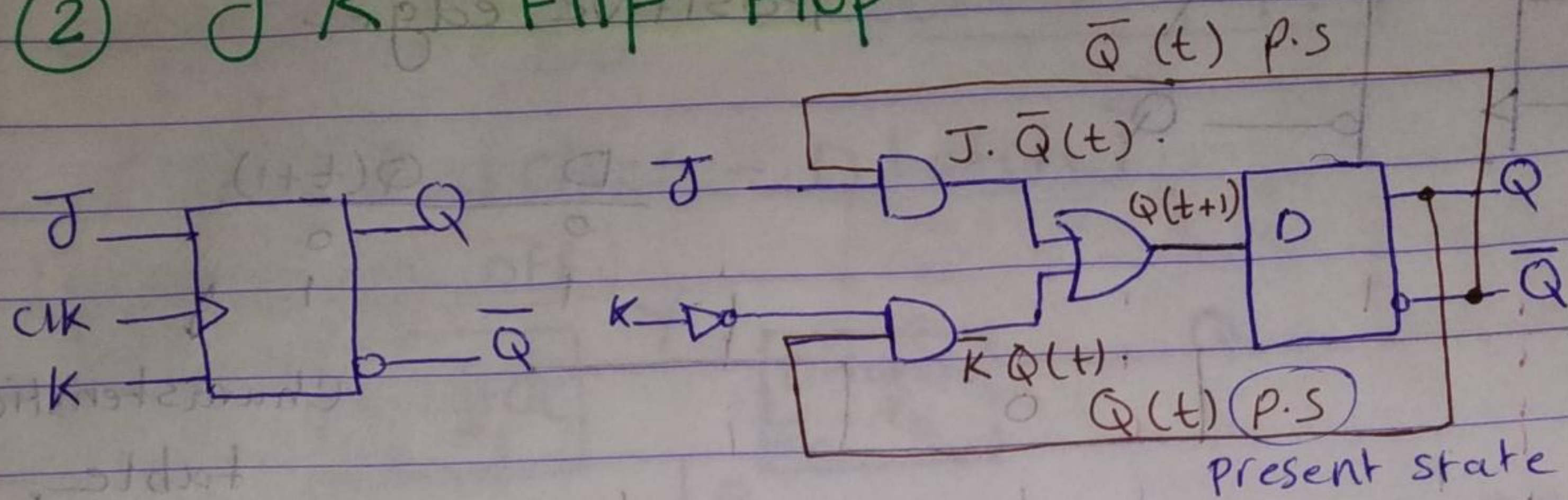


Next State (q_{next}) Combinational circuit

$$Q(t+1) = J \bar{Q}(t) + \bar{K} Q(t) \leftarrow \text{Characteristic equation.}$$

| J | K | |
|---|---|---|
| 0 | 0 | $Q(t+1) = Q(t) \leftarrow (\text{No change})$ |
| 0 | 1 | $Q(t+1) = 0$ |
| 1 | 0 | $Q(t+1) = 1$ |
| 1 | 1 | $Q(t+1) = \bar{Q}(t)$ |

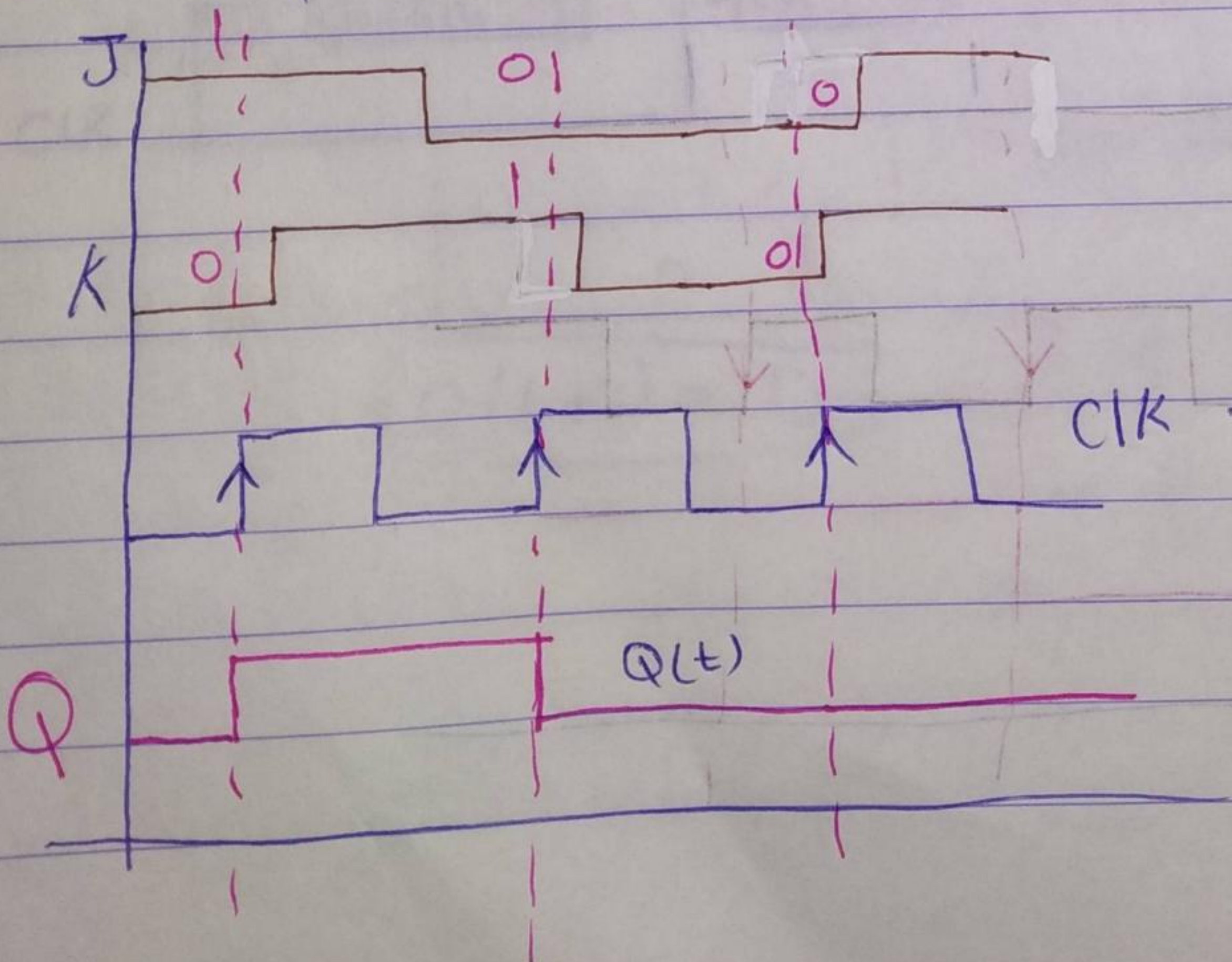


③ T Flip Flop.

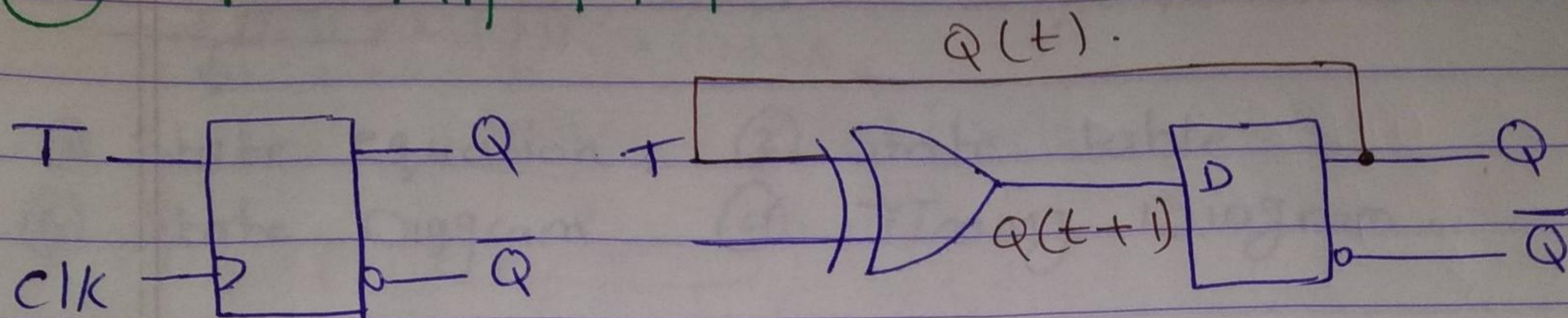

| T | |
|---|-----------------------|
| 0 | $Q(t+1) = Q(t)$ |
| 1 | $Q(t+1) = \bar{Q}(t)$ |


$$Q(t+1) = T \oplus Q(t)$$

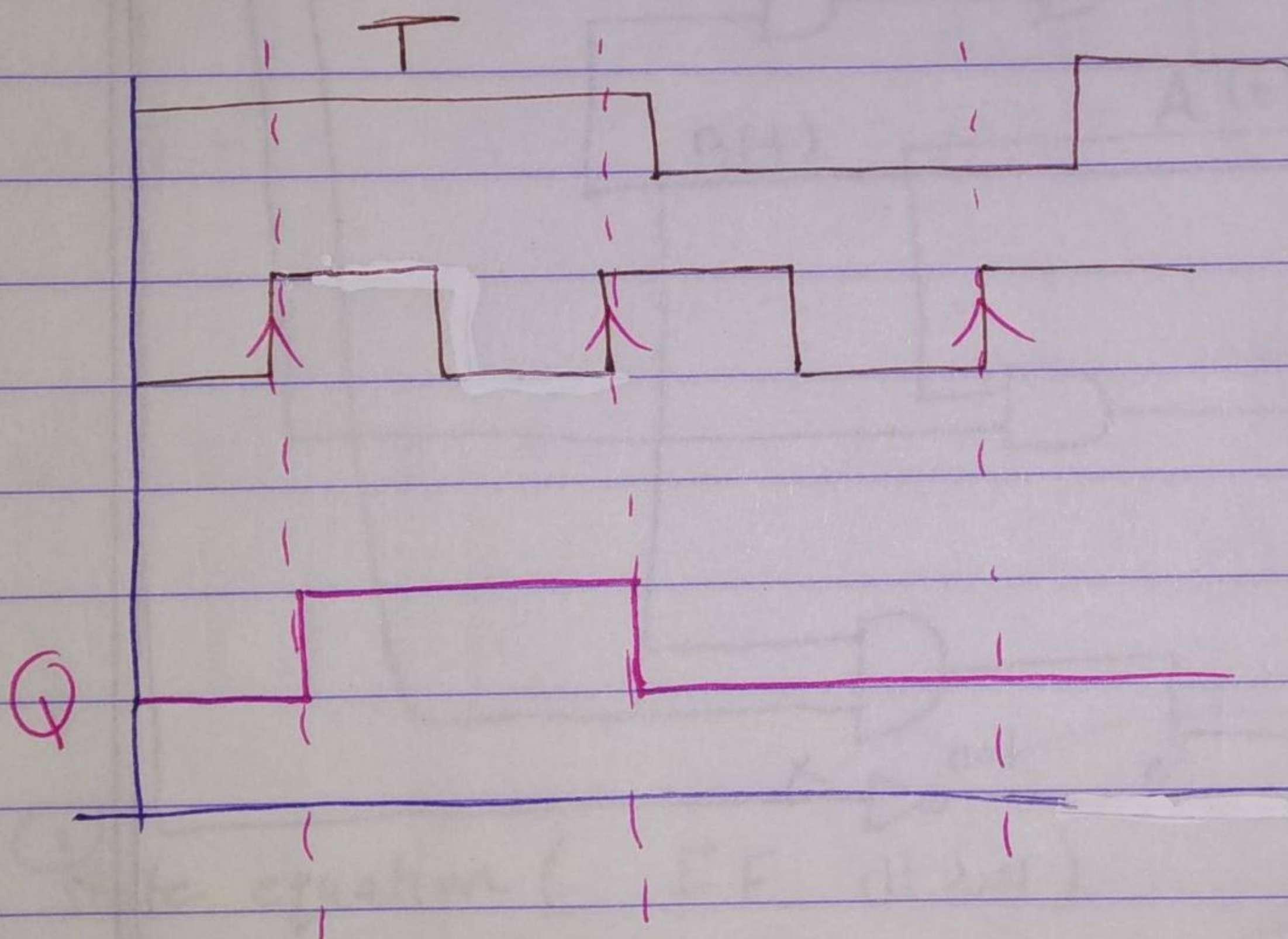

Analysis For clocked sequential circuit.

- ① State equation, ② State table.
- ③ State Diagram, ④ Timing Diagram.

ex

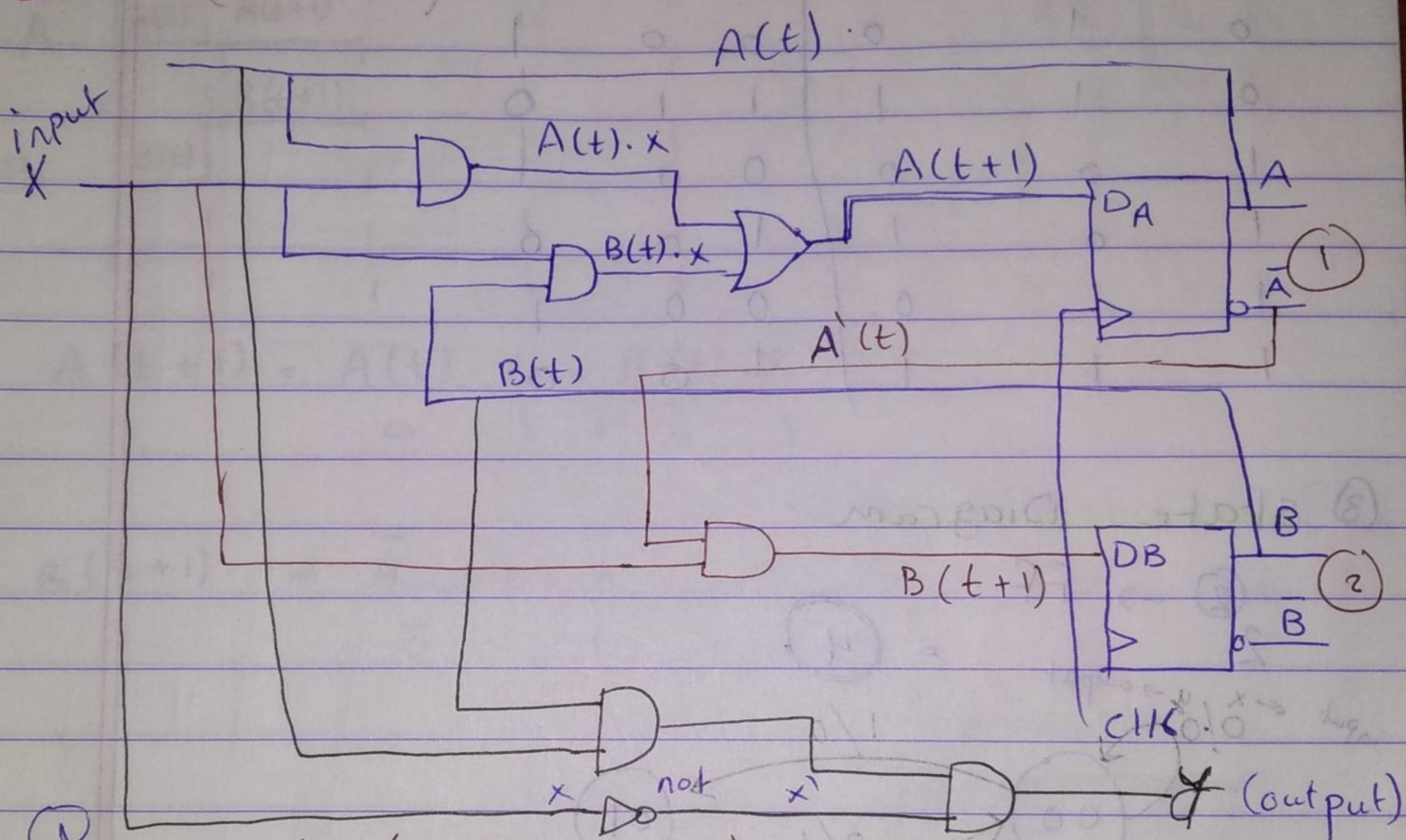

① State equation (FF بعد ال).

$$\begin{aligned} \textcircled{1} & A(t+1) = A(t) \cdot X + B(t) \cdot X \quad \text{---} \textcircled{1} \\ \textcircled{2} & B(t+1) = \bar{A}(t) \cdot X \end{aligned}$$

$$Y = [A(t) + B(t)] \cdot X' \quad \text{[P.S + input]}.$$

② State Table

$$A(t+1) = A(t) \cdot x + B(t) \cdot x$$

| P.S | | input | N.S | | output |
|-----|---|-------|-----|---|--------|
| A | B | x | A | B | y |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 |

$$B(t+1) = \bar{A}(t) \cdot x$$

$$(A(t) + B(t)) \cdot x$$


③ State Diagram

② → FF


2

= 4

input ← x / y → output

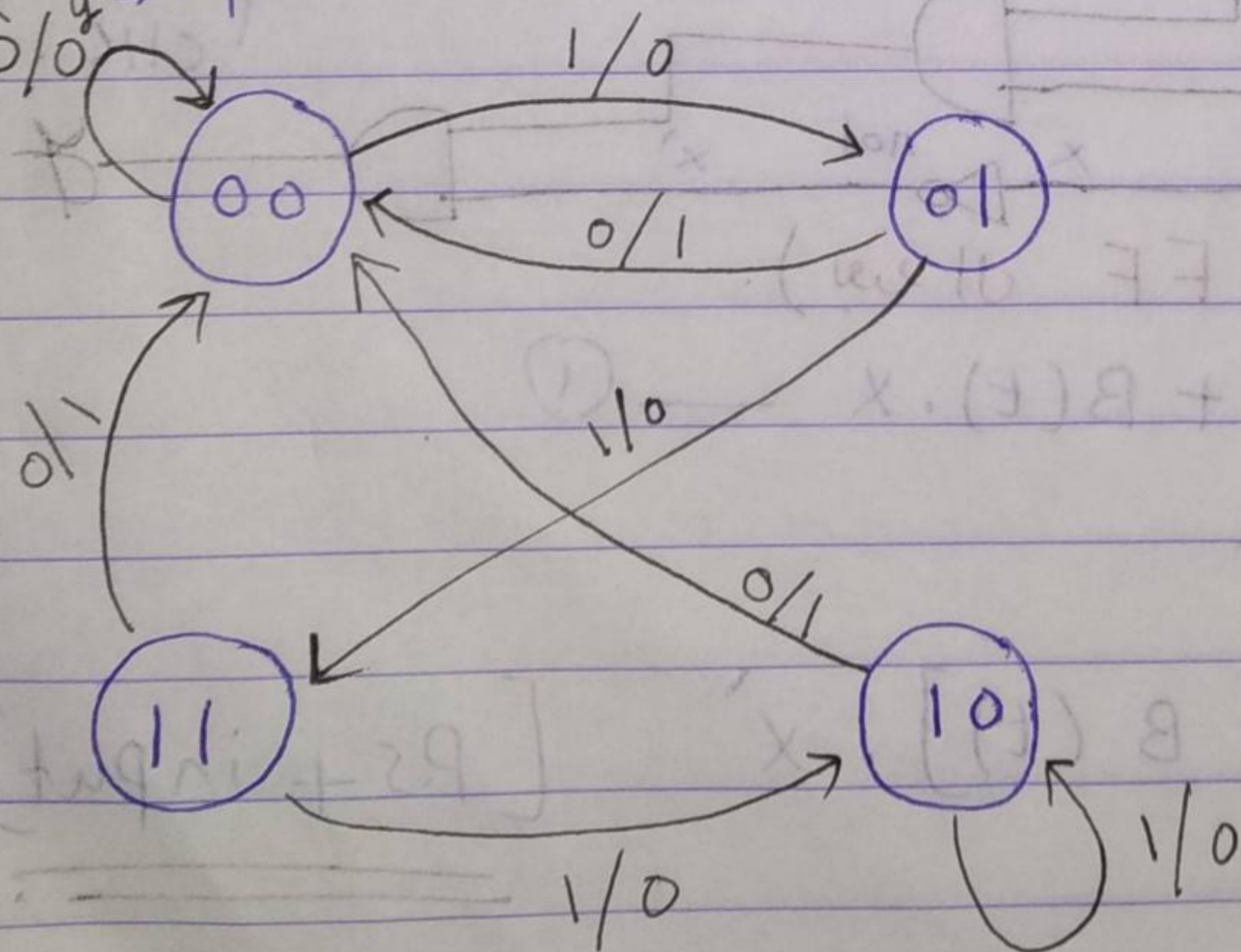

④ Timing Diagram

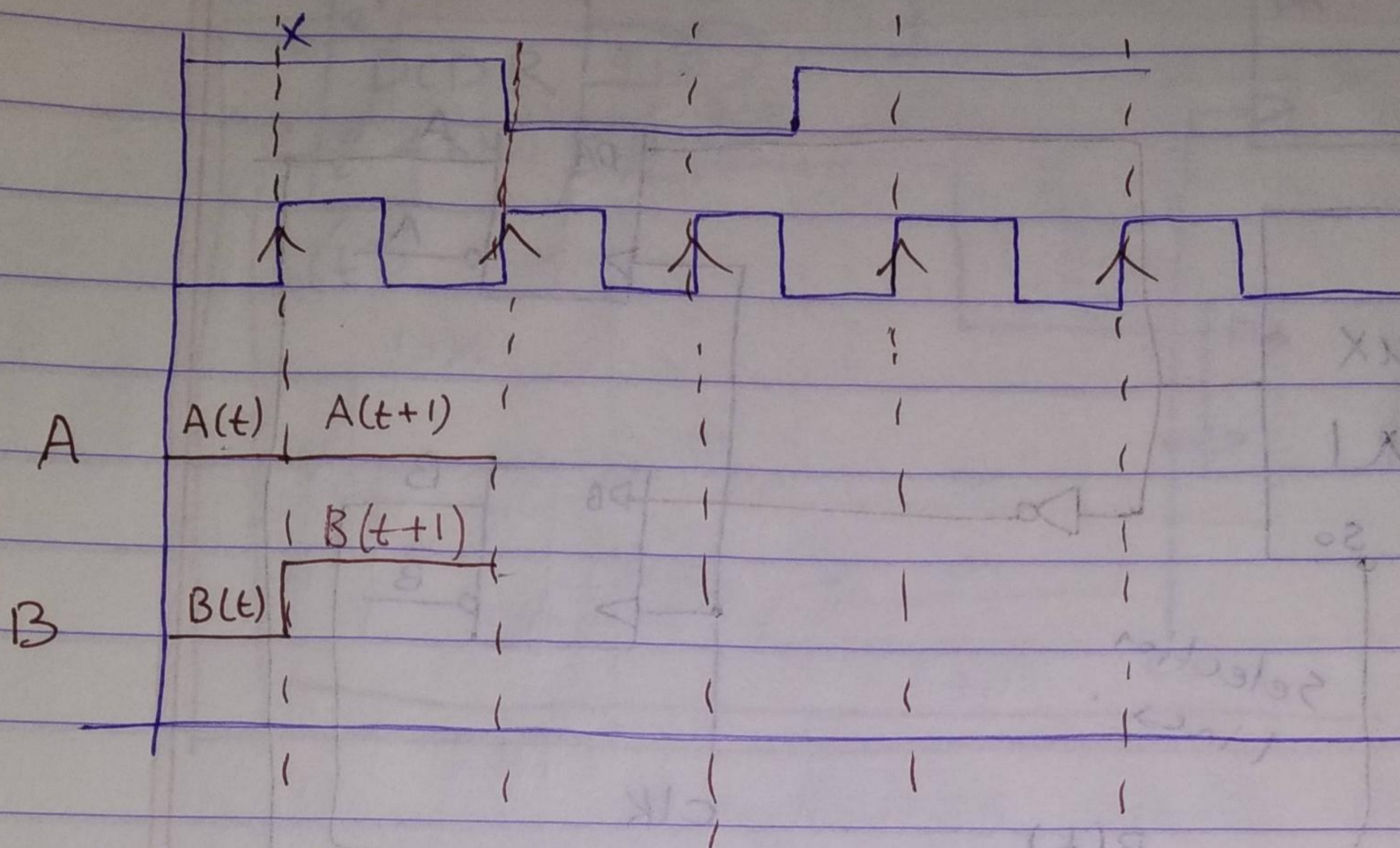

$$A(t+1) = A(t) \cdot X + B(t) \cdot X$$

$$0 \cdot 1 + 0 \cdot 1$$


$$B(t+1) = \bar{A}(t) \cdot X$$

$$0 \cdot 1$$

LglaSi

ex


$$A(t+1) = DA / B(t+1) = DB$$

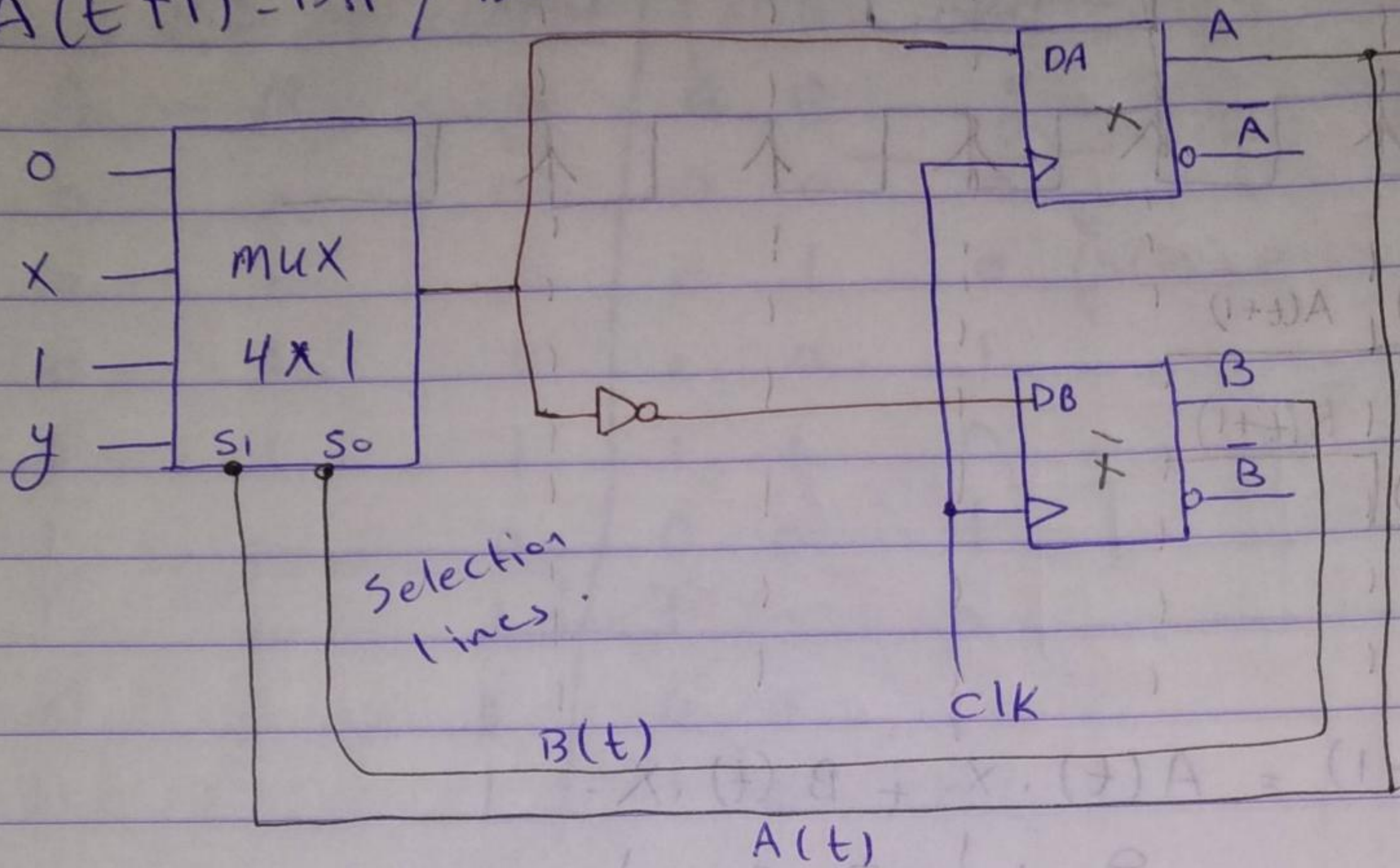

| P.S | | input | | N.S | |
|-----|---|-------|---|-----|---|
| A | B | x | y | A | B |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 |


| | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | | | | |
| 01 | | | 1 | 1 |
| 11 | | | | |
| 10 | | | | |

ex

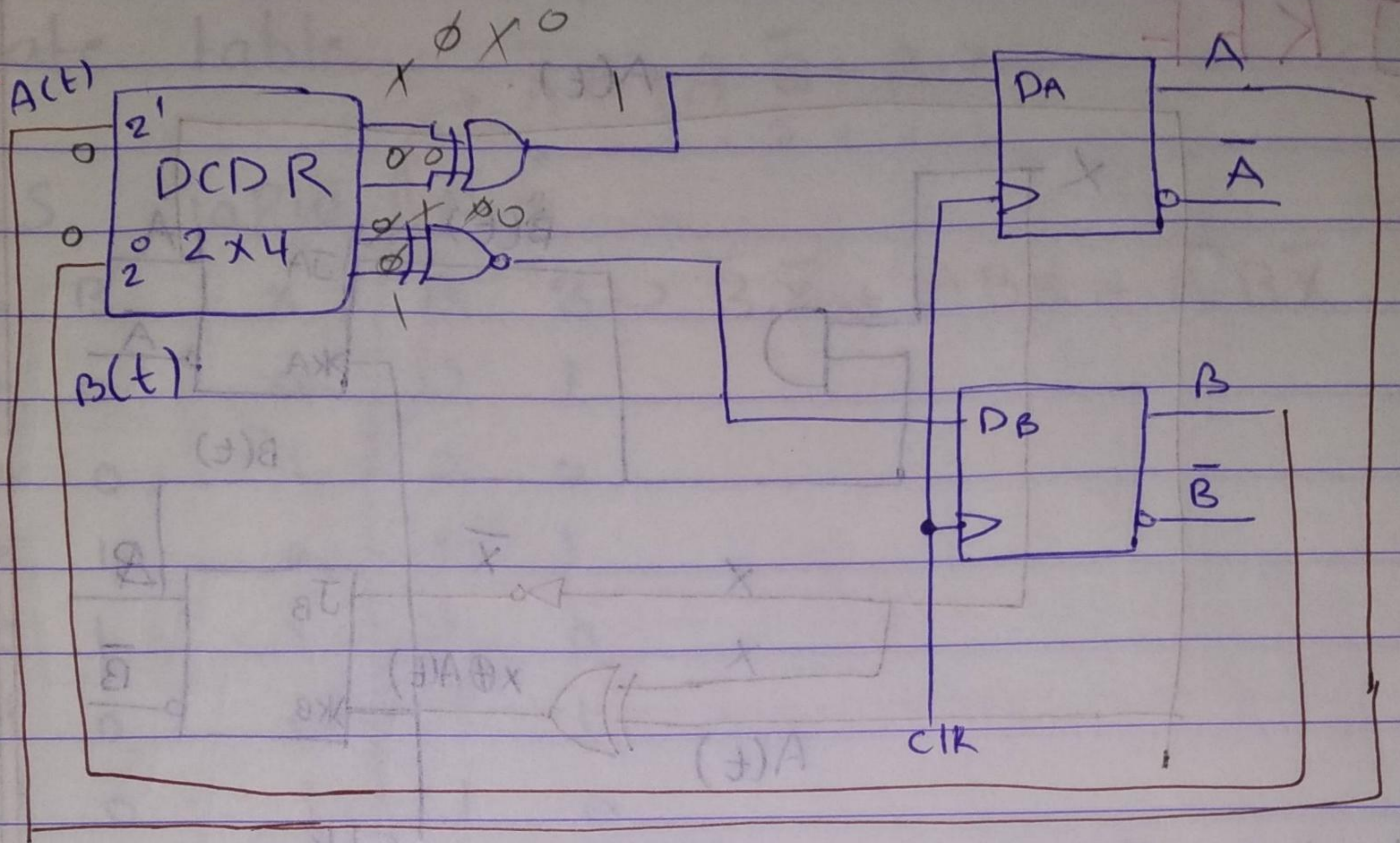

| P.S | | N.S | |
|-----|---|-----|---|
| A | B | A | B |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 |

JKFF

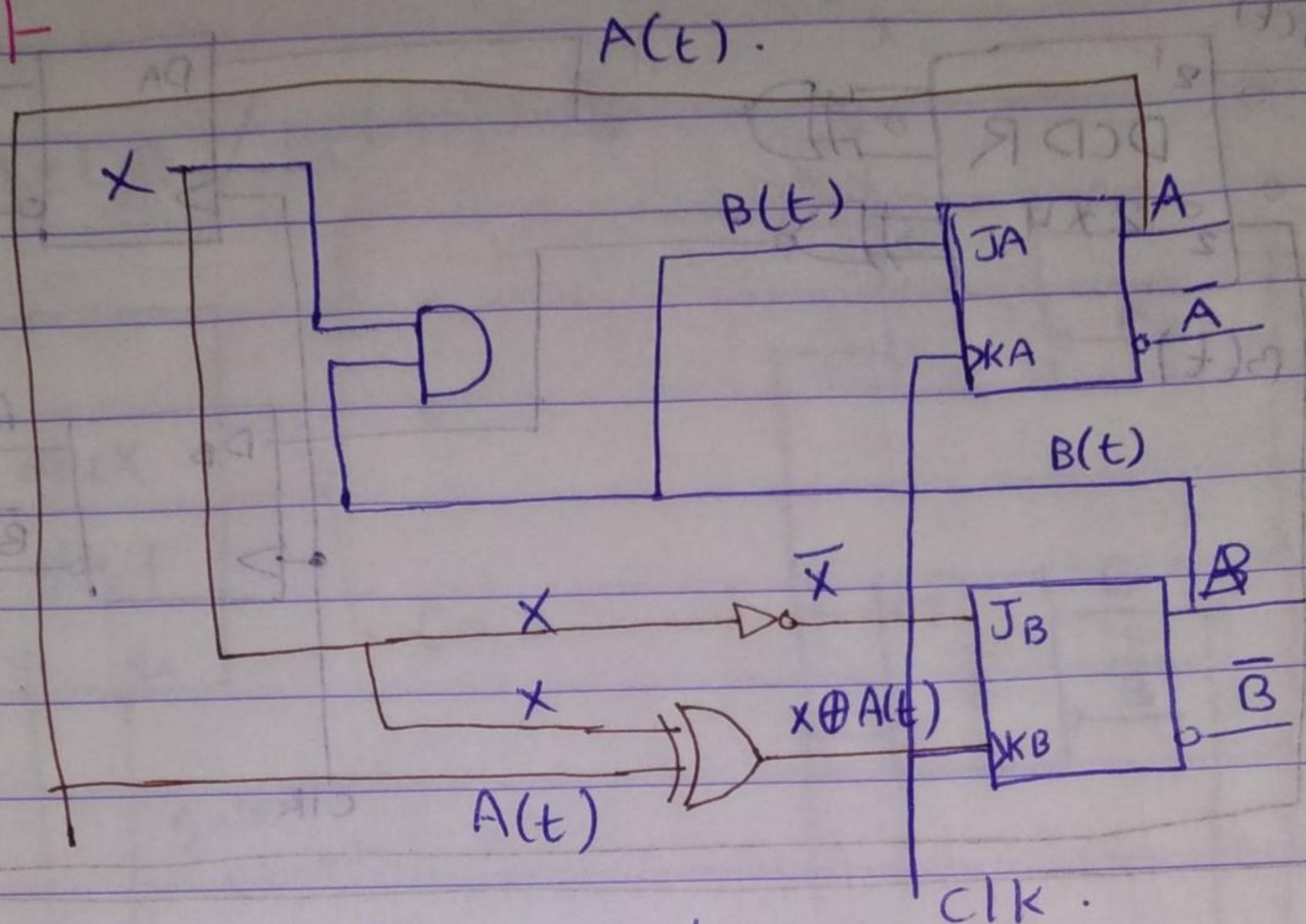

— what is the state equation

Two state eqn ..

$$A(t+1) = J_A \bar{A}(t) + \bar{K}_A A(t).$$

$$= B(t) \cdot \bar{A}(t) + [x \cdot B(t)] \cdot A(t).$$

$$A(t+1) = A'B + A\bar{B} + A \cdot x \quad \text{--- (1)}$$

$$B(t+1) = J_B \bar{B}(t) + \bar{K}_B B(t).$$

$$= \bar{x} \cdot \bar{B}(t) + (x \oplus A(t))' B(t).$$

$$= \bar{x} \cdot \bar{B}(t) + [\bar{x} \cdot A + x \bar{A}]' B(t).$$

$$= \bar{B} \bar{x} + ABx + \bar{A} B \bar{x}. \quad \text{--- (2)}$$

② State table.


| P.S | | | input | N.S | |
|-----|---|---|-------|-----|---|
| A | B | X | | A | B |
| 0 | 0 | 0 | | 0 | 1 |
| 0 | 0 | 1 | | 0 | 0 |
| 0 | 1 | 0 | | 1 | 1 |
| 0 | 1 | 1 | | 1 | 0 |
| 1 | 0 | 0 | | 1 | 1 |
| 1 | 0 | 1 | | 1 | 0 |
| 1 | 1 | 0 | | 0 | 0 |
| 1 | 1 | 1 | | 1 | 1 |

$$\bar{A} \cdot B + A \cdot \bar{B} + A \cdot X$$


$$\bar{0} \cdot 0 + 0 \cdot \bar{0} + 0 \cdot 1$$

$$\bar{B} \cdot \bar{X} + ABX + \bar{A} B \bar{X}$$

③ State Diagram.

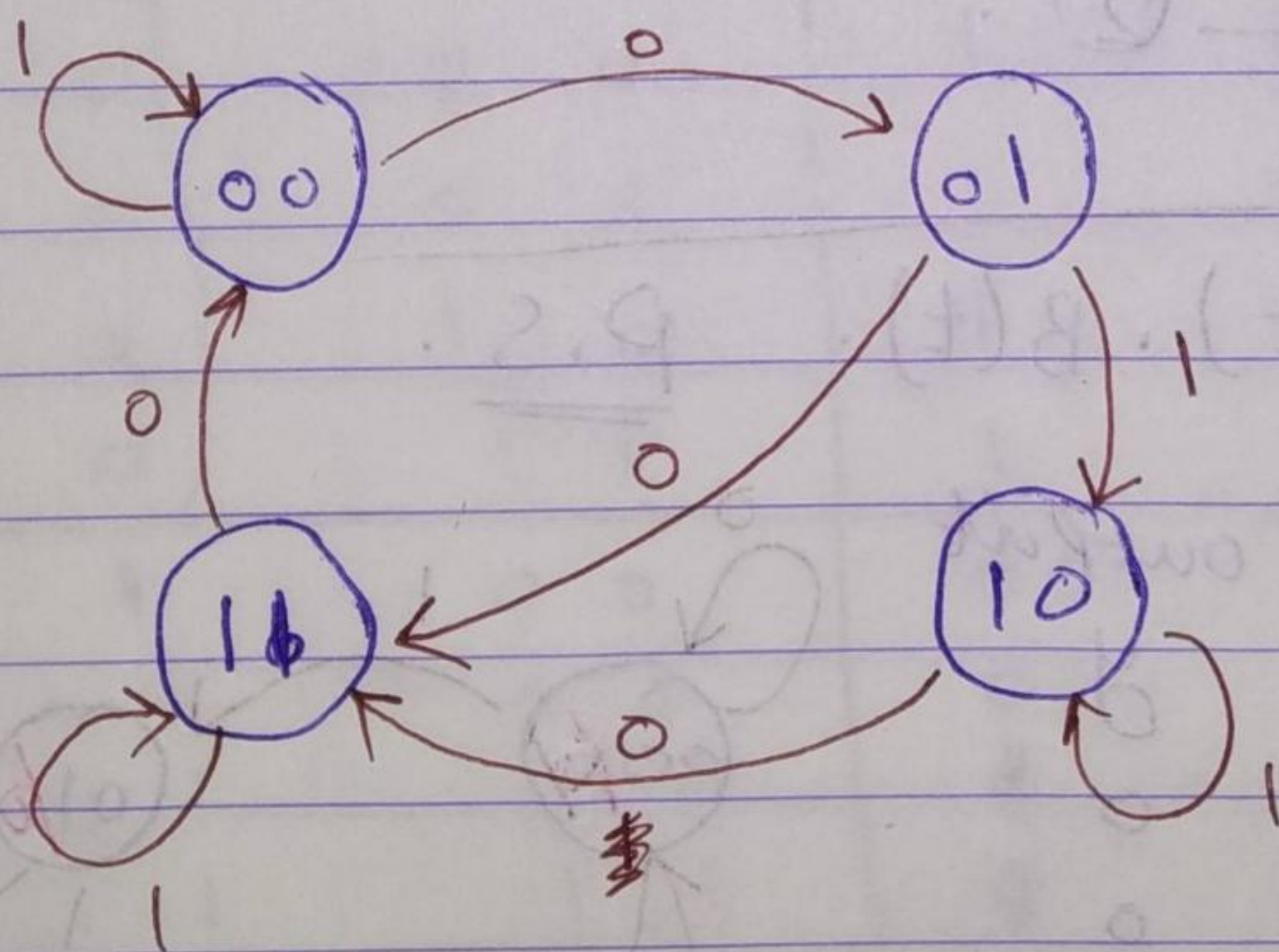

ex

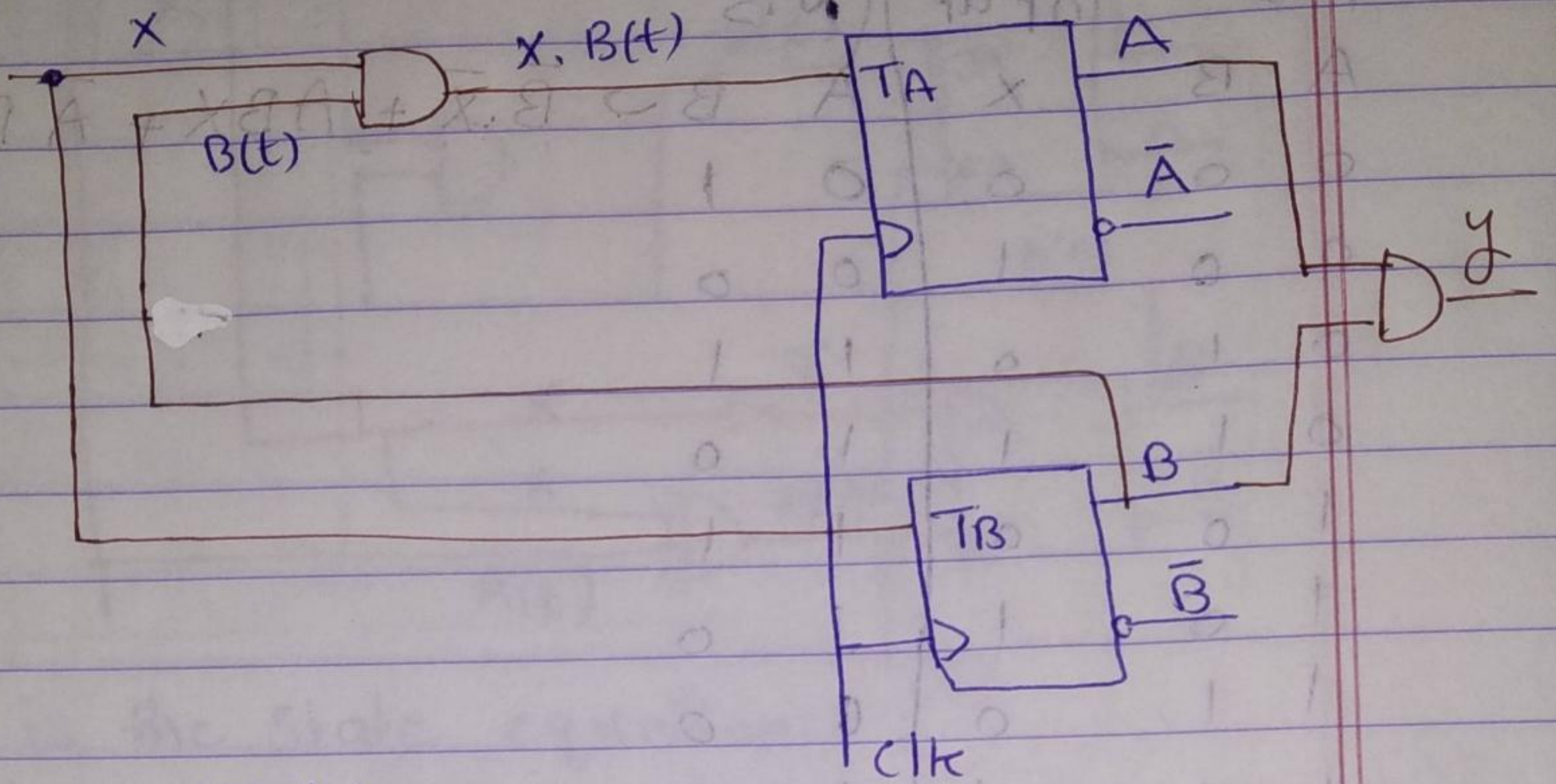

$$A(t+1) = T_A \oplus A(t).$$


$$A(t+1) = [X.B] \oplus A \quad \text{--- ①}$$

$$B(t+1) = T_B \oplus B(t).$$

$$= X \oplus B \quad \text{--- ②}$$


output $y = A(t) \cdot B(t)$ P.S.

| P.S | input | N.S | output |
|-----|-------|-----|--------|
| A B | x | A B | y |
| 0 0 | 0 | 0 0 | 0 |
| 0 0 | 1 | 0 1 | 0 |
| 0 1 | 0 | 0 1 | 0 |
| 0 1 | 1 | 1 0 | 0 |
| 1 0 | 0 | 1 0 | 0 |
| 1 0 | 1 | 1 1 | 0 |
| 1 1 | 0 | 1 1 | 1 |
| 1 1 | 1 | 0 0 | 1 |

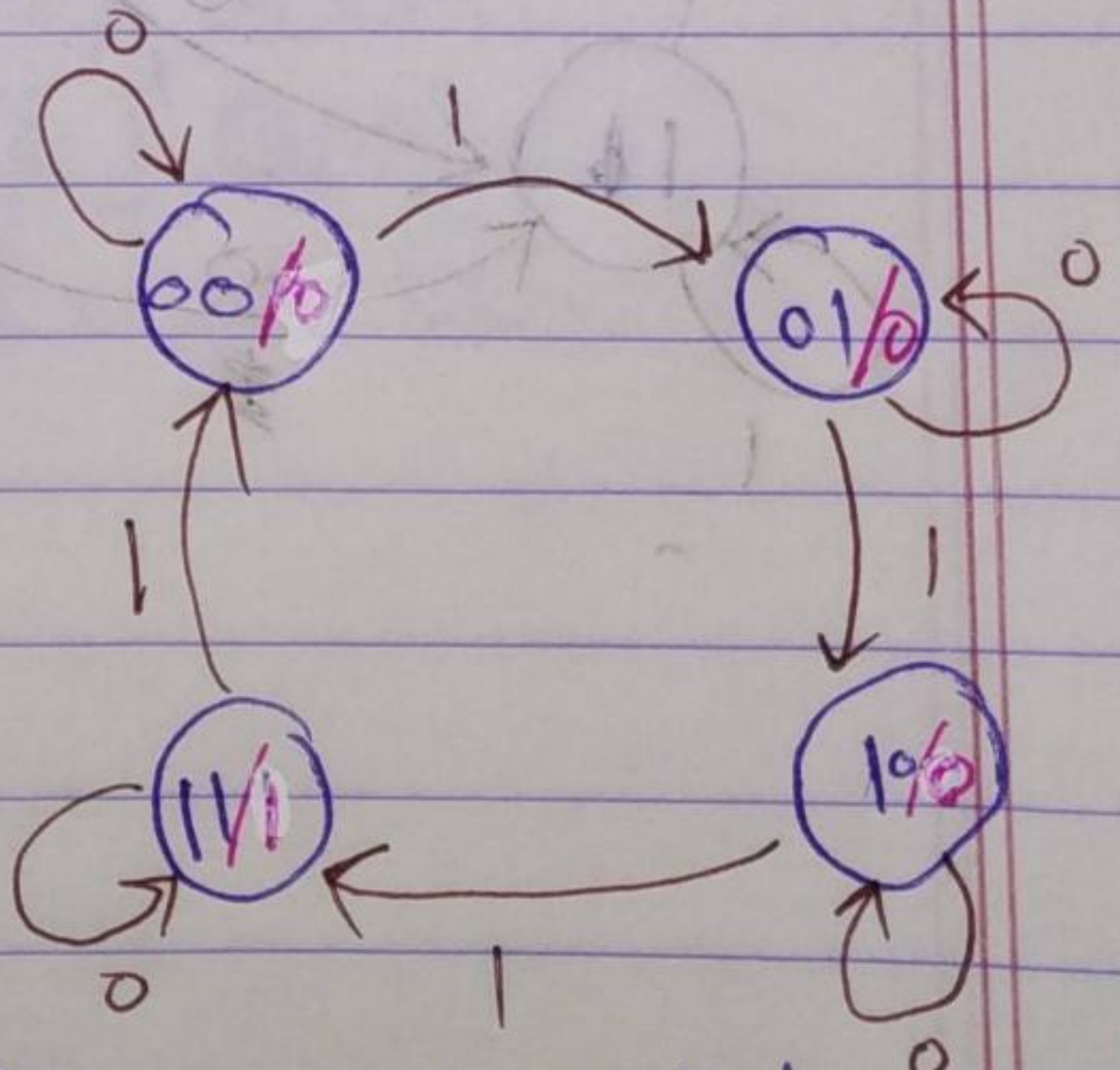

دعينا ان output داخل
الدوائر لأنه يعتمد على P.S فقط

et

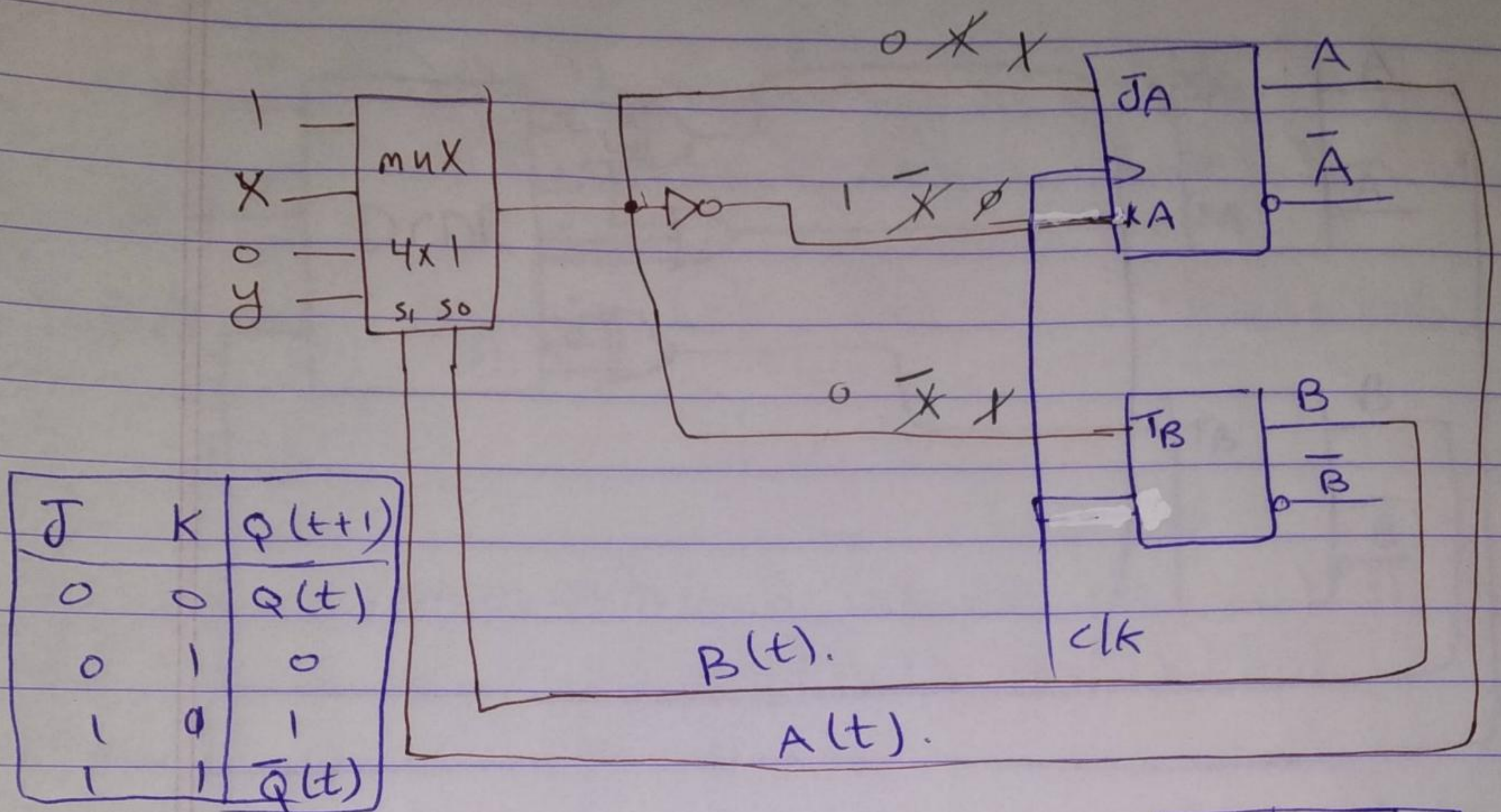


| T | $Q(t+1)$ |
|---|-------------------|
| 0 | $Q(t)$ |
| 1 | $\overline{Q}(t)$ |

| P.S | | input | | N.S | |
|-----------------|-----------------|-------|---|--------------|---|
| ^{SI} A | ^{SO} B | x | y | A | B |
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 |

من مأكلة
منه
(إذا غلب الحلو)
- (^ - ^)

Implication Chart for State Reduction.

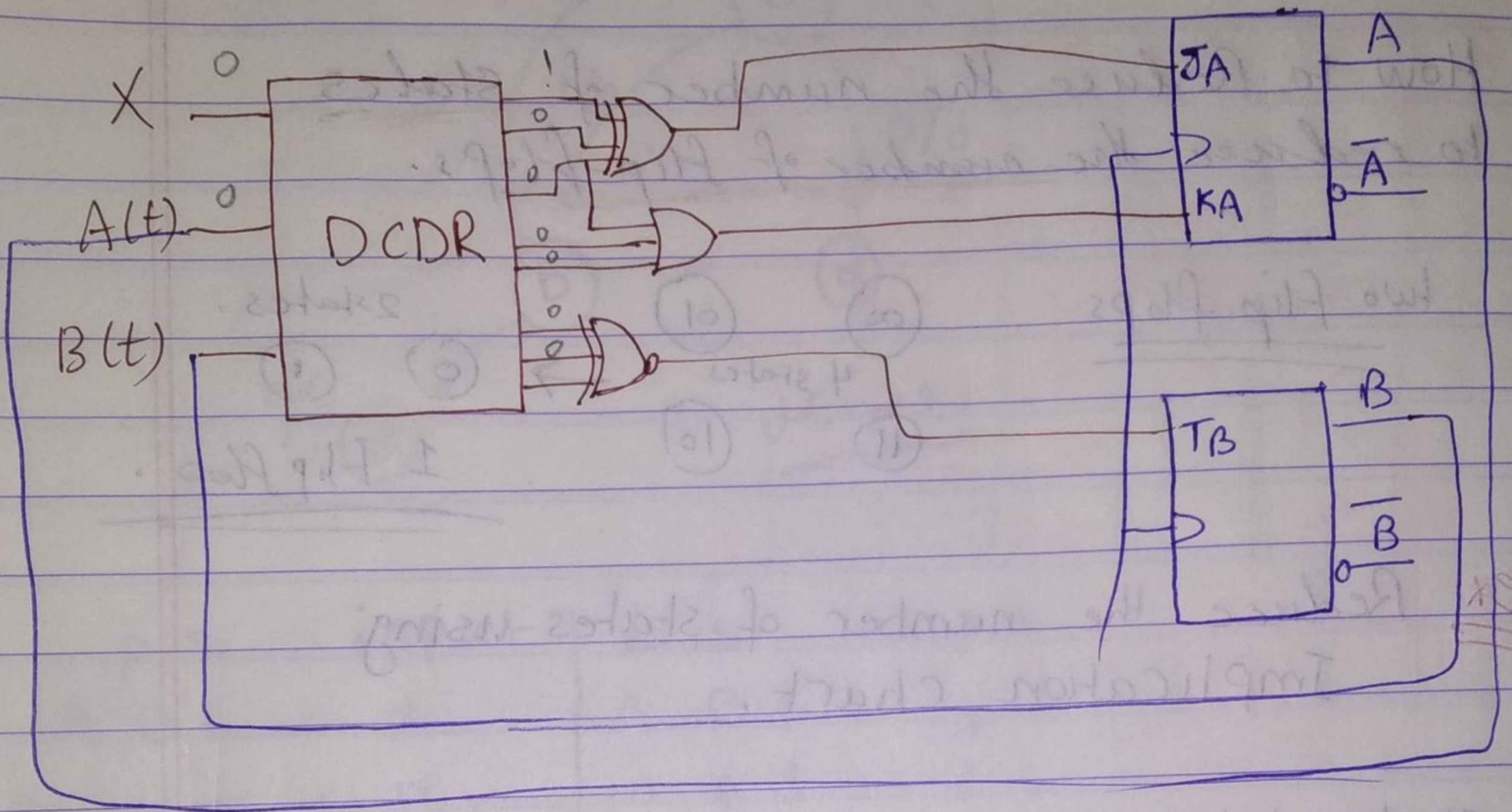


| input | P.S | | N.S | |
|-------|-----|-----|-----|-----|
| X | A | B | A | B |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

| J | K | $Q(t+1)$ |
|-----|-----|--------------|
| 0 | 0 | $Q(t)$ |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $\bar{Q}(t)$ |

| T | $Q(t+1)$ |
|-----|--------------|
| 0 | $Q(t)$ |
| 1 | $\bar{Q}(t)$ |

Implication chart for State Reduction.

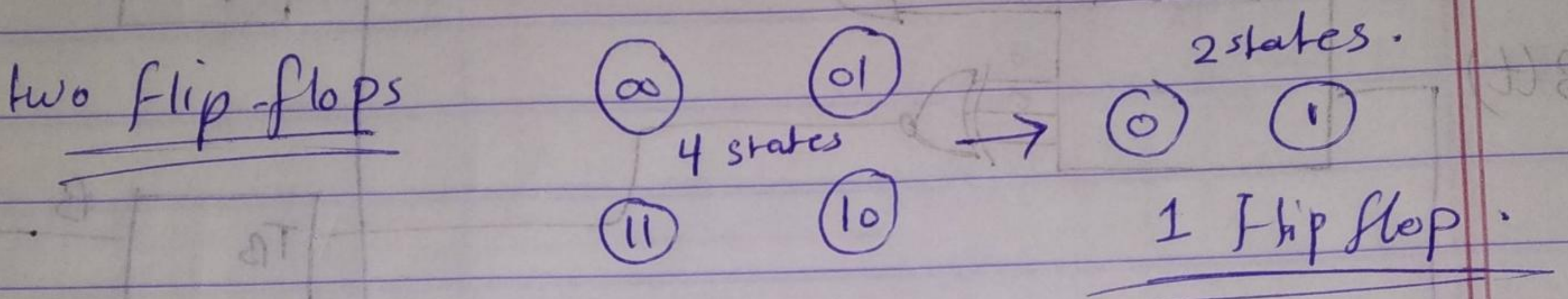How to Reduce the number of states
to reduce the number of flip-flops.



Reduce the number of states using
Implication chart.


State table


P.S

N.S

output.

| | | $x=0$ | $x=1$ | | $x=0$ | $x=1$ |
|-----|---|-------|-------|---|-------|-------|
| 000 | a | d | b | A | 0 | 0 |
| 001 | b | e | a | B | 0 | 0 |
| 010 | c | g | f | A | 0 | 1 |
| 011 | d | a | d | B | 1 | 0 |
| 100 | e | a | d | A | 1 | 0 |
| 101 | f | c | b | B | 0 | 0 |
| 110 | g | a | e | A | 1 | 0 |

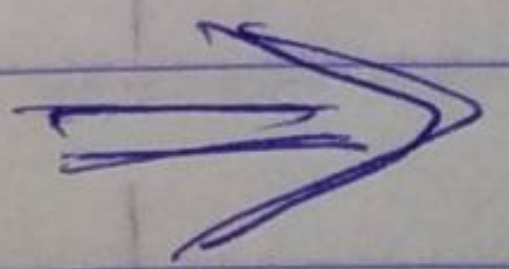

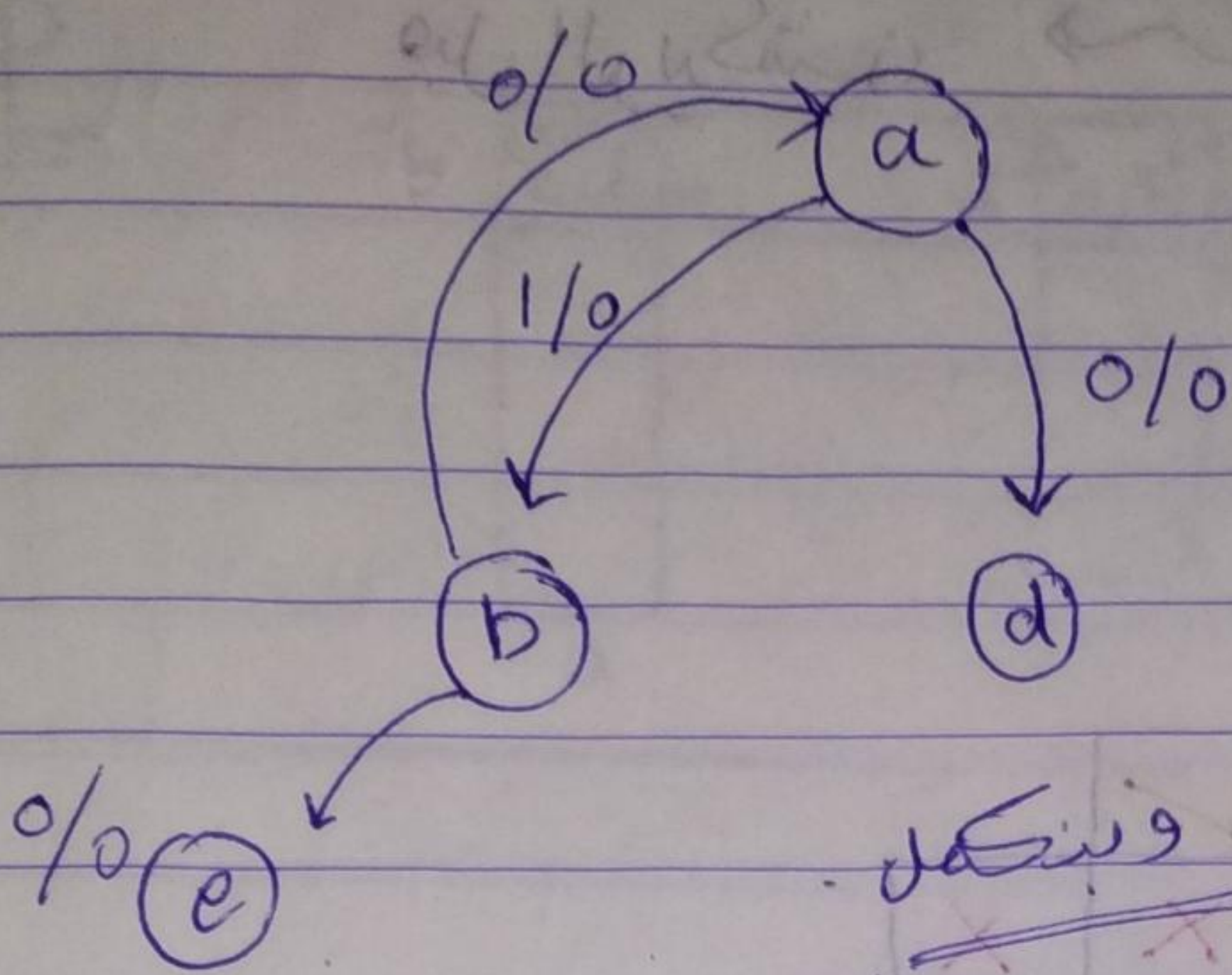

p.s input | N.s output.

A B C x

A B C y

0 0 0 0

0 0 1 0

0 0 0 1

0 0 1 0

0 0 1 0


1 0 0 0

0 0 1 1

0 0 0 0

0 1 0 0

1 1 1 1

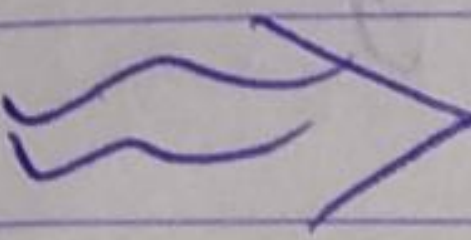

7 flip flops \rightarrow قبل الريدكشن

| | | | | | | |
|---|----------------|----------------|---|----------------|----------------|---|
| b | d, e a, b ✓ | | | | | |
| c | X | X | | | | |
| d | X | X | X | | | |
| e | X | X | X | ✓ | | |
| f | c, d b, b X | c, e a, b X | X | X | X | |
| g | X | X | X | a, a d, e ✓ | a, a d, e ✓ | X |
| | a | b | c | d | e | f |

- different output label two state \times *
 (2) two state \Rightarrow same output & same next state. (✓)


(a, b), (d, e), (d, g), (e, g) equivalent

(a, b) (d, e, g) \leftarrow

$$a \equiv b$$

$$d \equiv e \equiv g$$

| P.S | N.S | output | } 4 state 7 د |
|-----|------------|--------|------------------|
| a | d <u>a</u> | 0 0 | |
| c | <u>d</u> f | 0 1 | |
| d | a d | 1 0 | |
| f | c <u>a</u> | 0 0 | |

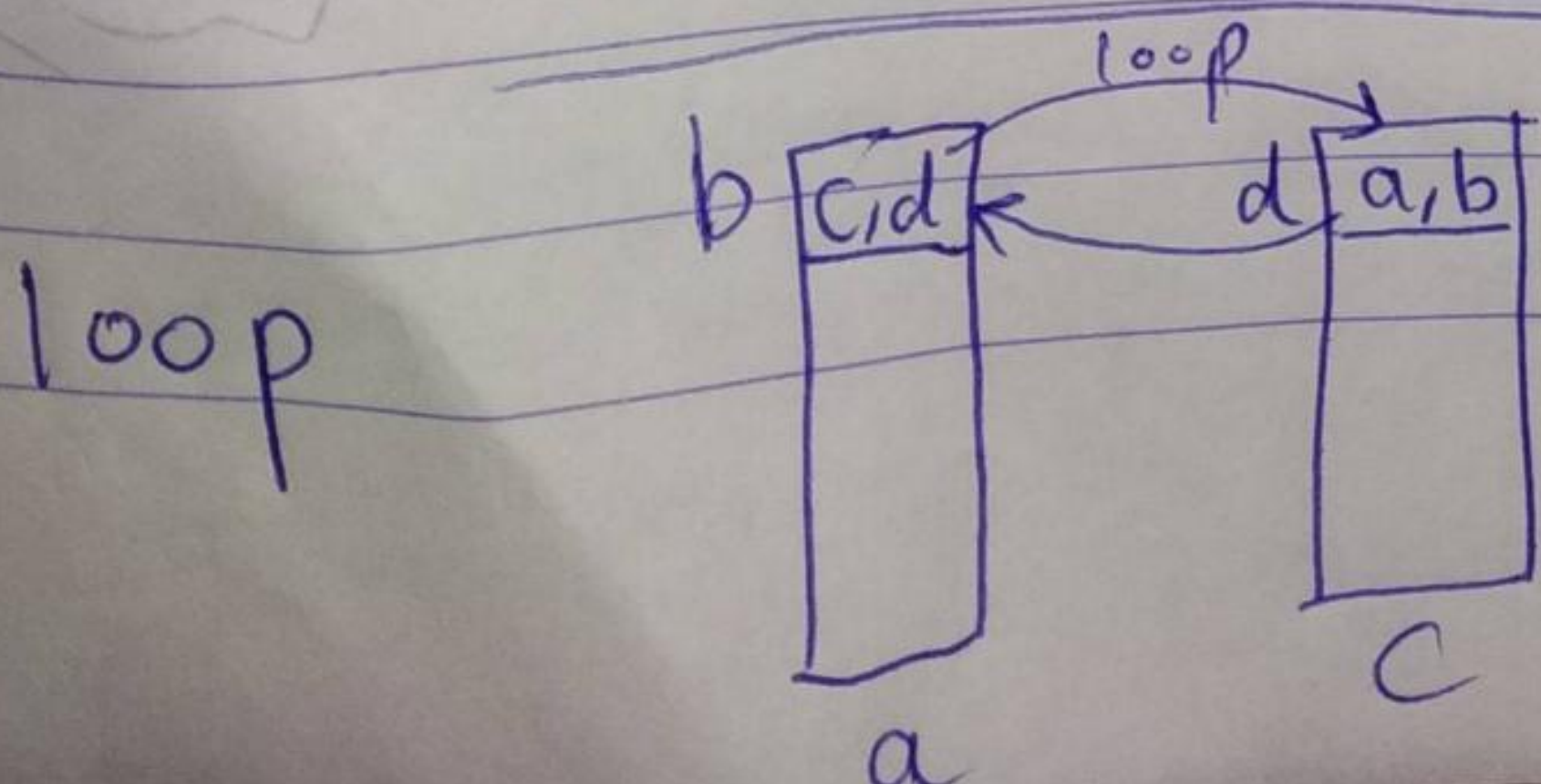


* Design procedure.

- ① Read the problem carefully.
- ② Derive the State Diagram.
- ③ Assign Binary values to the states.
- ④ State Table.
- ⑤ Determine the type of Flip flop.
- ⑥ Derive the input equation.
- ⑦ Draw the circuit.

ex Design a sequential circuit that detects three or more consecutive one's?

DFF

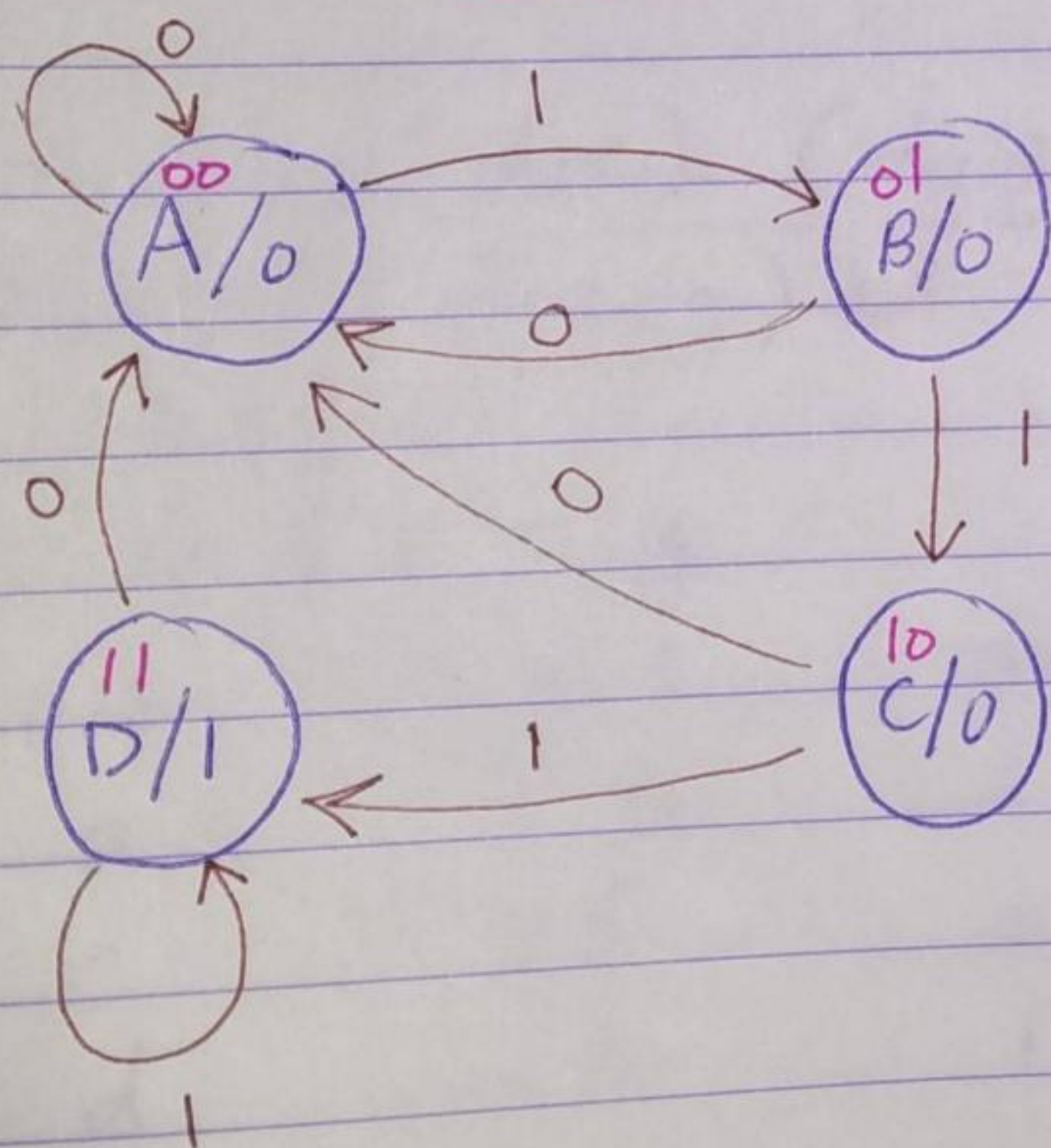

| p.s | | input | N.S | | output |
|-----|---|-------|---------|---------|--------|
| A | B | X | DA A | DB B | y |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 |

more a's p.s 01 10 11 output 0 1
 11/1 10/0 01/0 00/0


| $B(t) \backslash A(t)$ | 00 | 01 | 11 | 10 |
|------------------------|----|----|----|----|
| 0 | | | 1 | |
| 1 | | 1 | 1 | |

$$D(A) = A(t+1)$$


$$DA = B \cdot X + A \cdot X$$

| $A \backslash BX$ | 00 | 01 | 11 | 10 |
|-------------------|----|----|----|----|
| 0 | | 1 | | |
| 1 | | 1 | 1 | |

$$B(t+1) = DB = \bar{B}X + AX$$

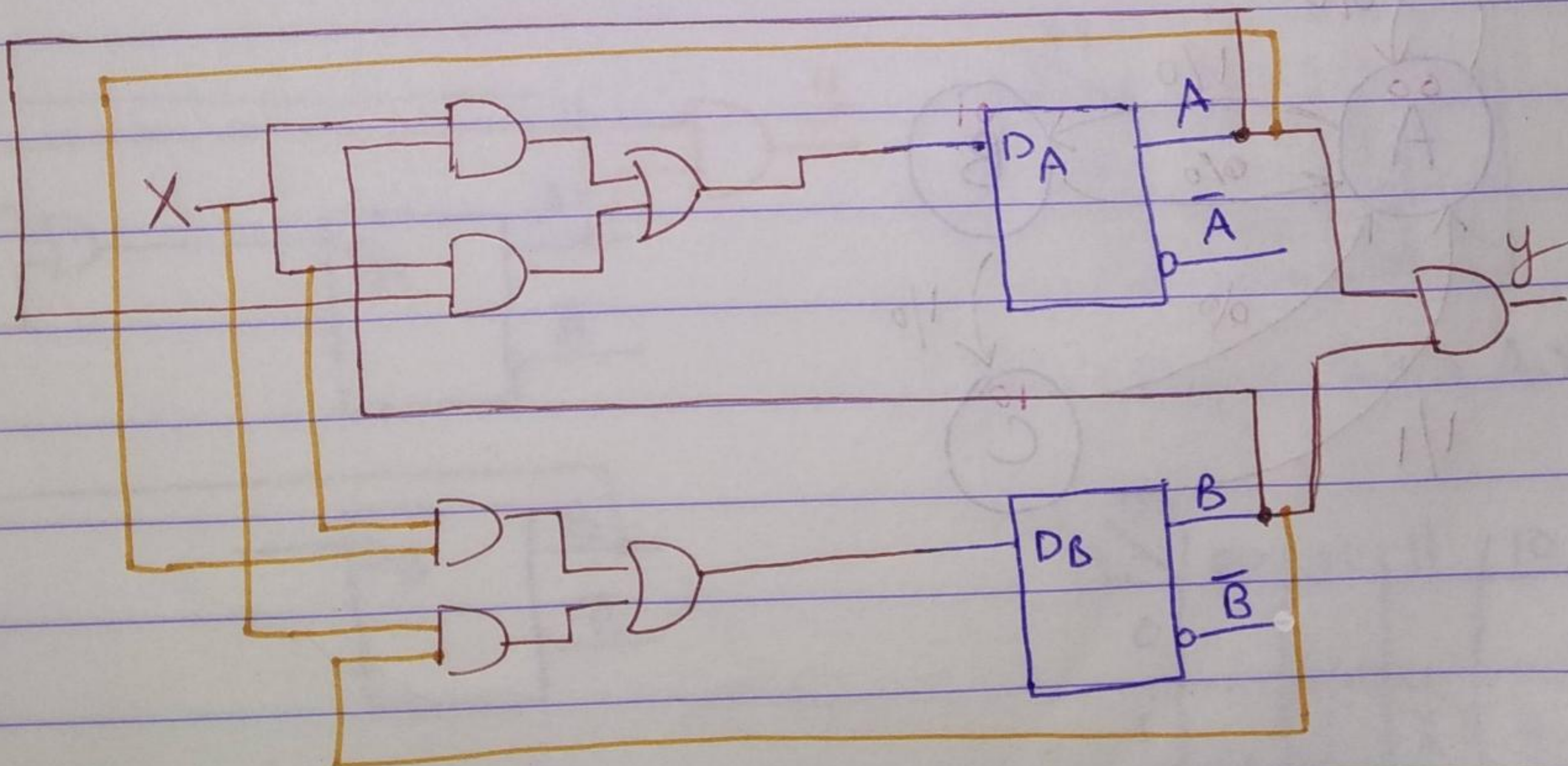


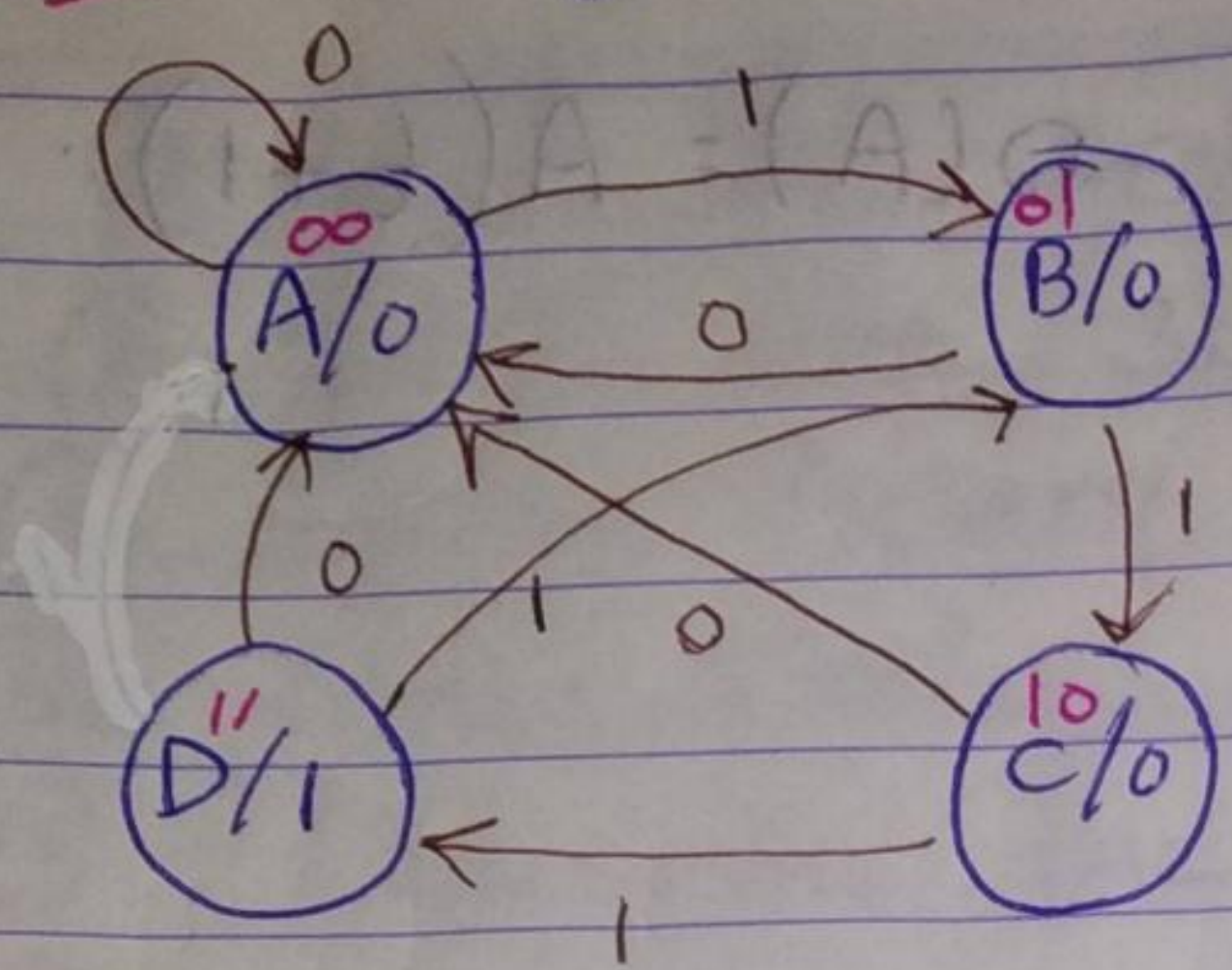ex Design to detect three consecutive ones?




| p.s | | input | N.s | | output |
|-----|---|-------|-----|---|--------|
| A | B | X | A | B | y |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 |

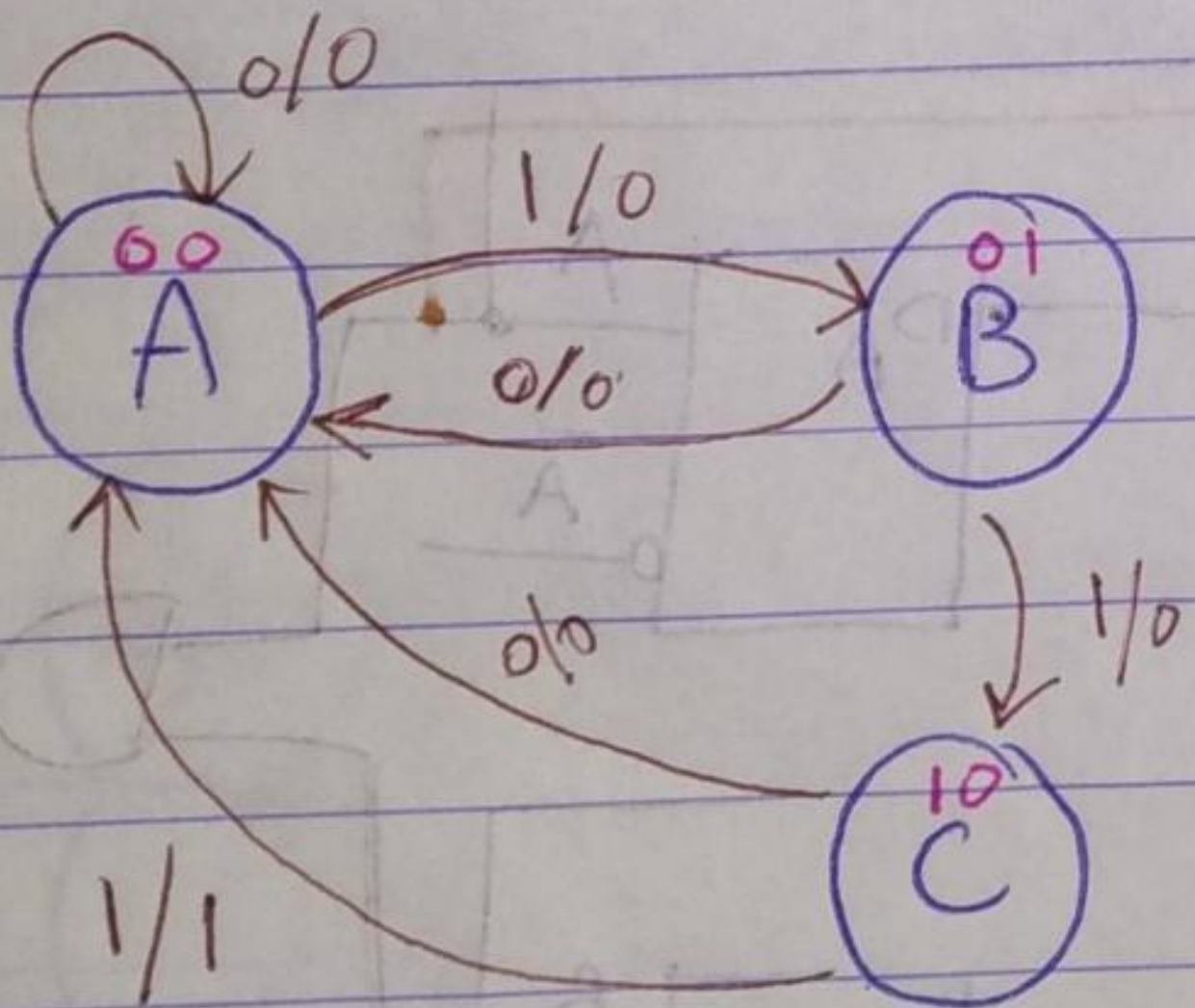ex Design a circuit to detect 3 consecutive ones? Mealy



ex Design synchronous sequential circuit to detect three or more consecutive ones?

mealy

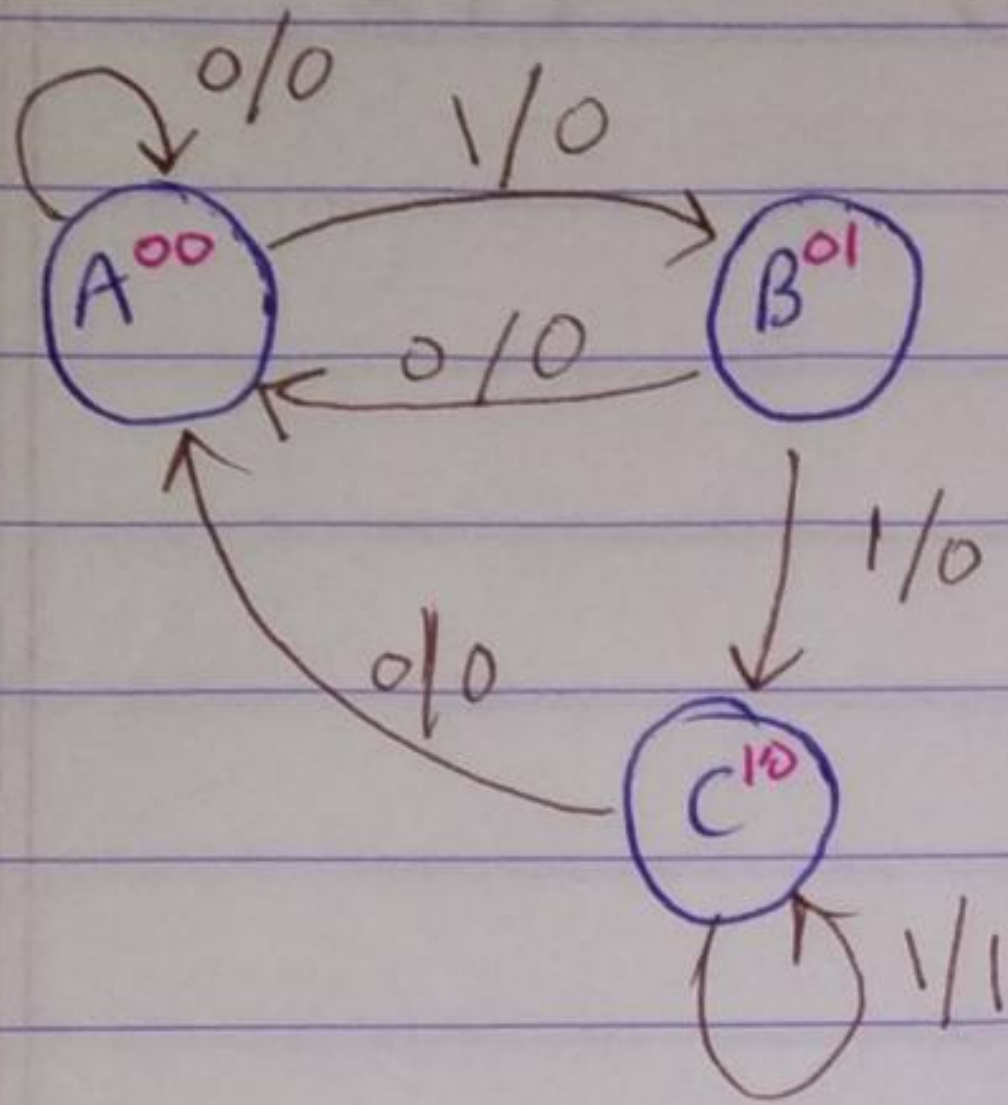


| P.S | | input | N.S | | output |
|-----|---|-------|-----|---|--------|
| A | B | x | A | B | y |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | X | X | X |
| 1 | 1 | 1 | X | X | X |

• Soooooo much

D-ff.

$$A(t+1) = D_A$$

$$B(t+1) = D_B$$

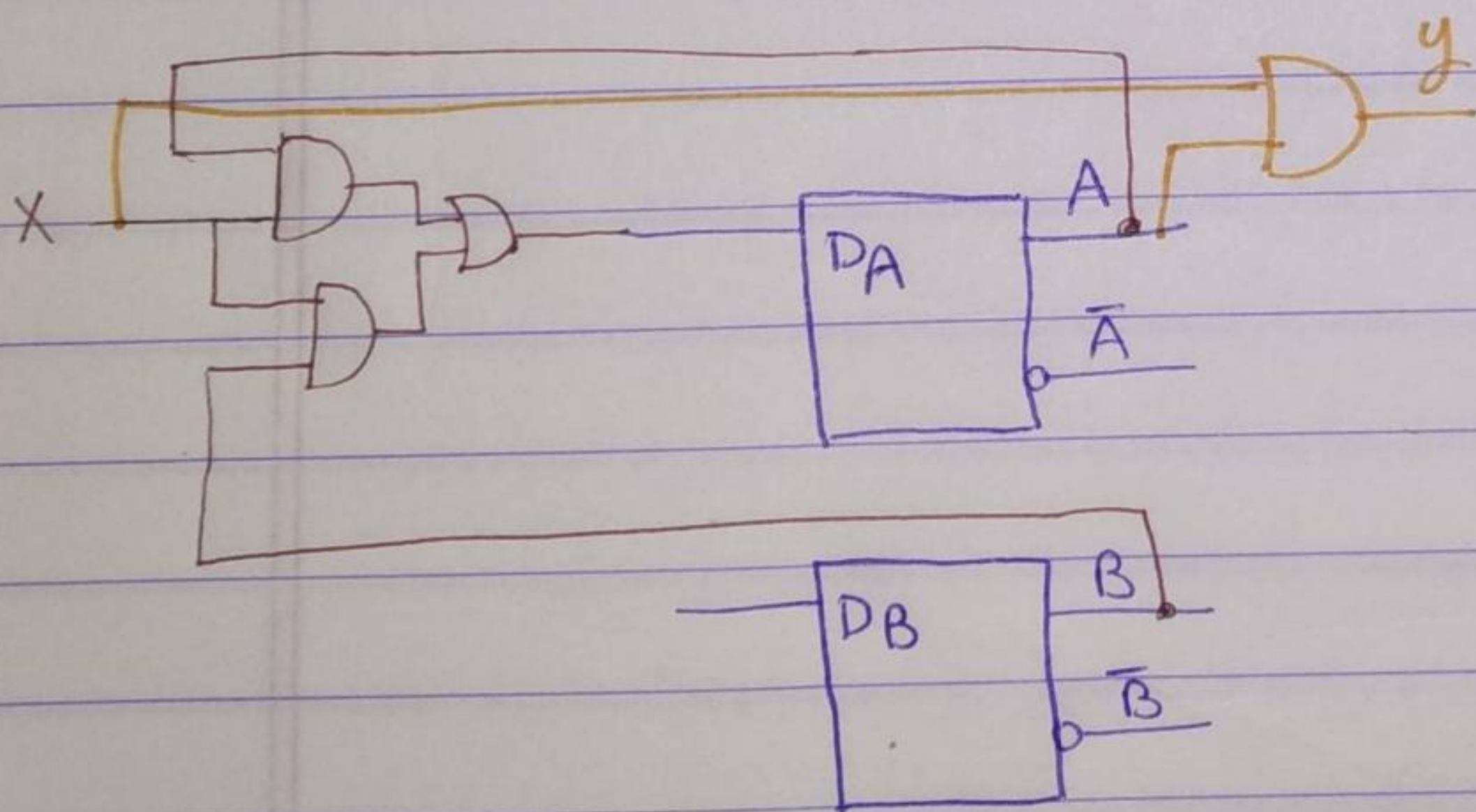

| A \ Bx | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | | | 1 | |
| 1 | | 1 | X | X |

$$D_A = B \cdot x + A \cdot x$$

| A \ Bx | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | | | | |
| 1 | | 1 | X | X |

$$y = A \cdot x$$

ex Design synchronous circuit to detect three or more ones? Consecutive

