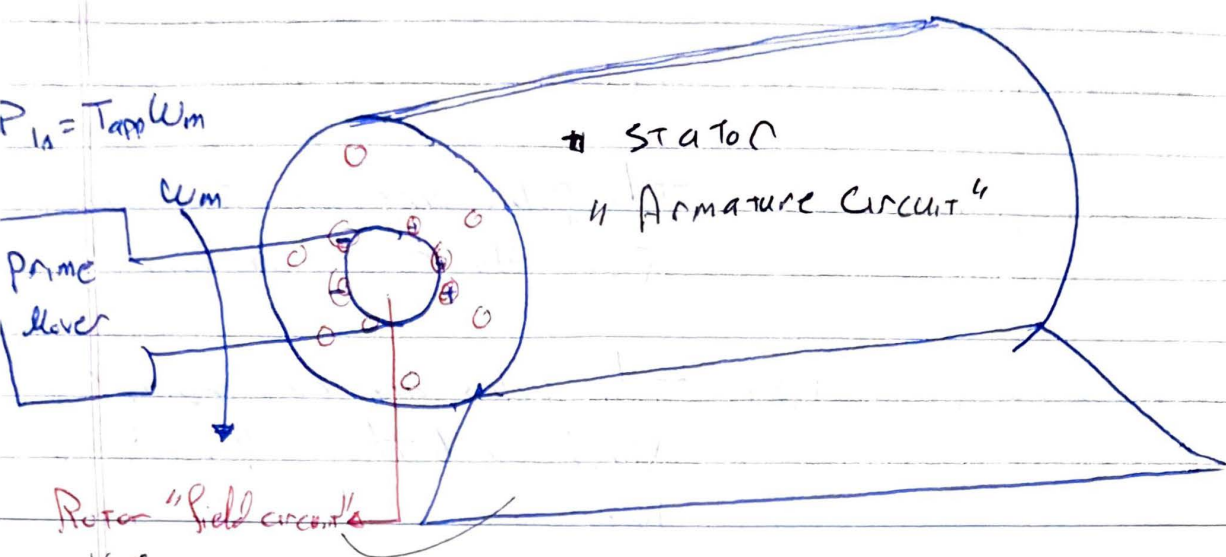


Synchronous Generator (SG)



flux

Prime mover: its the initial source of mechanical energy, it's any machine that converts fuel steam into a mechanical energy.

⊗ The synchronous generator has two main windings (flux is as 2nd)

1) Rotor or field winding where the machine flux is produced.

2) Stator or armature windings where the 3-φ voltage are induced (التي بـ 3φ قسمة)

⊗ Operating Principles

⊗ ~~A DC magnetic~~

⊗ A DC current is supplied to the rotor coil to produce a rotor magnetic field.


⊗ The Rotor rotates by means of external prime mover to produce a rotating magnetic field.

⊗ The rotating magnetic field will induce 3- ϕ Voltage across the stator (armature) winding.


⊗ Types of Rotor in Synchronous generator:

① Salient pole rotor ⅋ The poles are sticking out from the rotor surface.

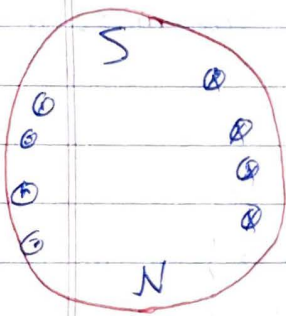② Cylindrical Rotor Type. The poles are constructed flush with the surface of the Rotor.



$P=2$, Cylindrical Type.

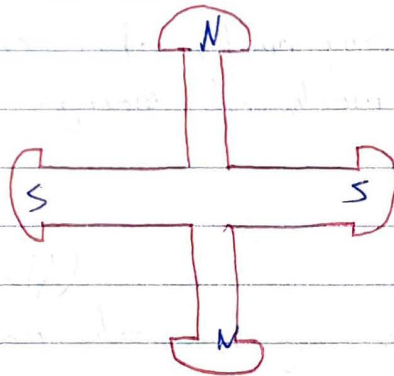


$P=4$
Salient-Pole Type

Note ⅋ when $P > 4$ Salient pole machine is selected
when $P = 2, 4$ Cylindrical is usually used.

⊗ Methods to feed the Rotor or field circuit

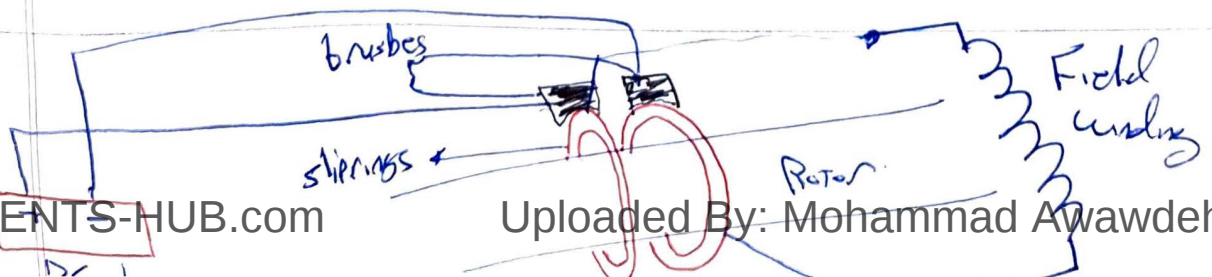① Sliprings & brushes ⅋
sliprings ⅋ Metal rings, encircling the shaft, but insulated.



Brushes go its a block of carbon compound that conducts electricity freely, but has very low friction.

This arrangement has two main problems :-


- 1) The brushes need regular maintenance.
- 2) The voltage drop across brushes may cause a power loss.

② Brushless exciter

③ Pilot excitor


Brushless excitor go its a small ac generator with its field circuit mounted on the stator of main generator, and its armature windings, mounted on the Rotor of main generator.

Don phase

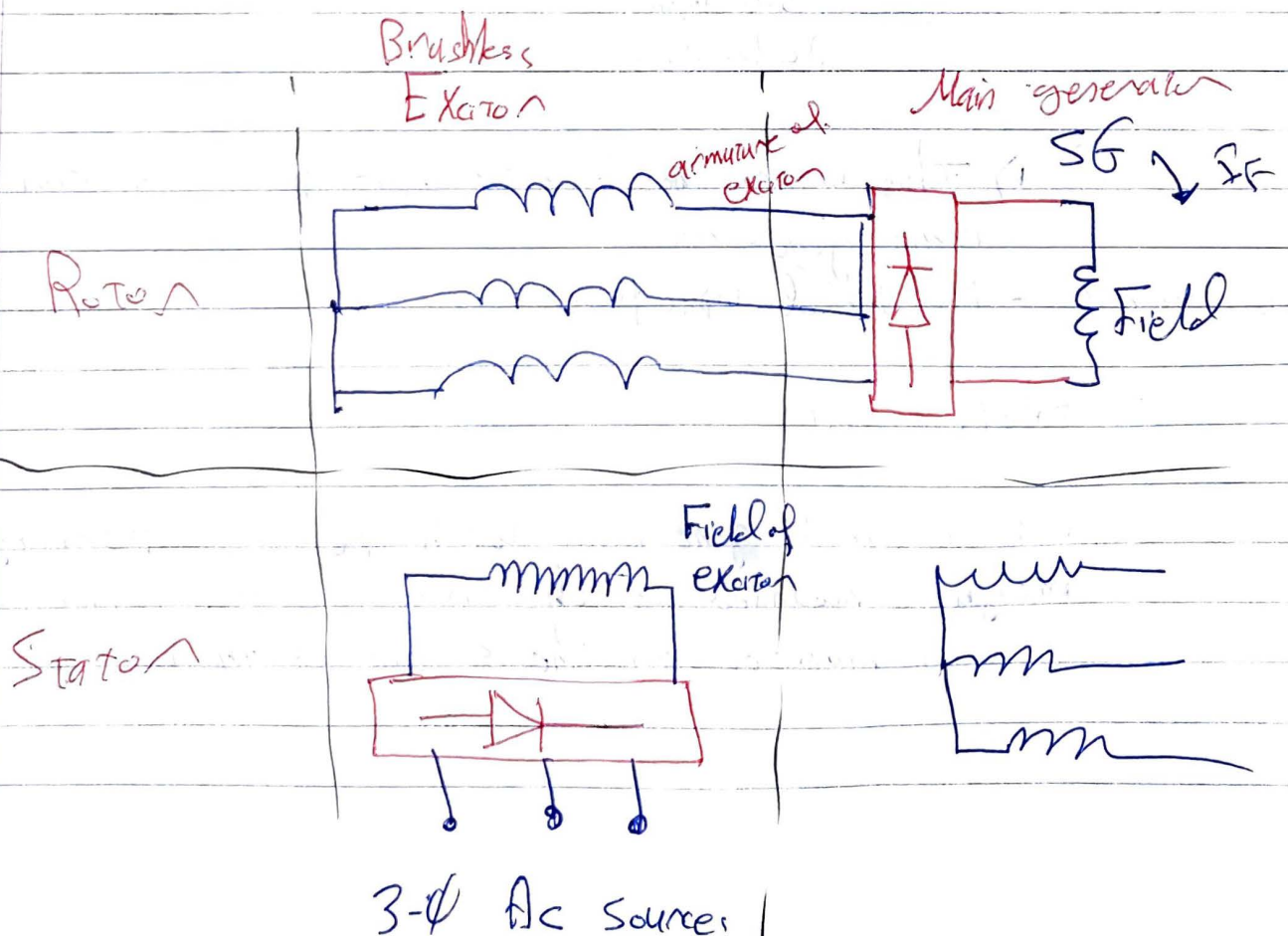

② Brushless exciter

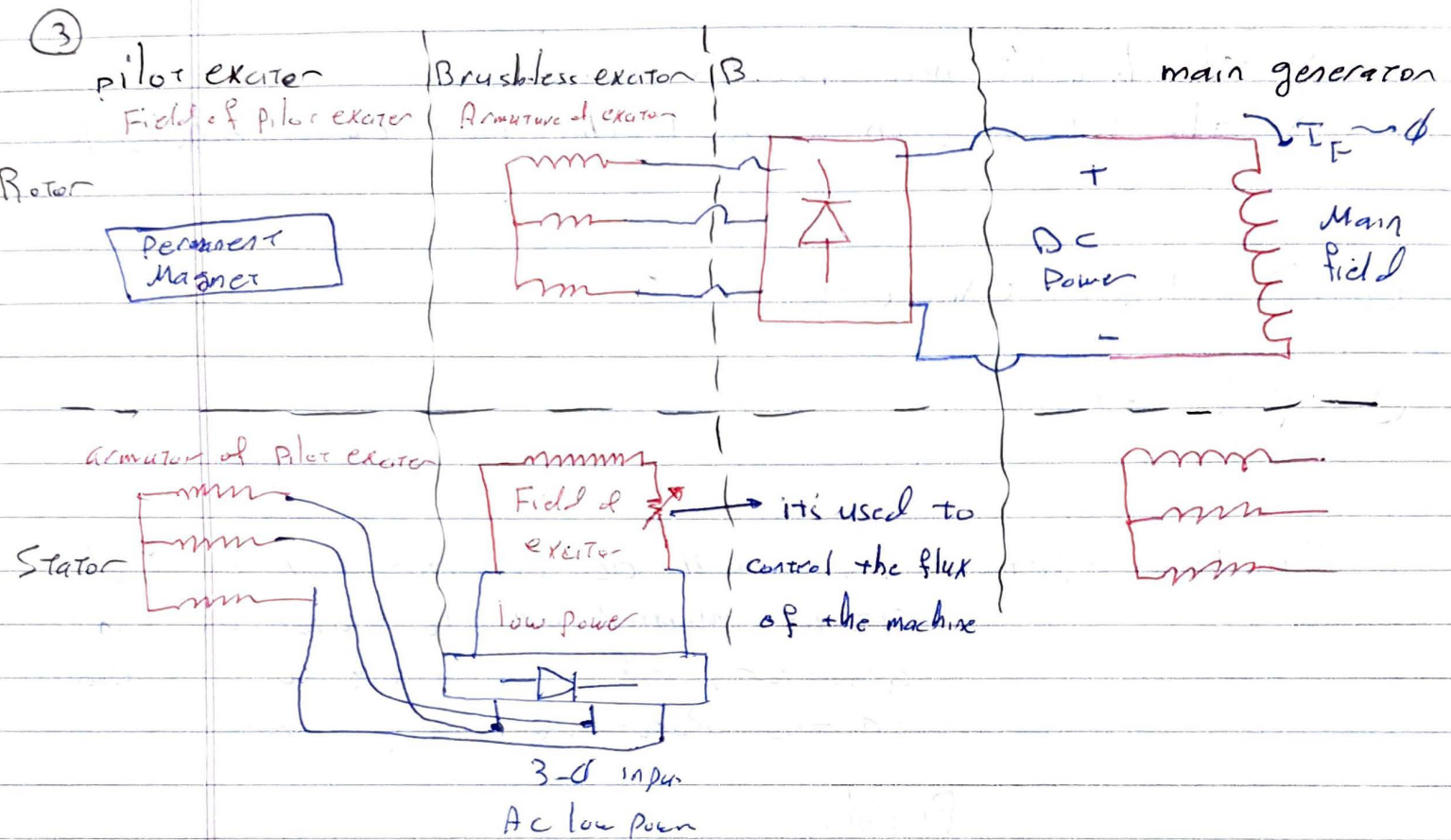it's a small AC generator with its field mounted on the stator and its armature mounted on the rotor.



Disadvantages ④ 1) This method needs a 3 ϕ input power to run the main generator.

Advantages - No Need input power

③ Pilot exciter

it's a small generator with ~~perameton~~ Permagneest magnet mounted on the rotor and its armature circuit mounted on the stator of the main generator.

The mechanical speed of SG

Synchronous → The mechanical speed is synchronized with the electric frequency.

$$n_m = n_s = \frac{120}{p} f_e$$

↓
Mechanical speed (Motor speed) → Synchronous speed

where p is the number of poles,
 f_e is the electric frequency

$$n [\text{rpm}] = 60 F [\text{Hz}] \quad \text{rev/sec.}$$

$$\omega_m = \frac{2}{p} \omega_e \quad \text{or} \quad \boxed{\omega_m = \frac{2}{p} \omega_e}$$

Internal or induced voltage of SG

The RMS value of L-N induced voltage, E_A , is given by

$$E_A = \frac{N_c \phi \omega_e}{\sqrt{2}} = \sqrt{2} \pi N_c \phi f_e$$

Armature →


In general, the induced voltage is given by

$$E_A = K \phi \omega_e$$


Flux of the machine
Speed of machine
Constant representing the construction of the machine

Note: $\phi \propto I_F \Rightarrow \phi = C I_F$

Constant

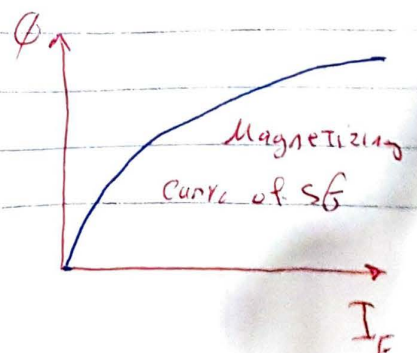

It is also called

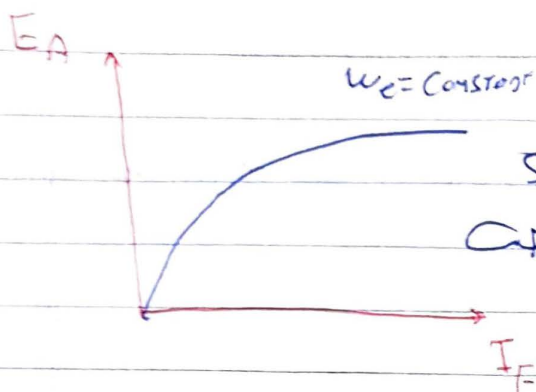

$$E_A = K\phi\omega_e = K\phi' = c'I_F$$


لأن ω_e ثابتة فإن E_A تتناسب طردياً مع ϕ أي مع I_F لأن ϕ يتناسب مع I_F في المنطقة الخطية من منحنى التبعثر.

اللمعة: $E_A = K\phi\omega$

Equivalent Circuit of SG

The terminal voltage, V_ϕ is different from the internal voltage, E_A of SG due to the armature reaction and the self impedance of the stator windings.

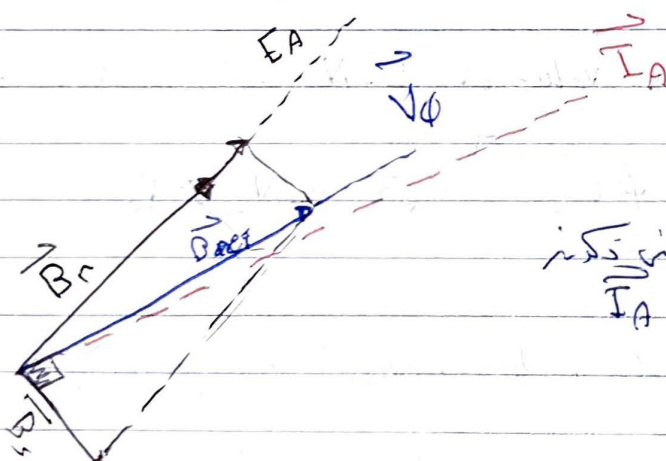Armature Reaction: Distortion of air gap magnetic field due to the current flowing in the stator windings.



في حالة الحمل المتأخر I_A يتسبب في إضعاف B

E_{stator}
Voltage due to
Reaction

$$\vec{V}_\phi = \vec{E}_A + \vec{E}_{\text{stator}}$$

$$\vec{E}_{\text{stator}} = -jX \vec{I}_A, \text{ where } X \text{ is the reaction of armature reaction.}$$

$$\vec{V}_\phi = \vec{E}_A$$

$$\vec{V}_\phi = \vec{E}_A - jX \vec{I}_A$$

we consider the self-impedance of the stator windings, the terminal phase voltage will be expressed as:


$$\vec{V}_\phi = \vec{E}_A - \underbrace{jX \vec{I}_A}_{\text{Self reactance}} - \underbrace{jX_A \vec{I}_A}_{\text{Self-reactance of stator winding}} - R_A \vec{I}_A$$

$$\vec{V}_\phi = \vec{E}_A - j(X + X_A) \vec{I}_A - R_A \vec{I}_A$$


$$\vec{V}_\phi = \vec{E}_A - jX_s \vec{I}_A - R_A \vec{I}_A$$

$$\text{where } X_s = X + X_A$$

$\rightarrow$ Synchronous reactance

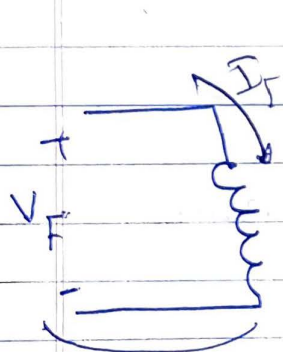





Field circuit

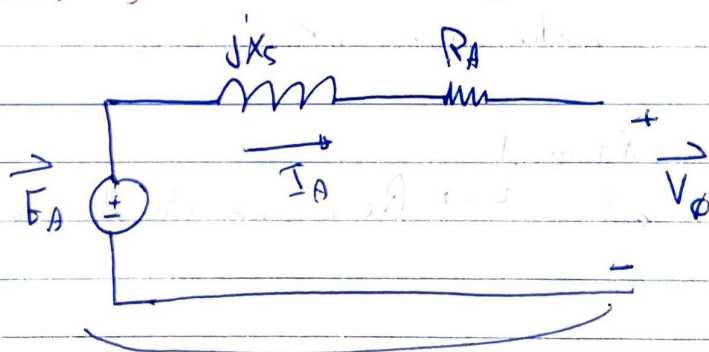

per-phase equivalent circuit

The full equivalent circuit of 3 ϕ SG

Dc supply

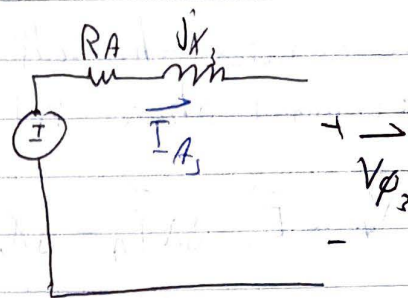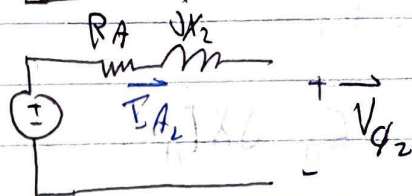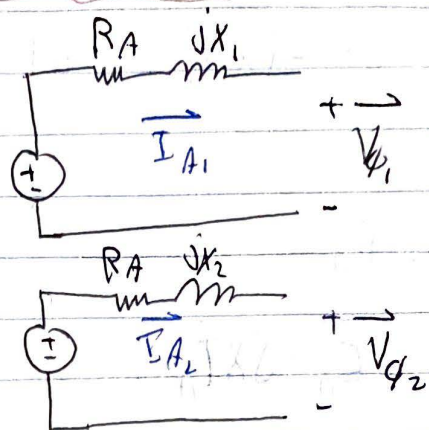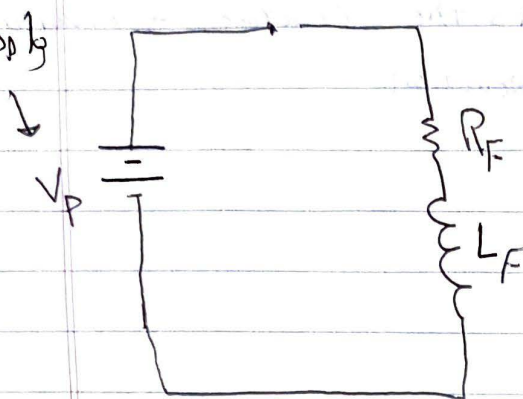

Field circuit
"Rotor"

Armature circuit
"Stator"

R_A : self-resistance of stator winding.

X_s : synchronous reactance

$$X_s = X_A + X$$

self-reactance
of stator winding

Reactance of Armature reaction

$$\left. \begin{matrix} B_r \\ B_s \end{matrix} \right\} \Rightarrow B_{net} \quad \swarrow \quad V_\phi$$

Δ - Connection

$$V_L = \sqrt{3} V_\phi$$


$$\vec{I}_L = \vec{I}_\phi + \vec{I}_A$$

Y - Connection

$$V_L = V_\phi$$

$$I_L = \sqrt{3} V_\phi = \sqrt{3} I_A$$

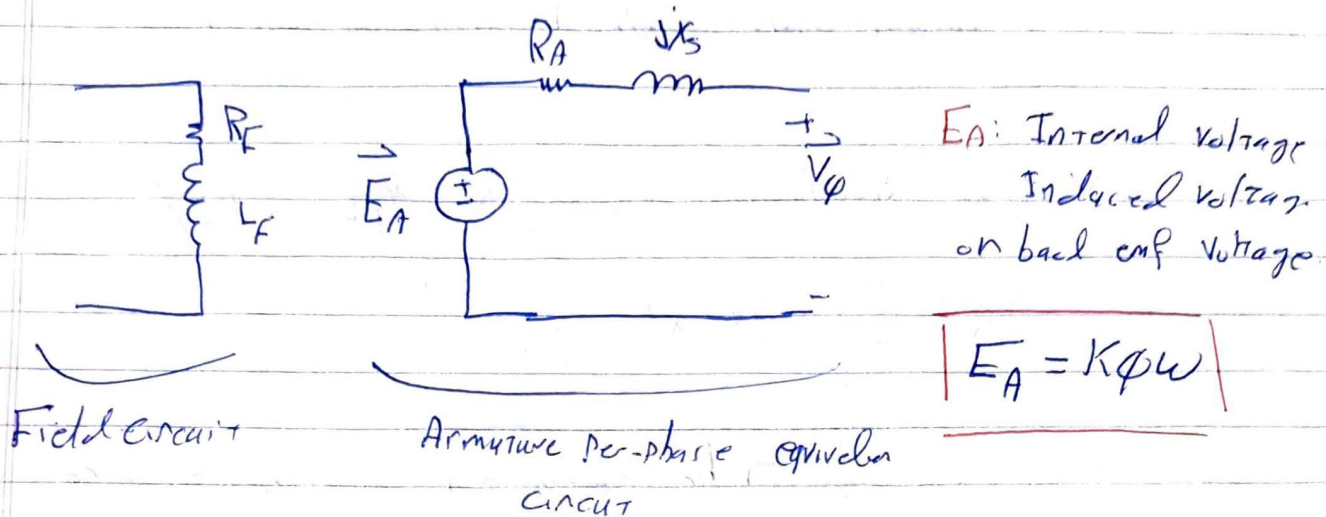The per phase equivalent circuit and machine KVL equation



Machine KVL equation:-

KVL in the armature per-phase equivalent circuit:-

$$\vec{E}_A = R_A \vec{I}_A + jX_s \vec{I}_A + \vec{V}_\phi$$


⊗ Phasor Diagram

$$\vec{E}_A = \vec{V}_\phi + R_A \vec{I}_A + jX_s \vec{I}_A$$

⊗ Assume that the Reference angle of $\vec{V}_\phi$ is zero

$$\Rightarrow \vec{V}_\phi = V_\phi \angle 0^\circ$$

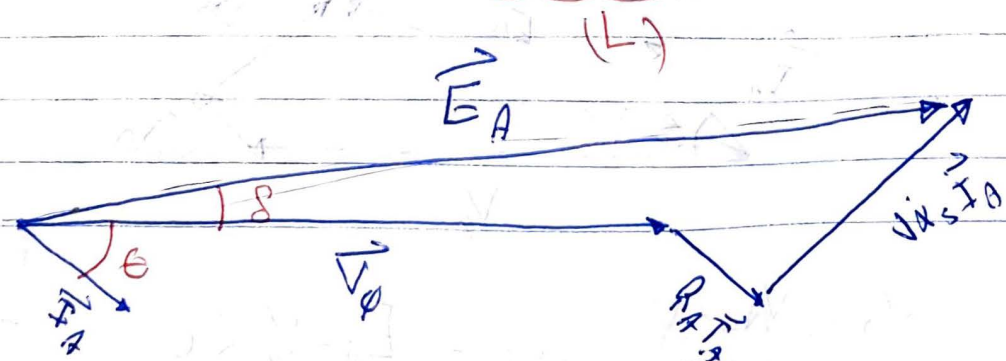① Lagging PF operation $\Rightarrow$ The SG is connected to an inductive load.




θ = PF angle
 δ = Torque angle (angle between $\vec{V}_\phi + \vec{E}_A$)

$$\text{Voltage Regulation} = V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$V_R = \frac{E_A - V_\phi}{V_\phi} \times 100\% > 0$$

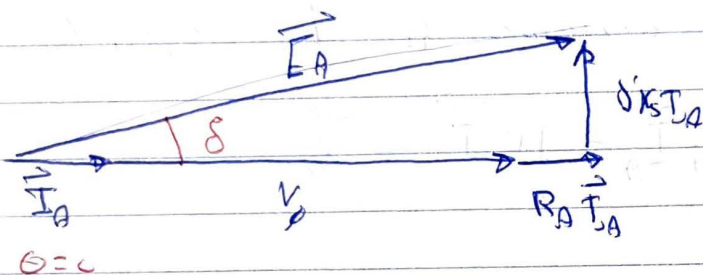② unity PF $\Rightarrow$ The generator is connected to a resistive load (R)




$$V_\phi < E_A$$

$$V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\% = \frac{E_A - V_\phi}{V_\phi} > 0$$

$$V_{R_{\text{unity}}} < V_{R_{\text{lagging}}}$$

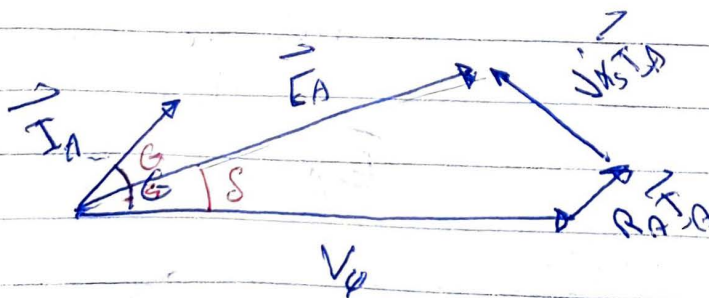② Leading PF $\rightarrow$ The generator is connected to a capacitive load (C)




$$V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\% = \frac{E_A - V_\phi}{V_\phi} < 0$$

$$[V_\phi > E_A]$$

Power and Torque equations.

- Power flow diagram

$$P_{in} = T_{app} \omega_{rms}$$

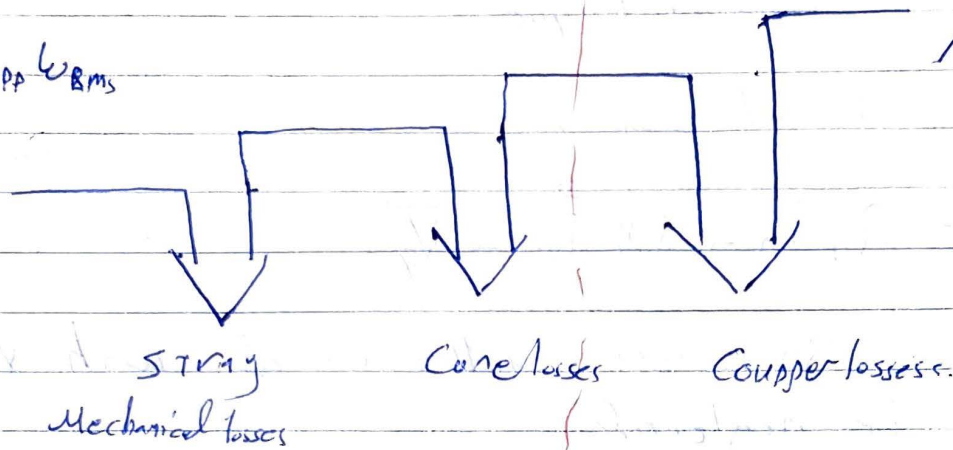

$$P_{out} = 3 V_{\phi} I_{\phi} \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$Q_{out} = 3 V_{\phi} I_{\phi} \sin \theta = \sqrt{3} V_L I_L \sin \theta$$

γ - Connections

Δ - Connections

$$V_L = \sqrt{3} V_{\phi}$$


$$I_L = I_{\phi}$$

$$V_L = V_{\phi}$$

$$I_L = \sqrt{3} I_{\phi}$$

T_{app} : Applied Torque

ω_{rms} : Synchronous speed.

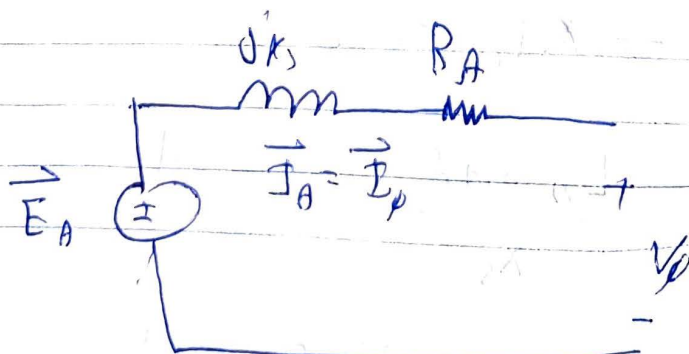

3-φ

$$P_{\text{conv}} = T_{\text{ind}} \omega_{ms} = 3 E_A I_A \cos \delta$$

Power converted
into electrical


T_{ind} = Induced torque, or developed torque or electro magnet torque

ⓐ Assume that the generator is connected to 3-φ inductive load

$$\vec{E}_A = R_A \vec{I}_A + jX_s \vec{I}_A + \vec{V}_\phi$$

Since R_A is very small compared with X_s its can be neglected.
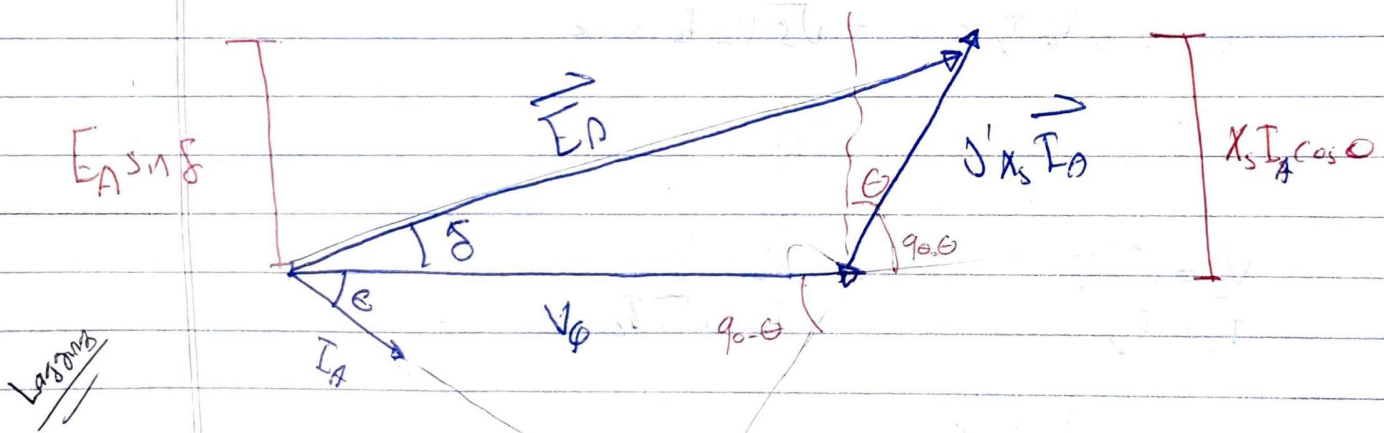
$$\vec{E}_A = jX_s \vec{I}_A + \vec{V}_\phi$$



From the phasor diagram

$$E_A \sin \delta = X_s I_A \cos \theta$$

$$\Rightarrow I_A \cos \theta = \frac{E_A \sin \delta}{X_s} \quad \times 3V_\phi$$

P_{conv} vs des gp

$$3 V_\phi I_A \cos \theta = 3 V_\phi E_A \sin \delta$$

$$\Rightarrow P_{out} = 3V_{\phi} I_A \cos \theta = \frac{3V_{\phi} E_A}{X_s} \sin \delta = P_{conv}$$

R_A is ignored

$$P_{conv} = T_{ind} \omega_{ms} = \frac{3V_{\phi} E_A}{X_s} \sin \delta$$

Machine Rated δ
0.88590

$$T_{ind} = \frac{3V_{\phi} E_A}{X_s \omega_{ms}} \sin \delta \rightarrow \text{Torque angle}$$

The maximum output power is ω .

$$P_{max} = \frac{3V_{\phi} E_A}{X_s} \Rightarrow \sin \delta = 1 \Rightarrow \delta_{max} = 90^\circ$$

(0.88590)

$\hookrightarrow$ This is the steady state stability limit.

Effect of load changes on SG operation.

Assume that - SG is connected to a 3 ϕ inductive load

- $E_A = \text{constant}$


Speed of prime mover = constant

Machine flux = constant

- R_A is ignored

- load increases at the same PF angle

□

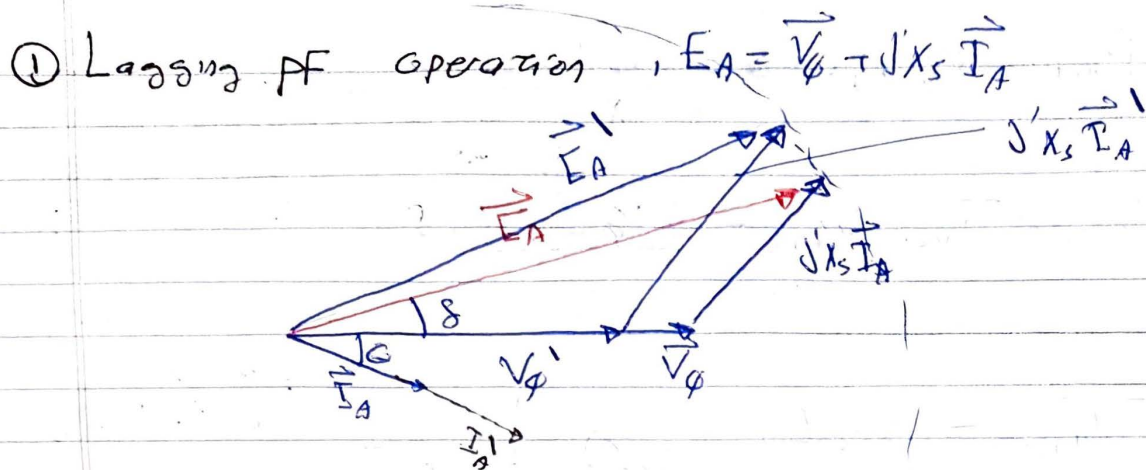


The phase voltage decreases as the load increases

AVR or Automatic Voltage Regulator


→ its a closed loop controller to keep the phase voltage of generator constant.

② unity PF

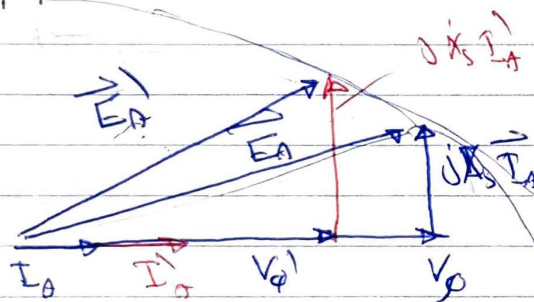


V_ϕ decreases as the load increases.

③ leading PF

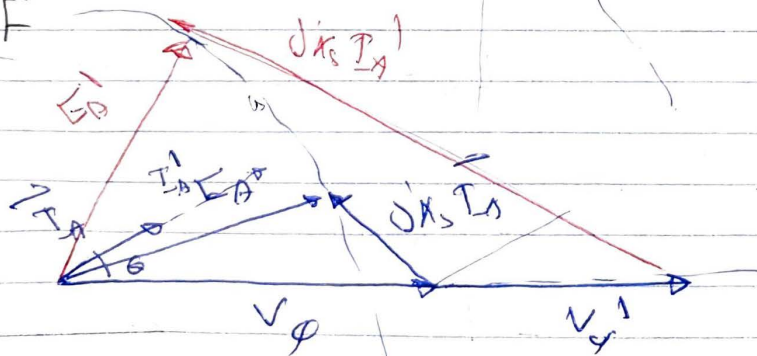

Parallel operation of Synchronous Generators

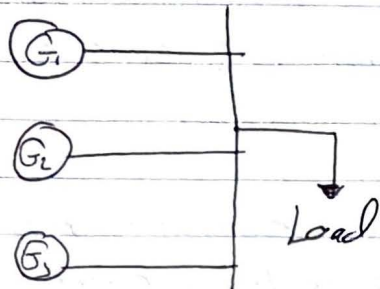
other than emergency generator, rarely there is a case where a single isolated generator supplies a load.



Major advantages

- 1) supplies a larger load
- 2) high reliability of power system
- 3) Allows one or more generator to be removed for shutdown & preventive maintenance.
- 4) if only one generator is used, and it's run running of full-load, it's a very inefficient process.

Conditions required for paralleling.


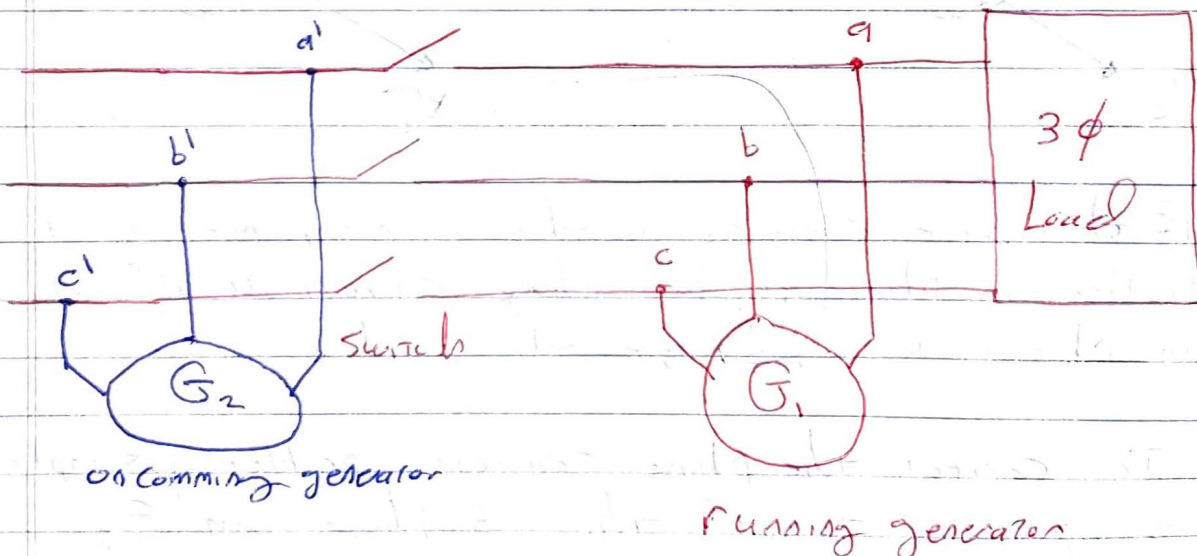


- 1) The generator ^{must} have the same Rms Line Voltage

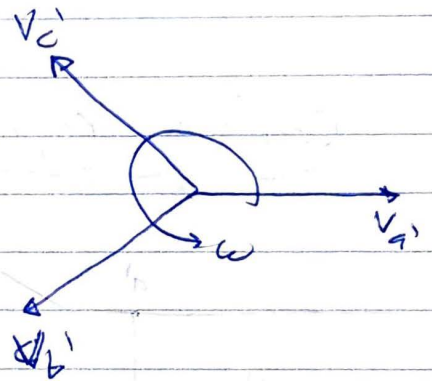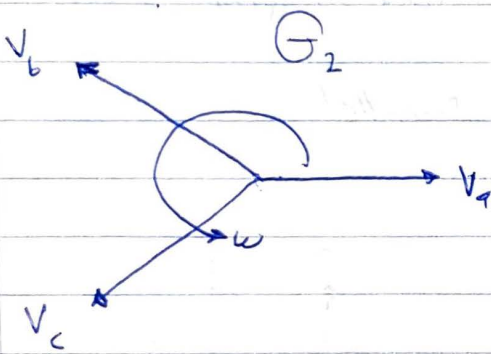- 2) The generator, must have the same phase sequence.
- 3) The phase angle of two "a" phases, "b" phases or "c" phases must be the same
- 4) The frequency of the oncoming generator must be slightly higher than the frequency of running generator.

Point ① → The RMS line voltages of the two generators must be the same to avoid any huge circulating current flowing the phases and damaging the generator.

Point ② → Assume the generators have an opposite phase sequence.





⊗ if they were connected in this manner, there would no problem in phases (a), but a huge current would flow in phases b & c, damaging the machine.

Solution →


To correct the phase sequence problem, simply swap any two of the 3 phases on G_2 .

Point 384 ω Assume that the frequency of G_1 is $\omega_1 = 2\pi f_1$, and the frequency of G_2 is $\omega_2 = 2\pi f_2$

Assume that $\omega_2 > \omega_1$

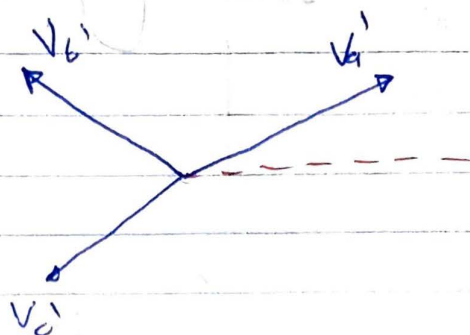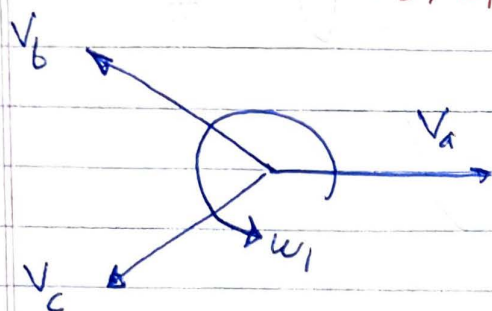

"In phase"

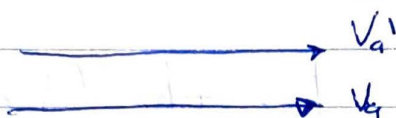


"out of phase"




Case 1 $\omega_1 \neq \omega_2$, but the difference is high


$$V_b = A \sin(2\omega_1 t)$$

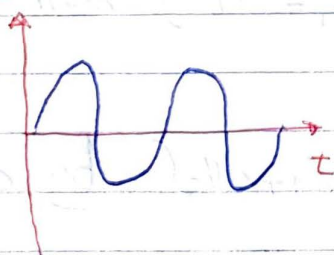

ON-OFF quickly

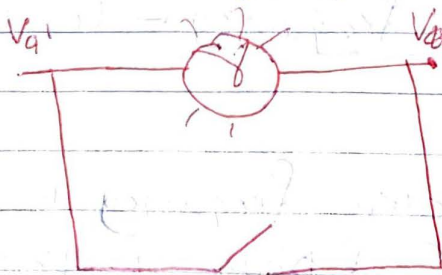

$$V_a = A \sin(\omega_1 t)$$

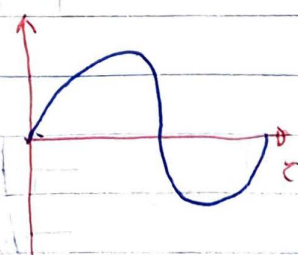

$$PD = V_a - V_a'$$


* Potential difference

$$\text{Flicker} = \omega_2 - \omega_1$$

$$\text{frequency} = \omega$$


120 out of 1 phase

$V_a = V_{a'}$
in phase

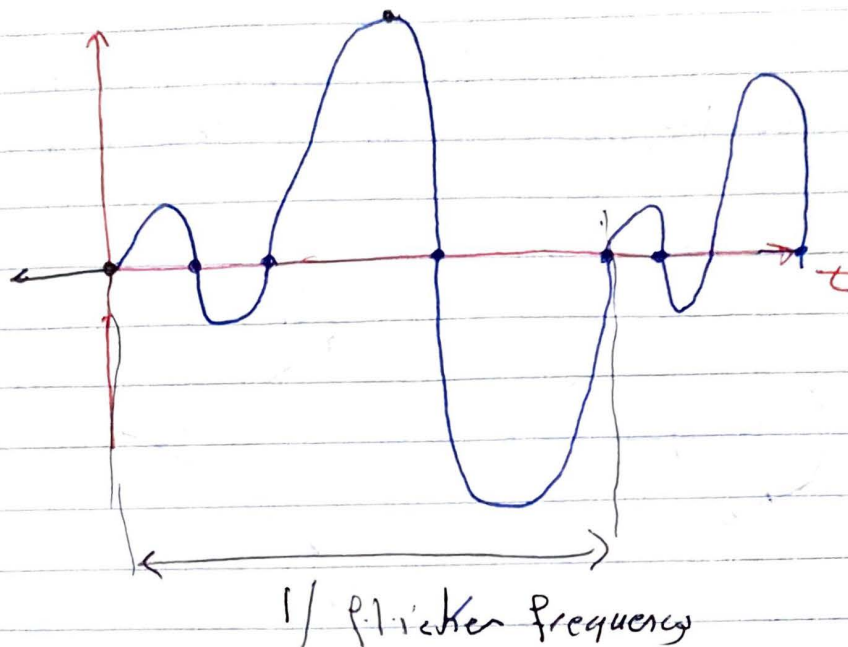

Case 2

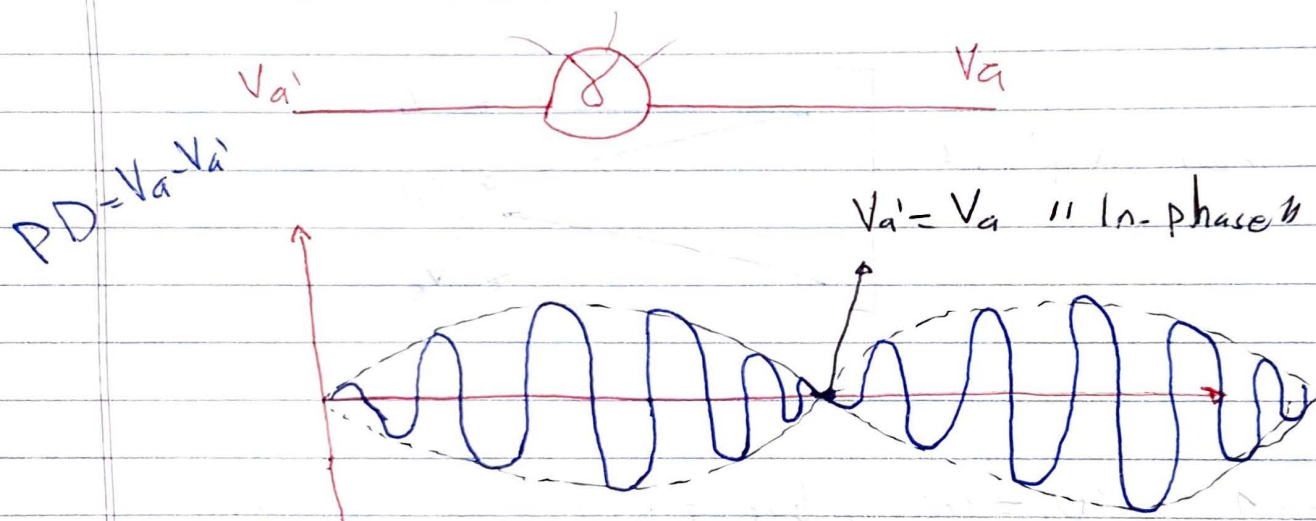$\omega_1 \neq \omega_2$ but the difference is very small



Flicker frequency = $\omega_2 - \omega_1$ = very small

Notes


The electric frequency is controlled by changing the speed of prime mover

$$M_m = \frac{120 f_e}{P}$$

$$M_m \uparrow \Rightarrow f_e \uparrow$$

$$M_m \downarrow \Rightarrow f_e \downarrow$$

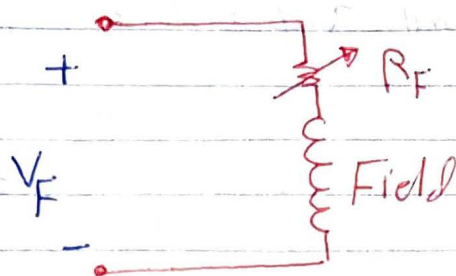Note The terminal voltage is controlled by changing the field current.




$$R_F \uparrow \Rightarrow (I_F = \frac{V_F}{R_F}) \downarrow \Rightarrow \phi \downarrow \Rightarrow E_A \downarrow \Rightarrow V_t \downarrow$$

$$R_F \downarrow \Rightarrow I_F \uparrow \Rightarrow \phi \uparrow \Rightarrow E_A \uparrow \Rightarrow V_t \uparrow$$

⊗ procedure of synchronizing


Switches

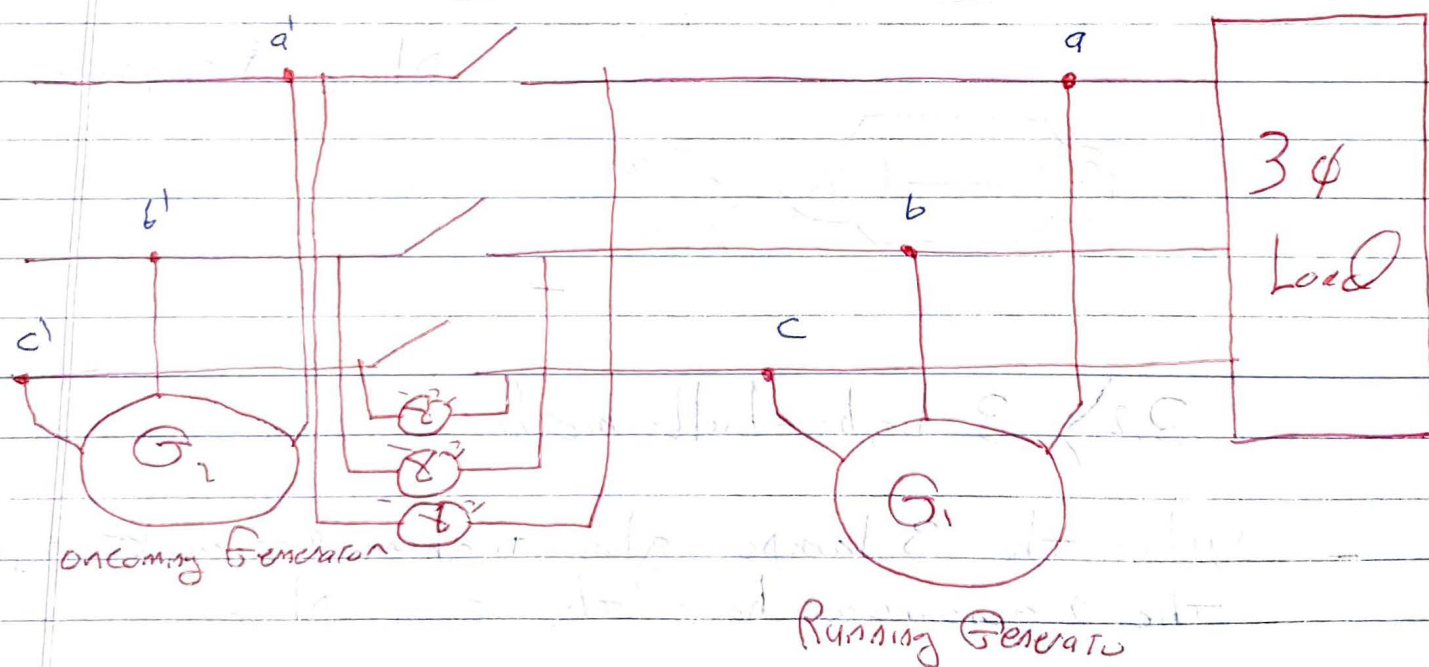



- 1) Adjust the speed of G_2 to match that of G_1 .
- 2) Using voltmeters, adjust I_F of G_2 to make the (V_T) terminal voltage of G_2 equals the terminal rms voltage of G_1 .

3) phase-sequence


3.1) small 3- ϕ induction motor method.

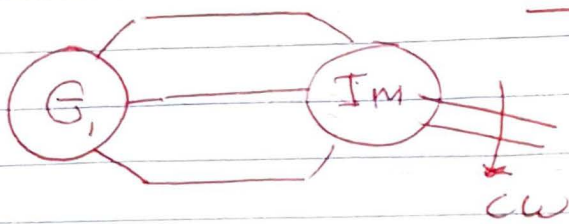

They have
the same phase
sequence.

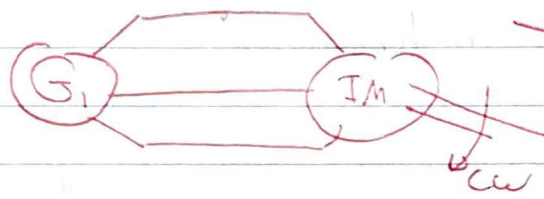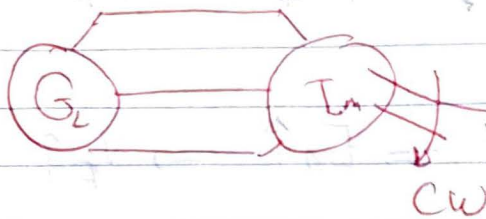

They have opposite
phase sequence

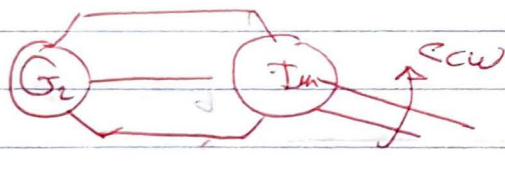


3.2) 3 light-bulbs method.

- When the 3 lamps glow together & turn off together
The 2 generators have the same phases

- When the 3 lamps glow in succession, then the
2 generator have opposite phase sequence.

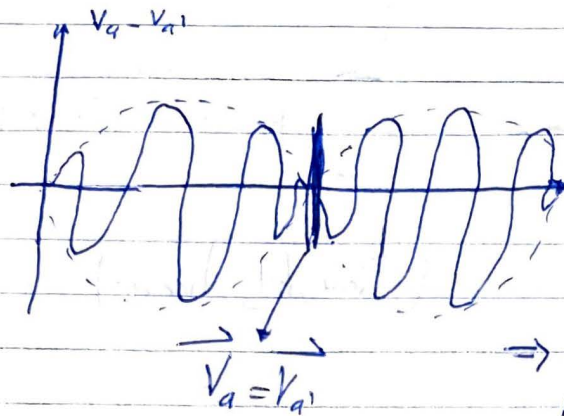
4) Frequency of G_2 is slightly higher than the frequency of G_1 .



when the 3 lamps go out V_a & $V_{a'}$ are in phase, and paralleling can be done.

⇒ This method is not very accurate. A better method should be used (synchroscope).

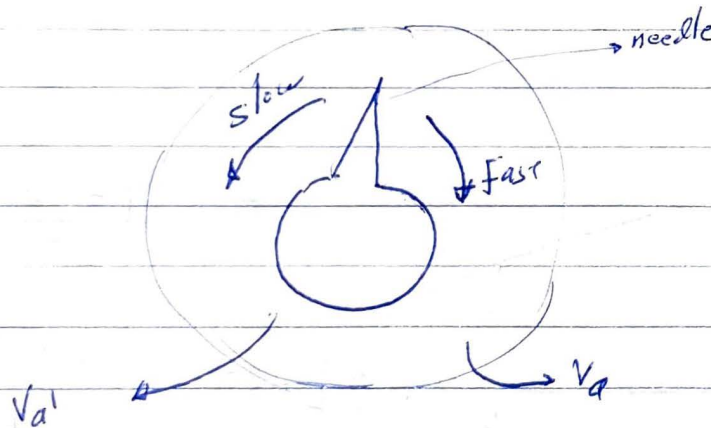Synchroscope → Device that gives an indication about the phase shift between V_a & $V_{a'}$.




$f_2 > f_1 \Rightarrow$ CW Rotation (Fast)



$f_2 < f_1 \Rightarrow$ CCW Rotation (Slow)

When the needle is in the vertical position, V_a is in phase with $V_{a'}$ and paralleling can be done.

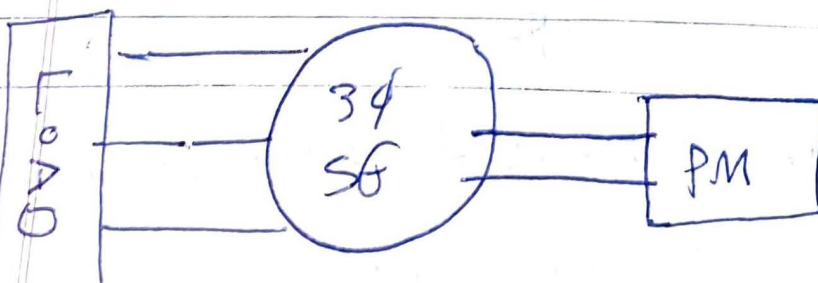
Frequency-power and Voltage-reactive power characteristics of generator.



wind turbine
water turbine

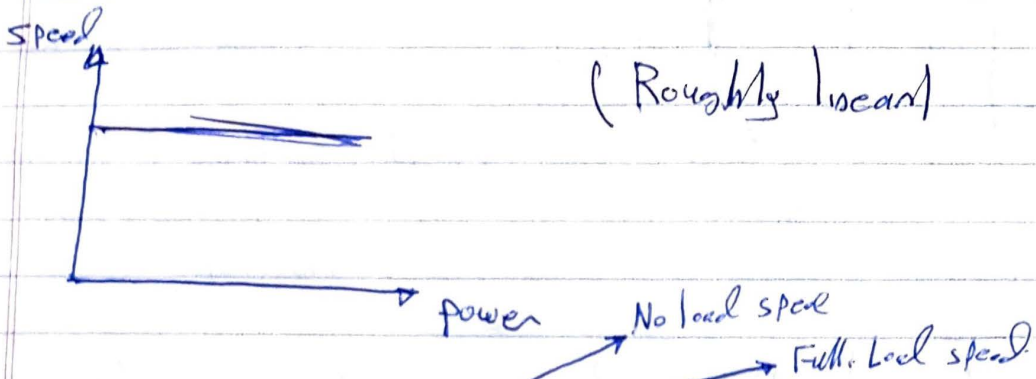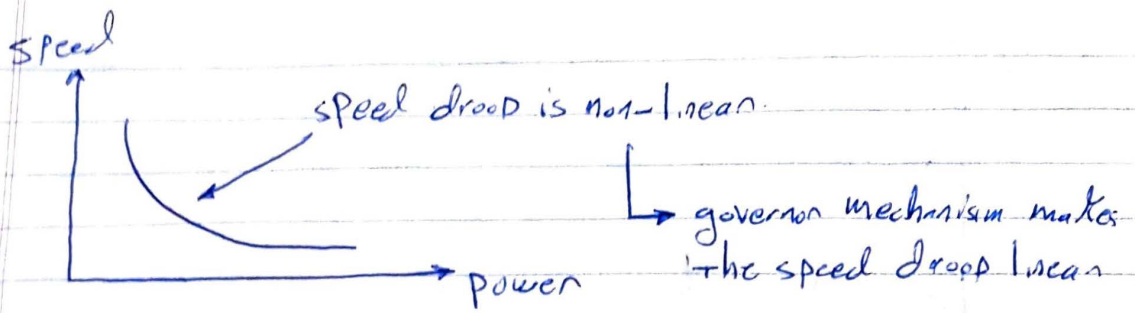

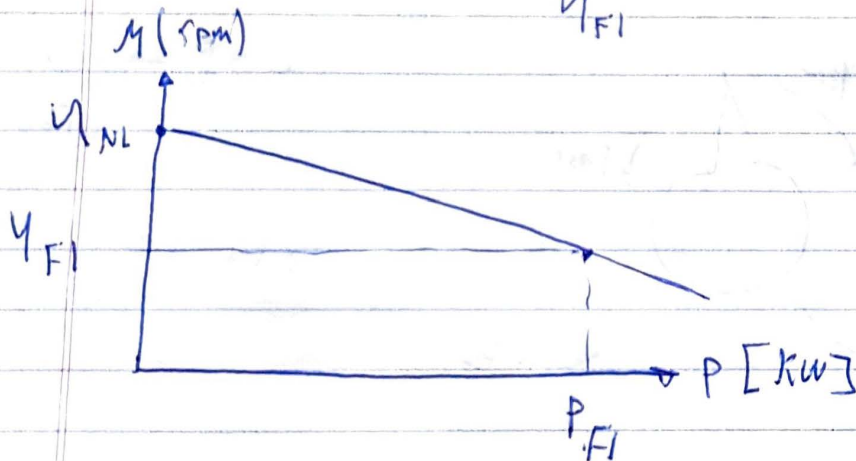
$$\text{Speed Drop} = SD = \frac{\omega_{NL} - \omega_{FL}}{\omega_{FL}} \times 100\%$$



$$\eta = \frac{120}{P} \%$$

$$f = \frac{n P}{120}$$

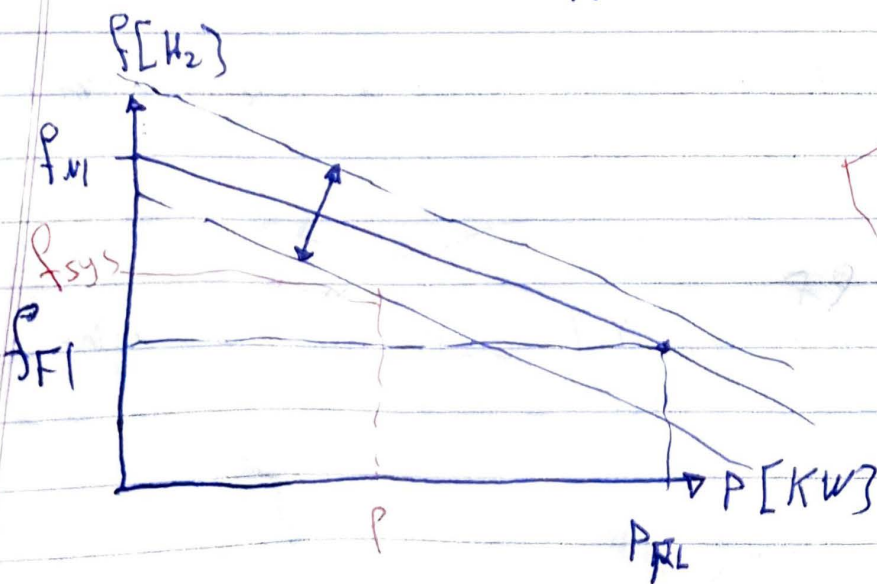

Speed governor

By adjusting the setpoint of the speed governor, we can

$$\text{slop} = \frac{g_2 - g_1}{x_2 - x_1} = \frac{P_{FI} - P_{NL}}{P_{FI}} \quad [\text{Hz/KW}]$$

$$P_{FI} = \frac{1}{\text{slop}} [P_{FI} - P_{NL}] = \frac{1}{\text{slop}} [P_{NL} - P_{FI}]$$

In general,
$$P = S_p [f_{NL} - f_{sys}]$$

System frequency

where S_p is the power slop $[\text{KW/Hz}]$.

⊗

Voltage-Reactive Power characteristic


$$S_p = \frac{(P)_{\max}}{S_{NL} - P_{FI}}$$

lagging load $\uparrow \Rightarrow$ The load absorbs more ϕ

$\Rightarrow$ The generation supplies more $\phi \Rightarrow V_T \downarrow$

$\Rightarrow$ The characteristic is non-linear

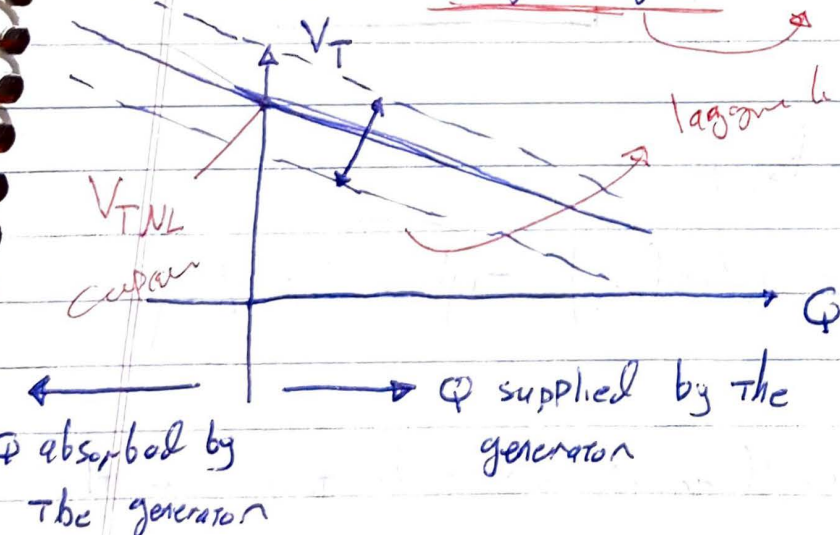$\Rightarrow$ The AC voltage regulation makes it linear.




AC Voltage Regulation

By adjusting the set points of the AC voltage regulator we can increase or decrease the no load terminal voltage

Example

$$f = 61 \text{ Hz}$$

$$S_p = 1 \text{ MW/Hz}$$

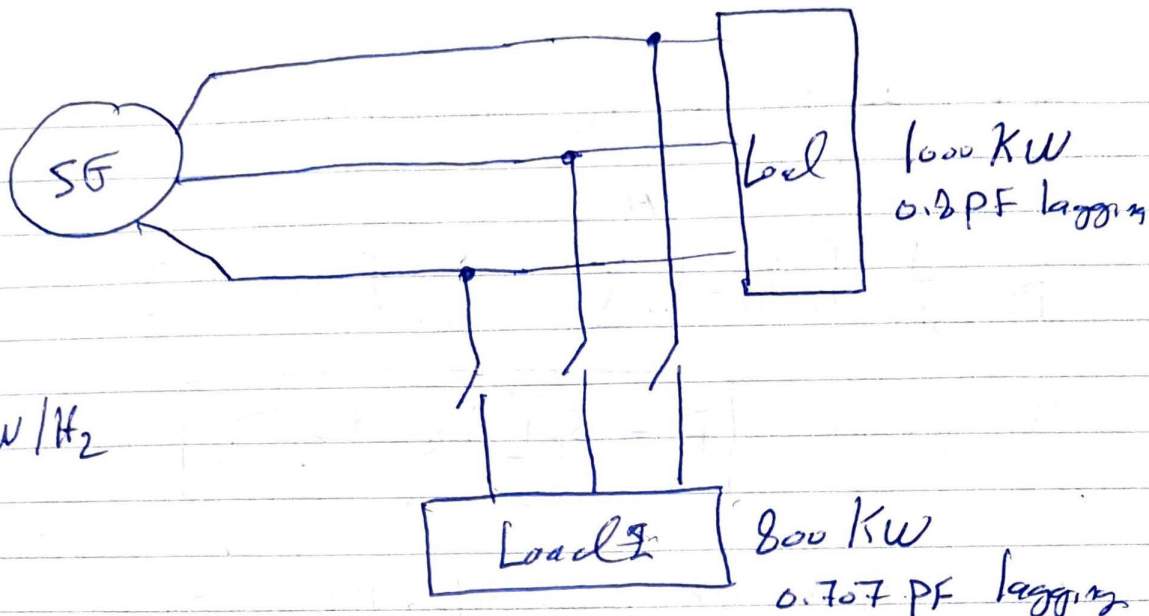

- a) before the switch is closed, what is the operating frequency of the system
- b) After, load 2 is connected, what is the operating frequency of the system

Solution

$$a) P = S_p (f_{NL} - f_{sys})$$

$$1000 = 1000 (61 - f_{sys}) \Rightarrow f_{sys} = 60 \text{ Hz}$$


$$b) P = S_p (f_{NL} - f_{sys})$$

$$1000 + 800 = 1000 (61 - f_{sys}) \Rightarrow f_{sys} = 59.2 \text{ Hz}$$

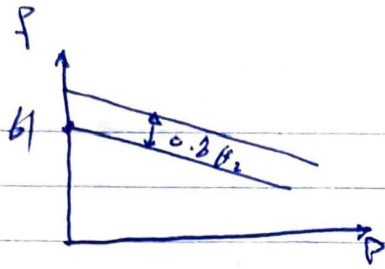c) what action could an operator take to restore the system frequency.


$$P = S_p (f_{NL} - f_{sys})$$

$$1000 + 800 = 1000 (f_{NL} - 60) \Rightarrow f_{NL} = 61.8$$





⊕ Parallel operation of Generators with large power system


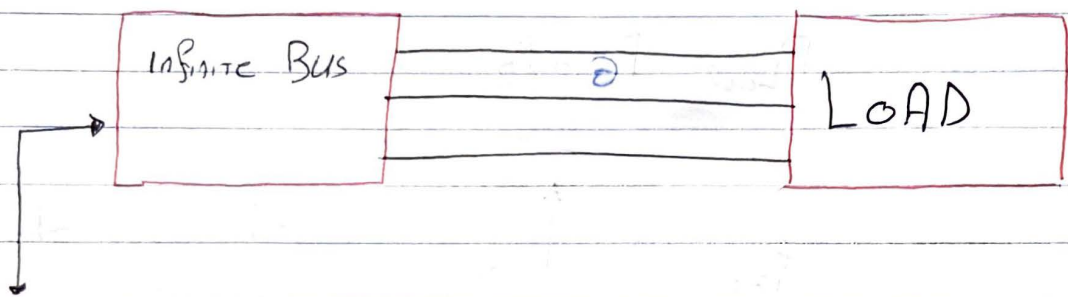
Infinite Bus is a large power system that its voltage and frequency do not vary regardless of how much power are drawn from or supplied to it.




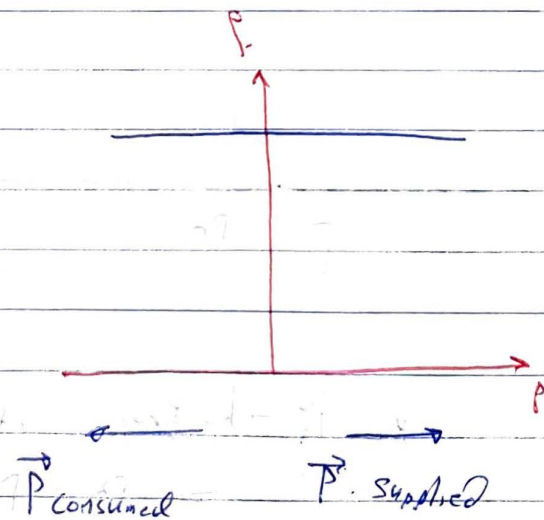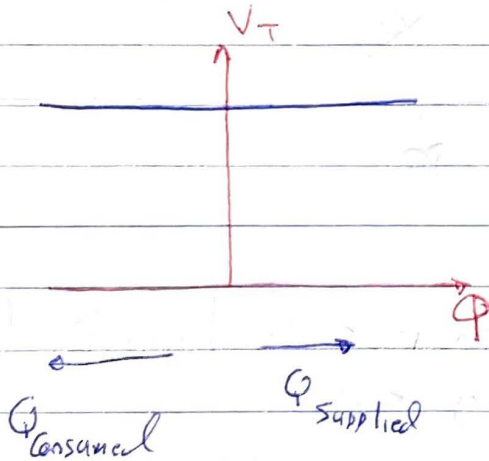high number of parallel connected generators in power station



⊕ Parallel operation

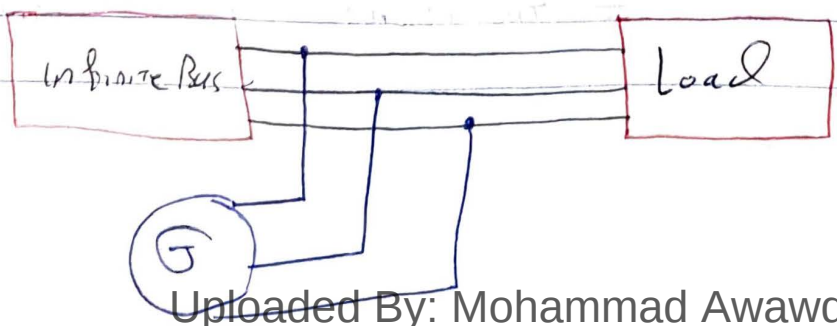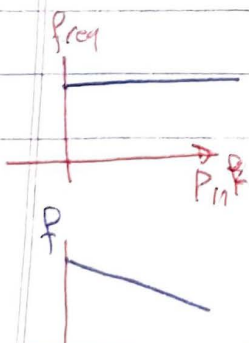


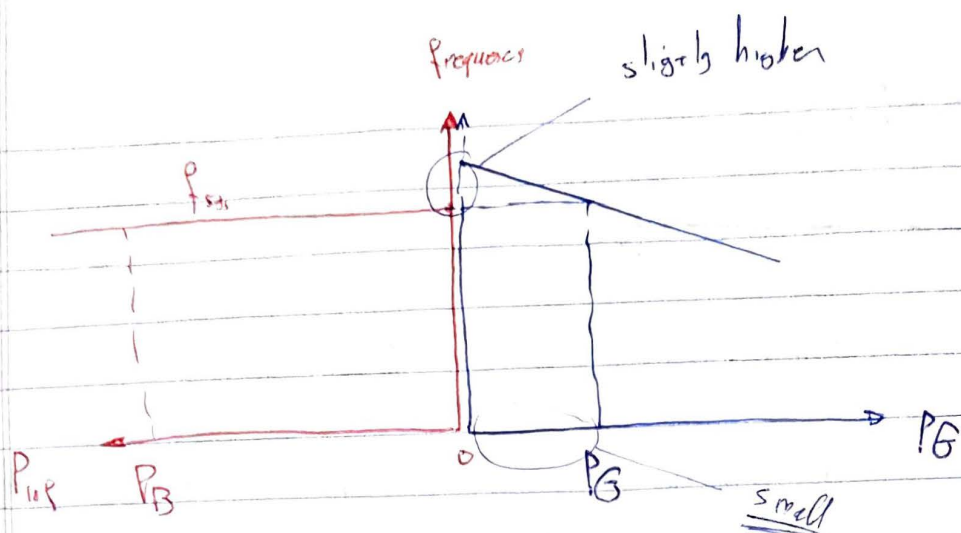

P_B : power supplied by infinite Bus

P_G : power supplied by the generator.



$$P_{Load} = P_G + P_B$$

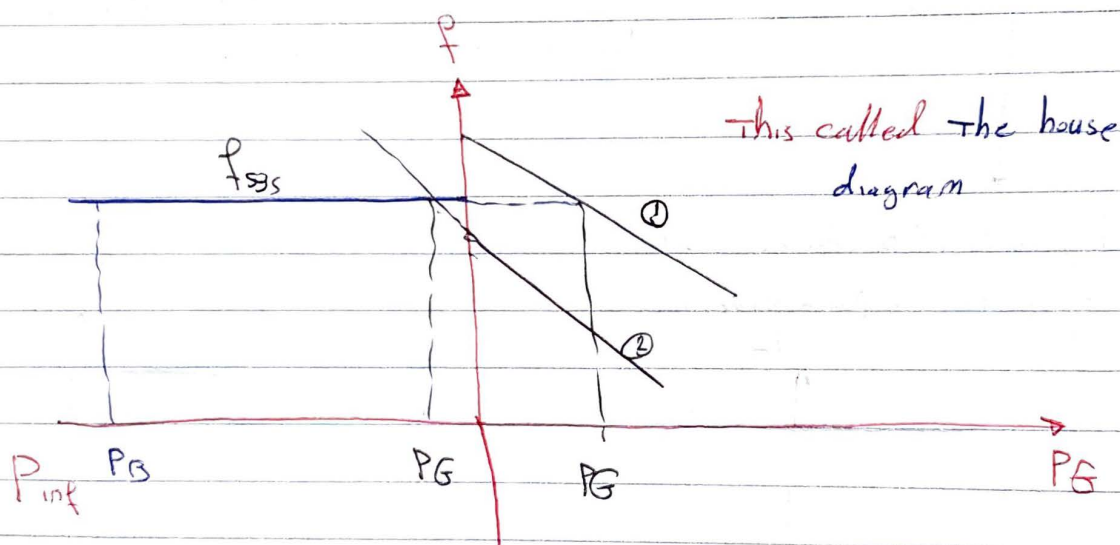

- * if the frequency of the generator is slightly higher ① than $f_{sys} \Rightarrow P_G$ is positive and very small $\Rightarrow$ the machine acts as a generator.

- * if the frequency of generator is slightly lower ② than $f_{sys} \Rightarrow P_G$ is negative & very small $\Rightarrow$ the machine acts as Motor.

* Increasing of governor setting

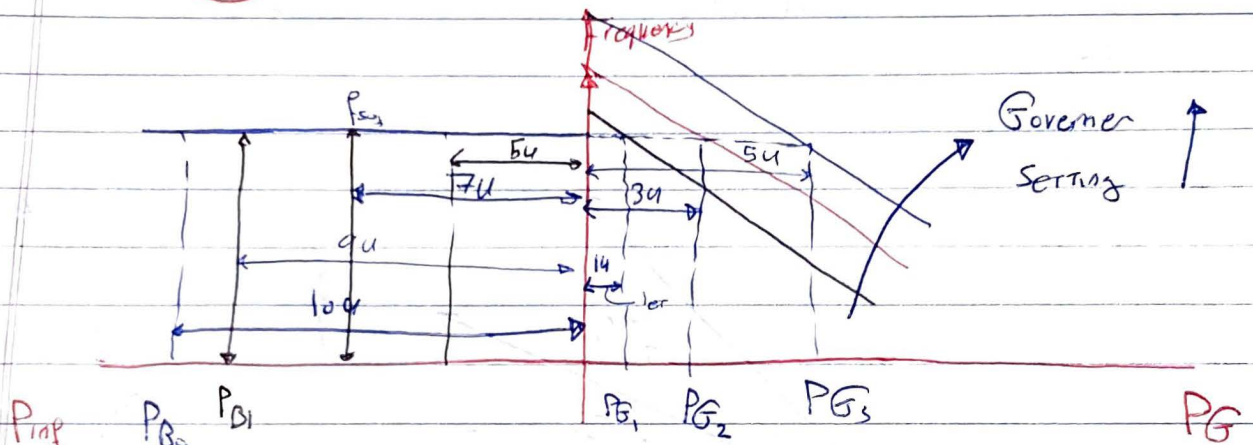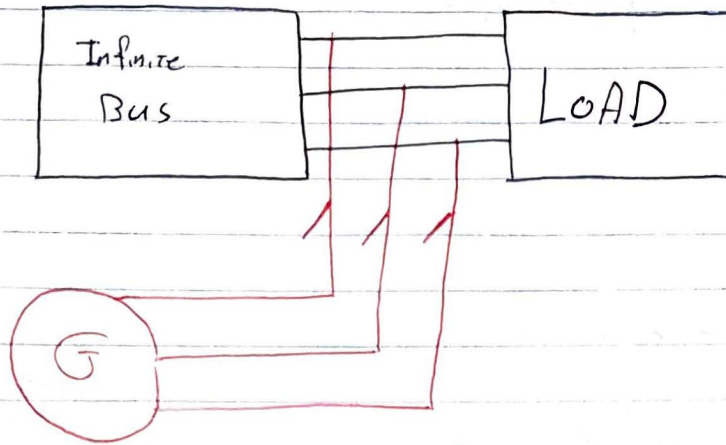

Before synchronizing $\Rightarrow P_{B_0} = 104$, $P_{G_0} = 0 \Rightarrow P_{Load} = P_{B_0} + P_{G_0} = 104$

After synchronizing $\Rightarrow P_{B_1} = 94$, $P_{G_1} = 10 \Rightarrow P_{Load} = P_{B_1} + P_{G_1} = 104$

Governor Setting $\uparrow \Rightarrow P_G \uparrow$ & $P_B \downarrow \Rightarrow P_{G_2} = 34 > P_{G_1}$ & $P_{B_2} = 74 < P_{B_1}$

$$\Rightarrow P_{Load} = P_{G_2} + P_{B_2} = 104$$

Governor Setting $\uparrow \Rightarrow P_G \uparrow$ & $P_B \downarrow \Rightarrow P_{G_3} = 54$ & $P_{B_3} = 54 \Rightarrow$

$$P_{Load} = P_{G_3} + P_{B_3} = 104$$

Phasor Diagram

$$P_G = \frac{3V_\phi E_A}{X_s} \sin \delta \rightarrow P_G \propto E_A \sin \delta$$


V_ϕ : constant

X_s : constant

$$E_A = K\phi\omega = \text{constant}$$

constant (Infinite Bus)
(I_f constant)
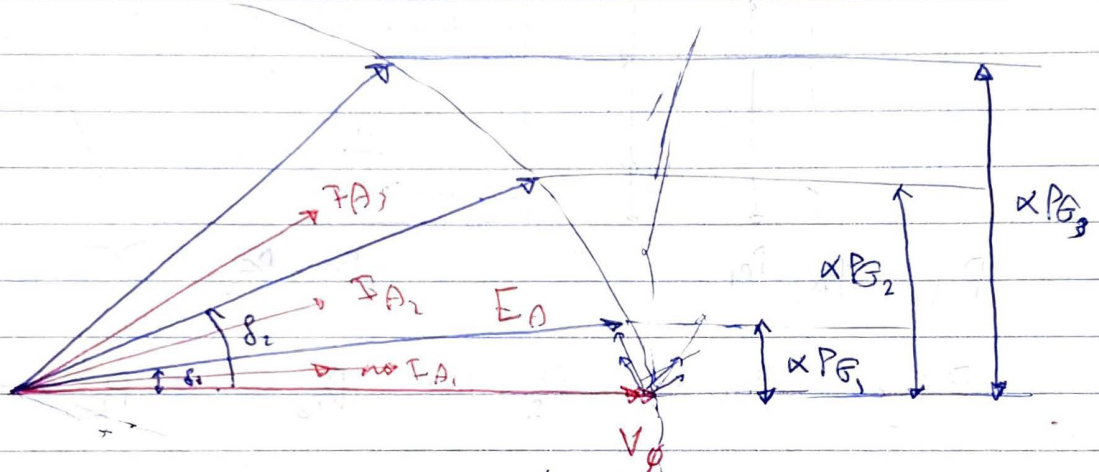
$$\vec{E}_A = \vec{V}_\phi + jX_s \vec{I}_A$$



The generator is operating at leading PF $\rightarrow$ supplies as (C)

$\Rightarrow$ The generator supplies a negative reactive power or it consumes reactive power from the infinite bus.

- ⊕ How can the generator be adjusted to supply reactive power?
 " by field current adjustment $\rightarrow Q = \frac{V_\phi^2}{X_s} \sin 2\delta$

⊗ Adjustment of Reactive power:


" changing the excitation / field current "

$$P_G = \frac{3 V_\phi E_A}{X_s} \sin \delta = 3 V_\phi I_A \cos \theta = \text{Constant} \quad \text{" by the user"}$$

$V_d = \text{constant "Infinite Bus"}$


$X_s = \text{Constant}$ "Infinite Bus"

Since P_G is constant $\Rightarrow E_A \sin \theta = \text{constant}$
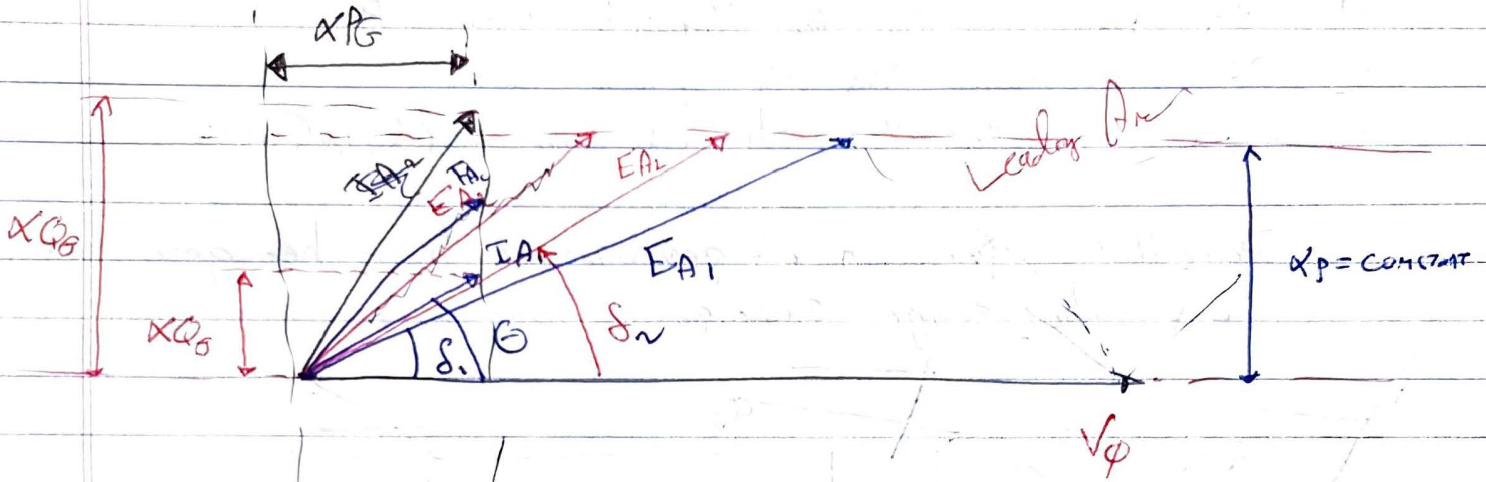
$$I_A \cos \theta = \text{constant}$$

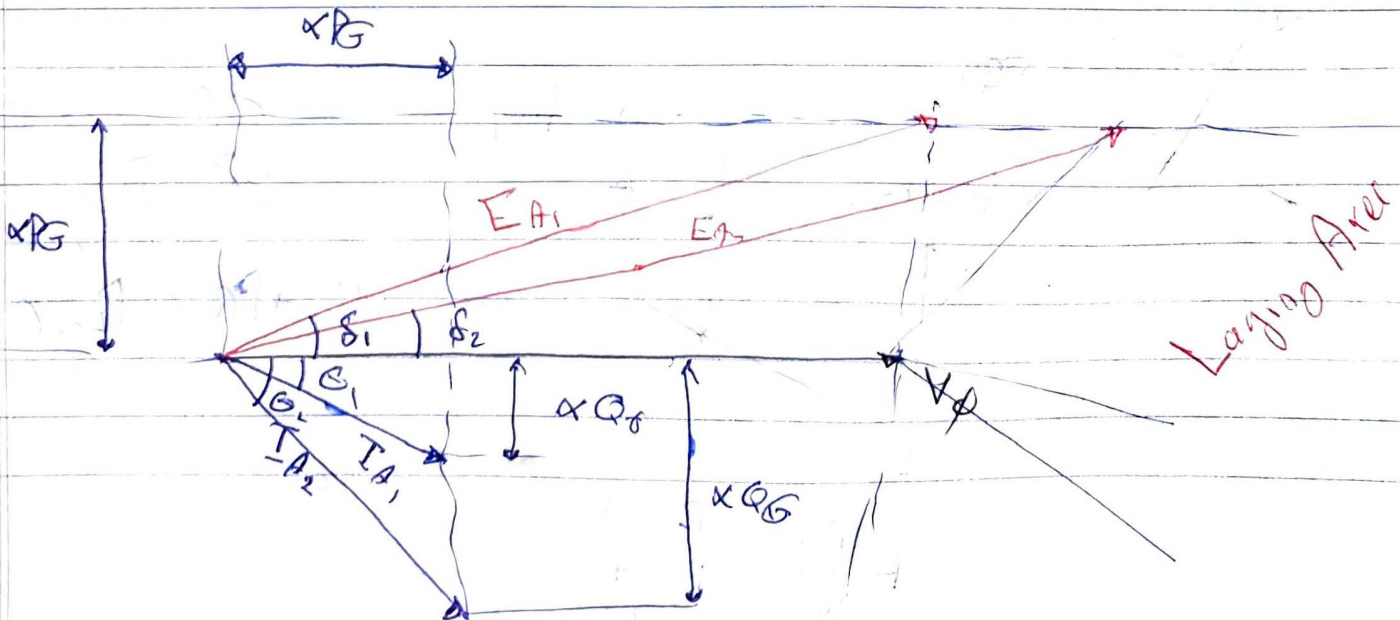
ii) The Generators absorbed Reactive power "underexcitation process"

$I_F \downarrow \Rightarrow G/G^+$ absorbed Leading Area
 Infinite Bulk $\Rightarrow$ no absorption $G \Rightarrow$ char. $\Rightarrow$ I_F smaller $\Rightarrow$ less $\Rightarrow$



② changing the excitation (field current)



$$I_F \uparrow \Rightarrow Q_G \uparrow_{\text{supplied}}$$

Lagging Area or The generator supplies reactive power "over-excitation"

Conclusion go

- ① V_T & P_{sys} are controlled via the infinite bus.
- ② PG is controlled via the governor setting.
- ③ Q_G is controlled via the excitation. (field current)

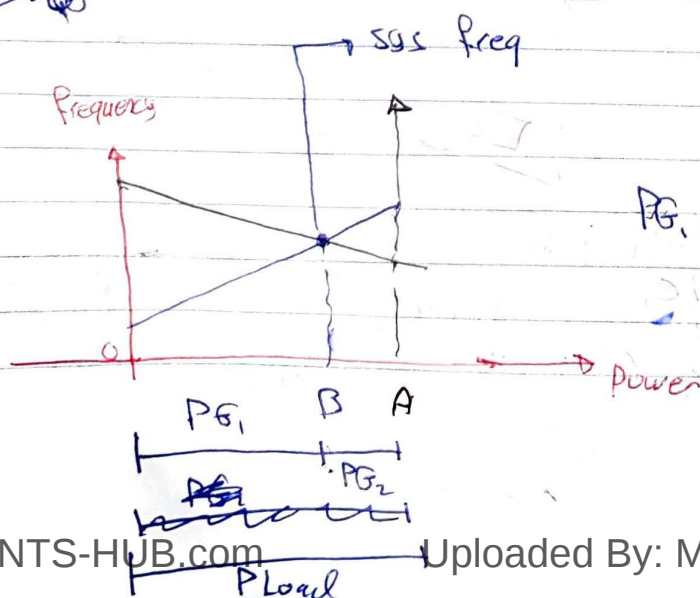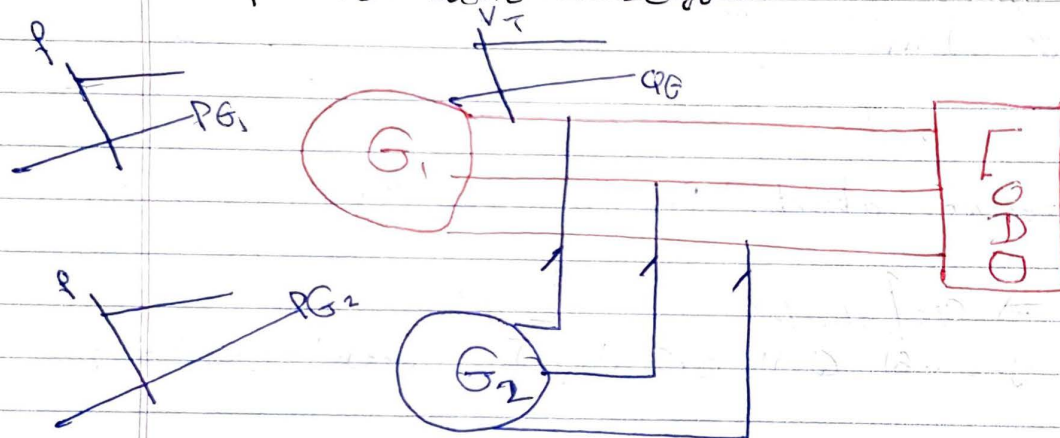
Parallel operation of generator with other generators of the same size go



OA: P_{Load}
 OB: PG_1
 BA: PG_2

$$PG_1 + PG_2 = P_{\text{Load}}$$

changing The governor setting.

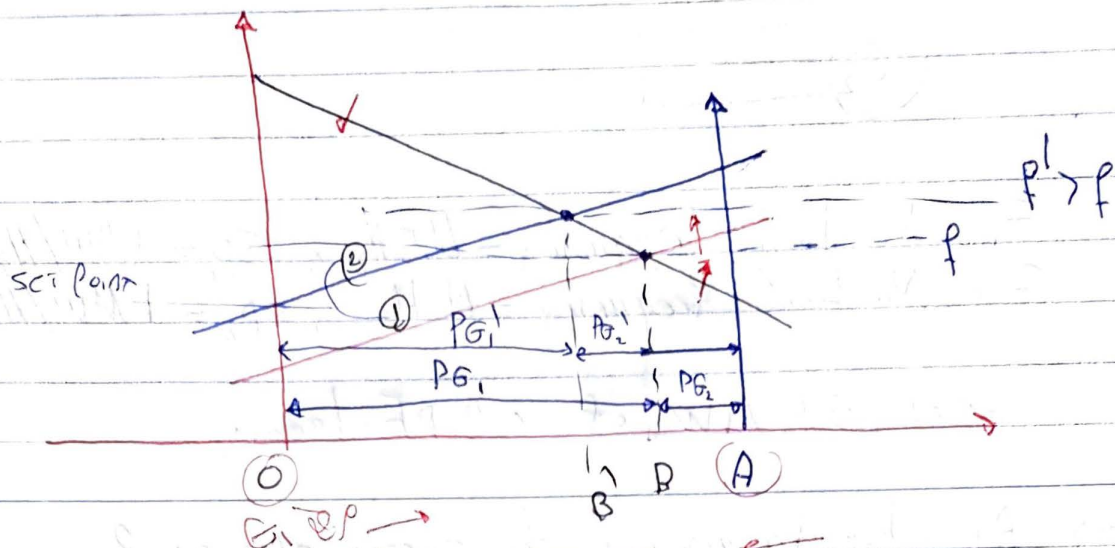

$$OB' = P_{G1}' \text{ @ } 1$$

$$BA = P_{G2}' \text{ @ } 2$$

$$OA = P_{Load}$$

$$OB = P_{G1} \text{ @ set point II}$$


$$BA = P_{G2} \text{ @ set point I}$$

Governor setting of $G_2 \uparrow$

$$f_{sys} \uparrow \quad P_{G1} \downarrow, \quad P_{G2} \downarrow$$

$$P_{G1} + P_{G2} = P_{Load}$$

changing the excitation

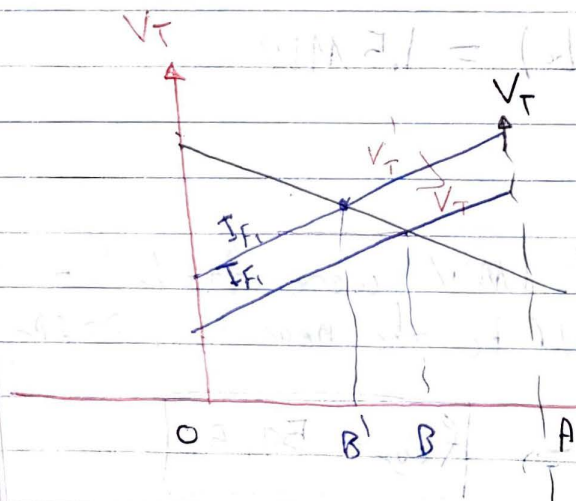

$$OA = P_{Load}$$

$$OB = P_{G1}$$

$$BA = P_{G2}$$

$$OB' = P_{G1}' \text{ @ } I_{F2}$$

$$BA = P_{G2}' \text{ @ } I_{F1}$$


$$OA = P_{Load} = P_{G1}' + P_{G2}'$$

P_{Load}

$$G_2 \left(\begin{matrix} I_F \\ \text{of Generator} \end{matrix} \right) \uparrow \Rightarrow V_T \uparrow \rightarrow P_{G1} \downarrow + P_{G2} \uparrow$$

Example

Q1

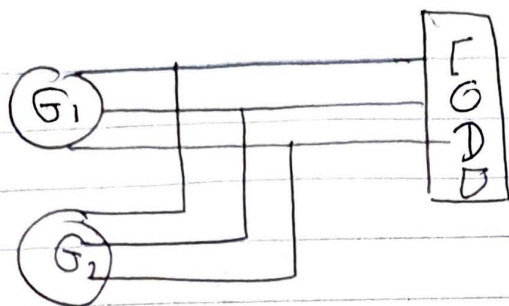

G₁: No load frequency = 61.5 Hz, $SP_1 = 1 \text{ MW/Hz}$
G₂: No load frequency = 61 Hz, $SP_2 = 1 \text{ MW/Hz}$

Load 2.5 MW of 0.8 PF lagging

a) At what frequency is the system operating?

$$P_{G1} = SP_1 (f_{NL1} - f_{sys})$$

$$P_{G2} = SP_2 (f_{NL2} - f_{sys})$$

$$P_{G1} + P_{G2} = 2.5 \Rightarrow \boxed{f_{sys} = 60 \text{ Hz}}$$

b) How much power is supplied by G₁ + G₂?

$$P_{G1} = SP_1 (61.5 - 60) = 1.5 \text{ MW}$$

$$P_{G2} = 1 \text{ MW}$$

c) Suppose an additional 1 MW were attached to the power system would be the new f_{sys} , P_{G1} & P_{G2} ?

$$\boxed{3.5 = P_{G1} + P_{G2}} \Rightarrow \boxed{f_{sys} = 59.5}$$

d) what will the system frequency and generation powers be if the governor setting of G₂ is increased by half Hz?

$$P_{N1} = 61.5 \quad P_{N2} = 61.5$$

$$P_{G1} + P_{G2} = 3.5 \Rightarrow P_{sgs} = 59.57$$

$$P_{G1} = 1.75 \text{ MW}$$

$$P_{G2} = 1.75 \text{ MW}$$

Example


A 480 V, 50 Hz, Y-connected, 6 poles SG has $X_s = 1 \Omega$
 its full load current is 60 A at 0.8 PF lagging friction &
 winding losses = 1.5 kW
 core losses = 1 kW

The field current has been adjusted so that
 $V_T = 480 \text{ V}$ at no load.

- what is the speed of rotation of this generator?
- what is the terminal voltage of the generator at full load?
- what is the efficiency under full load condition?

$$a) \quad \omega_m = \frac{2}{p} \omega_e = \frac{2}{6} (2\pi (50)) \Rightarrow \omega_m = \frac{1000\pi}{30} \text{ rad/sec}$$

$$= 1000 \text{ rpm}$$

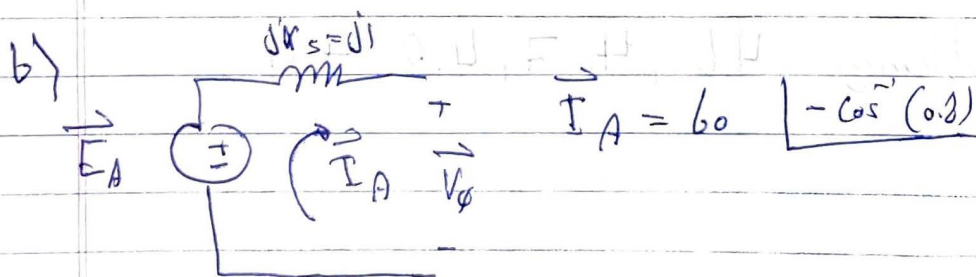

$$\vec{E}_A = (jX_s \vec{I}_A + \vec{V}_\phi) \Rightarrow \sqrt{\frac{1}{3}} 480 \angle \delta = \underbrace{60 + j1 (60 \angle -\cos^{-1}(0.8))}_{36.87^\circ}$$

$$\sqrt{\frac{1}{3}} (480) =$$

$$j1 (60 \cos(36.87^\circ)) + 60 \sin(36.87^\circ)$$

$$= V_{\phi} + b_0 \sin(36.27^\circ) + j b_0 \cos(36.27^\circ)$$

$$\sqrt{\frac{2}{3}} 480 = \sqrt{(V_{\phi} + b_0 \sin(36.27^\circ))^2 + (b_0 \cos(36.27^\circ))^2}$$

$$V_{\phi} = 236.8 \text{ V RMS}$$

$$V_T = \sqrt{3} (236.2) = 410 \text{ V}$$

$$c) P_{out} = \sqrt{3} V_T I_A \text{ PF}$$

$$P_{out} = 34.1 \text{ kW}$$

$$P_{in} = 34.1 + 1 + 1.5 = 36.6 \text{ kW}$$

$$\eta = \frac{34.1}{36.6} = 93.2\%$$

$$d) \text{ Find } T_{app}?$$

$$T_{app} = \frac{P_{in}}{\omega} = 291 \text{ N}$$

Homework Problems 4.6, 4.7, 4.8, 4.9