



BERZIET UNIVERSITY

FACULTY OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

ENEE 2102

Circuits Laboratory

Experiment.9 Prelab

AC & DC Power Analysis and Design

Prepared by:

Abeer awawda 1201848



Supervised by:

Dr.Jaser saed

Teacher assistance:

Eng.Shadi Bannoura

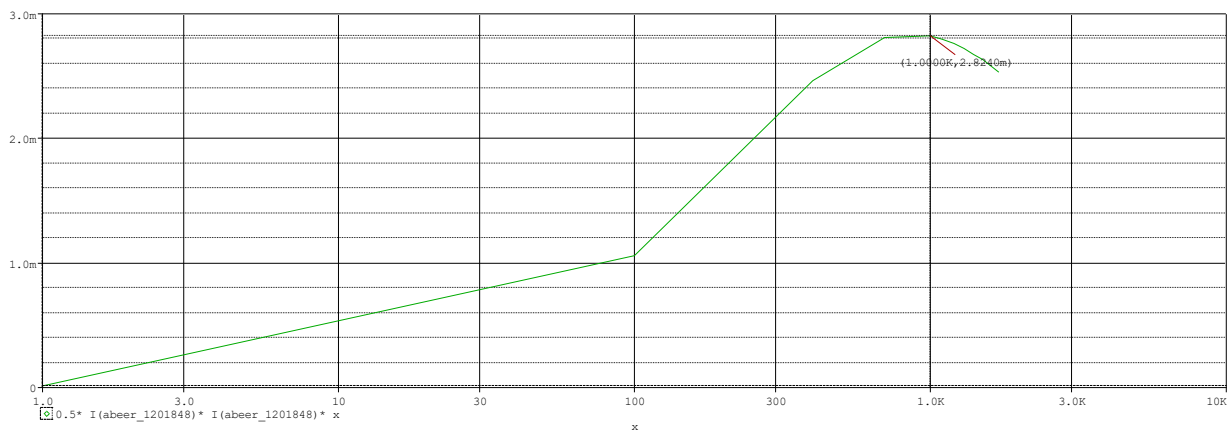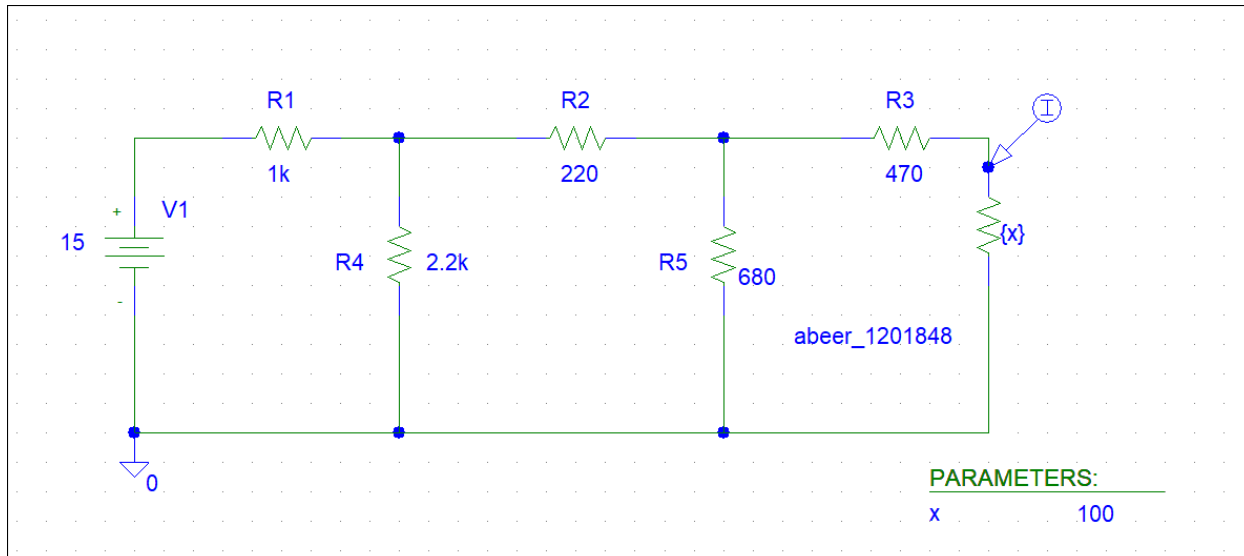1. Make a DC sweep for RL in the circuit of Figure 9.5 to produce a plot of (PLOAD vs. RL) for the range of values of RL shown in Table 9.2, use cursors to find the value of RL that results in maximum power transfer to RL



2. For the circuit of Figure 9.6:

- Use phasor analysis to calculate V_L and I_L , assume the input voltage $V_{in} = 8 \text{ VPP} \angle 0^\circ$.
- Calculate the complex power of the load" SL.

A. calculate V_L and I_L , assume the input voltage $V_{in} = 8V_{pp}$

$$V_{rms} = V_{pp} / 2\sqrt{2}$$

$$V_{rms} = 2.83 \text{ volt}$$

$$I_{in} = \frac{V_{in}}{Z}$$

$$Z = 100 + 680 + j942$$

$$Z = 780 + j942 \Omega$$

$$Z = 1223.4 \angle 50.38^\circ \text{ K } \Omega$$

$$V_{in} = 2.82 \angle 0^\circ \text{ volt}$$

$$I_{in} = \left(\frac{2.83 \angle 0^\circ}{1223.4 \angle 50.38^\circ} \right)$$

$$I_{in} = 2.305 \times 10^{-3} \angle -50.3^\circ \text{ mA}$$

Now,

$$I_L = I_{in} = 2.305 \times 10^{-3} \angle -50.38^\circ$$

$$V_L = I_L \times Z_L$$

$$V_L = 2.305 \times 10^{-3} \angle -50.3^\circ \times 1162.2 \angle 54.2^\circ$$

$$V_L = 2.67 \angle 3.82^\circ$$

$$s = V_{rms} * I_{rms} \quad \times$$

$$s = 2.67 < 3.82^0 * 2.305 < \cancel{+} 50.38^0$$

$$= 6.141 * 10^{-3} < \cancel{+} 46.56^0$$


$$Q = \frac{v^2}{X_c}$$

$$x_c = \frac{v^2}{Q}$$

$$= \frac{2.83^2}{6.141 * 10^{-3} \sin 90} = 1304.2 \mu F$$


$$\frac{1}{2 * \pi * f * c} = 1304.2$$

$$C = 1.2 * 10^{-7}$$

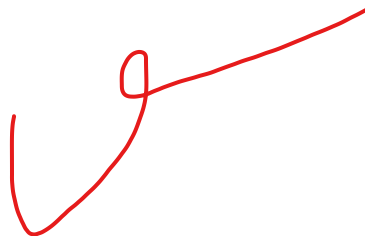

-Use PSPICE to do transient analysis of the circuit in Figure 9.6, show $I_L(t)$ and $V_L(t)$ on one graph, you will need different Y-axis, and measure the power factor (from the time difference between the two waveforms).

WITHOUT CAPACITOR

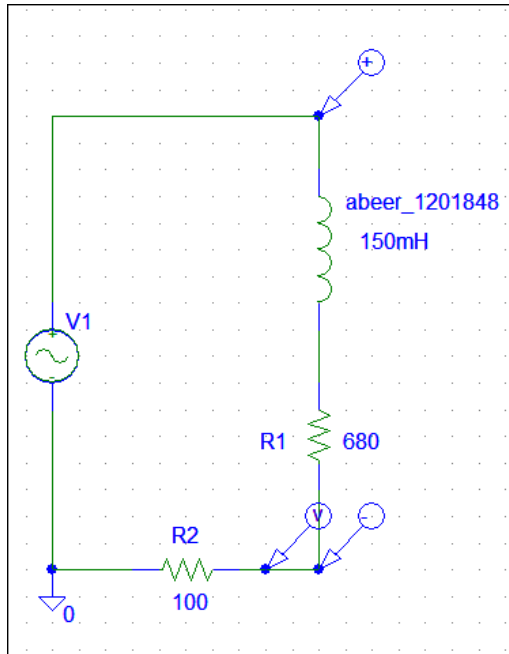

$$\Delta t = 376.721 * 10^{-6} - 242.009 * 10^{-6}$$

$$\Delta t = 1.34712 * 10^{-4} \text{ sec}$$

$$\text{Power factor} = \cos(\theta_v - \theta_i)$$

$$\Delta \theta = 360^\circ \times f \times \Delta t$$



$$\Delta \theta = 360^\circ \times 1 \times 10^3 \times 1.34712 * 10^{-4}$$

$$\Delta \theta = 48.49^\circ$$

$$\text{P.F} = \cos \theta = 0.6627$$

- Repeat the previous step with the added capacitor to show power factor improvement.

WITH CAPACITOR

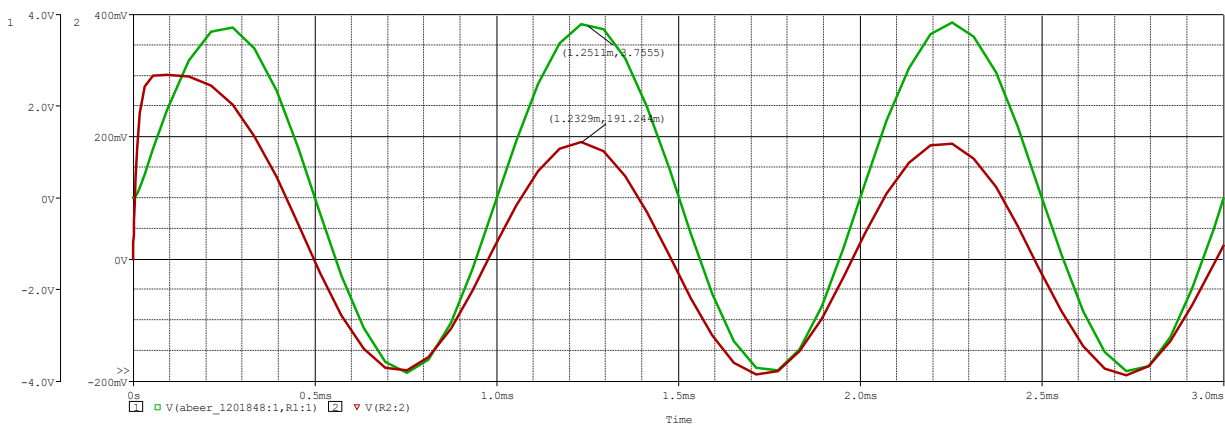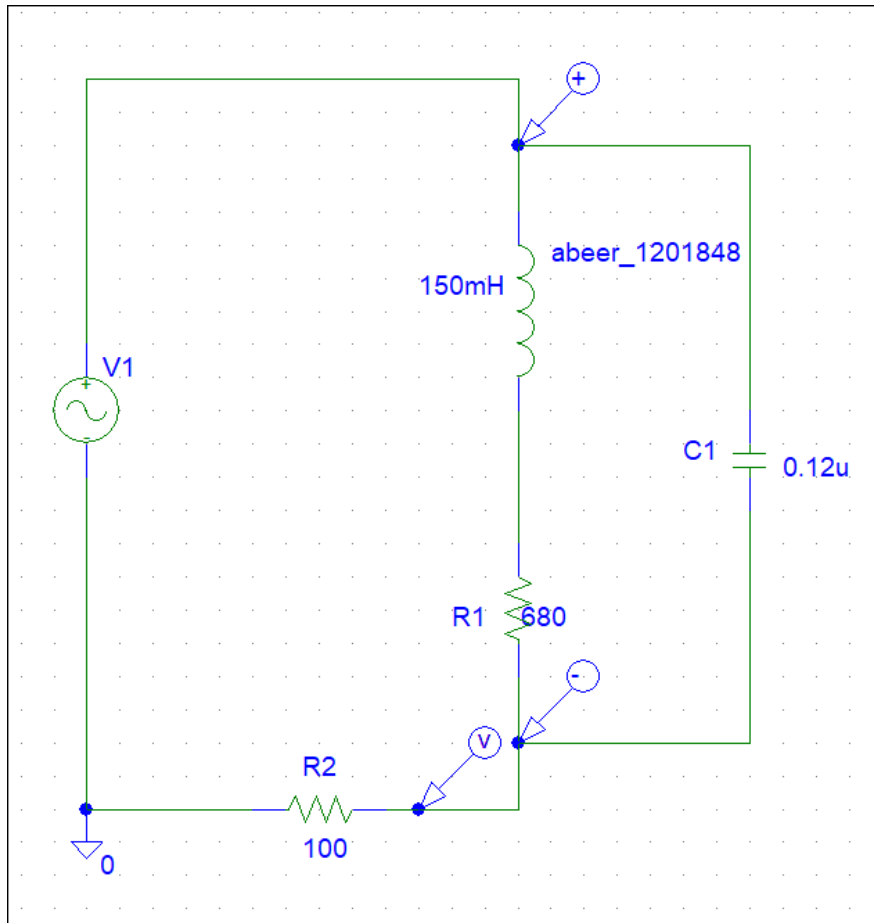

$$\Delta t = 1.2511 * 10^{-3} - 1.2329 * 10^{-3}$$

$$\Delta t = 1.34712 * 10^{-4} \text{ sec}$$


$$\text{Power factor} = \cos(\theta_v - \theta_i)$$

$$\Delta \theta = 360^\circ \times f \times \Delta t$$

$$\Delta \theta = 6.588^\circ$$

$$\text{P.F} = \cos \theta = 0.99$$

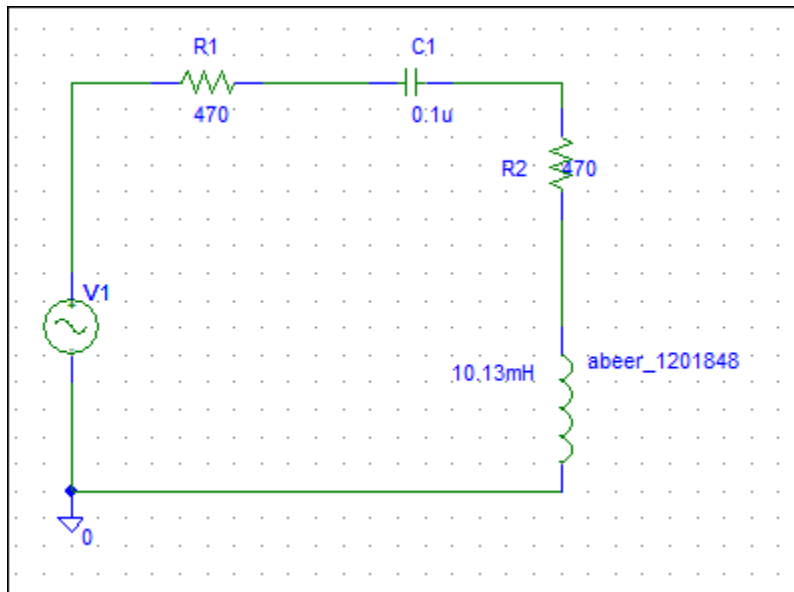1. For the circuit of Figure 9.8, design a load that is when connected to the output terminals of the circuit will extract maximum average power, then calculate magnitude of P_{Max} .



$$Z_L = Z_{TH}$$

$$Z_{TH} = 470 - j * x_C$$

$$Z_{TH} = 470 - jx_C = Z_L$$

$$Z_L = 470 + jx_L$$

$$R_L = 470$$

$$x_L = x_C$$

$$2 * \pi * F * L = \frac{1}{2 * \pi * f * c}$$

$$L = \frac{1}{(2 * \pi * f)^2 * c} = 10.13 \text{mH}$$