

7


السؤال

Experiment 4 Network Analysis II

The Thevenin and Norton Techniques

- * Kirchhoff's laws and SPP are useful techniques for analyzing networks that contain a few circuit elements
- * Complicated networks require methods such as the equivalent circuit techniques of Thevenin and Norton
- * Thevenin's theorem states that: any network of resistors and supplies having two output terminals can be replaced by a series combination of a voltage source (E_{eq}) and a resistor (R_{eq})

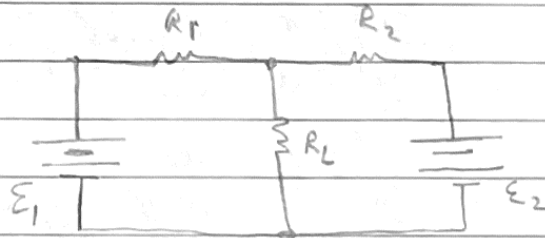
$$\begin{aligned} R_1 &= 1k\Omega \\ R_2 &= 3.3k\Omega \\ R_3 &= 6.2k\Omega \\ E_1 &= 12 \text{ volt} \\ E_2 &= 6 \text{ volt} \end{aligned}$$




* Thevenin :

① Finding $I_B \Rightarrow$ (So let $R_L = R_3$)

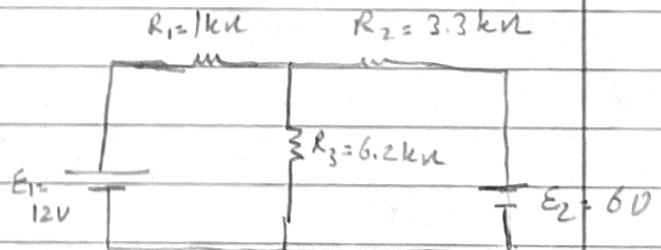- ① Remove R_L (Which is R_3 in our case), kill both sources and Find R_{eq} (by connecting ohmmeter or multimeter on ohm's mode)


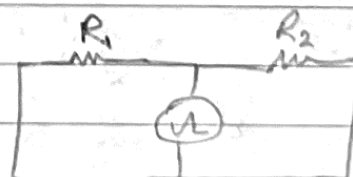
$$\begin{aligned} R_{eq} &= R_1 \parallel R_2 \\ R_{eq} &= \frac{R_1 R_2}{R_1 + R_2} \\ R_{eq} &= \frac{1 \times 3.3}{1 + 3.3} \end{aligned}$$



$$\begin{aligned} &\text{kelvin's law} \\ &k\Omega = 9681\Omega \end{aligned}$$

②


$$R_{eq} = 0.767 \text{ k}\Omega$$

- ② Return both sources ($\mathcal{E}_1, \mathcal{E}_2$) and find $\mathcal{E}_{eq}, I_{eq}$
 * by connecting voltmeter or multimeter for $\mathcal{E}_{eq}$
 * by connecting Ammeter or multimeter for I_{eq}

From the large loop

$$\mathcal{E}_1 - IR_1 - IR_2 - \mathcal{E}_2 = 0$$
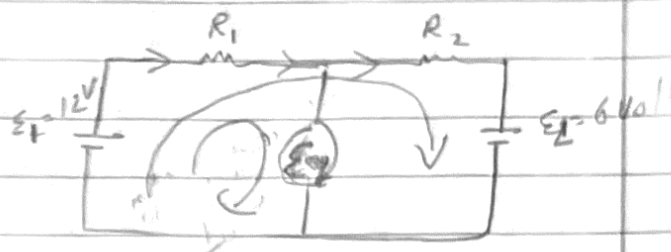
$$\mathcal{E}_1 - \mathcal{E}_2 - I(R_1 + R_2) = 0$$



$$I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{12 - 6}{(1 + 3.3) \text{ k}\Omega} = 1.395 \text{ mA}$$

From the small loop

$$\mathcal{E}_1 - IR_1 - \mathcal{E}_{eq} = 0 \Rightarrow \mathcal{E}_{eq} = \mathcal{E}_1 - IR_1 = 12 - 1.395 \text{ mA} \times 1 \text{ k}\Omega = 10.605 \text{ V}$$


using Norton's theorem

$$I_{eq} = \frac{\mathcal{E}_{eq}}{R_{eq}} = \frac{10.605}{0.767 \times 10^3} = 13.83 \text{ mA}$$

- ③ construct Thevenin's circuit

$$I_{L3} = \frac{\mathcal{E}_{eq}}{R_{eq} + R_3}$$
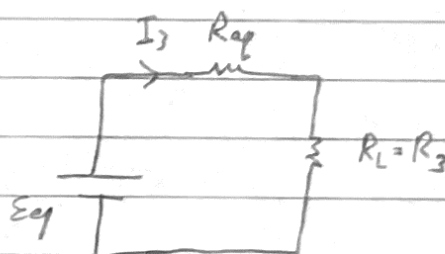
$$= \frac{10.605}{(0.767 + 6.2) \text{ k}\Omega}$$




$$I_3 = 1.522 \text{ mA} \Rightarrow I_{L3} = 1.522 \text{ mA}$$

(3)

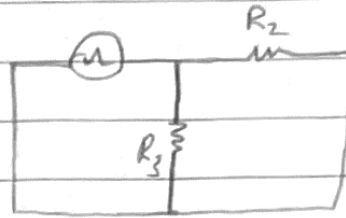(B) Finding $I_1 \Rightarrow$ (so let $R_L = R_1$)

① Remove R_L , kill both sources and find R_{eq}



$$R_{eq} = R_2 \parallel R_3$$

$$= \frac{R_2 R_3}{R_2 + R_3}$$


$$= \frac{3.3 \times 6.2}{3.3 + 6.2} \quad \text{كل واحد على كل واحد في مجموع}$$

$$R_{eq} = 2.15 \text{ k}\Omega$$

② Return both sources and find E_{eq}

Ⓐ

$$I R_3 + I R_2 - E_2 = 0$$

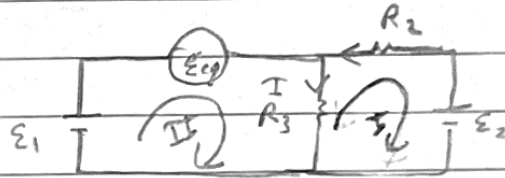

$$I(R_3 + R_2) - E_2 = 0$$

$$I = \frac{E_2}{R_3 + R_2} = \frac{6}{(6.2 + 3.3) \text{ k}\Omega} = 0.63 \text{ mA}$$

$$\text{Ⓑ} \quad E_1 - E_{eq} - I R_3 = 0$$

$$E_{eq} = E_1 - I R_3$$

$$= 12 - 0.63 \times 6.2$$


كل واحد من الآخر

$$E_{eq} = 8.094 \text{ Volt}$$

$$I_{eq} = \frac{E_{eq}}{R_{eq}} = 3.76 \text{ mA}$$

③ construct Thevenin's circuit R_{eq} و R_L التوازي E_{eq} الجهد

$$T_1 = \frac{E_{eq}}{R_{eq} + R_L}$$

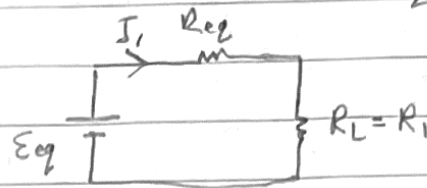

$$I_1 = \frac{8.094}{(2.15+1) \text{ kN}}$$

$$I_1 = 2.569 \text{ mA}$$

$$\Rightarrow I_L = 2.569 \text{ mA}$$

(5)


Norton's

Finding I_{L3} let $R_L = R_3$

- ① Remove $R_L \rightarrow (R_3)$, killing sources and find R_{eq} by connecting to ohmmeter

$$R_{eq} = R_1 \parallel R_3$$

$$R_{eq} = \frac{R_1 R_3}{R_1 + R_3}$$

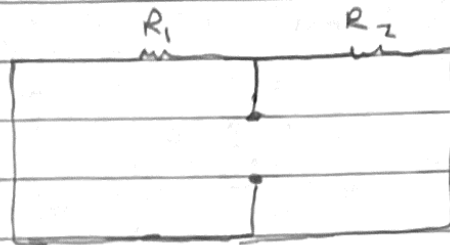

$$\Rightarrow R_{eq} = 0.767 \text{ k}\Omega$$


- ② Return both sources and calculate

I_{eq} (by connecting Ammeter or multimeter)

then find I_{eq} (I_{Norton})

$$I_{eq} + I_2 = I_1$$

$$I_{eq} = I_1 - I_2$$

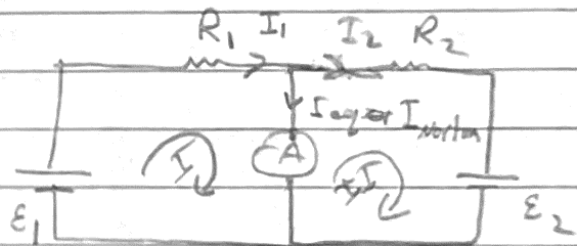

$$E_1 - I_1 R_1 = 0$$

$$I_1 = \frac{E_1}{R_1} = \frac{12}{1 \text{ k}\Omega} = 12 \text{ mA}$$

$$\textcircled{II} -I_2 R_2 - E_2 = 0$$

$$I_2 = \frac{-E_2}{R_2} = \frac{-6}{3.3 \text{ k}\Omega} = -1.82 \text{ mA}$$

$$I_{eq} = I_1 - I_2 = 12 \text{ mA} - (-1.82) = 13.82 \text{ mA}$$

(6)

③ construct Norton circuit

لـ 0 - L
 (ب) I_{eq} و R_{eq} و R_3 و R_L

$$I_3 R_3 = I_{eq} (R_3 \parallel R_{eq})$$


$$I_3 R_3 = I_{eq} \frac{R_3 R_{eq}}{R_3 + R_{eq}}$$

$$I_3 = \frac{I_{eq}}{R_3} \frac{R_3 R_{eq}}{R_3 + R_{eq}}$$

$$I_3 = \frac{I_{eq} R_{eq}}{R_3 + R_{eq}}$$

$$= \frac{13.82 \times 0.767}{6.2 + 0.767}$$
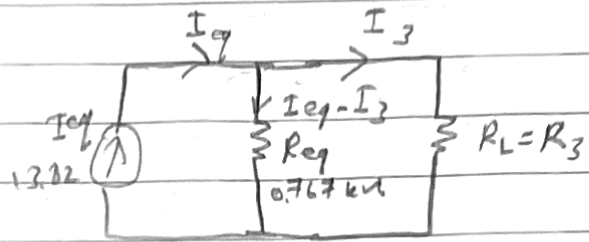
$$I_3 = 1.52 \text{ mA} \Rightarrow I_{L3} = 1.52 \text{ mA}$$




(7)

Norton

For $R_1 = R_1$, Finding I_{L1}

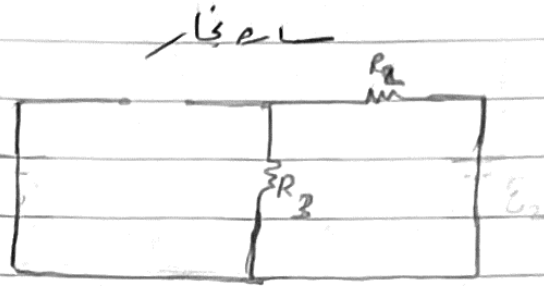
- ① Remove R_1 ($\times R_1$), killing sources and find R_{eq}



$$R_{eq} = R_2 \parallel R_3$$

$$= \frac{R_2 R_3}{R_2 + R_3} \Rightarrow R_{eq} = 2.15 \text{ k}\Omega$$

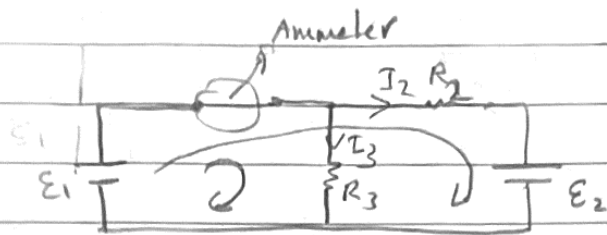- ② Return both sources and calculate I_{eq} (by connecting Ammeter or multimeter) then find I_{eq} (I_{Norton})



$$I_{eq} = I_2 + I_3$$

From small loop:

$$E_1 - I_3 R_3 = 0$$

$$I_3 = \frac{E_1}{R_3} = \frac{12}{6.2 \text{ k}\Omega} = 1.935 \text{ mA}$$

From the large loop:

$$E_1 - I_2 R_2 - E_2 = 0$$

$$I_2 R_2 = E_1 - E_2$$

$$I_2 = \frac{E_1 - E_2}{R_2} = \frac{12 - 6}{3.3 \text{ k}\Omega} = 1.82 \text{ mA}$$

$$\Rightarrow I_{eq} = I_3 + I_2 = 1.935 + 1.82 = 3.755 \text{ mA}$$

(8)

8

③ construct Norton circuit

isolate I_{eq} & R_{eq} & R_L does

$$V_{th} R_L = V_{th} (R_L \parallel R_{eq})$$

$$I_1 R_L = I_{eq} (R_L \parallel R_{eq})$$

$$I_1 R_L = I_{eq} \frac{R_L R_{eq}}{R_L + R_{eq}}$$


$$I_1 = \frac{I_{eq}}{R_L} \frac{R_L R_{eq}}{R_L + R_{eq}}$$

$$I_1 = \frac{I_{eq} R_{eq}}{R_L + R_{eq}}$$

$$= \frac{3.753 \times 2.15}{(1 + 2.15) \text{ k}\Omega}$$

$$I_1 = 2.56 \text{ mA}$$

$$\text{or } I_L = 2.56 \text{ mA}$$

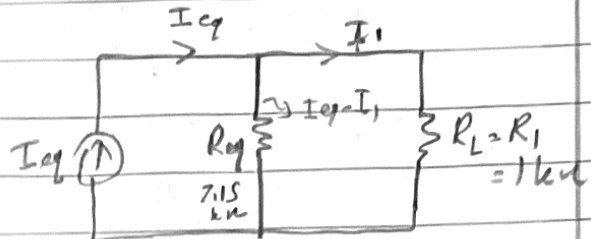


$\times 10^{-3} \times 10^{-3}$

Is P.L.
Theorin

قسم ياراله المهاد
ع ١، ع ٢


R3 و DMM 209
Regulator

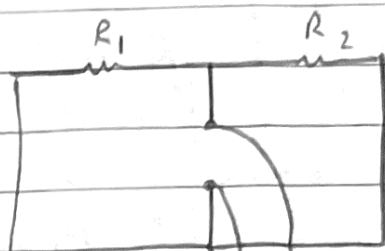

to DMM to measure R_{eq}

R_3 اذ: $b \neq 0$
 E_1 اذ: $a \neq 0$

E1 E2
 RISE DANCE
 E1 E2

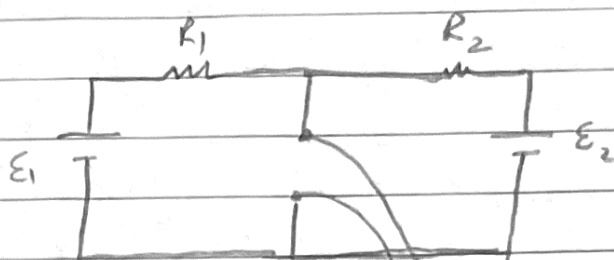

to DMM to measure E_{eq}

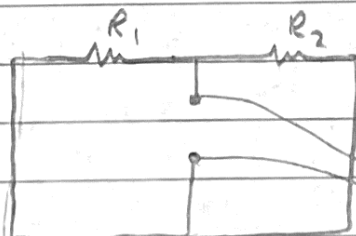

 A circuit diagram showing a cell with EMF E and internal resistance r connected in series with an external resistor R_1 and an ammeter A . The current flowing through the circuit is labeled I .

2. يوجد الآلة Reg, R_L مع ϵ_{eq} على التوالي، فاستنتج

⑤


Norton

$\sqrt{2}$ 1 2 3 4 5 6 7 8 9 10 11 12
 $\varepsilon_2 \varepsilon_1$
 100 100 100
 R_3



DMM to find Reg

1, 2, 3, 4, 5, 6, 7, 8

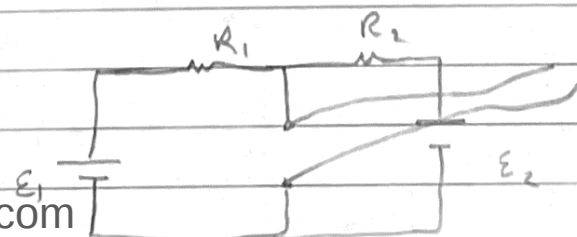

To DMU to find E_{eq}

step ③

