

15/7/2021
L6 online

/

ENEE2360
Analog Electronics

T4:
Diode Applications


Instructor: Nasser Ismail

Dc Power Supply

- All electronic circuits and systems require a stable source of dc voltage and current (or dc power) to operate correctly.






Lab


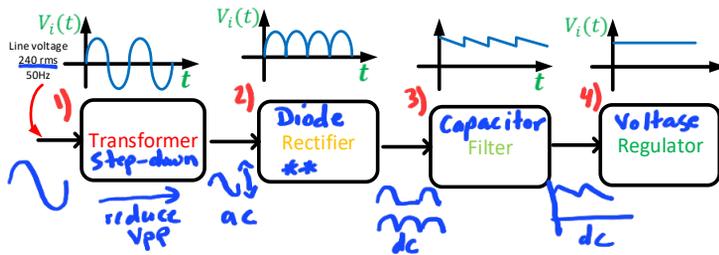



Apple 5W USB Charger (Credit: Apple)

chargers

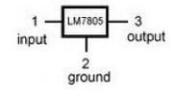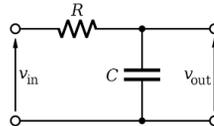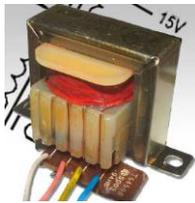

Block diagram of a dc power supply.

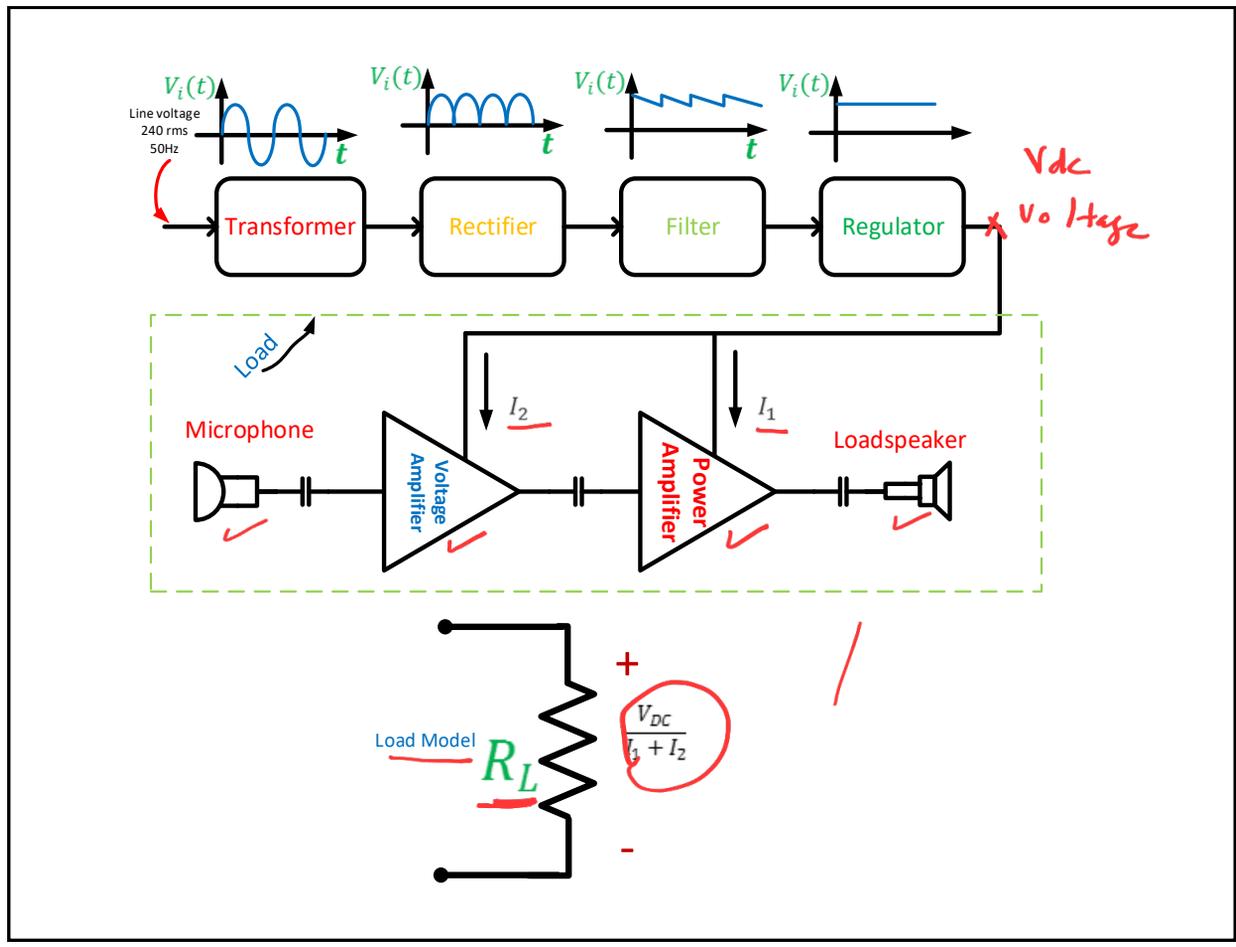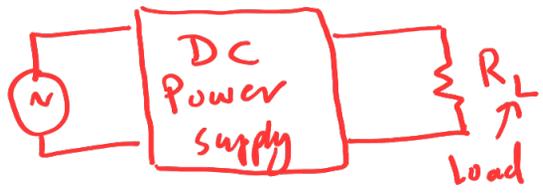


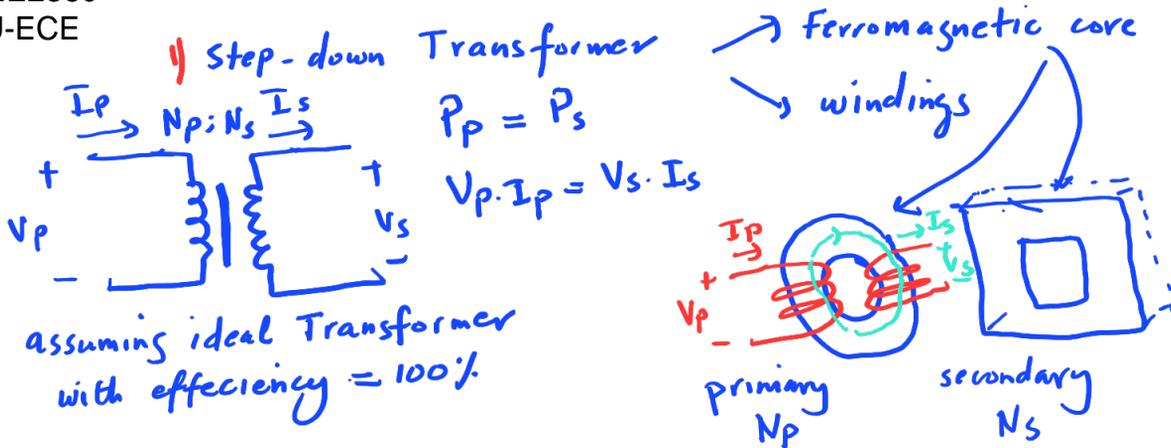

ENEE236 – Analog Electronics

Designing a power supply

1) Transformer → used for ac voltages **

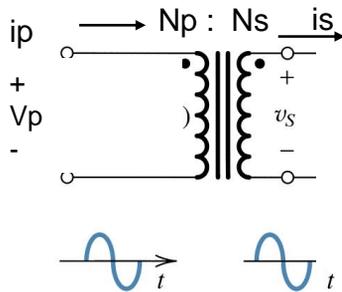

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$\frac{I_p}{I_s} = \frac{N_s}{N_p} = n$$

Usually steps down type to decrease the amplitude of the ac line voltage

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} \quad \checkmark$$

$$\frac{i_s}{i_p} = \frac{N_p}{N_s} \quad \checkmark$$


$$\frac{V_s}{V_p} = \frac{N_s}{N_p} = n$$

$$n = \frac{N_s}{N_p} \quad \text{transformer turns ratio}$$

$$\Rightarrow V_s = nV_p$$

Designing a power supply

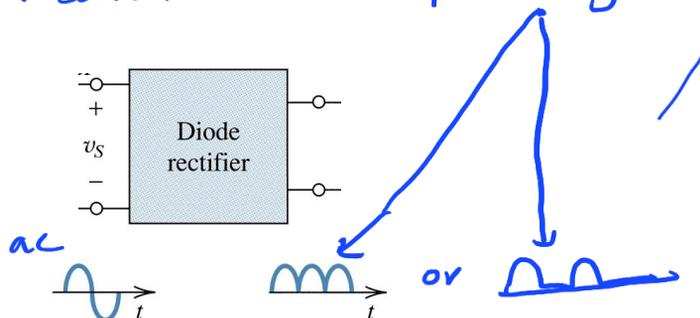2) Rectifier : *converts ac to pulsating dc*



➤ Used to convert ac voltage (with zero average value) to pulsating dc voltage (non zero average)


➤ Rectifiers are two types:




a) Half Wave Rectifier

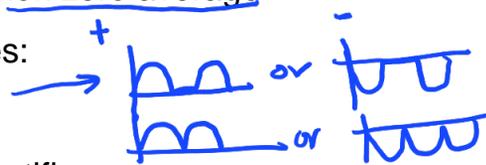b) Full Wave Rectifier

✓ - Bridge Full Wave Rectifier

✓ - Center Tapped Transformer Full Wave Rectifier



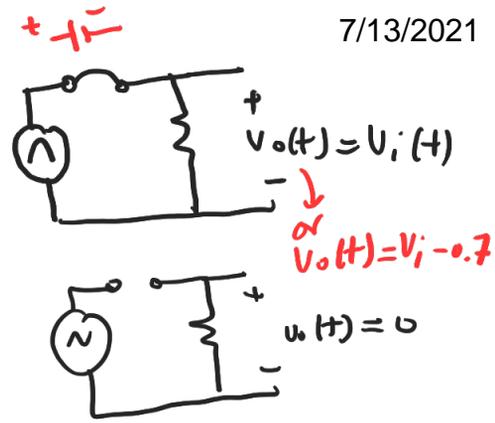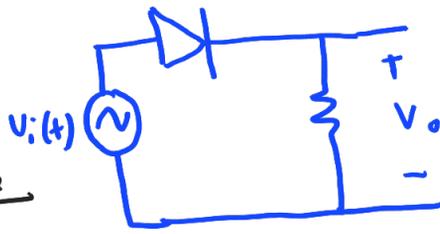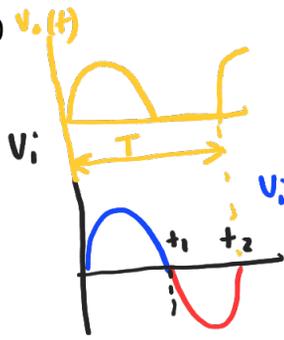


1) if $v_i(t) > 0 \rightarrow$ Diode is ON \rightarrow
 2) " " $< 0 \rightarrow$ " " off \rightarrow


ENEE236 – Analog Electronics

Half Wave Rectifier

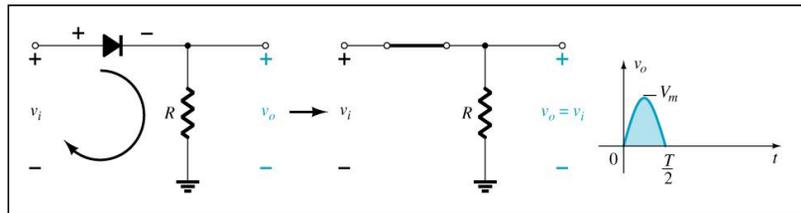1) When $V_i(t) > 0$,
 Diode is ON
 $V_o = V_i$



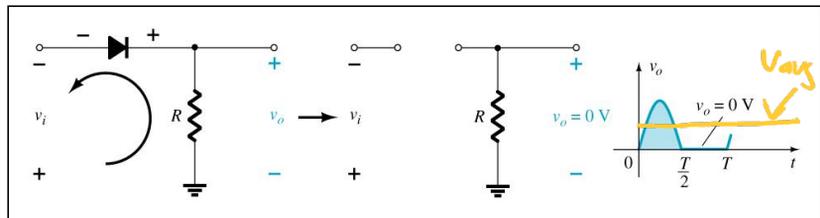2) When $V_i(t) < 0$,
 Diode is OFF
 $V_o = 0$



The diode conducts only when it is forward biased, therefore only half of the AC cycle passes through the diode to the output.

$$V_{AVG} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt \quad \leftarrow \text{by definition } V_{avg} \equiv V_{dc} \equiv V_{mean}$$


EENEE236 – Analog Electronics

Half Wave Rectifier

$$V_{AVG} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt$$

$$= \frac{1}{2\pi} \int_0^\pi V_m \sin(\theta) d\theta$$

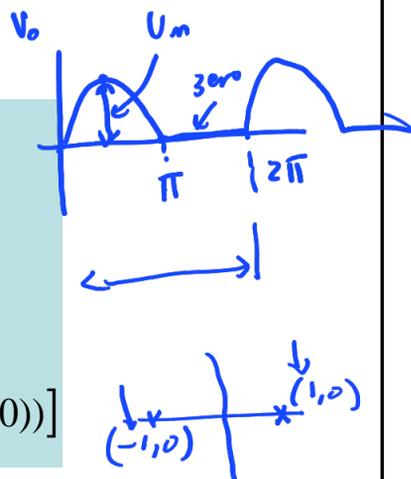
$$= \frac{1}{2\pi} [-V_m \cos(\theta)]_0^\pi = \frac{V_m}{2\pi} [-\cos(\pi) - (-\cos(0))]$$



$$V_{AVG} = \frac{V_m}{2\pi} [-(-1) - (-1)]$$



$$= \frac{2V_m}{2\pi} = \frac{V_m}{\pi} \approx 0.318V_m$$


to remember

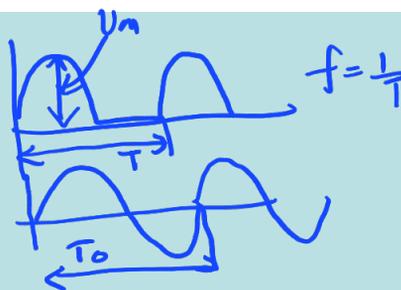

$T = T_o$ and $f = f_o$

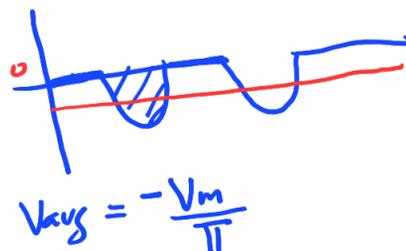
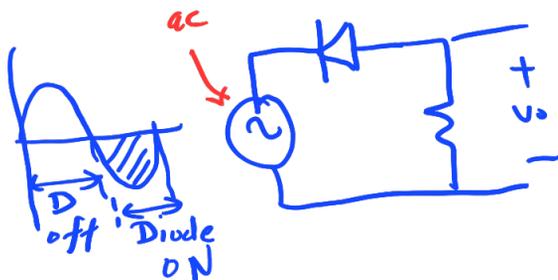
(period and frequency of the rectified waveform is the same as ac input)



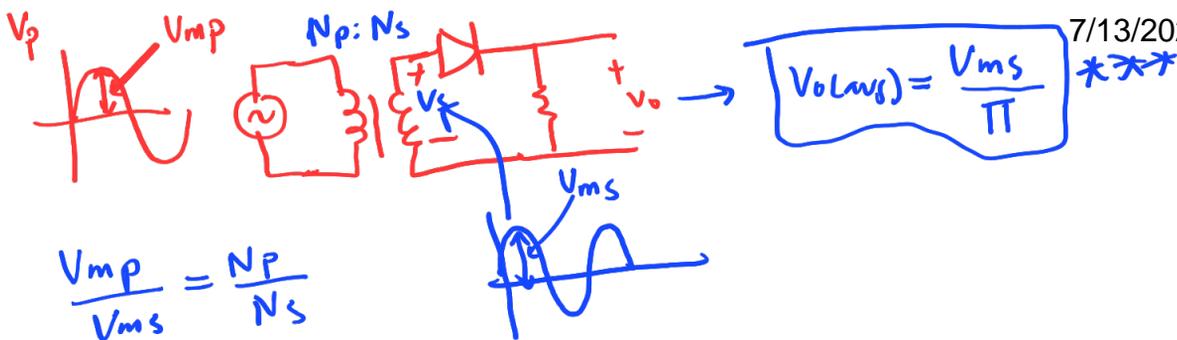

X Important Electrical Ratings *later*

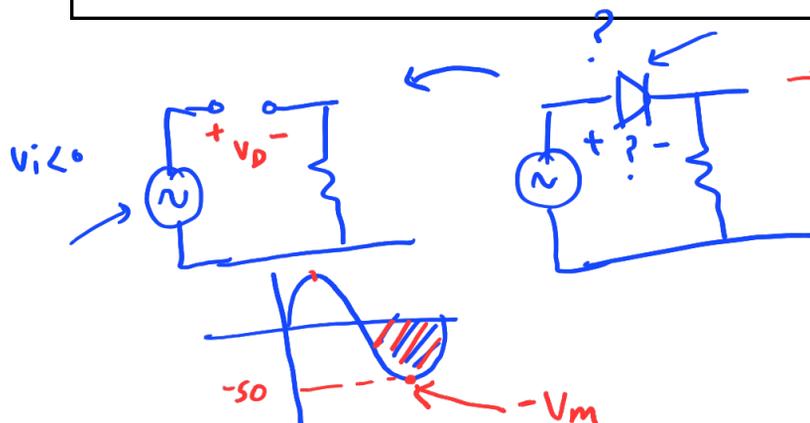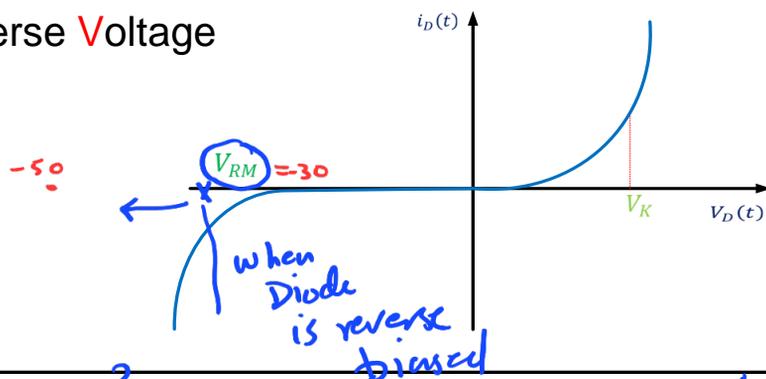- I_{FM} = maximum forward current
- I_{FM} = maximum average current that can safely be sustained by the diode when it is forward biased
- V_{RM} = maximum reverse voltage
- V_{RM} = maximum voltage that can be applied to the diode in the reverse bias polarity before voltage break down occur
- PIV \equiv Peak Inverse Voltage
- $PIV = V_{RM}$



\rightarrow We inspect what is the maximum reverse voltage that the diode will see in the given circuit

$\rightarrow PIV = -V_m = -50V$ in this case

PIV (For Half Wave Rectifier)

Because the diode is only forward biased for one-half of the AC cycle, it is also reverse biased for one-half cycle.

It is important that the reverse breakdown voltage rating of the diode be high enough to withstand the peak, reverse-biasing AC voltage.



$$V_D(t) = V_i(t)$$

$$V_D(t)_{\max} = -V_m$$

$$\text{PIV} = -V_m$$

$$I_{FM} = \frac{V_{\text{AVG}}}{R_L} = I_{RL}$$

$$I_{FM} = \frac{V_m}{\pi R_L}$$

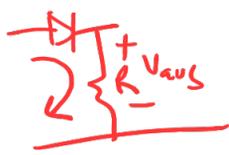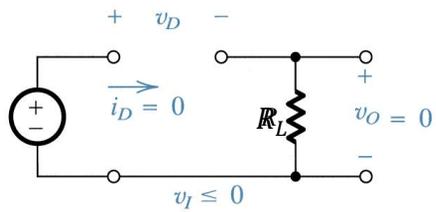

Full-Wave Rectification


The rectification process can be improved by using a full-wave rectifier circuit.




Full-wave rectification produces a greater DC output:

$$V_{avg} = \frac{1}{T} \int_0^T f(t) dt = \frac{1}{\pi} \int_0^{\pi} f(t) dt$$

Half-wave: $V_{dc} = 0.318 V_m = \frac{V_m}{\pi}$

Full-wave: $V_{dc} = 0.636 V_m = \frac{2V_m}{\pi}$

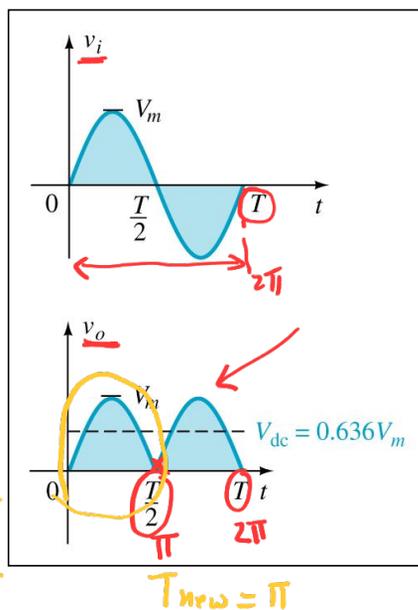

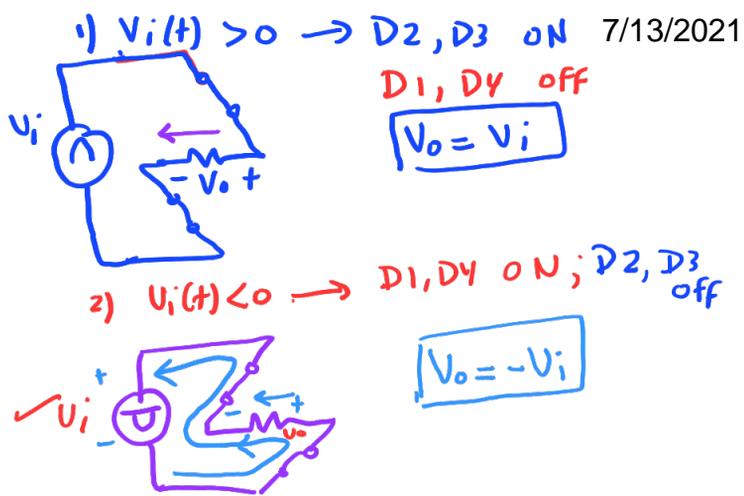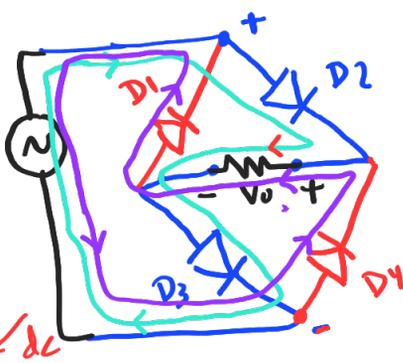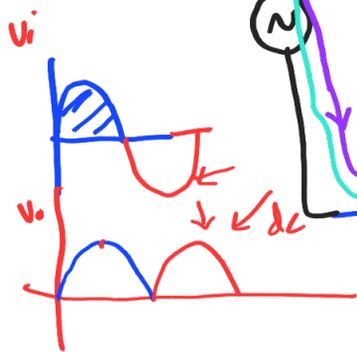

ENEE236 – Analog Electronics

Bridge Full-Wave Rectifier



A full-wave rectifier with four diodes that are connected in a bridge configuration

1) When $V_i(t) > 0$,
D2, D3 are ON
D1, D4 are OFF

$\Rightarrow V_o(t) = V_i(t)$

2) When $V_i(t) < 0$,
D2, D3 are OFF
D1, D4 are ON


$\Rightarrow V_o(t) = -V_i(t)$

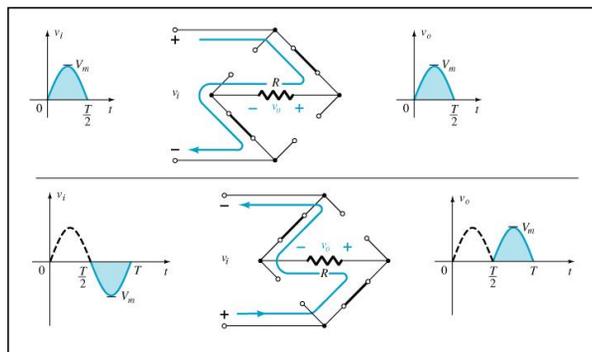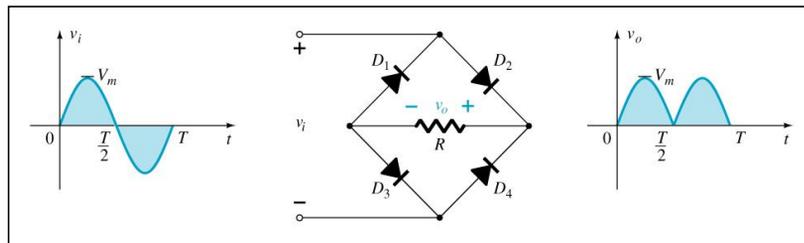

Bridge Full-Wave Rectifier

$$V_{AVG} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt$$
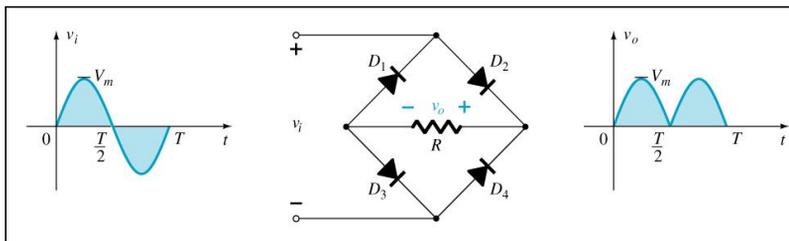
$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin(\theta) d\theta$$



$$V_{AVG} = \frac{2V_m}{\pi} \cong 0.636V_m$$

$$T = \frac{T_o}{2} \text{ and } f = 2f_o$$

(period and frequency of the rectified waveform is not the same as ac input)

ENEE236 – Analog Electronics


PIV for each of the 4 diodes

For ideal diode


$$V_{D1}(t) = -V_i(t)$$

$$V_{D1}(t)_{\max} = -V_m$$

$$\text{PIV} = -V_m$$

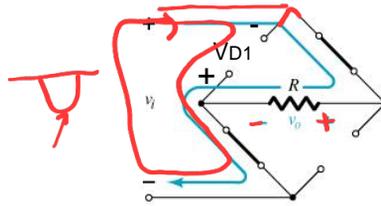

$$V_i + V_{D1} = 0$$
$$V_{D1} = -V_i$$

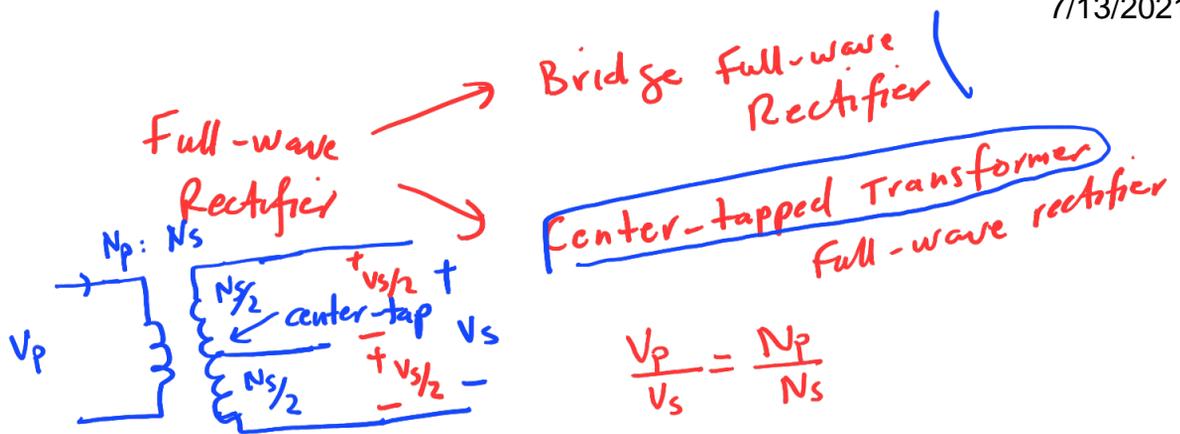

ENEE236 – Analog Electronics

Center Tapped Transformer Full-Wave Rectifier


Special case

$N_p = 1$
 $N_s = 2$

$\frac{V_p}{V_s} = \frac{1}{2}$


$V_s = 2 V_p$

$\frac{V_s}{2} = V_p$

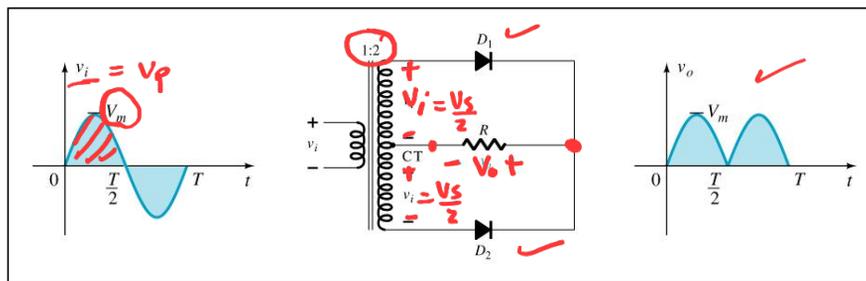

Requires two diodes and a center-tapped transformer

Note: *صلاطظ هامة جدا*
if turns ratio is other than 1:2, make sure to calculate V_m at the secondary side correctly

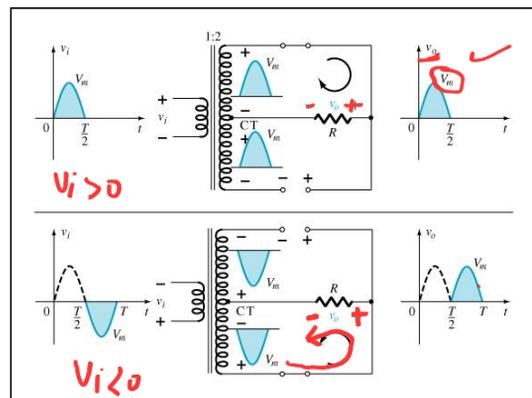

ENEE236 – Analog Electronics

CT Transformer Full-Wave Rectifier

1) When $V_i(t) > 0$,

D1 is ON

D2 is OFF

$$\Rightarrow V_o(t) = V_i(t)$$

2) When $V_i(t) < 0$,


D1 is OFF

D2 is ON

$$\Rightarrow V_o(t) = -V_i(t)$$

$$V_{AVG} = \frac{2V_m}{\pi} \cong 0.636V_m$$
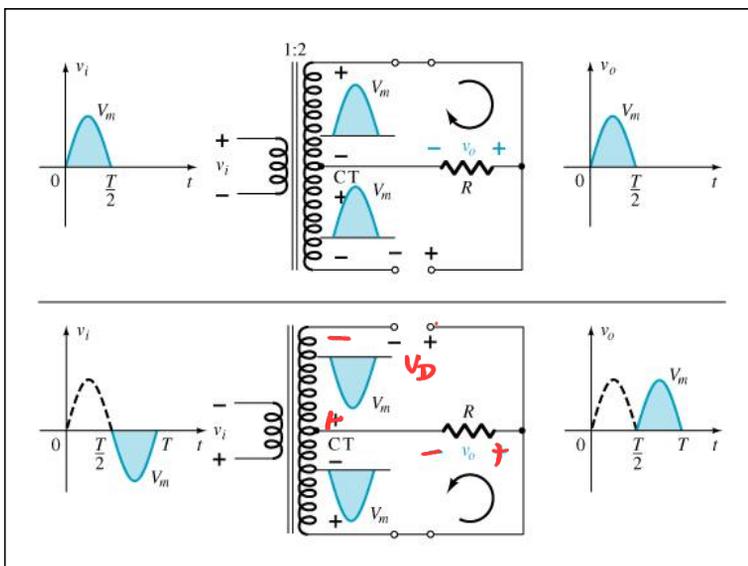
$$T = \frac{T_o}{2} \text{ and } f = 2f_o$$




$\nearrow PIV = -2V_m$

	Half wave	Bridge	center-tapped
Diodes	1	(4)	(2)
Transformer	regular	regular	center-tapped
avg-voltage	$0.318 V_m$	$0.636 V_m$	$0.636 V_m$
PIV	$-V_m$	$-V_m$	$-2V_m$


End of L6

dc Power supply


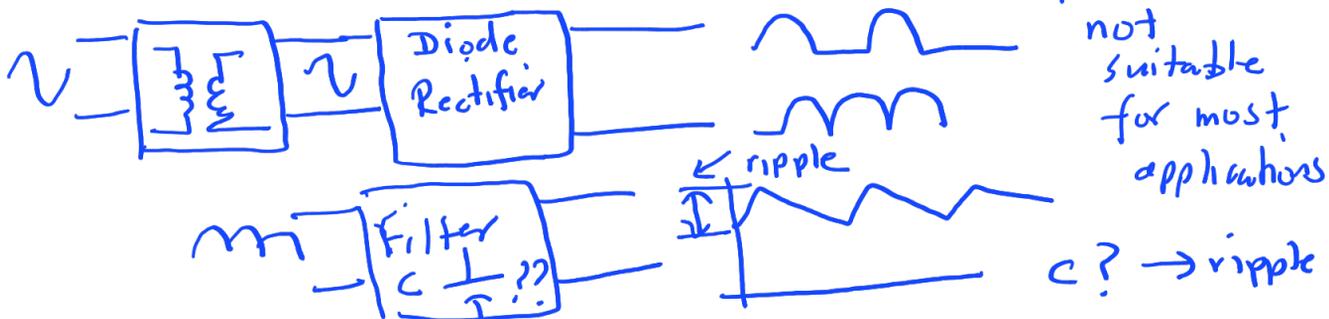


ENEE236 – Analog Electronics

3) Filter


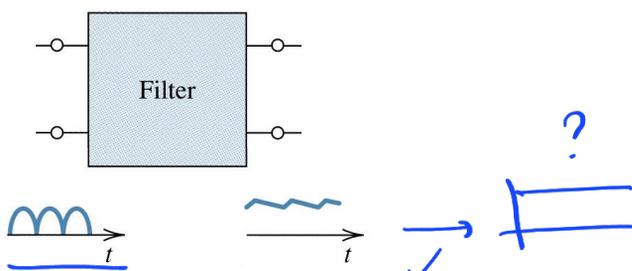


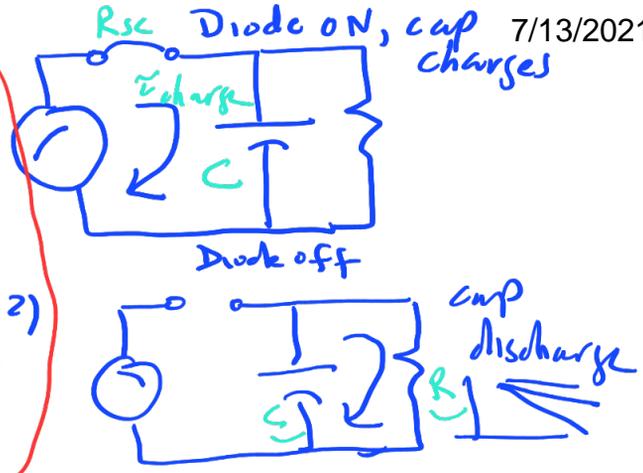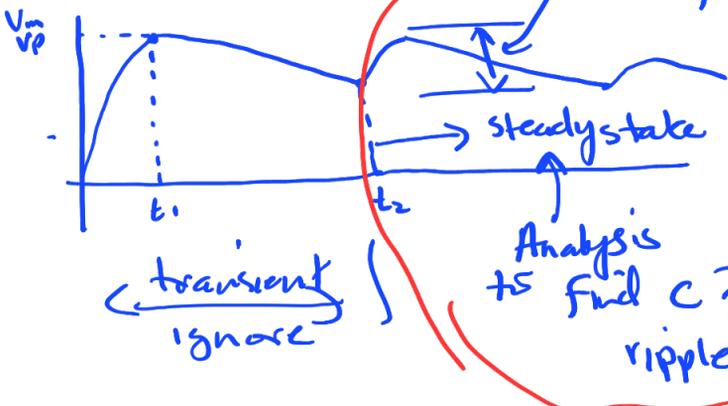
- One of dc power supply components
- Used to smooth out (remove) the pulsating DC produced by the rectifiers and to pass only the DC component (average value; mean value)



Simplified Circuit

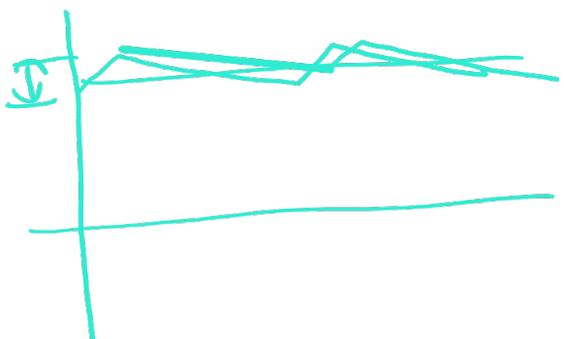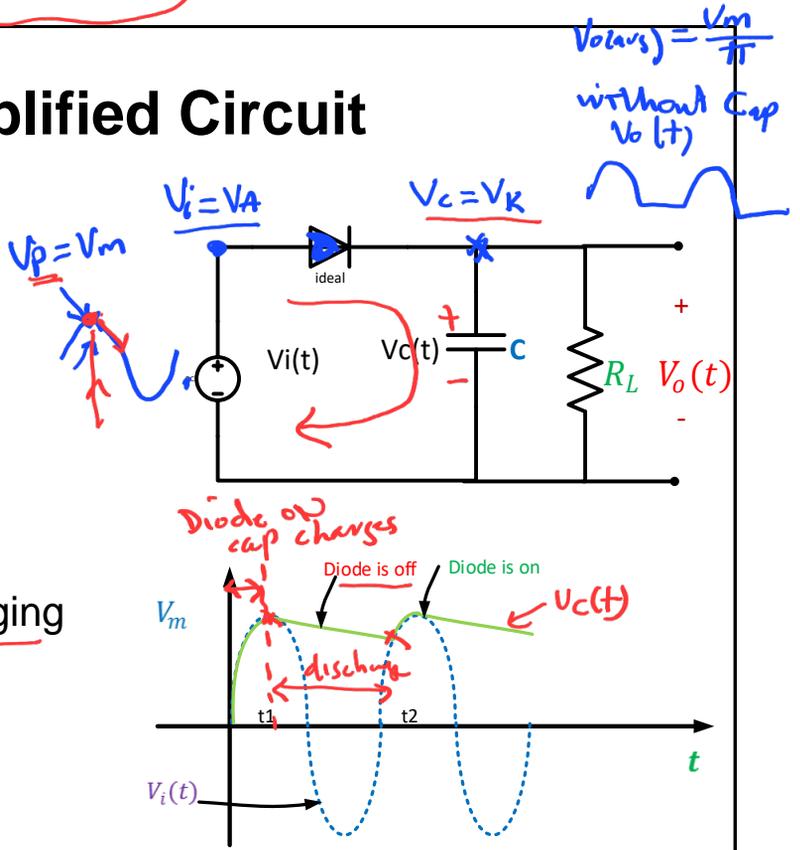- A) when $V_i(t) > V_c(t)$;
Diode is on and $V_o(t) = V_c(t) = V_i(t)$
- B) when $V_i(t) < V_c(t)$;
Diode is off and the capacitor starts discharging




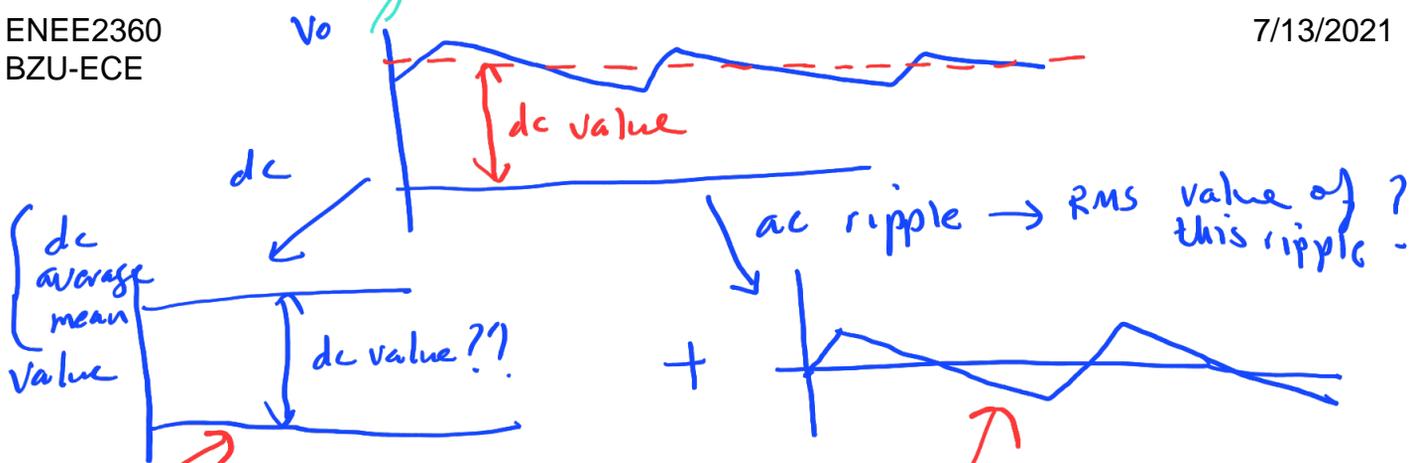

- Ripple factor is an indicator for the effectiveness of the filter

$$r\% = \frac{\text{RMS(ripple of output voltage)}}{\text{Average value of the output signal}} \times 100\%$$

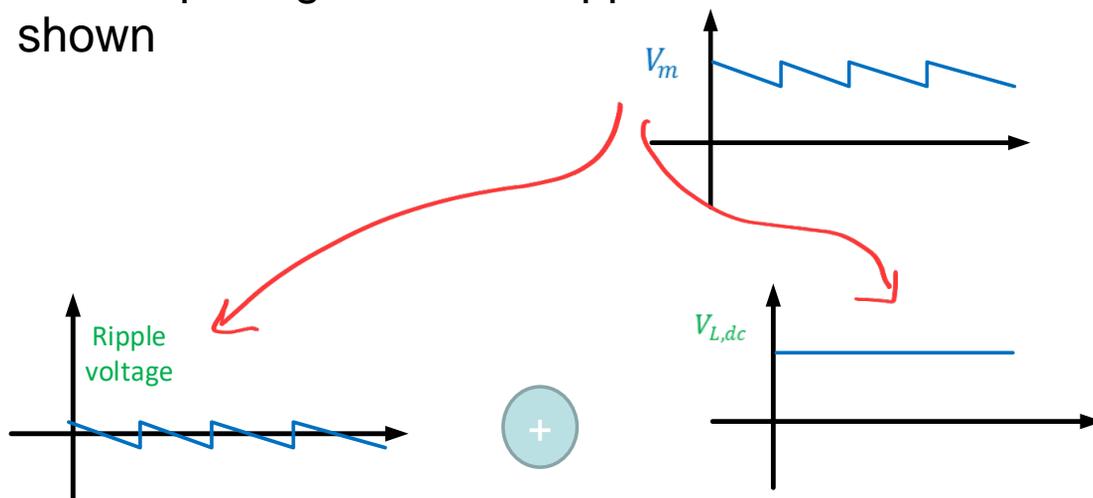- The output signal can be approximated as shown




Example

Find average output voltage?

$$V_{dc} = V_{avg} = \frac{1}{T} \int_0^T f(t) dt$$

peak to peak } → $V_{Lr, PP}$
 ripple →

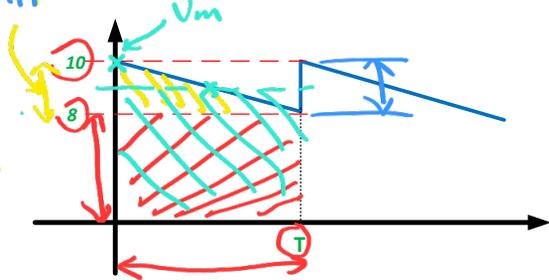

$$V_{O,DC} = V_{O,AVG} = \frac{1}{T} \int_0^T V_O(t) dt$$

$$= \frac{1}{T} (\text{Area})$$

$$= \frac{1}{T} (8T + \frac{2T}{2}) = 9 \text{ V}$$


OR

$$V_{O,DC} = V_m - \frac{1}{2} V_{Lr,p-p}$$

where $V_m = 10$
 $V_{Lr,p-p} = 2$

$$V_{O,DC} = 10 - \frac{1}{2} \cdot 2 = 9 \text{ V}$$

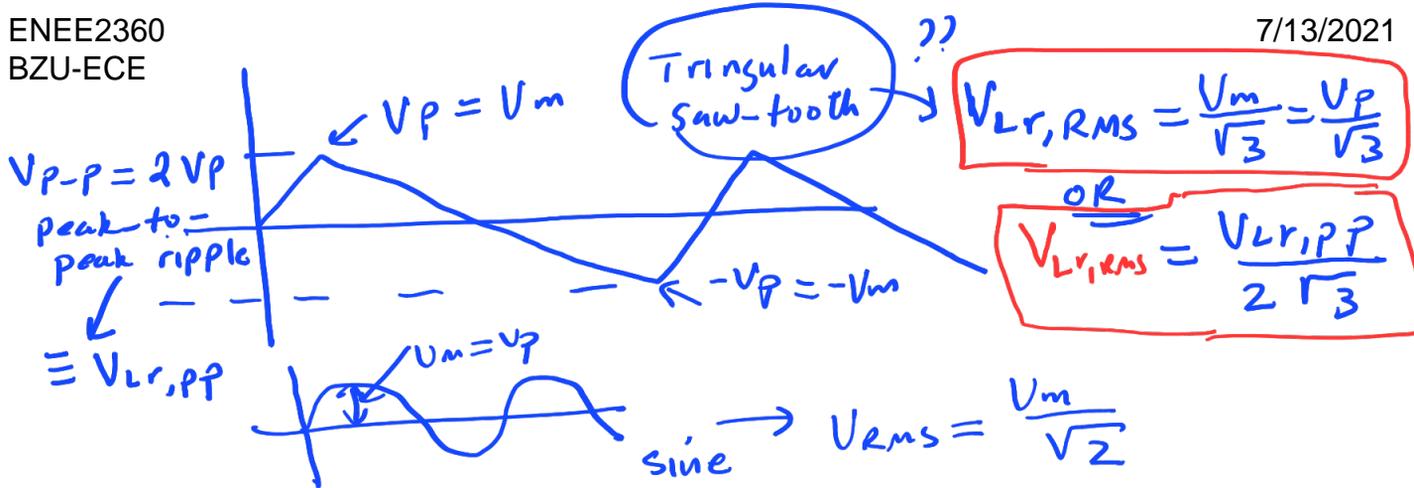? $r\% = \frac{\text{RMS value}}{\text{average}} \cdot 100\%$



- Also for a triangular signal,

RMS Value = $\frac{\text{Peak Value}}{\sqrt{3}}$ ***


OR

RMS Value = $\frac{\text{Peak to peak Value}}{2\sqrt{3}} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$

*** $\therefore r\% = \frac{\frac{V_{Lr,p-p}}{2\sqrt{3}}}{V_m - \frac{1}{2}V_{Lr,p-p}} \cdot 100\%$

\rightarrow RMS ripple

\rightarrow dc value

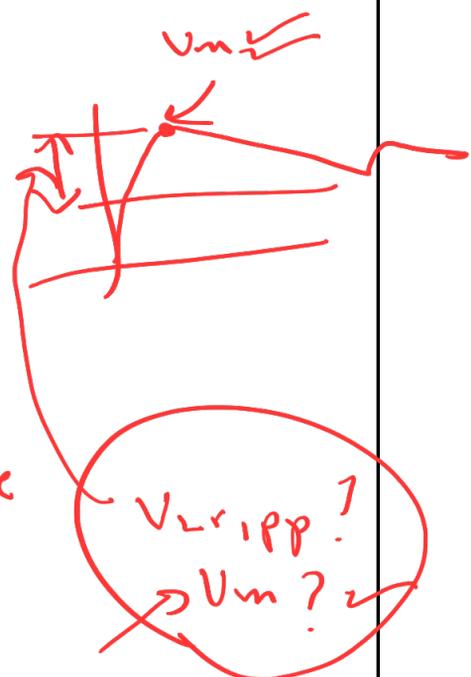

\Rightarrow To Determine the ripple factor we need to find the peak to peak ripple $V_{Lr,p-p}$

$\rightarrow V_m ?$
 $\rightarrow C$
 $\rightarrow f$
 $\rightarrow R$

$V_m = V_{max}$
 $V_c = V_{max} e^{-\frac{t}{\tau}}$
 $V_{min}!$ in general
 $= V_{max} e^{-\frac{(t-t_0)}{\tau}}$

Ripple Factor

For $t_2 > t > t_1$

discharge equation

$$V_L(t) = V_m e^{-\frac{(t-t_1)}{RC}}$$

$$V_{Lr,p-p} = V_L(t_1) - V_L(t_2)$$

$$V_{Lr,p-p} = V_m - V_m e^{-\frac{(t_2-t_1)}{RC}}$$

$$V_{Lr,p-p} = V_m \left[1 - e^{-\frac{(t_2-t_1)}{RC}} \right]$$

using $e^{-x} \approx 1 - x$

cap. discharge

V_m

V_0

$V_{Lr,pp}$

t_1

t_2

t

V_p

v_1

v_0

V_r

Δr

Conduction interval Δr

(b)

i_D

i_L

* $V_{Lr,pp} = V_m \left[1 - \left(1 - \frac{t_2-t_1}{RC} \right) \right] = V_m \left[\frac{t_2-t_1}{RC} \right]$ **

* $V_{L,dc} = V_{L,avg} = V_m - \frac{1}{2} V_{Lr,pp}$


* $r\% = \frac{RMS \text{ ripple}}{V_{L,dc}} \cdot 100\%$

ENEE236 – Analog Electronics

using $e^{-x} \cong 1 - x$

$$V_{Lr,p-p} = V_m \left[1 - e^{-\frac{(t_2 - t_1)}{RC}} \right] \Rightarrow V_{Lr,p-p} = V_m \left(\frac{(t_2 - t_1)}{RC} \right)$$

$$V_{L,dc} = V_m - \frac{1}{2} V_{Lr,p-p}$$

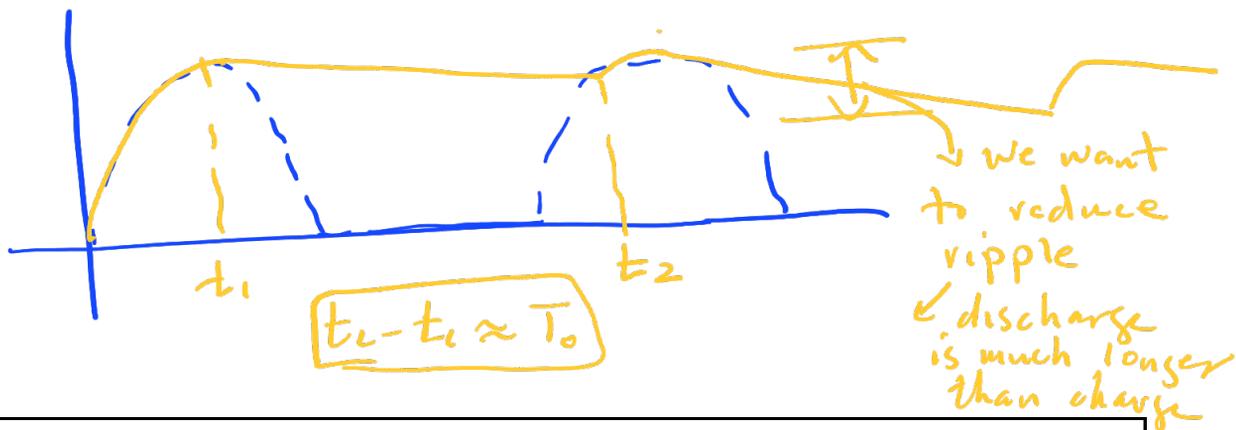

ENEE236 – Analog Electronics

a) For Half Wave Rectifier

$$t_2 - t_1 \cong T_0 = \frac{1}{f_0}$$

$$V_{Lr,p-p} = V_m \left(\frac{T_0}{RC} \right) = V_m \left(\frac{1}{f_0 RC} \right)$$

$$V_{L,dc} = V_m \left(1 - \frac{1}{2f_0 RC} \right)$$

$$(V_{L,r})_{RMS} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$(V_{L,r})_{RMS} = \frac{V_m}{2\sqrt{3}f_0 RC}$$

$$\therefore r \% = \frac{(V_{L,r})_{RMS}}{V_{L,dc}} 100\%$$

$$\therefore r \% = \frac{1}{\sqrt{3}[2f_0 RC - 1]} 100\%$$



ENEE236 – Analog Electronics

b) For Full Wave Rectifier

$$t_2 - t_1 \cong \frac{1}{2} T_0 = \frac{1}{2f_0}$$

$$V_{Lr,p-p} = V_m \left(\frac{T_0}{2RC} \right) = V_m \left(\frac{1}{2f_0 RC} \right)$$

$$V_{L,dc} = V_m \left(1 - \frac{1}{4f_0 RC} \right)$$

$$(V_{L,r})_{RMS} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$(V_{L,r})_{RMS} = \frac{V_m}{4\sqrt{3}f_0 RC}$$

Half wave

$$\rightarrow V_{ripp} = \frac{V_m}{f_0 RC}$$



$$\therefore r\% = \frac{1}{\sqrt{3}[4f_0 RC - 1]} 100\%$$

X

$$r\% = \frac{\text{RMS ripple}}{\text{dc value}} \cdot 100\%$$


$$V_{Lr,RMS} = \frac{V_{Lr,pp}}{2\sqrt{3}}$$

$$V_{Lr,pp} = \frac{V_m}{2f_0RC}$$

$$V_{in,p} = V_m = 30\sqrt{2}$$

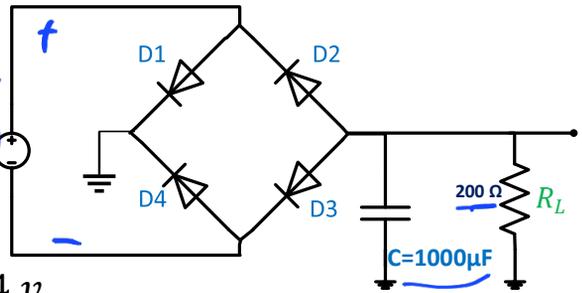Example

- Find the ripple factor $r\%$
- Input = 30V RMS
- $f = 60$ Hz



Full-wave rectifier


$$V_{L,dc} = V_m - \frac{1}{2} \frac{V_m}{2f_0RC} = 41.54 \text{ v}$$

$$V_{Lr,p-p} = \frac{V_m}{2f_0RC} = 1.7677 \text{ v} = \frac{30\sqrt{2}}{2 \times 60 \times 200 \times 1000 \mu\text{F}} = 1.7677$$

$$\text{RMS (ripple voltage)} = \frac{V_{Lr,p-p}}{2\sqrt{3}} = 0.51 \text{ v rms}$$


$$\therefore r = \frac{0.51}{41.54} \times 100\%$$

$$r = 1.2277\%$$

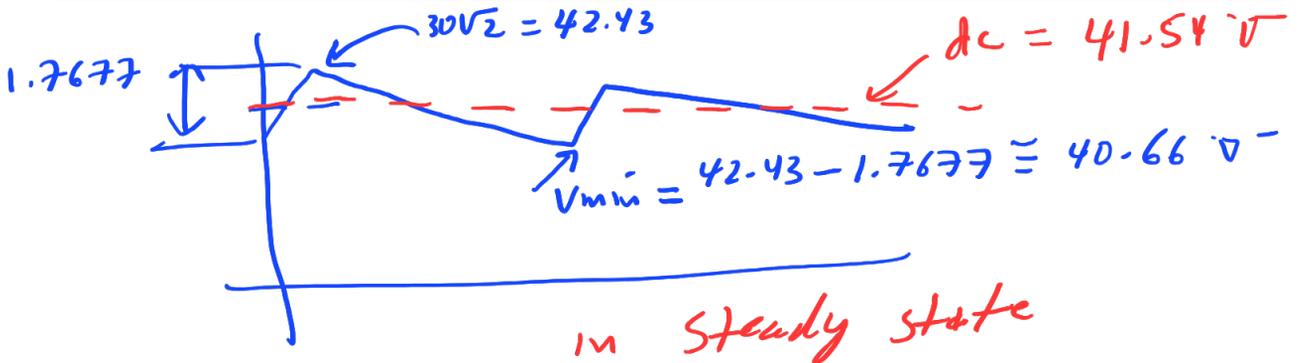

- Calculate $V_L(\text{avg})$ and $r\%$ if $C=400\mu\text{F}$

Full-wave

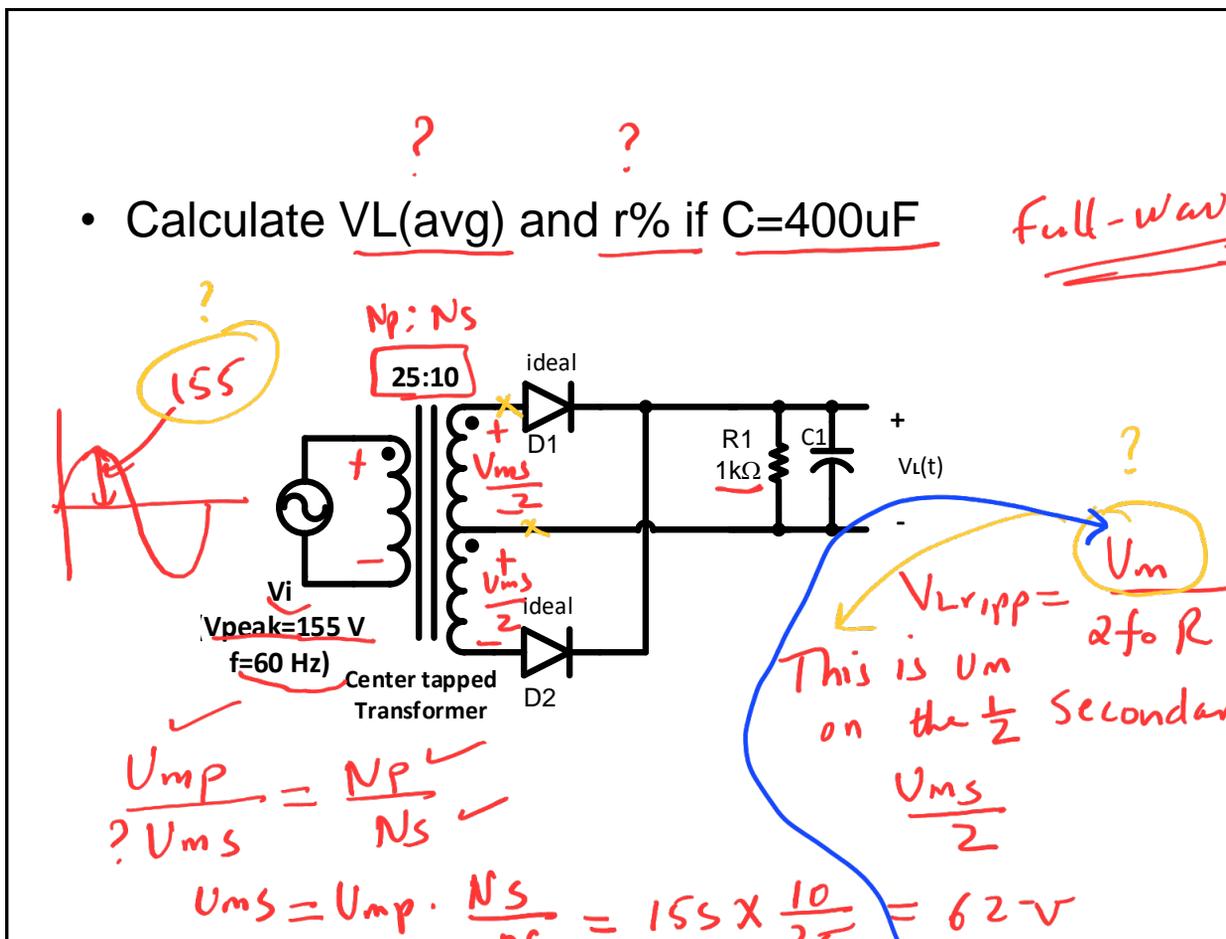

$$\frac{U_{mp}}{U_{ms}} = \frac{N_p}{N_s}$$

$$U_{ms} = U_{mp} \cdot \frac{N_s}{N_p} = 155 \times \frac{10}{25} = 62 \text{ V}$$

$$\frac{U_{ms}}{2} = \frac{62}{2} = 31 \text{ V}$$

$$V_{L, \text{ripple}} = \frac{31}{2 \times 60 \times 1k \times 400 \mu\text{F}} = 0.6458 \text{ V}$$

$$V_L, \text{avg} = U_m - \frac{1}{2} V_{L, \text{ripple}} = 31 - \frac{1}{2} (0.6458) = 30.677 \text{ V}$$

$$r\% = \frac{V_{L,ripple}}{2\sqrt{3}} \cdot 100\%$$

$$= \frac{0.6458}{2\sqrt{3}} \cdot 100\% =$$

$$= \frac{0.6458}{30.677} \cdot 100\% =$$

$$= 0.607\%$$

Home Work 1

Sample not to be solved

NOTE THAT EACH STUDENT WILL HAVE DIFFERENT DESIGN TARGET

- Design a rectifier with filter to provide an a load ($R_L = 0.45 \text{ kohm}$) with an average voltage equal to 20 Vdc with a ripple factor $= 4.5\%$, V_{in} is sinusoidal with 220 Vrms , $f = 50 \text{ Hz}$
- Perform the design three times using :


- Half Wave rectifier
- Bridge Full wave rectifier
- Center tapped full wave rectifier



Simulate your designed circuits using Pspice

+ Transfer + filter

محاكاة

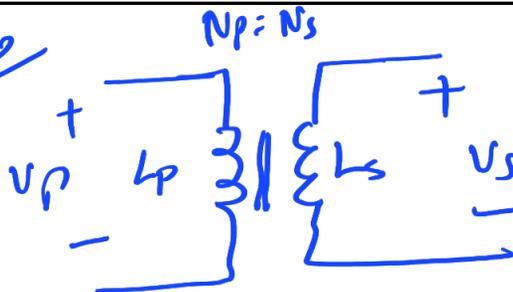

K-coupling
K = 1

$$\frac{V_P}{V_S} = \frac{N_P}{N_S} = \sqrt{\frac{L_P}{L_S}}$$