



ENEE236 CH4 Homework Problems

10. Given the information provided in Fig. 4.123, determine:

- a. R_C .
- b. R_E .
- c. R_B .
- d. V_{CE} .
- e. V_B .

11. Given the information provided in Fig. 4.124, determine:

- a. β .
- b. V_{CC} .
- c. R_B .

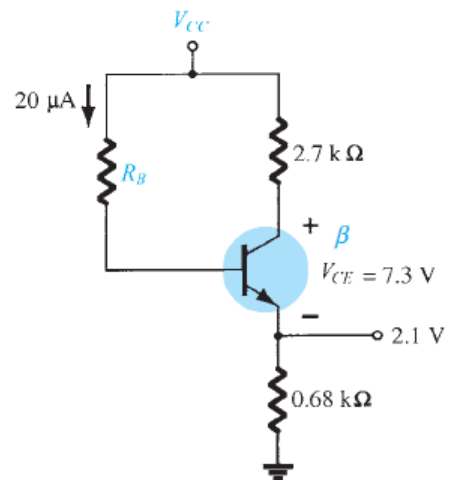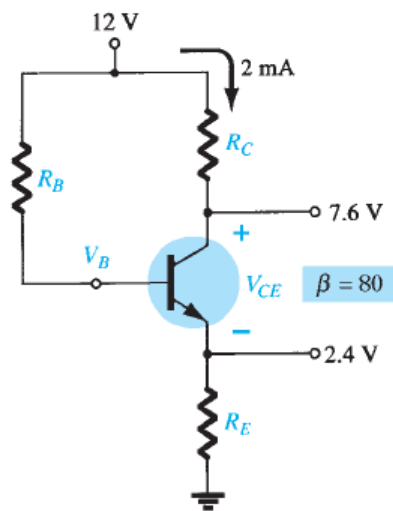

18. Given the information appearing in Fig. 4.127, determine:

- a. I_C .
- b. V_E .
- c. V_{CC} .
- d. V_{CE} .
- e. V_B .
- f. R_1 .

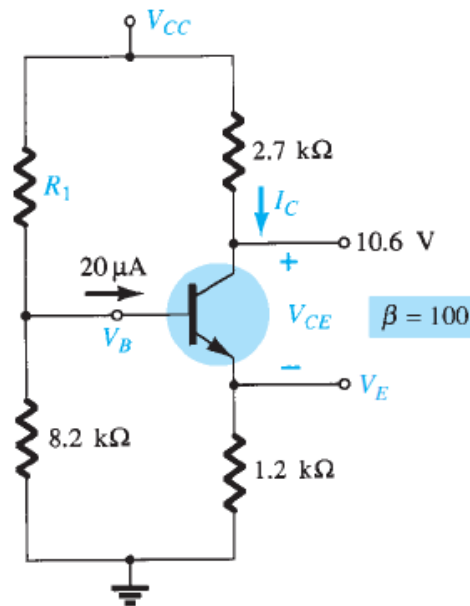


FIG. 4.127

*33. Given $V_B = 4\text{ V}$ for the network of Fig. 4.133, determine:

- a. V_E .
- b. I_C .
- c. V_C .
- d. V_{CE} .
- e. I_B .
- f. β .

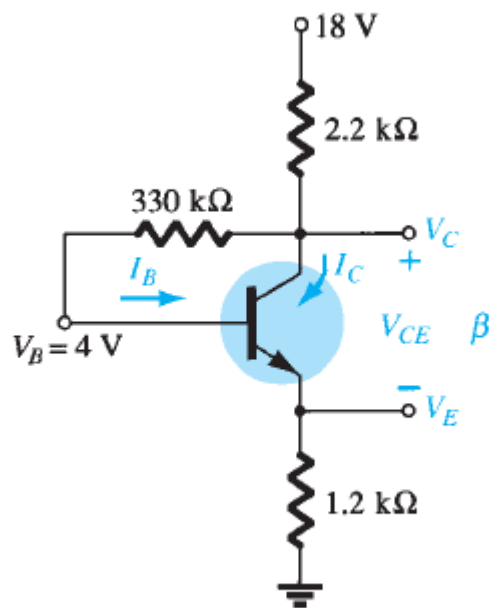


FIG. 4.133

*34. Determine the level of V_E and I_E for the network of Fig. 4.134.

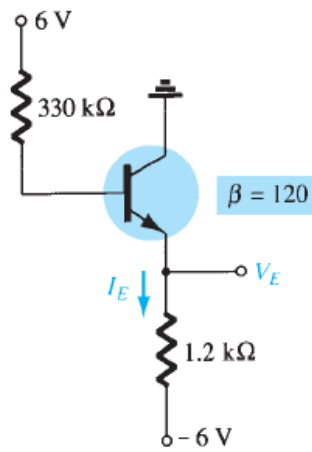


FIG. 4.134

43. Design a voltage-divider bias network using a supply of 24 V, a transistor with a beta of 110, and an operating point of $I_{CQ} = 4$ mA and $V_{CEQ} = 8$ V. Choose $V_E = \frac{1}{8}V_{CC}$. Use standard values.

46. For the Darlington amplifier of Fig. 4.142 determine
- the level of β_D .
 - the base current of each transistor.
 - the collector current of each transistor.
 - the voltages V_{C1} , V_{C2} , V_{E1} , and V_{E2} .

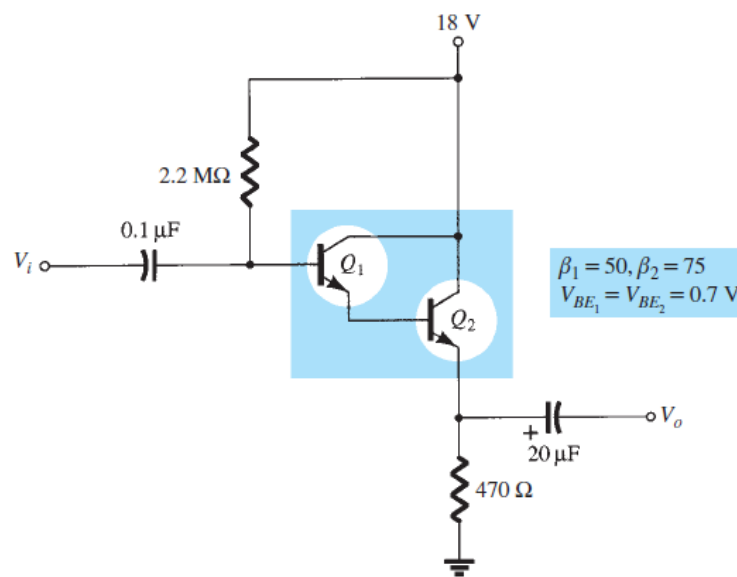


FIG. 4.142

56. Determine I_E and V_C for the network of Fig. 4.152.

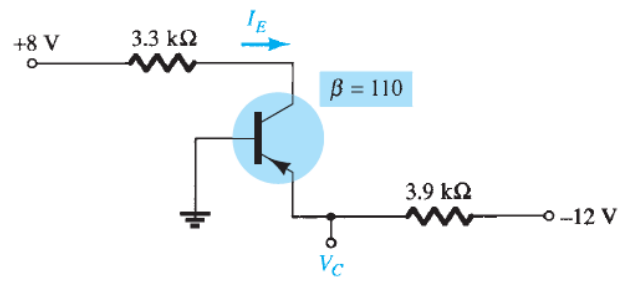


FIG. 4.152