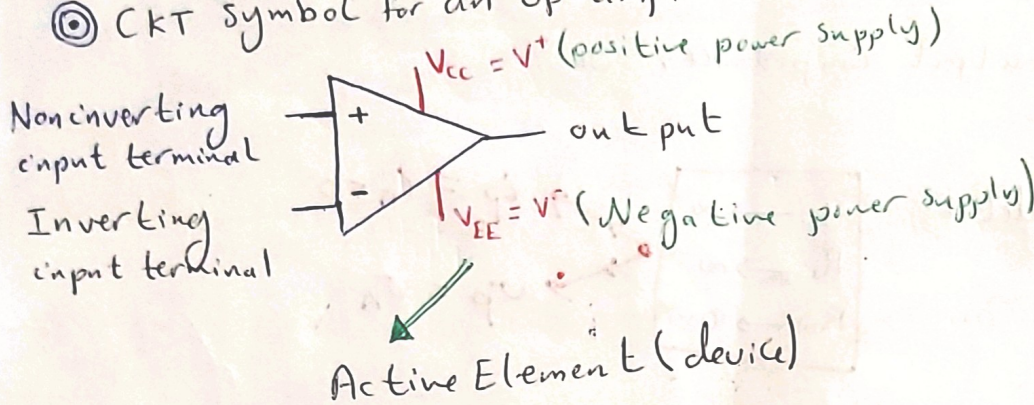





The Operational Amplifier ((Op-amp))

* It was referred to as operational because it was used to implement the mathematical operations of integration, differentiation, addition, sign changing, and scaling.

◎ CKT symbol for an op-amp.




◎ commercially available device (741)

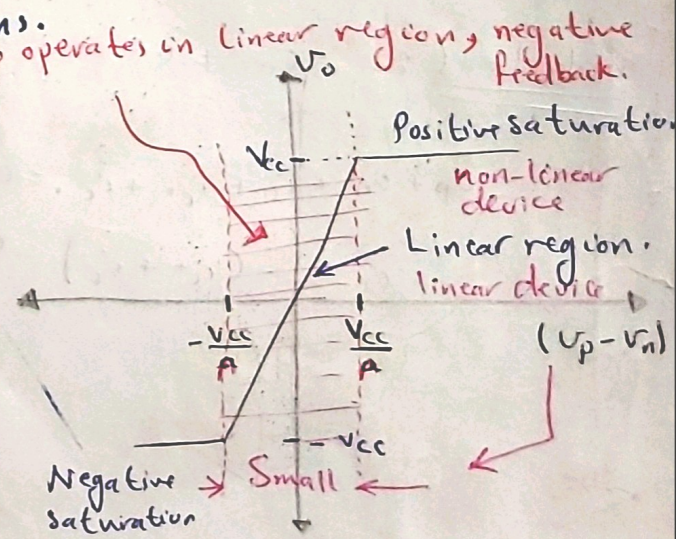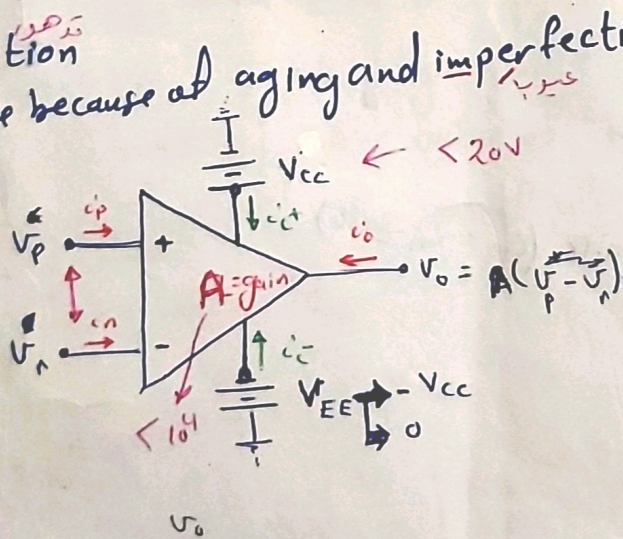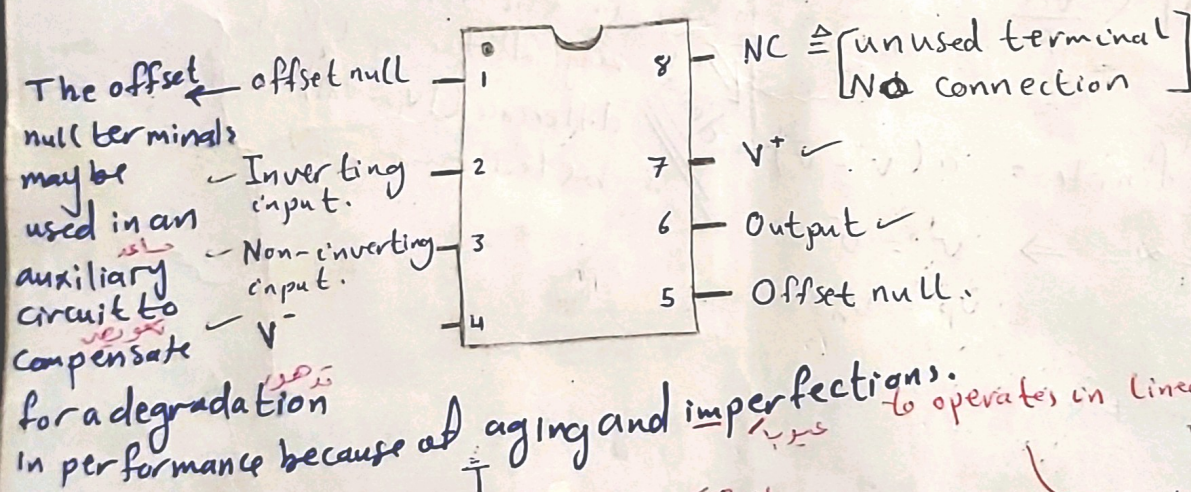

$$V_o = \begin{cases} +V_{cc} & A(V_p - V_n) > +V_{cc} \\ -V_{cc} & A(V_p - V_n) < -V_{cc} \\ A(V_p - V_n) & -V_{cc} \leq A(V_p - V_n) \leq +V_{cc} \end{cases}$$

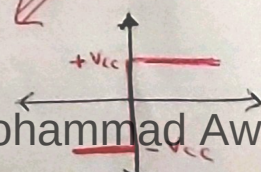• The voltage transfer characteristic of an op amp.



OP-Amp Properties :-

- 1) Very large gain [Ratio between v_o, v_i], a
10,000
- 2) Very large input impedance. $M\Omega$
- 3) Very small output impedance. Ω

Ideal Op-amp Model :-

① $i_p = i_n = 0$

$a \rightarrow \infty$
$R_i \rightarrow \infty$
$R_o \rightarrow 0$

$i_p = i_n = 0$

$v_p = v_n$

② $|v_o| < +V_{cc}$

$|A(v_p - v_n)| < V_{cc}$

$|v_p - v_n| < \frac{V_{cc}}{A} = \frac{20V}{10^4} \approx 2mV$

in the linear region, the mag. of the input voltage difference ($|v_p - v_n|$) must be less than 2mV


② $v_o = f_{in} = a(v^+ - v^-)$

$\frac{v_o}{a} = (v^+ - v^-)$, $a \approx \infty \Rightarrow v^+ = v^-$
 $v_p = v_n$

note that : $i_o \neq 0$


$i_p + i_n + i_o + i_c^+ + i_c^- = 0$

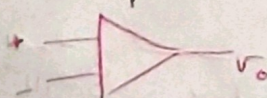$i_o = -(i_c^+ + i_c^-)$ Since $(i_p = i_n = 0)$



Some Important Op-Amp Circuits

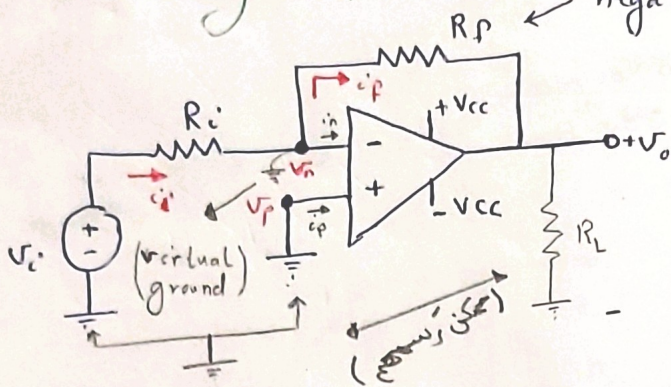1) Inverting Amplifier :- negative feedback.



$$\begin{aligned} v_p &= v_n \\ i_p &= i_n = 0 \end{aligned}$$


a) Since $v_p = 0$, $v_n = v_p = 0$

$$i_i = \frac{v_i}{R_i}$$

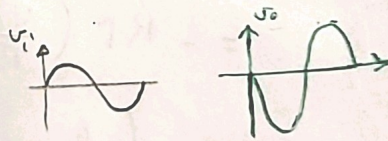b) Since $i_n = i_p = 0 \Rightarrow i_f = i_i = \frac{v_i}{R_i}$

$$v_o = -R_f i_f = -R_f \left[\frac{v_i}{R_i} \right] = -\frac{R_f}{R_i} v_i$$

$$\frac{v_o}{v_i} = \text{gain} = -\frac{R_f}{R_i}$$



inverting, input from inv terminal

* The upper limit on the gain $\frac{R_f}{R_i}$, is determined by the power supply voltages and the value of R_i the signal voltage v_i .


$\Rightarrow$ if $V^+ = V^- \Rightarrow V_{cc} = V_{EE} = V_{cc}$

$$|v_o| \leq V_{cc}$$


$$\left| \frac{R_f}{R_i} v_i \right| \leq V_{cc}$$

$$\frac{R_f}{R_i} \leq \left| \frac{V_{cc}}{v_i} \right|, \text{ if } V_{cc} = 15V, v_i = 10mV, \boxed{\frac{R_f}{R_i} \leq 1500}$$

practically not 15V

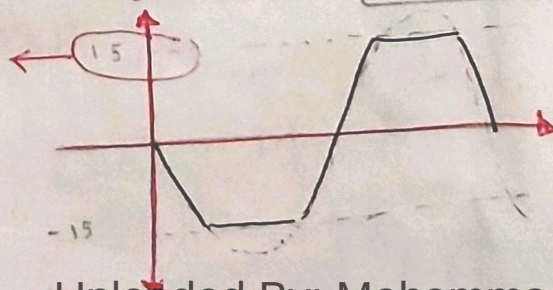

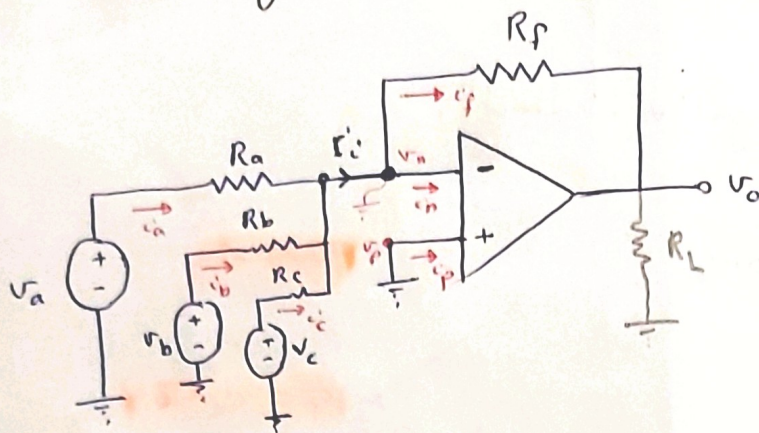7. Inverting Adder ((Summing Amplifier)) ((Mixer))



a) Since $v_p = 0 \Rightarrow v_p = v_n = 0$

$$i_a = \frac{v_a}{R_a}, \quad i_b = \frac{v_b}{R_b}, \quad i_c = \frac{v_c}{R_c}$$

$$i_i = i_a + i_b + i_c$$

b) Since $i_n = i_p = 0 \Rightarrow i_i = i_f$

$$v_o = -R_f i_f = -R_f (i_a + i_b + i_c)$$

$$= -R_f \left(\frac{v_a}{R_a} + \frac{v_b}{R_b} + \frac{v_c}{R_c} \right)$$

$$= - \left(\frac{R_f}{R_a} v_a + \frac{R_f}{R_b} v_b + \frac{R_f}{R_c} v_c \right)$$

Special Cases

i) if $R_a = R_b = R_c = R_i$

$$v_o = - \frac{R_f}{R_i} (v_a + v_b + v_c)$$

ii) if $R_a = R_b = R_c = R_i = R_f$

$$v_o = -(v_a + v_b + v_c) \quad \text{op-amp as an adder}$$

iii) if $R_a = R_b = R_c = R_i$, and



$$R_f = \frac{R_i}{3}$$

$$v_o = - \left(\frac{v_a + v_b + v_c}{3} \right) \quad \text{((average))}$$

3) Non-inverting Amplifier:-

- non-inverting input terminal
- output = (gain) (v_i)

negative feedback.

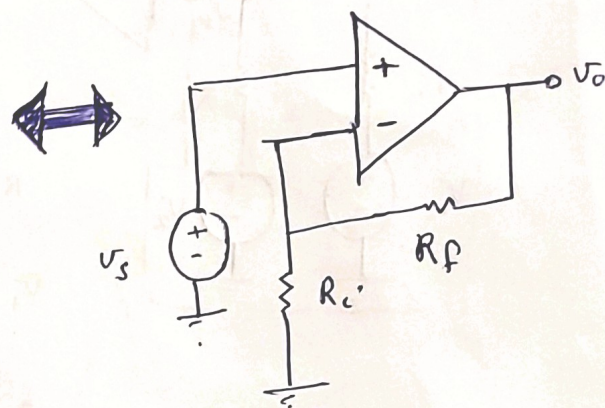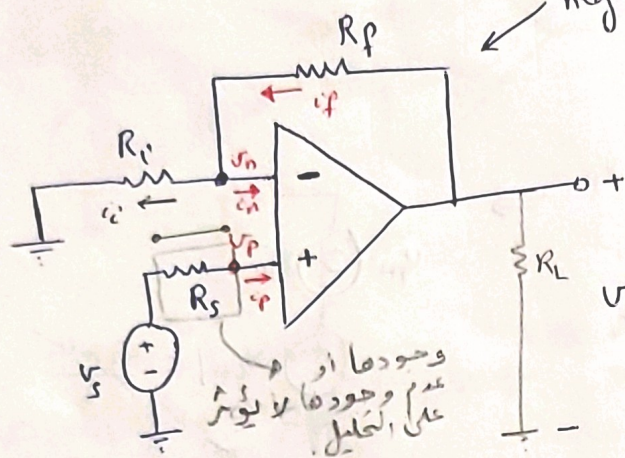

* Since $v_p = v_n \Rightarrow v_p = v_s$ because ($v_n = v_p = 0$)

$$i_i = \frac{v_s - 0}{R_i} = \frac{v_s}{R_i}$$


* Since $v_n = 0 \Rightarrow i_i = i_f$

$$v_o = R_f i_f + v_s$$

$$= R_f \left(\frac{v_s}{R_i} \right) + v_s$$

$$v_o = \left(1 + \frac{R_f}{R_i} \right) v_s$$


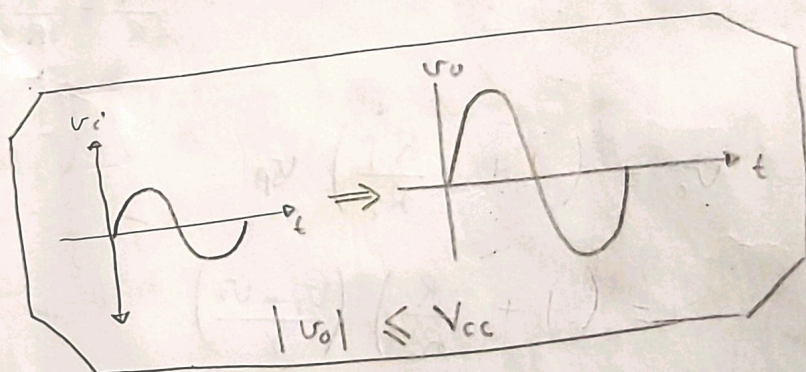
$$\boxed{\frac{v_o}{v_i} = \text{gain} = 1 + \frac{R_f}{R_i}}$$





Special Case:-

if $R_i = \infty$ (open CKT) $\Rightarrow$ v_i موجوده
 $R_f = 0$ (short CKT) $\Rightarrow$ سلك

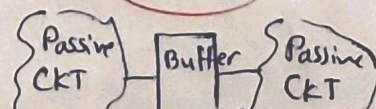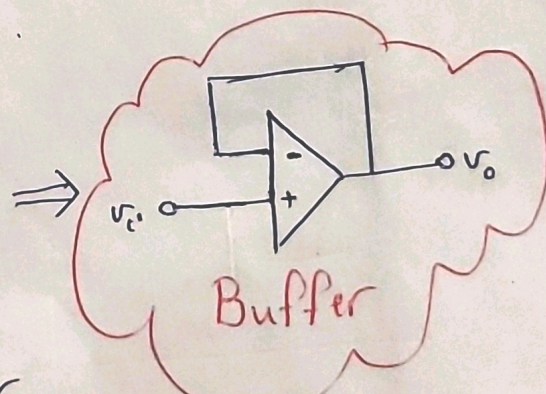$\frac{v_o}{v_i} = 1 = A \triangleq$ unity gain Amplifier
 $\triangleq$ Buffer



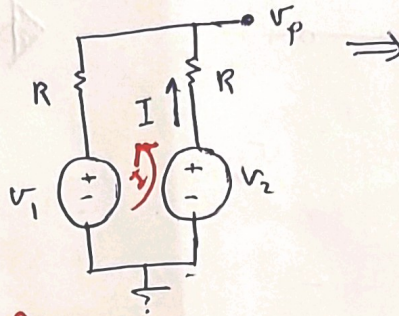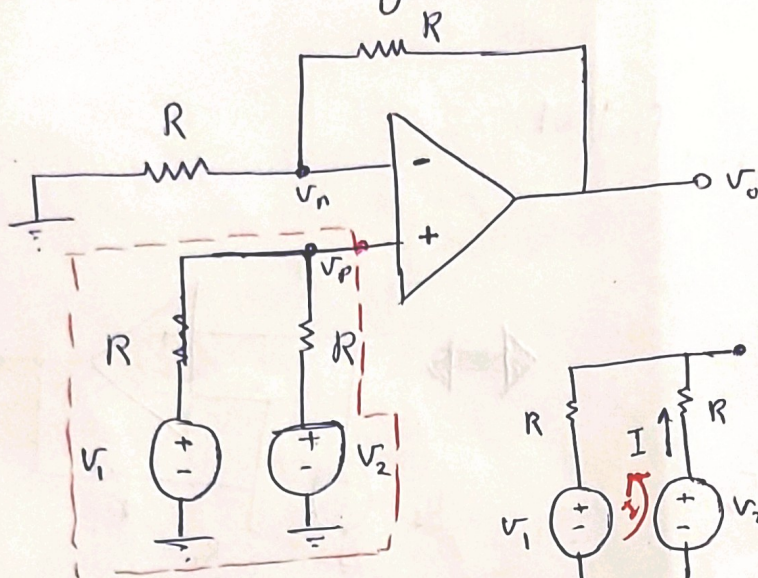4) Non-inverting Adder (Summing Amp) (Mixer)



~~Loop~~
 $V_2 = RI + RI + V_1 =$


$$I = \frac{V_2 - V_1}{2R}$$

$$= \frac{V_2}{2R} - \frac{V_1}{2R}$$

$$V_0 = \left(1 + \frac{R_f}{R_i}\right) V_p$$

$$= \left(1 + \frac{R}{R}\right) \left(\frac{V_1 + V_2}{2}\right)$$

$$\boxed{V_0 = V_1 + V_2}$$

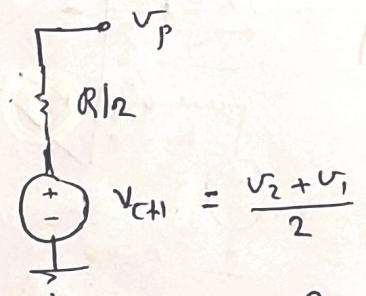

$$R_{TH} = R_{OC} = \frac{R}{2}$$


$$V_{TH} = -RI + V_2$$

$$= -\frac{V_2}{2} + \frac{V_1}{2} + V_2$$

$$= \frac{V_2}{2} + \frac{V_1}{2}$$

$$= \frac{V_2 + V_1}{2}$$

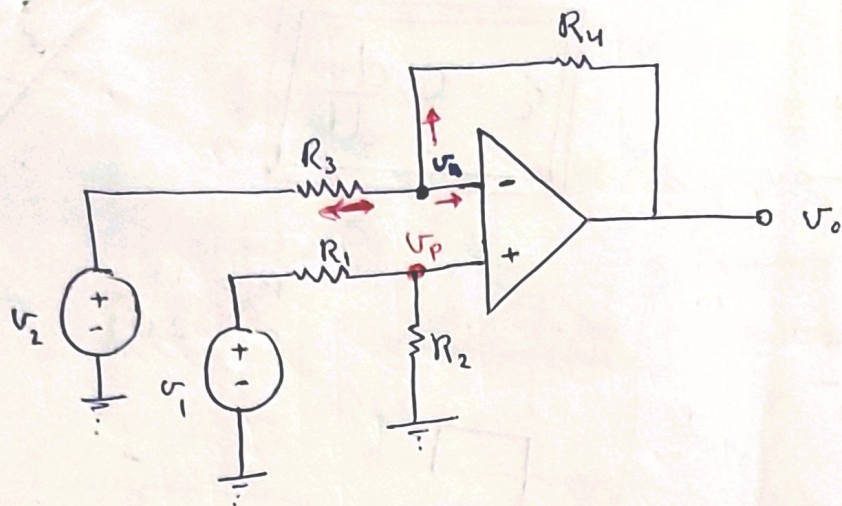5) Difference Amplifier ((Voltage Subtraction))



$$\cancel{0} \quad \frac{V_n - V_2}{R_3} + \frac{V_n - V_0}{R_4} + i_n = 0$$

* $i_p = i_n = 0$

* $V_p = V_n = \frac{R_2}{R_2 + R_1} V_1$

using superposition :-

$$V_0 = \overset{\text{kill } V_1}{V_{01}} + \overset{\text{kill } V_2}{V_{02}}$$

$$= V_2 \left(-\frac{R_4}{R_3} \right) + \left(1 + \frac{R_4}{R_3} \right) V_p \quad \leftarrow \text{voltage divider}$$

$$= V_2 \left(-\frac{R_4}{R_3} \right) + \left(1 + \frac{R_4}{R_3} \right) \left(\frac{R_2}{R_1 + R_2} \right) V_1$$

$\underbrace{\quad}_{b}$
 $\underbrace{\quad}_{a}$

$$= a V_1 - b V_2$$

if

$$R_4 = \infty$$

$$R_3 = 0$$

$$R_2 = \infty$$

$$R_1 = 0$$

$$V_0 = V_2 (-\infty) + (1 + \infty)(\infty)V_1$$


Special Case :-

$$\frac{R_2}{R_1} = \frac{R_4}{R_3} = A \Rightarrow A = \left(\frac{R_2}{R_1} \right) = \left(\frac{R_4}{R_3} \right)$$


$$V_0 = A (V_1 - V_2)$$

$$= -V_2 \left(\frac{aR}{A} \right) + \left(1 + \frac{aR}{A} \right) \left(\frac{aR}{A + aR} \right) V_1$$

6] Differentiator

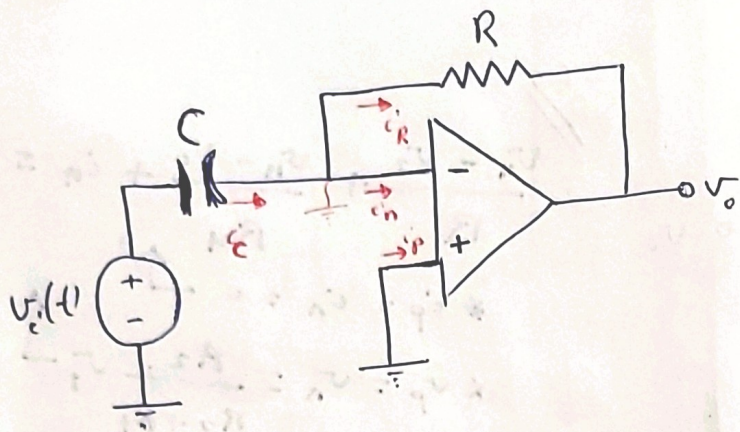

$$i_c = C \frac{dv}{dt}$$

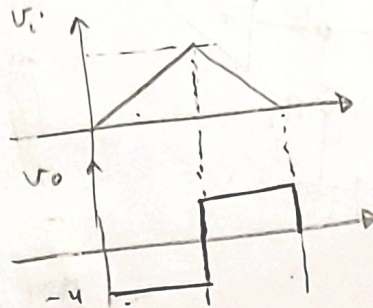

$$i_c = i_R$$

$$C \frac{dv_c}{dt} = i_R = C \frac{d}{dt} (v_i(t) - 0) = C \frac{dv_i}{dt}$$

$$v_o = -R i_R = -R \left[C \frac{dv_i}{dt} \right] = -RC \frac{dv_i(t)}{dt}$$

$$v_o(t) = -RC \frac{dv_i(t)}{dt}$$


$$* \quad \begin{array}{c} \text{---} \text{---} \text{---} \\ + \quad v(t) - \\ \text{---} \text{---} \text{---} \end{array} \rightarrow i(t)$$

$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i dt + v(t_0)$$

in many practical app.
the initial time is
zero, $t_0 = 0$
 $v(t) = \frac{1}{C} \int_0^t i dt + v(0)$

7] Integrator

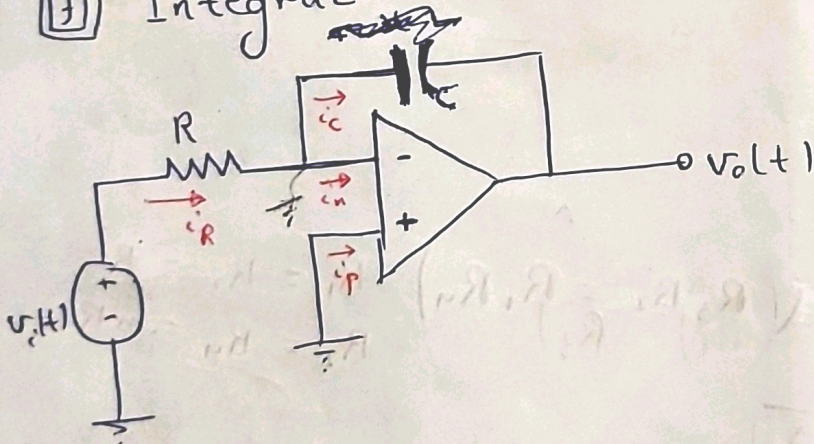


$$i_R = \frac{v_i(t)}{R}$$

$$v_o(t) = -v_c(t) = -\frac{1}{C} \int_{t_0}^t i_c(t) dt + v_o(t_0)$$

$$v_o(t) = -\frac{1}{RC} \int_{t_0}^t v_i(t) dt + v_o(t_0)$$

if $t_0 = 0$

(Capacitor initially discharged)

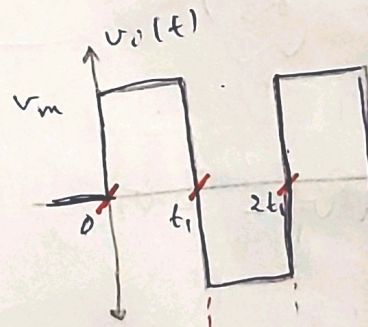

assume that
the initial value
of $v_o(t)$ is zero
at the instant
 v_i steps from 0
to V_m

$$1) \quad v_o = -\frac{1}{RC} V_m t + 0$$

$$0 \leq t \leq t_1$$





$$2) \quad v_o = -\frac{1}{RC} \int_{t_1}^t v_i dt$$

$$= -\frac{1}{RC} V_m t_1$$

$$= \frac{V_m}{RC} t - \frac{2 V_m t_1}{RC}$$

$$t_1 \leq t \leq 2t_1$$

8) Comparators

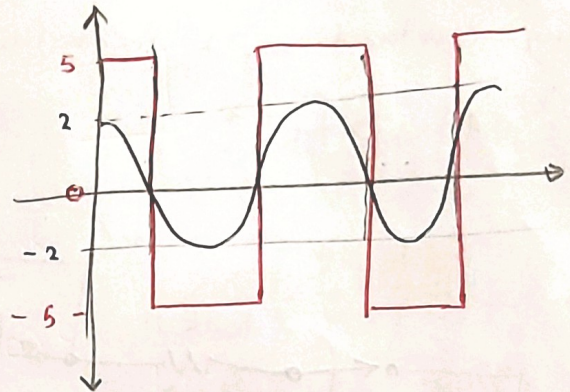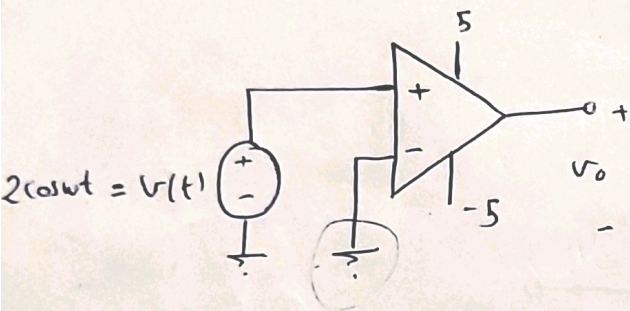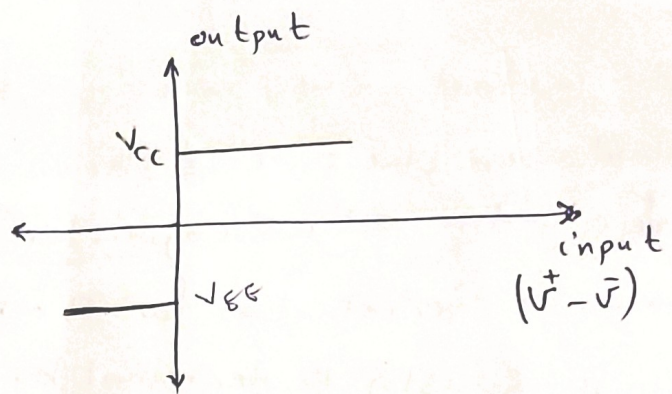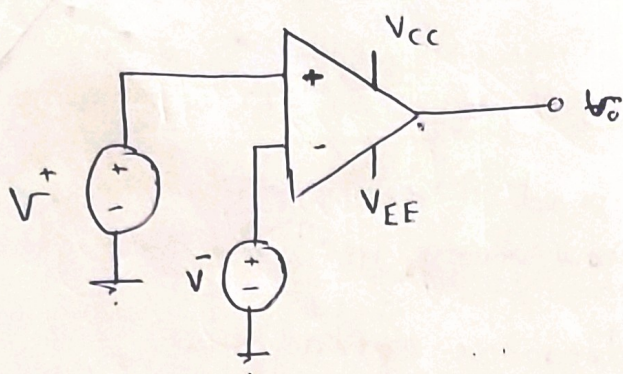

9) Other Op-Amp CKTs



Use:-
 (a) $i_p = i_n = 0$, $v_p = v_n$

(b) Apply nodal analysis to the resulting CKT

(c) Solve nodal equations to express the output voltage in terms of the op-amp input signals.

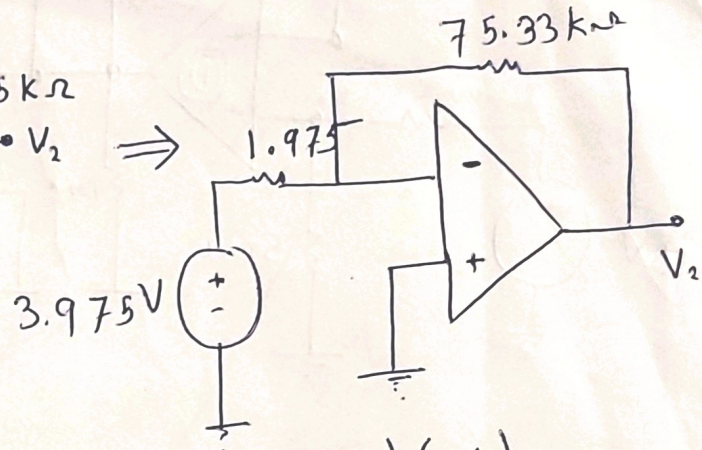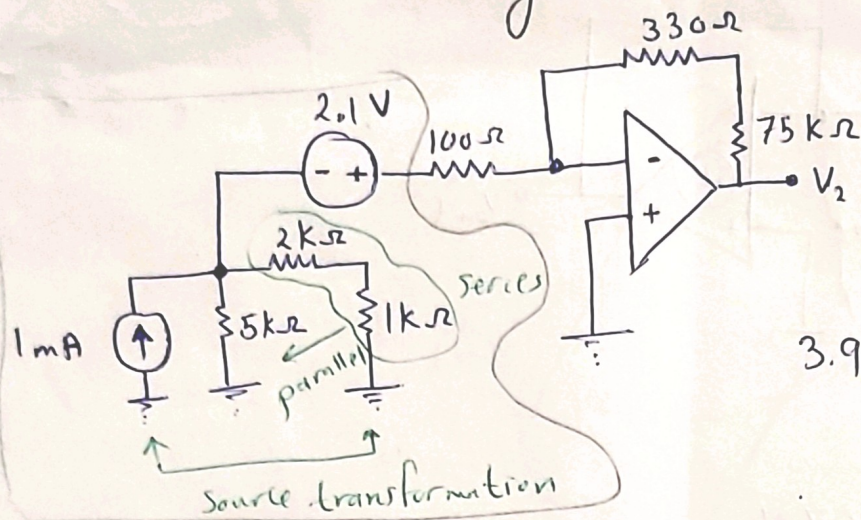Examples

① For the circuit of Figure E1, Calculate the Voltage V_2 .




$$V_2 = -\left(\frac{R_F}{R_i}\right)(V_1)$$

$$= -\left(\frac{75.33k}{1.975k}\right)(3.975)$$

$$= -151.6V$$

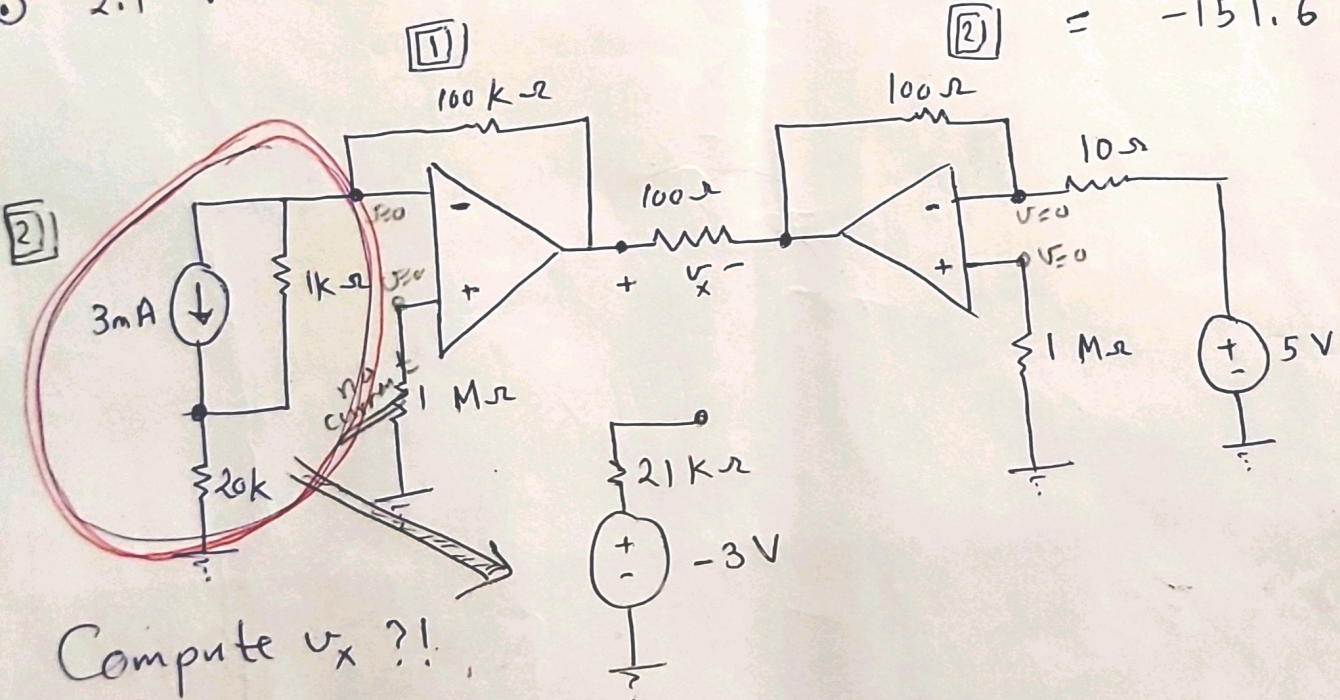- ① $(5k \parallel 1k) = 1.875k\Omega$
- ② $(1mA)(1.875k\Omega) = 1.875V$
- ③ $2.1V + 1.875V = 3.975V$



$$V_{out1} = -\left(\frac{100k}{21k}\right)(-3) = 14.29$$


$$V_{out2} = -\left(\frac{100}{10}\right)(5) = -50$$

$$V_x = V_{out1} - V_{out2} = 14.29 + 50 = 64.29V$$

10

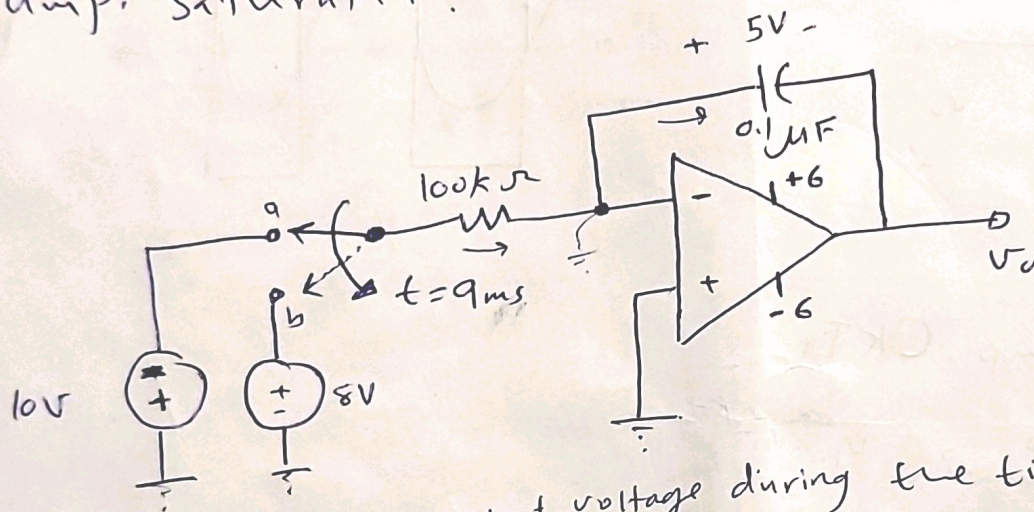example

At the instant the switch makes contact with terminal a in the circuit shown in Figure c1, the voltage on the $0.1 \mu F$ capacitor is $5V$. The switch remains at terminal a for $9ms$ and then moves instantaneously to terminal b. How many ms after making contact with terminal ~~a~~ does the operational amp. saturate.?



The expression for the output voltage during the time the switch is at terminal a is

$$V_o = -\frac{1}{RC} \int_{t_0}^t V_s dt + V_o(t_0)$$

$$= -\frac{1}{(10^2)0} \int_0^t (10) dt - 5$$

$$= (-5 + 1000t) V$$

at $t = 9ms$

$$V_o = -5 + 9 = 4V$$

The expression for the output voltage after the switch moves to terminal b is

$$V_o = 4 - \frac{1}{10^2} \int_{9 \times 10^{-3}}^t 8 dt = 4 - 800(t - 9 \times 10^{-3})$$

$$= (11.2 - 800t) V$$

$$\Rightarrow 11.2 - 800t_s = -6$$

$$t_s = 21.5ms$$