Ac Small Signal Analysis



now

$$i_D(t) = I_{DQ+} i_d(t)$$

$$V_D(t) = V_{DQ} + v_d(t)$$

$$\blacktriangleright i_D(t) = I_S(e^{\frac{V_D(t)}{\eta V_T}} - 1)$$



And since the diode is forward biased

•
$$i_D(t) = I_S(e^{\frac{V_D(t)}{\eta V_T}})$$

• $i_D(t) = I_S(e^{\frac{V_{DQ} + v_d}{\eta V_T}})$
• $i_D(t) = I_S e^{\frac{V_{DQ}}{\eta V_T}} \cdot e^{\frac{V_d}{\eta V_T}}$
• $i_D(t) = I_{DQ}(e^{\frac{v_d}{\eta V_T}})$
• using $e^x = 1 + x$; x is very small

but
$$i_D(t) = I_{DQ+} i_d(t)$$

 $\therefore i_d(t) = \frac{v_d(t)}{\eta V_{T/I_{DQ}}} = \frac{v_d}{r_d}$
where $r_d = \frac{\eta V_T}{I_{DQ}} = \frac{V_T}{I_{DQ}}$

$$i_D(t) = I_{DQ} (1 + \frac{v_d(t)}{\eta V_T}) = I_{DQ+} \frac{v_d(t)}{\eta V_{T/I_{DQ}}}$$

1

- $\therefore \text{ If } V_S(t) = V_S + vs(t)$
- V_S = Dc component
- vs(t) = ac component

and the amplitude of vs(t) is small and the diode is always on ; we could use the superposition theorem to find the response ($V_{D(t)}$, $i_{D}(t)$).



Since we have a dc source (1.2 v) and an ac signal $(4x10^{-3} \sin\omega t v)$ and the diode is always on ; we use superposition theorem to find $V_D(t)$



1) to find V_{DQ} (DC Analysis)



$$\therefore V_{DQ} = 0.3 \text{ v}$$

$$1.2 \text{ v}$$

$$I_{DQ} = \frac{1.2 \text{ v} - 0.3 \text{ v}}{200} = 4.5 \text{ mA}$$

$$\therefore r_{d} = \frac{V_{T}}{I_{DQ}} = \frac{25.69 \text{ mv}}{4.5 \text{ mA}} = 5.69 \Omega$$

$$1.2 \text{ v}$$

$$I_{DQ} = \frac{1.2 \text{ v} - 0.3 \text{ v}}{1.2 \text{ v}} = \frac{1.$$



