
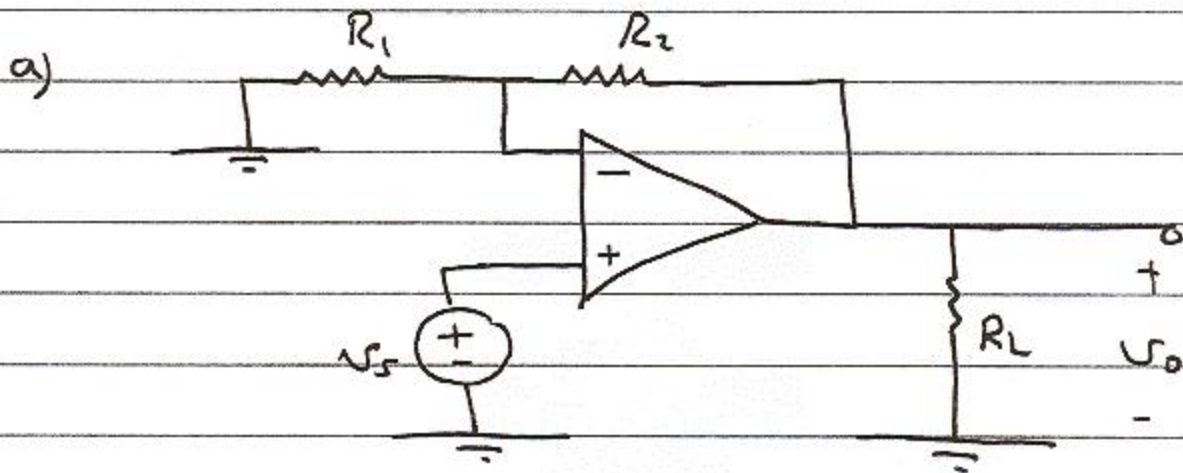


Homework Solution Electronics II EF338

8.26

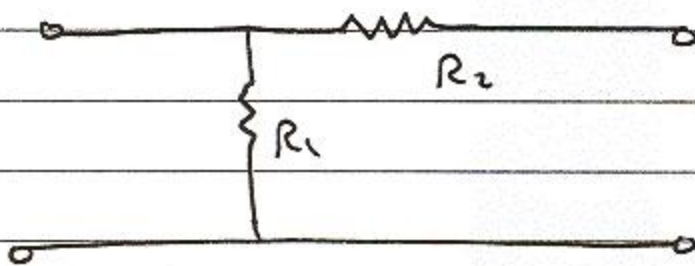


Series-shunt feedback



$$h_{11} = R_1 \parallel R_2, \quad h_{22} = \frac{1}{R_2 + R_1}$$

$$h_{12} = \beta = \frac{R_1}{R_1 + R_2}$$

To find A:

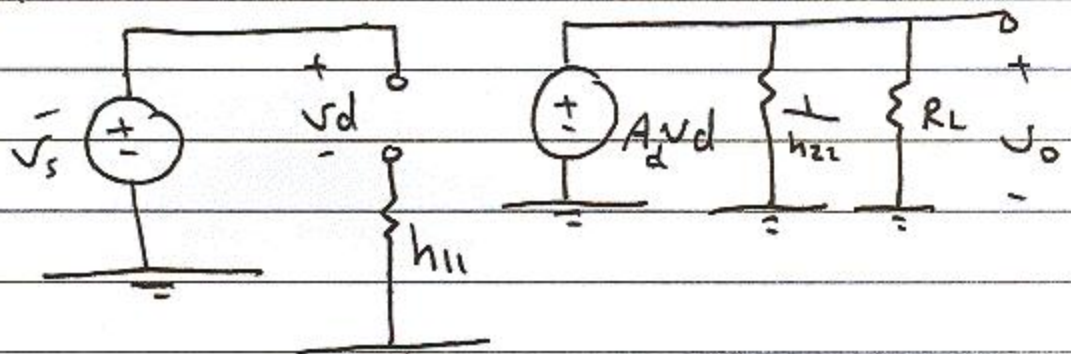


$$v_o = A_d v_d, \quad v_d = v_s$$


$$\therefore A = \frac{v_o}{v_s} = A_d; \quad A_f = \frac{A_d}{1 + A_d \beta} \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$$

8.26



b)

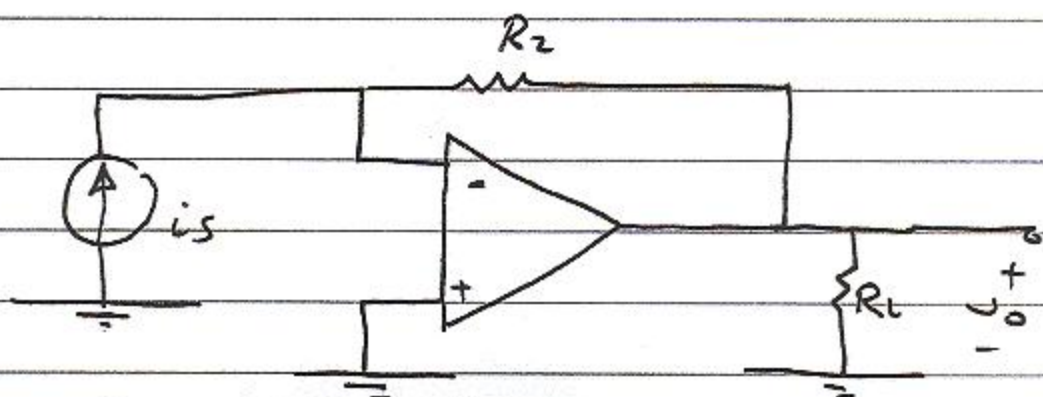

Shunt - Shunt feedback

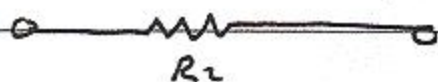

$$y_{11} = \frac{1}{R_2} ; y_{22} = \frac{1}{R_2} ; y_{12} = \beta = -\frac{1}{R_2}$$

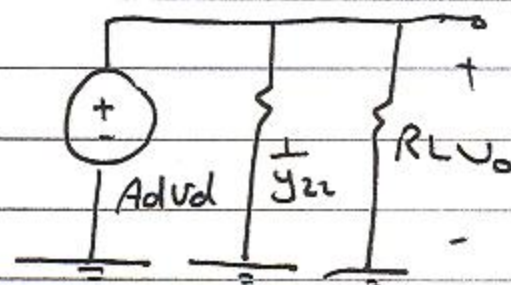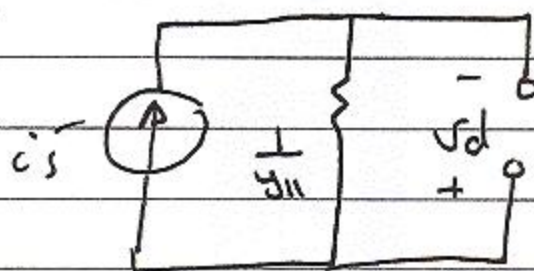To find A

$$v_o = A_d v_d ; v_d = -i_s \cdot \frac{1}{y_{11}} = -i_s R_2$$

$$A = \frac{v_o}{i_s} = -A_d R_2$$

$$A_f = \frac{A}{1 + A\beta} = \frac{-A_d R_2}{1 + (A_d R_2) \left(\frac{1}{R_2} \right)}$$


$$A_f = \frac{-A_d R_2}{1 + A_d}$$

$$A_f \rightarrow -R_2 = \frac{1}{\beta}$$


as $A_d \rightarrow \infty$

8.26

c)

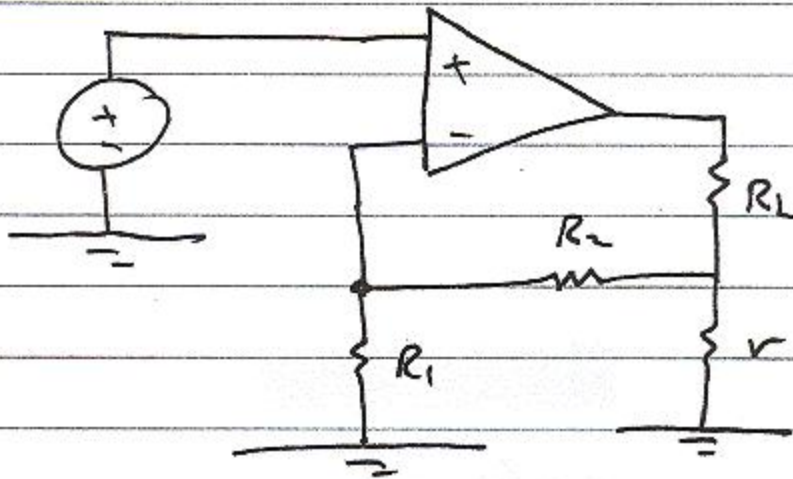


Series - series feedback

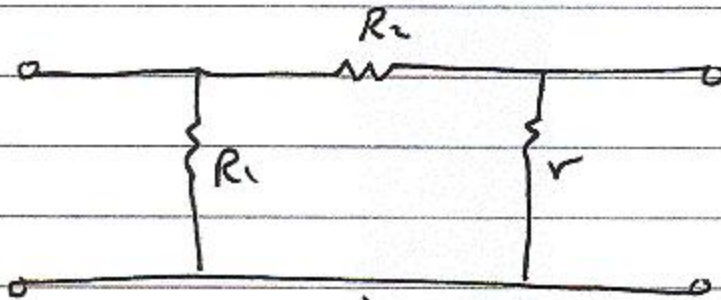

$$Z_{11} = R_1 \parallel (R_2 + r)$$

$$Z_{22} = r \parallel (R_1 + R_2)$$

$$Z_{12} = \beta = \frac{R_1 r}{r + R_1 + R_2}$$

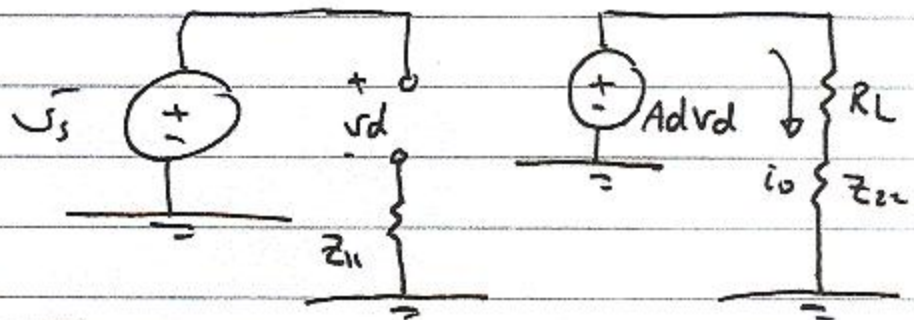To find A:


$$i_o = \frac{A_d v_d}{R_L + Z_{22}} ; v_d = v_s$$

$$A = \frac{v_o}{v_s} = \frac{A_d}{R_L + Z_{22}}$$


$$A_f = \frac{A}{1 + A\beta} = \frac{A_d / (R_L + Z_{22})}{1 + (A_d / (R_L + Z_{22})) \left(\frac{R_1 r}{r + R_1 + R_2} \right)} \approx \frac{r + R_1 + R_2}{R_1 r} \text{ as } A_d \rightarrow \infty$$

8.26

d)

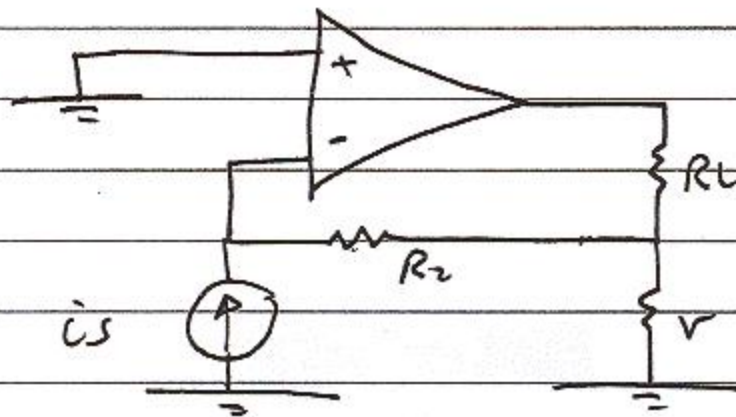


shunt-series feedback

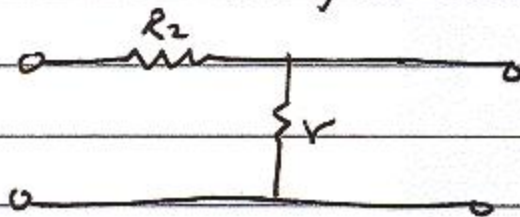

$$g_{11} = \frac{1}{R_2 + r}$$

$$g_{22} = r \parallel R_2$$

$$g_{12} = \beta = \frac{-r}{r + R_2}$$

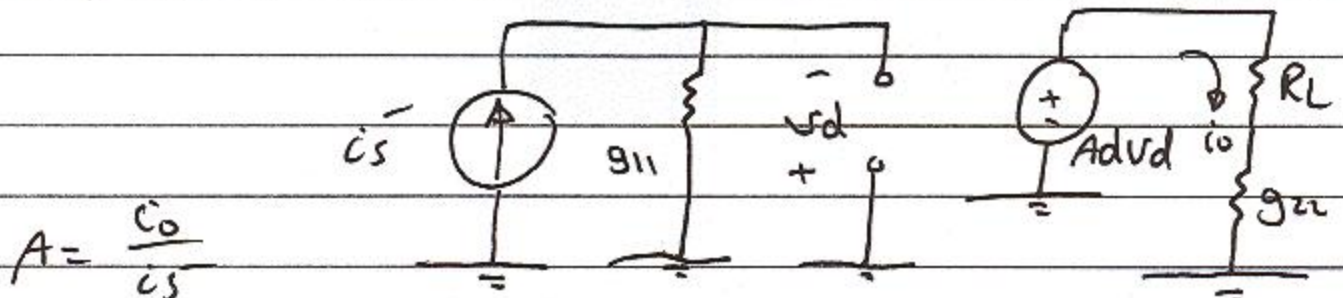To find A 

$$A = \frac{i_o}{i_s}$$

$$i_o = \frac{Ad v_d}{R_L + g_{22}} ; v_d = -i_s \left(\frac{1}{g_{11}} \right)$$

$$A = \frac{-Ad \left(\frac{1}{g_{11}} \right)}{R_L + g_{22}} = -Ad \frac{R_2 + r}{R_L + r \parallel R_2}$$

$$A_f = \frac{A}{1 + AB} = \frac{-Ad \frac{(R_2 + r)}{R_L + r \parallel R_2}}{1 + \frac{Ad (R_2 + r)}{R_L (r \parallel R_2)} \cdot \left(-\frac{r}{r + R_2} \right)}$$

$$A_f \approx -\frac{r + R_2}{r}$$