
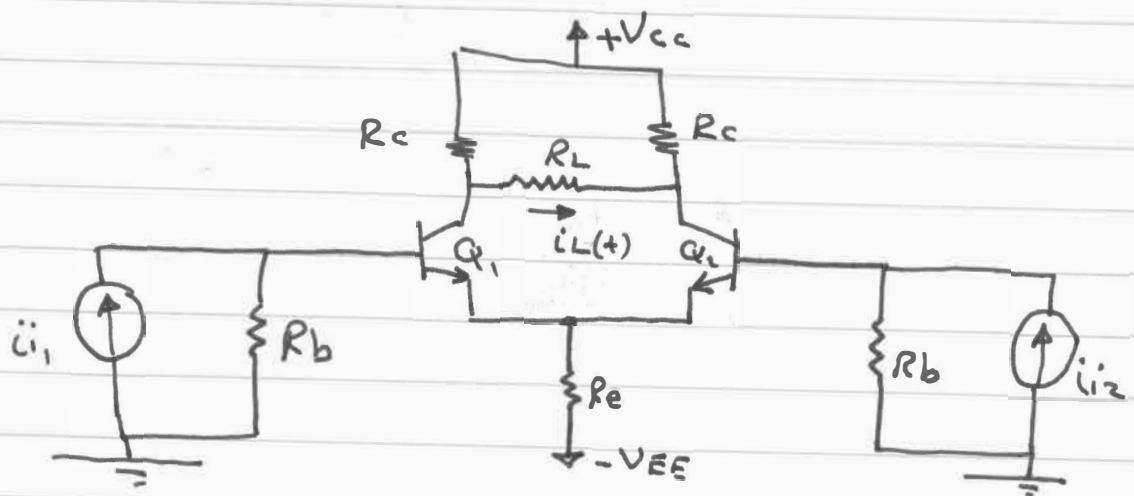


Homework Solution

7.1-4

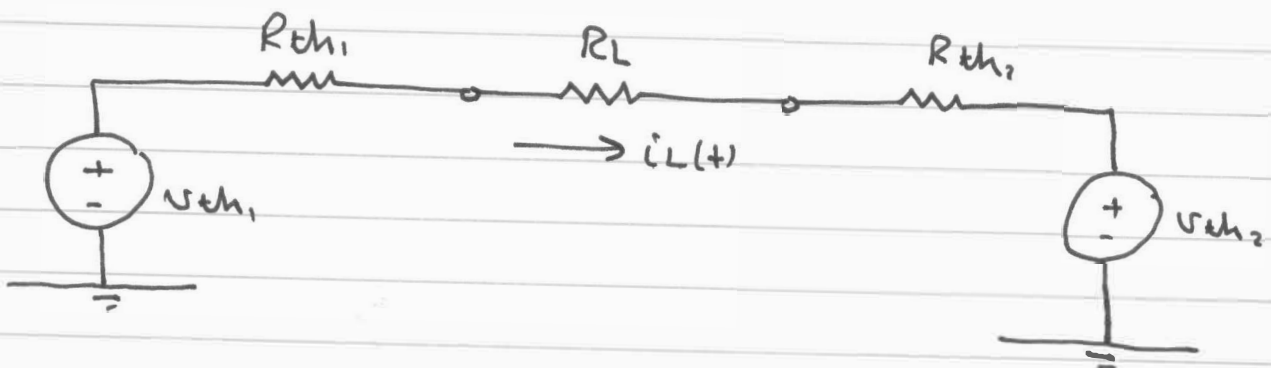

Using Thevenin's equivalent circuits



$$i_L(t) = \frac{V_{th1} - V_{th2}}{R_{th1} + R_{th2} + R_L}$$

$$V_{th1} = \frac{R_c v_d}{2 \left(h_{ib} + \frac{R_b}{h_{fe} + 1} \right)} - \frac{R_c v_c}{2 R_e + h_{ib} + \frac{R_b}{h_{fe} + 1}}$$

$$V_{th2} = \frac{-R_c v_d}{2 \left(h_{ib} + \frac{R_b}{h_{fe} + 1} \right)} - \frac{R_c v_c}{2 R_e + h_{ib} + \frac{R_b}{h_{fe} + 1}}$$

$$R_{th1} = R_{th2} = R_c$$


$$v_d = R_b i_2 - R_b i_1$$

$$V_c = \frac{R_b i_{i2} + R_b i_{i1}}{2}$$

$$\therefore i_L(t) = \frac{R_c R_b (i_{i2} - i_{i1})}{(2R_c + R_L) \left(h_{ib} + \frac{R_b}{h_{fe} + 1} \right)}$$

$$\therefore i_L(t) = K (i_{i2} - i_{i1})$$

7.4-1

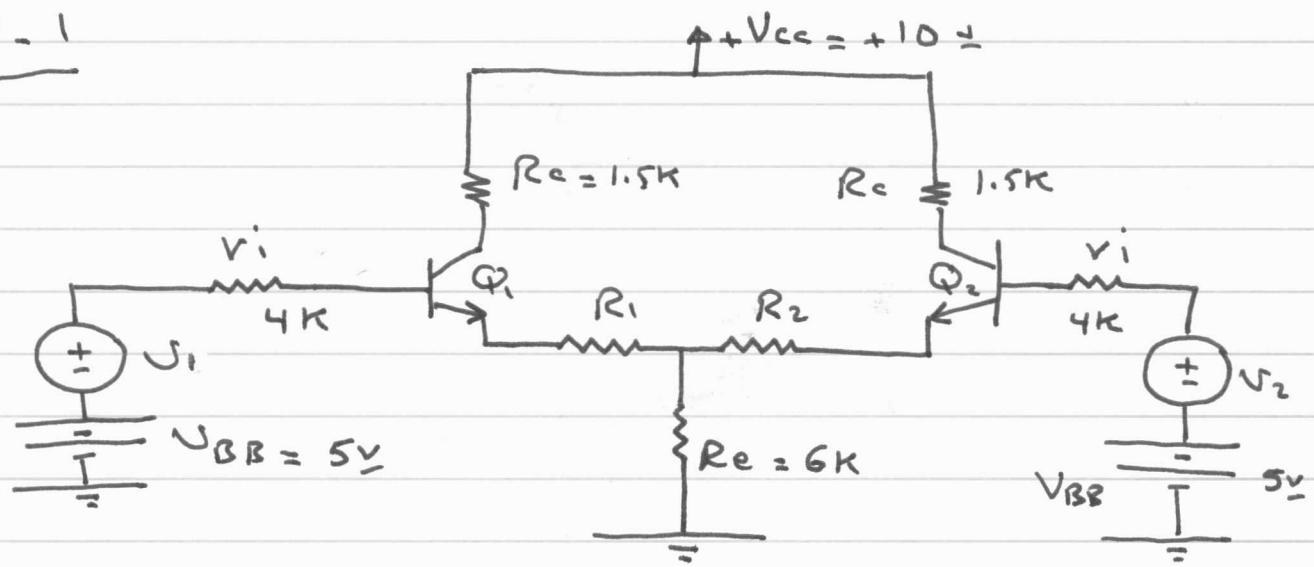

$$h_{fe1} = 100 \quad ; \quad h_{fe2} = 200 \quad ; \quad R_x = R_1 + R_2 = 100\Omega$$

$$V_{BB} + v_i I_{B1} + V_{BE1} + R_1 I_{E1} = V_{BB} + v_i I_{B2} + V_{BE2} + R_2 I_{E2}$$

$$v_i I_{B1} + R_1 I_{E1} = v_i I_{B2} + R_2 I_{E2}$$

To make $I_{E1} = I_{E2}$

$$\frac{v_i}{h_{fe1} + 1} + R_1 = \frac{v_i}{h_{fe2} + 1} + R_2$$

$$\therefore R_2 - R_1 = \frac{v_i}{h_{fe1} + 1} - \frac{v_i}{h_{fe2} + 1}$$

and $R_1 + R_2 = R_x$ given

Solving

$$R_1 = \frac{R_x}{2} - \frac{v_i}{2} \left(\frac{1}{h_{fe1} + 1} - \frac{1}{h_{fe2} + 1} \right)$$

$$R_2 = \frac{R_x}{2} + \frac{v_i}{2} \left(\frac{1}{h_{fe1} + 1} - \frac{1}{h_{fe2} + 1} \right)$$

$$\therefore R_1 = 40 \Omega$$

$$R_2 = 60 \Omega$$


To Find $I_{E1} = I_{E2}$

$$V_{BB} = r_i I_{B1} + V_{BE1} + R_1 I_{E1} + 2R_e I_{E1}$$

$$\therefore I_{E1} = I_{E2} = 0.356 \text{ mA}$$

$$h_{ib1} = h_{ib2} = \frac{V_T}{I_{E1}} = 70 \Omega$$

To Find A_d , A_c , and $CMRR$

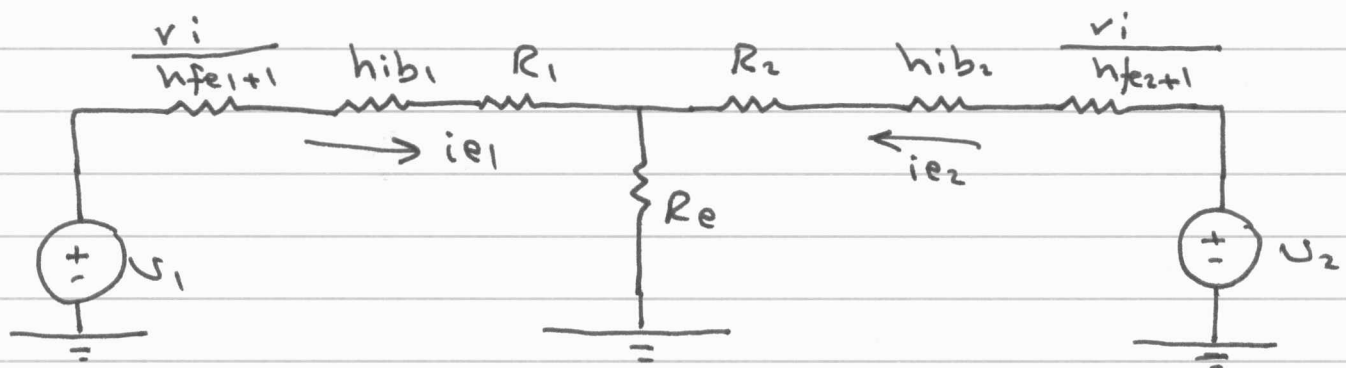

$$1) \text{ To Find } A_d = \left. \frac{V_o}{V_d} \right|_{V_c=0}$$

$$V_o \approx -i_{e2} R_c$$

$$i_{e2} = \frac{V_d}{2 \left(R_2 + h_{ib2} + \frac{V_i}{h_{fe2} + 1} \right)}$$

$$\therefore A_d = -5$$

$$2) \text{ To find } A_c = \frac{v_o}{v_c} \Big|_{v_d=0}$$

$$v_o \approx -i_{e1} R_c$$


$$i_{e1} = \frac{v_c}{2R_e + R_2 + h_{ib1} + \frac{r_i}{h_{fe1} + 1}}$$

$$\therefore A_c = -0.123$$

$$CMRR = \left| \frac{A_d}{A_c} \right|$$

$$CMRR = 40.7$$

7.6-6

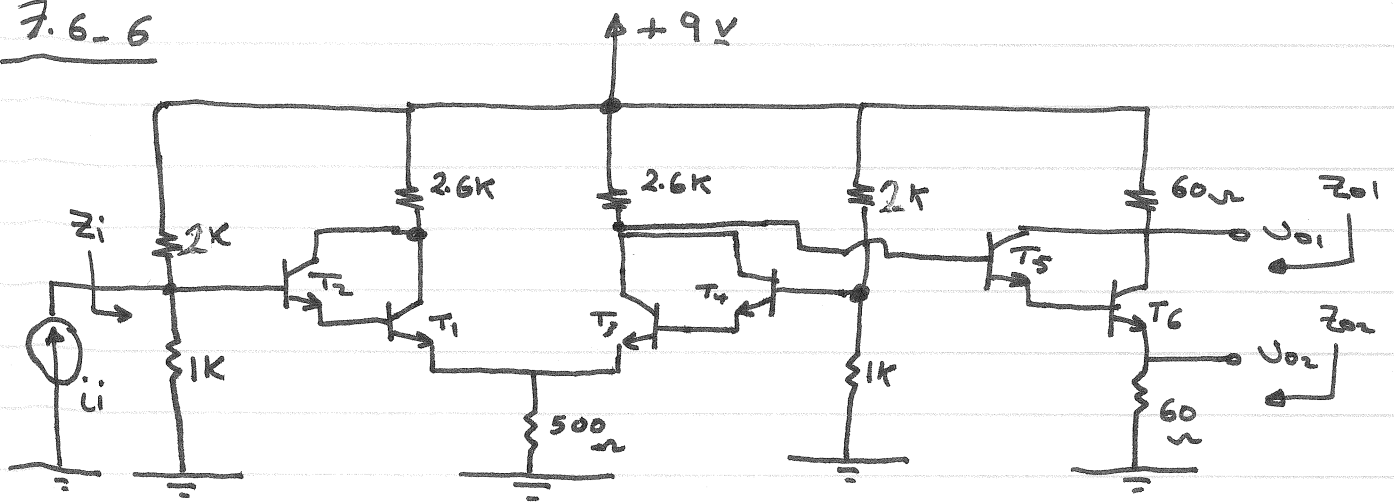

DC Analysis

$$R_{TH} = 1K \parallel 2K = 0.667K$$

$$V_{TH} = \frac{1K}{2K+1K} (9) = 3V$$

$$V_{TH} = R_{TH} I_{B2} + V_{BE2} + V_{BE1} + (0.5K)(2I_{E1})$$

$$I_{E1} = (\beta+1)(\beta+1) I_{B2}$$

$$\therefore I_{E1} = 1.6 \text{ mA}$$

$$I_{E2} \approx 0.016 \text{ mA}$$

$$h_{ie2} = \frac{\beta V_T}{I_{E2}} = 162.5K$$

$$h_{ieD_{1n}} = h_{ieD_{2,n}} = 325K$$



$$9 = 2.6K (I_{C3} + I_{C4} + I_{B5}) + V_{BE5} + V_{BE6} + 60\Omega I_{E6}$$

$$\therefore I_{E6} \approx 56.4 \text{ mA}$$

$$\therefore I_{E5} \approx 0.564 \text{ mA}$$

$$h_{ieD_{5,6}} = 9.22k$$

ac small signal equivalent CKT

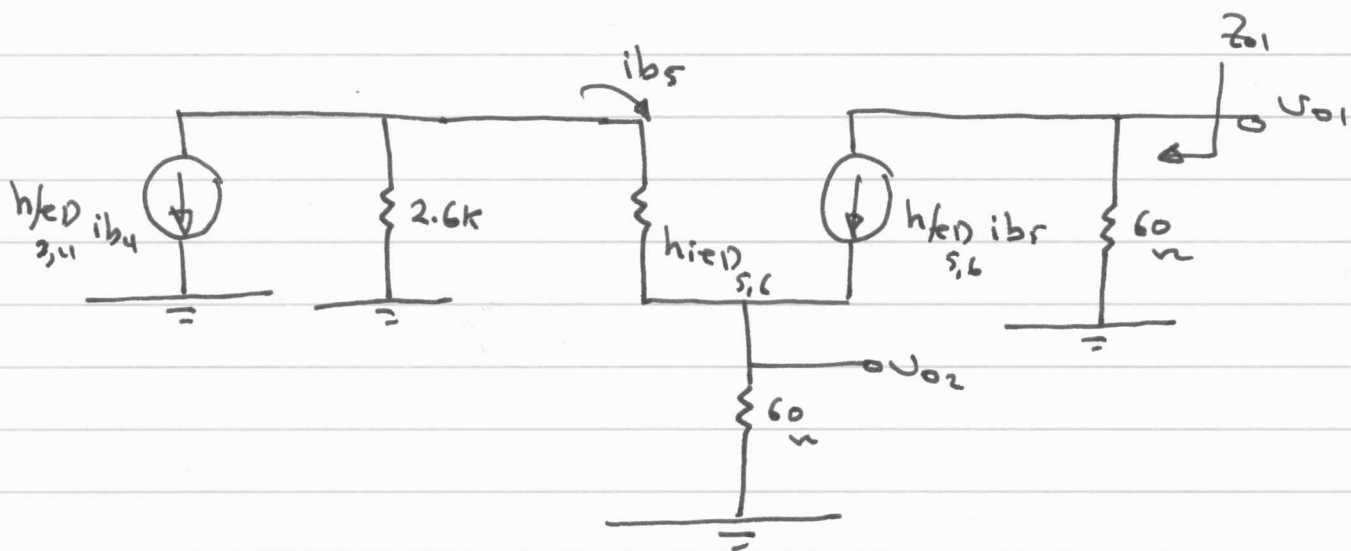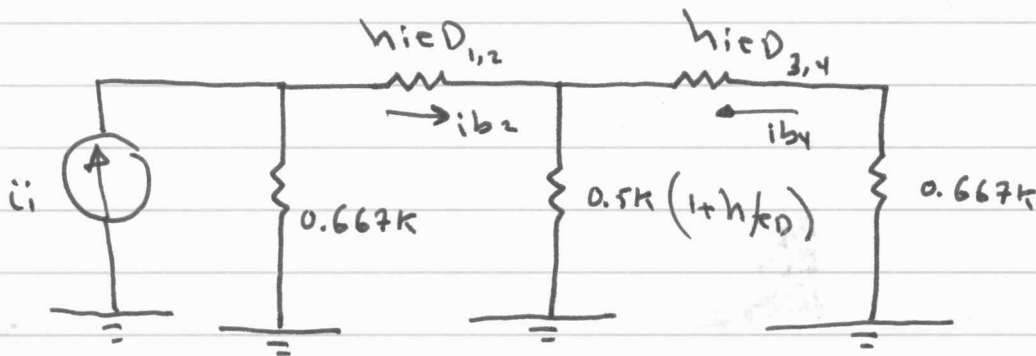

Differential mode Analysis

$$v_{o1} = -h_{feD_{5,6}} i_{b5} (60\Omega)$$

$$i_{b5} = -h_{feD_{3,4}} i_{b4} \frac{2.6k}{2.6k + h_{ieD_{5,6}} + 60\Omega (1+h_{feD_{5,6}})}$$

$$i_{b4} = -i_{b2}$$

$$i_{b2} = i_i \frac{0.667k}{0.667k + h_{ieD_{1,2}} + h_{ieD_{3,4}} + 0.667k}$$

$$\therefore \frac{V_{o1}}{i_i} = -26.1 \times 10^3$$

$$Z_i = 0.667k \parallel \left(h_{ieD_{1,2}} + h_{ieD_{3,4}} + 0.667k \right)$$

$$Z_i \approx 0.667k$$


$$Z_{o1} = 60\Omega$$

$$Z_{o2} = 0.06k \parallel \left(\frac{2.6k + h_{ieD_{5,6}}}{h_{feD_{5,6}}} \right) \approx 1\Omega$$

$$\frac{V_{o2}}{i_i} \approx -26.1 \times 10^3$$

-8-

7.7-2

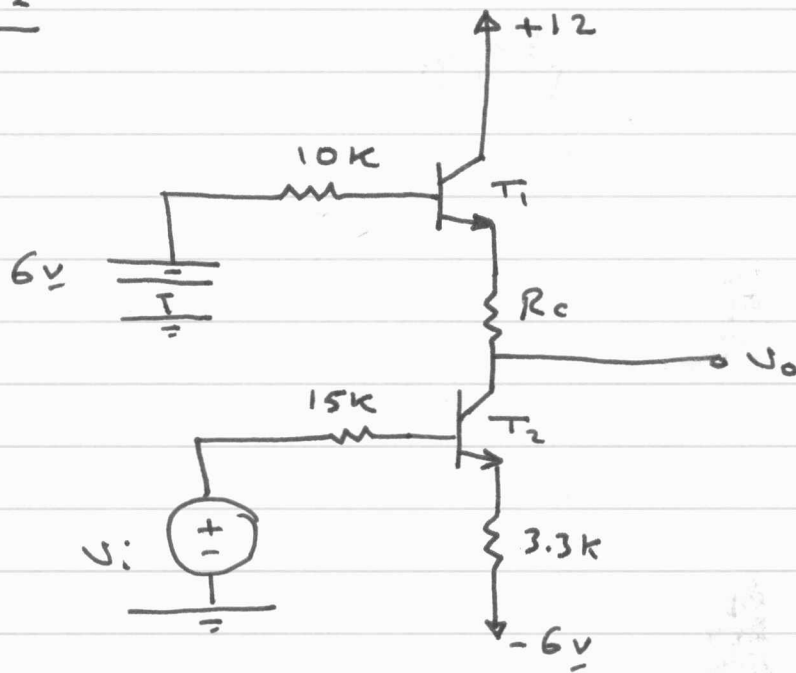

$$(15K) I_{B2} + 0.7 + (3.3K) I_{E2} - 6 = 0$$


$$\therefore I_{E2} = 1.57 \text{ mA}$$

$$6 = (10K) I_{B1} + 0.7 + R_c I_{E1} + 0$$

$$I_{E1} = I_{C2} \approx I_{E2} = 1.57 \text{ mA}$$

$$\therefore R_c = 3.326 K$$

ac small signal equivalent ckt

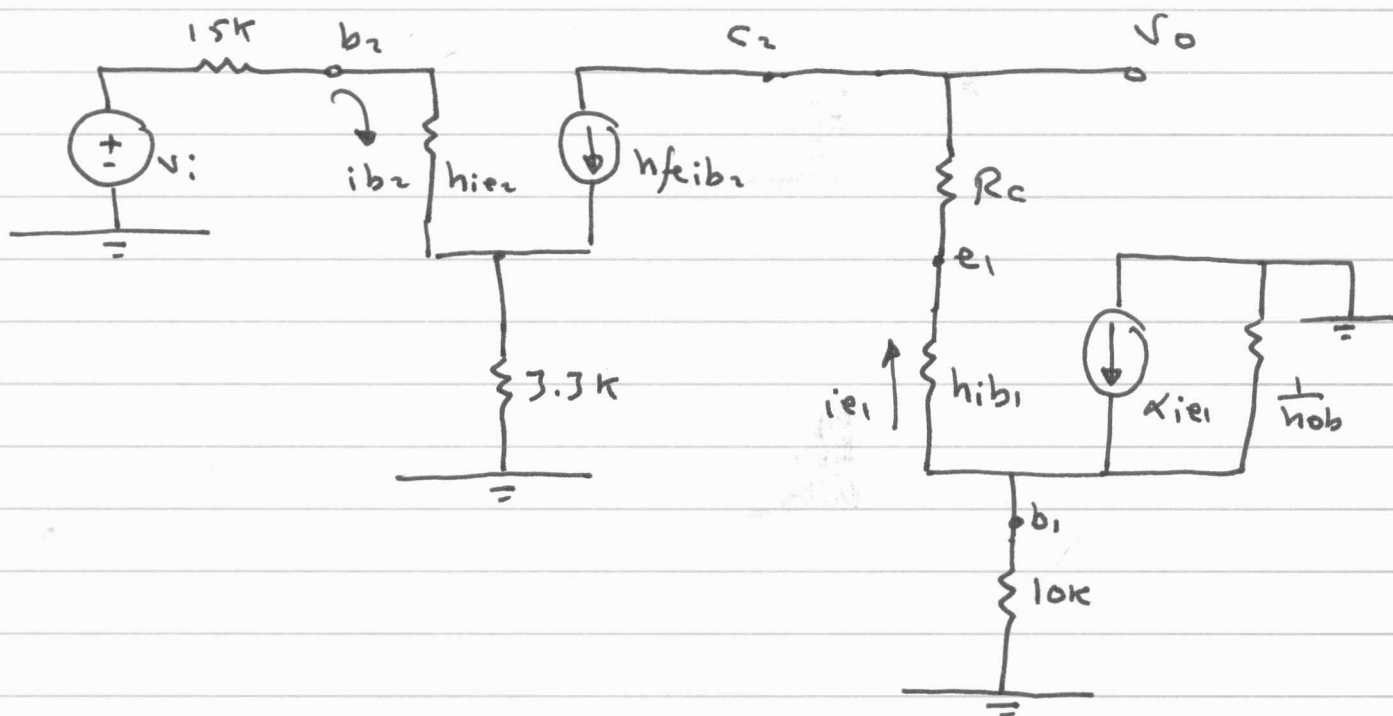

$$V_o = -i_{e1} \left(R_c + h_{ie1} + \frac{10k \parallel \frac{1}{h_{ob}}}{1 + h_{fe}} \right)$$

$$i_{e1} = h_{fe} i_{b2}$$

$$i_{b2} = \frac{V_i}{15k + h_{ie2} + 3.3k(1 + h_{fe})}$$

$$\therefore A_v \approx -0.99$$