

## CH 11: Balanced Three-phase Circuit.

Three sources  
Three-phase  $\equiv 3-\phi$   
single-phase  $\equiv 1-\phi$

### Balanced 3- $\phi$ Voltages:

They are 3 voltage sources that have identical amplitudes and frequency, but are out of phase with each other by exactly  $120^\circ$


sequences of balanced 3- $\phi$  systems

1) Positive sequence "abc sequence"

$$V_a(t) = V_m \cos(\omega t + \theta_v) \quad , \quad \vec{V}_a = V_m \angle \theta_v$$

$$V_b(t) = V_m \cos(\omega t + \theta_v - 120^\circ) \quad , \quad \vec{V}_b = V_m \angle \theta_v - 120^\circ$$

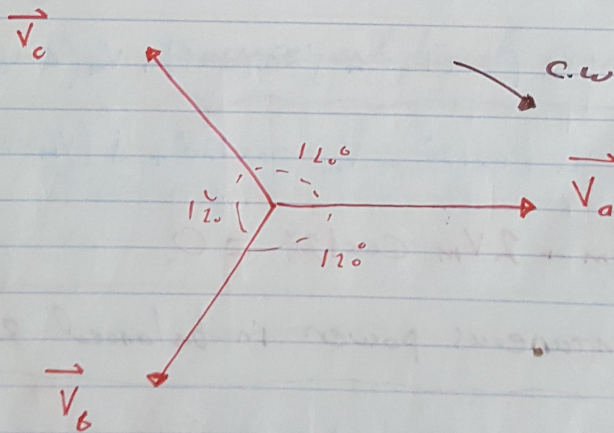
$$V_c(t) = V_m \cos(\omega t + \theta_v + 120^\circ) \quad , \quad \vec{V}_c = V_m \angle \theta_v + 120^\circ$$



2) Negative sequence "acb sequence"



$$\begin{aligned}\vec{V}_a &= V_m \angle 0^\circ \\ \vec{V}_b &= V_m \angle 0^\circ + 120^\circ \\ \vec{V}_c &= V_m \angle 0^\circ - 120^\circ\end{aligned}$$

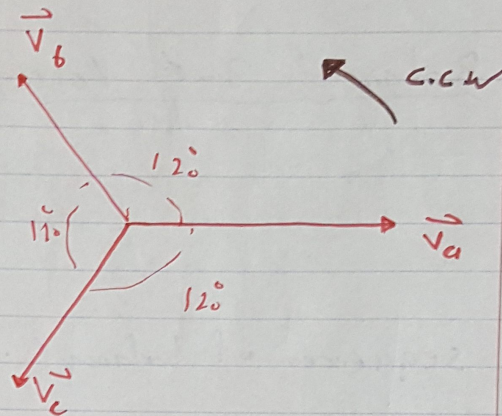

Balanced 3- $\phi$  voltages:

$$\boxed{0^\circ = 0}$$

$$V_a(t) + V_b(t) + V_c(t) \quad \text{t-domain}$$

$$\vec{V}_a + \vec{V}_b + \vec{V}_c \quad \text{phasor-domain}$$




$$= V_m \angle 0^\circ + V_m \angle -120^\circ + V_m \angle 120^\circ$$

$$= V_m + V_m (\cos 120^\circ + j \sin(-120^\circ)) + V_m (\cos 120^\circ + j \sin 120^\circ)$$

$$= V_m + V_m \cos 120^\circ + V_m \cos 120^\circ + j (V_m \sin(-120^\circ) + V_m \sin 120^\circ)$$

$$= V_m + 2V_m \cos 120^\circ = 0$$

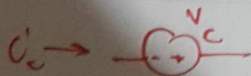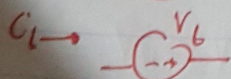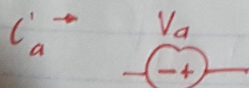Instantaneous power in balanced 3- $\phi$  systems



$$P(t) = P_a(t) + P_b(t) + P_c(t)$$

↑  
Total instantaneous power



$$P_a = V_a(t) i_a(t) \quad , \quad P_b = V_b(t) i_b(t) \quad , \quad P_c = V_c(t) i_c(t)$$

Assume  $\phi$ .

$$V_a(t) = V_m \cos(\omega t + \theta_v) \quad , \quad i_a = I_m \cos(\omega t + \theta_c)$$

$$V_b(t) = V_m \cos(\omega t + \theta_v - \frac{2\pi}{3}) \quad , \quad i_b = I_m \cos(\omega t + \theta_c - \frac{2\pi}{3})$$

$$V_c(t) = V_m \cos(\omega t + \theta_v + \frac{2\pi}{3}) \quad , \quad i_c = I_m \cos(\omega t + \theta_c + \frac{2\pi}{3})$$

$$P(t) = V_a(t) i_a(t) + V_b(t) i_b(t) + V_c(t) i_c(t)$$

$$P(t) = \frac{3}{2} V_m I_m \cos(\theta_v - \theta_c) = \text{Average Power}$$

↑  
3-φ

(No double frequency component)


Instantaneous  
Power

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_c) + P(2\omega t)$$


↑  
1-φ

Source and Load Connections


Source  $\Delta$  on  $\Delta$

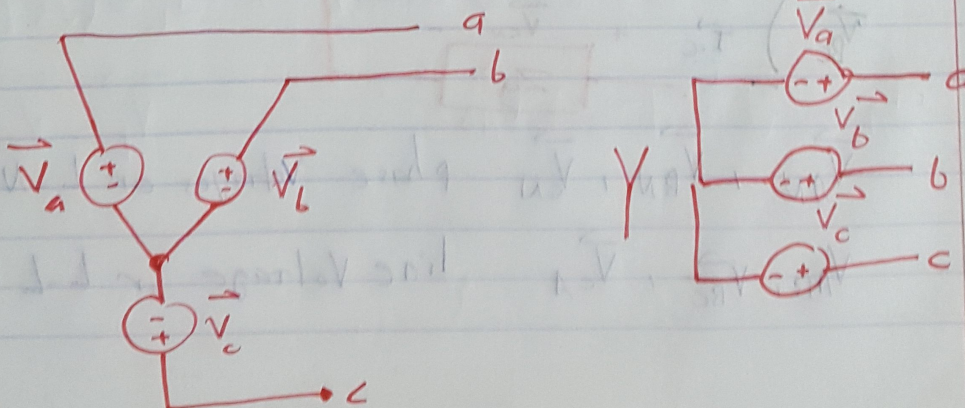




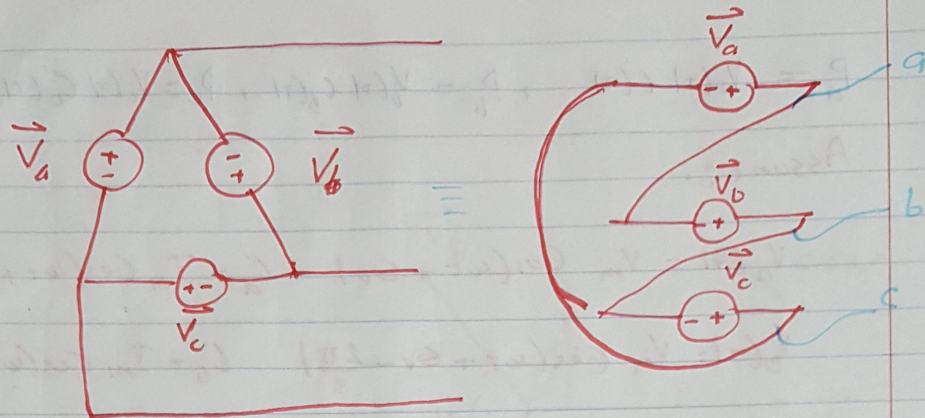


Source

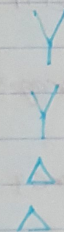

Load

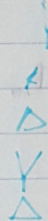

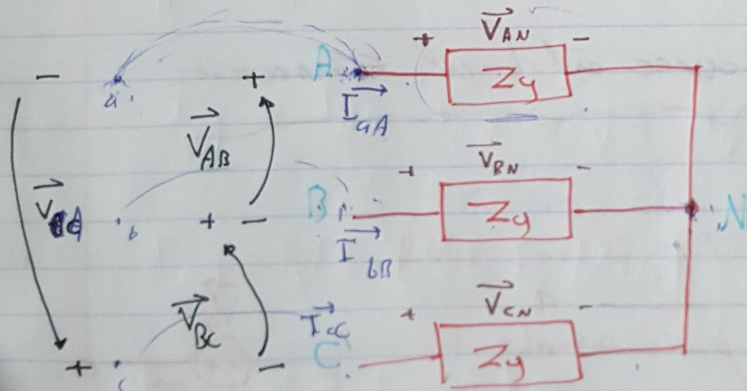line and phase voltages in Y-connected load or source.



in this case  
 $\vec{I}_L = \vec{I}_\phi$

$\vec{V}_{AN}, \vec{V}_{BN}, \vec{V}_{CN}$  phase voltages on L-N voltages,

$\vec{V}_{AB}, \vec{V}_{BC}, \vec{V}_{CA}$  line voltage or L-L voltages



$\vec{I}_{aA}, \vec{I}_{bB}, \vec{I}_{cC}$  line currents.

Assume  $\phi_1$

$$\vec{V}_{AN} = V_\phi \angle \theta_{V\phi}$$

$$\vec{V}_{BN} = V_\phi \angle \theta_{V\phi} - \frac{2\pi}{3}$$

$$\vec{V}_{CN} = V_\phi \angle \theta_{V\phi} + \frac{2\pi}{3}$$

$$\vec{V}_{AB} = \vec{V}_{AN} - \vec{V}_{BN} = V_\phi \angle \theta_{V\phi} - V_\phi \angle \theta_{V\phi} - \frac{2\pi}{3}$$

$$\vec{V}_{AB} = (V_\phi \cos(\theta_{V\phi}) + j V_\phi \sin(\theta_{V\phi})) - (V_\phi \cos(\theta_{V\phi} - \frac{2\pi}{3}) + j V_\phi \sin(\theta_{V\phi} - \frac{2\pi}{3}))$$


$$\vec{V}_{AB} = \sqrt{3} V_\phi \angle \theta_{V\phi} + 30^\circ$$

$$\vec{V}_{AB} = (\sqrt{3} \angle 30^\circ) \vec{V}_{AN}$$

$$\vec{V}_{LL} = (\sqrt{3} \angle 30^\circ) \vec{V}_{L-N}$$



$\Delta$  - connected Load on source

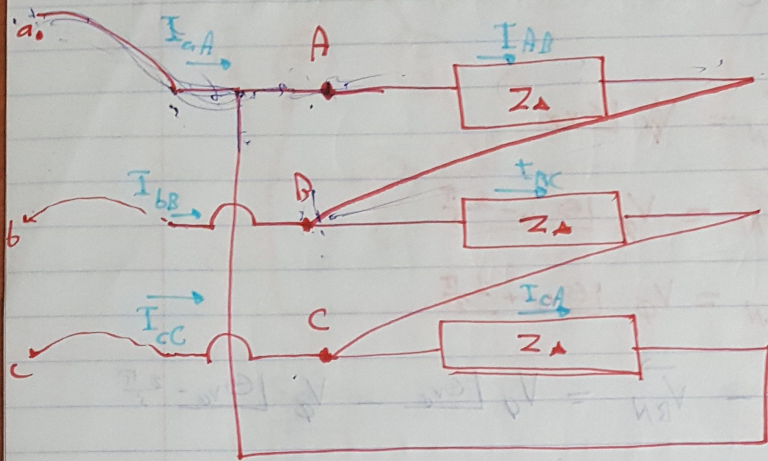

$I_{AB}, I_{BC}, I_{CA} \Rightarrow$  phase current

$I_{aA}, I_{bB}, I_{cC} \Rightarrow$  line current

$V_{AB}, V_{BC}, V_{CA}$  Phase voltages

$$\vec{I}_{AB} = I_\phi \angle \theta_\phi, \quad \vec{I}_{BC} = I_\phi \angle \theta_\phi - \frac{2\pi}{3}, \quad \vec{I}_{CA} = I_\phi \angle \theta_\phi + \frac{2\pi}{3}$$

$$\vec{I}_{aA} = \vec{I}_{AB} - \vec{I}_{CA} = \sqrt{3} I_\phi \angle \theta_\phi - 30^\circ$$

$$I_{aA} = (\sqrt{3} \angle -30^\circ) (I_\phi \angle \theta_\phi) \quad , \quad \vec{I}_L = (\sqrt{3} \angle -30^\circ) \vec{I}_\phi$$

$$\vec{I}_{aA} = (\sqrt{3} \angle -30^\circ) \vec{I}_{AB} \quad \vec{V}_L = \vec{V}_\phi$$



Y-connected load or source

$$\vec{V}_L = (\sqrt{3} \angle 30^\circ) \vec{V}_\phi$$

$$\vec{I}_L = \vec{I}_\phi$$

Δ-Connected load or source


$$\vec{V}_L = \vec{V}_\phi$$

$$\vec{I}_L = (\sqrt{3} \angle -30^\circ) \vec{I}_\phi$$

## Y-Y Analysis

Source Load

winding impedance

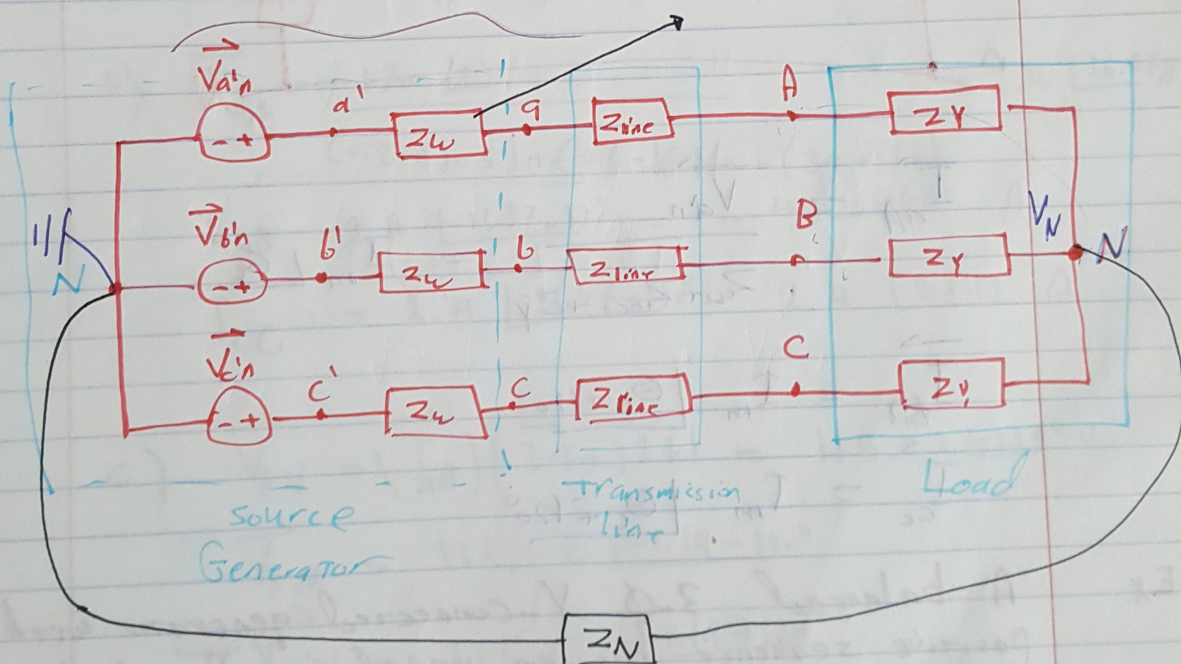

KCL at Node N

$$\frac{\vec{V}_N - \vec{V}_{a'n}}{Z_\phi} + \frac{\vec{V}_N - \vec{V}_{b'n}}{Z_\phi} + \frac{\vec{V}_N - \vec{V}_{c'n}}{Z_\phi} + \frac{\vec{V}_N}{Z_N} = 0$$




$$\frac{3}{Z_0} \vec{V}_N - \frac{1}{Z_0} \left( \vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} \right) + \frac{V_N}{Z_N} = 0$$

$$\left( \frac{3}{Z_0} + \frac{1}{Z_N} \right) \vec{V}_N = 0$$

$$\boxed{\vec{V}_N = 0} \Rightarrow \boxed{I_N = 0}$$

1- $\phi$  equivalent Circuit

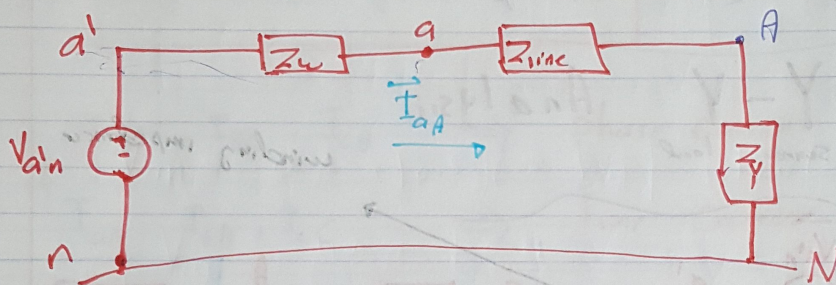

$$\vec{I}_{aA} = \frac{\vec{V}_{an}}{Z_w + Z_{line} + Z_Y} = I_m \angle \theta_c$$


$$\vec{I}_{bB} = I_m \angle \theta_c + 120^\circ$$

$$\vec{I}_{cC} = I_m \angle \theta_c + 120^\circ$$

Ex A balanced 3- $\phi$  Y-connected generator with positive sequence has an impedance of  $0.2 + j0.5 \Omega/\phi$  and an internal voltage  $120V/\phi$ . The generator feeds a balanced 3- $\phi$  Y-connected Load having an impedance of  $39 + j28 \Omega/\phi$ . The impedance of TLI is  $0.8 + j1.5 \Omega/\phi$



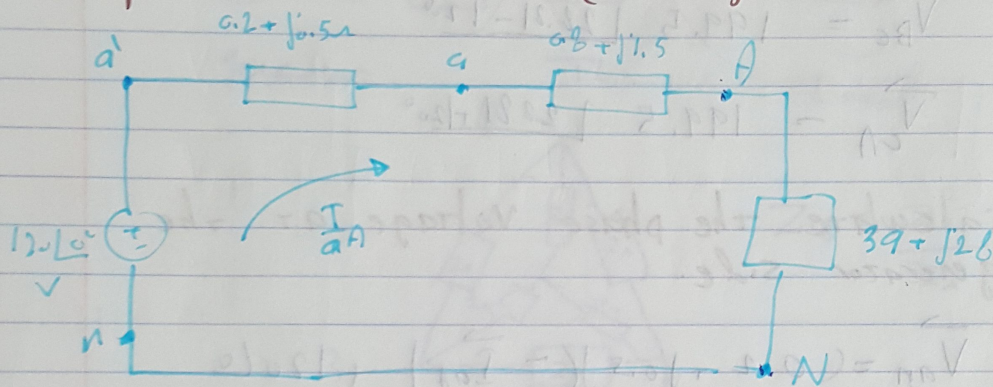- Draw the 1- $\phi$  equivalent circuit
- Calculate the line current
- Calculate the phase voltage at the load side.
- " " " " " "



$$b) \vec{I}_{aA} = \frac{120 \angle 0^\circ}{(0.2 + j0.5) + (0.6 + j1.5) + (39 + j26)} = 2.4 \angle -36.87^\circ \text{ A}$$

$$\vec{I}_{bB} = 2.4 \angle -36.87^\circ - 120^\circ = 2.4 \angle -156.87^\circ \text{ A}$$

$$\vec{I}_{cC} = 2.4 \angle -36.87^\circ + 120^\circ = 2.4 \angle 83.13^\circ \text{ A}$$

$$c) \vec{V}_{AN} = (\vec{I}_{aA})(39 + j26) = 115.22 \angle -1.19^\circ \text{ V}$$

$$\vec{V}_{bN} = 115.22 \angle -1.19^\circ - 120^\circ$$

$$\vec{V}_{cN} = 115.22 \angle -1.19^\circ + 120^\circ$$





$$\begin{aligned}
 \vec{V}_{AB} &= \sqrt{3} \angle 120^\circ (\vec{V}_{AN}) \\
 \vec{V}_{AB} &= (\sqrt{3} \angle 30^\circ) (115.22 \angle -1.19^\circ \text{ V}) \\
 &= 199.5 \angle 28.81^\circ \\
 \vec{V}_{BC} &= 199.5 \angle 28.81 - 120^\circ \\
 \vec{V}_{CA} &= 199.5 \angle 28.81 + 120^\circ
 \end{aligned}$$

E Calculate the phase voltage at the generator side.

$$\begin{aligned}
 \vec{V}_{an} &= (0.2 + j0.5)(-\vec{I}_{aA}) + 120 \angle 0^\circ \\
 \vec{V}_{an} &= 118.9 \angle -0.32^\circ \\
 \vec{V}_{bn} &= 118.9 \angle -0.32 - 120^\circ \\
 \vec{V}_{cn} &= 118.9 \angle -0.32 + 120^\circ
 \end{aligned}$$




$Y \rightarrow \Delta$

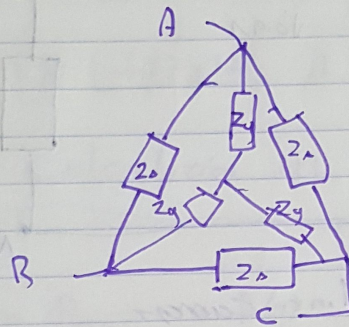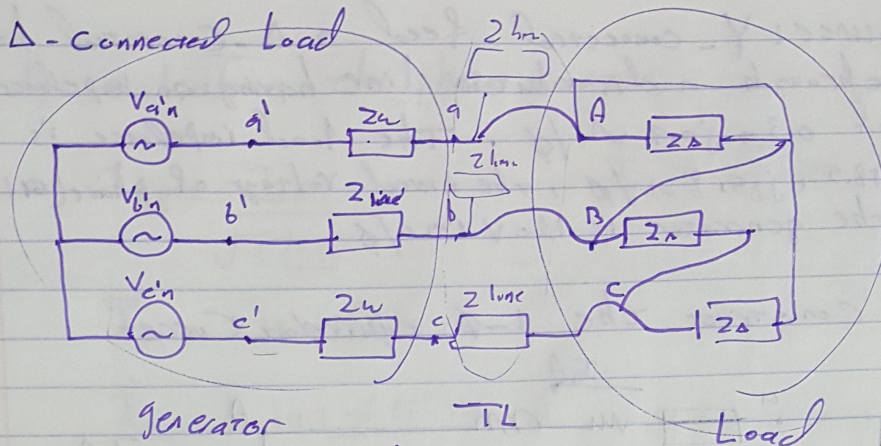

$$Z_Y = \frac{Z_{\Delta}^2}{3Z_{\Delta}} = \frac{Z_{\Delta}}{3}$$

1- $\phi$  equivalent circuit

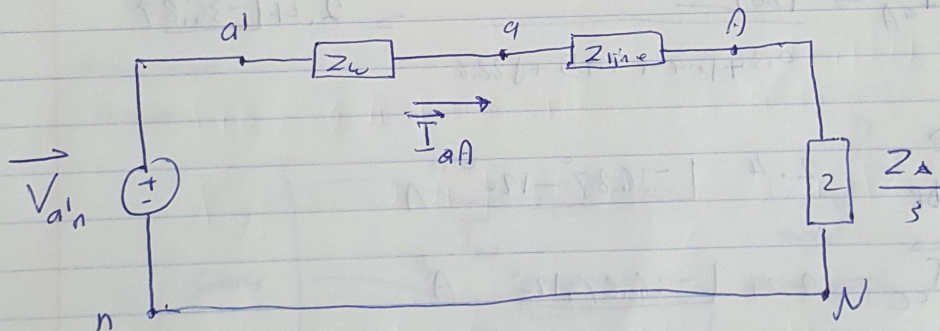

$$\vec{I}_{a'n} = \frac{\vec{V}_{a'n}}{Z_w + Z_{line} + \frac{2Z_{\Delta}}{3}}$$

$$\vec{I}_L = (\sqrt{3} \angle -30^\circ) \vec{I}_a$$


$$\vec{V}_L = \vec{V}_{\phi}$$



positive sequence.

Source:  $Y$ -connected feed a  $\Delta$ -connected load through a distribution line having an impedance of  $0.3 + j0.9 \Omega/\phi$ . The load impedance is  $118.5 + j85.8 \Omega/\phi$ , the internal voltage of phase (a) of the generator is  $120 \text{ V rms}/\phi$

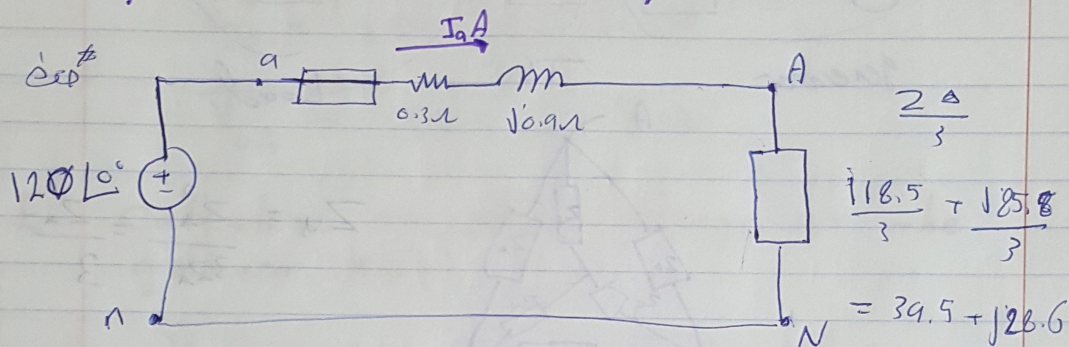a) Construct the 1- $\phi$  equivalent circuit



b) Calculate the line current

$$\vec{I}_{aA} = \frac{120 \angle 0^\circ}{0.3 + j0.9 + 39.5 + j28.6} = 2.4 \angle -36.87^\circ$$

$$\vec{I}_{bB} = 2.4 \angle -36.87^\circ - 120^\circ \text{ A}$$

$$\vec{I}_{cC} = 2.4 \angle -36.87^\circ + 120^\circ \text{ A}$$

Here  $\otimes$  c) Calculate the phase voltages at the load sides.

$$\vec{V}_N = \left( \frac{Z_\Delta}{3} \right) (\vec{I}_{aA}) = 114.04 \angle -0.96^\circ$$

$$\vec{V}_{AB} = \left( \sqrt{3} \angle 13^\circ \right) \vec{V}_N = 202.72 \angle 29.04^\circ \text{ V}$$

$$\vec{V}_{BC} = 202.72 \angle 29.04^\circ - 120^\circ$$

$$\vec{V}_{CA} = 202.72 \angle 29.04^\circ + 120^\circ$$

note  $\Delta$  is  
a three phase  
line so  
line to  
line  
 $\boxed{AB}$



d) calculate the phase current.

$$\vec{I}_{AB} = \frac{I_{aA}}{\sqrt{3} \angle -30^\circ}$$

$$\vec{I}_L = \sqrt{3} \angle -30^\circ \vec{I}_\phi$$

$$\vec{I}_{AB} = 1.39 \angle -6.87^\circ \text{ A}$$


$$\vec{I}_{BC} = 1.39 \angle -6.87^\circ - 120^\circ \text{ A}$$

$$\vec{I}_{CA} = 1.39 \angle -6.87^\circ + 120^\circ \text{ A}$$

power calculation in 3- $\phi$  circuit

$$P_{3-\phi}(t) = P_{avg} \quad , \quad P(t) = P_{avg} + p(2\omega t)$$

↑  
INSTANTANEOUS  
POWERS

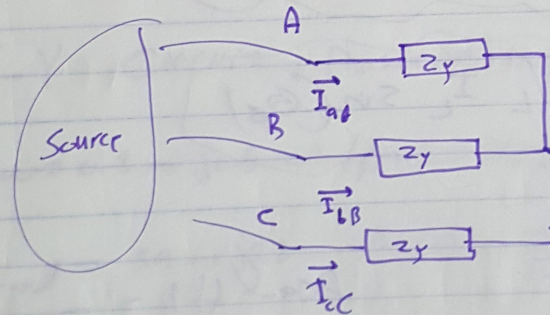

$$P_T = 3 P_\phi$$

↓  
Total average power      Power of each phase

$$P_\phi = V_\phi I_\phi \cos(\theta_\phi)$$

↑  
Power factor angle

$$P_a = V_{AN} \cos(\theta_{V_{AN}} - \theta_{I_{aA}})$$

$$P_b = V_{BN} I_{bB} \cos(\theta_{V_{BN}} - \theta_{I_{bB}})$$

$$P_c = V_{CN} I_{cC} \cos(\theta_{V_{CN}} - \theta_{I_{cC}})$$



$$V_{AN} = V_{BN} = V_{CN} = V_{\phi}$$

$$I_{aA} = I_{bB} = I_{cC} = I_{\phi}$$

$$\theta_{V_{AN}} - \theta_{I_{aA}} = \theta_{V_{BN}} - \theta_{I_{bB}} = \theta_{V_{CN}} - \theta_{I_{cC}} = \theta_{\phi}$$

$$P_a = P_b = P_c = P_{\phi}$$

$$P_T = 3 V_{\phi} I_{\phi} \cos(\theta_{\phi})$$

$$V_L = \sqrt{3} V_{\phi}$$

$$I_L = I_{\phi}$$

$$P_T = 3 \left( \frac{V_L}{\sqrt{3}} \right) (I_L) \cos(\theta_{\phi})$$

$$P_T = \sqrt{3} V_L I_L \cos(\theta_{\phi})$$

$$Q_T = \sqrt{3} V_L I_L \sin(\theta_{\phi})$$

Ex  $P = \frac{3}{2} VI \cos \phi$

power (1) - -

$P = \frac{\sqrt{3}}{2} VI \cos \phi$

power ( $\frac{1}{2}$ ) -






$$\vec{S} = P_T + jQ_T$$

$$\vec{S} = \sqrt{3} V_L I_L \angle \theta_\phi$$

$$\theta_{V_\phi} - \theta_{I_\phi}$$

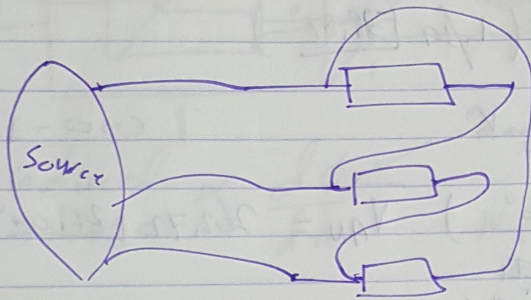

$$P_T = 3 V_\phi I_\phi \cos(\theta_\phi)$$

$$V_L = V_\phi \quad I_L = \sqrt{3} I_\phi$$

$$P_T = 3 V_L \frac{I_L}{\sqrt{3}} \cos(\theta_\phi) = \sqrt{3} V_L I_L \cos(\theta_\phi)$$


Ex

Y-Y Circuit, positive sequence generator,  $Z_w$

$$Z_w = 0.2 + j0.5 \Omega/\phi \quad V_{a'n} = 120 \text{ V}/\phi$$

$$Z_{Load} = 39 + j26 \Omega/\phi, \quad Z_{line} = 0.6 + j1.5 \Omega/\phi$$

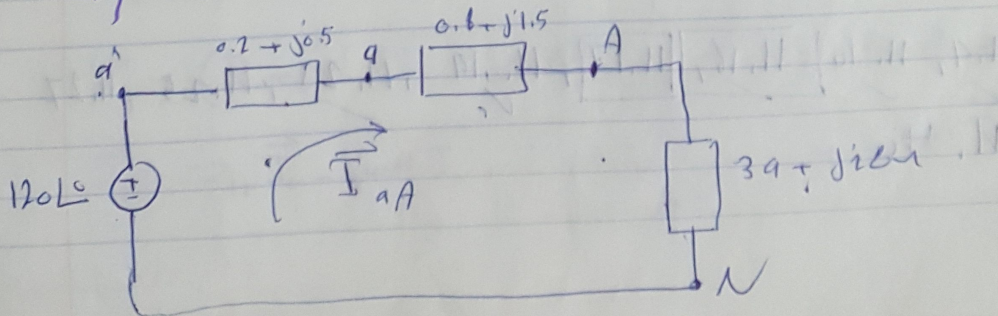a) calculate the total power delivered to the load.





$$e^{-j\omega t}$$

$$\vec{I}_{9A} = \frac{120 \angle 0^\circ}{40 + j30} = \frac{2.4}{1 \angle -6.87^\circ} \text{ A}$$

$$\alpha \quad \vec{I}_L = 1.39$$

$$\vec{V}_{AN} = (39 + j28) (1.39 \angle -6.87^\circ)$$

$$\vec{V}_{AN} = 115.11 \angle -1.19^\circ \text{ V} \quad \cos 0 + j \sin 0$$

$$\vec{V}_L = (\sqrt{3} \angle 30^\circ) \vec{V}_{AN} = 202.72 \angle 29.04^\circ \text{ V}$$

$$P_T = \sqrt{3} (1.39) (202.72) \cos(-1.19^\circ - 6.87^\circ)$$

$$P_T = 672.98 \text{ W}$$

b) Calculate the total reactive and complex power delivered to the load

$$Q_T = \sqrt{3} (1.39) (202.72) \sin(-1.19^\circ + 6.87^\circ)$$

$$S_T = P_T + jQ_T = 162$$

c) Calculate the total avg power lost in the TL


$$P_{\text{line}} = 3 I_{9A}^2 (0.2) = (3)(2.4)^2 (0.8) = 13.824 \text{ W}$$

Problems  
resub.

11.9, 11.10, 11.16, 11.17, 11.19, 11.23, 11.25, 11.27  
11.40.




# Transformer

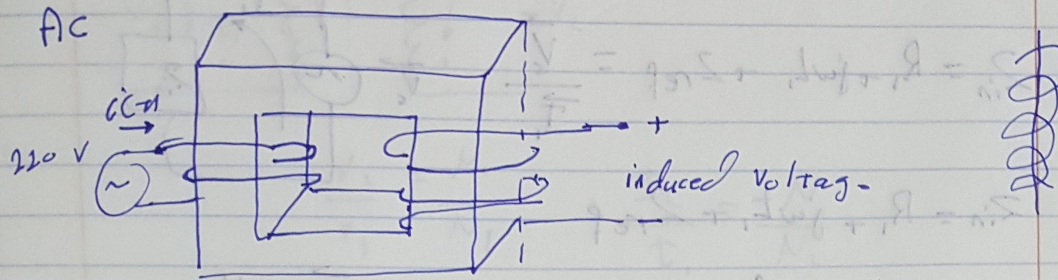

induced voltage  $\propto \frac{d\phi}{dt} \cdot N_2$  "magnetic flux"

$V_s \propto \frac{d\phi}{dt} \cdot N_1$

## Linear Transformer "Real Transformer"

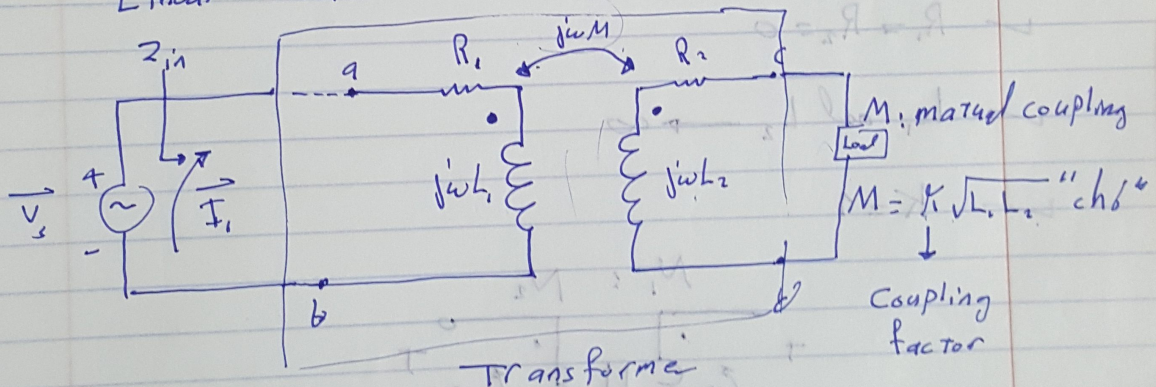

KVL in loop 1

$$\vec{V}_s = (R_1 + j\omega L_1) \vec{I}_1 - j\omega M \vec{I}_2$$

$$\vec{V}_s = Z_{11} \vec{I}_1 - j\omega M \vec{I}_2$$

KVL in loop 2:


$$0 = (Z_L + R_2 + j\omega L_2) \vec{I}_2 - j\omega M \vec{I}_1$$

$$0 = Z_{22} \vec{I}_2 - j\omega M \vec{I}_1$$


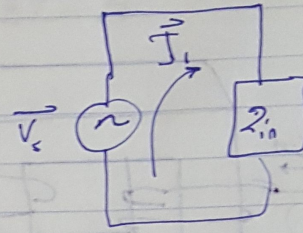
## Reflected impedance

$$Z_{in} = R_1 + j\omega L_1 + Z_{ref} = \frac{\vec{V}_s}{\vec{I}_1}$$



$$Z_{in} = R_1 + j\omega L_1 + Z_{ref}$$

$$Z_{ref} = \left( \frac{\omega M}{|Z_{22}|} \right)^2 Z_{22}^*$$

$$\vec{I}_1 = \frac{V_s}{Z_{in}}$$


$$|Z_{22}| = |R_2 + j\omega L_2 + Z_L|$$

## Ideal Transformer

$$\checkmark R_1 = R_2 = 0$$

$$\checkmark L_1 \text{ and } L_2 \rightarrow \infty$$


$$\checkmark K = 1$$

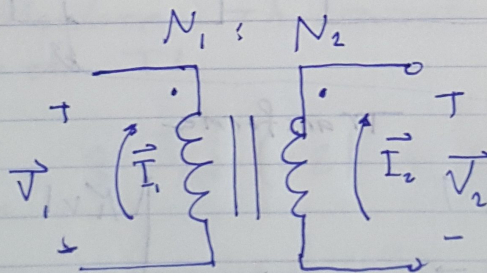

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}, \quad \frac{I_1}{I_2} = \frac{N_1}{N_2}, \quad \frac{N_2}{N_1} = a$$

Transformer  
Transition



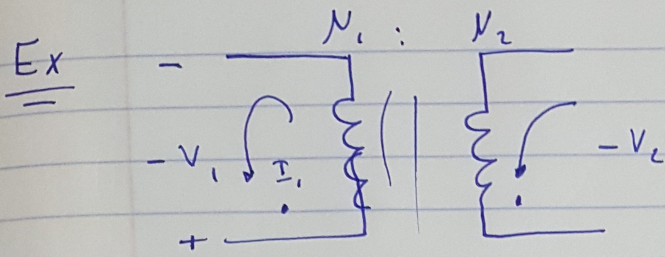

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}, \quad \frac{I_2}{I_1} = -\frac{N_1}{N_2}$$

$$Z_{ref} = \frac{1}{a^2} Z_L$$

$$a = \frac{N_2}{N_1}$$

Ex