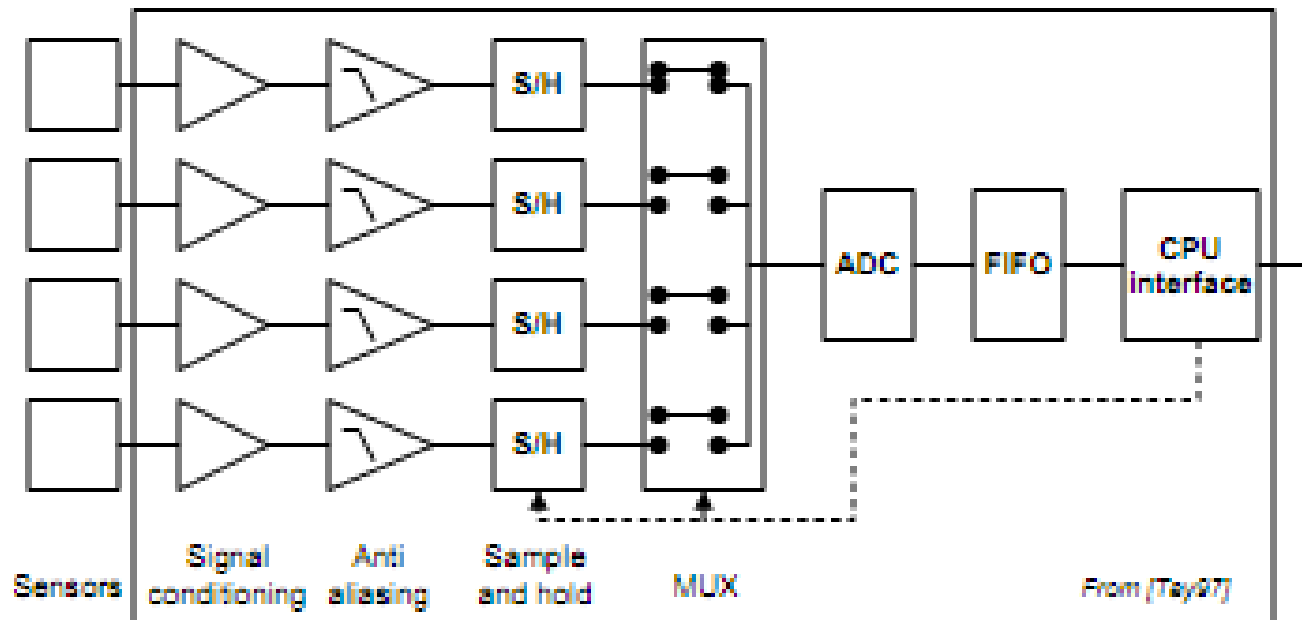


Data Acquisition I

- ▶ Architecture of DAQ systems
- ▶ Signal conditioning
- ▶ Aliasing

Architecture of data acquisition systems





Signal conditioning

- ▶ Instrumentation amplifiers
- ▶ Filters
- ▶ Integrators/differentiators

Instrumentation amplifiers

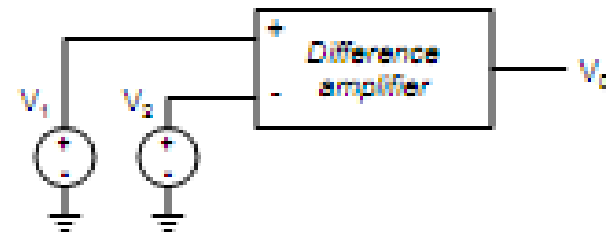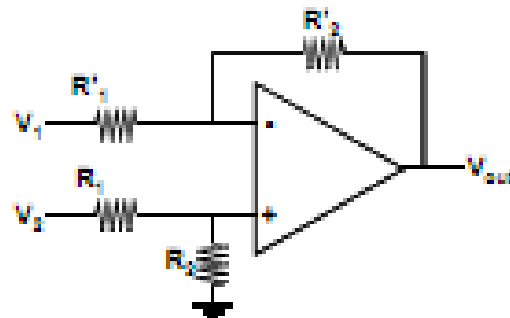
- Consider the difference amplifier we saw in the previous lecture



- We define COMMON-MODE and DIFFERENCE-MODE voltage as

$$V_{CM} = \frac{V_2 + V_1}{2}$$

$$V_D = V_2 - V_1$$

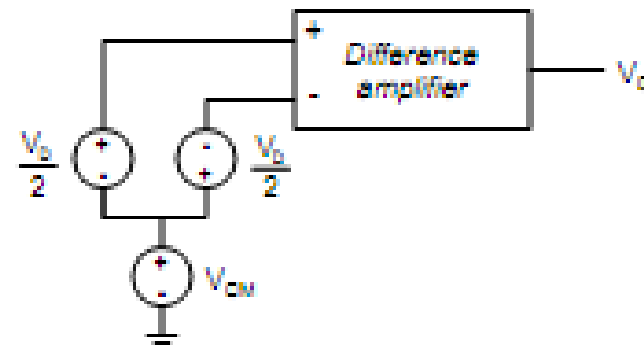

Instrumentation amplifiers

- As a result of a mismatch in the resistors ($R'_k \neq R_k$), the differential inputs may not have the same gain

$$\begin{aligned} V_o &= G(V_2 - V_1) \stackrel{R'_k \neq R_k}{=} G_2 V_2 - G_1 V_1 = G_2 \left(-\frac{V_D}{2} + V_{CM} \right) - G_1 \left(\frac{V_D}{2} + V_{CM} \right) = \\ &= -V_D \left(\frac{G_2 + G_1}{2} \right) + V_{CM} (G_2 - G_1) = -V_D G_D + V_{CM} G_{CM} \end{aligned}$$


- We define **COMMON-MODE REJECTION RATIO** as

$$CMRR = 20 \log_{10} \left(\frac{G_D}{G_{CM}} \right) = 20 \log_{10} \left(\frac{G_2 + G_1}{2(G_2 - G_1)} \right)$$

- CMRR is, in practice, a function of frequency, and its magnitude decreases with increasing frequency
- An additional shortcoming of the difference amplifier is its **LOW INPUT IMPEDANCE**


Instrumentation amplifiers

- ▶ The term INSTRUMENTATION AMPLIFIER is used to denote a difference amplifier with
 - High gain (INA2126)
 - Single-ended output
 - High input impedance
 - High CMRR
- ▶ High input impedance may be achieved by buffering the differential inputs
 - This solution, however, requires high CMRR both in the followers and in the final op-amp
 - Otherwise, since the input buffers have unity gain, all the CM rejection must come in the output op-amp, requiring precise resistor matching

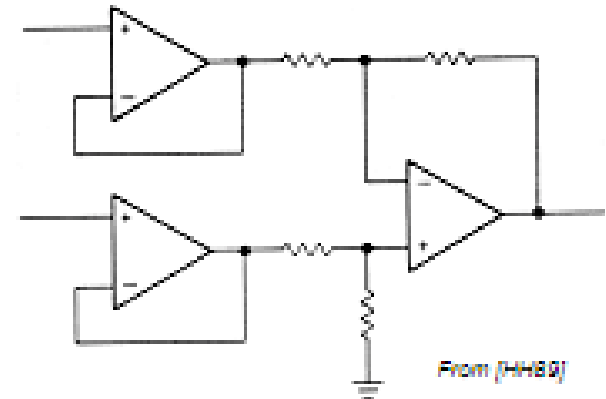


Common mode rejection ratio

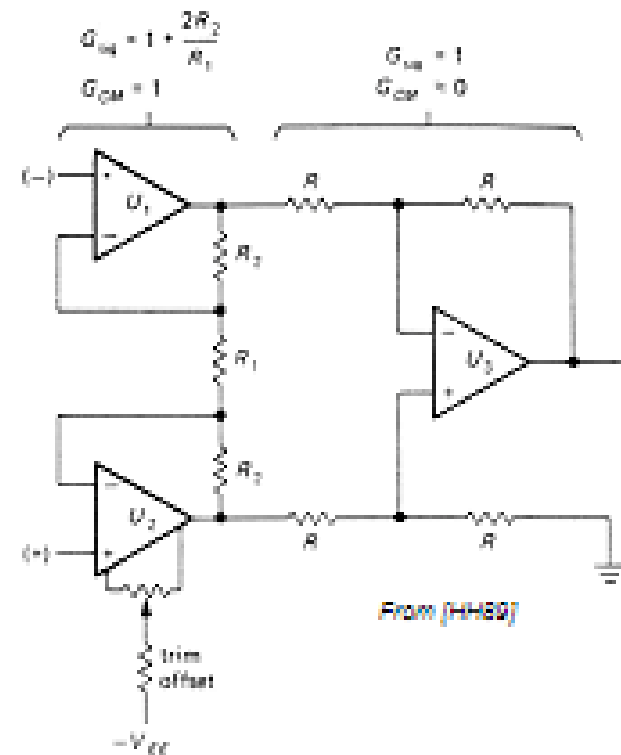
- ▶ A better solution is the “standard” instrumentation amplifier shown below
 - Input stage provides high GD and unity GCM
 - Close resistor (R_2) matching is NOT critical
 - As a result, the output op-amp (U_3) does not require exceptional CMRR and resistor matching in U_3 is not critical
 - Offset trimming can be done at one of the input op-amps



INA...

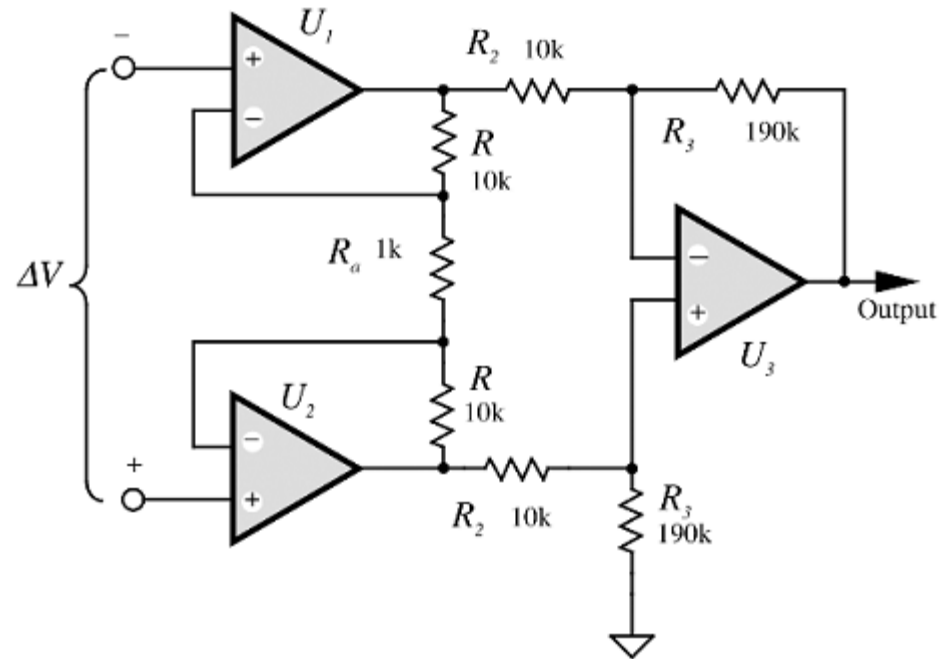

$$A = \left(1 + \frac{2R}{R_a} \right) \frac{R_3}{R_2}$$

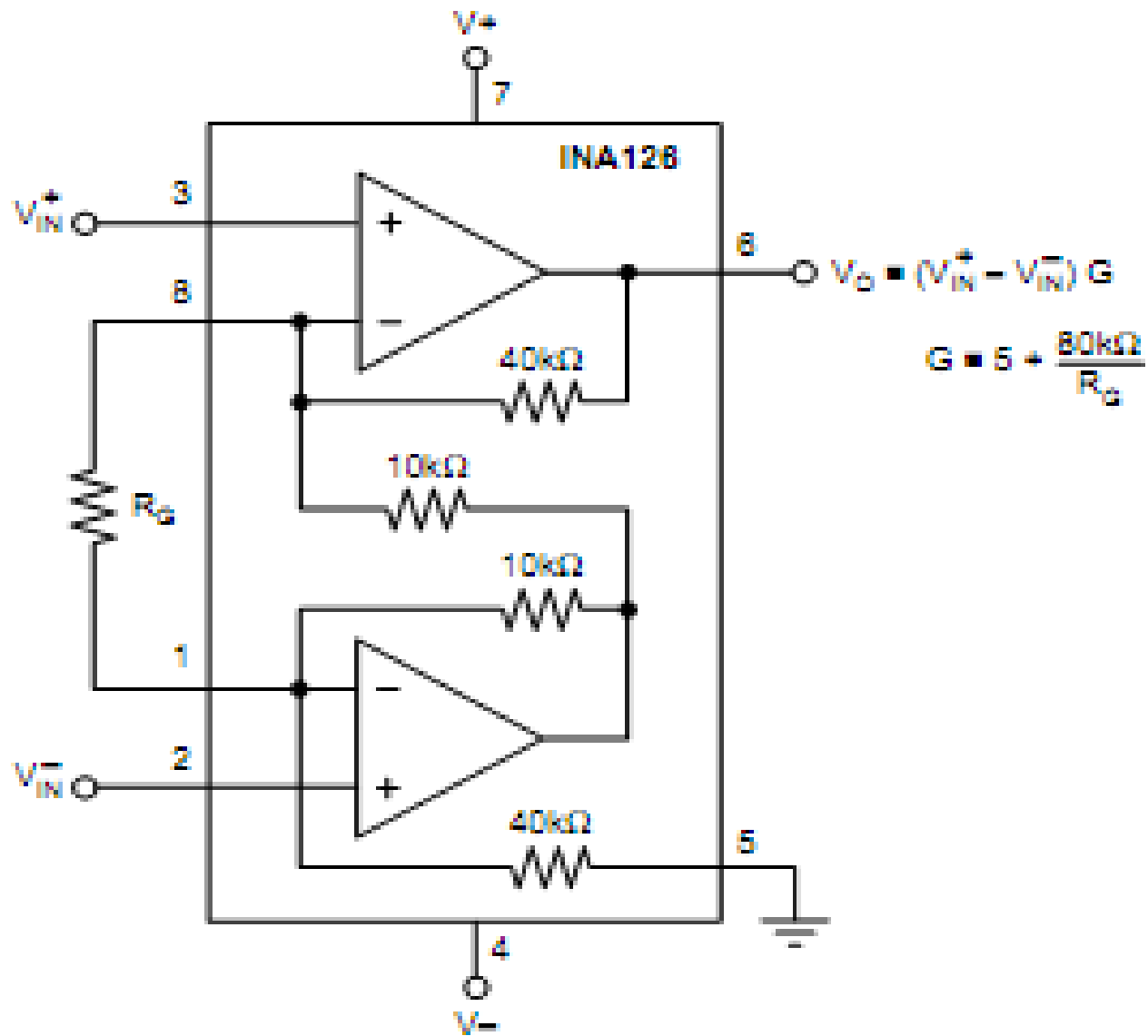


INA126.....



APPLICATIONS

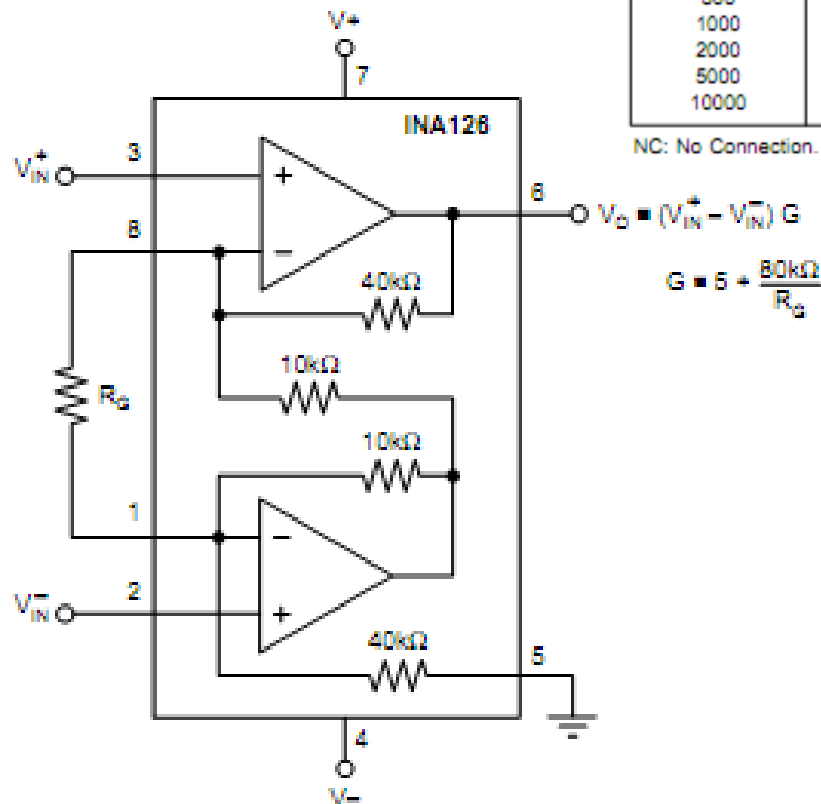- INDUSTRIAL SENSOR AMPLIFIER:
Bridge, RTD, Thermocouple
- PHYSIOLOGICAL AMPLIFIER:
ECG, EEG, EMG
- MULTI-CHANNEL DATA ACQUISITION
- PORTABLE, BATTERY OPERATED SYSTEMS




DESIRED GAIN (V/V)	R_G (Ω)	NEAREST 1% R_G VALUE
5	NC	NC
10	16k	15.8k
20	5333	5360
50	1779	1780
100	842	845
200	410	412
500	162	162
1000	80.4	80.6
2000	40.1	40.2
5000	16.0	15.8
10000	8.0	7.87

PIN CONFIGURATION (Single)

Top View

8-Pin DIP, SO-8, MSOP-8

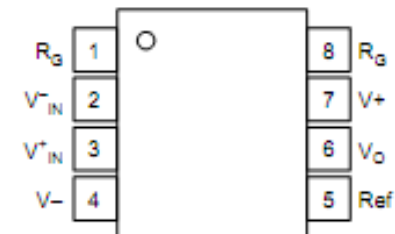


Filters

- ▶ Filters are used to remove unwanted bandwidths from a signal
- ▶ Filter classification according to implementation
 - Active filters include RC networks and op-amps
 - Suitable for low frequency, small signal
 - Active filters are preferred since avoid the bulk and non-linearity of inductors and can have gains greater than 0dB
 - However, active filters require a power supply
 - Passive filters consist of RCL networks
 - Simple, more suitable for frequencies above audio range, where active filters are limited by the op-amp bandwidth
- ▶ Digital filters
 - DSP is beyond the scope of this course


Filters

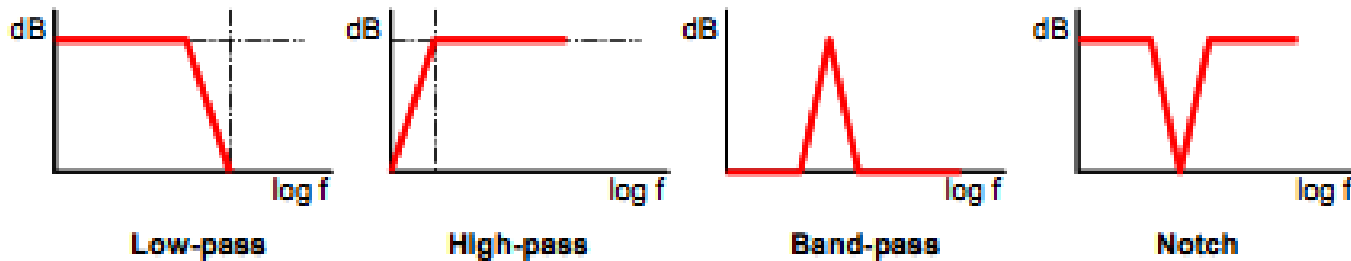- ▶ Filter classification according to frequency response
 - Low-pass filter
 - High-pass filter
 - Band-pass filter
 - Band-stop (Notch)





Low- and high-pass filters

Low pass filters

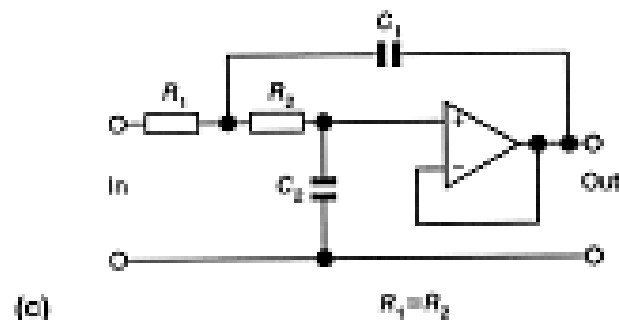

From [Ram96]

High pass filters

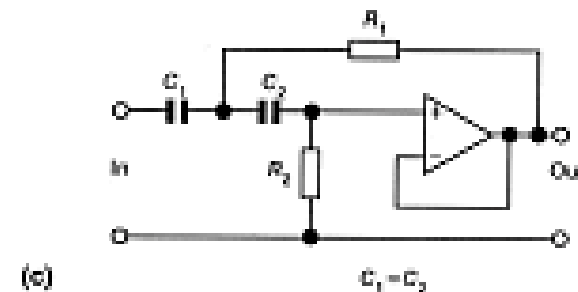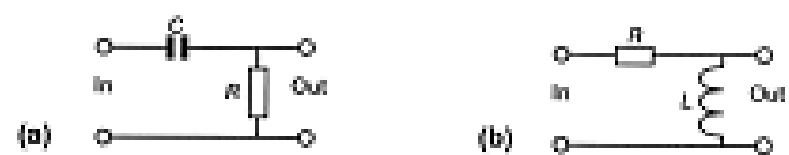


From [Ram96]

Band-pass and band-stop filters


■ Band-pass

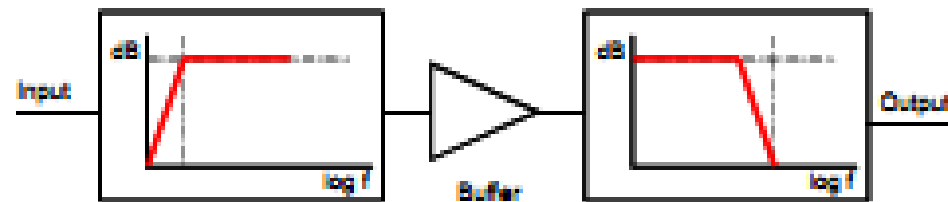- High-pass and low pass in series
 - High-pass should usually precede
 - Corner frequency of low-pass must then be higher
 - If these are passive filters they should be buffered in between




■ Band-stop

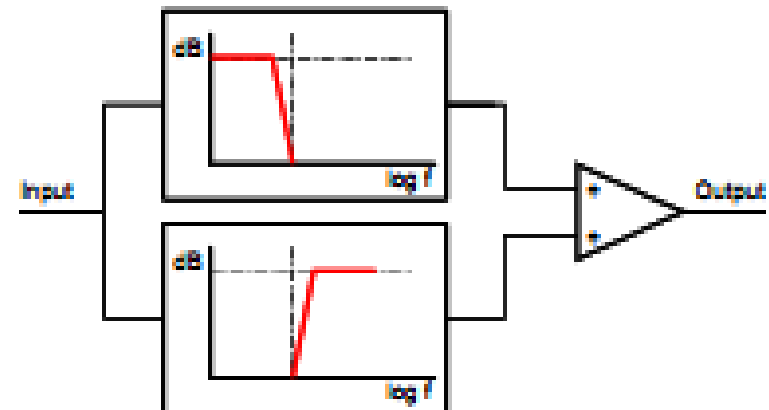- High-pass and low-pass in parallel followed by a summer
 - Corner frequency of high-pass must be higher




Types of Filters

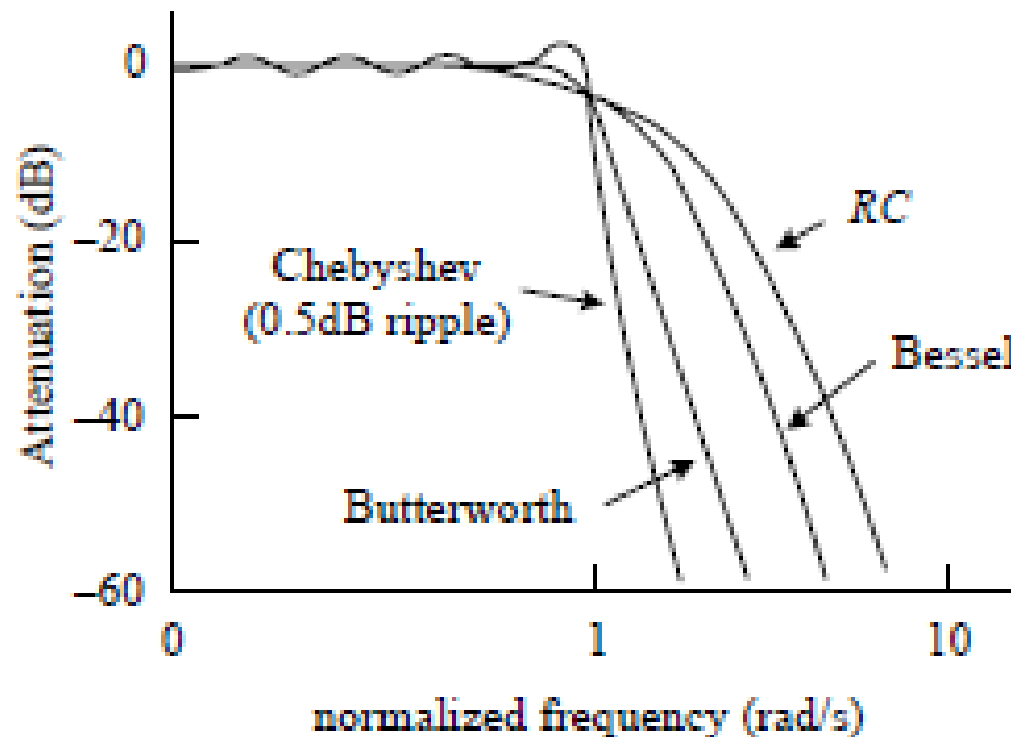
$$T(S) = \frac{V_{out}}{V_{in}} = \frac{N_m S^m + N_{m-1} S^{m-1} + \dots + N_1 S + N_0}{D_n S^n + D_{n-1} S^{n-1} + \dots + D_1 S + D_0}$$



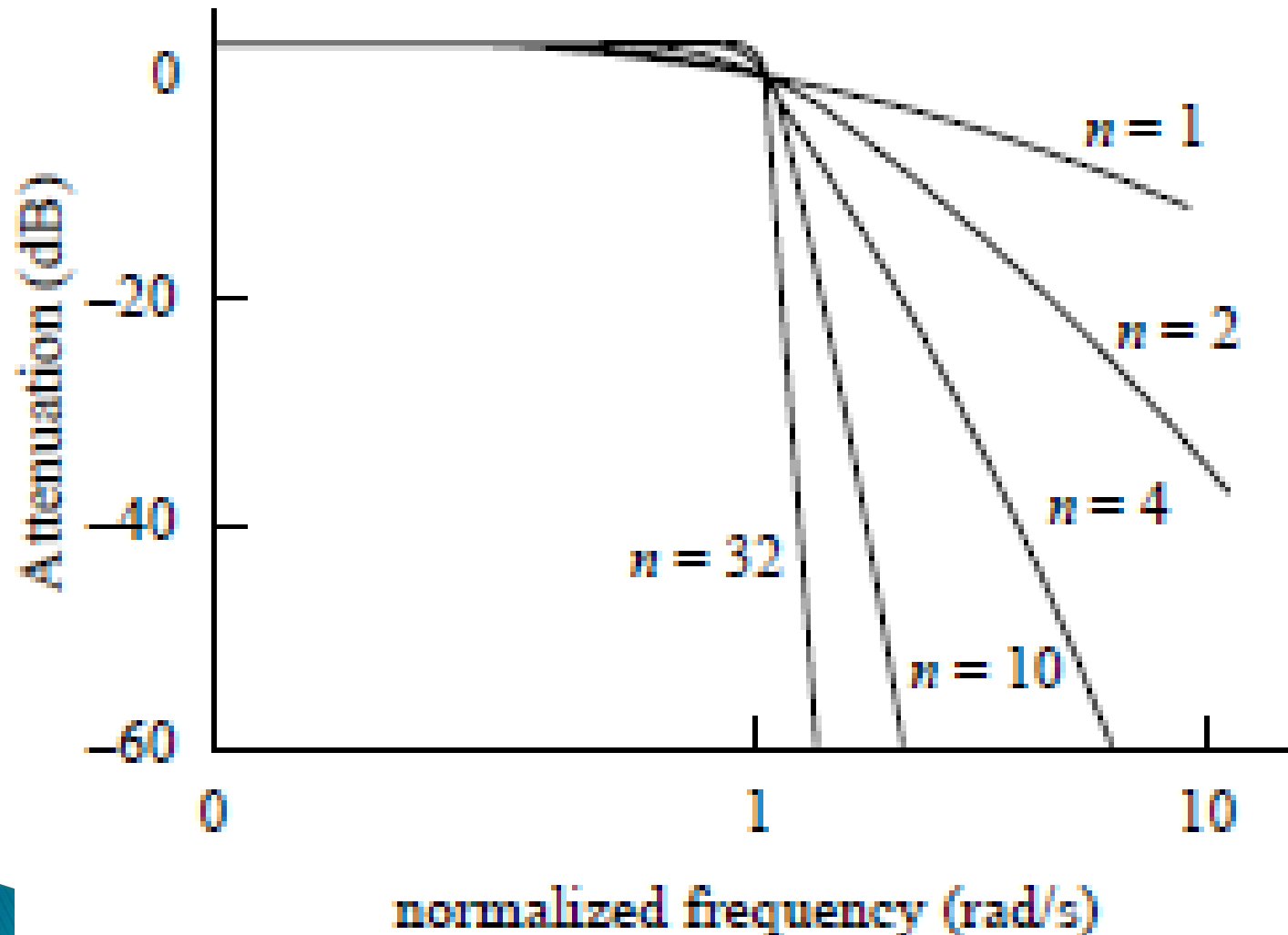
Normalized low-pass Butterworth filter reponse curves



Attenuation curves for Butterworth LPF

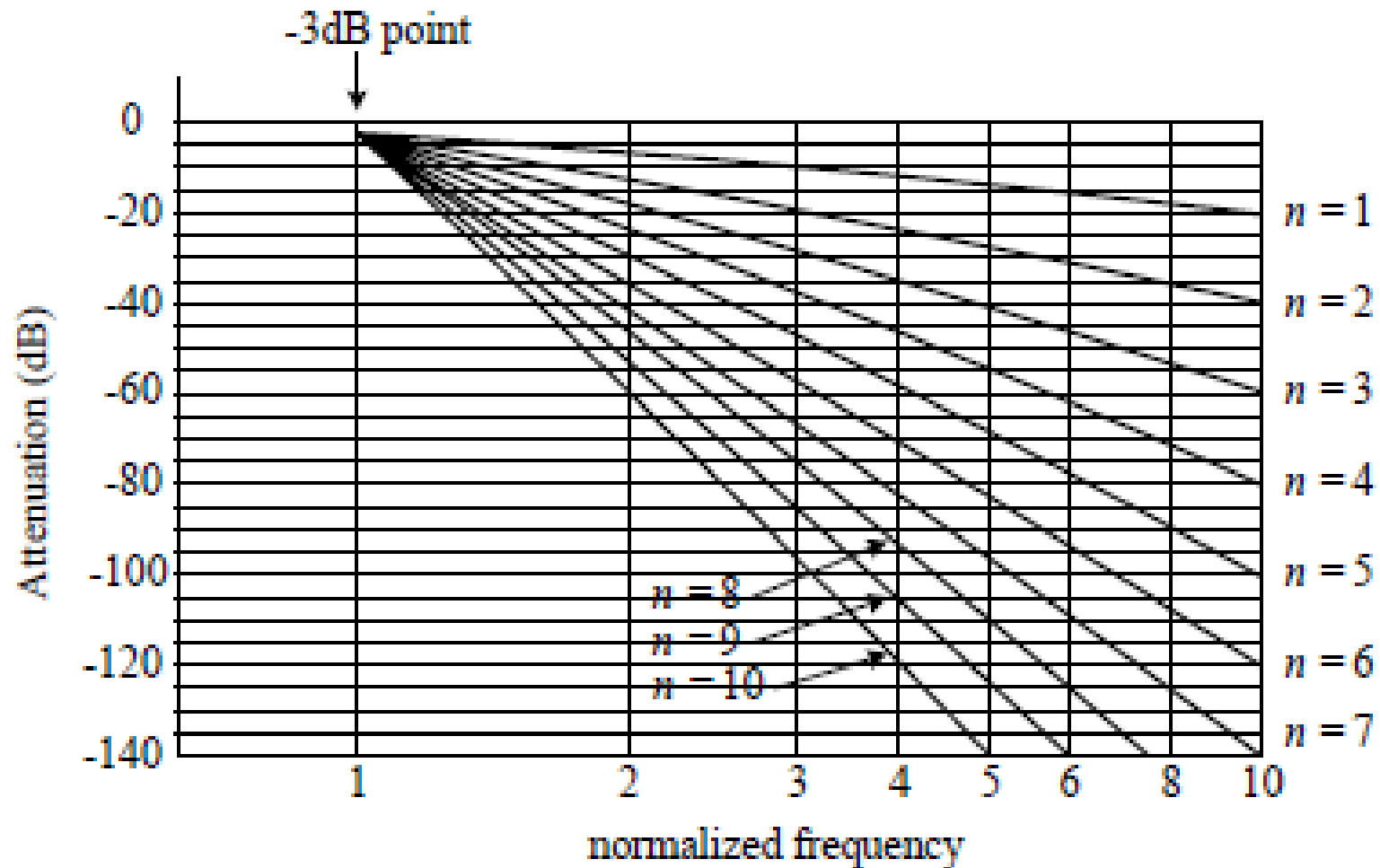

LC Low Pass Filter network

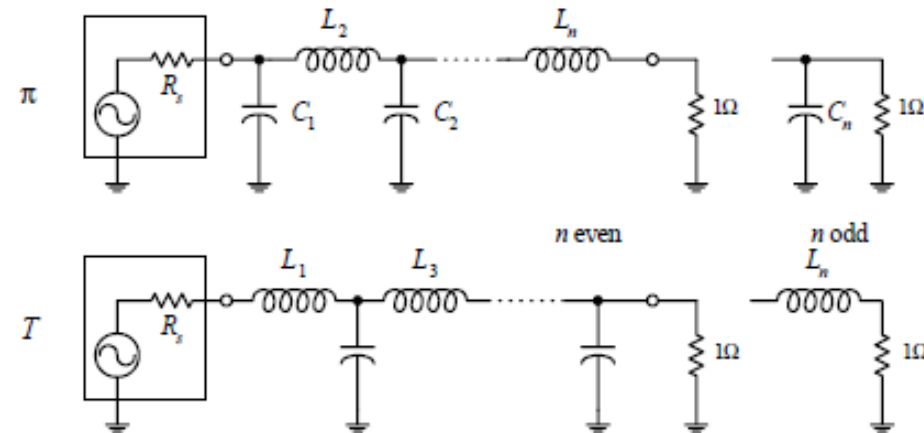



π (T)								
n	R_s ($1/R_s$)	C_1 (L_1)	L_2 (C_2)	C_3 (L_3)	L_4 (C_4)	C_5 (L_5)	L_6 (C_6)	C_7 (L_7)
2	1.000	1.4142	1.4142					
3	1.000	1.0000	2.0000	1.0000				
4	1.000	0.7654	1.8478	1.8478	0.7654			
5	1.000	0.6180	1.6180	2.0000	1.6180	0.6180		
6	1.000	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176	
7	1.000	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450

Note: Values of L_n and C_n are for a 1Ω load and -3 -dB frequency of 1 rad/s and have units of H and F. These values must be scaled down. See text.

Example

Suppose that you want to design a low-pass filter that has a $f_{3\text{dB}} = 3000 \text{ Hz}$ (attenuation is -3 dB at 3000 Hz) and an attenuation of -25 dB at a frequency of 9000 Hz —which will be called the *stop frequency* f_s . Also, let's assume that both the signal-source impedance R_s and the load impedance R_L are equal to 50Ω . How do you design the filter?


Step 1: Normalization

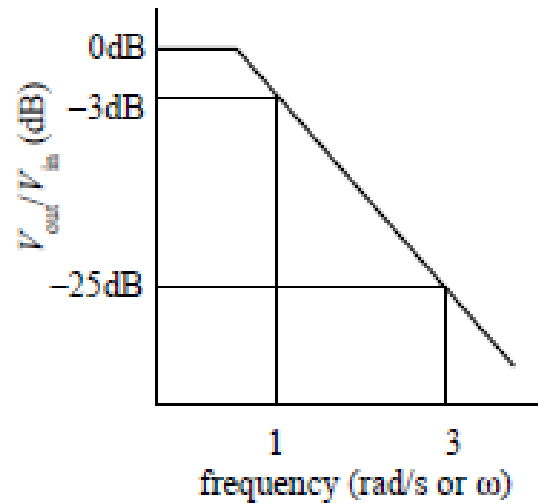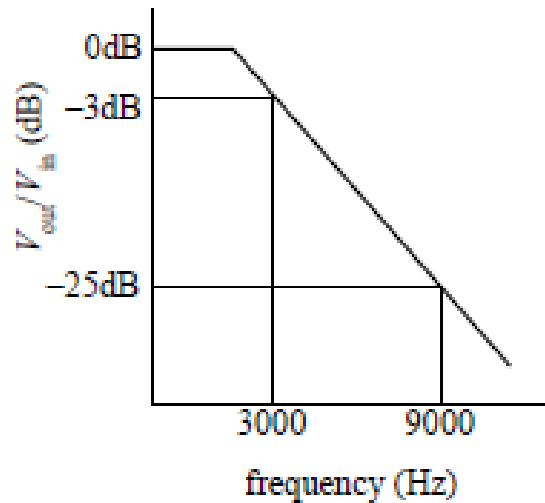

Step 2&3: Pick Response Curve and determine number of Poles

$n=3$ from the curve for Butterworth

Step 4: Create Normalized Filter

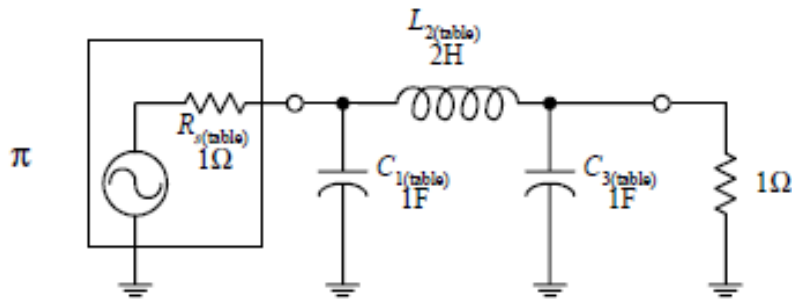


Step 5: Frequency and Impedance Scaling

$$L_{2(actual)} = \frac{R_L L_{2(table)}}{2\pi f_{3dB}} = \frac{(50\Omega)(2\text{ H})}{2\pi(3000\text{ Hz})} = 5.3\text{ mH}$$


$$C_{1(actual)} = \frac{C_{1(table)}}{2\pi f_{3dB} R_L} = \frac{1\text{ F}}{2\pi(3000\text{ Hz})(50\Omega)} = 1.06\text{ }\mu\text{F}$$
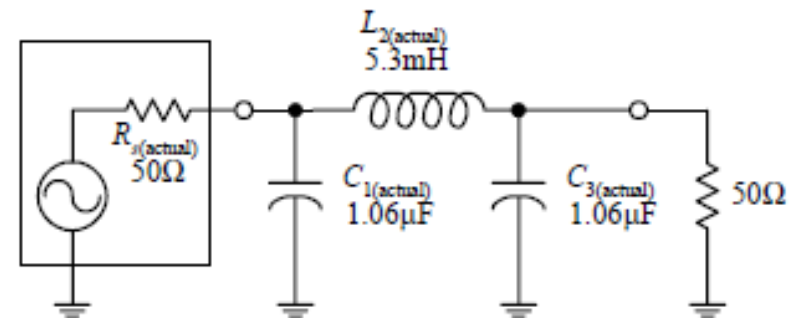
$$C_{3(actual)} = \frac{C_{3(table)}}{2\pi f_{3dB} R_L} = \frac{1\text{ F}}{2\pi(3000\text{ Hz})(50\Omega)} = 1.06\text{ }\mu\text{F}$$




Active Filter Design

Basic two-pole section

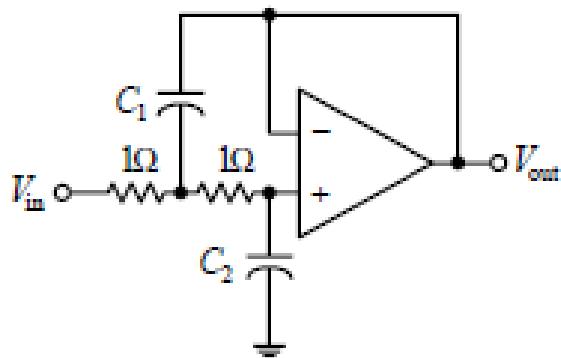

Basic three-pole section

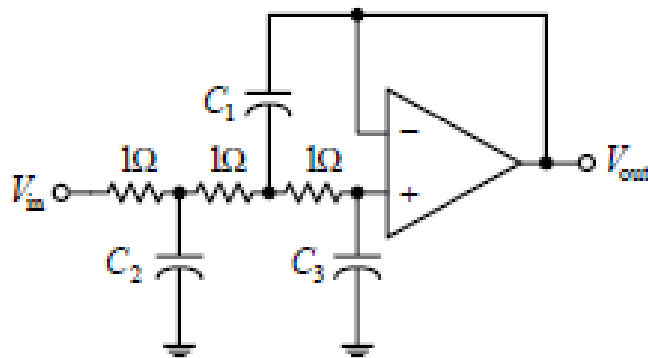

Normalized Curves



TABLE 8.2 Butterworth Normalized Active Low-Pass Filter Values

ORDER n	NUMBER OF SECTIONS	SECTIONS	C_1	C_2	C_3
2	1	2-pole	1.414	0.7071	
3	1	3-pole	3.546	1.392	0.2024
4	2	2-pole 2-pole	1.082 2.613	0.9241 0.3825	
5	2	3-pole 2-pole	1.753 3.235	1.354 0.3090	0.4214
6	3	2-pole 2-pole 2-pole	1.035 1.414 3.863	0.9660 0.7071 0.2588	
7	3	3-pole 2-pole 2-pole	1.531 1.604 4.493	1.336 0.6235 0.2225	0.4885
8	4	2-pole 2-pole 2-pole 2-pole	1.020 1.202 2.000 5.758	0.9809 0.8313 0.5557 0.1950	

Example



Suppose that you wish to design an active low-pass filter that has a 3-dB point at 100 Hz and at least 60 dB worth of attenuation at 400 Hz—which we'll call the *stop frequency* f_s .

Solution

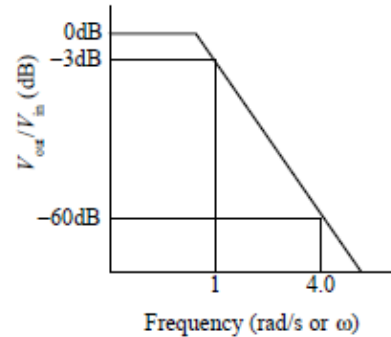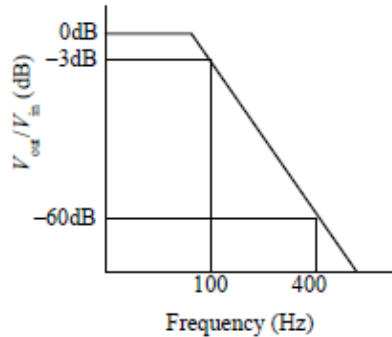

$$A_s = \frac{f_s}{f_{3dB}} = \frac{400 \text{ Hz}}{100 \text{ Hz}} = 4$$

$n=5$ from the curves

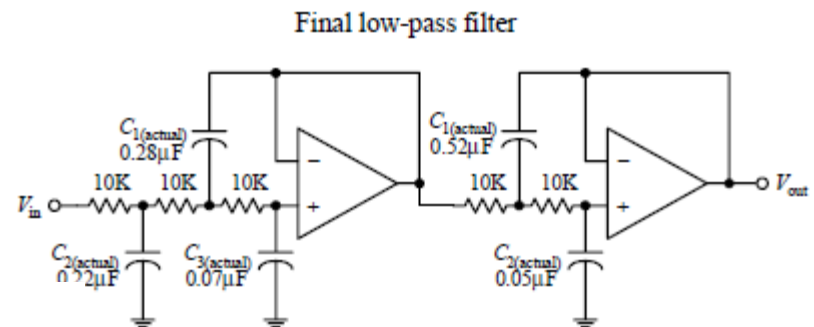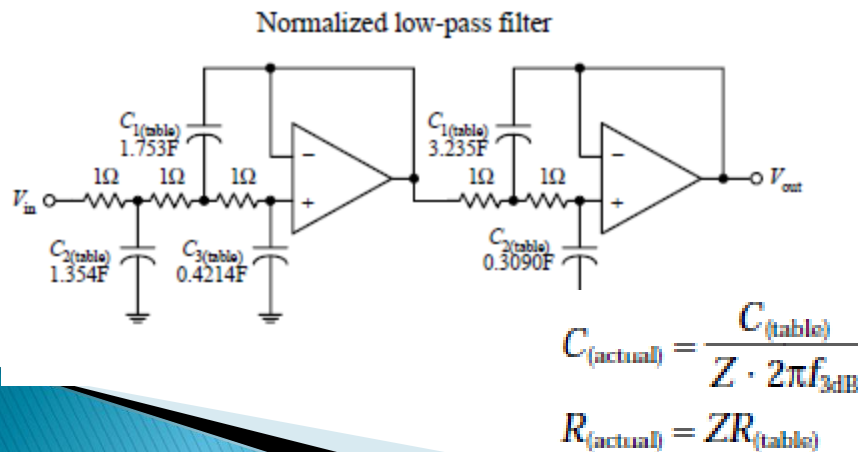


High Pass Filter –Passive–

Suppose that you want to design a high-pass filter that has an $f_{3dB} = 1000 \text{ Hz}$ and an attenuation of at least -45 dB at 300 Hz —which we call the *stop frequency* f_s . Assume that the filter is hooked up to a source and load that both have impedances of 50Ω and that a Butterworth response is desired


How do you design the filter?

Solution

Frequency Response Curve

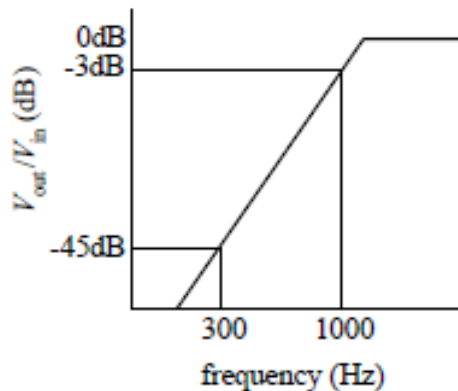

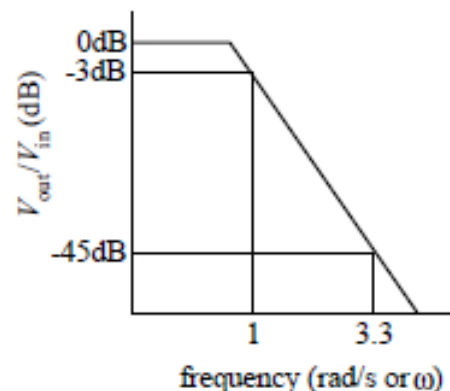Normalized translation to low-pass filter



$$A_s = \frac{f_{3dB}}{f_s} = \frac{1000 \text{ Hz}}{300 \text{ Hz}} = 3.3$$


To convert the low-pass into a high-pass filter, replace the inductors with capacitors that have value of $1/L$, and replace the capacitors with inductors that have values of $1/C$. In other words, do the following:

$$L_{2(transf)} = 1/C_{2(table)} = 1/1.6180 = 0.6180 \text{ H}$$


$$L_{4(transf)} = 1/C_{4(table)} = 1/1.6180 = 0.6180 \text{ H}$$

$n=5$ from the curves

Start with a "T" low-pass filter...

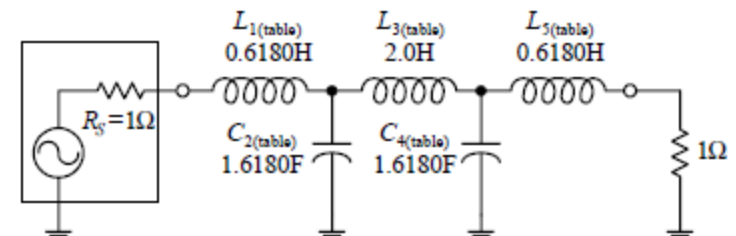

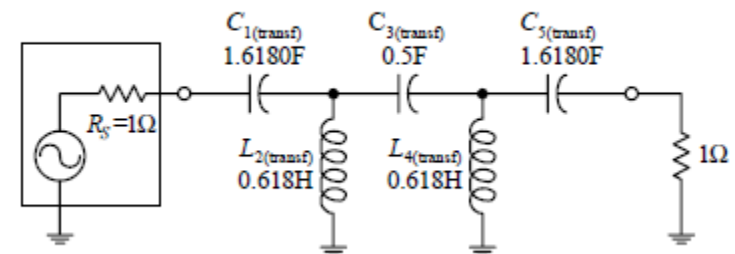Transform low-pass filter into a high-pass filter...



$$C_{1(transf)} = 1/L_{1(table)} = 1/0.6180 = 1.6180 \text{ F}$$

$$C_{3(transf)} = 1/L_{3(table)} = 1/2.0 = 0.5 \text{ F}$$

$$C_{5(transf)} = 1/L_{5(table)} = 1/0.6180 = 1.6180 \text{ F}$$

Now Scaling


Next, frequency and impedance scale to get the actual component values:

$$C_{1(\text{actual})} = \frac{C_{1(\text{trans})}}{2\pi f_{3\text{dB}} R_L} = \frac{1.618 \text{ H}}{2\pi(1000 \text{ Hz})(50 \Omega)} = 5.1 \mu\text{F} \quad L_{2(\text{actual})} = \frac{L_{2(\text{trans})} R_L}{2\pi f_{3\text{dB}}} = \frac{(0.6180 \text{ F})(50 \Omega)}{2\pi(1000 \text{ Hz})} = 4.9 \text{ mH}$$

$$C_{3(\text{actual})} = \frac{C_{3(\text{trans})}}{2\pi f_{3\text{dB}} R_L} = \frac{0.5 \text{ H}}{2\pi(1000 \text{ Hz})(50 \Omega)} = 1.6 \mu\text{F} \quad L_{4(\text{actual})} = \frac{L_{4(\text{trans})} R_L}{2\pi f_{3\text{dB}}} = \frac{(0.6180 \text{ F})(50 \Omega)}{2\pi(1000 \text{ Hz})} = 4.9 \text{ mH}$$

$$C_{5(\text{actual})} = \frac{C_{5(\text{trans})}}{2\pi f_{3\text{dB}} R_L} = \frac{1.618 \text{ H}}{2\pi(1000 \text{ Hz})(50 \Omega)} = 5.1 \mu\text{F}$$

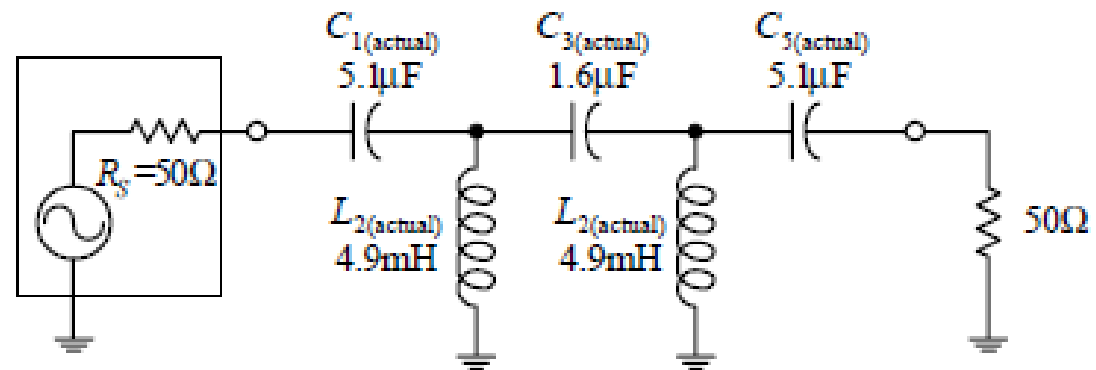Impedance and frequency scale high-pass filter to get final circuit




High Pass Filter–Active–

suppose


that you want to design a high-pass filter with a -3 -dB frequency of 1000 Hz and 50 dB worth of attenuation at 300 Hz. What do you do?

$n=5$ from the curves


High-pass frequency response

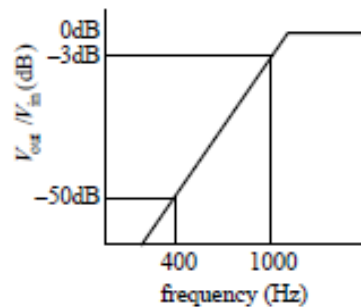

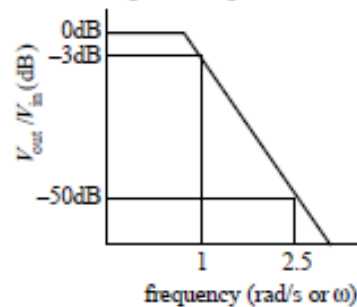Translation to normalized low-pass response




Normalized low-pass filter

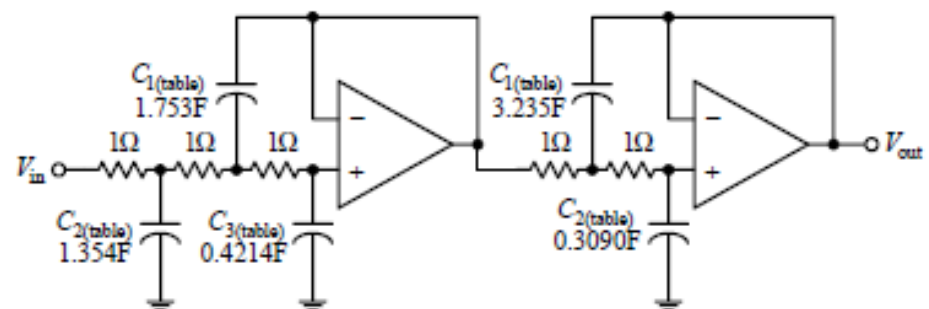

Next, the normalized low-pass filter must be converted into a normalized high-pass filter. To make the conversion, exchange resistors for capacitors that have values of $1/R$ F, and exchange capacitors with resistors that have values of $1/C$ Ω .

Follow.....

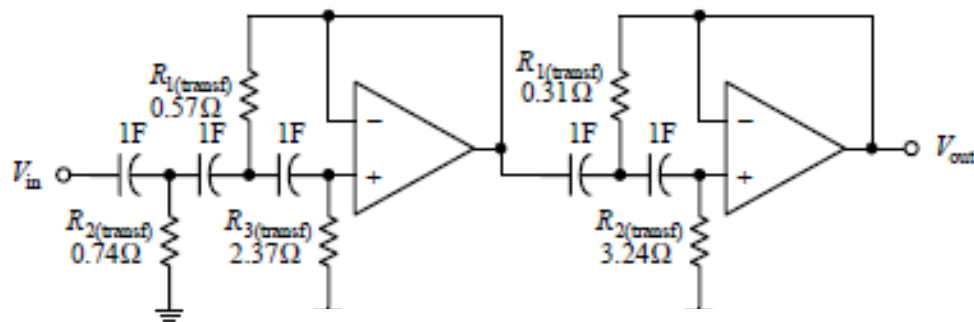Normalized high-pass filter (transformed low-pass filter)




$$C_{\text{(actual)}} = \frac{C_{\text{(transf)}}}{Z \cdot 2\pi f_{\text{3dB}}}$$

$$R_{\text{(actual)}} = Z R_{\text{(transf)}}$$

let $Z = 10,000 \Omega$.

Final high-pass filter

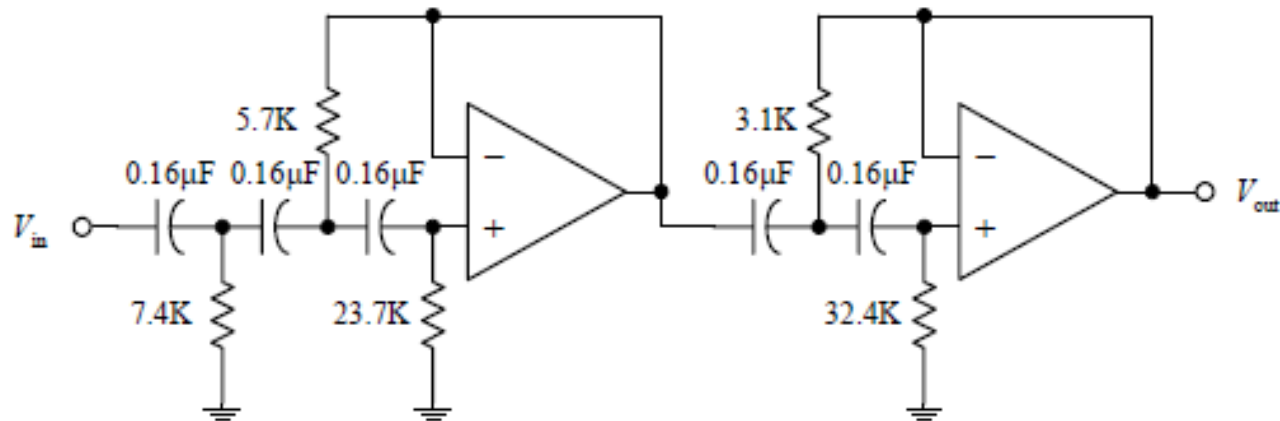

Bandpass Filter Design–Wide Band–Passive–

When is the filter wide band??



If f_2/f_1 is greater than 1.5,

Suppose that you want to design a bandpass filter that has -3 -dB points at $f_1 = 1000$ Hz and $f_2 = 3000$ Hz and at least -45 dB at 300 Hz and more than -25 dB at 9000 Hz. Also, again assume that the source and load impedances are both $50\ \Omega$ and a Butterworth design is desired.

Low-pass -3 dB at 3000 Hz
 -25 dB at 9000 Hz

High-pass -3 dB at 1000 Hz
 -45 dB at 300 Hz

Bandpass Response Curve

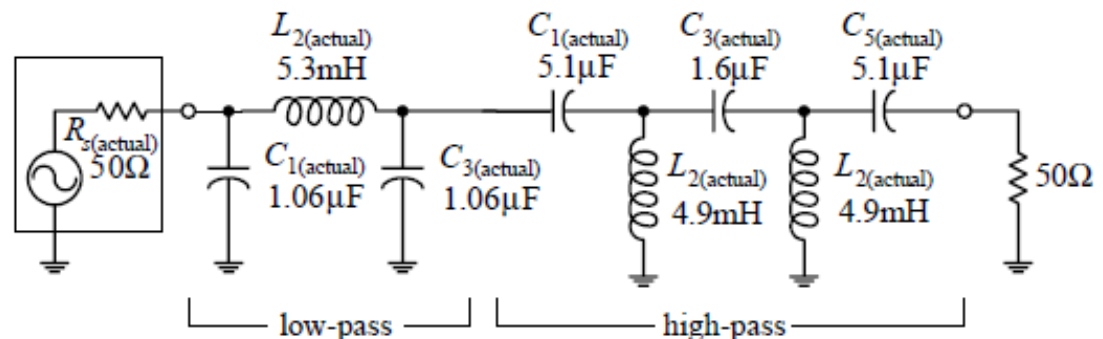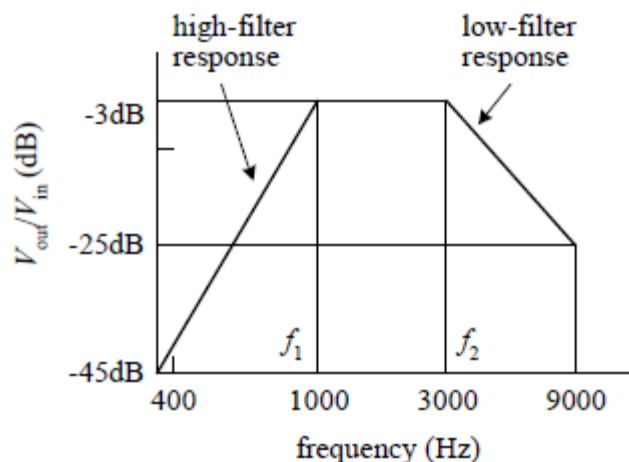

Just Cascade

Bandpass Filter Design–Wide Band–Active–

Suppose that you want to design a bandpass filter that has -3-dB points at $f_1 = 1000$ Hz and $f_2 = 3000$ Hz and at least -30 dB at 300 and 10,000 Hz. What do you do?

$$\frac{f_2}{f_1} = \frac{3000\text{ Hz}}{1000\text{ Hz}} = 3$$

Low-pass: -3 dB at 3000 Hz
 -30 dB at 10,000 Hz
 High-pass: -3 dB at 1000 Hz
 -30 dB at 300 Hz


The steepness factor for the low-pass filter is

$$A_s = \frac{f_s}{f_{3\text{dB}}} = \frac{10,000\text{ Hz}}{3000\text{ Hz}} = 3.3$$

while the steepness factor for the high-pass filter is


$$A_s = \frac{f_{3\text{dB}}}{f_s} = \frac{1000\text{ Hz}}{300\text{ Hz}} = 3.3$$

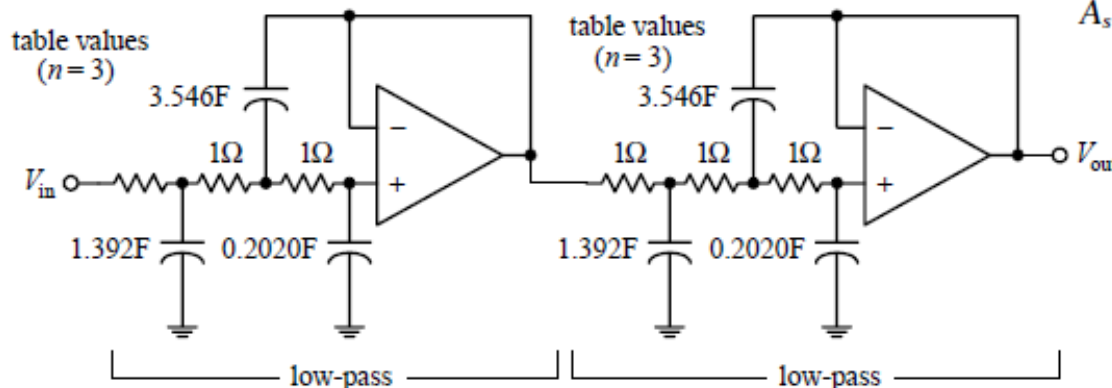Normalized low-pass/low-pass initial setup



Follow...

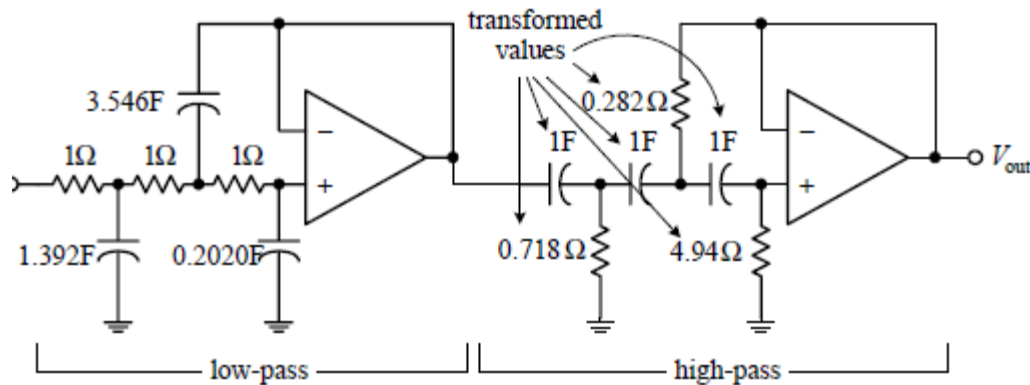Normalized and transformed bandpass filter




Low-pass section:

$$C_{(\text{actual})} = \frac{C_{\text{table}}}{Z \cdot 2\pi f_{3\text{dB}}} = \frac{C_{\text{table}}}{Z \cdot 2\pi(3000 \text{ Hz})}$$

High-pass section:

$$C_{(\text{actual})} = \frac{C_{\text{table}}}{Z \cdot 2\pi f_{2\text{dB}}} = \frac{C_{\text{table}}}{Z \cdot 2\pi(1000 \text{ Hz})}$$

Final bandpass filter

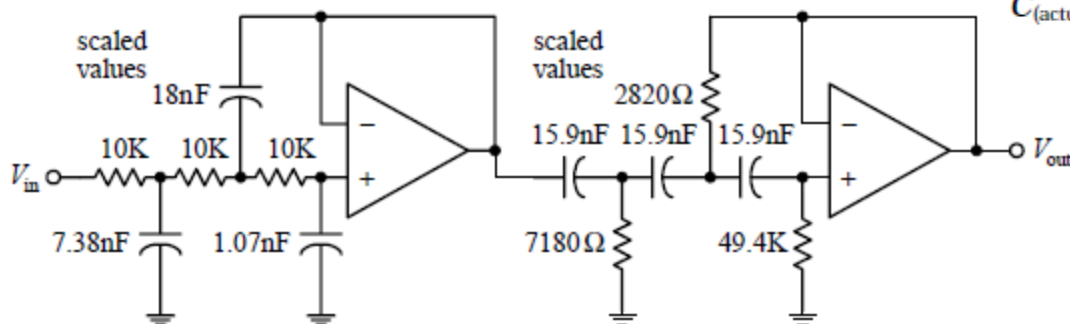

Narrow Bandwidth BPF–Passive (optional)

Suppose that you want to design a bandpass filter with -3 -dB points at $f_1 = 900$ Hz and $f_2 = 1100$ Hz and at least -20 dB worth of attenuation at 800 and 1200 Hz. Assume that both the source and load impedances are $50\ \Omega$ and that a Butterworth design is desired.

Since $f_2/f_1 = 1.2$, which is less than 1.5, a narrow-band filter is needed.

geometric center frequency $f_0 = \sqrt{f_1 f_2} = \sqrt{(900\text{ Hz})(1100)} = 995\text{ Hz}$

Next, compute the two pair of geometrically related stop-band frequencies by using

$$f_a f_b = f_0^2$$


$$f_a = 800\text{ Hz} \quad f_b = \frac{f_0^2}{f_a} = \frac{(995\text{ Hz})^2}{800\text{ Hz}} = 1237\text{ Hz} \quad f_b - f_a = 437\text{ Hz}$$

$$f_b = 1200\text{ Hz} \quad f_a = \frac{f_0^2}{f_b} = \frac{(995\text{ Hz})^2}{1200\text{ Hz}} = 825\text{ Hz} \quad f_b - f_a = 375\text{ Hz}$$

Choose the pair having the least separation, which represents more severe requirements—375 Hz

Follow.....


Low-pass bandpass relationship

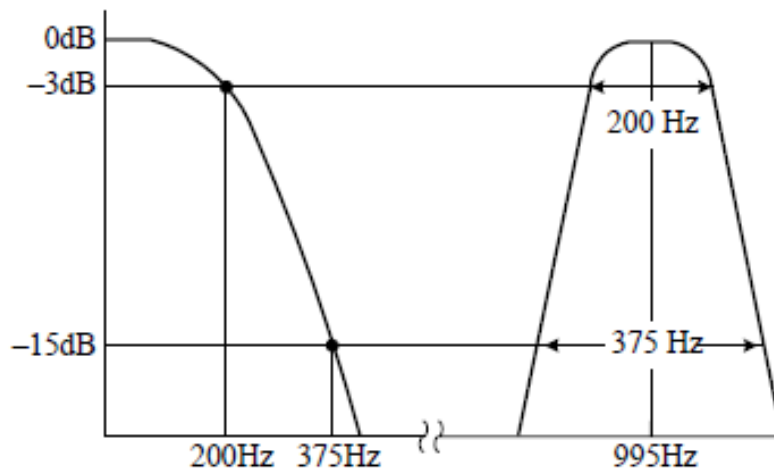


$$A_s = \frac{\text{stop-band bandwidth}}{\text{3-dB bandwidth}} = \frac{375 \text{ Hz}}{200 \text{ Hz}} = 1.88$$

From the curve $n=3$

Normalized low-pass response

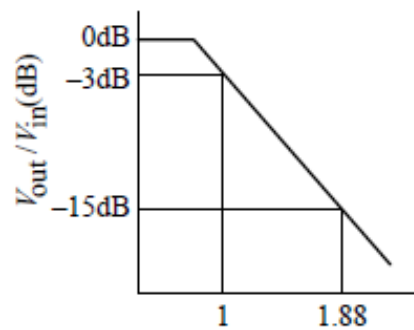

Normalized low-pass filter

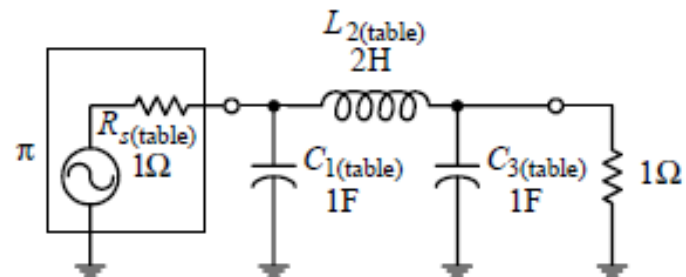


Follow.....

Impedance and frequency scaled low-pass filter

$$C_{1(\text{actual})} = \frac{C_{1(\text{table})}}{2\pi(\Delta f_{BW})R_L} = \frac{1 \text{ F}}{2\pi(200 \text{ Hz})(50 \Omega)} = 15.92 \mu\text{F}$$

$$C_{3(\text{actual})} = \frac{C_{3(\text{table})}}{2\pi(\Delta f_{BW})R_L} = \frac{1 \text{ F}}{2\pi(200 \text{ Hz})(50 \Omega)} = 15.92 \mu\text{F}$$
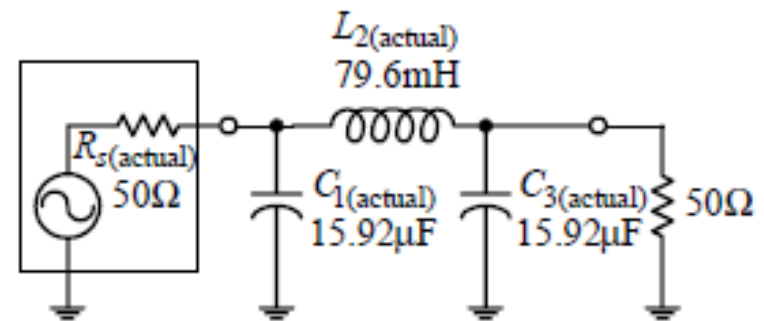
$$L_{2(\text{actual})} = \frac{L_{2(\text{table})}R_L}{2\pi(\Delta f_{BW})} = \frac{(2 \text{ H})(50 \Omega)}{2\pi(200 \text{ Hz})} = 79.6 \text{ mH}$$



The important part comes now. Each circuit branch of the low-pass filter must be resonated to f_0 by adding a series capacitor to each inductor and a parallel inductor to each capacitor. The LC resonant equation is used to determine the additional component values:


$$L_{(\text{parallel with } C1)} = \frac{1}{(2\pi f_0)^2 C_{1(\text{actual})}} = \frac{1}{(2\pi \cdot 995 \text{ Hz})^2 (15.92 \mu\text{F})} = 1.61 \text{ mH}$$

$$L_{(\text{parallel with } C3)} = \frac{1}{(2\pi f_0)^2 C_{3(\text{actual})}} = \frac{1}{(2\pi \cdot 995 \text{ Hz})^2 (15.92 \mu\text{F})} = 1.61 \text{ mH}$$

$$C_{(\text{series with } L2)} = \frac{1}{(2\pi f_0)^2 L_{2(\text{actual})}} = \frac{1}{(2\pi \cdot 995 \text{ Hz})^2 (79.6 \text{ mH})} = 0.32 \mu\text{F}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Final bandpass filter

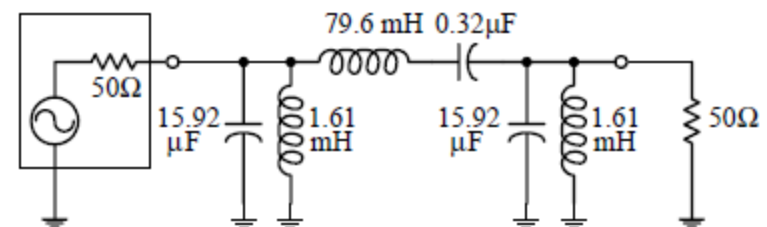


BPF–Narrow Band–Active Design

Suppose that you want to design a bandpass filter that has a center frequency $f_0 = 2000$ Hz and a -3 -dB bandwidth $\Delta f_{BW} = f_2 - f_1 = 40$ Hz. How do you design the filter?

Since $f_2/f_1 = 2040 \text{ Hz}/1960 \text{ Hz} = 1.04$,

No Cascading

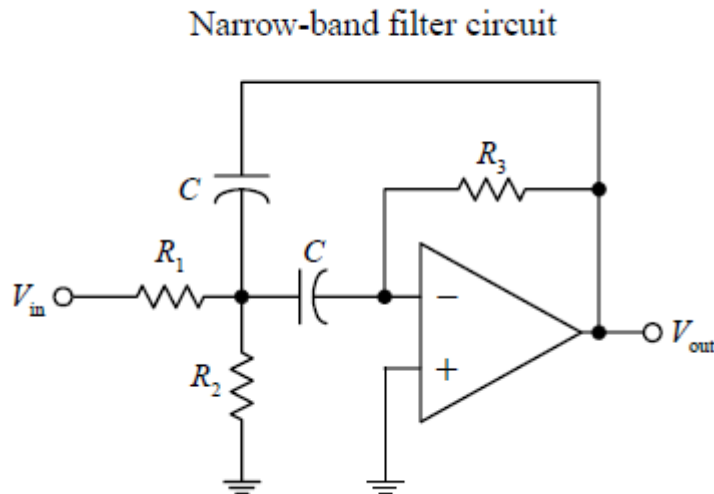

$$Q = \frac{f_0}{f_2 - f_1} = \frac{2000 \text{ Hz}}{40 \text{ Hz}} = 50$$

$$R_1 = \frac{Q}{2\pi f_0 C}$$

$$R_2 = \frac{R_1}{2Q^2 - 1}$$

$$R_3 = 2R_1$$

$$R_1 = \frac{50}{2\pi(2000 \text{ Hz})(0.01 \mu\text{F})} = 79.6 \text{ k}\Omega$$


$$R_2 = \frac{79.6 \text{ k}\Omega}{2(50)^2 - 1} = 400 \Omega$$

$$R_3 = 2(79.6 \text{ k}\Omega) = 159 \text{ k}\Omega$$

Choose convenient value of C, let it $0.01 \mu\text{F}$

Final Design ...

Final filter circuit

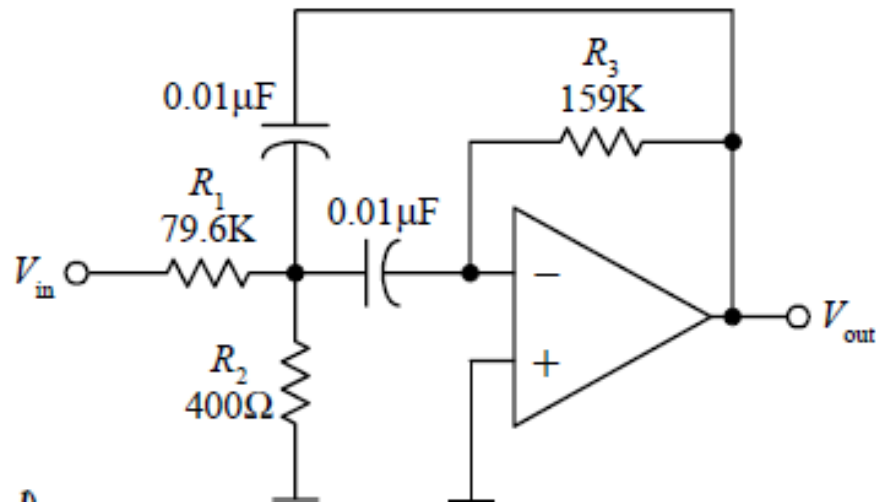

Passive Notch Filter (optional)

EXAMPLE

Suppose that you want to design a notch filter with -3 -dB points at $f_1 = 800$ Hz and $f_2 = 1200$ Hz and at least -20 dB at 900 and 1100 Hz. Let's assume that both the source and load impedances are $600\ \Omega$ and that a Butterworth design is desired.

First, you find the geometric center frequency:

$$f_0 = \sqrt{f_1 f_2} = \sqrt{(800\text{ Hz})(1200\text{ Hz})} = 980\text{ Hz}$$

Next, compute the two pairs of geometrically related stop-band frequencies:

$$f_a = 900\text{ Hz} \quad f_b = \frac{f_0^2}{f_a} = \frac{(980\text{ Hz})^2}{900\text{ Hz}} = 1067\text{ Hz}$$

$$f_b - f_a = 1067\text{ Hz} - 900\text{ Hz} = 167\text{ Hz}$$


$$f_b = 1100\text{ Hz} \quad f_a = \frac{f_0^2}{f_b} = \frac{(980\text{ Hz})^2}{1100\text{ Hz}} = 873\text{ Hz}$$

$$f_b - f_a = 1100\text{ Hz} - 873\text{ Hz} = 227\text{ Hz}$$

Choose the pair of frequencies that gives the more severe requirement—227 Hz.

Follow....

High-pass bandpass relationship

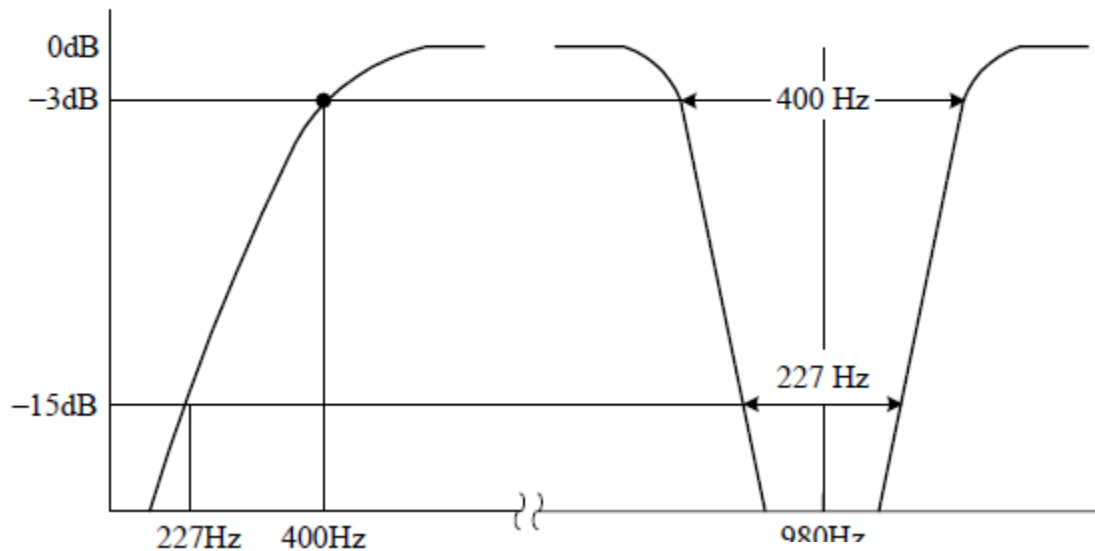


$$A_s = \frac{\text{3-dB bandwidth}}{\text{stop-band bandwidth}} = \frac{400 \text{ Hz}}{227 \text{ Hz}} = 1.7$$

$$L_{1(\text{transf})} = 1/C_{1(\text{table})} = 1/1 = 1 \text{ H}$$


$$L_{3(\text{transf})} = 1/C_{3(\text{table})} = 1/1 = 1 \text{ H}$$

$$C_{2(\text{transf})} = 1/L_{2(\text{table})} = 1/2 = 0.5 \text{ F}$$

Normalized low-pass filter

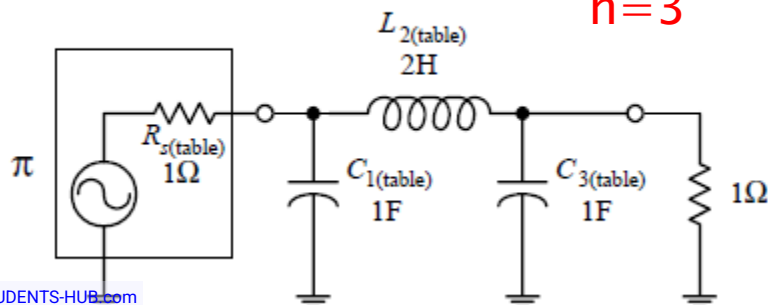


Normalized high-pass filter

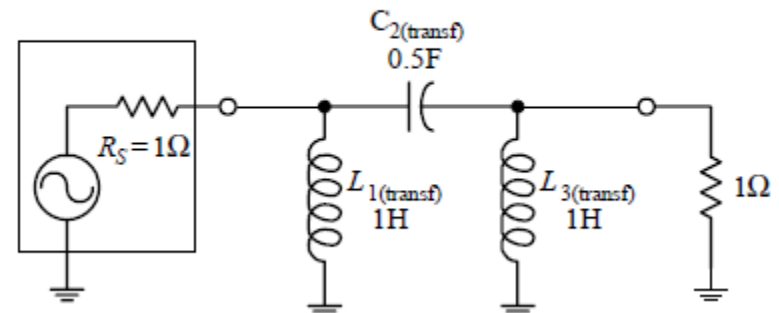

Follow...

Actual high-pass filter

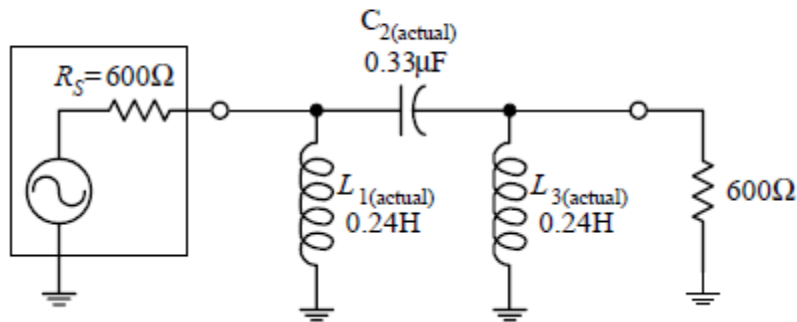


$$L_{1(actual)} = \frac{R_L L_{1(transf)}}{2\pi(\Delta f_{BW})} = \frac{(600\ \Omega)(1\ \text{H})}{2\pi(400\ \text{Hz})} = 0.24\ \text{H}$$

$$L_{3(actual)} = \frac{R_L L_{3(transf)}}{2\pi(\Delta f_{BW})} = \frac{(600\ \Omega)(1\ \text{H})}{2\pi(400\ \text{Hz})} = 0.24\ \text{H}$$

$$C_{2(actual)} = \frac{C_{1(transf)}}{2\pi(\Delta f_{BW}) R_L} = \frac{(0.5\ \text{F})}{2\pi(400\ \text{Hz})(600\ \Omega)} = 0.33\ \mu\text{F}$$

Final bandpass filter

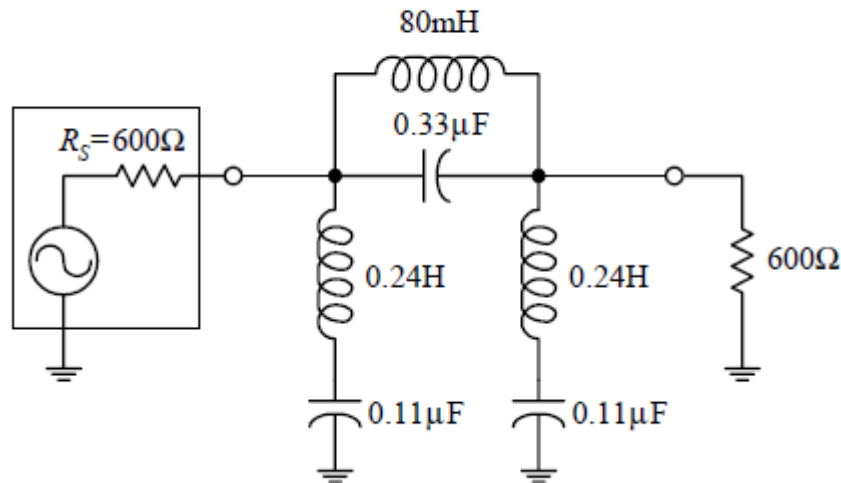


$$C_{(\text{series with } L1)} = \frac{1}{(2\pi f_0)^2 L_{1(actual)}} = \frac{1}{(2\pi \cdot 400\ \text{Hz})^2 (0.24\ \text{H})} = 0.11\ \mu\text{F}$$

$$C_{(\text{series with } L3)} = \frac{1}{(2\pi f_0)^2 L_{3(actual)}} = \frac{1}{(2\pi \cdot 400\ \text{Hz})^2 (0.24\ \text{H})} = 0.11\ \mu\text{F}$$

$$L_{(\text{parallel with } L1)} = \frac{1}{(2\pi f_0)^2 C_{2(actual)}} = \frac{1}{(2\pi \cdot 400\ \text{Hz})^2 (0.33\ \mu\text{F})} = 80\ \text{mH}$$

Active Notch Filter –Wide–Band


Basic wide-band notch filter

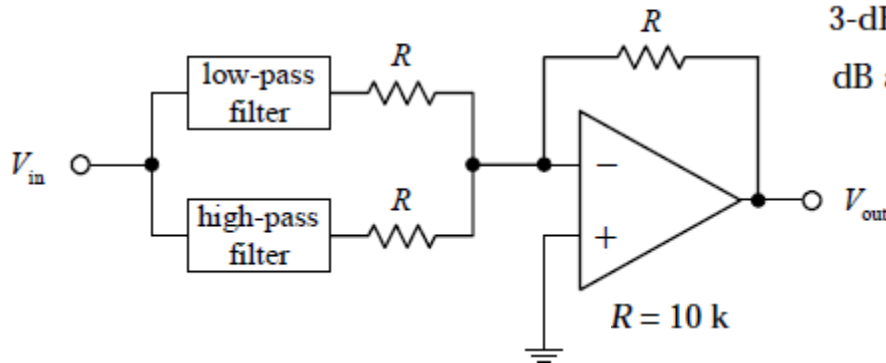

For example, if you need a notch filter to have –3-dB points at 500 and 5000 Hz and at least –15 dB at 1000 and 2500 Hz,

Narrow-Band Notch Filter

Improved notch filter

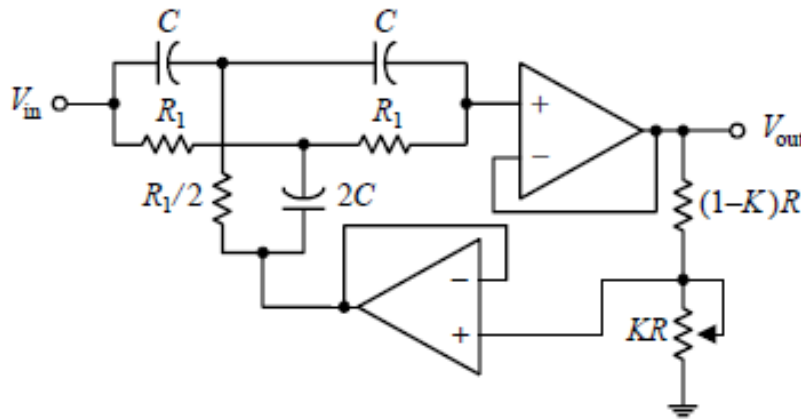

Suppose that you want to make a “notch” at $f_0 = 2000$ Hz and desire a -3 -dB bandwidth of $\Delta f_{BW} = 100$ Hz. To get this desired response, do the following: First determine the Q :

$$Q = \frac{\text{“notch” frequency}}{-3\text{-dB bandwidth}} = \frac{f_0}{\Delta f_{BW}} = \frac{2000 \text{ Hz}}{100 \text{ Hz}} = 20$$

$$R_1 = \frac{1}{2\pi f_0 C} \quad \text{and} \quad K = \frac{4Q - 1}{4Q}$$

Now arbitrarily choose R and C ; say, let $R = 10$ k and $C = 0.01$ μF . Next, solve for R_1 and K :


$$R_1 = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi(2000 \text{ Hz})(0.01 \mu\text{F})} = 7961 \Omega$$

$$K = \frac{4Q - 1}{4Q} = \frac{4(20) - 1}{4(20)} = 0.9875$$

Anti-aliasing

► The sampling theorem

- A continuous signal can be represented completely by, and reconstructed from, a set of instantaneous measurements or samples of its voltage which are made at equally-spaced times. The interval $T(=1/f_s)$ between such samples must be less than one-half the period of the highest-frequency component f_{MAX} in the signal
- In other words: you must sample at least twice the rate of the maximum frequency in your signal to prevent aliasing ($F_s \geq 2F_{MAX}$)
- The sampling rate $F_s = 2F_{MAX}$ is called the Nyquist rate

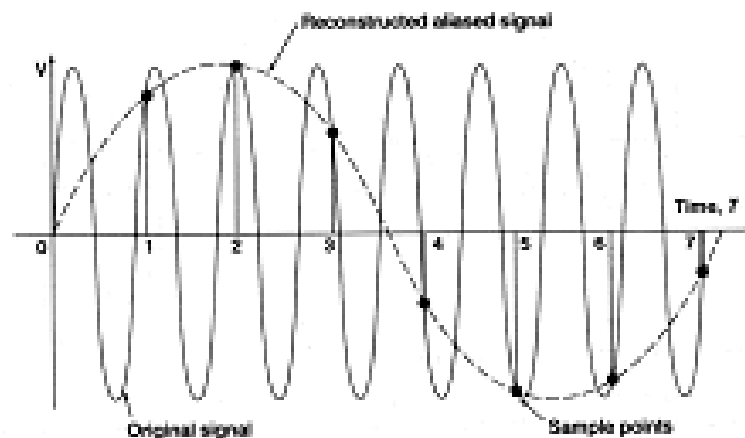

Anti-aliasing

- The effects of aliasing can also be observed on the frequency spectrum of the signal
- In the figures below
 - F_1 appears correctly since $F_1 \leq F_s/2$
 - F_2 , F_3 and F_4 have aliases at 30, 40 and 10Hz, respectively
 - You can compute these aliased frequencies by folding the spectrum around $F_s/2$ or with the expression

$$\text{Alias frequency } \hat{F} = \min |kF_s - F|_{k \text{ Integer}}$$

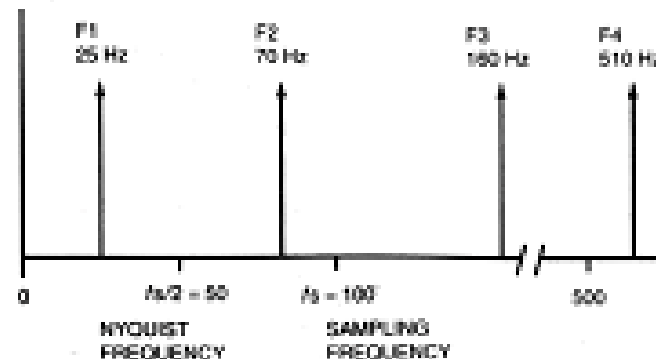


FIGURE 117.5 Spectral of signal with multiple frequencies.

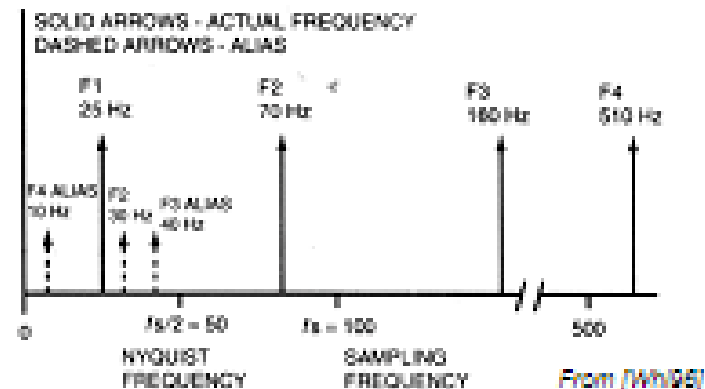


FIGURE 117.6 Spectral of signal with multiple frequencies after sampled at $f_s = 100$ Hz.

Anti-aliasing filters

- ▶ An anti-aliasing filter is a low-pass filter designed to filter out frequencies higher than the sampling frequency
 - An anti-aliasing filter should have
 - Steep cut-off and
 - Flat response in the frequency band
- ▶ Typical filters are:
 - Butterworth: flattest response in the frequency band but phase shifts well below the break frequency
 - Bessel: phase shift proportional to frequency, so the signal is not distorted by the filter
 - Recommended for anti-aliasing if it is important to preserve the waveform
 - Chebyshev: steepest cut-off but it has ripples in the band-pass

