

ENEE236 (CH10+ CH11)Homework Problems

13. Calculate the output voltages V_2 and V_3 in the circuit of Fig. 10.72.


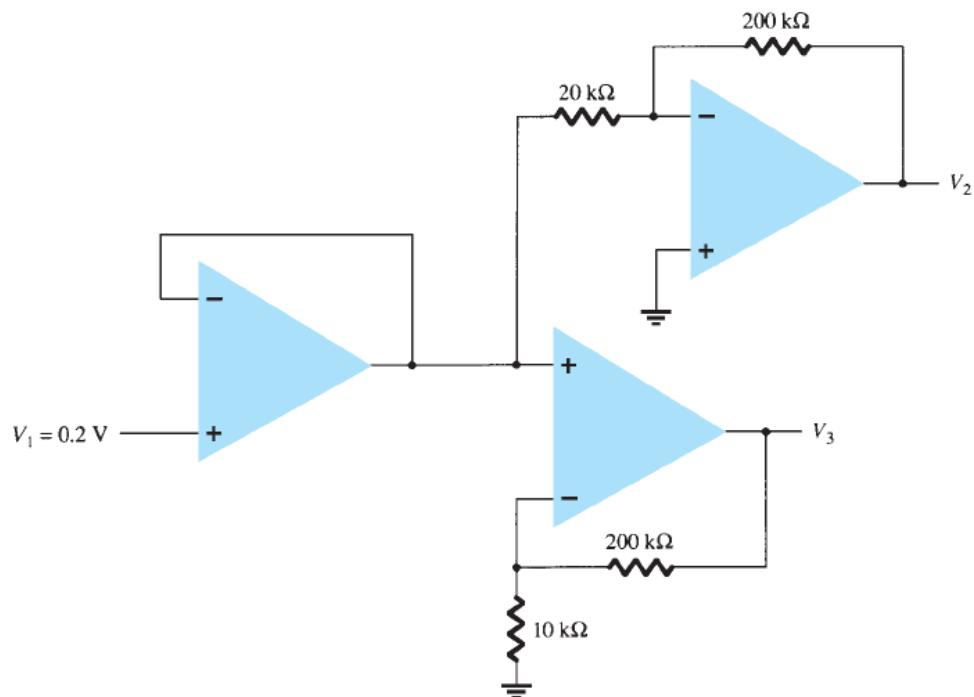



FIG. 10.72

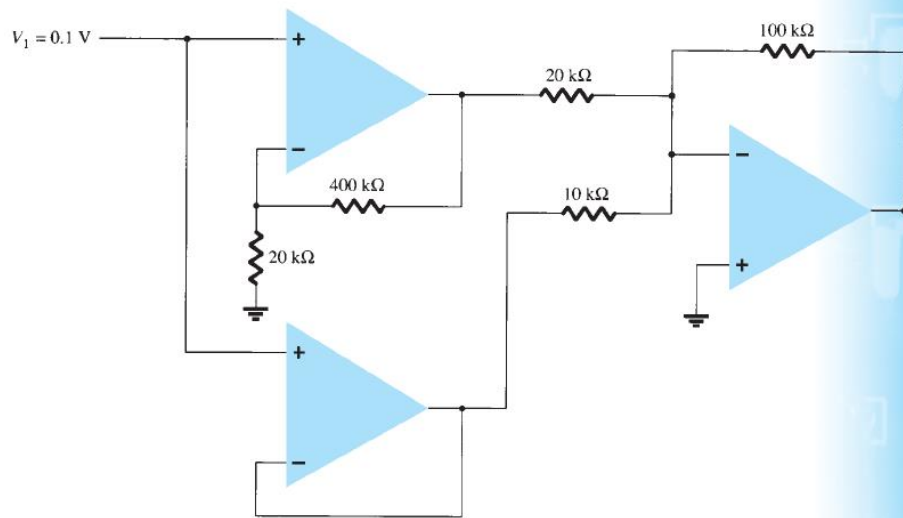14. Calculate the output voltage, V_o , in the circuit of Fig. 10.73.



11.5 Instrumentation Circuits

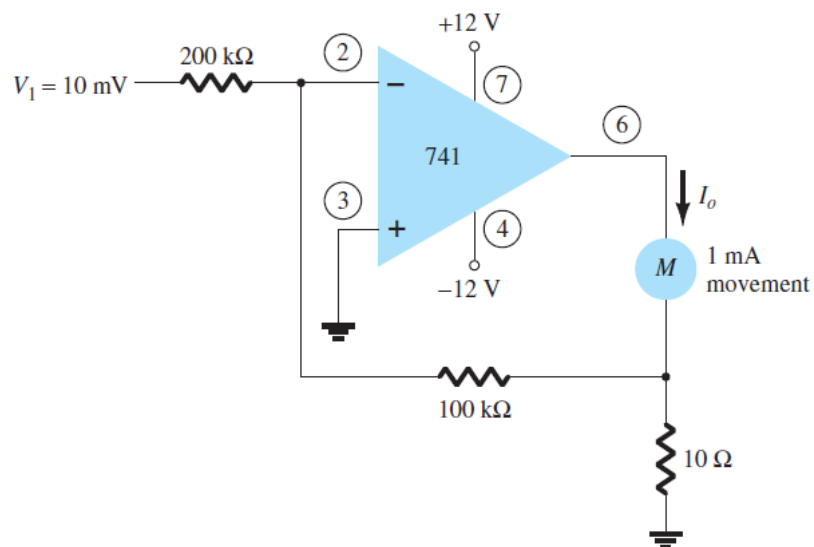13. Calculate the output current I_o in the circuit of Fig. 11.55.



*14. Calculate V_o in the circuit of Fig. 11.56.

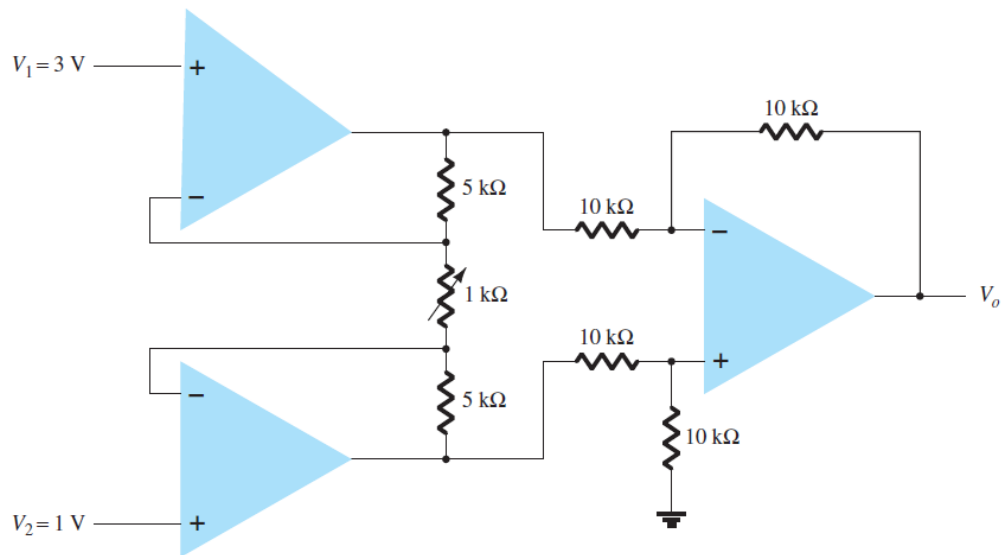


FIG. 11.56