

Negative Feedback

Negative Feedback

Advantages

- 1-Stabilizes the gain of the amplifier against parameters changes in the active devices due to temperature .
- 2- Modifies the input and output impedance in any desired fashion.
- 3- Increases the Bandwidth .

Disadvantages

- 1- Decreases the gain .
- 2- Oscillation .

Negative Feedback

General Feedback equation

$$S_o = A S_\epsilon$$


$$S_\epsilon = S_i - S_{fb}$$

$$A_f = \frac{S_o}{S_i} = \frac{A}{1+AB}$$

$AB \equiv$ Loop gain

If $AB \gg 1$

$$\therefore A_f = \frac{1}{B}$$

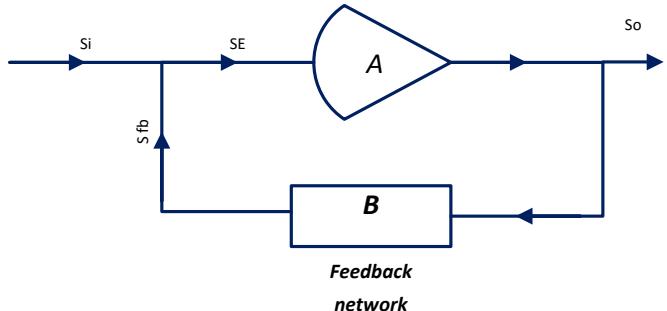

Negative Feedback

General Feedback equation

$$S_\epsilon = S_i - S_{fb}$$


$$S_\epsilon = S_i - BS_o$$

$$S_\epsilon = S_i - B \frac{A}{1+AB} S_i$$

$$S_\epsilon = S_i \left(1 - \frac{AB}{1+AB}\right)$$

If $AB \gg 1$
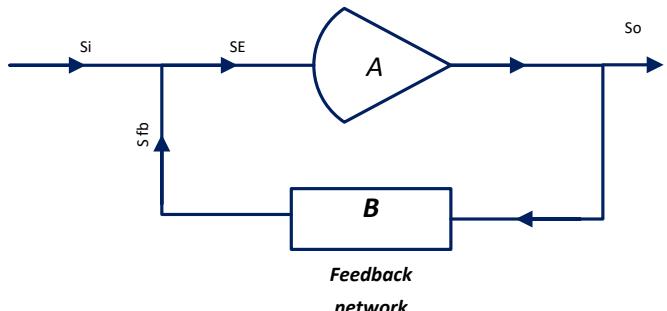
$$S_\epsilon \approx S_i \left(1 - \frac{AB}{AB}\right) \approx 0$$



Negative Feedback

Gain stabilization

$$\text{let } A = 10,000$$

$$B = 0.01$$

$$\therefore AB = 100$$

$$Af = \frac{A}{1 + AB} = 99$$

$$\text{let } A = 9000$$


$$B = 0.01$$

$$\therefore AB = 90$$

$$Af = \frac{A}{1 + AB} = 98.9$$

Change in A → change in Af

$$10\% \rightarrow 0.1\%$$

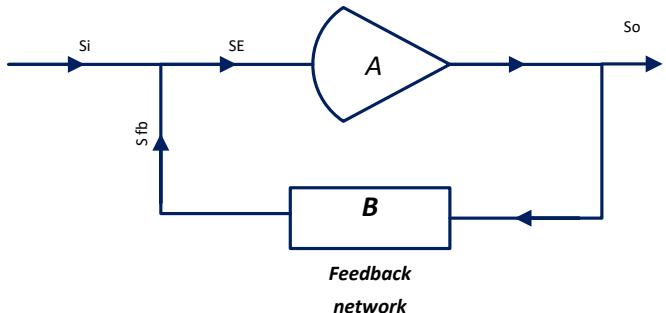

Negative Feedback

Increasing the Bandwidth.

In high frequency

$$A(jw) = \frac{Am}{1 + \frac{jw}{w_2}}$$

$$\therefore wH = w_2$$

With Negative Feedback

$$Af(jw) = \frac{Am}{1 + AmB} = \frac{1}{1 + \frac{jw}{w_2(1 + AmB)}}$$

$$\therefore wH = w_2(1 + AmB)$$

Types Of Negative Feedback1) Series – Shunt Feedback

$$V_o = A V_e$$


$$V_e = V_i - V_{fb}$$

$$V_{fb} = B V_o$$

$$\therefore \frac{V_o}{V_i} = \frac{A}{1 + AB} = A_f$$

$$Z_{if} = \frac{V_i}{i_i}$$

$$\begin{aligned} V_i &= V_e + V_{fb} \\ &= R_i i_i + B V_o \\ &= R_i i_i + B A V_e \\ &= R_i i_i + B A R_i i_i \end{aligned}$$

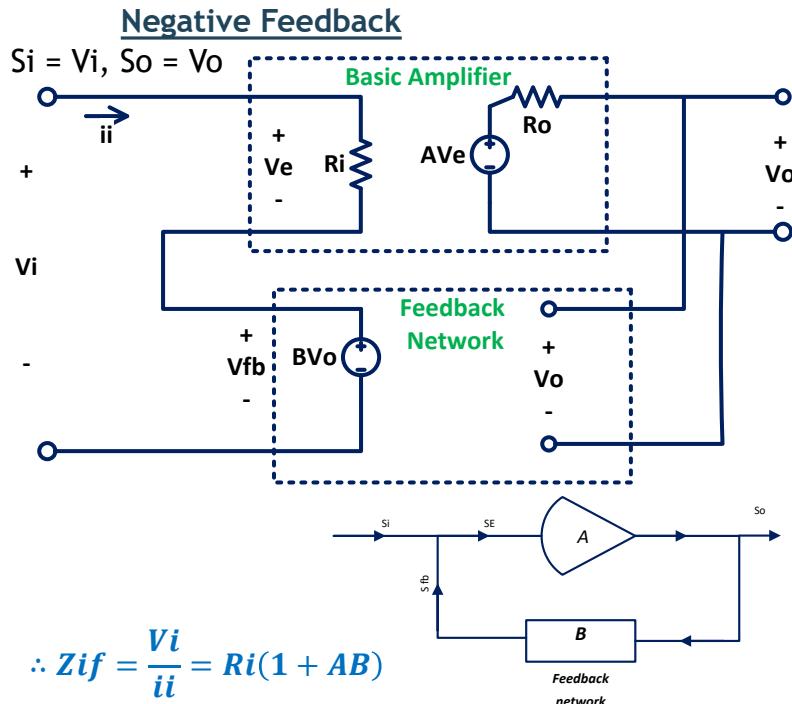1) Series – Shunt Feedback


$$Z_{of} = \frac{V_x}{i_x} \Big|_{V_i = 0}$$

$$i_x = \frac{V_x - A V_e}{R_o}$$

$$V_e = -B V_x$$

$$i_x = \frac{V_x + AB V_x}{R_o}$$

$$\therefore \frac{V_x}{i_x} = \frac{R_o}{1 + AB}$$

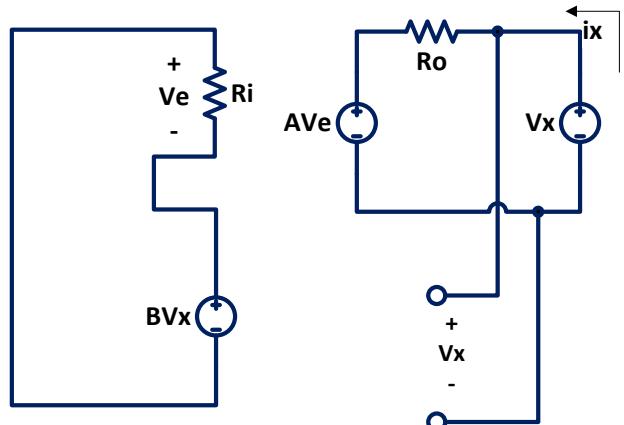Negative Feedback

Series Feedback at the input always raises the input impedance by $(1+AB)$

shunt Feedback at the output always lowers the output impedance by $(1+AB)$

Negative Feedback


1) Series – Shunt Feedback

Equivalent ckt of Series - shunt amplifier

$$Zif = (1+AB) Ri$$

$$Zof = \frac{Ro}{1+AB}$$

$$Af = \frac{A}{1+AB} = \frac{Vo}{Vi}$$

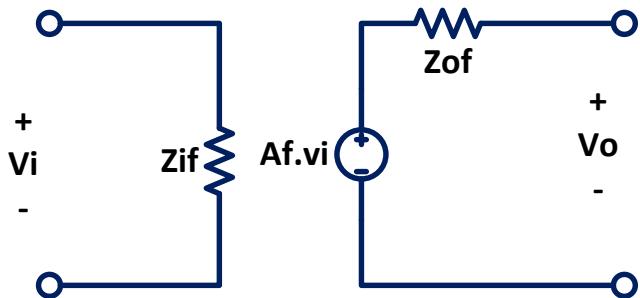

1) Series – Shunt Feedback

Negative Feedback





Equivalent ckt of Series shunt amplifier

If $A \rightarrow \infty$;

$$Zif = \infty ;$$

$$Zof = 0 ;$$

$$Af = \frac{1}{B}$$

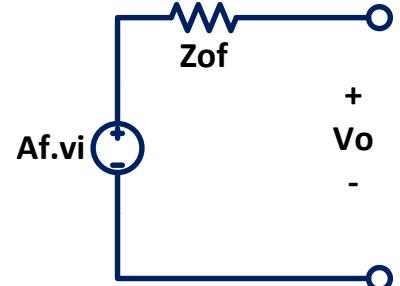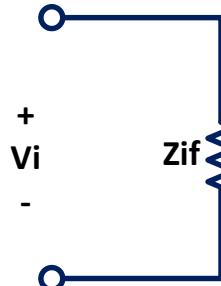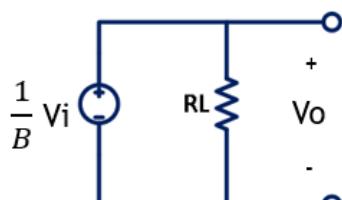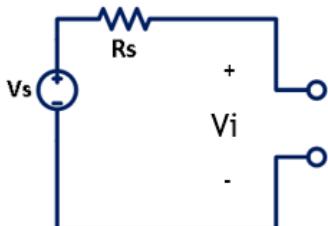

$$Zif = (1+AB) Ri$$

$$Zof = \frac{Ro}{1+AB}$$

$$Af = \frac{A}{1+AB} = \frac{Vo}{Vi}$$



Negative Feedback1) Series – Shunt FeedbackEquivalent ckt of Series shunt amplifier

If we have R_s and R_L

$$V_o = \frac{1}{B} V_i$$

$$V_i = V_s$$

$$\therefore \frac{V_o}{V_s} = \frac{1}{B}$$

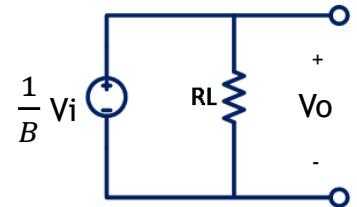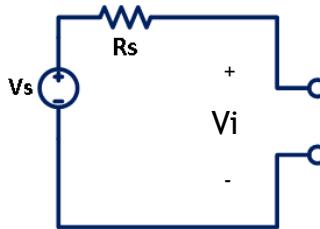2) Shunt - Shunt Feedback

$$S_i = i_i, S_o = V_o$$

Negative Feedback

$$V_o = A i_e$$

$$i_e = i_i - i_{fb}$$




$$i_{fb} = B V_o$$

$$V_o = A(i_i - B V_o)$$

$$\therefore \frac{V_o}{i_i} = A f = \frac{A}{1 + AB}$$

$$A = \frac{V_o}{i_e}$$

$$B = \frac{i_{fb}}{V_o}$$

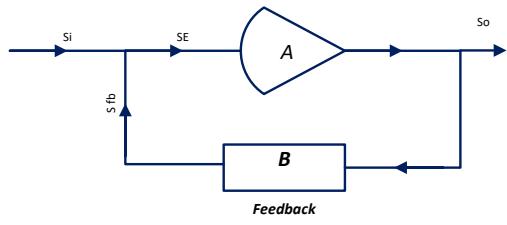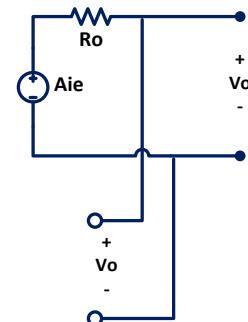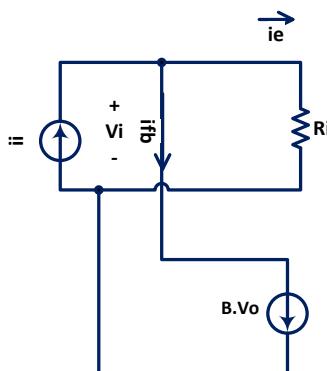

AB is dimensionless

2) Shunt - Shunt FeedbackNegative FeedbackThe input impedance

$$Z_{if} = \frac{Vi}{ii}$$



$$Vi = Ri ie$$

$$ie = ii - ifb$$

$$ifb = BVo$$

$$Vo = \frac{A}{1+AB} ii$$

$$\therefore Z_{if} = \frac{Ri}{1+AB}$$

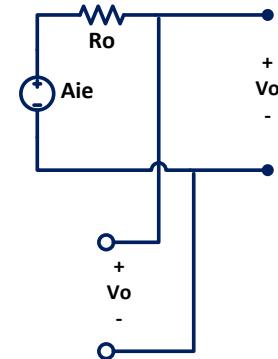
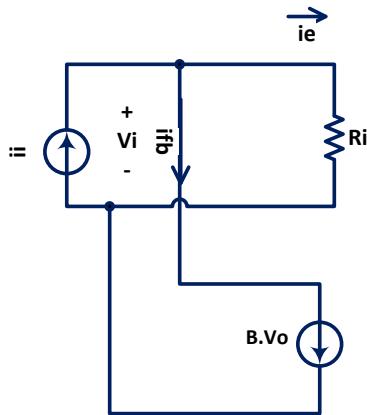
The output impedance

► it is easy to show

$$Z_{of} = \frac{Ro}{1+AB}$$

► using :

$$Z_{of} = \frac{Vt}{it} | ii = 0$$


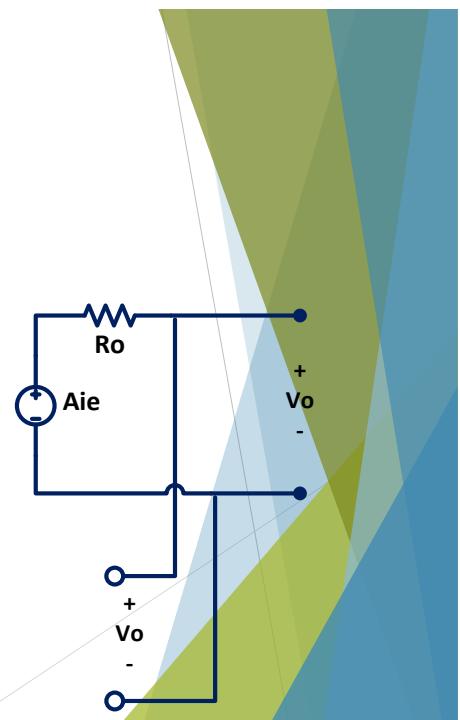
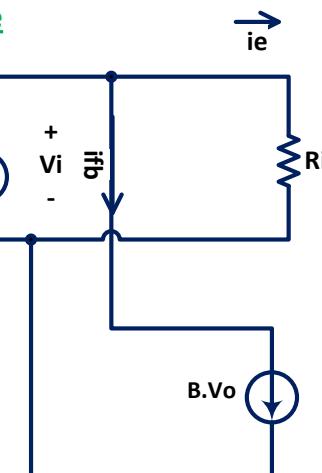


Negative Feedback2) Shunt - Shunt FeedbackEquivalent ckt of Shunt Shunt amplifierIf $A \rightarrow \infty$;

$$Zif = 0$$

$$Zof = 0$$

$$Af = \frac{1}{B}$$

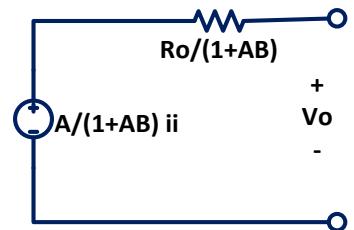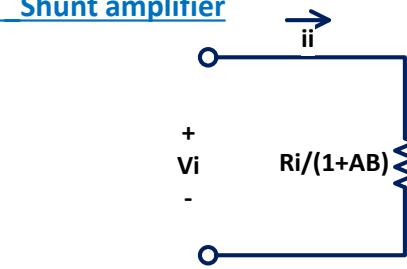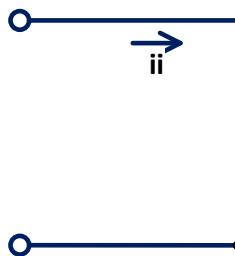

$$Zif = \frac{Ri}{1 + AB}$$

$$Zof = \frac{Ro}{1 + AB}$$





$$Af = \frac{A}{1 + AB}$$

Negative Feedback2) Shunt - Shunt FeedbackEquivalent ckt of Shunt Shunt amplifierIf we have R_s and R_L

$$Vo = \frac{1}{B} ii$$

$$ii = is$$

$$\frac{Vo}{is} = \frac{1}{B}$$

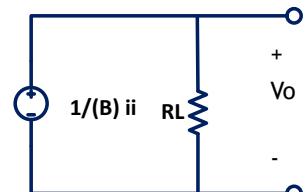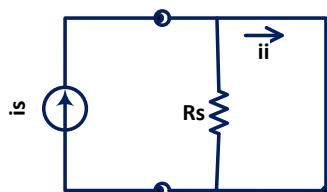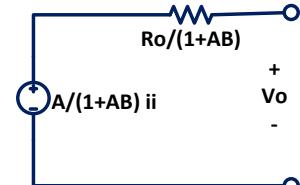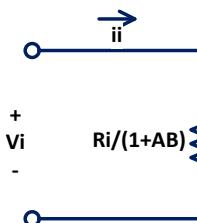

3) Shunt - Series Feedback

$$io = Aie \frac{Ro}{Ro + Zl}$$

if $Zl \ll Ro$

$$io = A ie$$


$$ie = ii - ifb$$

$$ifb = B io$$

$$\therefore \frac{io}{ii} = Af = \frac{A}{1 + AB}$$

Negative Feedback

$$Si = ii, So = io$$

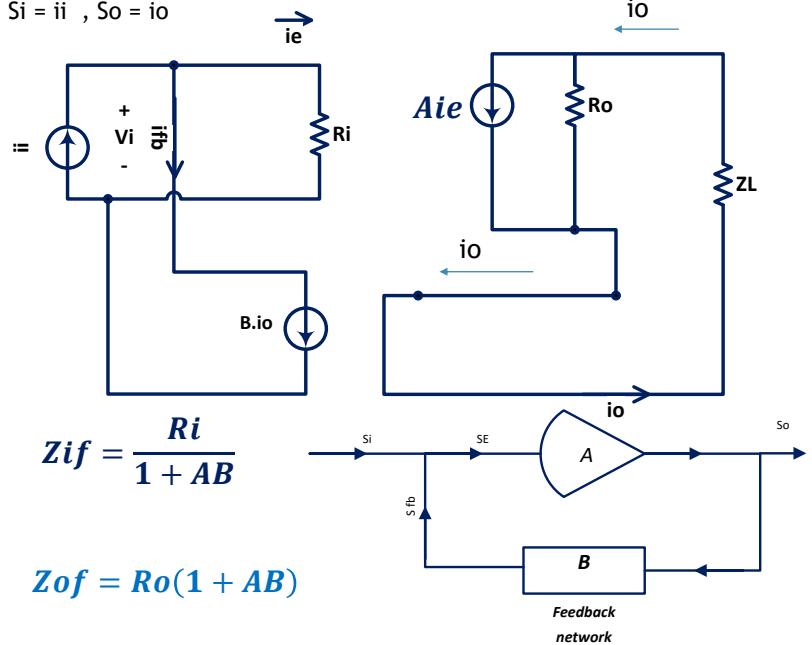

$$Zof = Ro(1 + AB)$$

Negative Feedback4) Series - Series Feedback


$$Si = Vi, So = io$$

if $Zl \ll Ro$

$$\frac{io}{Vi} = Af = \frac{A}{1 + AB}$$

$$Zif = Ri(1 + AB)$$

$$Zof = Ro(1 + AB)$$

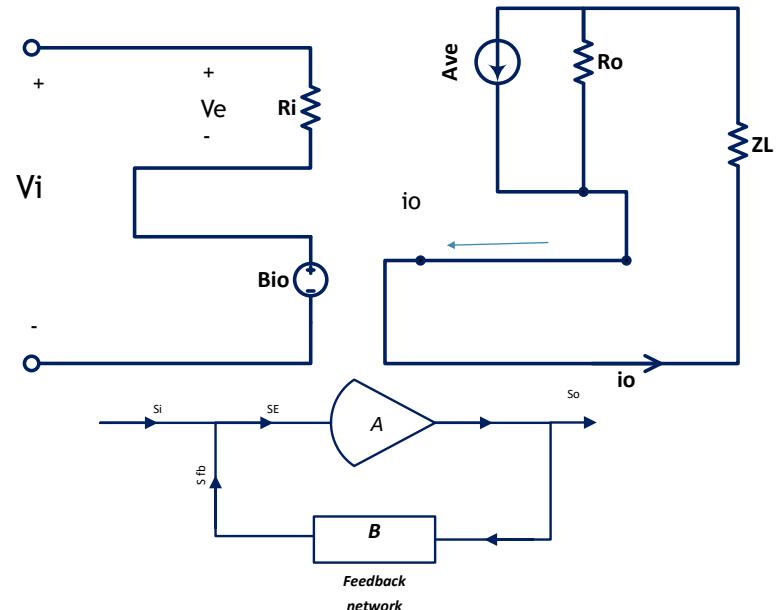

Negative Feedback

Practical configuration and the effect of loading

1) Shunt - Shunt Feedback


$$S_i = i_s$$

$$S_o = V_o$$


$$A_f = \frac{V_o}{i_s} = \frac{A}{1 + AB}$$

$$|Y_{12a}| \ll |Y_{12f}|$$

$$|Y_{21a}| \gg |Y_{21f}|$$

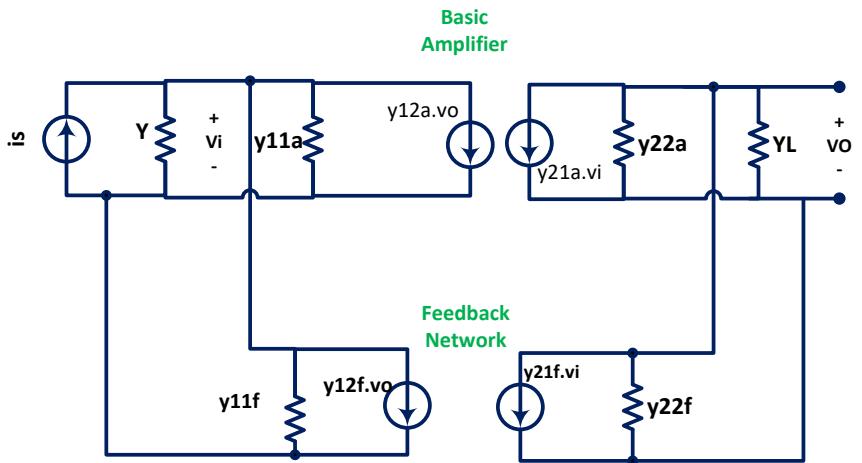

1) Shunt - Shunt Feedback

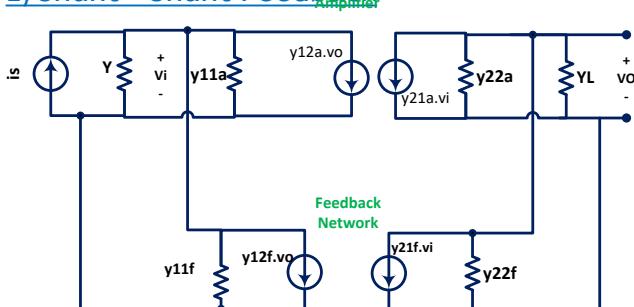


New basic amplifier =
basic amplifier + loading

New basic amplifier

$$Y_{11} = y_{11a} + y_{11f} + Y$$

$$Y_{22} = y_{22a} + y_{22f} + Y_L$$

$$\therefore y_{12f} = B$$

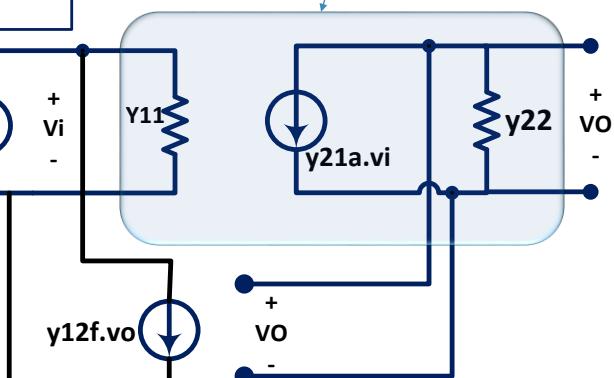


Negative Feedback

Practical configuration and the effect of loading

1) Shunt - Shunt Feedback

Example:

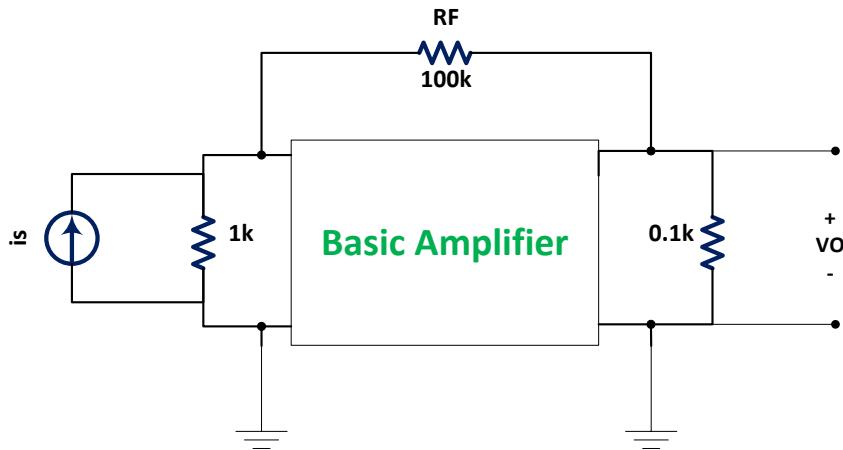



Negative Feedback

Practical configuration and the effect of loading


1) Shunt - Shunt Feedback

Example:

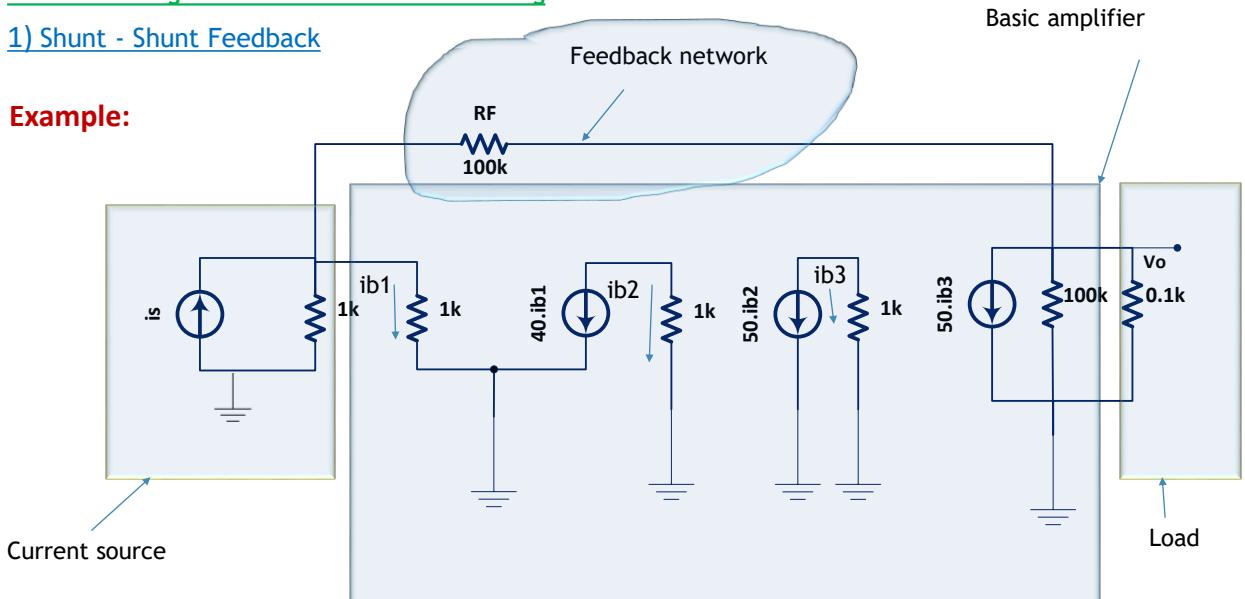

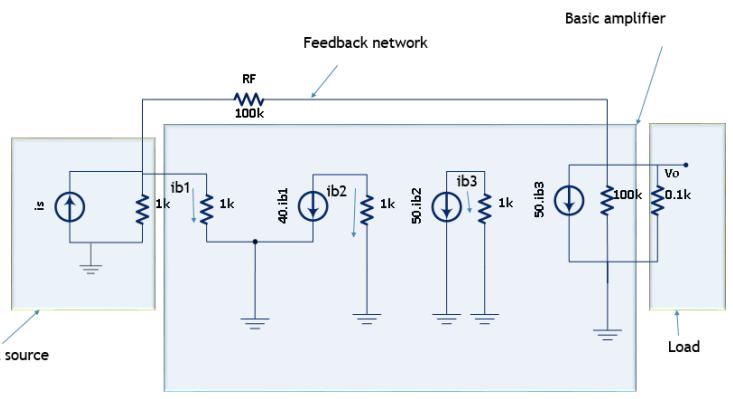1) Shunt - Shunt Feedback


$$\text{New Basic Amplifier: } A = \frac{V_o}{i_s}$$

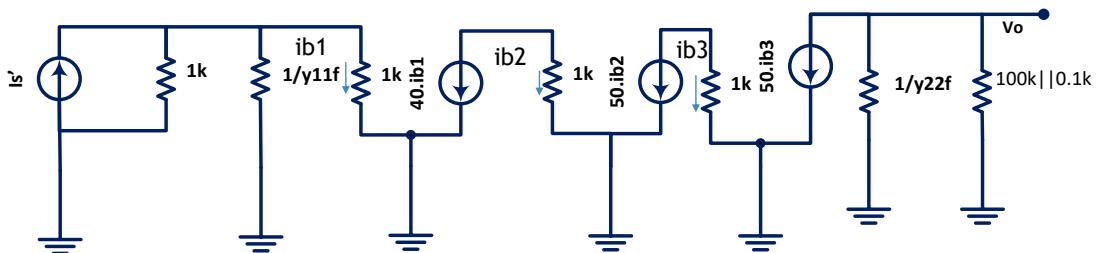Negative FeedbackPractical configuration and the effect of loading1) Shunt - Shunt Feedback**The Feedback network**


$$y_{11} = \frac{1}{RF} = \frac{1}{100k}$$

$$y_{22} = \frac{1}{RF} = \frac{1}{100k}$$
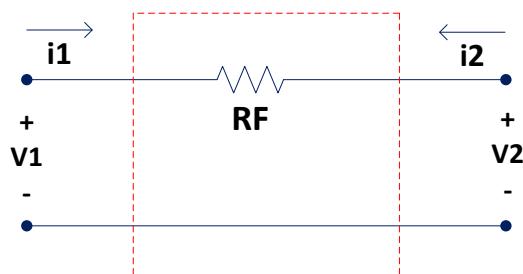
$$y_{12} = \frac{-1}{RF} = \frac{-1}{100k}$$



$$B = y_{12} f$$

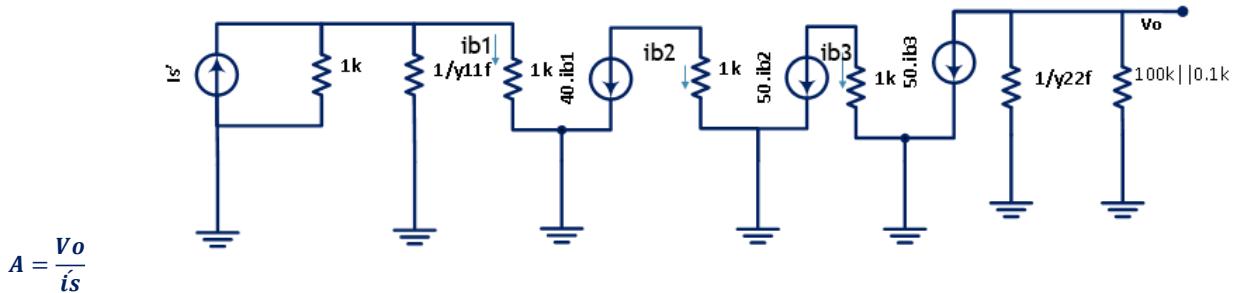Negative Feedback1) Shunt - Shunt Feedback**To calculate A : New basic amplifier**


$$A = \frac{v_o}{i_s}$$

$$ib_2 = -40ib_1$$



$$v_o = -50ib_3 \left(100k \parallel 0.1K \parallel \frac{1}{y_{22}f} \right)$$

$$ib_3 = -50ib_2$$
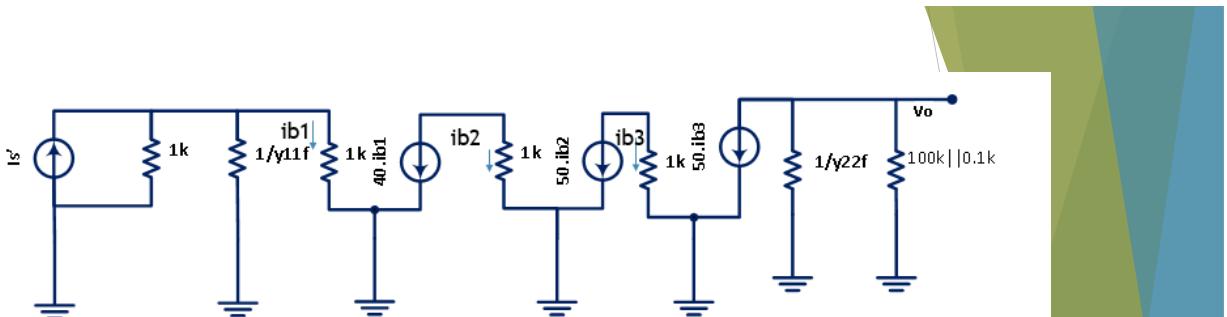
$$ib_1 = i_s \frac{\frac{1}{K} \parallel \frac{1}{y_{11}f}}{1k \parallel \frac{1}{y_{11}f} + 1k}$$



- ▶ $\therefore A = -4965 k\Omega$
- ▶ $B = -0.01 mV$
- ▶ $AB = 49.65$
- ▶ $A_f = \frac{v_o}{i_s} = \frac{A}{1+AB} = -98K\Omega$
- ▶ $\frac{1}{B} = -100k\Omega$

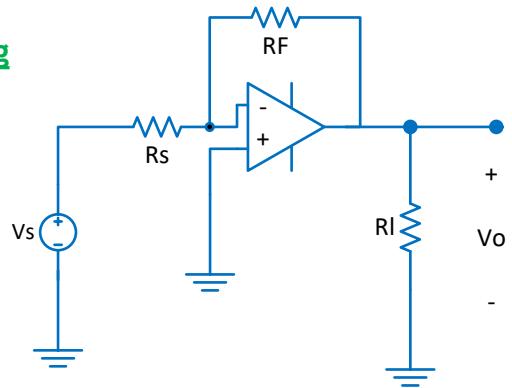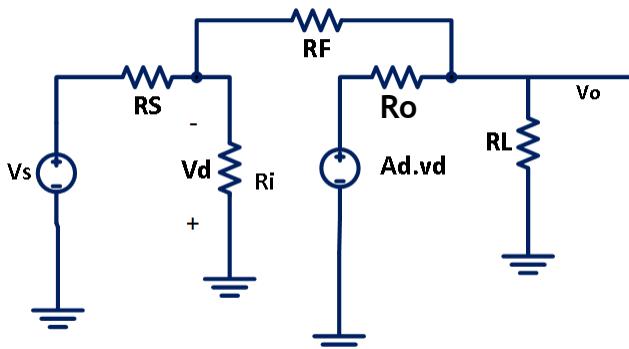Negative FeedbackPractical configuration and the effect of loading1) Shunt - Shunt Feedback**Example: Inverting Amplifier**


$$\begin{aligned}
 R_s &= 100k\Omega \\
 R_f &= 1M\Omega \\
 R_l &= 10k\Omega \\
 R_o &= 75 \Omega \\
 R_i &= 2 M\Omega \\
 A_d &= 200,000
 \end{aligned}$$

Negative FeedbackPractical configuration and the effect of loading1) Shunt - Shunt Feedback**The Feed-Back Network:**

$$y_{11} f = \frac{1}{R_F};$$

$$y_{22} f = \frac{1}{R_F}$$

$$y_{12} f = -\frac{1}{R_F} = \beta$$

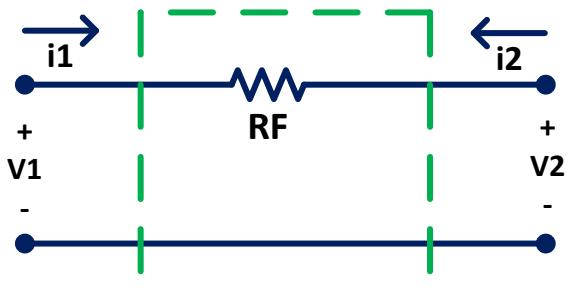




Practical configuration and the effect of load1) Shunt - Shunt Feedback

$$\text{New Basic Amplifier : } A = \frac{V_o}{i_s}$$

$$V_o = \frac{R_l || \frac{1}{y_{22}f}}{R_l || \frac{1}{y_{22}f} + R_o} AdV_d$$

$$V_d = -i_s'(R_s || \frac{1}{y_{11}f} || R_i)$$
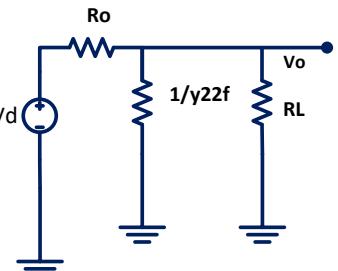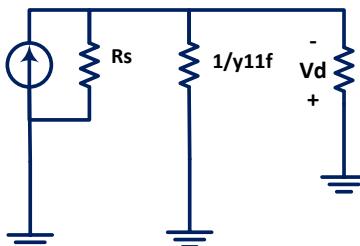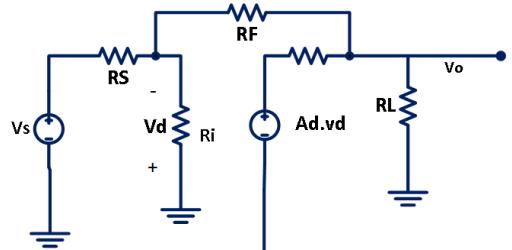
$$A = \frac{V_o}{i_s} = -1.726 \times 10^{10}$$



$$B = \frac{-1}{RF} = -1 \times 10^{-6}$$

$$AB = 17260$$

$$Af = \frac{V_o}{i_s} = \frac{A}{1 + AB} = -999.94k \Omega$$

$$\text{To find } Av = \frac{V_o}{V_s}$$

$$\frac{V_o}{V_s} = \frac{V_o}{i_s} \cdot \frac{i_s}{V_s} = Af \cdot \frac{1}{R_s}$$

$$Av = -9.9994$$

If the Op.amp is ideal

$$Av = -\frac{RF}{RS} = -10$$



Negative FeedbackPractical configuration and the effect of loading2) Series - Shunt Feedback

$$V_1 = h_{11}i_1 + h_{12}V_2$$


$$i_2 = h_{21}i_1 + h_{22}V_2$$

$$|h_{12a}| \ll |h_{12f}|;$$

$$|h_{21a}| \gg |h_{21f}|;$$

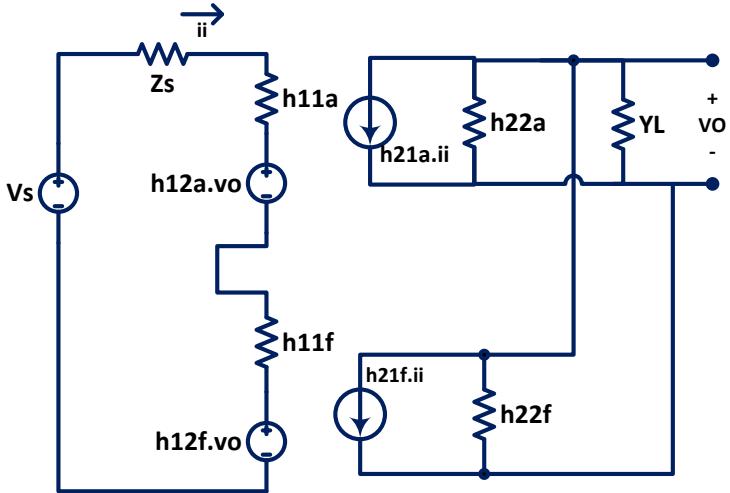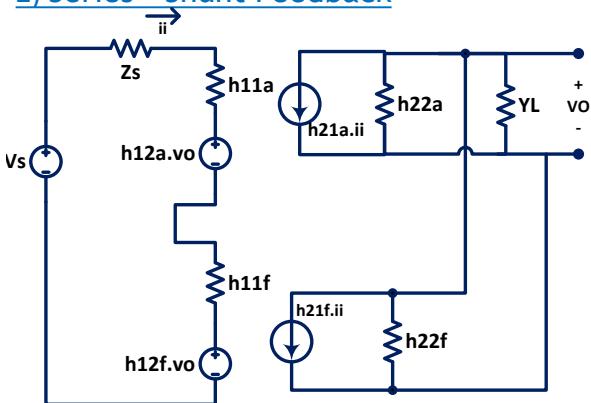
2) Series - Shunt Feedback

The new basic amplifier

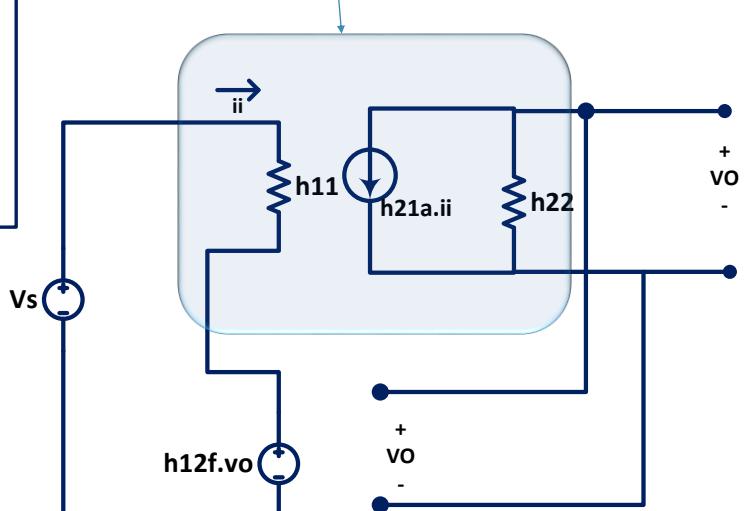

$$B = h_{12f};$$


$$Af = \frac{V_o}{V_s} = \frac{A}{1 + AB}$$

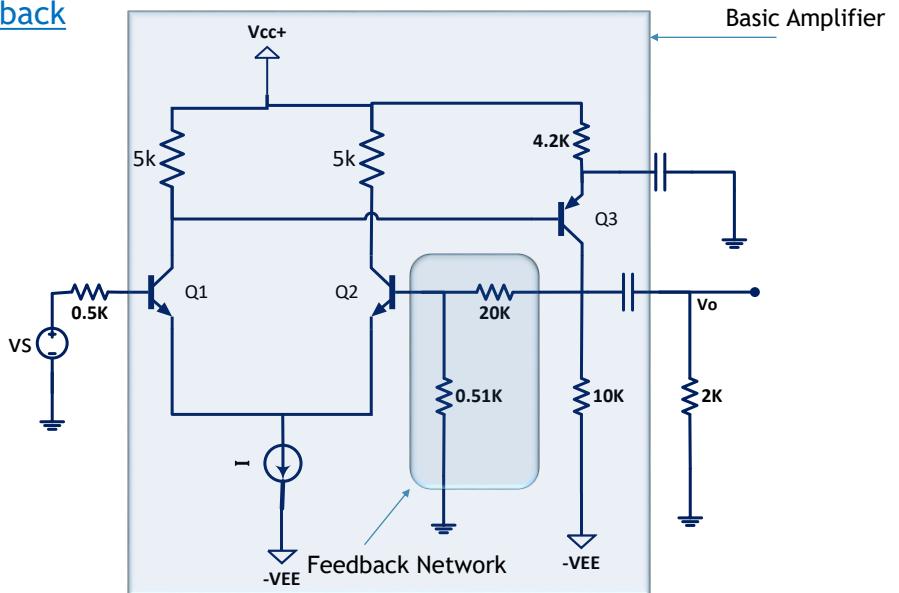Negative FeedbackPractical configuration and the effect of loading2) Series - Shunt Feedback**Example:**Negative FeedbackPractical configuration and the effect of loading2) Series - Shunt Feedback**Example:**

$$h_{11f} = 0.51 \parallel 20k$$

$$h_{22f} = \frac{1}{20k + 0.51k}$$


$$h_{12f} = \frac{0.51k}{0.51k + 20k} = B$$

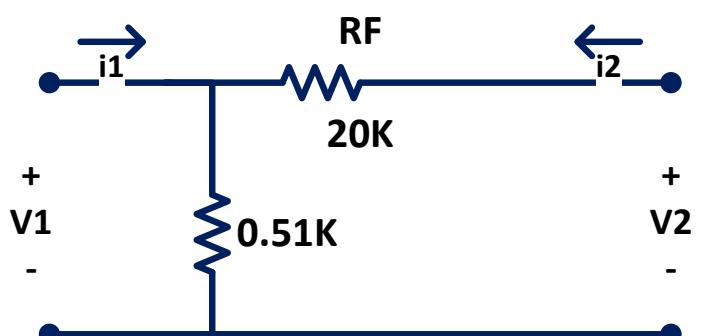The Feed-Back Network:


Practical configuration and the effect of loading

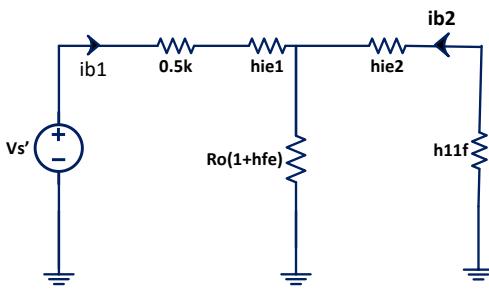2) Series - Shunt Feedback

$$\text{New Basic Amplifier : } A = \frac{V_o}{V_s}$$



$$hfe = 100, hie = 3k$$

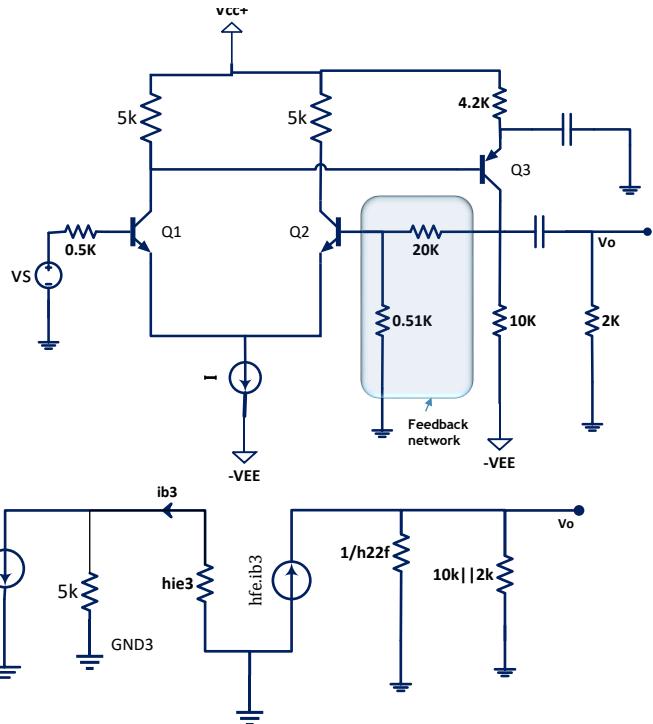Negative FeedbackPractical configuration and the effect of loading

2) Series - Shunt Feedback



Differential Mode Analysis:

$$V_o = hfe \cdot i_b3 \left(\frac{1}{h_{22f}} || 10k || 2k \right)$$

$$i_b3 = hfe \cdot i_b1 \frac{5k}{5k + 3k}$$

$$i_b1 = -i_b2$$
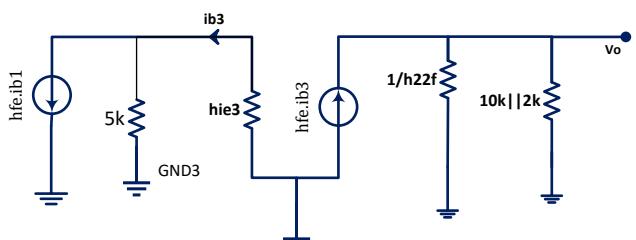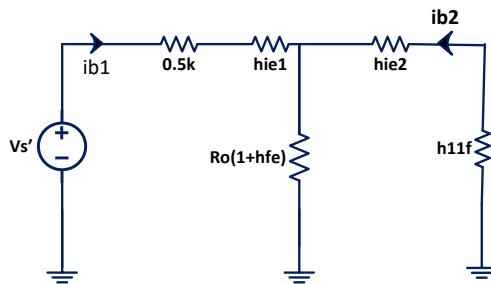
$$i_b1 = \frac{V_s}{0.5k + hie1 + hie2 + h11f}$$



$$\blacktriangleright A = \frac{V_o}{V_s} = 1379$$



$$\blacktriangleright AB = 34.3$$


$$\blacktriangleright Af = \frac{V_o}{V_s} = \frac{A}{1+AB} = 39$$

$$\blacktriangleright \frac{1}{B} = 40.2$$

2) Series - Shunt Feedback

Example: Non-Inverting Amplifier

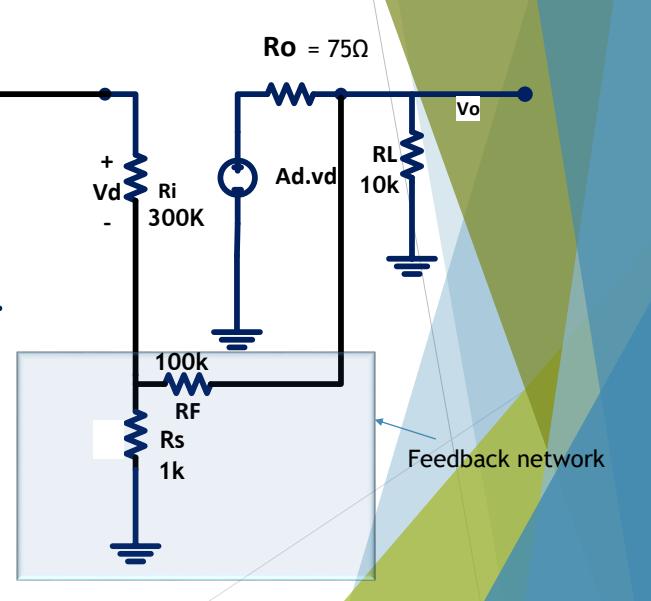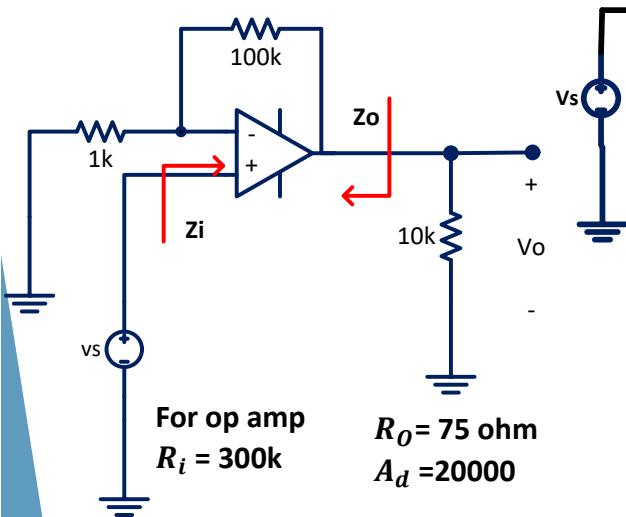


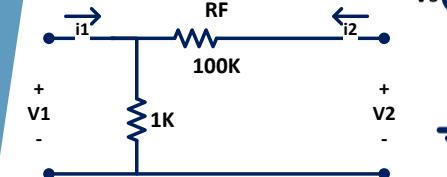Negative FeedbackPractical configuration and the effect of loading2) Series - Shunt Feedback**Example: Non-Inverting Am****The Feed-Back Network:**

$$h_{11f} = 100k \parallel 1k$$

$$h_{22f} = \frac{1}{1k + 100k}$$

$$h_{12f} = \frac{1}{1k + 100k} = B$$

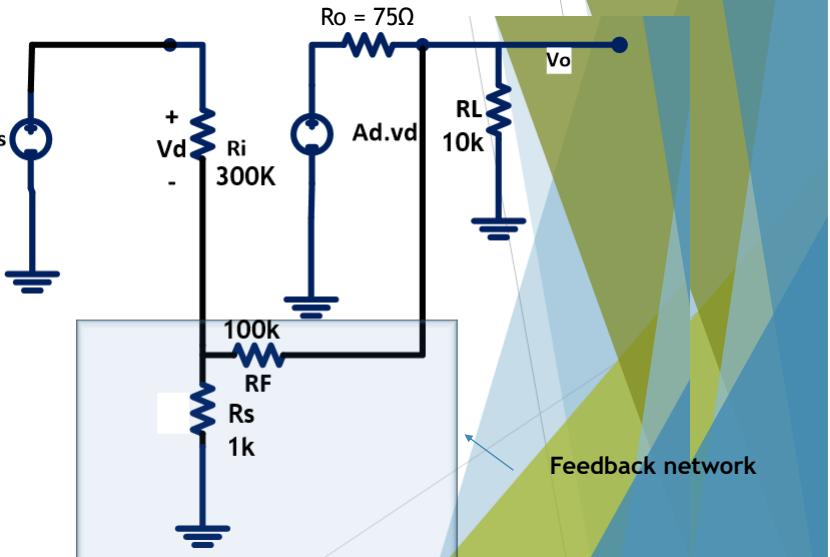2) Series - Shunt Feedback**Example: Non-Inverting Amplifier**



$$A = \frac{V_o}{V_s}$$

$$V_o = \frac{\left(10k \parallel \frac{1}{h_{22f}}\right)(20000 V_d)}{\left(10k \parallel \frac{1}{h_{22f}}\right) + 75}$$

$$V_d = \frac{300k}{300k + h_{11f}} V_s$$

$$A = 19771$$

$$AB = 195.75$$

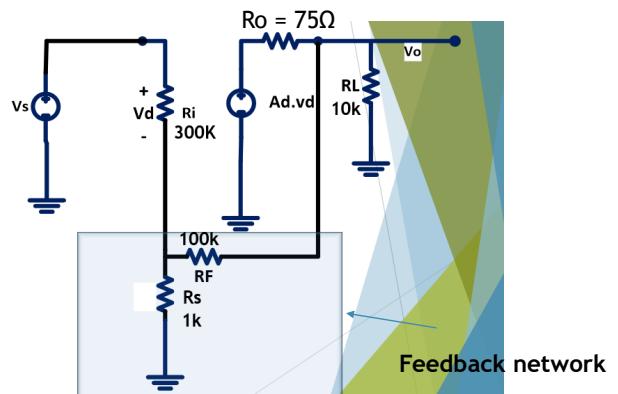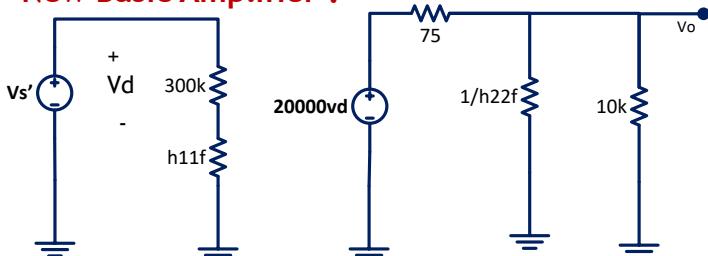**New Basic Amplifier :**

$$\blacktriangleright Af = \frac{V_o}{V_s} = \frac{A}{1+AB} = 100.487$$


$$\blacktriangleright \frac{1}{B} = 101$$

If the op amp is ideal $\therefore A_v = (1+R_f/R_s) = 101$

$$Z_{if} = R_i(1 + AB);$$

$$R_i = 300k + h_{11f}$$

$$\therefore Z_{if} = 59.221M\Omega$$

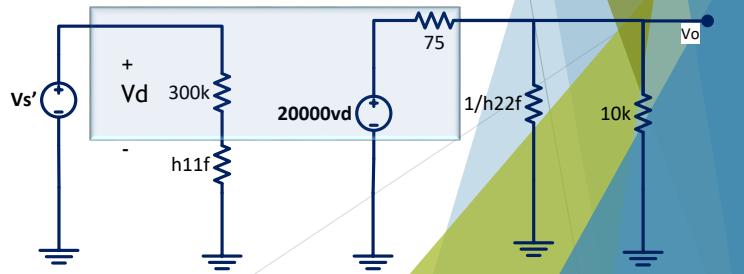

2) Series - Shunt Feedback

Negative Feedback

Example: Non-Inverting Amplifier

$$Z_{of} = \frac{R_o}{1 + AB}$$

$$R_o = 10k | 101k | 75$$


$$R_o = 74.4 \Omega$$

$$\therefore Z_{of} = 0.377 \Omega$$

$$Z_{of} = Z_o | 10k$$

$$\therefore Z_o = 0.378 \Omega$$

New Basic Amplifier

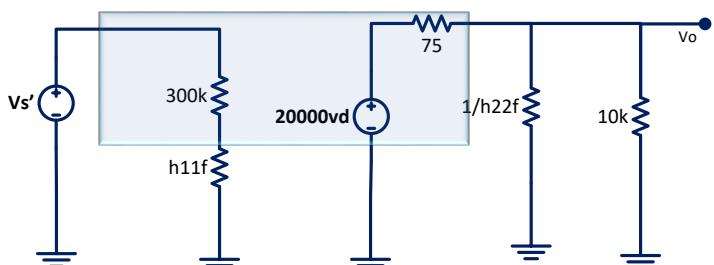

Negative Feedback

Practical configuration and the effect of loading


3) Shunt - Series Feedback

$$i_1 = g_{11}V_1 + g_{12}i_2$$


$$V_2 = g_{21}V_1 + g_{22}i_2$$

$$|g_{12f}| \gg |g_{12a}|;$$


$$|g_{21a}| \gg |g_{21f}|$$

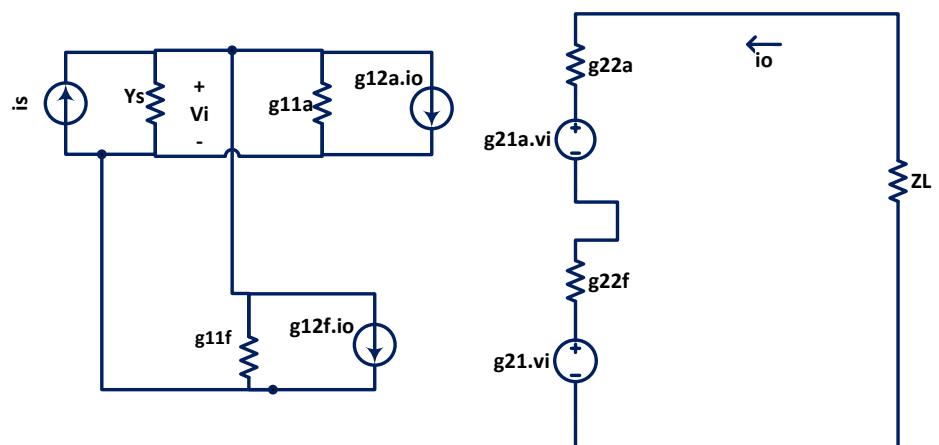

3) Shunt - Series Feedback

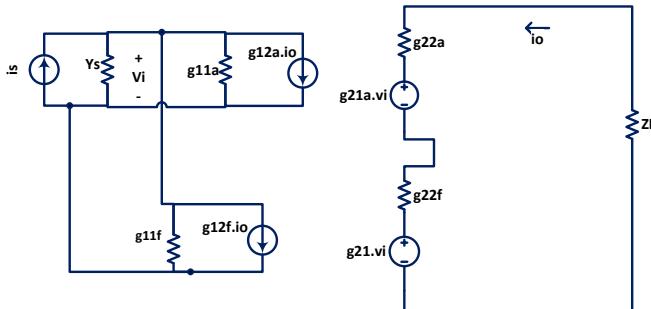

The new basic amplifier

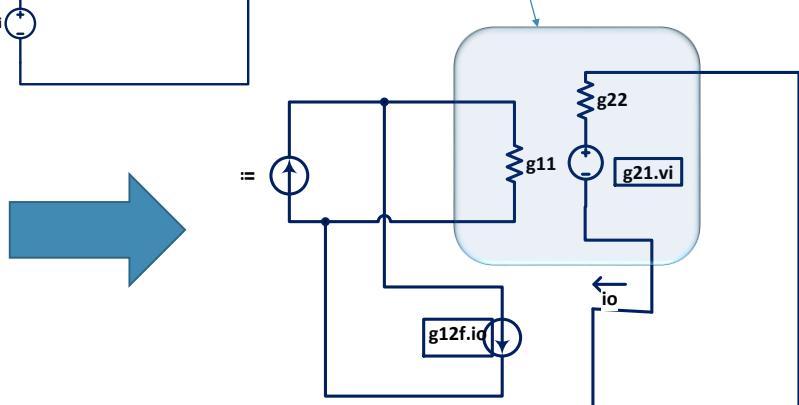

Negative Feedback

3) Shunt - Series Feedback


Example:

$$R1||R2 = 24k$$

$$hfe = 50$$

$$hie1 = 1.3k ;$$

$$hie2 = 1k$$

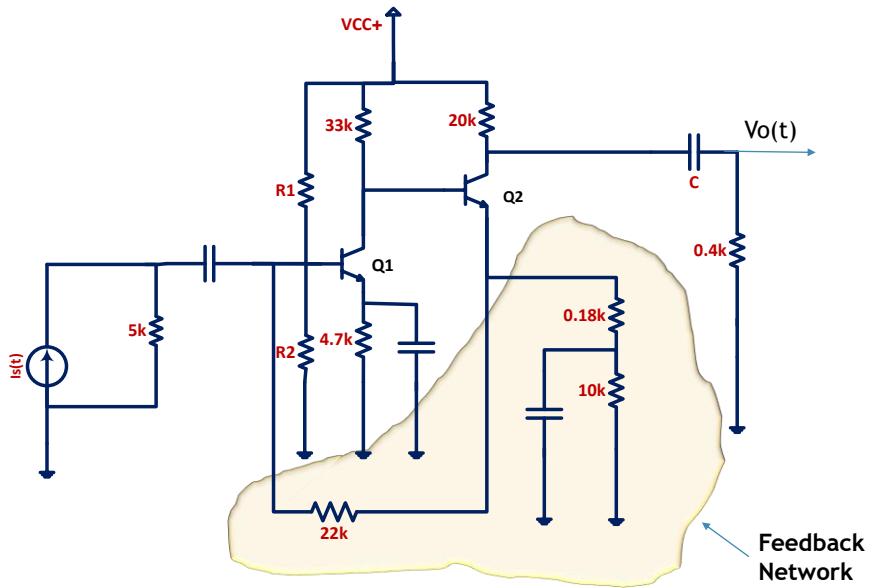Negative FeedbackPractical configuration and the effect of loading


3) Shunt - Series Feedback



Example:**The Feed-Back Network:**

$$g_{11f} = \frac{1}{22k + 0.18k}$$


$$g_{22f} = 22k || 0.18k$$
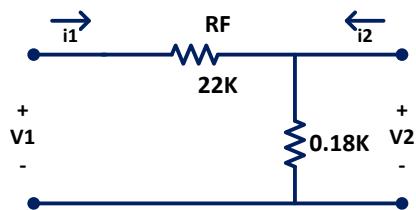
$$g_{12f} = -\frac{0.18k}{0.18k + 22k} = B$$



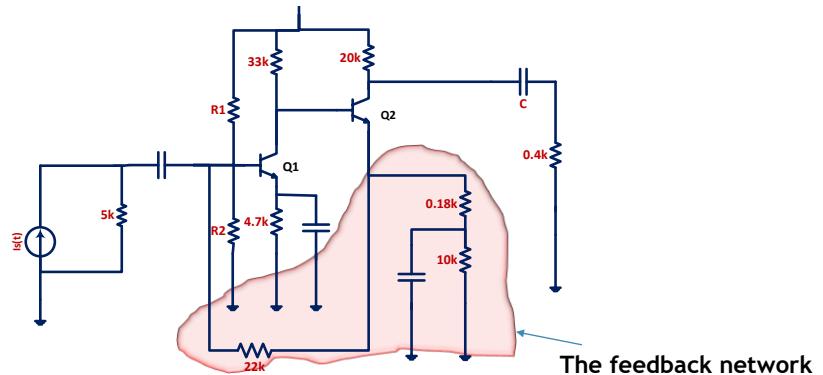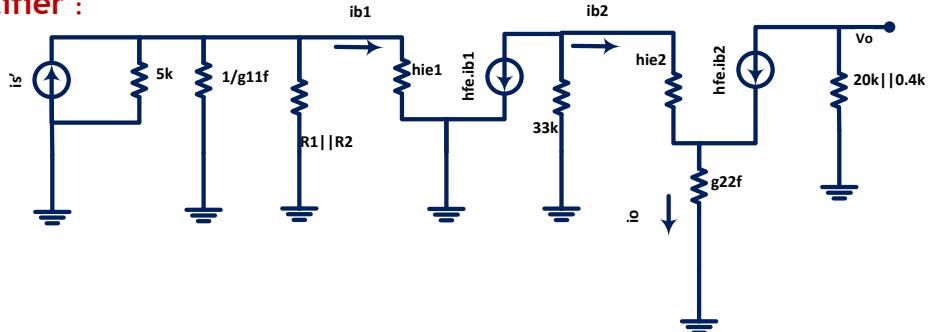3) Shunt - Series Feedback**Example:****New Basic Amplifier :**Negative FeedbackPractical configuration and the effect of loading3) Shunt - Series Feedback**Example:**

$$A = \frac{i_o}{i_s'}$$

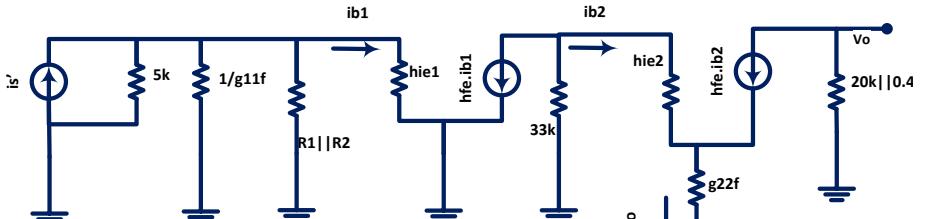

$$i_o = (1 + hfe)ib_2$$

$$ib_2 = -hfe ib_1 \frac{33k}{33k + hie_2 + g_{22f}(1 + hfe)}$$

$$A = -1429$$

$$ib_1 = i_s' \frac{5k || \frac{1}{g_{11f}} || R_1 || R_2}{5k || \frac{1}{g_{11f}} || R_1 || R_2 + hie_1}$$

$$AB = 11.5$$

$$Af = \frac{i_o}{i_s} = \frac{A}{1 + AB} = -113.45$$

Negative FeedbackPractical configuration and the effect of loading


4) Series - Series Feedback

$$V_1 = Z_{11} i_1 + Z_{12} i_2$$


$$V_2 = Z_{21} i_1 + Z_{22} i_2$$

$$|Z_{12f}| \gg |Z_{12a}|$$

$$|Z_{21a}| \gg |Z_{21f}|$$

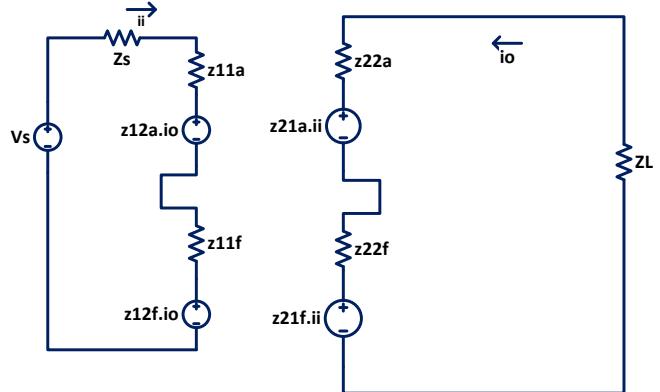


4) Series - Series Feedback

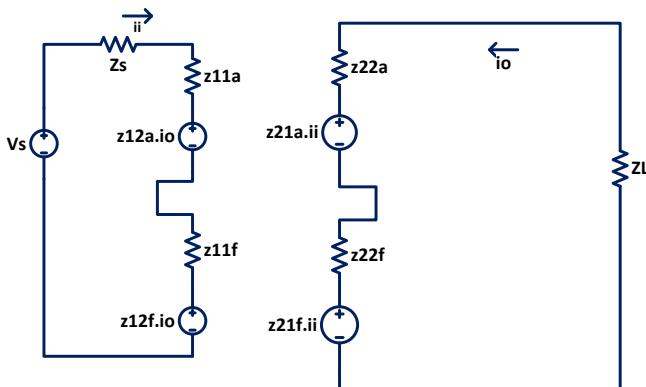

The new basic amplifier

$$Z_{12f} = B$$

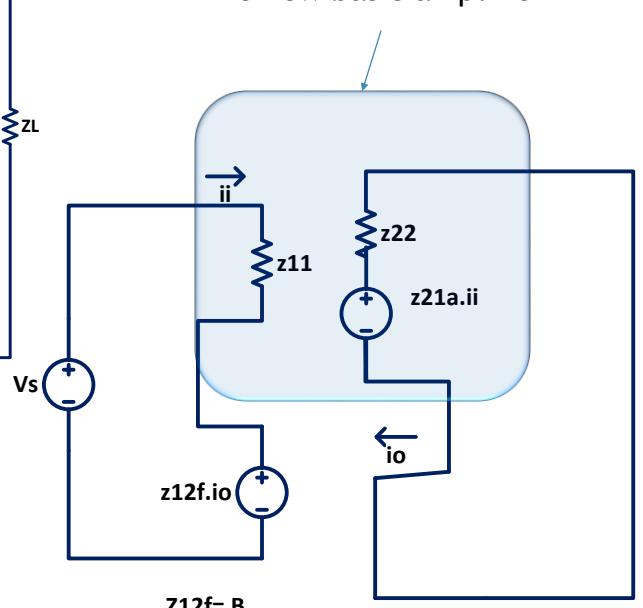

Negative FeedbackPractical configuration and the effect of loading

4) Series - Series Feedback




Example:

$$R_s = 0.6k \text{ , , } R_C || R_L = 2k$$




$$R_E = 0.2k \text{ , , } R_1 || R_2 = 50k$$


$$h_{ie} = 1k \text{ , , } h_{fe} = 100$$

Ac small signal equivalent circuit

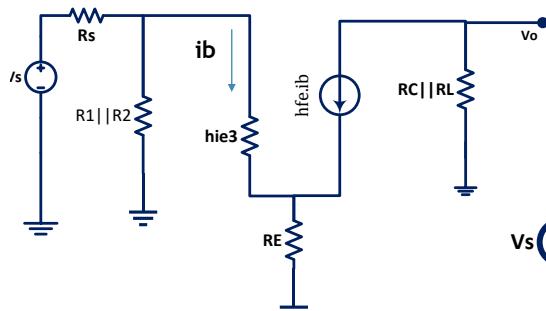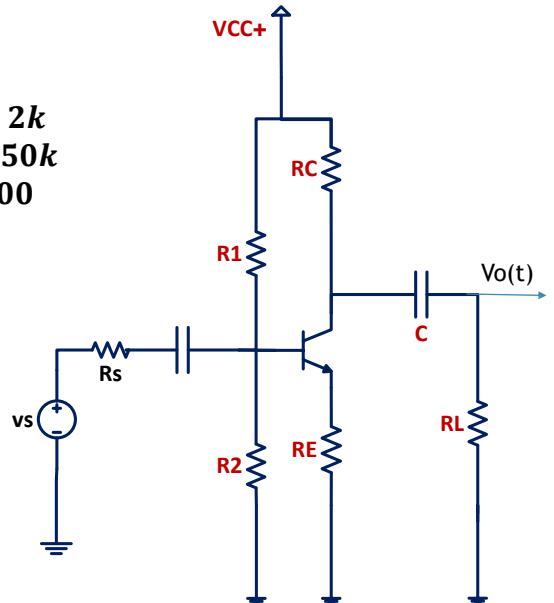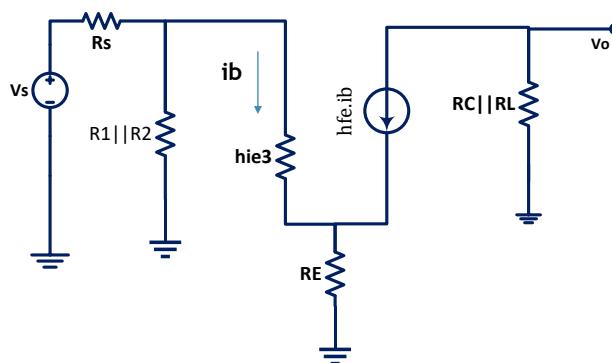Negative Feedback

The Feed-Back Network:

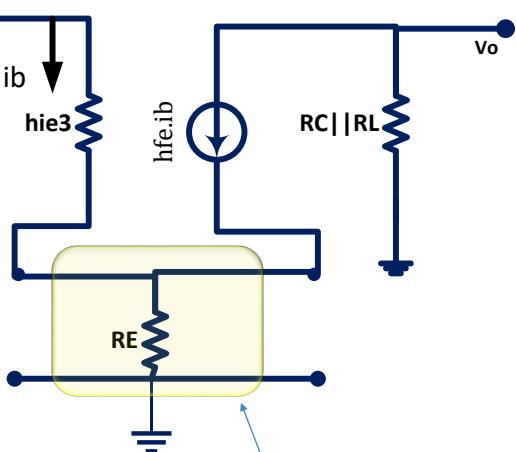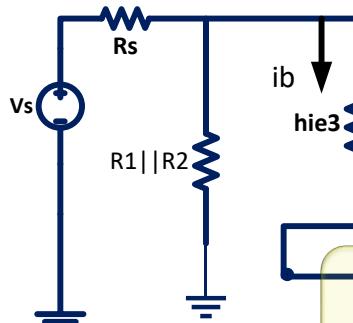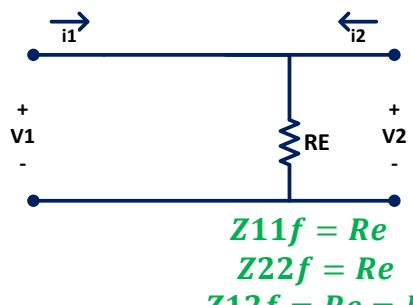

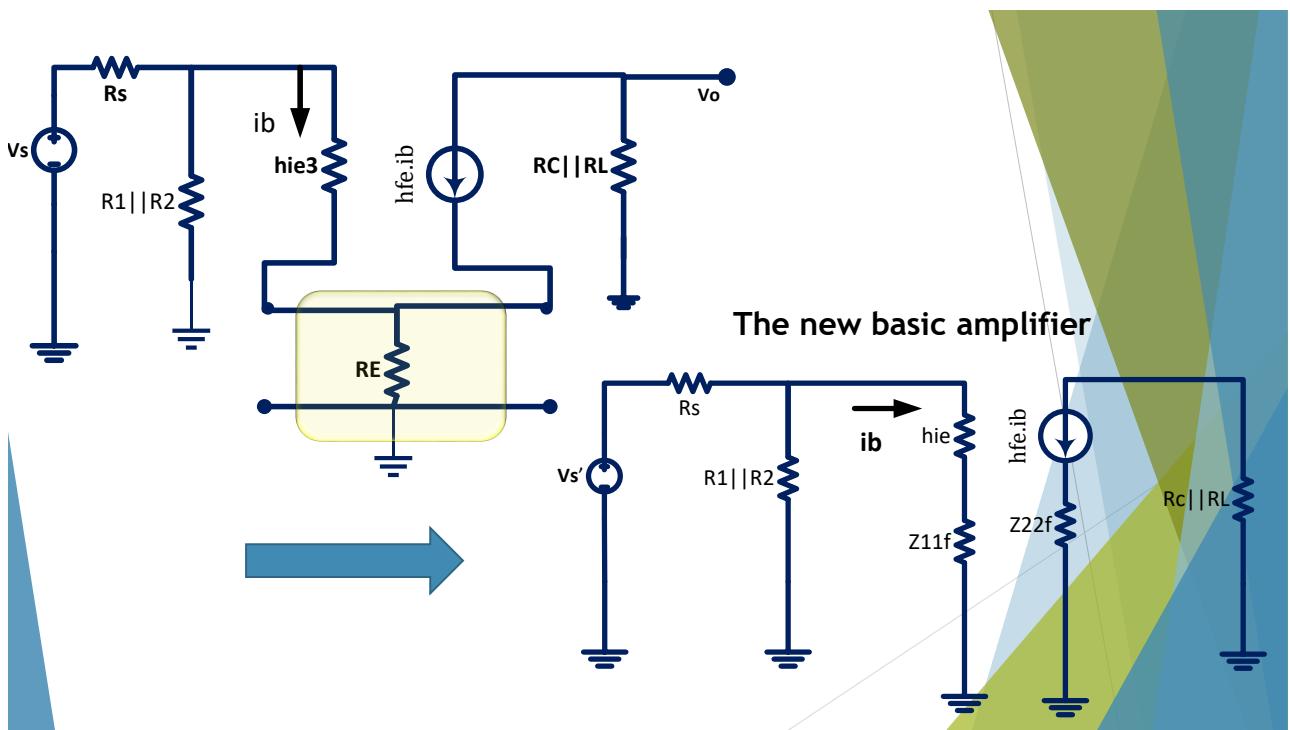


4) Series - Series Feedback

$$A = \frac{i_o}{V_{s'}}$$

$$i_o = (h_{fe})i_b$$

$$i_b = ii \frac{R_1 || R_2}{R_1 || R_2 + h_{ie} + Z_{11f}}$$

$$ii = \frac{V_s}{R_s + R_1 || R_2 || (h_{ie} + Z_{11f})}$$

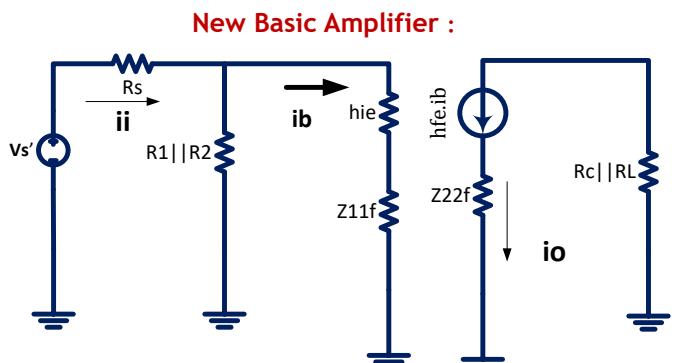

$$A = 56.4$$

$$AB = 11.29$$

$$Af = \frac{i_o}{V_s} = \frac{A}{1 + AB} = 4.59$$

$$\begin{aligned} Av &= \frac{V_o}{V_s} = \frac{i_o}{V_s} \cdot \frac{V_o}{i_o} \\ &= - Af \cdot (R_L || R_C) \\ Av &= -9.18 \end{aligned}$$