

Bipolar Junction Transistors

Instructor
Nasser Ismail

ENEE236 Analog Electronics

1

The First Transistor

Co-inventors of the first transistor at Bell Laboratories: Dr. William Shockley (seated); Dr. John Bardeen (left); Dr. Walter H. Brattain. (Courtesy of AT&T Archives.)

Dr. Shockley Born: London, England, 1910
PhD Harvard, 1936

Dr. Bardeen Born: Madison, Wisconsin, 1908
PhD Princeton, 1936

Dr. Brattain Born: Amoy, China, 1902
PhD University of Minnesota, 1928

All shared the Nobel Prize in 1956 for this contribution.

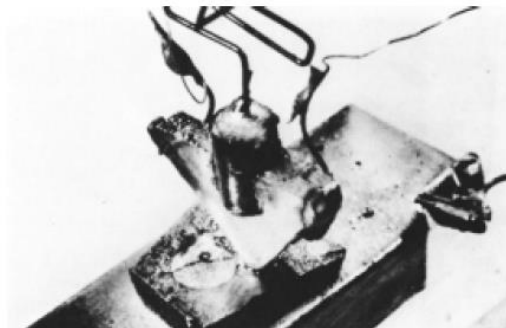


Figure 3.1 The first transistor. (Courtesy Bell Telephone Laboratories.)

Bipolar junction Transistor (BJT):



BJT:


1. It's a semiconductor device that can amplify electrical signals such as radio or television signals.
2. Its essential ingredient of every electronic circuits; from the simplest amplifier or oscillator to the most elaborate digital computer.
3. It's a three terminal device;
Base, **Emitter**, and **Collector**.




There are two type of BJT:

➤ **n**pn type

➤ **p**np type

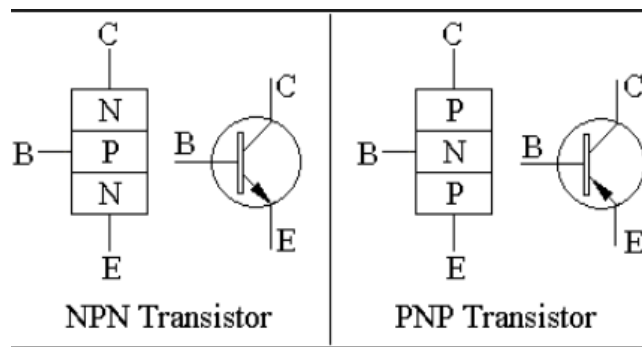

Transistor structure:

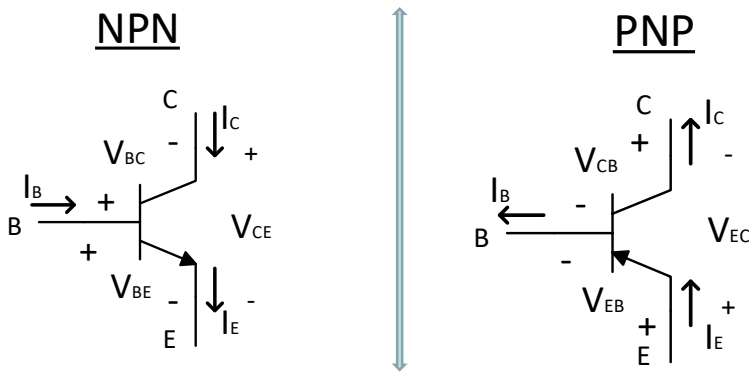


Transistor biasing:

- ✓ In order to operate properly as an amplifier, it's necessary to correctly bias the two pn-junctions with external voltages.
- ✓ Depending upon external bias voltage polarities used; the transistor works in one of **four regions** (modes). npn transistor modes of operation
- ✓ For transistor to be used as an Active device (**Amplifier**); the **emitter-base** junction must be **forward** bias, while the **collector-base** junction must be **reverse** biased.

Junction/ Mode	BE	BC	Remarks
Saturation Mode	Forward	Forward	Equivalent to short circuit $I_c = I_{c(sat)}$ $V_{ce} = V_{ce(sat)} \approx 0.2V$
Active Mode (Linear Region)	Forward	Reverse	I_c proportional to I_b V_{ce} defined by circuit
Cut-off Mode	Reverse	Reverse	Equivalent to open circuit $I_c = I_b = 0$ V_{ce} defined by circuit
Inverse Mode	Reverse	Forward	Rarely used and will not be discussed in this course

In active region

- ✓ The base region is thin and lightly doped
- ✓ The base-emitter junction is forward biased, thus the depletion region at this junction is reduced.
- ✓ The base-collector junction is reverse biased, thus the depletion region at this junction is increased.
- ✓ The forward biased BE-junction causes the electrons in the n-type emitter to flow toward the base; this constitutes the emitter current I_E .
- ✓ As these electrons flow through the P-type base; they tend to recombine with holes in p-type base.

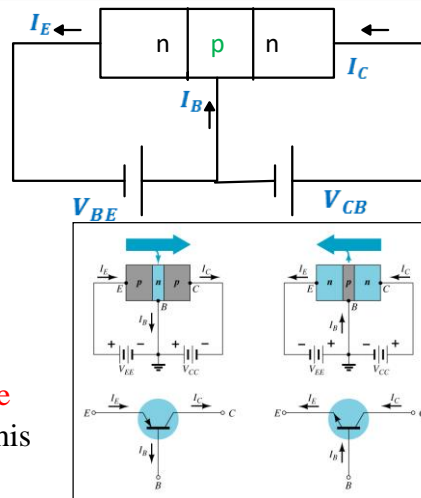

- ✓ Since the base region is lightly doped; very few of the electrons injected into the base from the emitter recombine with holes to constitute base current I_B and the remaining large number of electrons cross the base and move through the collector region to the positive terminal of the external DC source; this constitute collector current I_C
- ✓ There is another component for I_C due to the minority carrier; I_{CBO} which will be ignored

$$I_C = \alpha I_E + I_{CBO}$$

Majority
Minority

$$0.998 > \alpha > 0.9$$

In active region:

(for info only)

$$I_C = \alpha I_E + I_{CBo}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha(I_C + I_B) + I_{CBo}$$

$$\diamond I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBo}$$

Let Beta, $\beta = \frac{\alpha}{1-\alpha}$


$$\diamond I_C = \beta I_B + (\beta + 1) I_{CBo}$$

$$I_C = \beta I_B + I_{CEo}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

If $\alpha = 0.99 \longrightarrow \beta = 99$

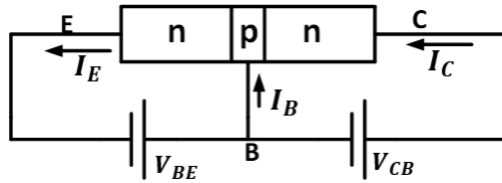If $\alpha = 0.995 \longrightarrow \beta = 199$



Approximate relationships:

Will be used in this course

$$I_E = I_C + I_B$$

$$I_C \cong \alpha I_E \cong I_E$$

$$I_C \cong \beta I_B$$

$$I_E \cong (\beta + 1) I_B$$



$$\beta = \frac{\alpha}{1-\alpha}$$

$$\alpha = \frac{\beta}{\beta + 1}$$



- <https://www.youtube.com/watch?v=7ukDKVHnac4>

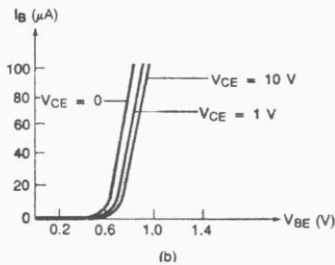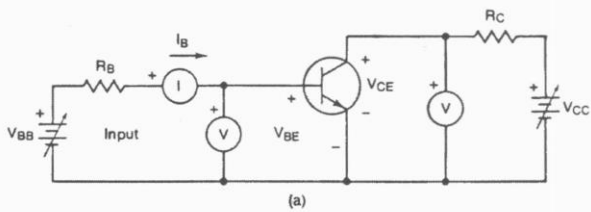Input characteristic curve (Common Emitter):





$$i_{B(t)} = I_{B0} \left(e^{\frac{V_{BE(t)}}{\eta V_T}} - 1 \right)$$

$$i_{B(t)} \cong I_{B0} \left(e^{\frac{V_{BE(t)}}{\eta V_T}} \right)$$

$$i_{C(t)} \cong I_S \left(e^{\frac{V_{BE(t)}}{\eta V_T}} \right)$$

Output characteristic curve:


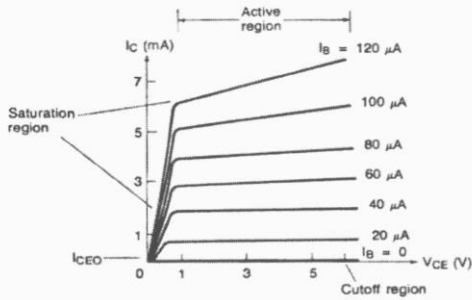
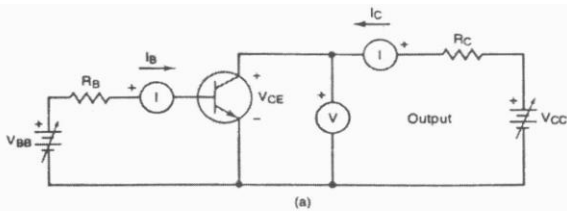


Basic BJT Amplifiers Circuits

C-E Circuits I-V Characteristics

Collector characteristic (output characteristic)

$$i_C = f(V_{CE}) \Big|_{i_B = C}$$

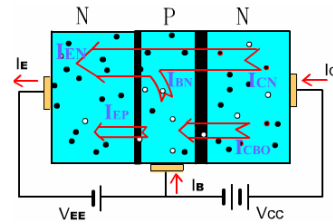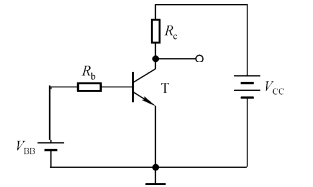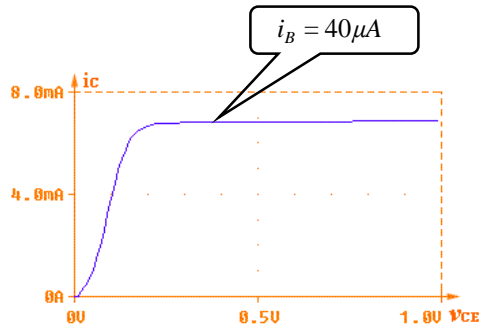


Basic BJT Amplifiers Circuits

C-E Circuits I-V Characteristics

Collector characteristic (output characteristic)

$$i_C = f(V_{CE}) \Big|_{i_B = C}$$

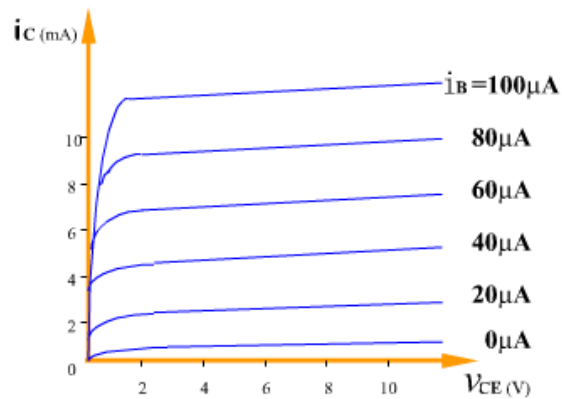

Summary

1. In the **cutoff** region :

$$I_B = I_C = I_E = 0$$

2. In the **active** region :

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

$$V_{BE} = 0.7 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{nnp}$$

$$V_{BE} = -0.7 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{pnp}$$

$$V_{CE} > V_{CE,sat} = 0.2 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{nnp}$$

$$V_{CE} < V_{CE,sat} = -0.2 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{pnp}$$

3. In the **saturation** region :


$$V_{CE} = V_{CE,sat}$$

$$V_{BE} = 0.8 \text{ V} \quad , \quad \text{Si} \quad , \quad \text{nnp}$$

$$V_{BE} = -0.8 \text{ V} \quad , \quad \text{Si} \quad , \quad \text{pnp}$$

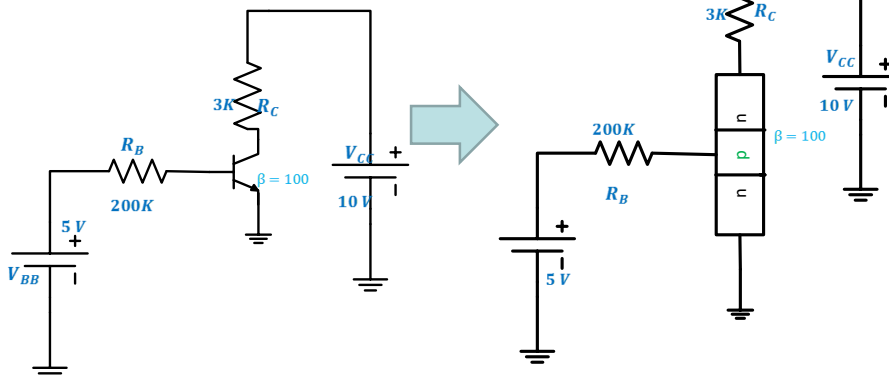Example:

Find mode of operation and the Q point V_{CEQ} , I_{CQ}



Since the **base emitter** junction is **forward bias**; the transistor could be either in the **active** or the **saturation** region



➤ Assume that the transistor is in the **active** region:

KVL: $5 = 200k I_B + V_{BE}$

$$I_B = \frac{5 - 0.7}{200k} = 0.0215 \text{ mA}$$

$$I_C = \beta I_B = 100 * 0.0215 = 2.15 \text{ mA}$$

KVL: $10 = R_C I_C + V_{CE}$

$$V_{CE} = 10 - R_C I_C$$


$$\diamond V_{CE} = 10 - 3k * 2.15 \text{ mA} = 3.55 \text{ Volt}$$

Since

$V_{CE} > V_{CE,sat} >>>$ The transistor is in the **active** region

➤ $V_{CEQ} = 3.55 \text{ Volt}$

➤ $I_{CQ} = 2.15 \text{ mA}$

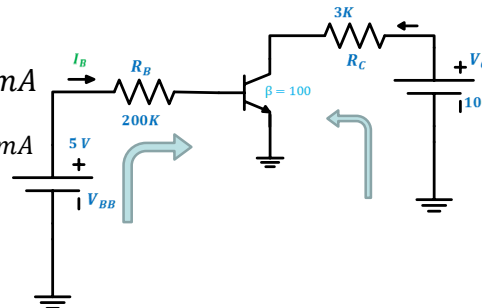

Example

Find the Q point V_{CEQ} , I_{CQ}

Solution:

Since the base emitter junction is forward bias ; the transistor could be either in the active or the saturation region

➤ Assume that the transistor is in the active region

KVL: $5 = 200k I_B + V_{BE} + 2k I_E$

$$I_E = (\beta + 1) I_B$$

$$I_B = \frac{5 - 0.7}{200k + 101 * 2k} = 0.0107 \text{ mA}$$

$$I_C = \beta I_B = 100 * 0.0107 = 1.07 \text{ mA}$$

KVL: $10 = R_C I_C + V_{CE} + R_E I_E$


$$V_{CE} = 10 - R_C I_C - R_E I_E$$

Since $\diamond V_{CE} = 4.63 \text{ Volt}$

$V_{CE} > V_{CE,sat} >>>$ The transistor is in the **active** region

➤ $V_{CEQ} = 4.63 \text{ Volt}$

➤ $I_{CQ} = 1.07 \text{ mA}$

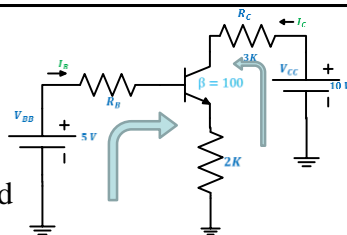

Second Method


1) In the active region:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - R_C I_C$$

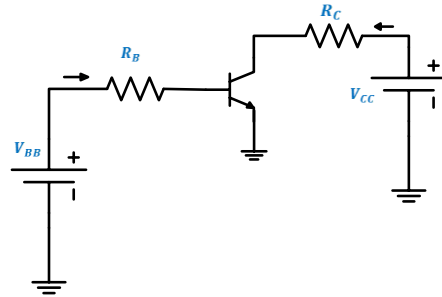As : $R_B \downarrow$, $I_B \uparrow$, $I_C \uparrow$, $V_{CE} \downarrow$




2) In the saturation region:

$$V_{CE} = V_{CE,sat} = 0.2 \text{ v} , \text{ Si} , \text{ npn}$$

$$I_C = I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_C}$$
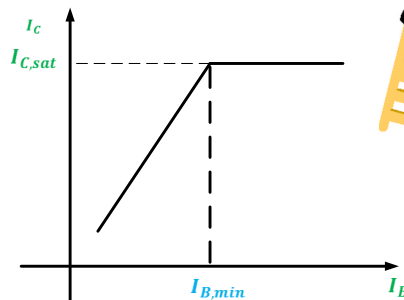
$$\text{Let define: } I_B(\min) = \frac{I_{C,sat}}{\beta}$$



$$I_B(\min) = \frac{I_{C,sat}}{\beta}$$

✚ If $I_B > I_B(\min)$ the transistor is in the **Saturation** region.

✚ If $I_B < I_B(\min)$ the transistor is in the **Active** region.

OR Second method: Assume Saturation

- 1) Since BE junction is forward biased \Rightarrow Q1 can be either in Active (Linear) or Saturation mode
- Assume it is in **saturation mode**:

$$10 - I_{C(sat)} \cdot 3k\Omega - I_{E(sat)} \cdot 2k\Omega = V_{CE(sat)}$$

$$\text{assume } I_{E(sat)} = I_{C(sat)}$$

$$\therefore I_{C(sat)} = \frac{10 - 0.2}{5k\Omega} = 1.96 \text{ mA}$$



$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = 19.6 \text{ }\mu\text{A}$$

Now we find the actual value of I_B

$$I_{B(actual)} = 10.7 \text{ }\mu\text{A (it was found previously)}$$

since

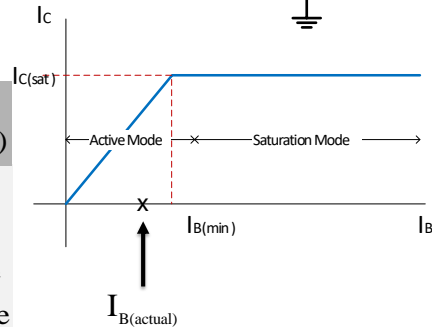
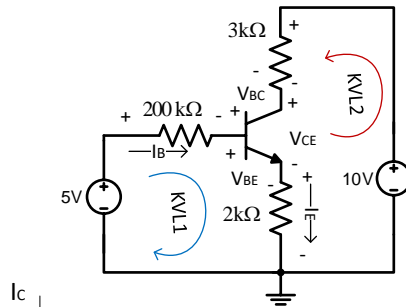
$I_{B(actual)} < I_{B(sat)} = I_{B(min)} \Rightarrow$ the assumption made earlier that BJT in saturation mode is wrong, and actually it is in active mode



BJT as switch:

Example:



Find $V_o(t)$ for the input given below:

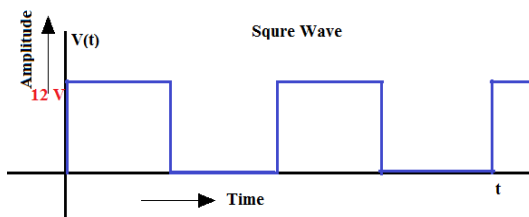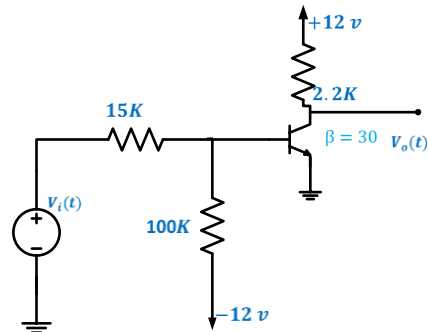

Solution:

❖ Let $V_i(t) = +12 \text{ volt}$

Calculate V_{th} & R_{th}

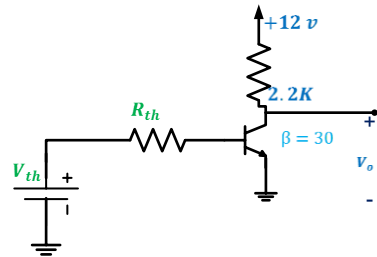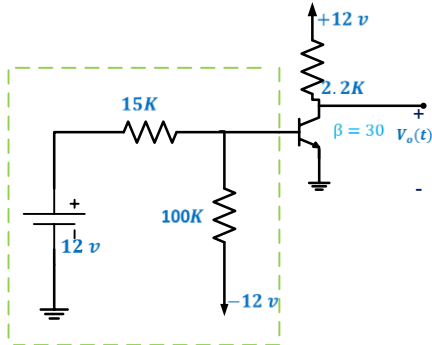

$$R_{th} = 15k // 100k = \frac{100k \cdot 15k}{15k + 100k} = 13k$$

$$V_{th} = 8.9 \text{ volt} \quad \text{Proof!!}$$



Since the base emitter junction is forward bias; the transistor could be either in the active or the saturation region

➤ Assume that the transistor in the saturation region

$$I_C = I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_C} = \frac{12 - 0.2}{2.2k} = 5.36 \text{ mA}$$

$$I_B(\min) = \frac{I_{C,sat}}{\beta} = \frac{5.36 \text{ mA}}{30} = 0.18 \text{ mA}$$


$$I_B = \frac{V_{th} - V_{BE}}{R_{TH}} = \frac{8.9 - 0.8}{13k} = 0.62 \text{ mA}$$

✚ Since $I_B > I_B(\min)$ the transistor is in the saturation region.

$$\checkmark V_o = V_{CE,sat} = 0.2 \text{ volt}$$

$$\checkmark I_C = 5.36 \text{ mA}$$

❖ Let $V_i(t) = 0 \text{ volt}$

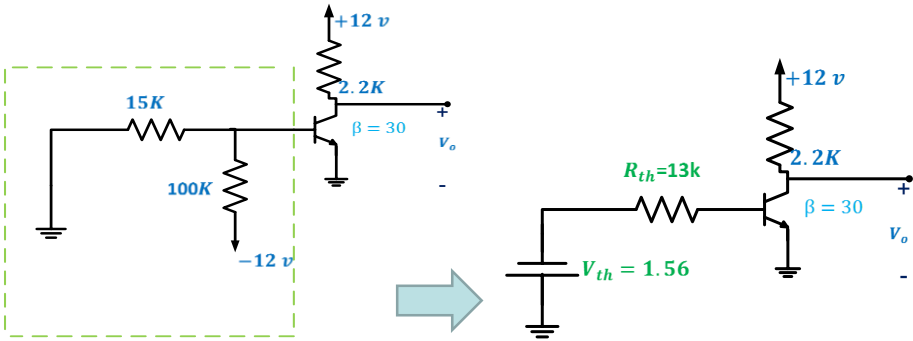


Since $V_{th} = -1.56 \text{ volt}$

Base emitter junction is revers biased the transistor in cutoff region

✓ $V_o = V_{CE} = 12 \text{ volt}$

✓ $I_C = 0 \text{ mA}$

The circuit acts as inverter or not gate

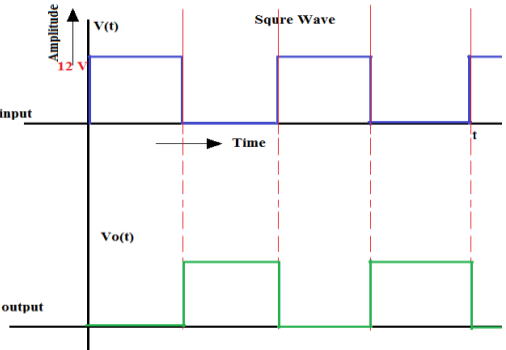

NOT gate truth table

Input  Output

Input	Output
0	1
1	0