

Resonance

Def:- Resonance is a phenomenon that occurs when the Reactance of the capacitor & inductor is the same



$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Delta f = f_2 - f_1$$

= band width

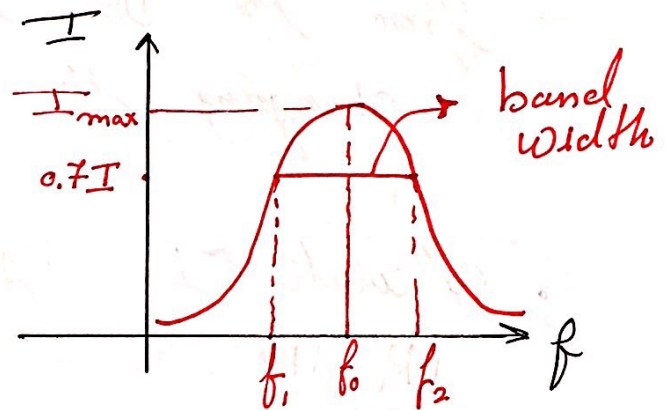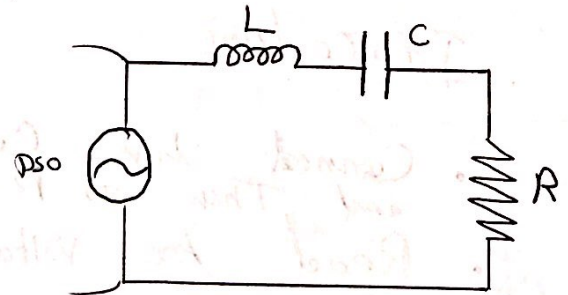

Quality factor

- A measure of the sharpness of the Resonance Curve

$$\rightarrow Q = \frac{f_0}{\Delta f} \quad (\text{experimentally})$$

$$\rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (\text{Theoretically})$$


Alaa Elaiw

What we use :-


- L, C, R
- signal Generator & DSO

Procedure :-

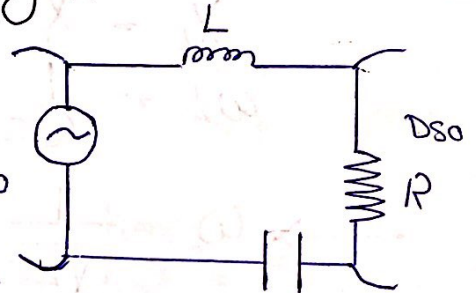- Connect this circuit :- Using R once as $R = 1 \text{ k}\Omega$ and then as $R = 2 \text{ k}\Omega$
- Read the voltage values from the DSO when changing the frequency.



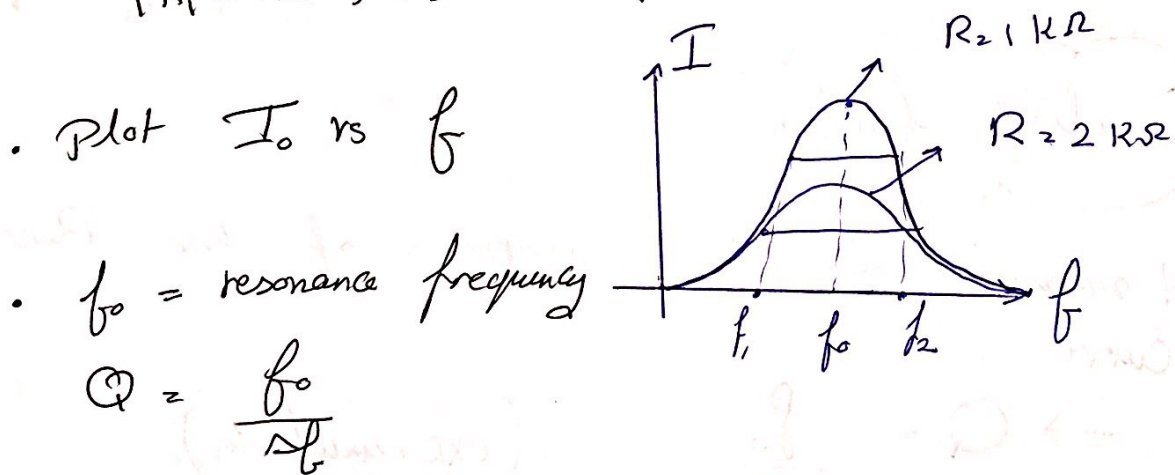- Calculate I_0 By dividing each value on R ($R_1 = 1 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega$)



- قيم بحد الارتفاع كما هو موضح كيف تتغير R :- $1 \text{ k}\Omega$ ثم $2 \text{ k}\Omega$
- قم بقراءة قيم V من DSO عند كل نقطة f
- قم بحساب التيار المقاسه قيم V على R
- ارسم I vs f واحد Q و f_0

Alaa Itaiwi