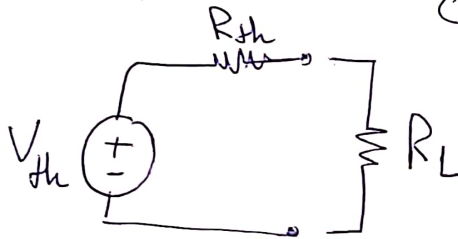


Exp 4: Thevenin and Norton techniques.

- Kirchhoff's Law and SPP are useful for analyzing networks that contain a few circuit elements
- Dealing with complicated networks requires more adequate methods like Thevenin and Norton techniques.

* Thevenin's Theorem:

- we can take any complicated circuit and reduce it down to voltage source and eq resistance, if you have one section of the circuit you care about.



- Steps :-


- (1). remove the R_L
- (2). remove all the sources and find R_{Th}
- (3). put the sources back and find V_{Th} through Kirchhoff's loop.
- (4). construct Thevenin equivalent circuit.
- (5).
$$I_{RL} = \frac{V_{Th}}{R_{Th} + R_L}$$

Norton's %


2. replace R_L with a short then find I_{eq} (put sources back)

2. To find R_{eq} use the same way as Thevenin.

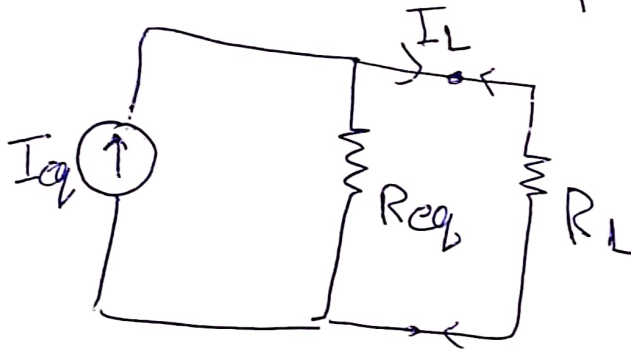3. Construct Norton's equivalent circuit using a current source and parallel resistance.




procedure :-

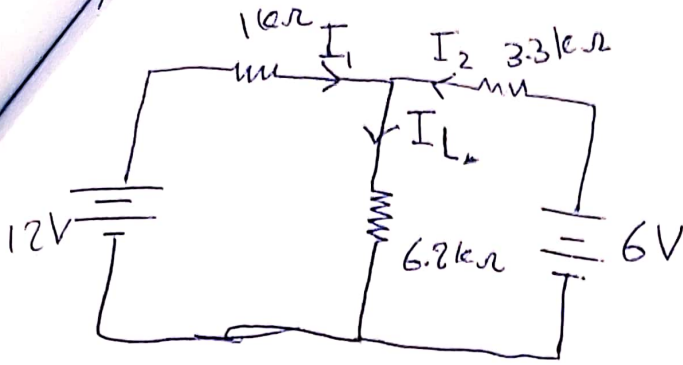

1. Construct the circuit as shown, let $6.2k\Omega$ be the Load.

For Thevenin's Theo^y:

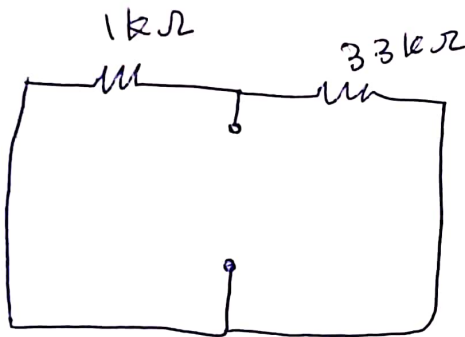2. remove R_L , kill sources to find R_{th} or R_{eq}




$$R_{th} = 1k\Omega // 3.3k\Omega$$

$$= \frac{(1 \times 3.3)(k\Omega)^2}{(1 + 3.3)k\Omega}$$

$$R_{th} \approx 769\Omega$$

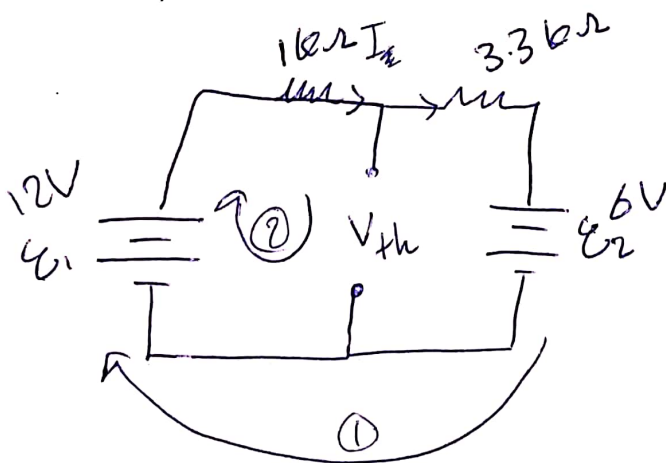3. put the sources back and calculate V_{th} , V_{eq}



By Kirchhoff's loop.

$$\textcircled{1} \rightarrow \epsilon_1 - \epsilon_2 = I(R_1) + IR_2$$


$$\textcircled{2} \rightarrow \epsilon_1 - IR - V_{th} = 0$$

$$V_{th} = \epsilon_1 - IR$$

$$V_{th} = \frac{\varepsilon_1 - (\varepsilon_1 - \varepsilon_2)R_1}{R_1 + R_2}$$

$$V_{th} \approx 10.63$$

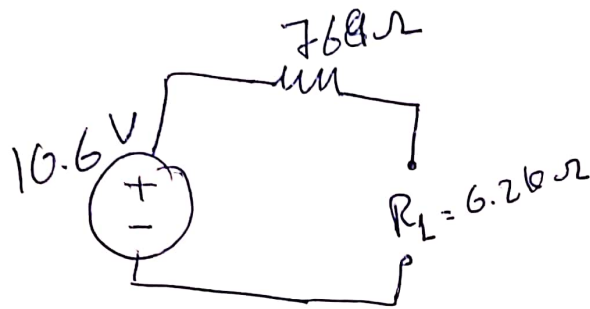④ Construct the Thevenin equivalent circuit.




$$\cancel{I_L} = \frac{V_{th}}{R_{eq} + R_L}$$

$$= \frac{10.6}{6.3 \times 10^3 + 769}$$

$$= \cancel{\times}$$

Norton's

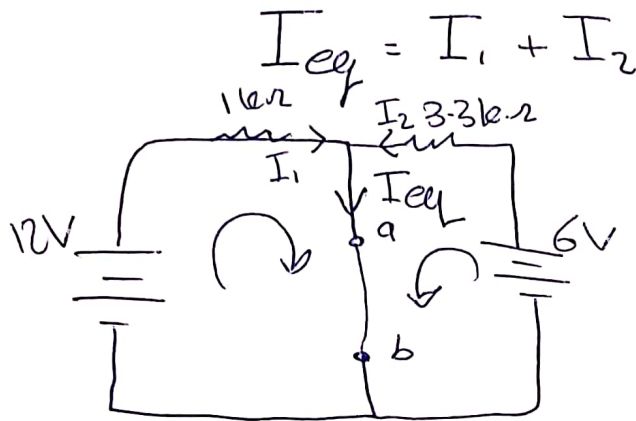② Replace R_L with a short, calculate I_{eq}




$$I_{eq} \text{ like } V_{th}$$

Since R_{eq} would be found in the same way as Thevenin. $\therefore$ then we take the value that we found earlier R_{eq}

$$I_{eq} = \frac{E_1}{R_1} + \frac{E_2}{R_2}$$

③ Construct Norton's equivalent circuit.

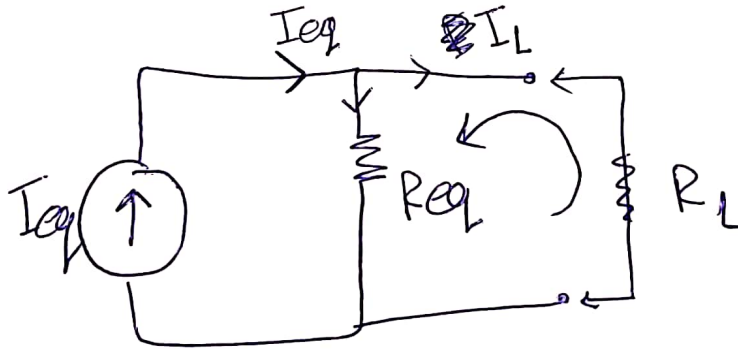

To find I_L

$$I_L R_L = (I_{eq} - I_L) R_{eq}$$

$$I_L = \frac{I_{eq} R_{eq}}{R_{eq} + R_L}$$

Data

	Exp	Theo
$(R_{Th}) R_{eq}$		
$(V_{Th}) \mathcal{E}_{eq}$		
$(Norton) I_{eq}$		
$(Theve) I_L$		
$(Norton) I_L$		

After constructing the circuit.

I_{eq} in Norton like V_{Th} (R_{eq}) in Thevenin.

R_{eq} in Both Cases is the same.