

**Question 1:** Find  $f(t)$  if  $F(s)$  is given by the expression

$$F(s) = \frac{24s}{(s+2)(s+4)(s+6)}$$

**Question 2:** Find  $f(t)$  if  $F(s)$  is given by the expression

$$F(s) = \frac{4(s+4)}{s(s^2 + 8s + 20)}$$

**Question 3:** Find  $f(t)$  if  $F(s)$  is given by the expression

$$F(s) = \frac{12(s+2)}{(s^2 + 2s + 1)(s+3)}$$

**Question 4:** Given the function

$$F(s) = \frac{24(s+10)}{s(s+2)(s+4)}$$

Find the initial and final values of the function by evaluating it in both the s-domain and time domain.

**Question 5:** Find  $v_o(t)$ ,  $t > 0$  in the circuit in Fig. 14.1 using (a) nodal analysis, (b) source transformation and (c) Norton's Theorem.

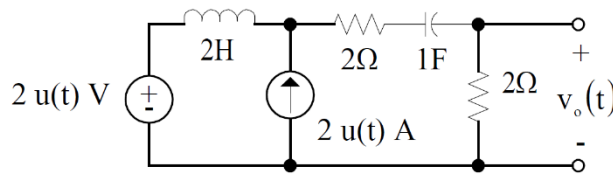


Fig. 14.1

**Question 6:** Find  $i_o(t)$ ,  $t > 0$  in the circuit in Fig. 14.2 using (a) loop equations and (b) Thevenin's Theorem

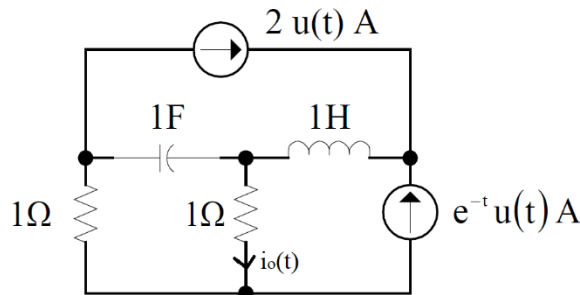


Fig. 14.2

**Question 7:** Find  $i_o(t)$ ,  $t > 0$  in the circuit in Fig. 14.3.

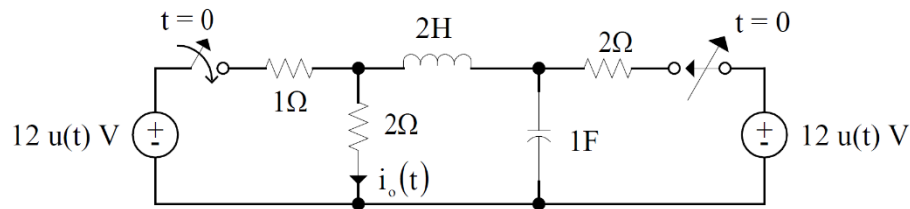


Fig. 14.3

**Question 8:** Given the network in Fig. 14.4, determine (a) the voltage transfer function  $G(s) = \frac{V_o(s)}{V_s(s)}$ ,  
(b) from the  $G(s)$ , draw pole-zero map (c) is the system stable? (d) find the step response.

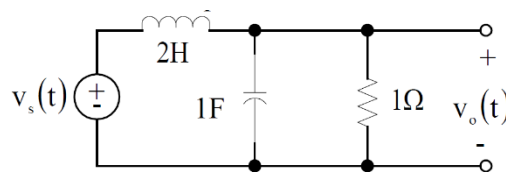


Fig. 14.4

**Question 9:** For the network shown in Fig. 14.5, (a) Find the voltage transfer function  $G(s) = \frac{V_o(s)}{V_s(s)}$ ,  
(b) from the  $G(s)$ , draw pole-zero map (c) is the system stable (d) find the impulse response.

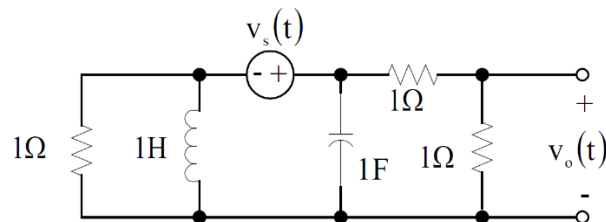


Fig. 14.5