



ANSWER BOOKLET


Student: <u>Digital</u>	Number: <u>11</u>
Course: Department: _____	Number: _____
Division: <u>"ch5"</u>	Instructor: _____
Date: _____	
Day	Month Year

For Instructor's Use

Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

* Synchronous Sequential Logic

* Sequential Circuit

 

- in combinational circuits, the outputs are entirely dependent on the current inputs.

- in sequential circuits, the outputs are function of the current inputs and the present state of the memory element (feedback.)


- also the next state of the storage element is a function of the external inputs and current state.

* Two main types of sequential circuits (the classification depends on the timing of their signals).

1) Synchronous sequential circuits: the behaviour can be defined from the knowledge of its signals at discrete instants of time.

2) asynchronous sequential circuit: depends upon the input signals at any instant of time and the order of the inputs.


* clocked sequential Circuits

 

② LATCHES

- Basic circuits from which all flip-flops are constructed
- flip-flop ~~is~~ ^{is} ~~the~~ ^{the} storage element used in clocked sequential circuit. A flip-flop is able to store one bit of information.
- The major differences among various types of flip-flops ^(latches) are in the number of inputs they possess and in the manner in which inputs affect the binary state.

 
③ SR Latch (Set - Reset) Latch, using Complementary NOR gates



(Stable state)

S	R	Q	Q'	
1	0	1	0	(set state)
0	0	1	0	after $S=1, R=0$
0	1	0	1	
0	0	0	1	after $S=0, R=1$
1	1	0	0	(undefined state or Indeterminate).


④ SR Latch using Couple Nand gates:-

 

(Sometimes referred as $S'-R'$ Latch)

because $S=0$ sets $Q=1$
 $R=0$ resets $Q=0$


④ SR Latch with Control Input

 

C	S	R	Next State
0	X	X	No change
1	0	0	No change
1	0	1	$Q=0$ (Reset)
1	1	0	$Q=1$ (Set)
1	1	1	undefined


* D-Latch

 one way to eliminate the undesirable condition of the undefined state is SR latch is to ensure that inputs S and R are never equal to 1




C	D	Next state of Q
0	X	No Change
1	0	$Q = 0$ (Reset)
1	1	$Q = 1$ (Set)


(transparent latch is D latch)

 

NOR
SR

 

NAND
SR

 

D

⑧ Flip-Flops:

- Latch without control input, always respond to the change in the inputs.
- ~~both~~ Latch with control input, responds to the change of inputs (e.g. SR) only when the control is in the positive level



- unpredictable situation may occur since the state of the latches may keep changing for as long as the clock pulse stays in the active level.

⇒ Flip-flop circuits are constructed in such a way as to make them operate properly when they are connected to a sequential circuit that employs a common clock.




positive-edge response (+ve edge trigger)




Negative-edge response (-ve edge trigger)

⑧ Master-Slave D-FF

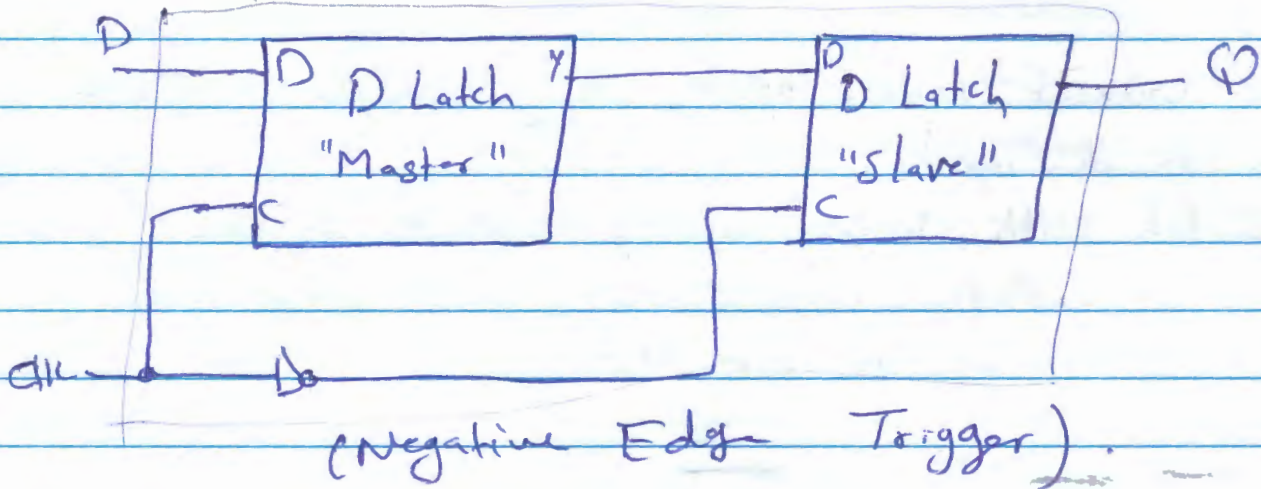


 +ve Edge Triggered

⑨ D-type +ve-Edge-Triggered FF.

 

+ve-Edge Triggered
Symbol

 

-ve-Edge Triggered
Symbol

Types of FF


① SR

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	undefined	

Next state

\Rightarrow S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Undefined

Characteristic Table

 

② ~~DEF~~

3

\Rightarrow S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

③ JK FF

J	K	$Q(t+1)$	
0	0	$Q(t)$	Same as SR FF
0	1	0	1, 1, 1, 1, 1, 1, 1, 1
1	0	1	1, 1, 1, 1, 1, 1, 1, 1
1	1	$Q'(t)$	New feature

→

J	K	$Q(t)$	$Q(t+1)$	S	R	D
0	0	0	0	0	X	0
0	0	1	1	X	0	1
0	1	0	0	0	X	0
0	1	1	0	0	1	0
1	0	0	1	1	0	1
1	0	1	1	X	0	1
1	1	0	1	1	0	1
1	1	1	0	0	1	0

- implement JK using SR FF


JK \ Q	0	1
00	X	X
01	X	0
10	1	X
11	1	1

$$S = JQ'$$

$$R = J'K + JKQ$$

JK \ Q	0	1
00		1
01		
11	1	
10	1	1


$$D = JQ' + K'Q$$

 

$$D = JQ' + KQ$$

characteristic equation

$$Q(t+1) = JQ' + KQ$$

 

④ Toggle FF (T-FF)


T	$Q(t+1)$	
0	$Q(t)$	(characteristic)
1	$Q'(t)$	


\Rightarrow

T	$Q(t)$	$Q(t+1)$	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0


T \ Q	0	1
0	0	1
1	1	0

$$D = TQ' + T'Q = T \oplus Q$$

 

 

(derive this)

 


characteristic equation

$$Q(t+1) = T \oplus Q$$

* Asynchronous Inputs of Flip-Flops (direct input)

- Some FF have asynchronous inputs that are used to force the flip-flop to a particular state independent of the clock. (Initial state of the FF is unknown ??). (When powered is turned on.)
- input that sets flip-flop to 1 is preset or direct set
- input that reset flip-flop to 0 is called clear or direct reset)

* D-FF with direct reset (clear)

 

R	C	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

*

* HDL for sequential Circuits:

* Behavioural Modelling

* Two kinds of behavioral statements in Verilog HDL : initial and always

- initial: executes once beginning at time = 0
- always: executes repeatedly until the simulation terminate.

* generation of clock for simulation

①

initial

begin

clock = 1'b0; // clock is a variable name

repeat (30)

#10 clock = ~clock;

end

② initial

begin

clock = 1'b0;

#300 \$finish;

end

always

#10 clock = ~clock;

*
④ always @ (event control expression)
procedural assignments

④ two kinds of events

① Level sensitive events (mainly in combinational circuits)
always @ (A or B or select)

② Edge-triggered events

Two keywords: posedge and negedge

always @(posedge clock or negedge reset)

④ A procedural assignment is an assignment within an initial or always statement.

* Description of D-Latch with control input

```
module D-Latch (Q, D, Control);
```

```
output Q;
```

```
input D, Control;
```

```
reg Q;
```

```
always @ (Control or D)
```

```
if (Control == 1) Q = D;
```

```
endmodule
```


*

* D flip flop

```
module D-FF (Q, D, CLK);  
    output Q;  
    input D, CLK;  
    reg Q;  
    always @ (posedge CLK)  
        Q = D;  
endmodule
```

* Functional Description of JK Flip-flop

```
module JK-FF (J, K, CLK, Q, Qnot);
```

```
    output Q, Qnot;
```

```
    input J, K, CLK;
```

```
    reg Q;
```

```
    assign Qnot = ~Q;
```

```
    always @ (posedge CLK)
```

```
        case ({J, K})
```

```
            2'b00 : Q = Q;
```

```
            2'b01 : Q = 1'b0;
```

```
            2'b10 : Q = 1'b1;
```

```
            2'b11 : Q = ~Q;
```

```
        endcase
```

```
    endmodule
```


④ Functional Description of T-FF

```
module T-FF (T, clk Q, Qnot)
  output Q, Qnot;
  input T, CLK;
  reg Q;
  assign Qnot = ~Q;
  always @(posedge CLK)
    if (T == 0) Q = Q;
    if (T == 1) Q = ~Q;
endmodule
```

④ Analysis of Clocked Sequential Circuits:

④ 3 important things in the analysis of sequential circuits: State equation, state table and state diagram.

- if you know one of these 3 things \Rightarrow you can derive the others.

① State equation (or transition equation): specifies the next state as a function of the present state and inputs.

Ex:

Figure 5-15

- since the D input of a flip-flop determines the value of the next state \Rightarrow

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = A'(t)x(t)$$

or for simplicity:

$$A(t+1) = Ax + Bx$$

$$B(t+1) = A'x$$

} next state

and the output

~~$y(t)$~~ $y = (A+B)x'$ (no clock)

⑧ State table (or transition table)

- specifies the time sequence of inputs, outputs and flip-flop states.
- The table consists of four sections labeled present state, input, next state, and output

