



DEPARTMENT OF COMPUTER SYSTEM ENGINEERING

Digital Integrated Circuits - ENCS333


Dr. Khader Mohammad

Lecture #6- CMOS Inverter

Integrated-Circuit Devices and Modeling

Creating Logic Gates in CMOS

- All standard Boolean logic functions (INV, NAND, OR, etc.) can be produced in CMOS push-pull circuits.
- Rules for constructing logic gates using CMOS
 - use a complementary nMOS/pMOS pair for each input
 - connect the output to VDD through pMOS txs
 - connect the output to ground through nMOS txs
 - ensure the output is always either high or low
- CMOS produces “inverting” logic
 - CMOS gates are based on the inverter
 - outputs are always inverted logic functions e.g., NOR, NAND rather than OR, AND

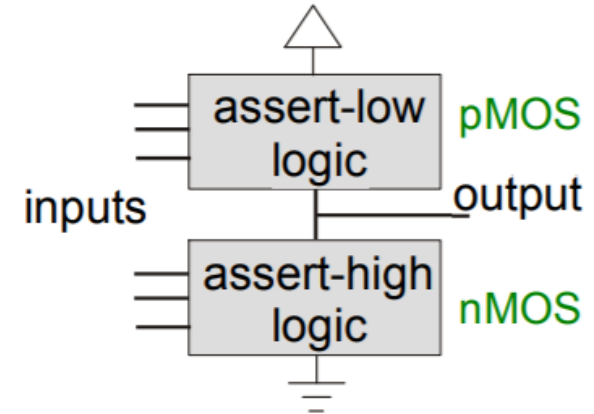

Logic Properties

DeMorgan's Rules

$$(a \cdot b)' = a' + b'$$

$$(a + b)' = a' \cdot b'$$

Useful Logic Properties

$$1 + x = 1 \quad 0 + x = x$$

$$1 \cdot x = x \quad 0 \cdot x = 0$$

$$x + x' = 1 \quad x \cdot x' = 0$$

$$a \cdot a = a \quad a + a = a$$

$$ab + ac = a(b+c)$$

Properties which can be proven


$$(a+b)(a+c) = a+bc$$

$$a + a'b = a + b$$

CMOS Inverter

- Inverter Function
 - toggle binary logic of a signal



- Inverter Symbol

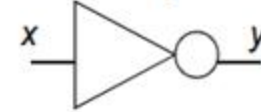

- Inverter Switch Operation

- Inverter Truth Table

x	$y = \overline{x}$
0	1
1	0

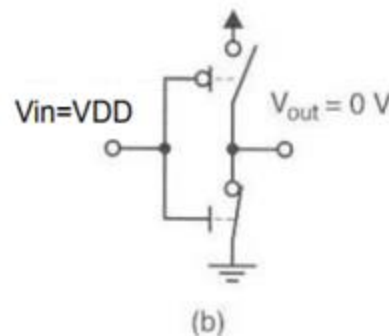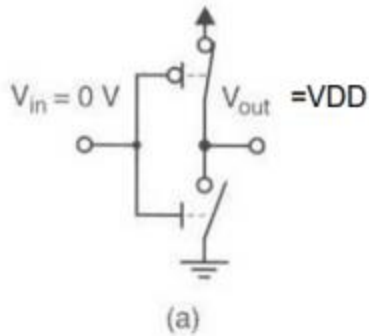


input low $\rightarrow$ output high
nMOS off/open
pMOS on/closed

pMOS "on"
 $\rightarrow$ output high (1)

input high $\rightarrow$ output low
nMOS on/closed
pMOS off/open

nMOS "on"
 $\rightarrow$ output low (0)


- CMOS Inverter Schematic

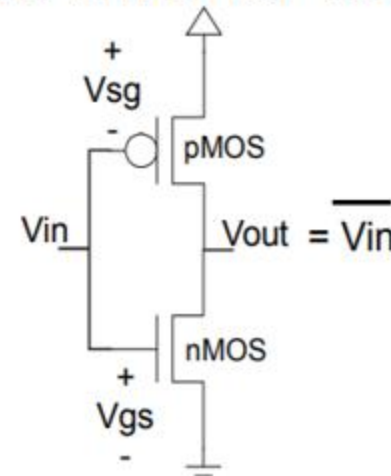

nMOS Logic Gates

- Study nMOS logic first, more simple than CMOS
- nMOS Logic
 - assume a resistive load to VDD
 - nMOS switches pull output low based on inputs



nMOS Inverter

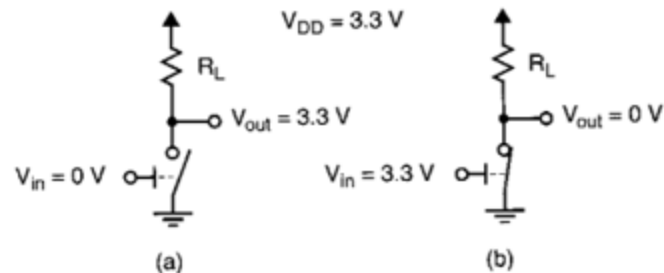

(a) nMOS is **off**
→ output is high (1)



(b) nMOS is **on**
→ output is low (0)

nMOS NOR

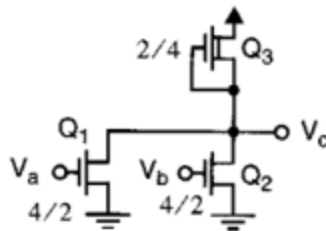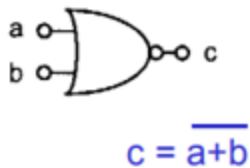

- parallel switches = OR function
- nMOS pulls low (NOTs the output)

nMOS NAND

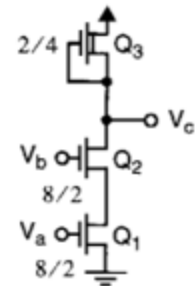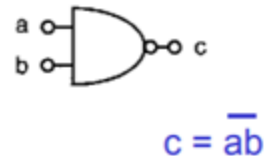

- series switches = AND function
- nMOS pulls low (NOTs the output)


Abstraction Level

Structural Verilog:

```
wire s;  
wire sbar;  
NOT not1(s, sbar);
```

Behavioral Verilog:

```
wire s, sbar;  
sbar = ~s;
```

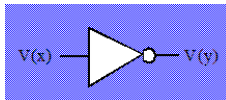

Architecture SPEC

RTL

Schematics

Physical Design (Layout)

Silicon


High



Abstraction Level




Low

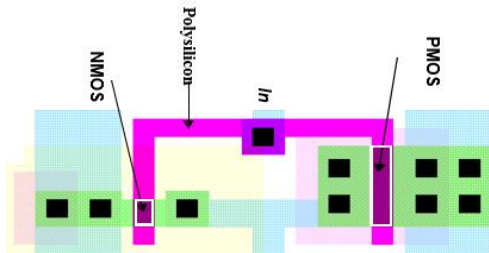

NMOS

PMOS

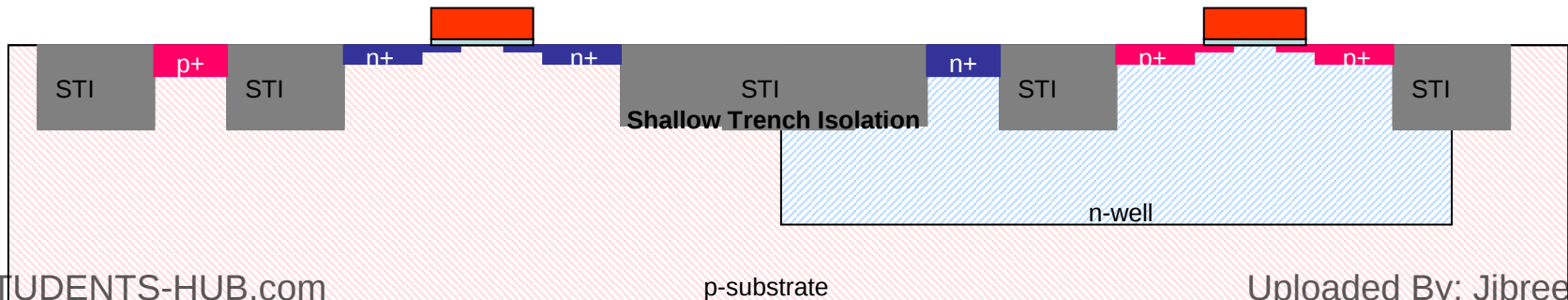


DIGITAL GATES


Fundamental Parameters

- Functionality
- Reliability, Robustness
- Area
- Performance
 - Speed (delay)
 - Power Consumption
 - Energy

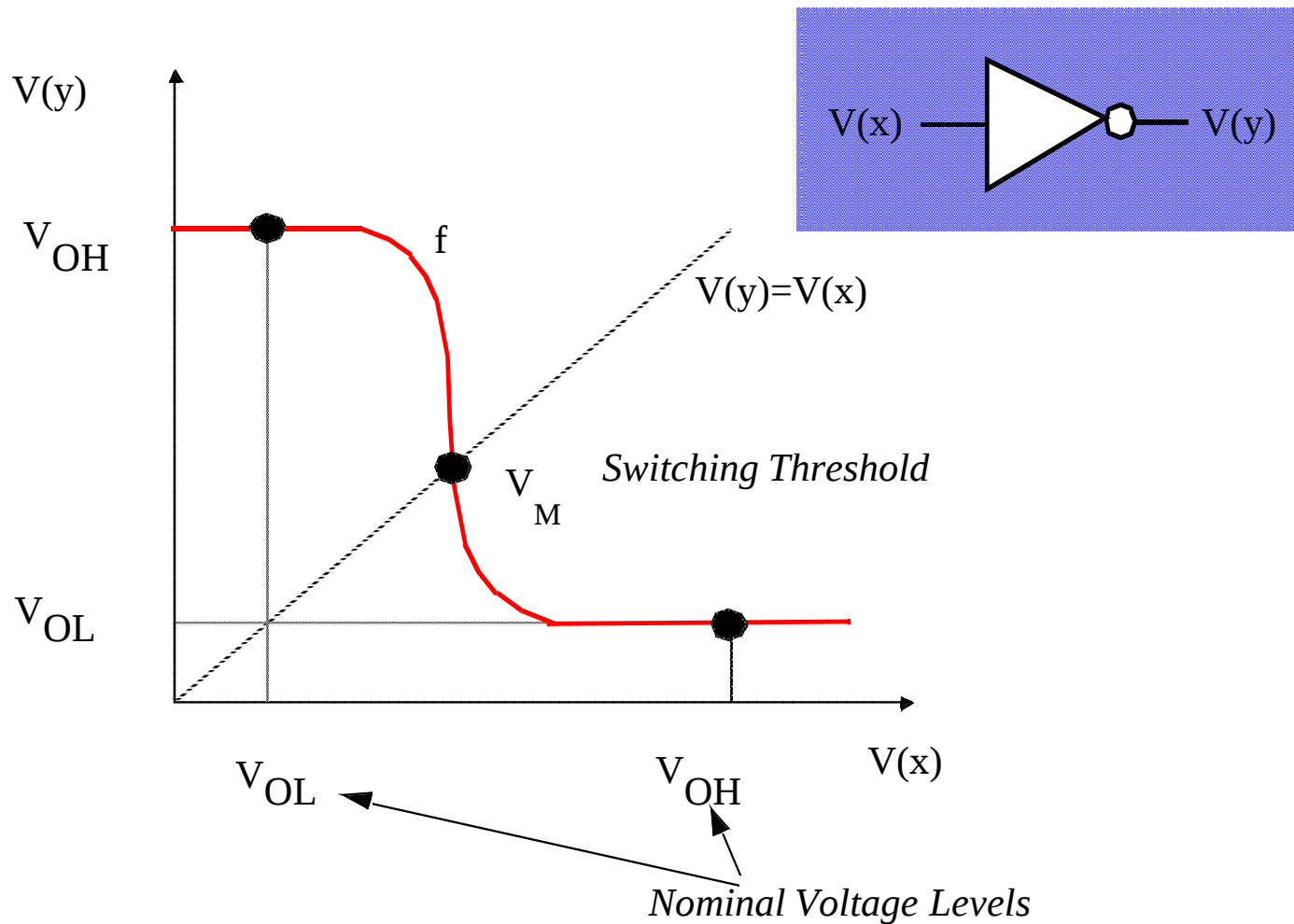
DC Operation: Voltage Transfer Characteristic




The CMOS Inverter: A First Glance

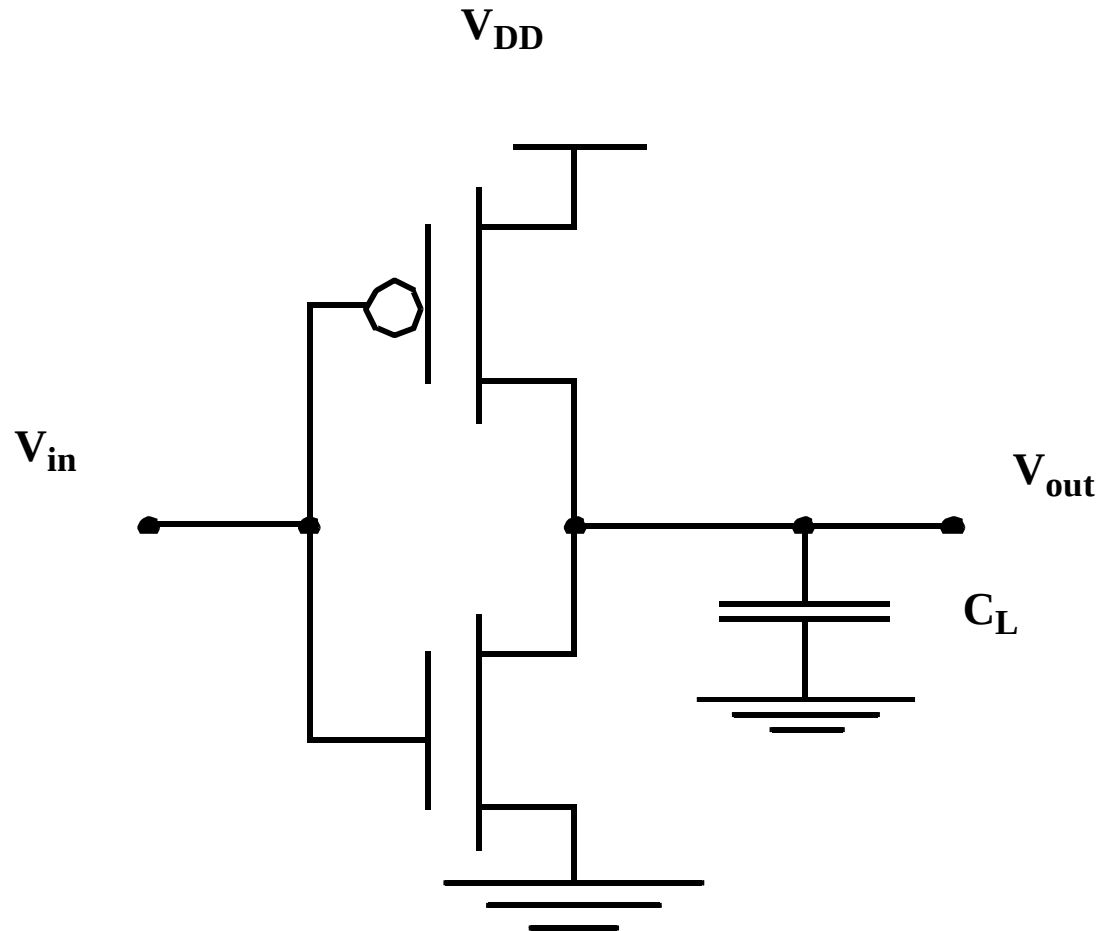

The CMOS Inverter

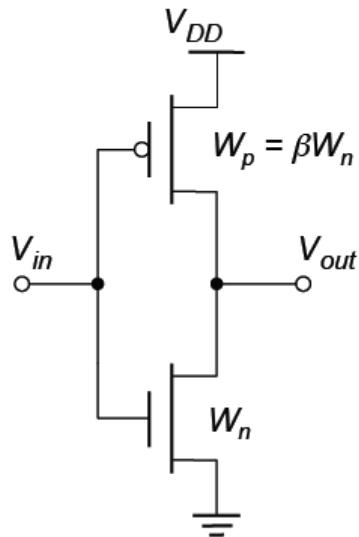


CMOS Inverter VTC

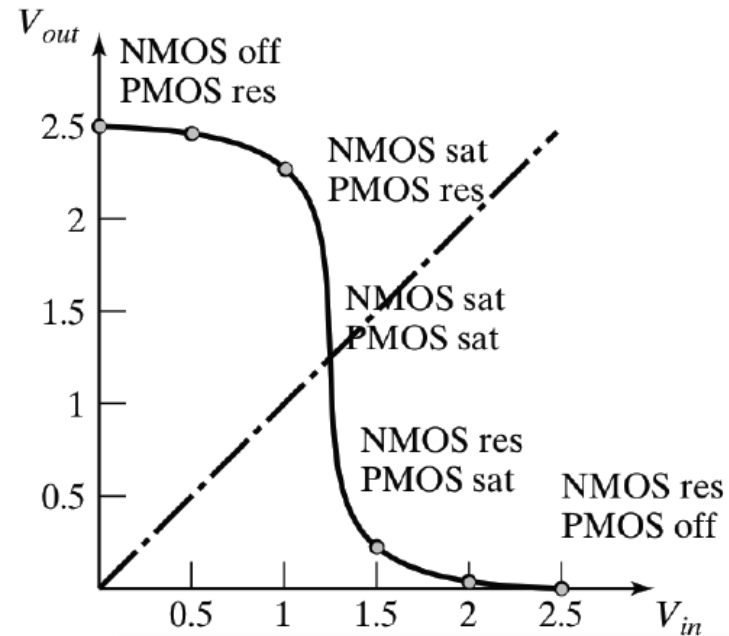


- **Cut-off** : $I_{ds} = 0$ (for now)
when $V_{gs} < V_T$
- **Linear** : $I_{ds} = \beta([V_{gs} - V_T] V_{ds} - \frac{V_{ds}^2}{2})$
when $0 < V_{ds} < V_{gs} - V_T$
- **Saturation** : $I_{ds} = \frac{\beta}{2}(V_{gs} - V_T)^2$ (for now)
when $0 < V_{gs} - V_T < V_{ds}$
This is obtained by using $V_{ds} = V_{gs} - V_T$ in the equation for linear I_{ds} (see comment two pages prior to this one)

- **Cut-off** : $V_{gs} < V_T$
- **Linear** : $0 < V_{ds} < V_{gs} - V_T$
- **Saturation** : $0 < V_{gs} - V_T < V_{ds}$


Switch Model of CMOS Transistor

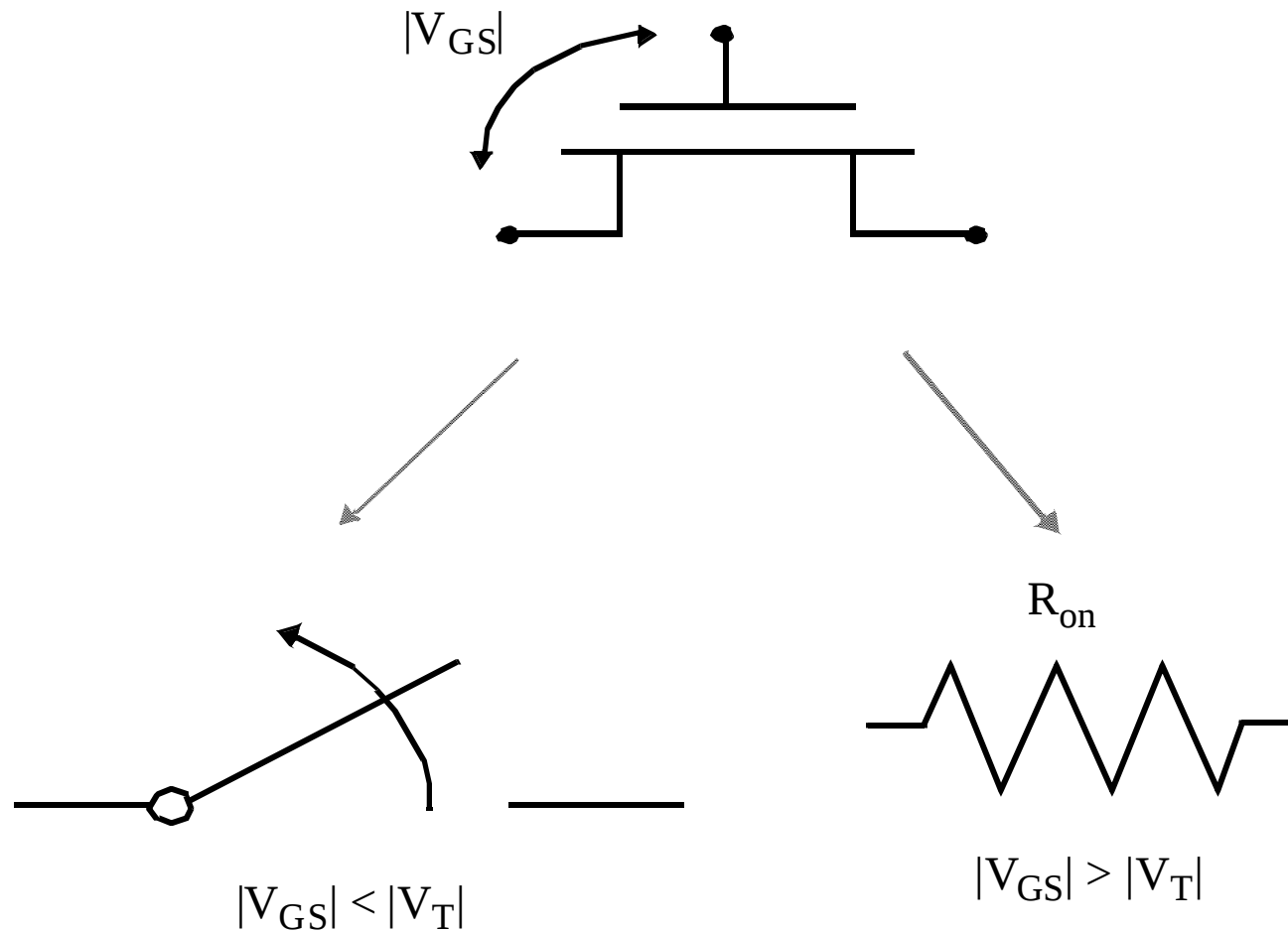


CMOS Inverter: Steady State Response

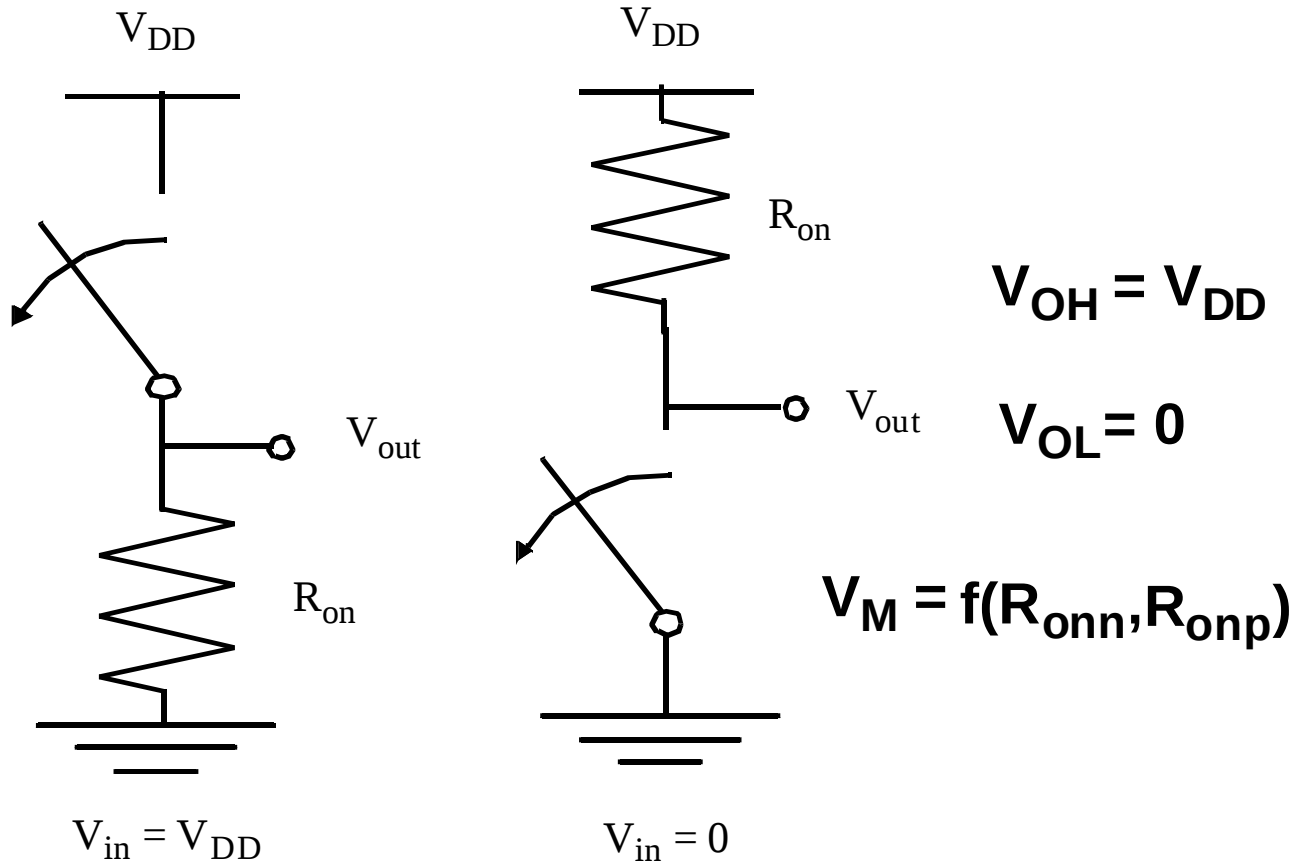


CMOS Inverter: Transient Response

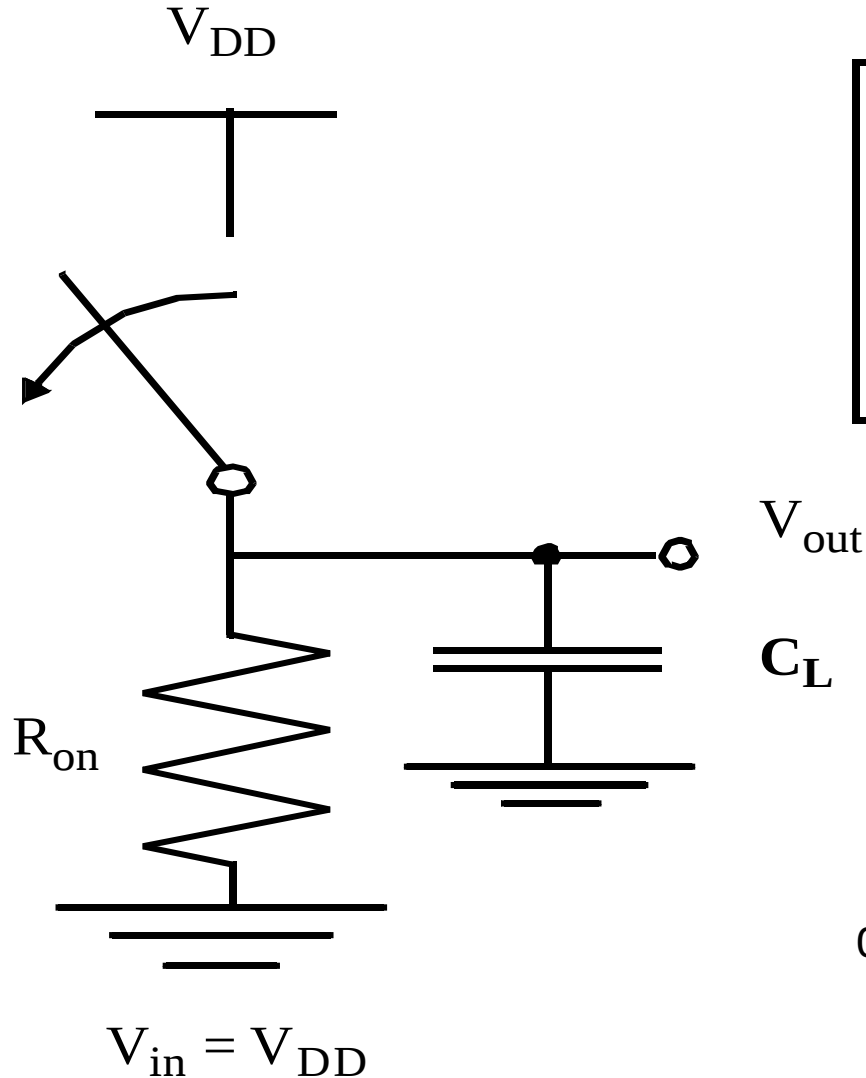

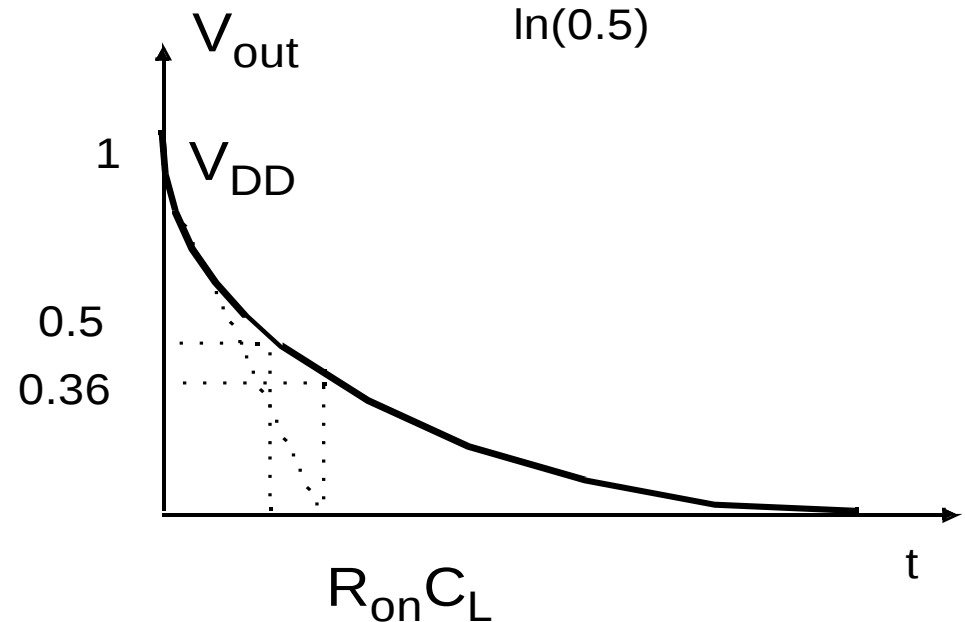
$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$



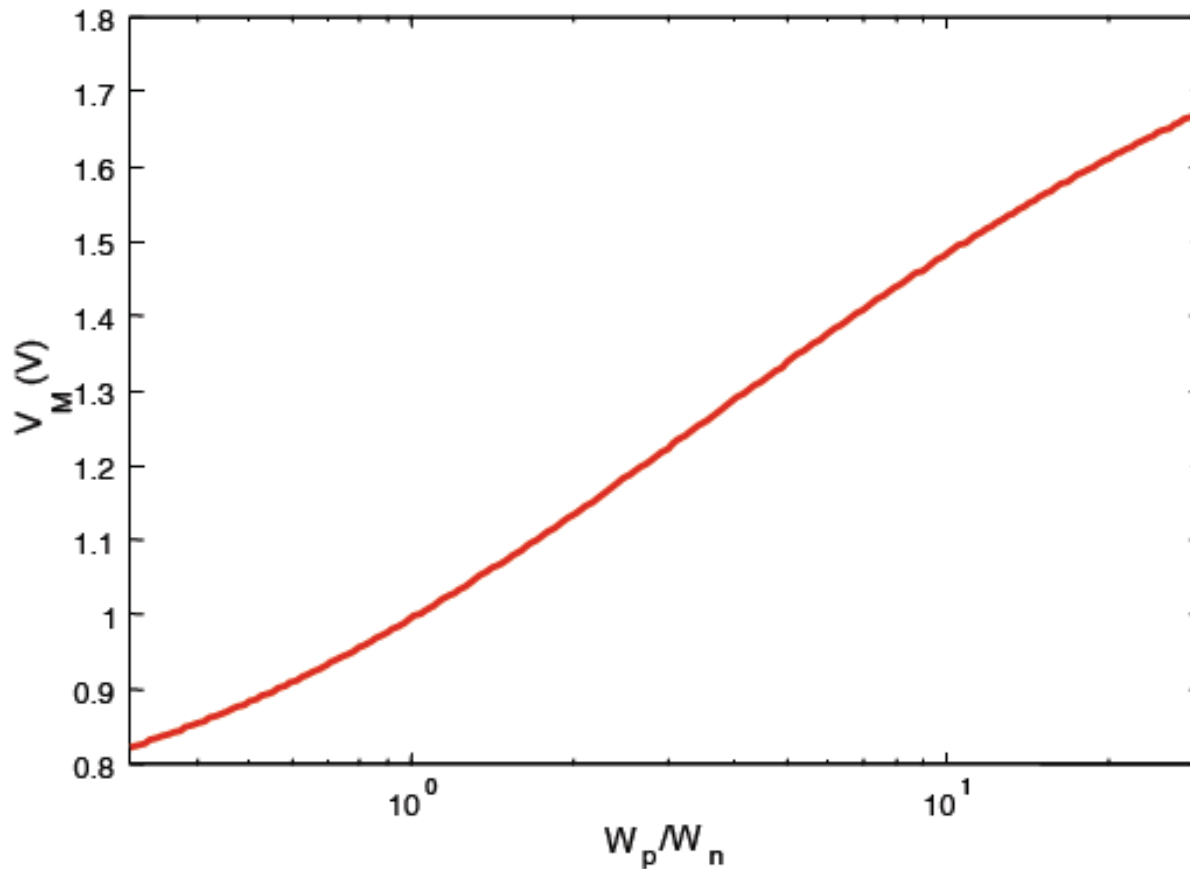
Switching Threshold as a Function of Transistor Ratio




$$I_{dn}(V_M) = I_{dp}(V_M)$$

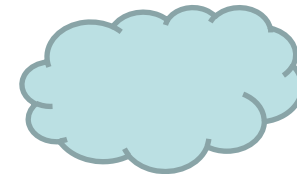

Impact of Sizing

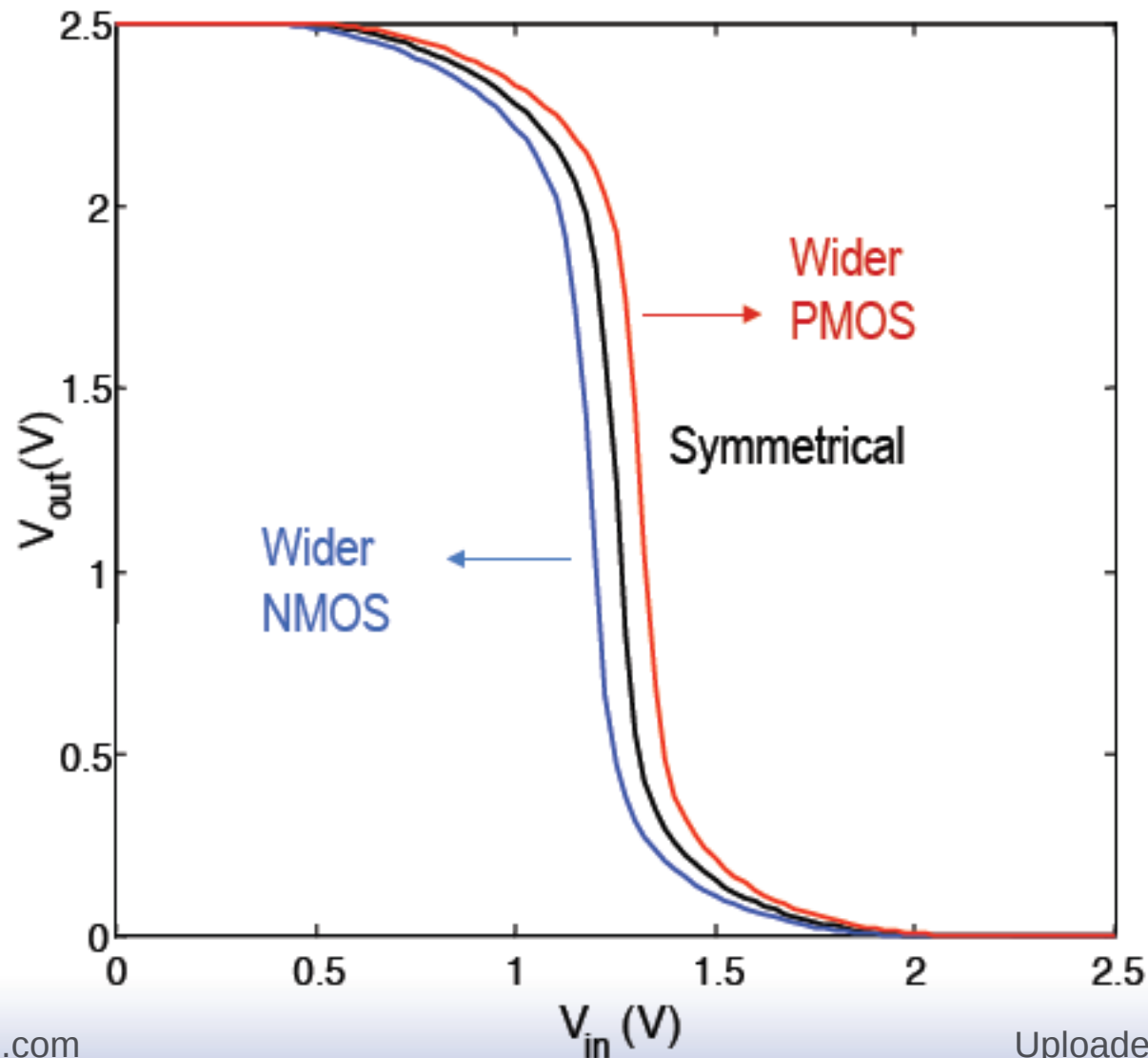

DC inverter Characteristics

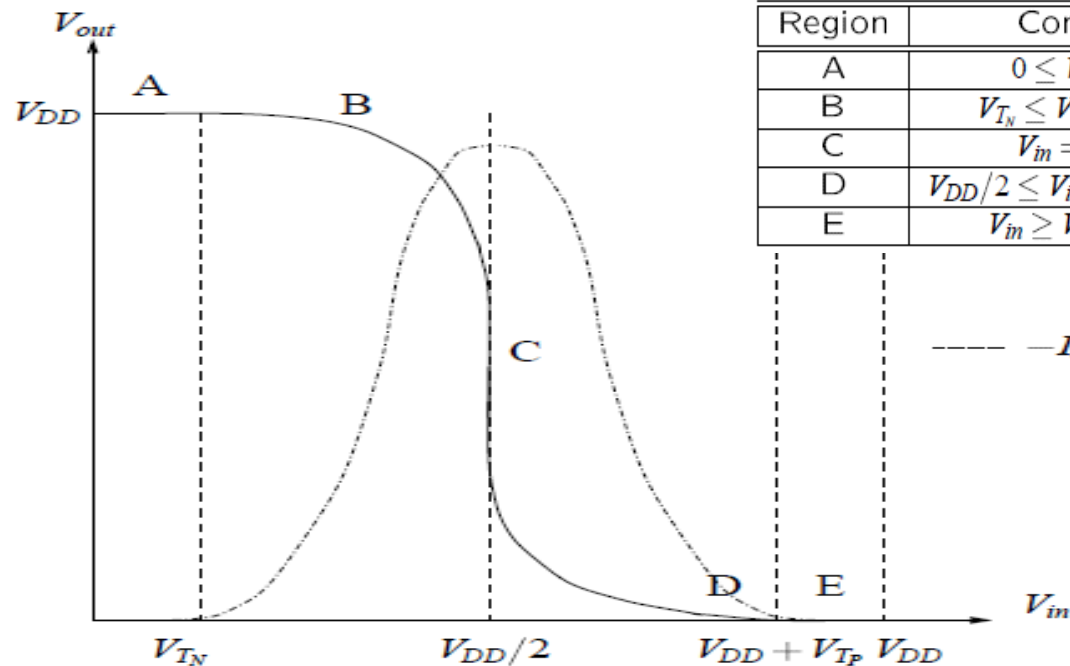

Region	Condition	PMOS	NMOS	V_{out}
A	$0 \leq V_{in} \leq V_{T_N}$	linear	cutoff	V_{DD}
B	$V_{T_N} \leq V_{in} \leq V_{DD}/2$	linear	sat	see below
C	$V_{in} = V_{DD}/2$	sat	sat	$V_{out} \neq f(V_{in})$
D	$V_{DD}/2 \leq V_{in} \leq V_{DD} - V_{T_P} $	sat	linear	see below
E	$V_{in} \geq V_{DD} - V_{T_P} $	cutoff	linear	0

- NMOS is easy to see, but how do we determine PMOS device state? For this, assume an inverter with $V_{DD} = 5V$, $V_{T_N} = -V_{T_P} = 1V$.


Regions A, B, C, D and E based on state of P and N devices

DC characteristics, so no capacitors involved. We will talk about capacitors when we consider AC characteristics.

V_{in}	$V_{gsP} - V_{T_P}$	Relation	V_{dsP}	Device state
0	$-5 + 1$	$<$	0	linear
1	$-4 + 1$	$<$	~ -1	linear
2.5	$-2.5 + 1$	$>$	~ -2.5	saturation
4	$-1 + 1$	$>$	~ -4	saturation
5	$0 + 1 \geq 0$	-	-	cutoff

MOS Transistor as a Switch


- Discharging a capacitor

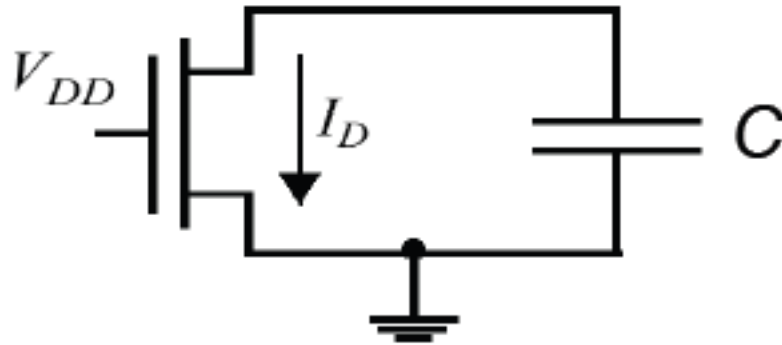

$$i_D = i_D(v_{DS})$$

$$i_D = C \frac{dV_{DS}}{dt}$$

- We modeled this with:

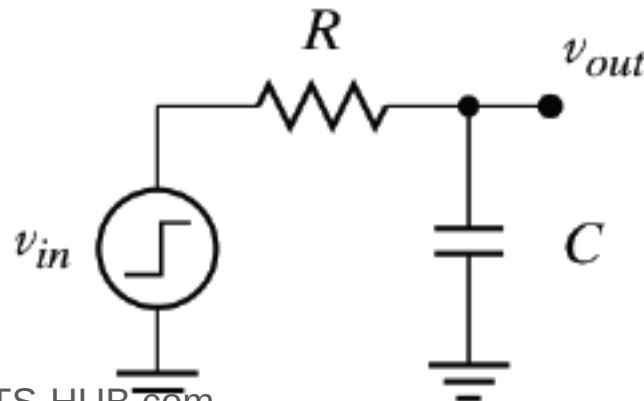



$$t_p = \ln(2) RC$$

MOS Transistor as a Switch

- ❑ Real transistors aren't exactly resistors
 - Look more like current sources in saturation
- ❑ Two questions:
 - Which region of IV curve determines delay?
 - How can that match up with the RC model?

Transistor Discharging a Capacitor



- With a step input:

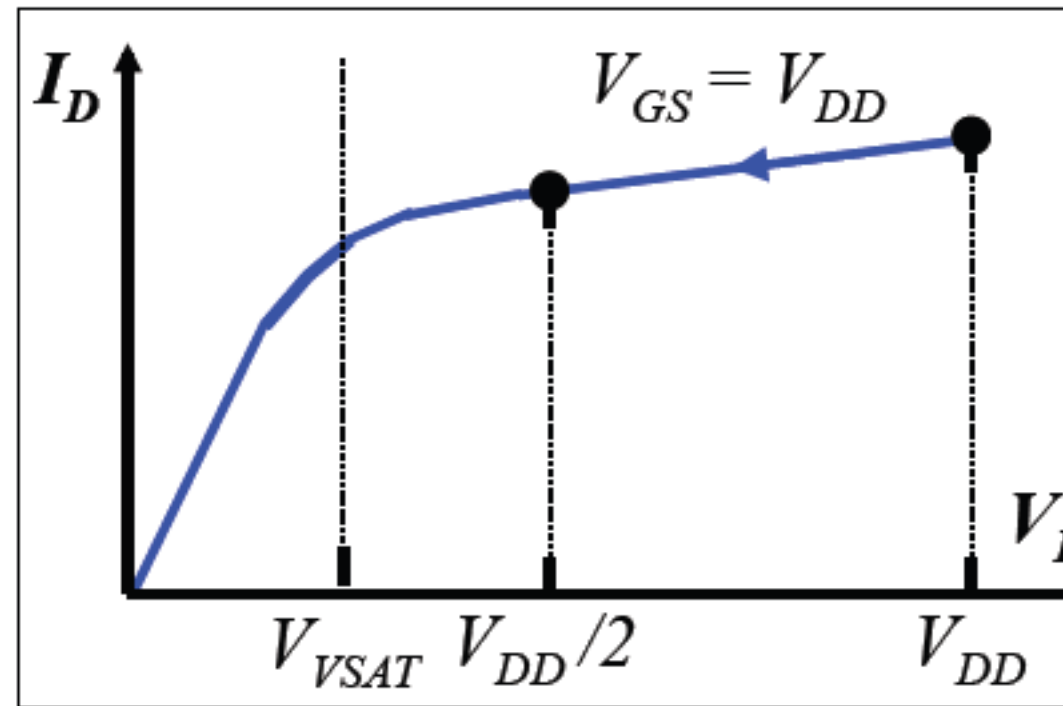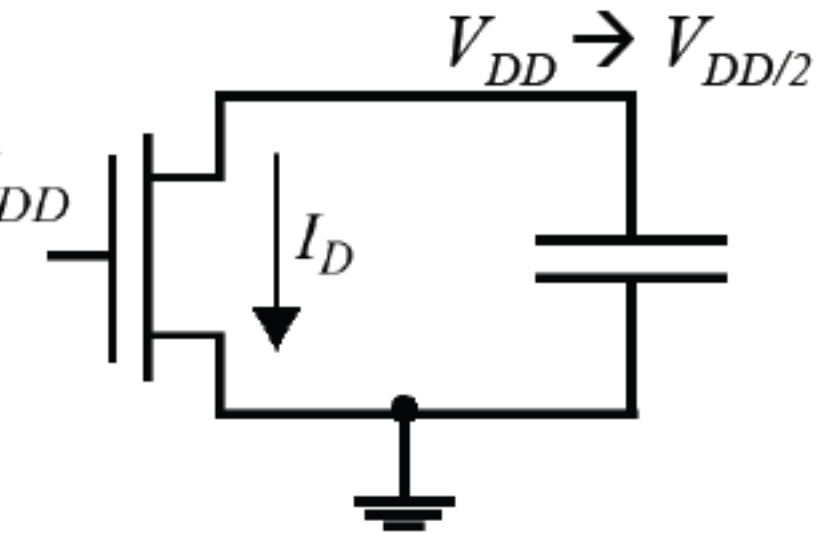

Transistor is in (velocity) saturation during entire transition from V_{DD} to $V_{DD}/2$

Switching Delay

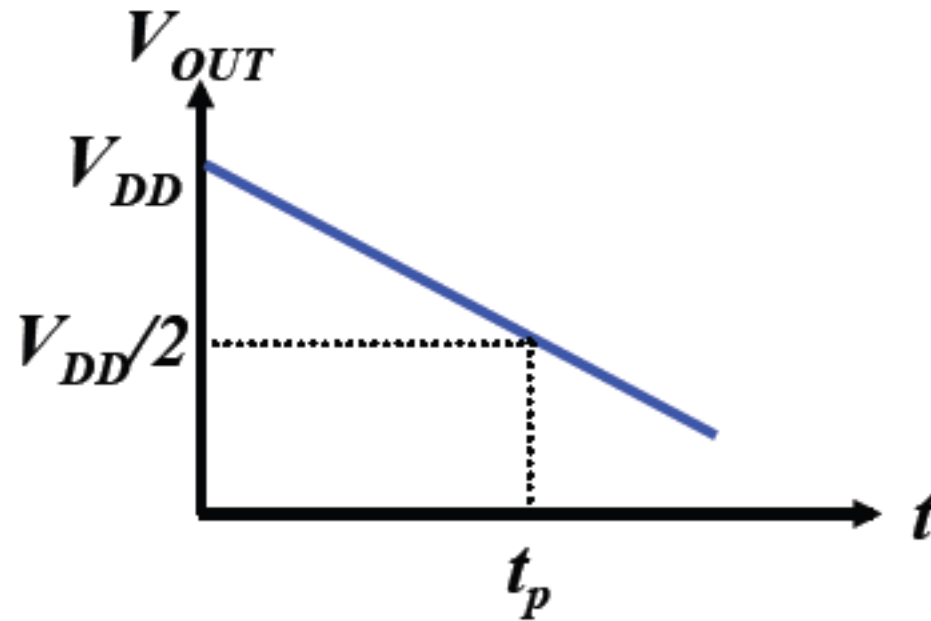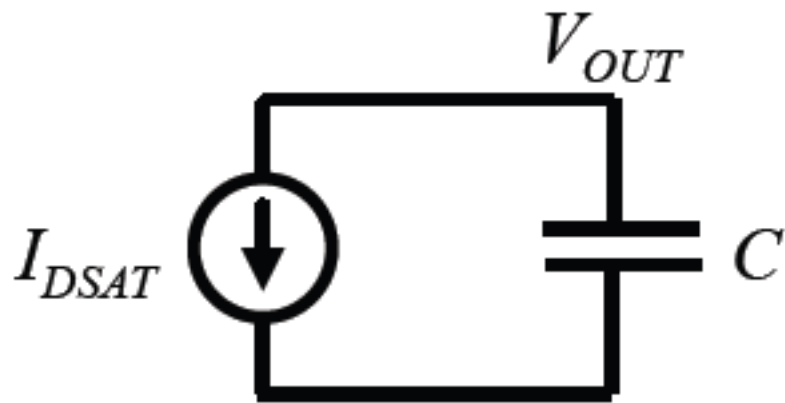
- In saturation, transistor basically acts like a current source



$$V_{OUT} = V_{DD} - (I_{DSAT}/C)t \longrightarrow \boxed{t_p = C(V_{DD}/2)/I_{DSAT}}$$

Switching Delay (with Output Conductance)

- Including output conductance:

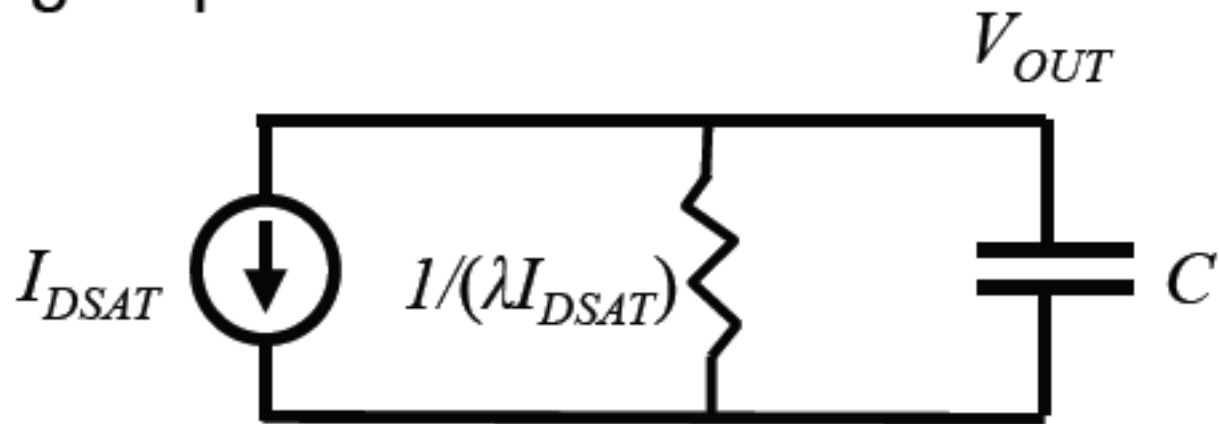


$$V_{OUT} = (V_{DD} + \lambda^{-1}) e^{-t/(C/\lambda I_{DSAT})} - \lambda^{-1}$$

- For “small” λ :

$$t_p \approx \frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}}$$

The Transistor as a Switch


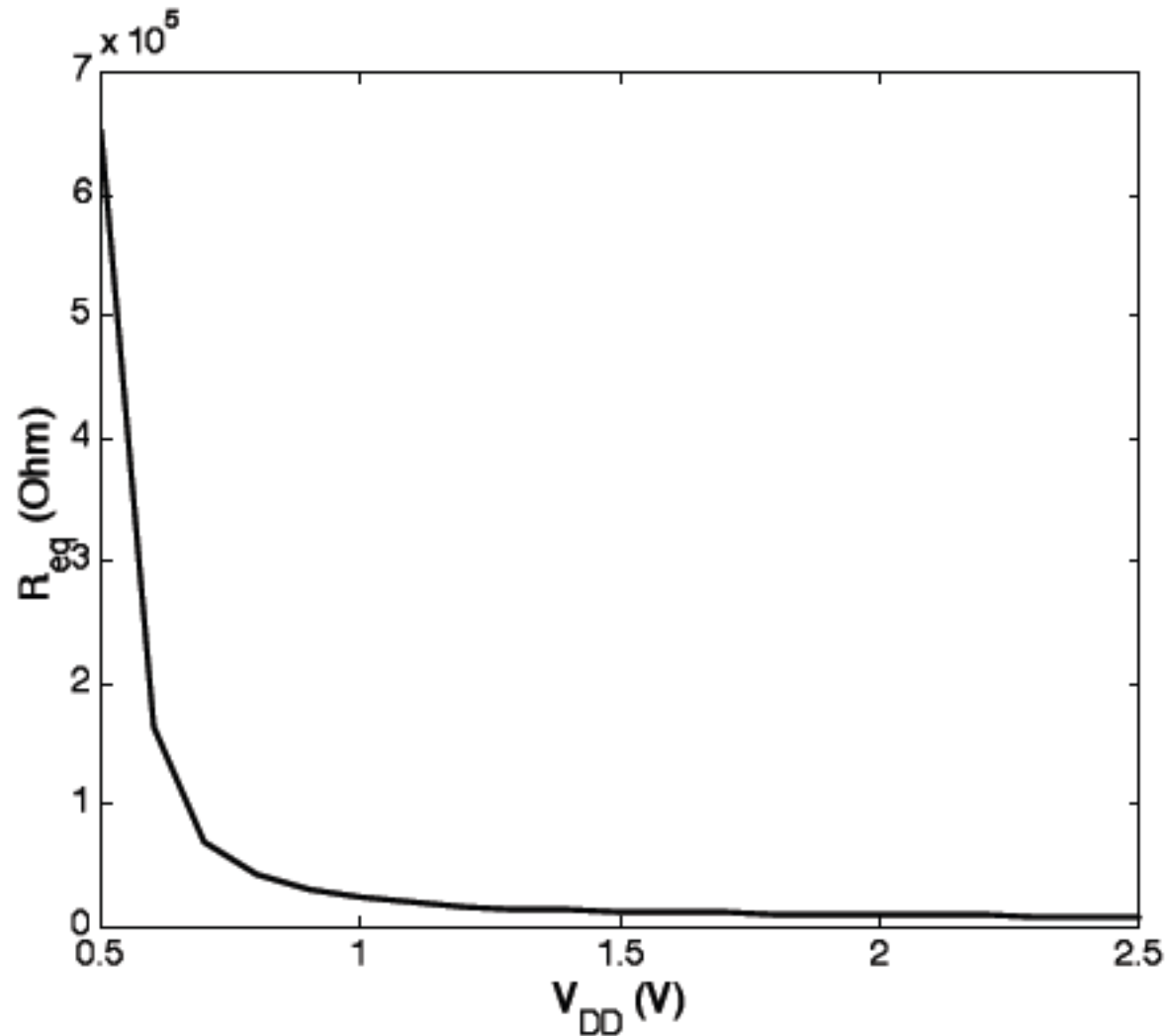


The Transistor as a Switch


Table 3.3 Equivalent resistance R_{eq} ($W/L = 1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L = L_{min}$). For larger devices, divide R_{eq} by W/L .

V_{DD} (V)	1	1.5	2	2.5
NMOS ($k\Omega$)	35	19	15	13
PMOS ($k\Omega$)	115	55	38	31

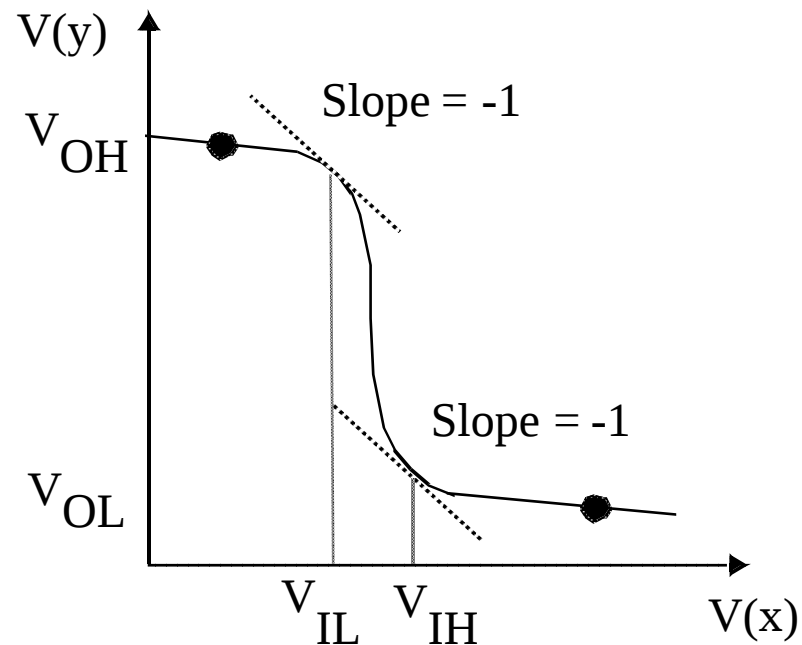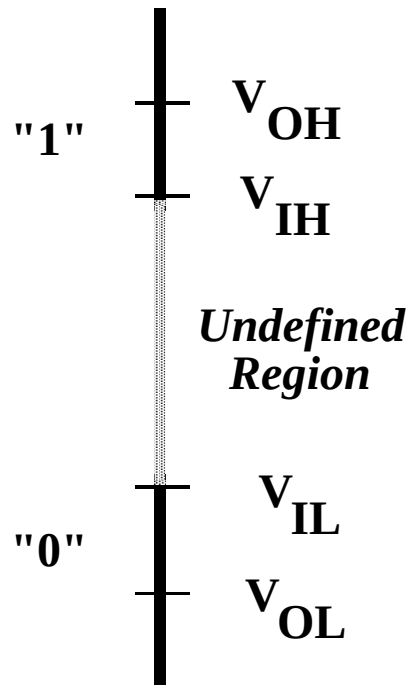Mapping between analog and digital signals







Definition of Noise Margins

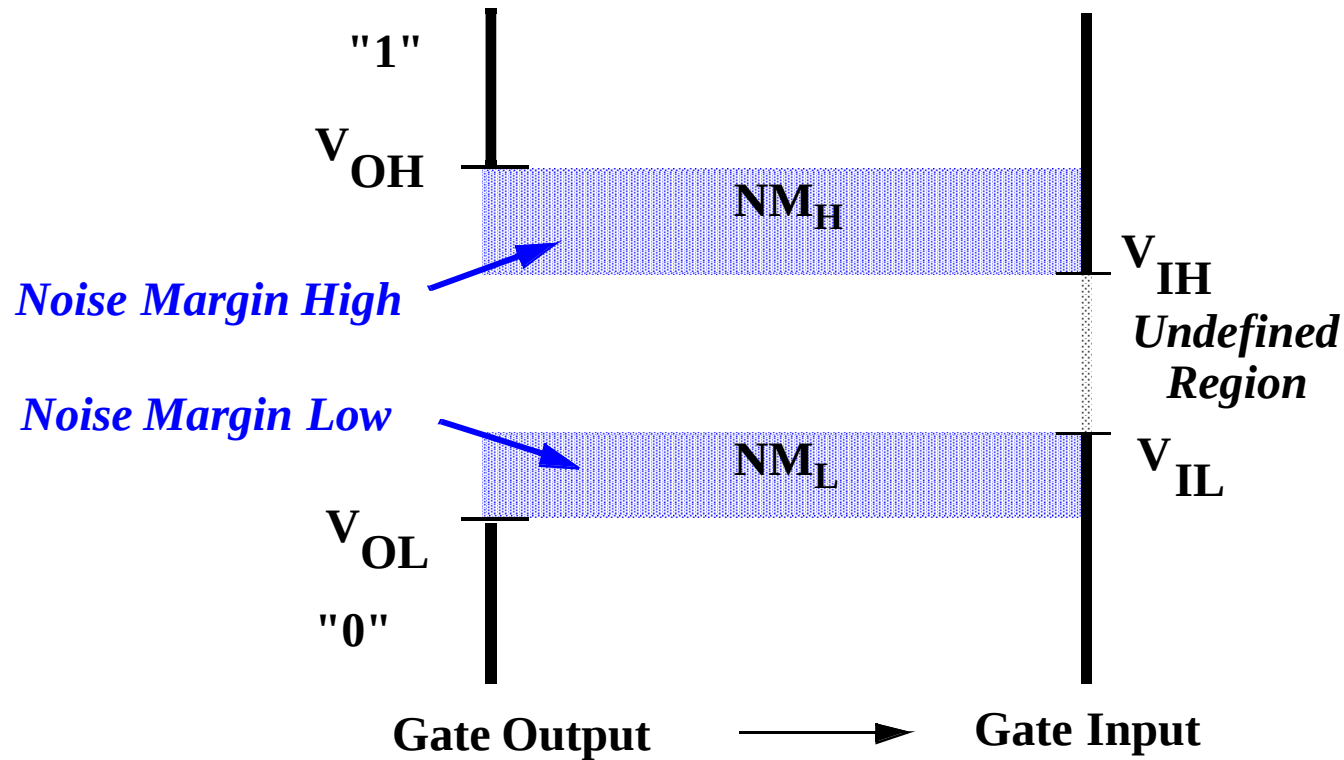


Noise Margin

- NM_H and NM_L are the high-side and low-side noise margins.
- The high output excursion should **not** be larger than the high input excursion. Same for the low excursions. If this is violated, then the corresponding noise margin is negative.
- Why worry about it? Perhaps the V_{DD} or GND of the driver glitches relative to the driven gate. In that situation, I want to know what magnitude of glitch can I tolerate before a wrong value is interpreted.

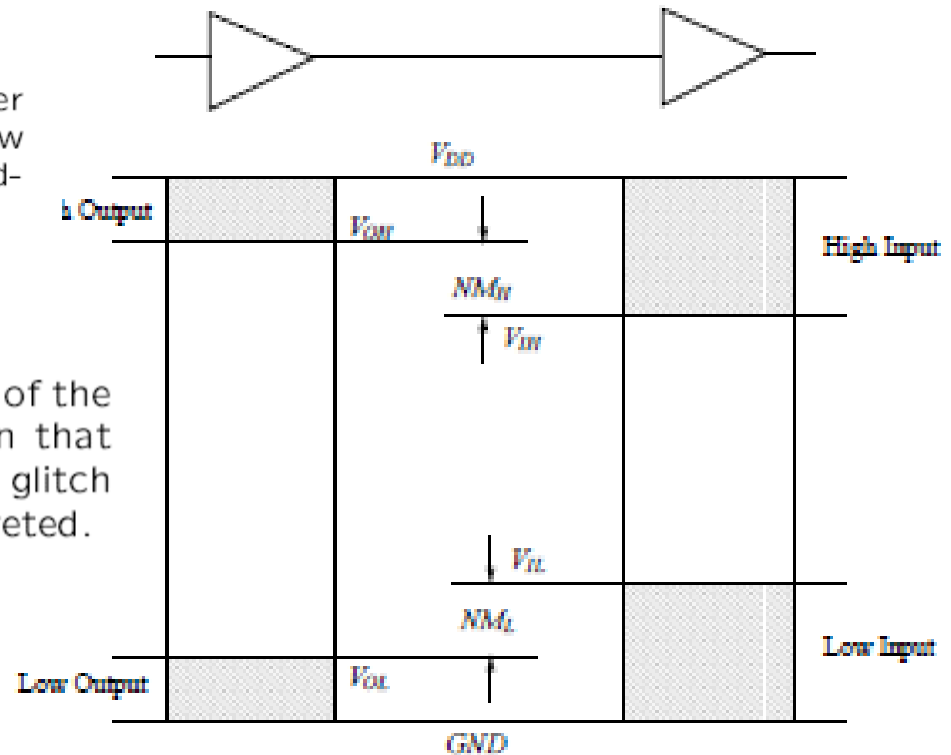


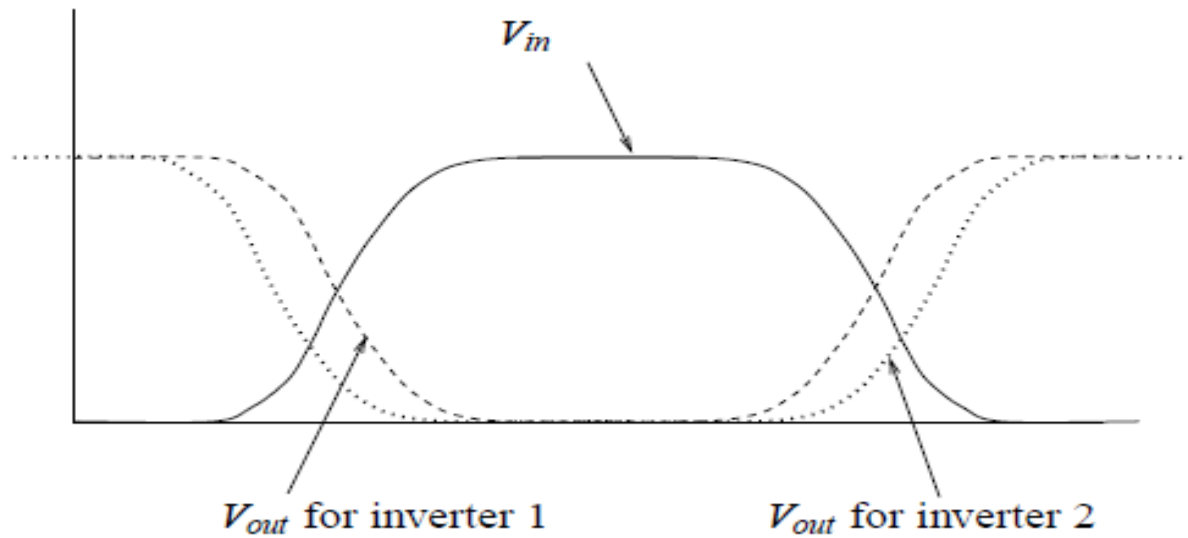
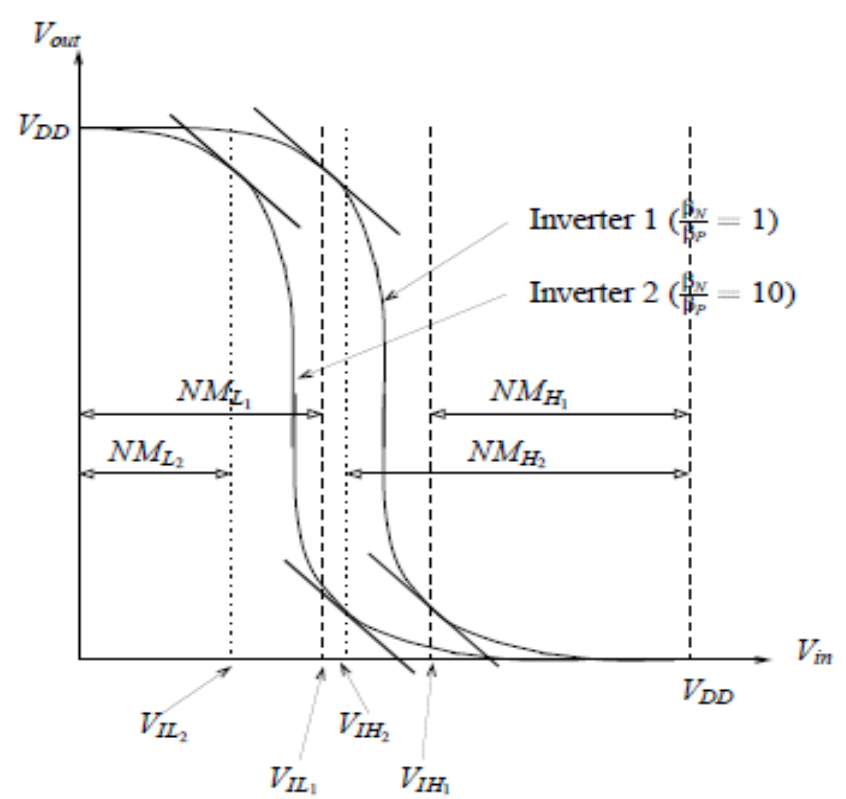
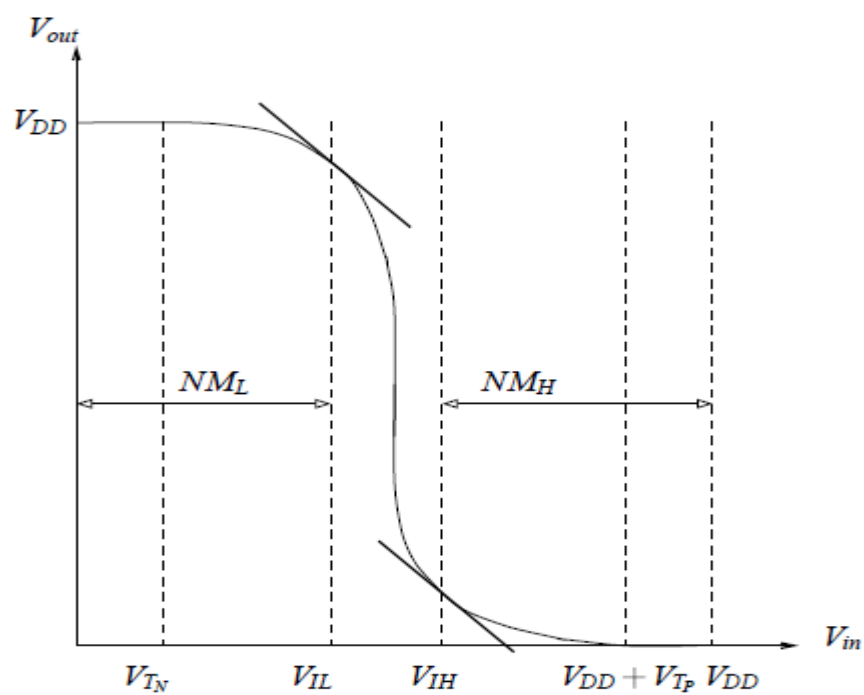


The Ideal Gate

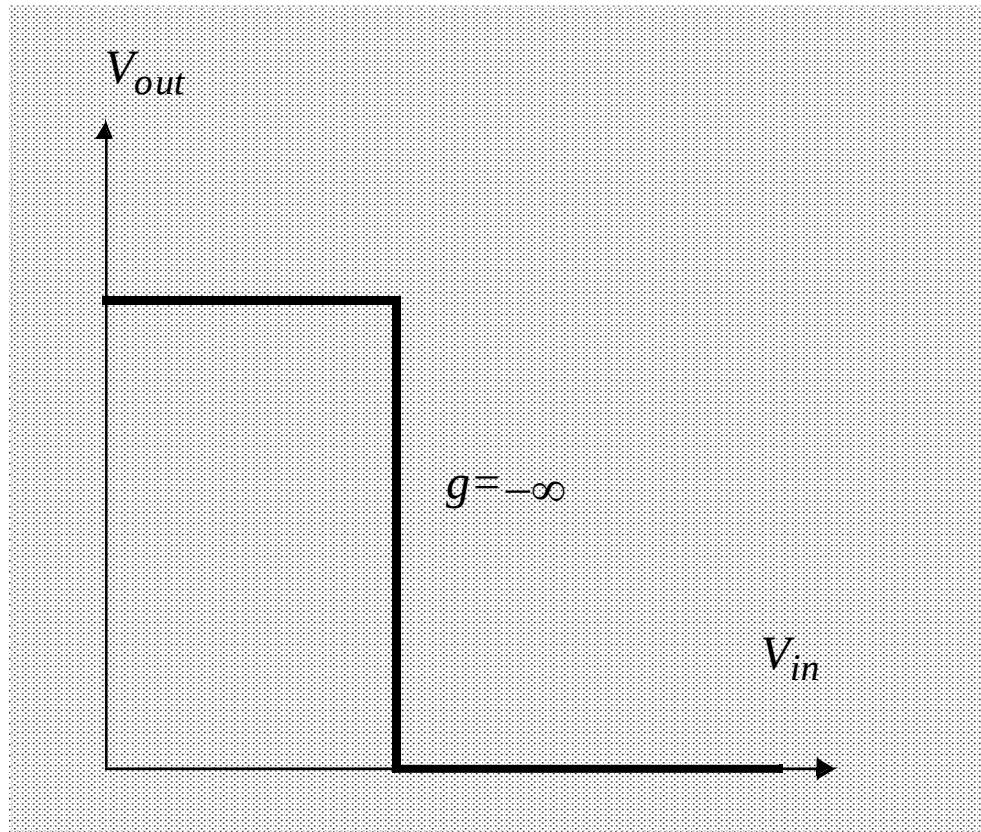


$$R_i = \infty$$


$$R_o = 0$$

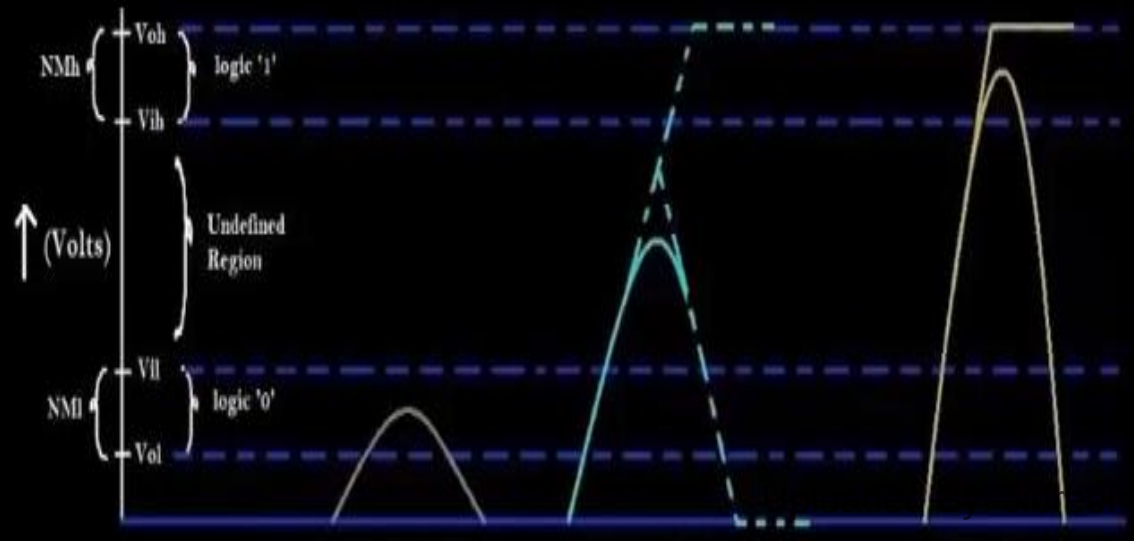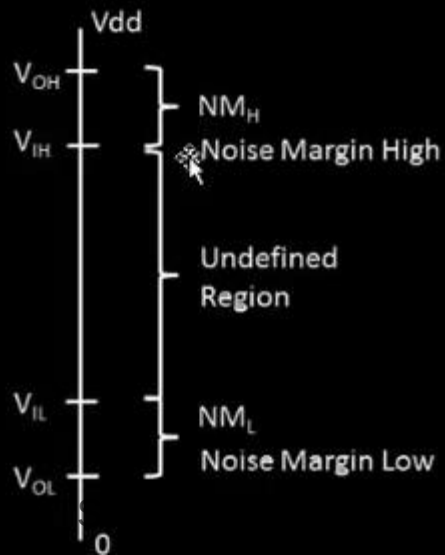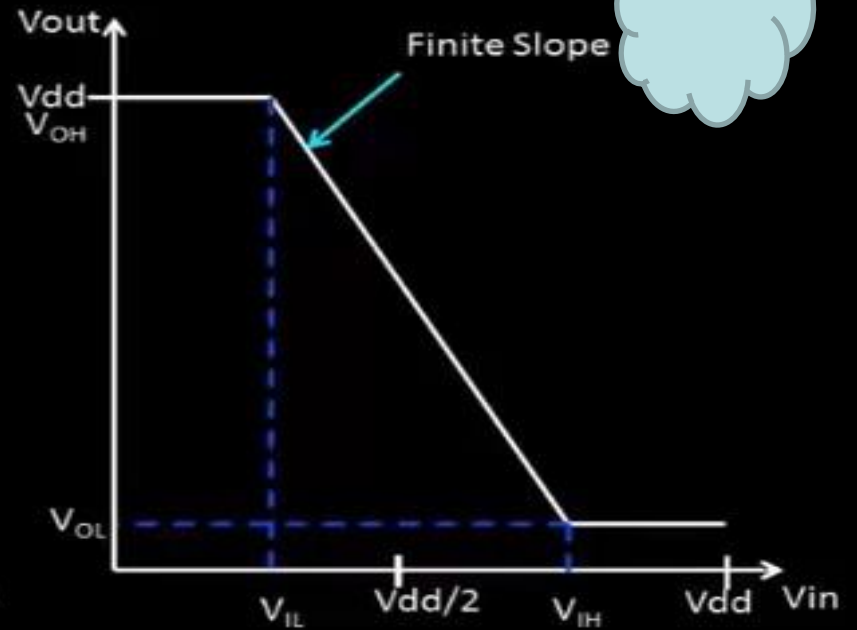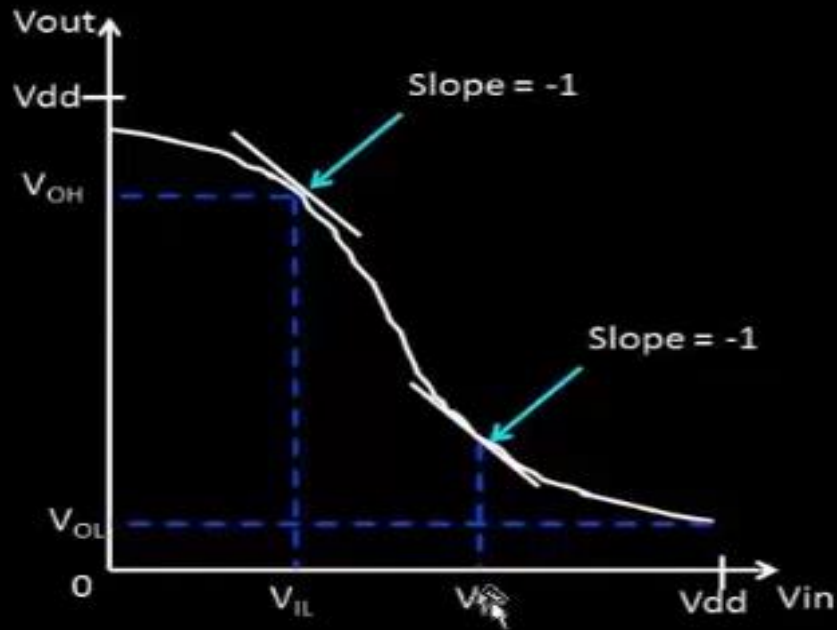


The Regenerative Property

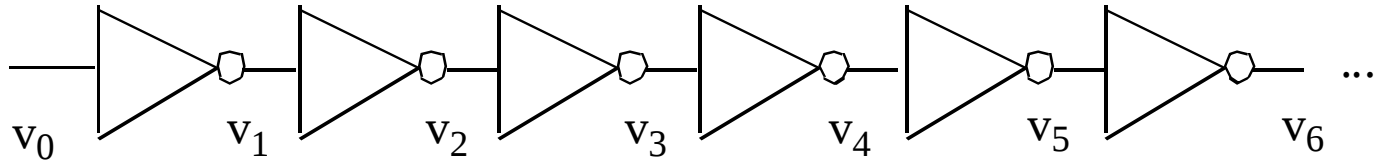

(a) A chain of inverters.


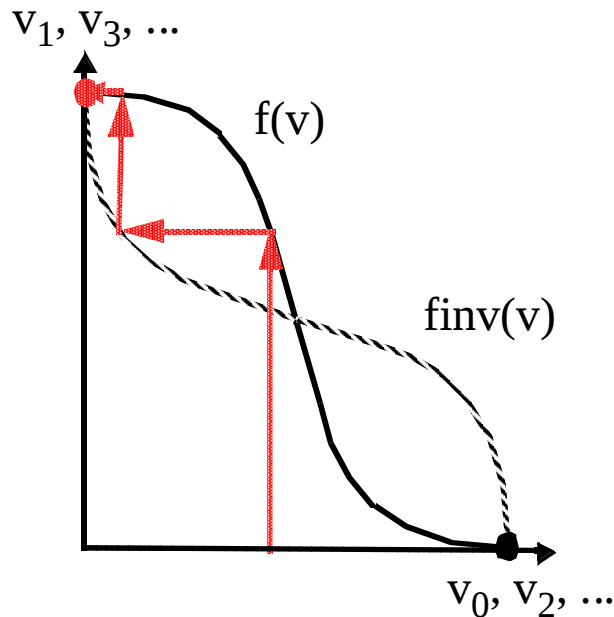


(b) Regenerative gate

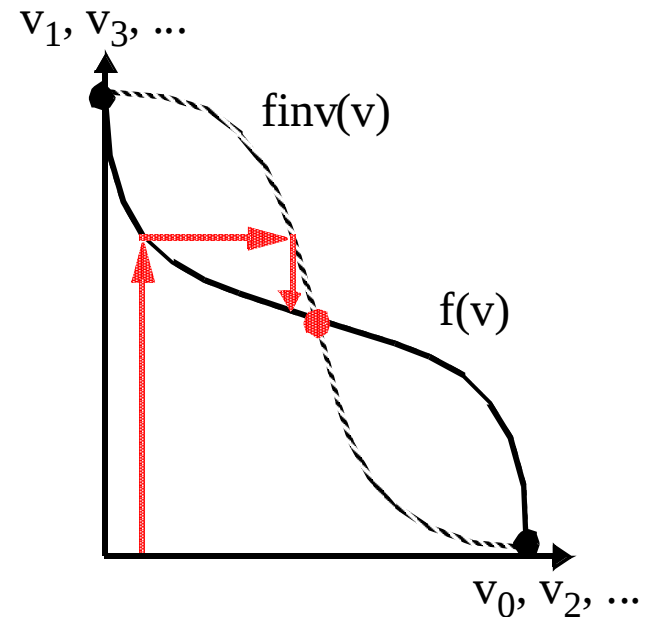


(c) Non-regenerative gate


Fan-in and Fan-out

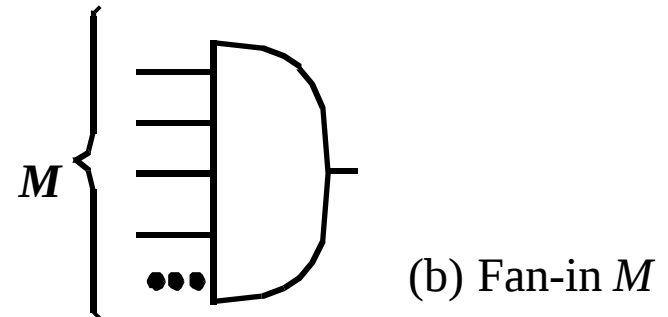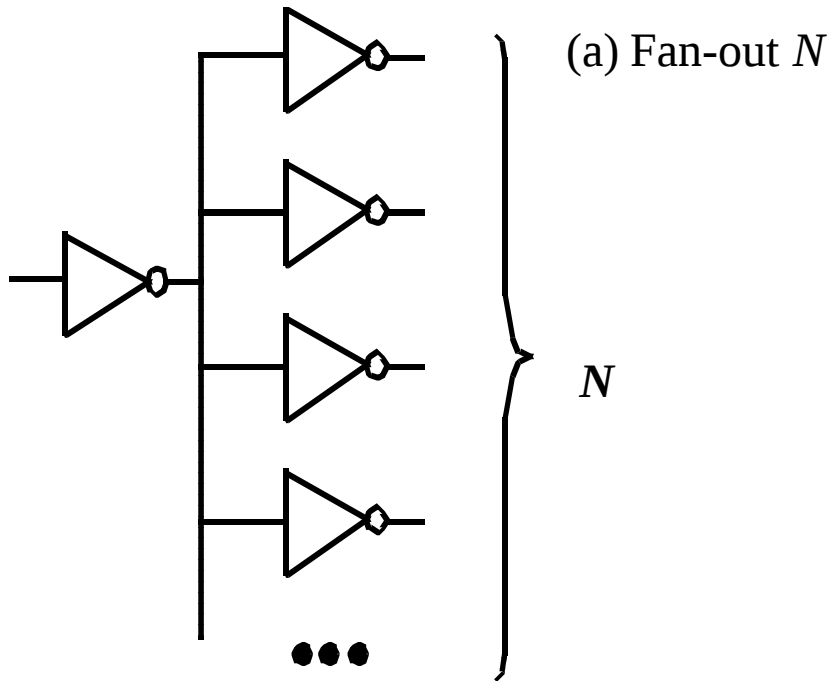



VTC of Real Inverter

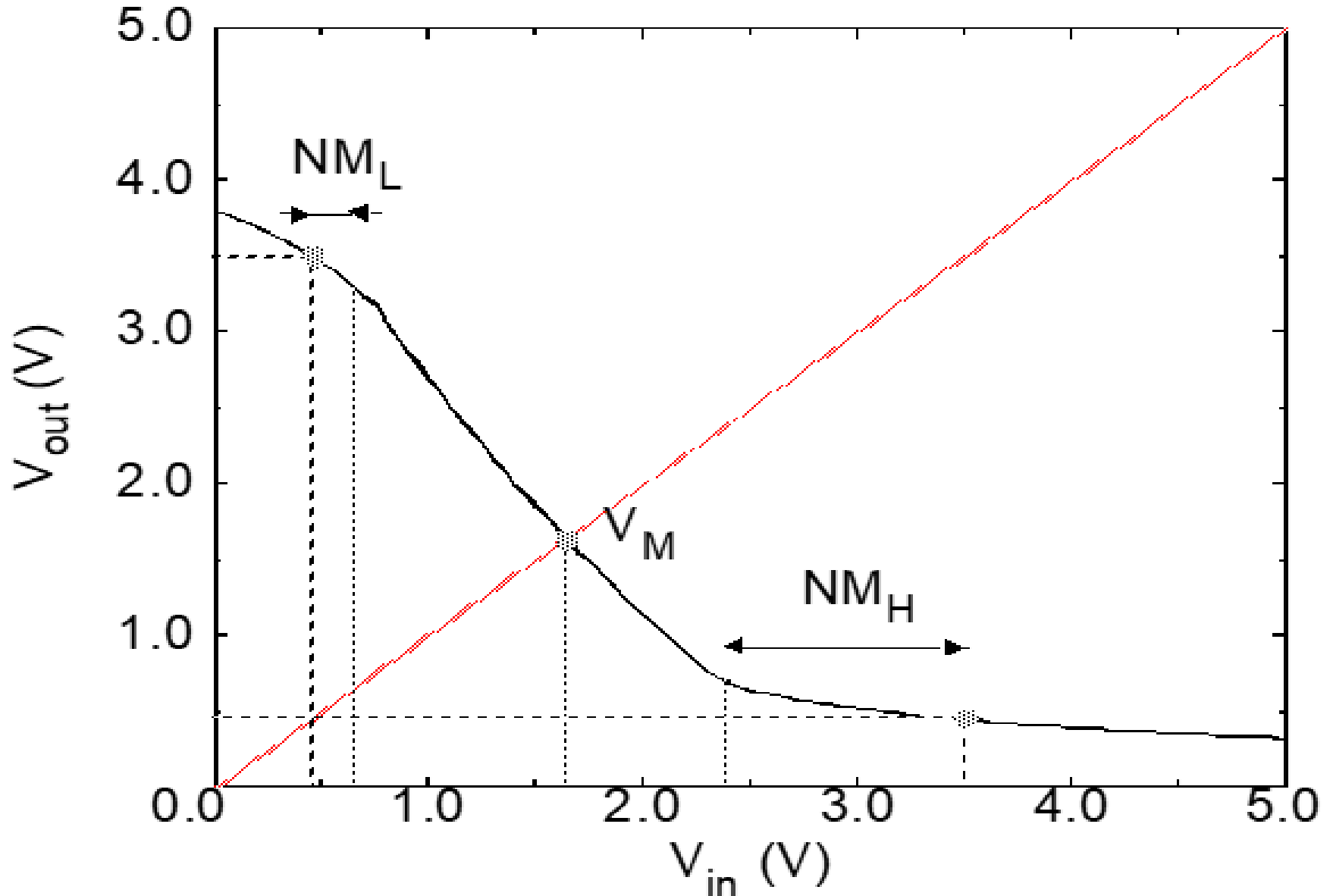

Delay Definitions

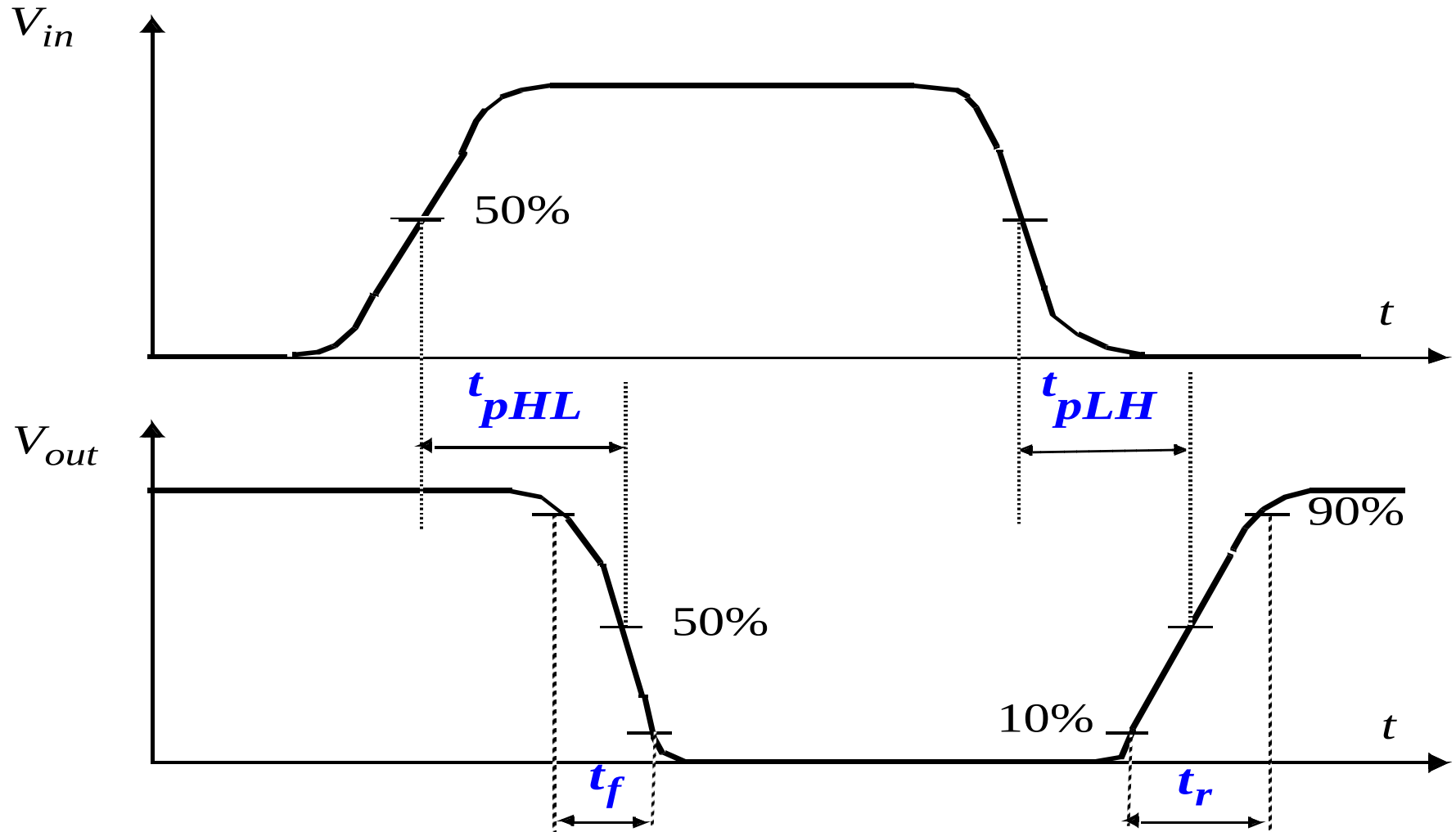

Ring Oscillator

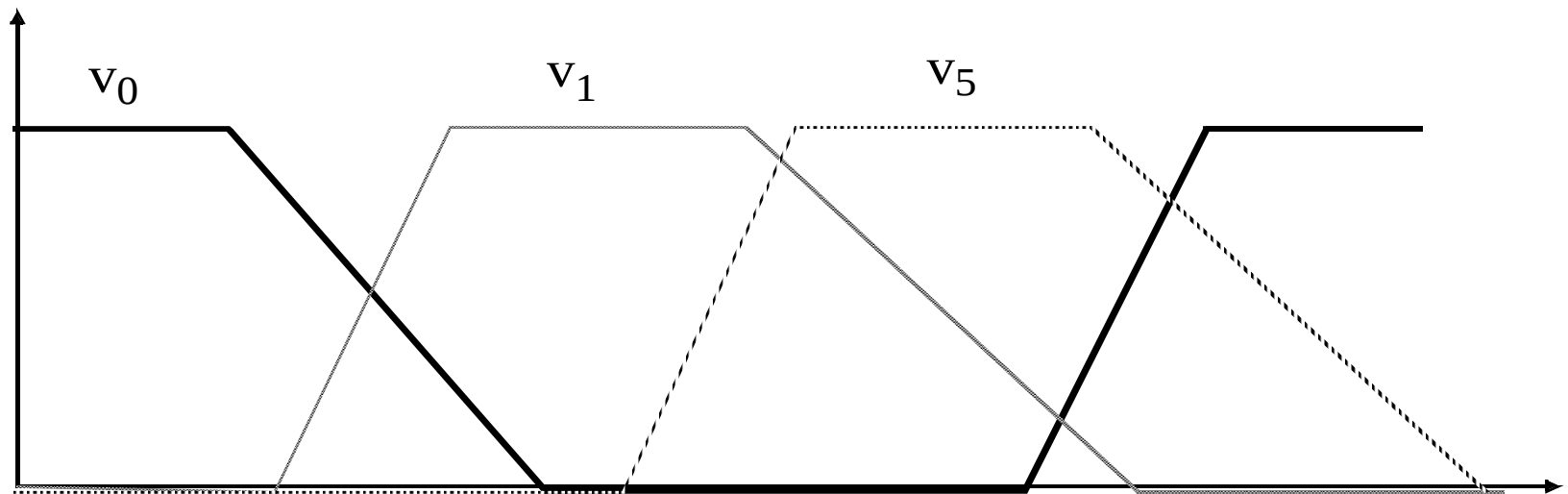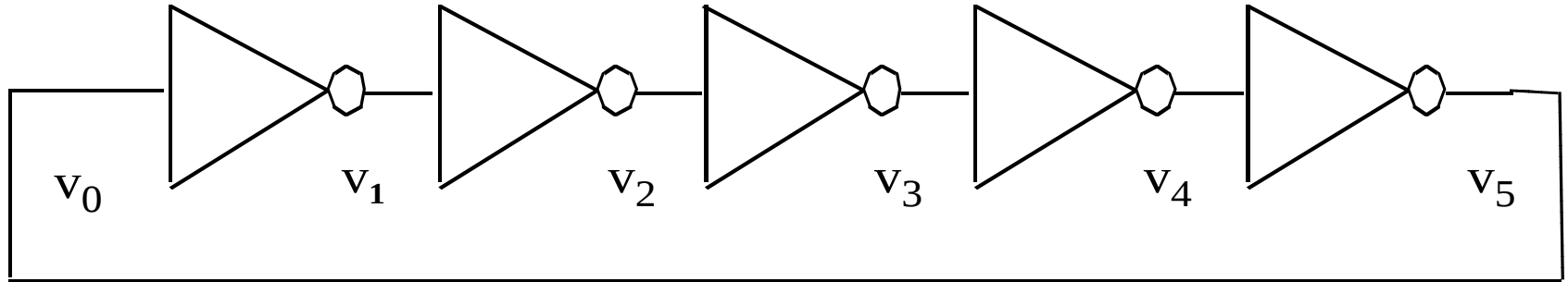

$$T = 2 \times t_p \times N$$

Power Dissipation

$$P_{peak} = i_{peak} V_{supply} = \max(p(t))$$

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_{supply}}{T} \int_0^T i_{supply}(t) dt$$

Power-Delay Product

$$PDP = t_p \times P_{av}$$


= Energy dissipated per operation


CMOS Properties

- Full rail-to-rail swing
- Symmetrical VTC
- Propagation delay function of load capacitance and resistance of transistors
- No static power dissipation
- Direct path current during switching


Voltage Transfer Characteristic

CMOS Inverter Load Characteristics

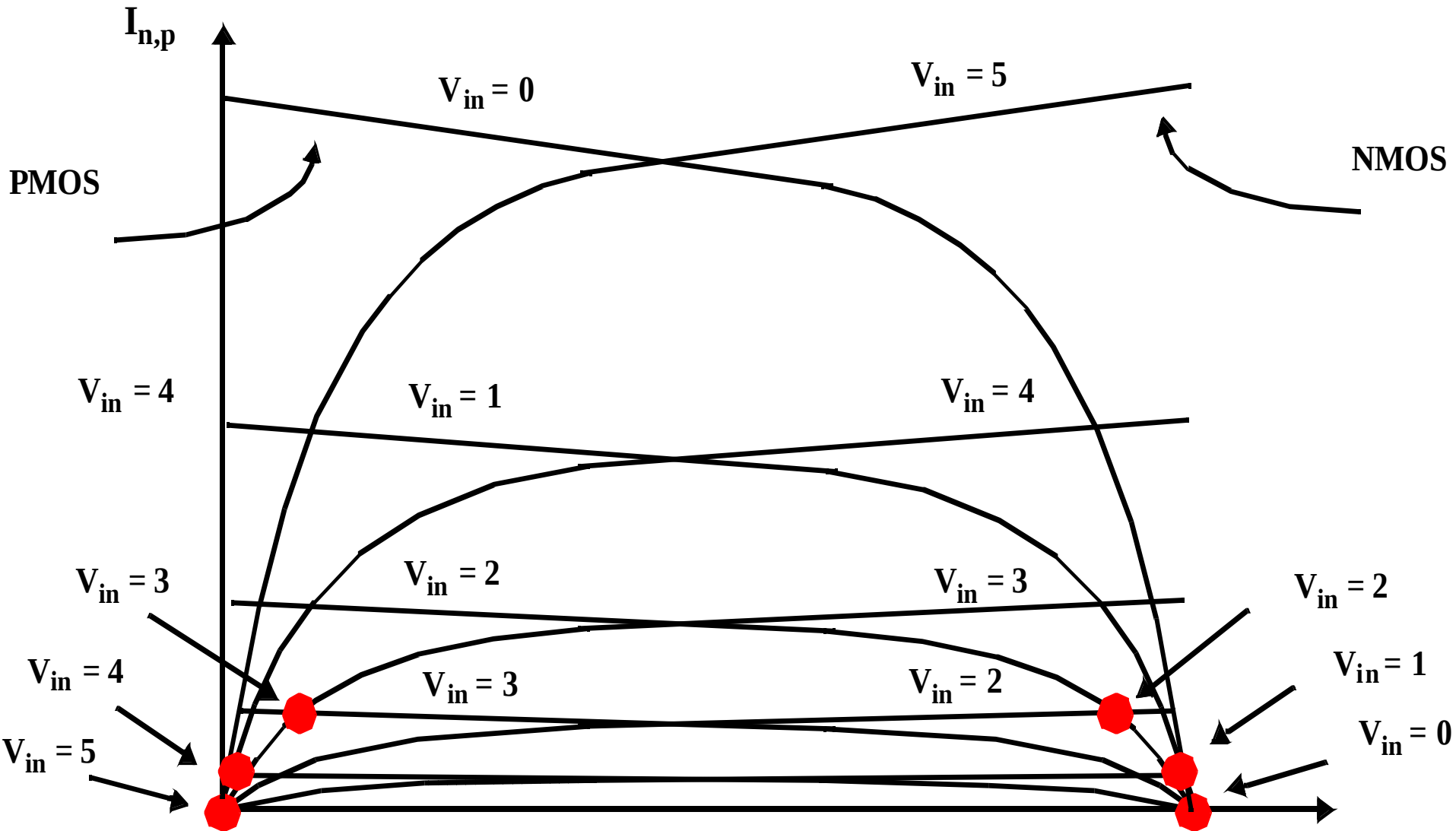


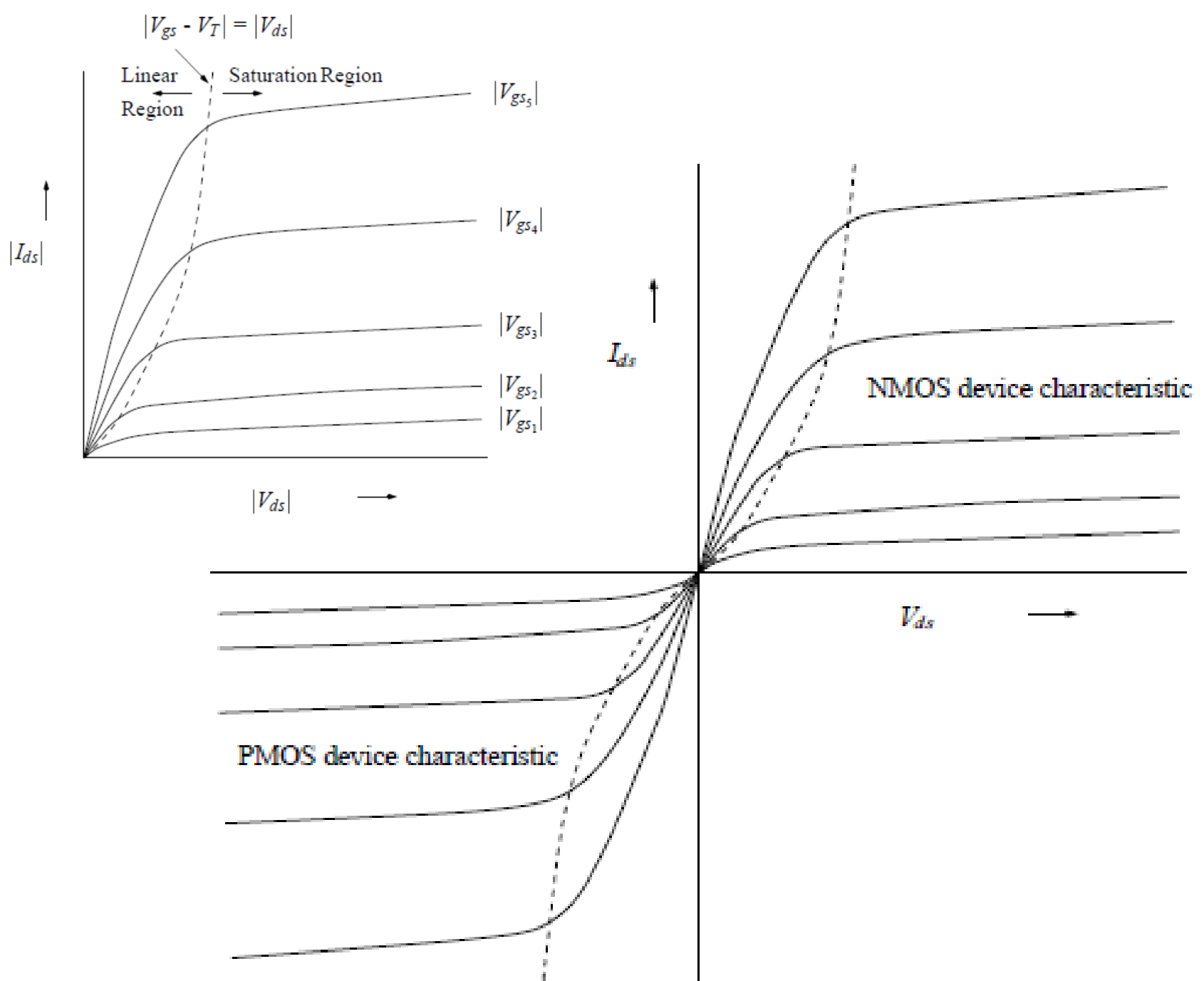

Simulated VTC

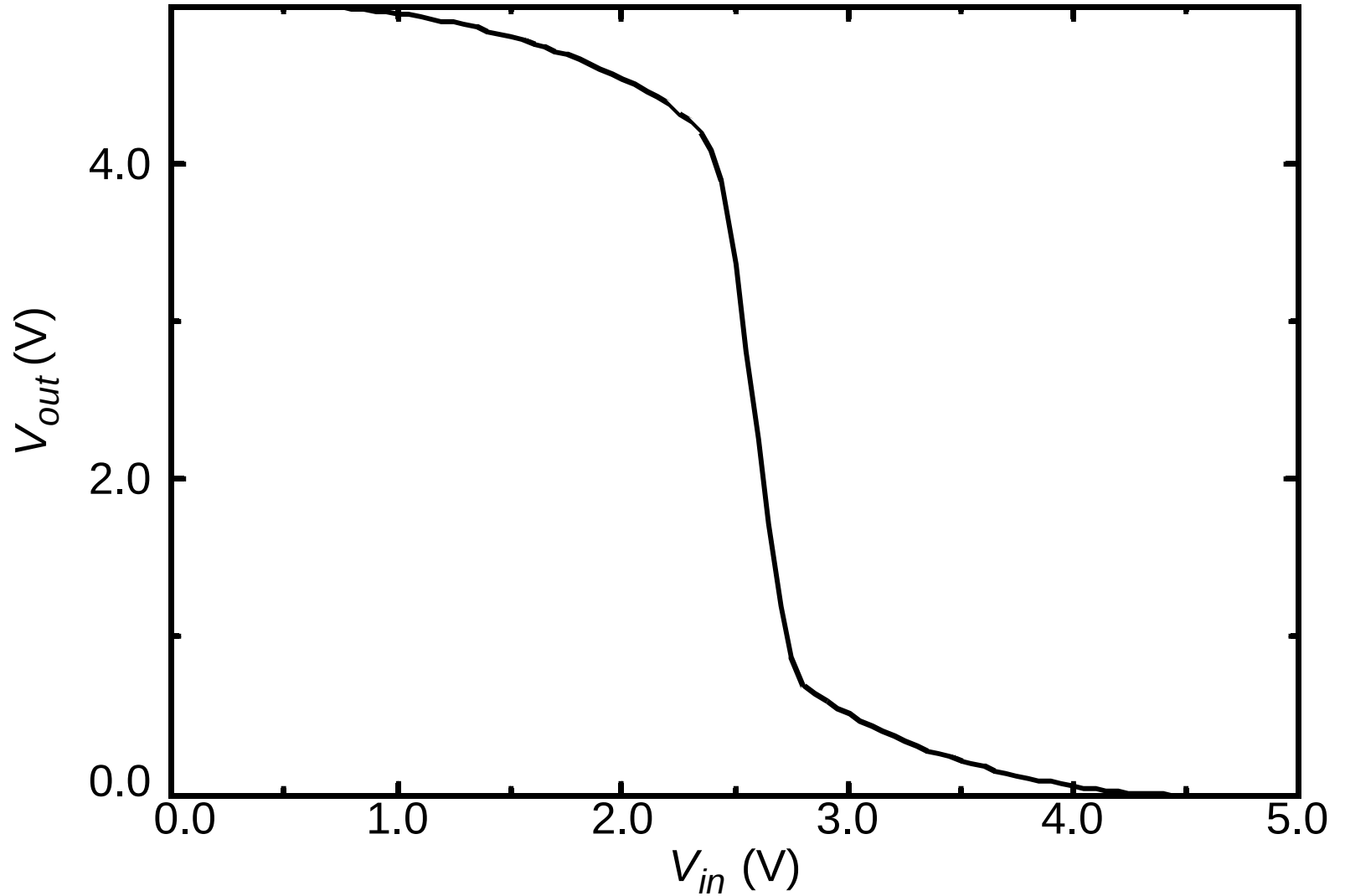

Gate Switching Threshold

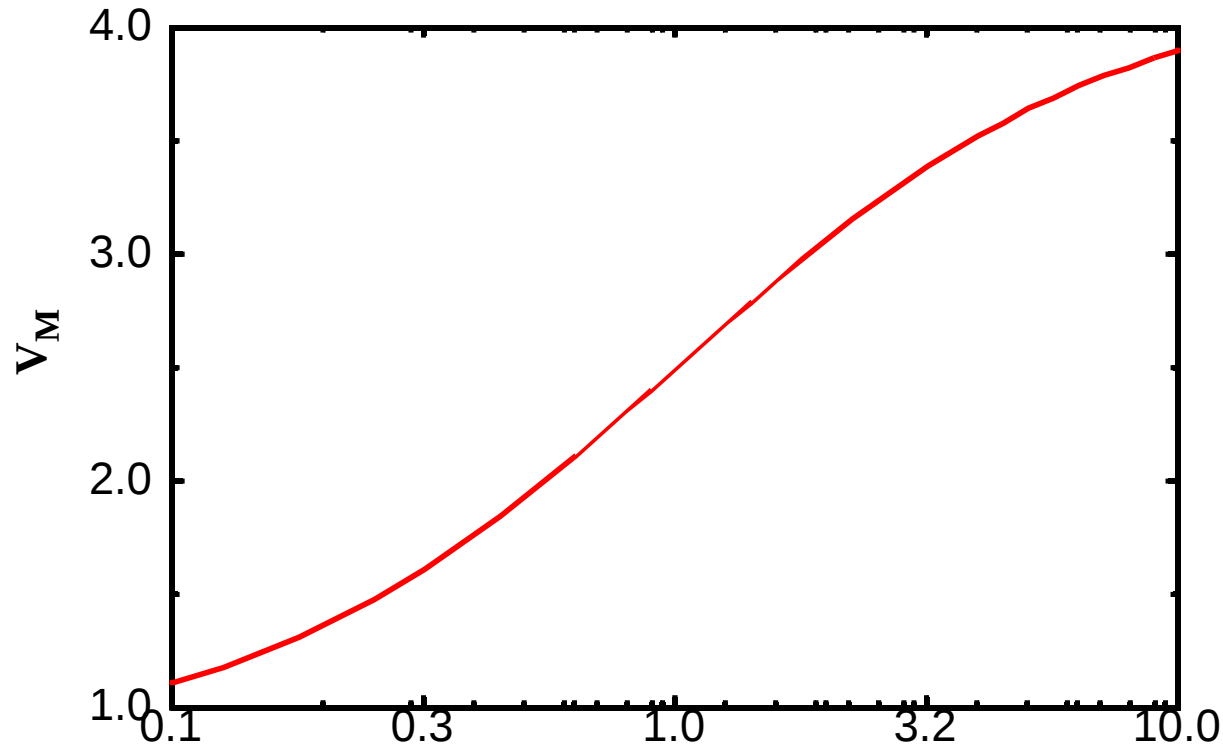

$$V_M = \frac{r(V_{DD} - |V_{Tp}|) + V_{Tn}}{1 + r} \quad \text{with} \quad r = \sqrt{\frac{k_p}{k_n}}$$

CMOS Inverter VTC

- In linear region :

- Channel resistance = $R_{c_{lin}} =$

$$\lim_{V_{ds} \rightarrow 0} \left(\frac{dI_{ds}}{dV_{ds}} \right)^{-1}$$

$$= \frac{1}{\beta(V_{gs} - V_T)}$$


- Depends on V_{gs}

- Transconductance = $g_m = \left(\frac{dI_{ds}}{dV_{gs}} \right) = \beta V_{ds}$


- Higher current gain with higher V_{ds}

- In saturation region :

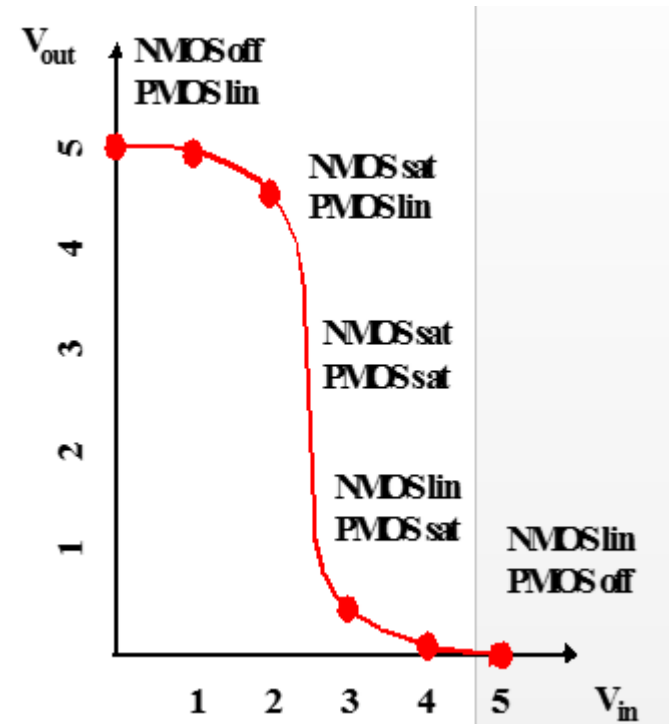- Transconductance = $g_m = \left(\frac{dI_{ds}}{dV_{gs}} \right) = \beta(V_{gs} - V_T)$



MOS Transistor Small Signal Model

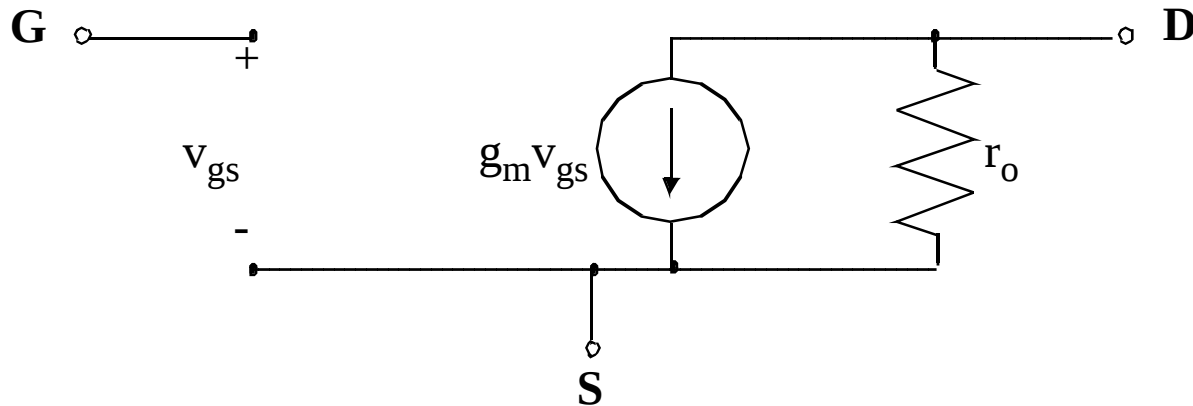


	g_m	r_o
linear	kV_{DS}	$[k(V_{GS}-V_T-V_{DS})]^{-1}$
saturation	$k(V_{GS}-V_T)$	$1/I_D$

Determining V_{IH} and V_{IL}

At V_{IH} (V_{IL}): $\frac{\partial V_{out}}{\partial V_{in}} = -1$


small-signal model of inverter

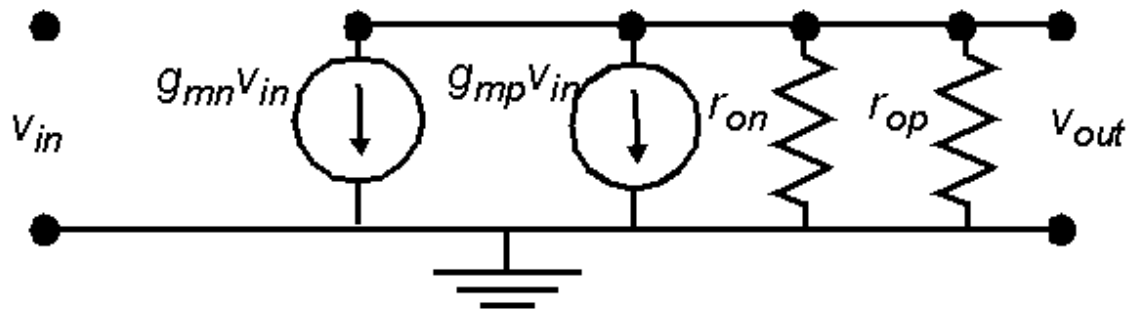


$$g = \frac{v_{out}}{v_{in}} = -(g_{mn} + g_{mp}) \times (r_{on} \parallel r_{op}) = -1$$

Propagation Delay


CMOS Inverter: Transient Response

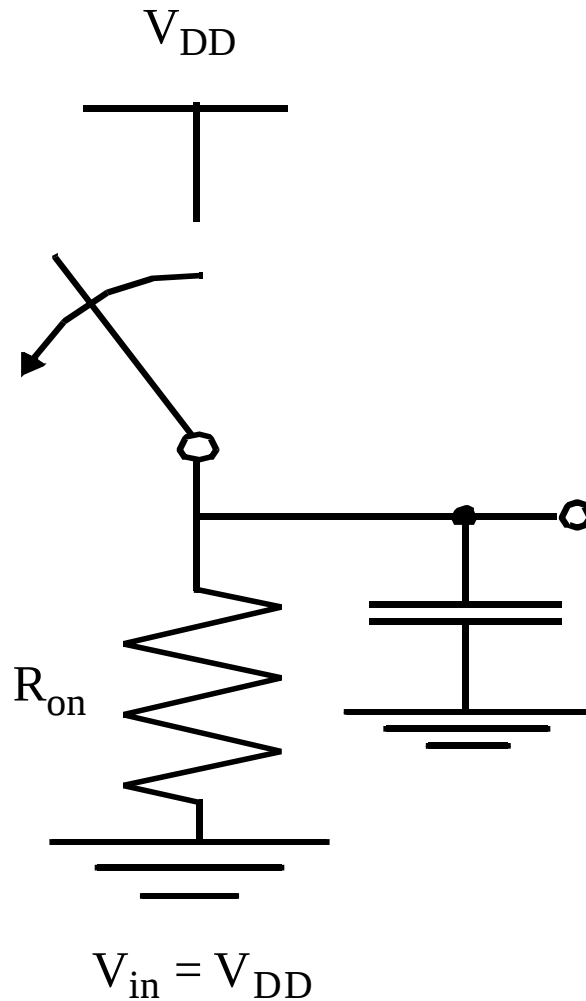
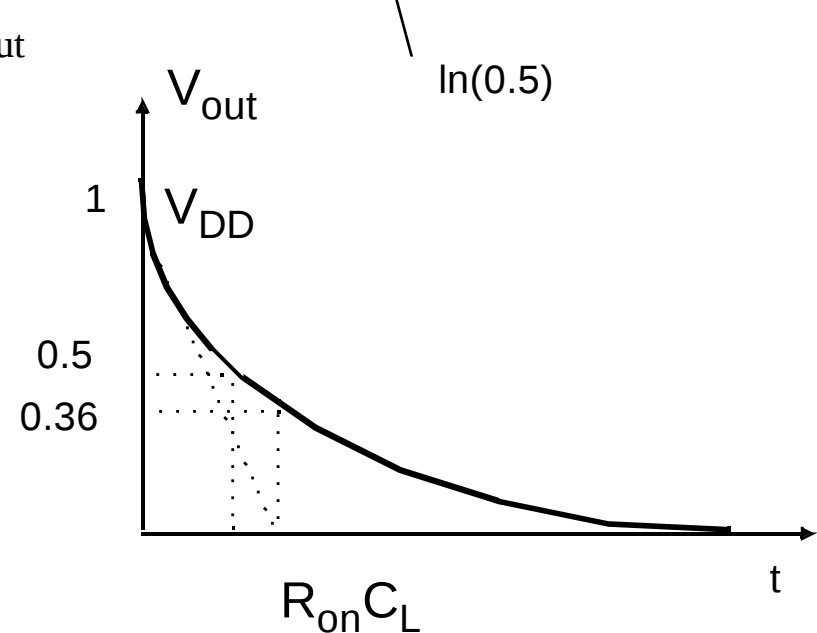
$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$





CMOS Inverter Propagation Delay

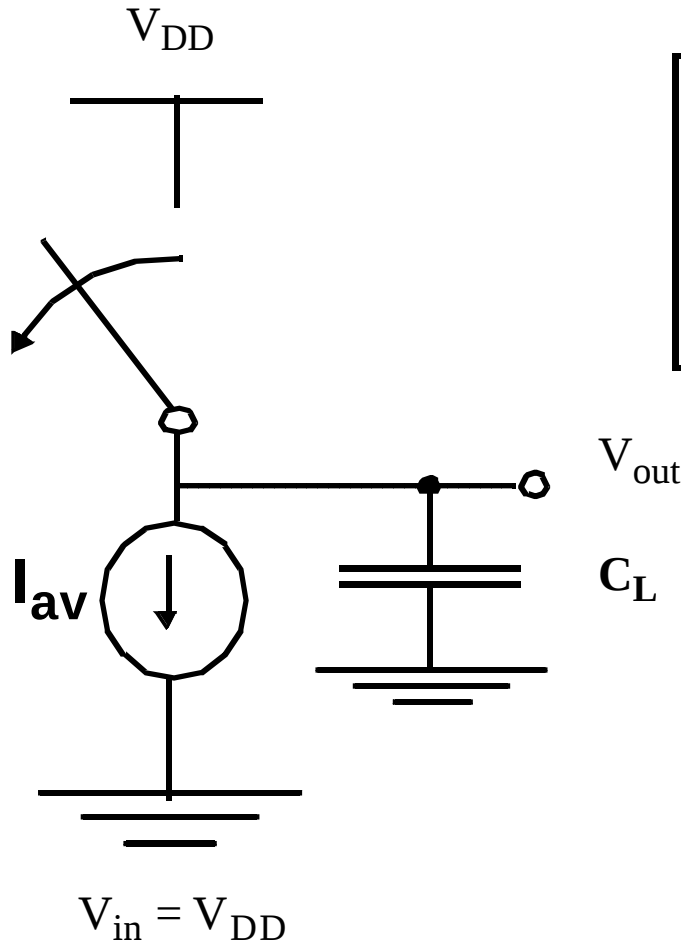


$$t_{pHL} = \frac{C_L V_{swing}/2}{I_{av}}$$

$$\sim \frac{C_L}{k_n V_{DD}}$$

Computing the Capacitances

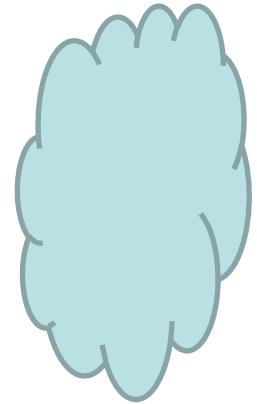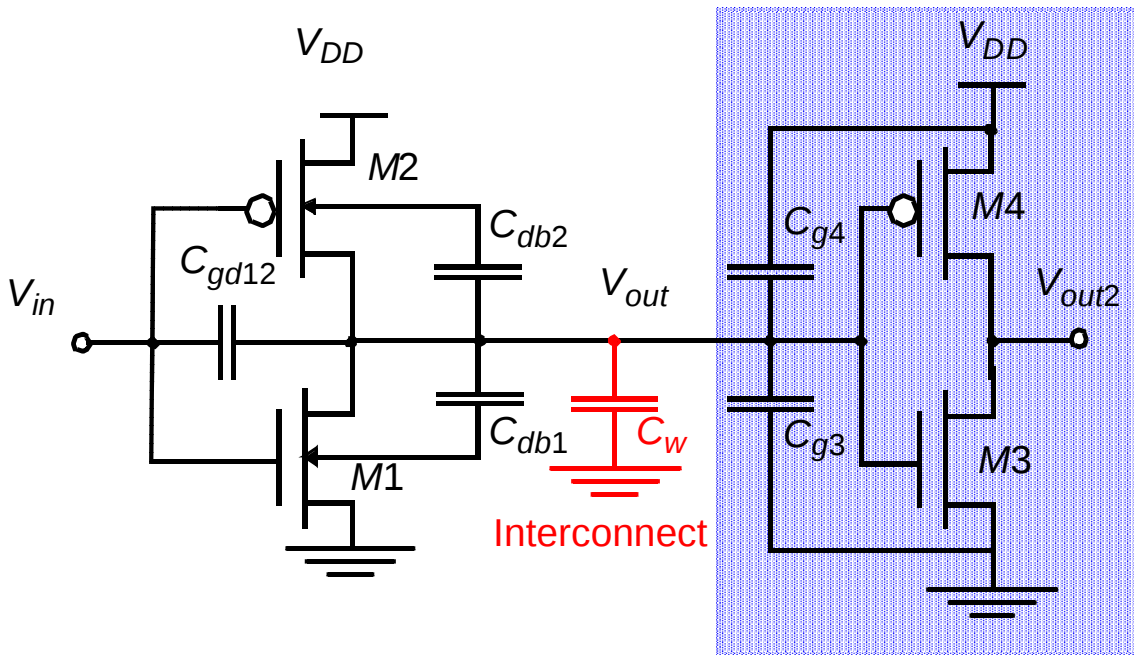


Simplified Model

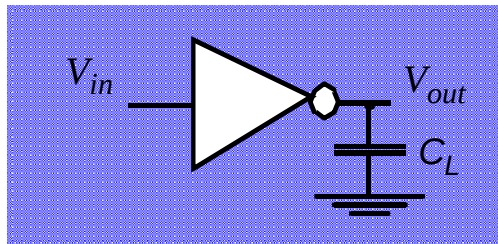


Fanout

Capacitor	Expression
C_{gd1}	$2 \text{ CGD0 } W_n$
C_{gd2}	$2 \text{ CGD0 } W_p$
C_{db1}	$K_{eqn} (AD_n \text{ CJ} + PD_n \text{ CJSW})$
C_{db2}	$K_{eqp} (AD_p \text{ CJ} + PD_p \text{ CJSW})$
C_{g3}	$C_{ox} W_n L_n$
C_{g4}	$C_{ox} W_p L_p$
C_w	From Extraction
C_L	Uploaded By: Jibreel Bornat

CMOS Inverters

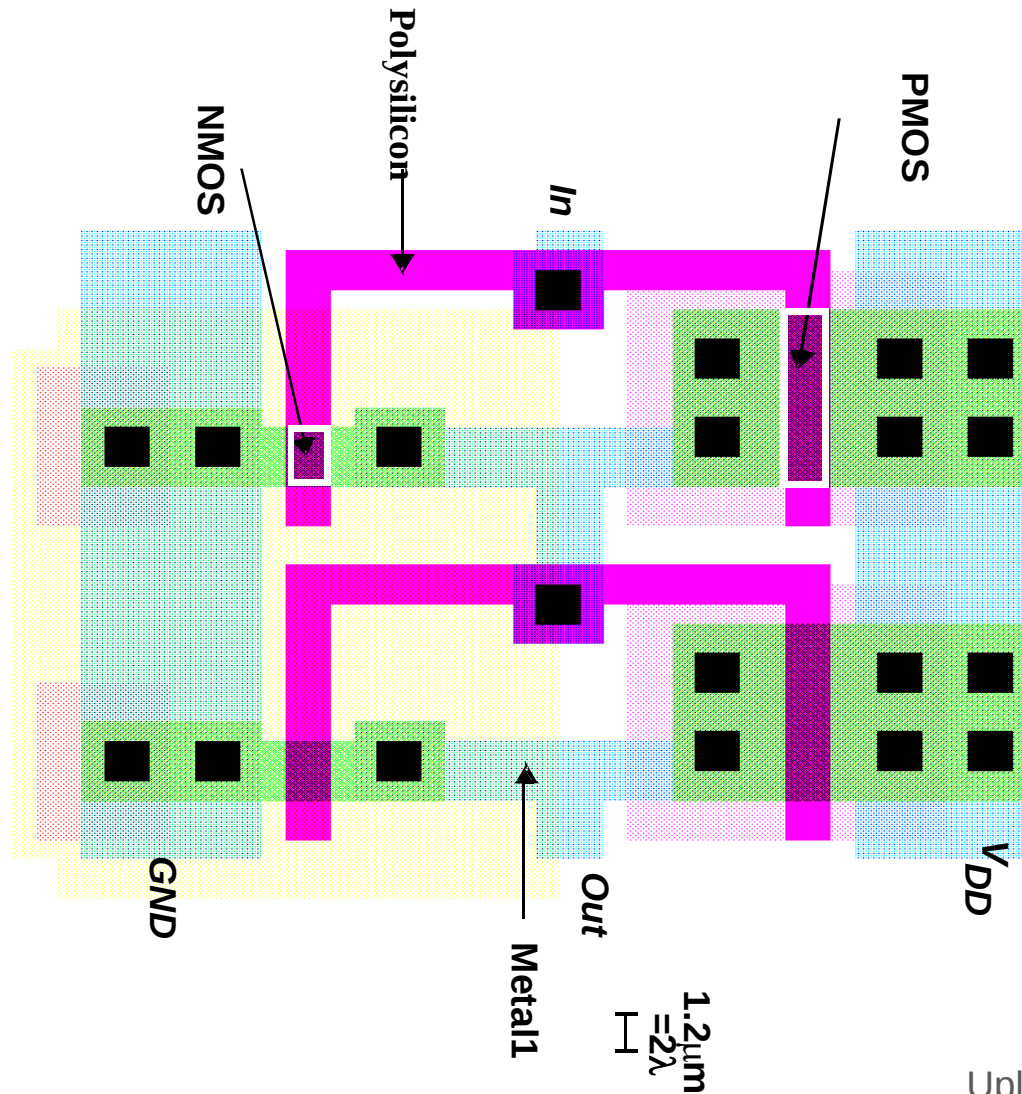


The Miller Effect

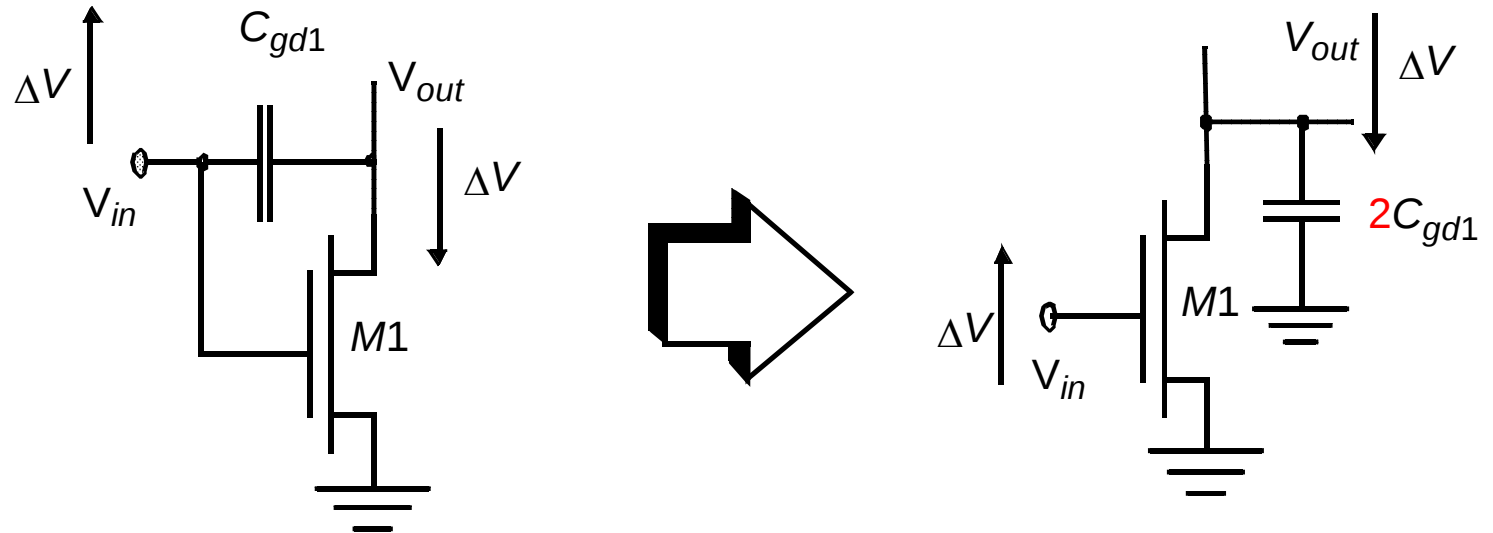


“A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.”

Impact of Rise Time on Delay

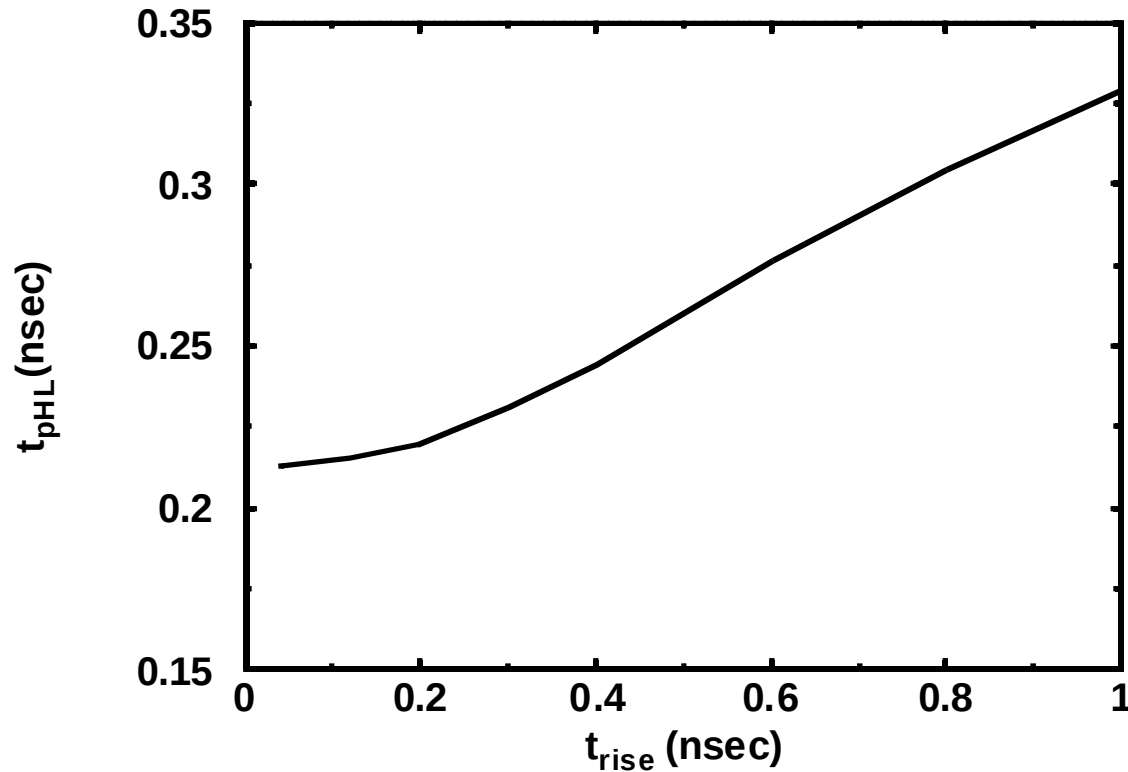

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$

Delay as a function of V_{DD}

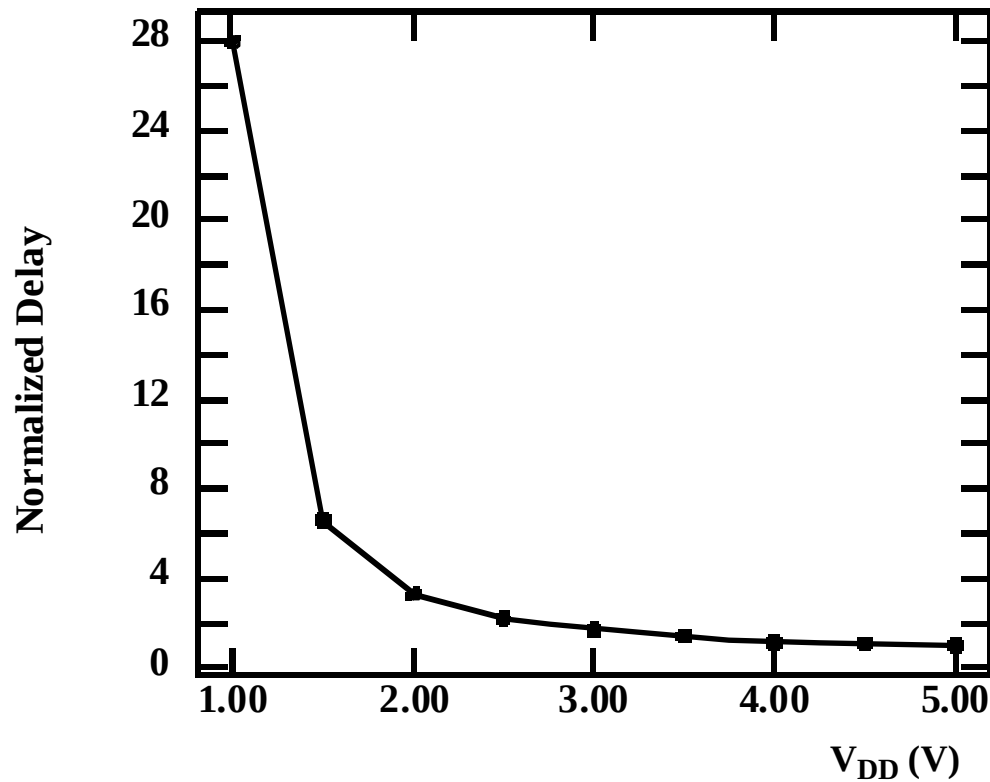

Where Does Power Go in CMOS?

- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

Dynamic Power Dissipation

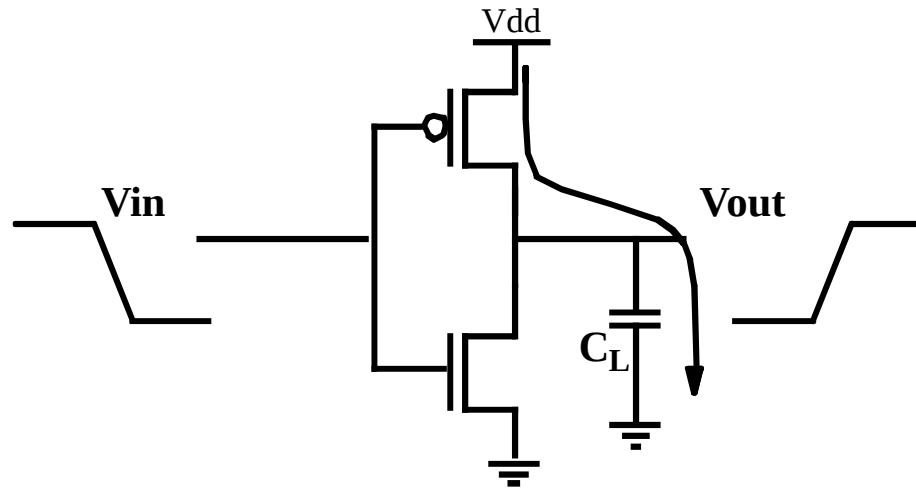

$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

- Not a function of transistor sizes!
- Need to reduce C_L , V_{dd} , and f to reduce power.

Power Dissipation

- Energy from power supply needed to charge up the capacitor:

$$E_{charge} = \int V_{DD} i(t) dt = V_{DD} Q = V_{DD}^2 C_L$$

- Energy stored in capacitor:

$$E_{store} = 1/2 C_L V_{DD}^2$$

- Energy lost in p-channel MOSFET during charging:

$$E_{diss} = E_{charge} - E_{store} = 1/2 C_L V_{DD}^2$$

- During discharge the n-channel MOSFET dissipates an identical amount of energy. • If the charge/discharge cycle is repeated f times/second, where f is the clock frequency, the dynamic power dissipation is:

$$P = 2E_{diss} * f = C_L V_{DD}^2 f$$


In practice many gates do not change state every clock cycle which lowers the power dissipation.

Impact of Technology Scaling

Technology Evolution


Year of Introduction	1994	1997	2000	2003	2006	2009
Channel length (μm)	0.4	0.3	0.25	0.18	0.13	0.1
Gate oxide (nm)	12	7	6	4.5	4	4
V_{DD} (V)	3.3	2.2	2.2	1.5	1.5	1.5
V_T (V)	0.7	0.7	0.7	0.6	0.6	0.6
NMOS I_{Dsat} (mA/ μm) (@ $V_{GS} = V_{DD}$)	0.35	0.27	0.31	0.21	0.29	0.33
PMOS I_{Dsat} (mA/ μm) (@ $V_{GS} = V_{DD}$)	0.16	0.11	0.14	0.09	0.13	0.16

Technology Scaling (1)

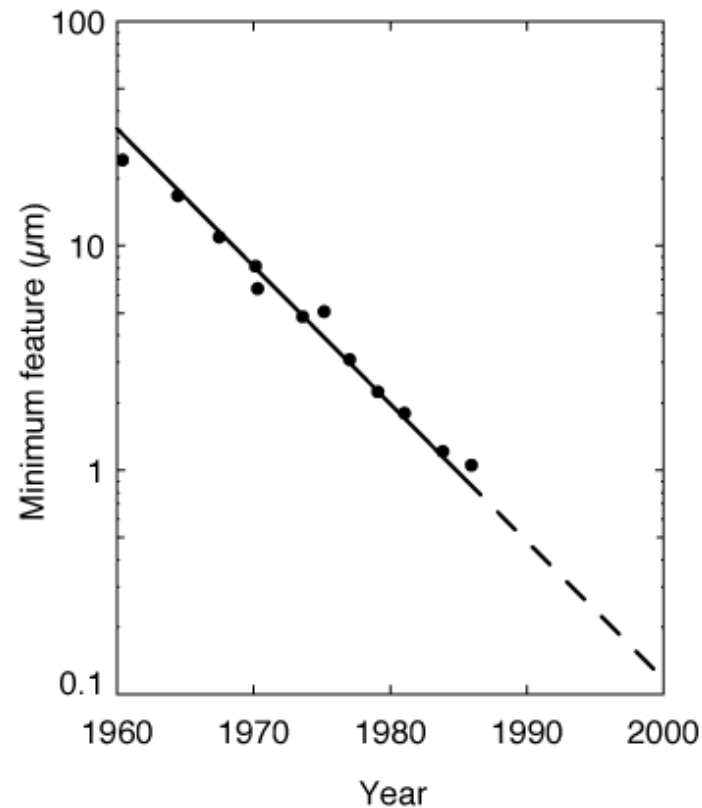


Minimum Feature Size

Technology Scaling (2)

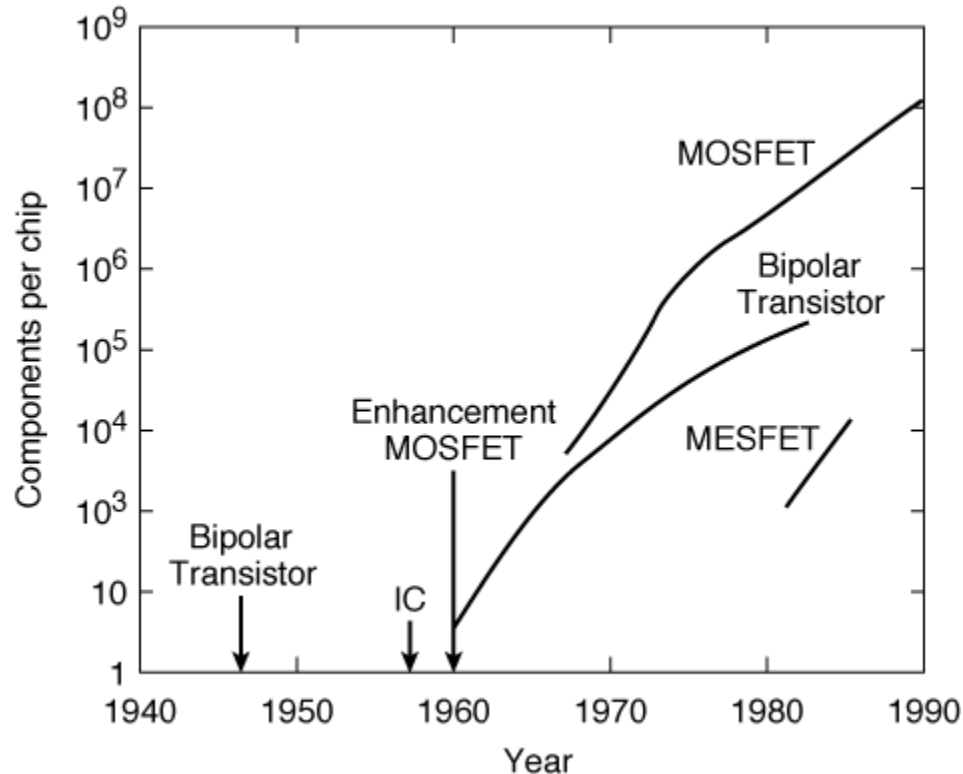

Number of components per chip

Propagation Delay Scaling

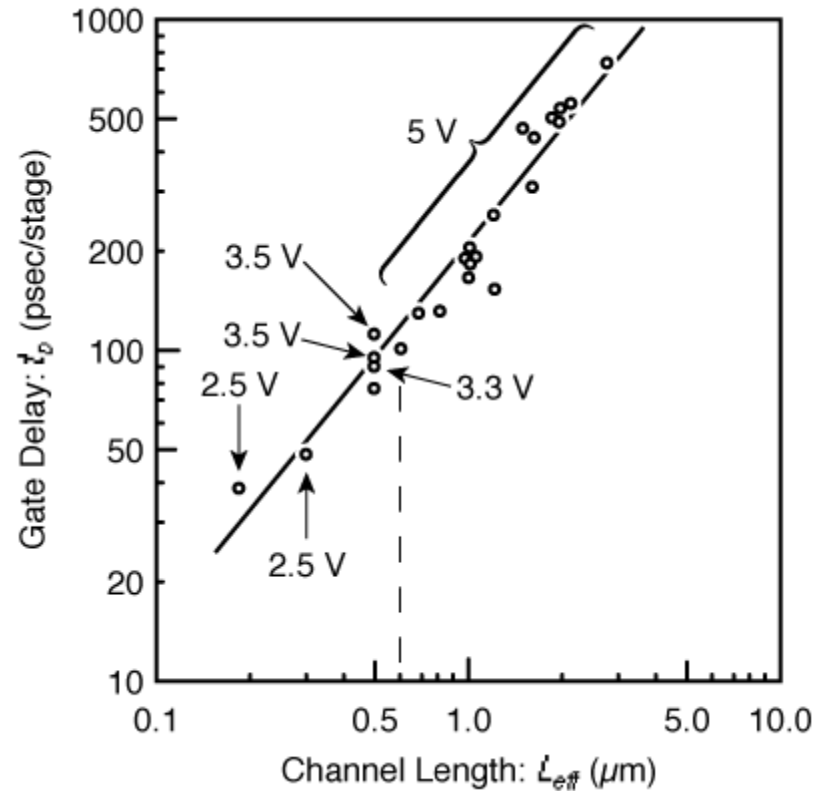

Technology Scaling Models

- **Full Scaling (Constant Electrical Field)**

ideal model — dimensions and voltage scale together by the same factor S


- **Fixed Voltage Scaling**

most common model until recently —
only dimensions scale, voltages remain constant


- **General Scaling**

most realistic for today's situation —
voltages and dimensions scale with different factors


Delay as a function of VDD

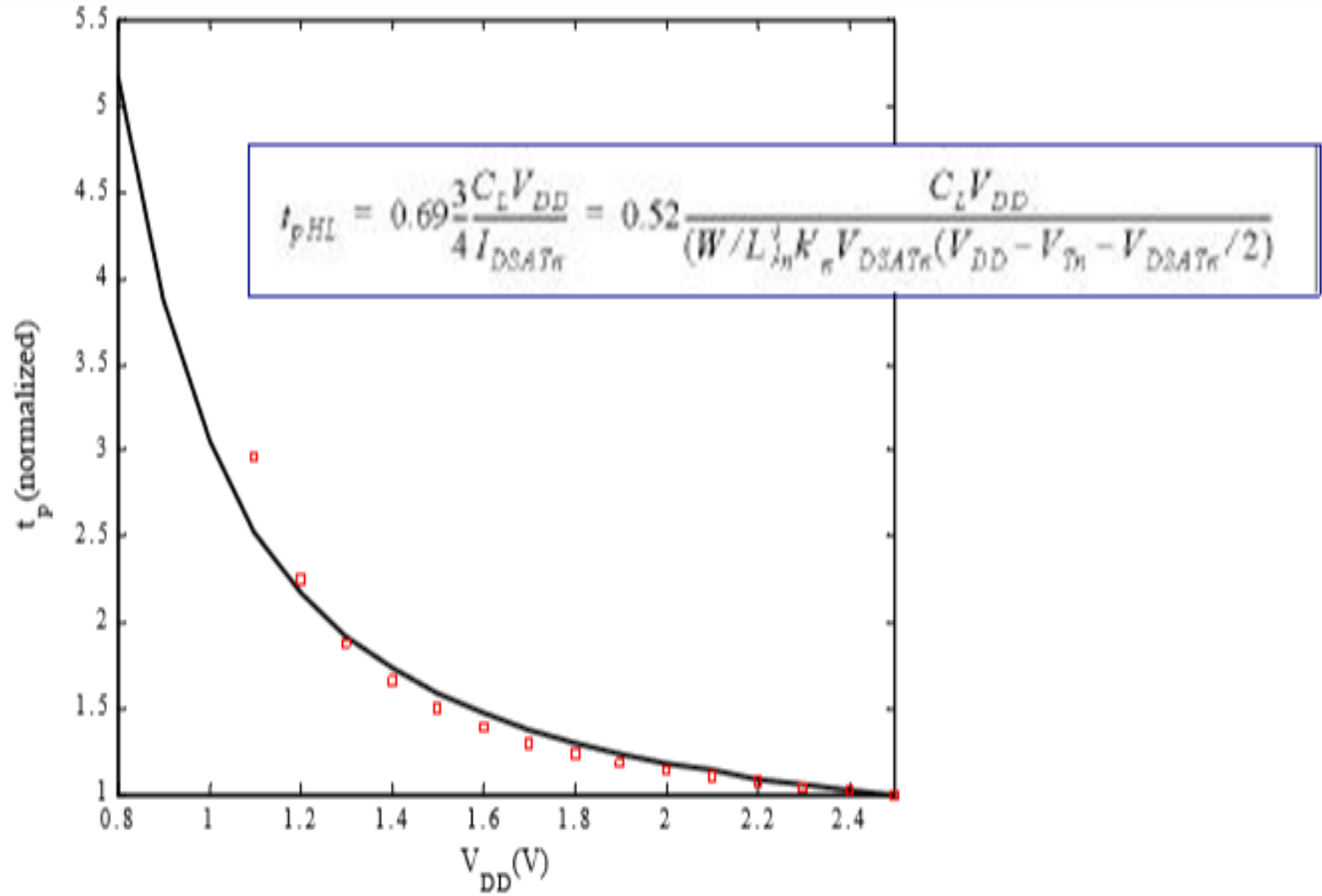

Device Sizing

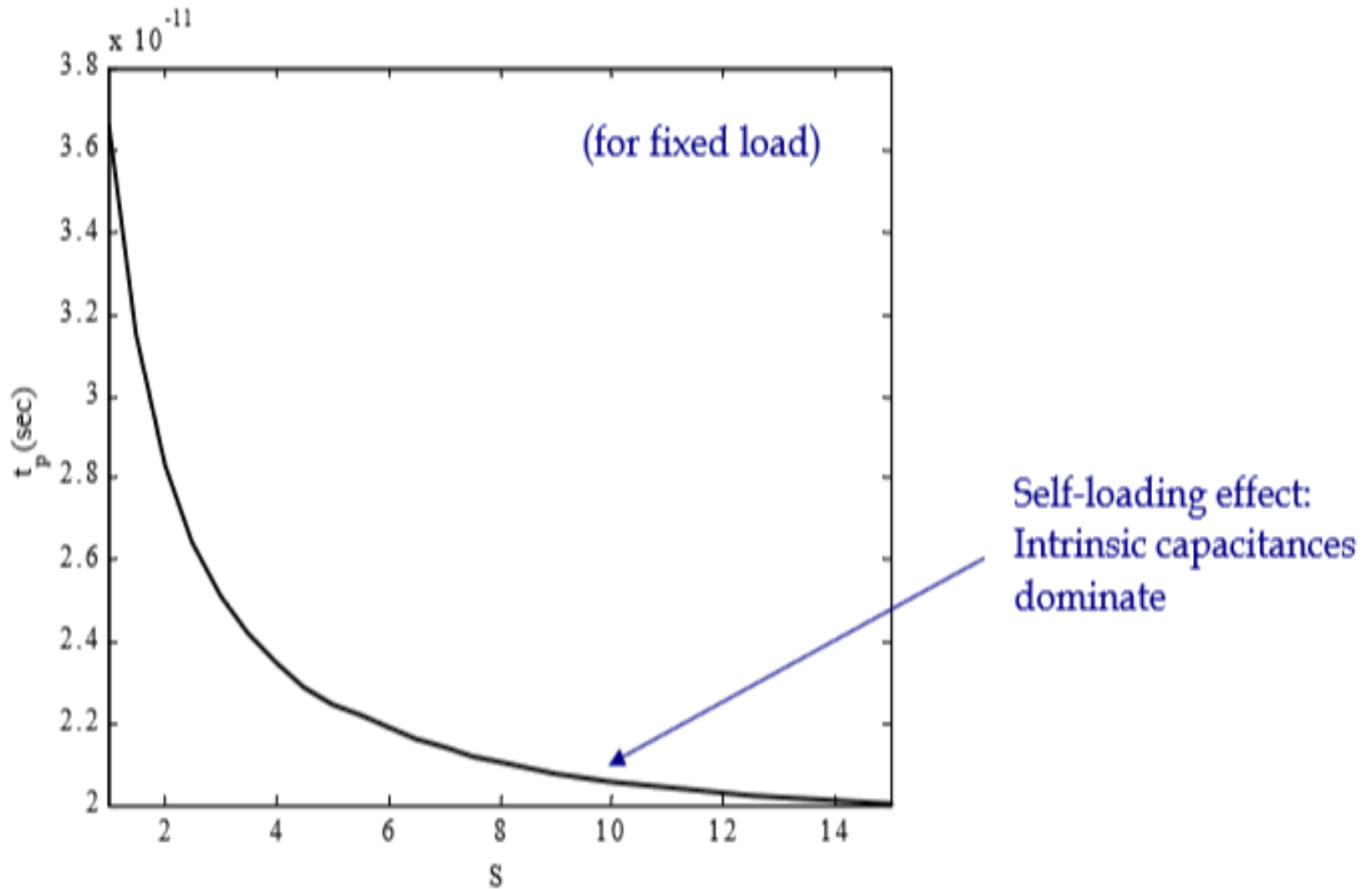

NMOS/PMOS ratio

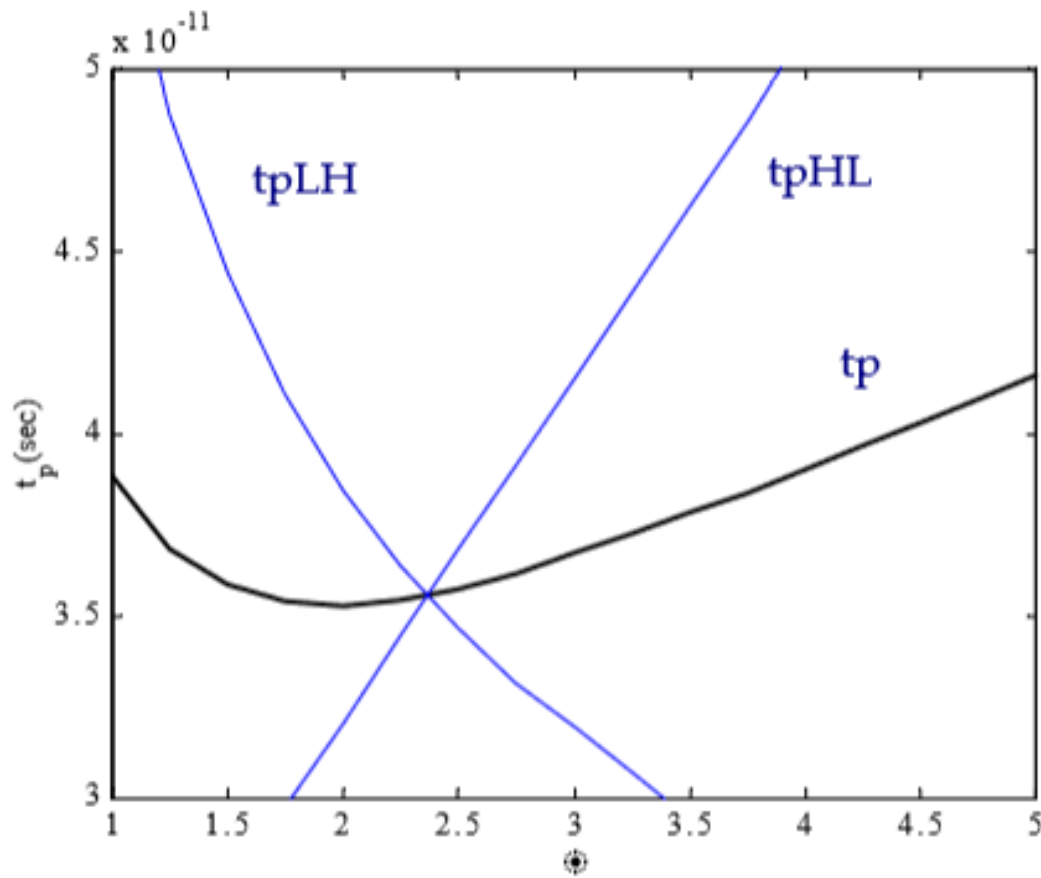

$$\beta = W_p/W_n$$



Inverter Chain/Sizing

If C_L is given: - How many stages are needed to minimize the delay?

How to size the inverters?

May need some additional constraints.

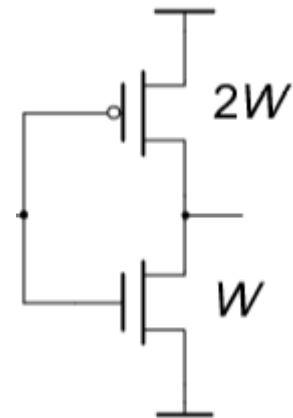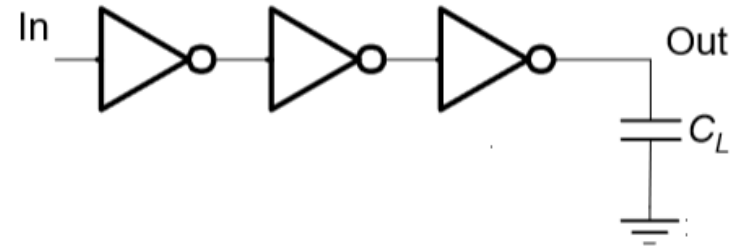- Minimum length devices, $L=0.25\mu\text{m}$
- Assume that for $W_P = 2W_N = 2W$
- same pull-up and pull-down currents
- approx. equal resistances $R_N = R_P$
- approx. equal rise t_{pLH} and fall t_{pHL} delays
- Analyze as an RC network



$$R_P = R_{unit} \left(\frac{W_P}{W_{unit}} \right)^{-1} \approx R_{unit} \left(\frac{W_N}{W_{unit}} \right)^{-1} = R_N = R_W$$

$$\text{Delay (D): } t_{pHL} = (\ln 2) R_N C_L \quad t_{pLH} = (\ln 2) R_P C_L$$

Load for the next stage: $C_{gin} = 3 \frac{W}{W_{unit}} C_{unit}$



Inverter Chain/Sizing

$$t_p = k R_W C_L$$

k is a constant, equal to 0.69



Assumptions: no load $\rightarrow$ zero delay

$$W_{unit} = 1$$

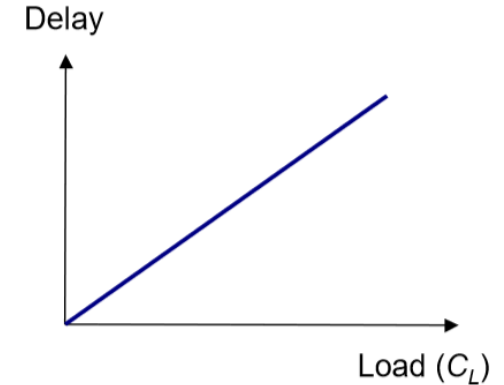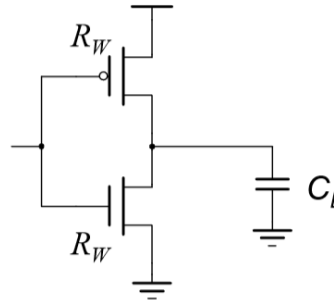

$$\begin{aligned} \text{Delay} &= kR_W(C_{int} + C_L) = kR_W C_{int} + kR_W C_L = kR_W C_{int}(1 + C_L / C_{int}) \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \end{aligned}$$
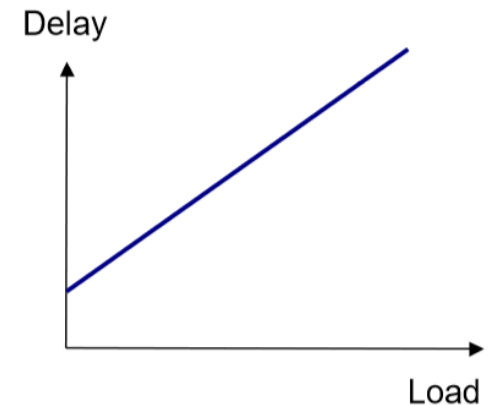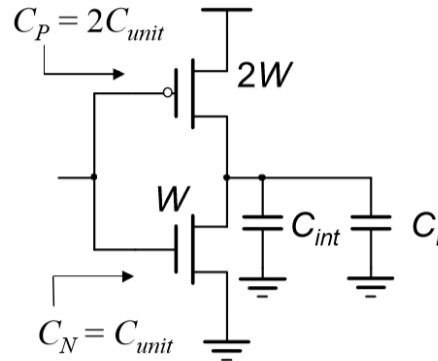
$$\text{Delay} \sim R_W (C_{int} + C_L)$$



$$t_p = kR_W C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / g)$$

nFET vs. pFET

$$R_n = \frac{1}{\beta_n (V_{DD} - V_{Tn})} \quad \beta_n = \mu_n C_{ox} \left(\frac{W}{L} \right)_n$$
$$R_p = \frac{1}{\beta_p (V_{DD} - |V_{Tp}|)} \quad \beta_p = \mu_p C_{ox} \left(\frac{W}{L} \right)_p$$

$$\frac{\mu_n}{\mu_p} = \gamma \quad \text{Typically} \\ (2 \dots 3)$$

(μ is the carrier mobility through device)

(We will return to this later ...)