

ENEE2360 CH8 Homework Problems

23. a. Find the value of R_S to obtain a voltage gain of 2 for the network of Fig. 8.74 using $r_d = \infty \Omega$.
b. Repeat part (a) with $r_d = 30 \text{ k}\Omega$. What was the impact of the change in r_d on the gain and the analysis?

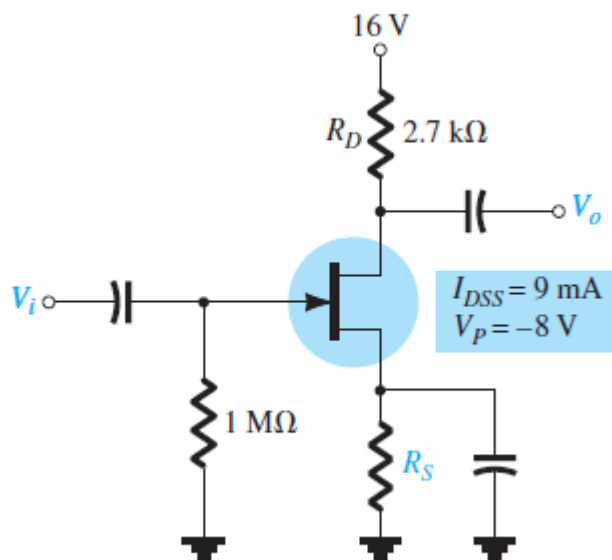


FIG. 8.74

$r_{ds} = 30 \text{ k}\Omega$

46. Design the fixed-bias network of Fig. 8.88 to have a gain of 8.
47. Design the self-bias network of Fig. 8.89 to have a gain of 10. The device should be biased at $V_{GS_Q} = \frac{1}{3}V_P$.

$$r_{ds} = 50\text{K}\Omega$$

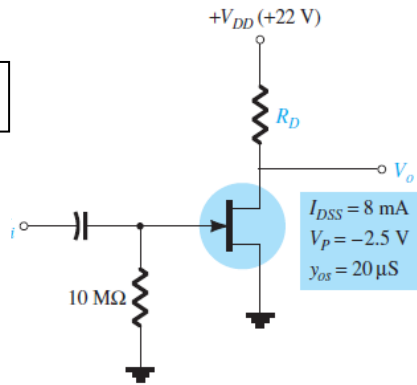


FIG. 8.88

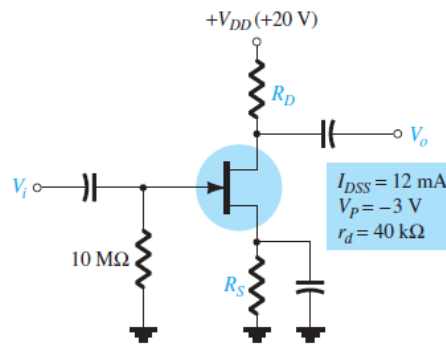


FIG. 8.89

56. For the cascade amplifier of Fig. 8.94, calculate the dc bias voltages currents of each stage.
57. For the amplifier circuit of Fig. 8.94, calculate the voltage gain of each stage and the overall amplifier voltage gain.
58. Calculate the input impedance (Z_i) and output impedance (Z_o) for the amplifier circuit of Fig. 8.94.


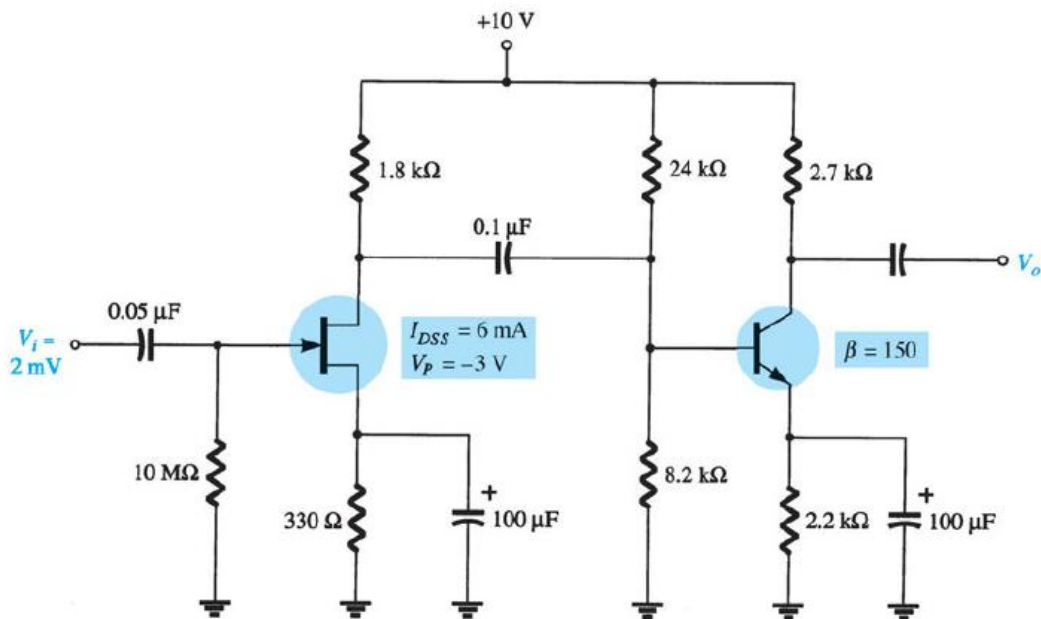


FIG. 8.94


8.23

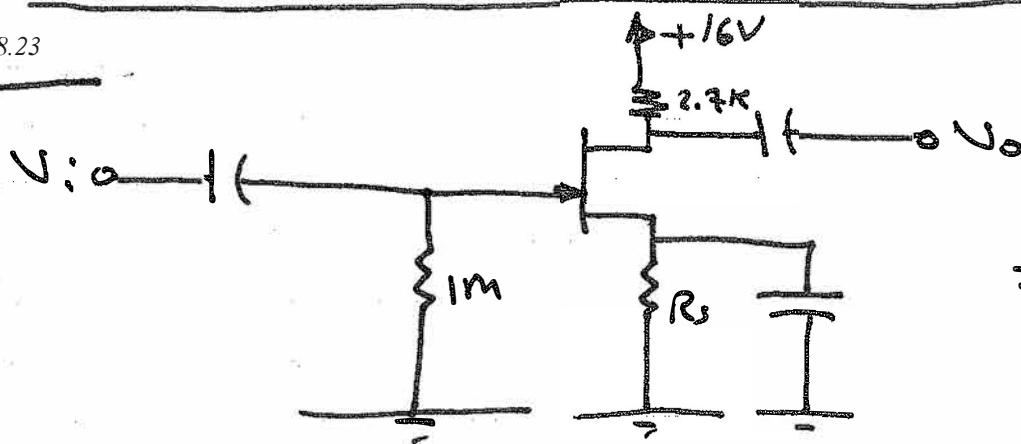

$$I_{DSS} = 9\text{mA}$$

$$V_p = -8\text{V}$$

ac small signal equivalent circuit:

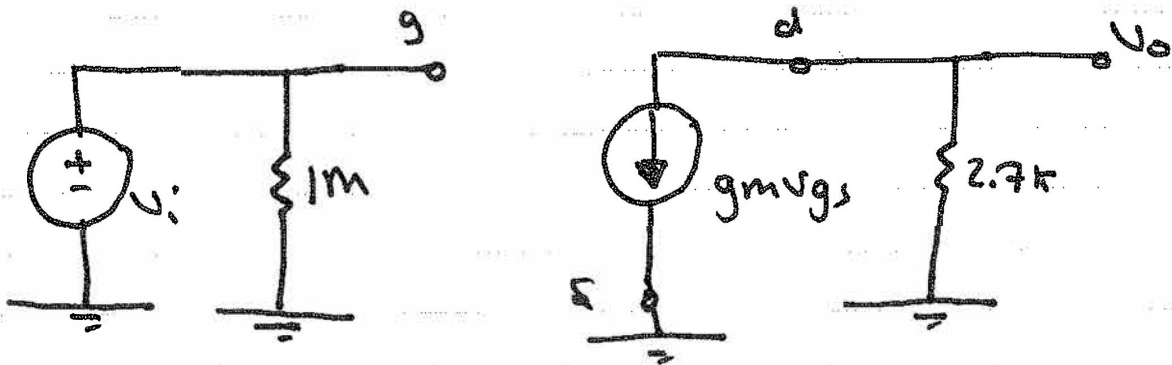

$$V_o = -g_m V_{gs} (2.7\text{k})$$

$$V_{gs} = V_o - V_s = V_i$$

$$\therefore A_v = \frac{V_o}{V_i} = -g_m (2.7\text{k}) = -2$$

$$\therefore g_m = 0.741 \text{ mA/V}$$

$$g_m = \frac{-2 I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p} \right)$$

$$\therefore V_{GS} = -5.37\text{V}$$

-1-

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\therefore I_{DS} = 0.973 \text{ mA}$$

$$\therefore V_{GS} = V_G - V_S = 0 - R_S I_{DS} = -5.37 \text{ V}$$

$$\therefore R_S = \frac{5.37}{0.973} = 5.5 \text{ k}$$

b) if $r_{ds} = 30 \text{ k}$

$$A_{vo} = -g_m r_{ds} (2.7 \text{ k} \parallel 30 \text{ k}) = -2$$


$$\therefore g_m = 0.8 \text{ mA/V}$$

$$\therefore V_{GS} = -5.129 \text{ V}$$


$$\therefore I_{DS} = 1.159 \text{ mA}$$

$$\therefore R_S = 4.425 \text{ k}$$

8.46

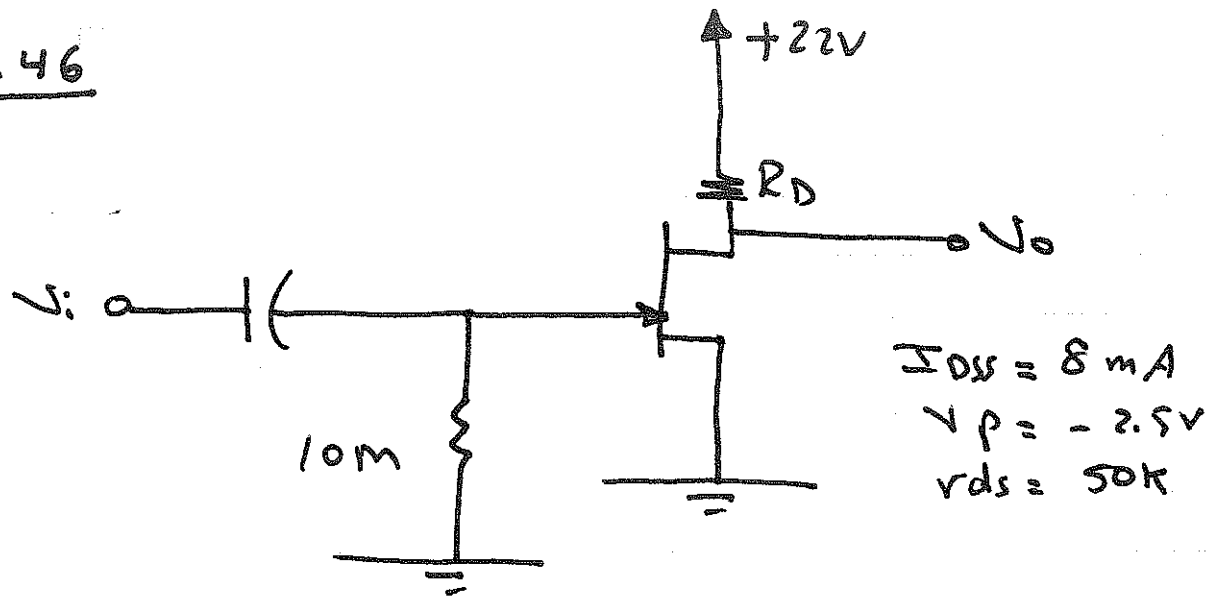

ac small signal equivalent circuit:

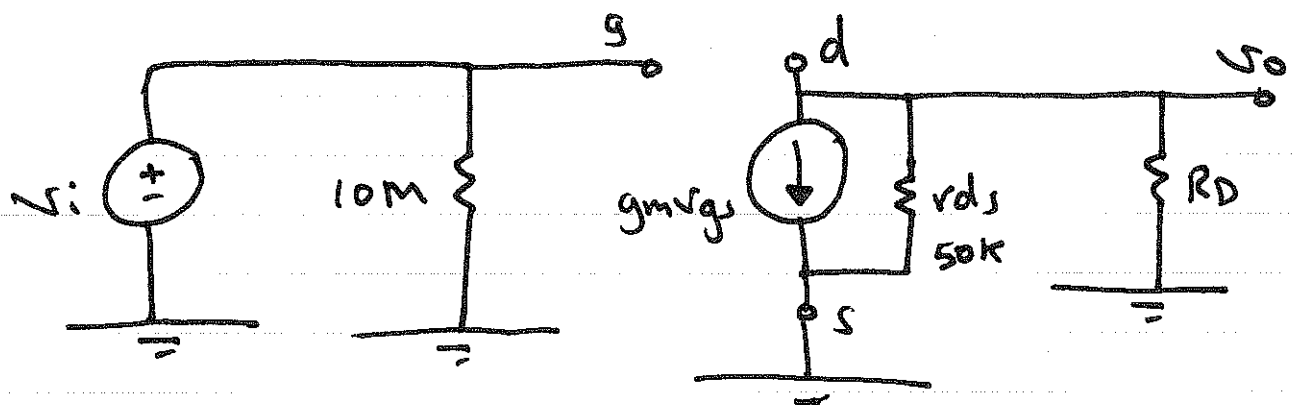

$$V_o = -g_m V_{gs} (50\text{k} \parallel R_D)$$

$$g_m = \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P} \right)$$


$$V_{GS} = 0$$

$$\therefore g_m = 6.4\text{ mA/V}$$

$$A_v = -8 = -g_m (50\text{k} \parallel R_D)$$

$$\therefore R_D = 1.28\text{ k}\Omega$$

8.47

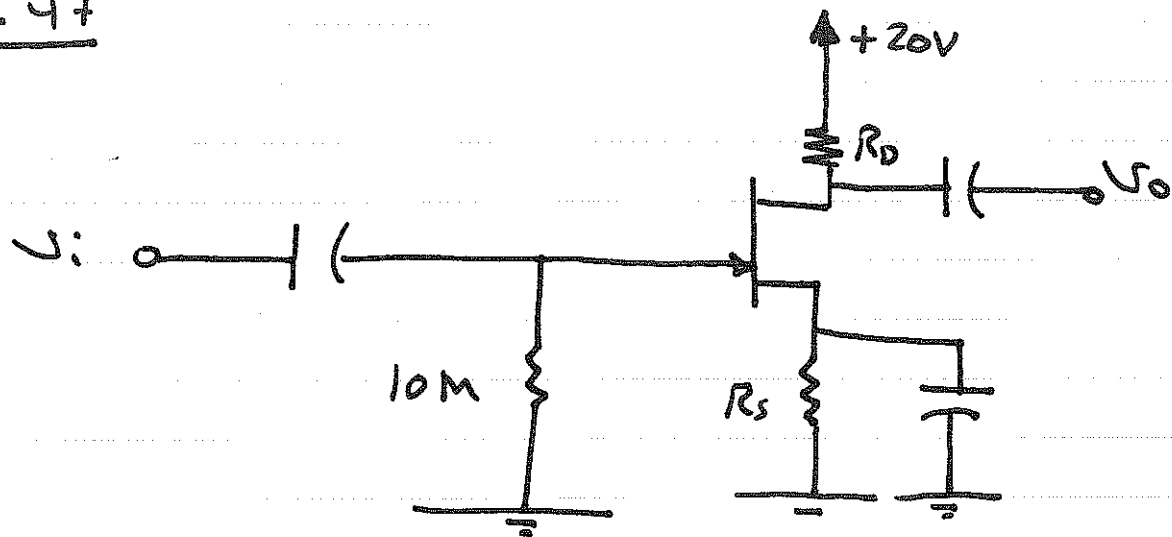


$$I_{DSS} = 12\text{mA}$$

$$V_P = -3\text{V}$$

$$r_{ds} = 40\text{k}\Omega$$

$$V_{GS} = -1\text{V}$$

ac small signal equivalent circuit:

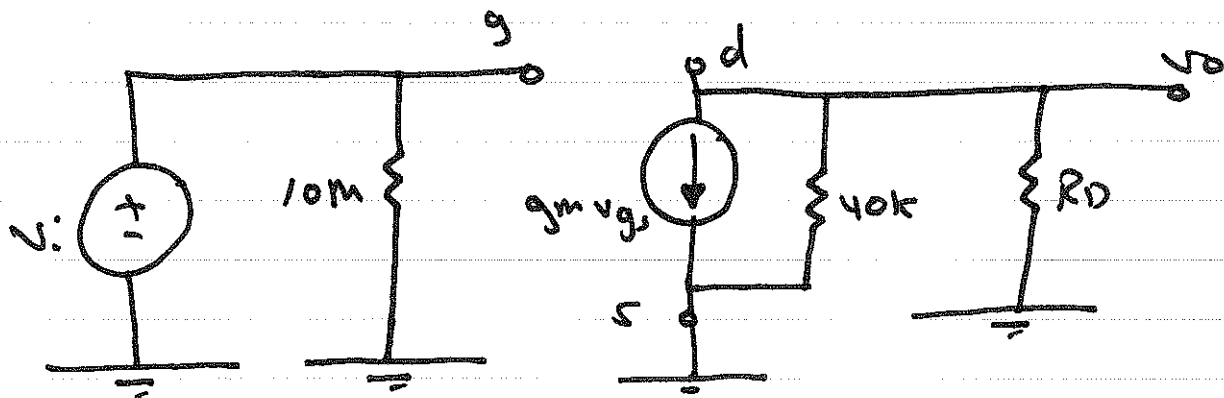

$$A_v = -g_m (R_D \parallel 40\text{k}) = -10$$

$$g_m = \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$V_{GS} = -1\text{V}$$

$$\therefore g_m = 5.33\text{mA/V}$$

\therefore for $A_v = -10$

$$R_D = 1.97 \text{ k}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$


$$\therefore I_{DS} = 5.77 \text{ mA}$$

$$V_{GS} = -1 = V_G - V_S = 0 - R_S I_{DS}$$

$$\therefore R_S = \frac{1 \text{ V}}{5.77 \text{ mA}} = 0.187 \text{ k}$$

8.56

DC Analysis :

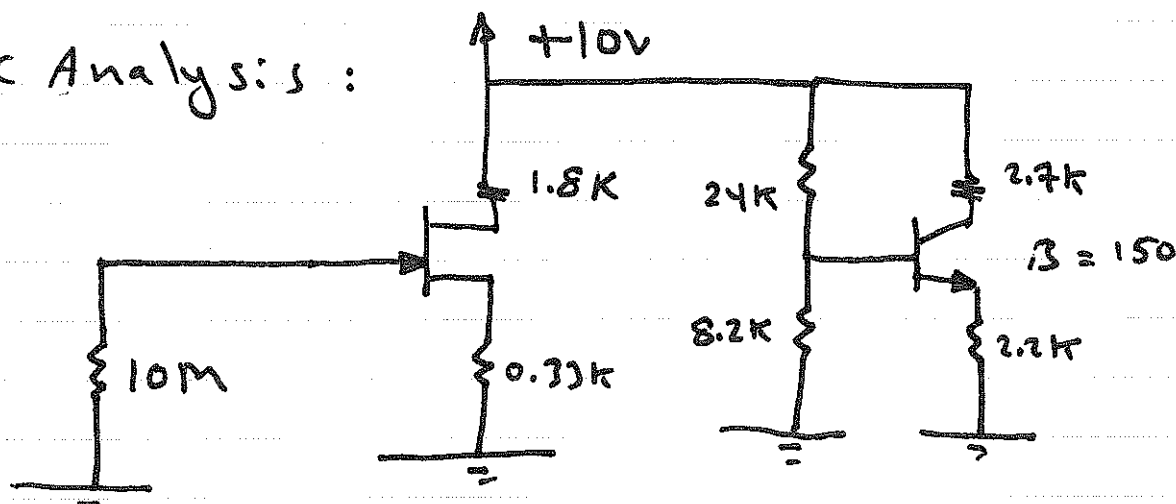

$$I_{DSS} = 6 \text{ mA} , V_p = -3 \text{ V}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{GS} = V_G - V_S = (-0.33 \text{ K}) I_{DS}$$

Solving for I_{DS} , we get

$$I_{DS} = 2.84 \text{ mA}$$

$$R_{TH} = 24 \text{ K} \parallel 8.2 \text{ K} = 6.11 \text{ K}$$

$$V_{TH} = \frac{8.2 \text{ K}}{8.2 \text{ K} + 24 \text{ K}} (+10) = 2.55 \text{ V}$$

$$\therefore I_E = \frac{2.55 - 0.7}{2.2 \text{ K} + \frac{6.11 \text{ K}}{151}} = 0.824 \text{ mA}$$

$$V_{CE} = 10 - 2.7 \text{ K} I_C - 2.2 \text{ K} I_E \approx 5.96 \text{ V}$$

$$V_{DS} = 10 - (1.8 \text{ K} + 0.33 \text{ K}) I_{DS} = 3.95 \text{ V}$$

$$V_D = 10 - (1.8k)(2.84mA) = 4.89V$$

$$V_S = (0.33k)(2.84mA) = 0.937V$$

$$\therefore V_{DS} = 3.95V ; V_G = 0$$

$$|V_{DS}| > |V_P| - |V_G|$$

$$|V_{DS}| > 3 - 0.937 = 2.063 \quad \checkmark$$


$$\frac{8.57}{h_{ie}} = \frac{(\beta+1) V_T}{I_E} = 4.71k$$

$$g_m = \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$g_m = 2.75 \text{ mA/V}$$

$$V_{GS} = -0.33k I_{DS} = -0.937V$$

ac small signal equivalent circuit:

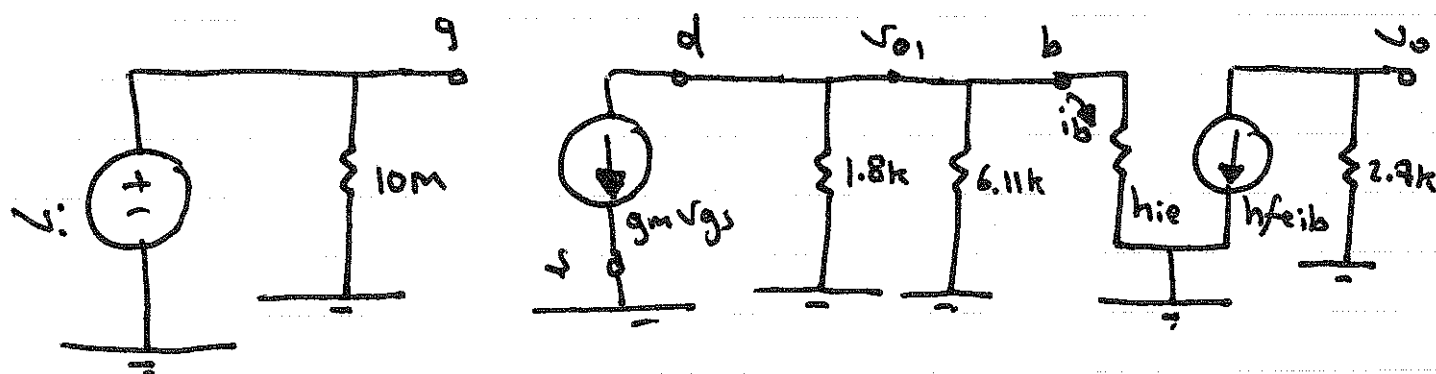

$$A_{v1} = \frac{V_{o1}}{V_i} ; V_{o1} = -g_m V_{gs} (1.8k \parallel 6.11k \parallel h_{ie})$$

$$V_{gs} = V_g - V_s = V_g = V_i$$

$$\therefore A_{v1} = -2.75$$

$$A_{v2} = \frac{V_o}{V_{i2}} = \frac{V_o}{V_{o1}} ; V_o = -h_{fe} i_b (2.7k)$$

$$i_b = \frac{V_{o1}}{h_{ie}}$$

$$\therefore A_{v2} = -85.98$$

$$A_{vt} = A_{v1} \cdot A_{v2} = 236.5$$

8.58

$$Z_i = 10 \text{ M}\Omega$$

$$Z_o = 2.7 \text{ K}\Omega$$