

ENEE2360

Analog Electronics

T5: Zener Diode


INSTRUCTOR: NASSER ISMAIL

ENEE236 – Analog Electronics


Zener Diode Simple Voltage Regulator

- *The Zener is used as a voltage regulator to maintain a constant dc output under variations in load current and ac line voltage*
- *It can also be used as protection device against overvoltage*
- *Analysis starts by defining state of diode followed by using appropriate model, then find unknown quantities*

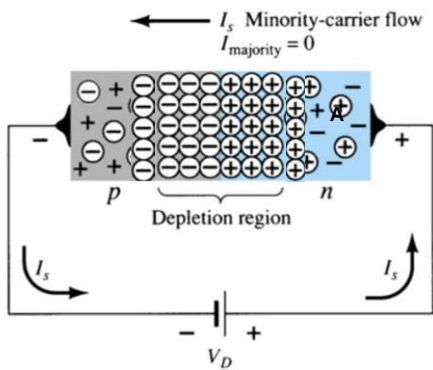Reverse bias of a pn junction Breakdown Voltage




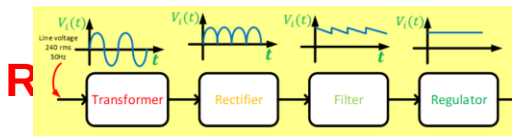The electric field may become large enough for the covalent bond to break, causing electron-hole pairs to be created.




Used to maintain a constant dc output voltage under variation in the load current from the dc power supply and under variation in the ac line voltage

$$V_o = \frac{RL}{RL+RS} \cdot Vs$$

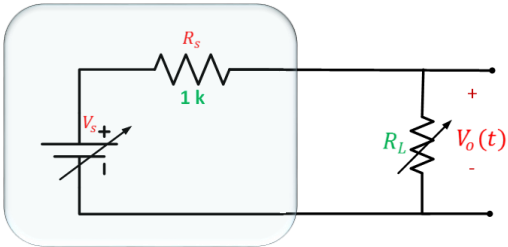




Voltage Regulator

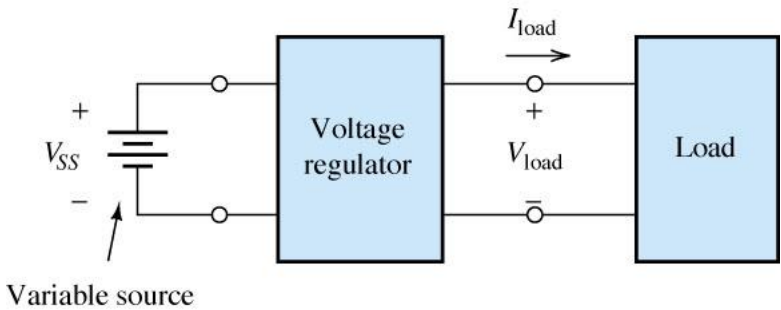

A voltage regulator supplies constant voltage to a load.


Simple voltage regulator

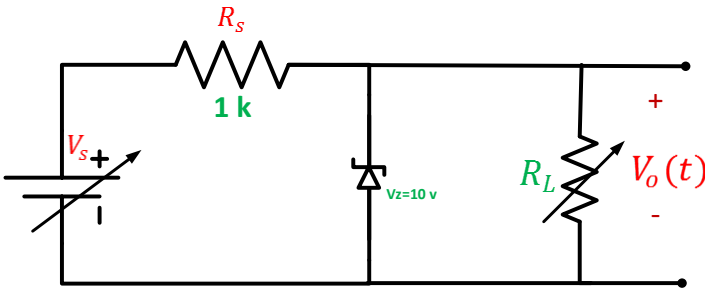

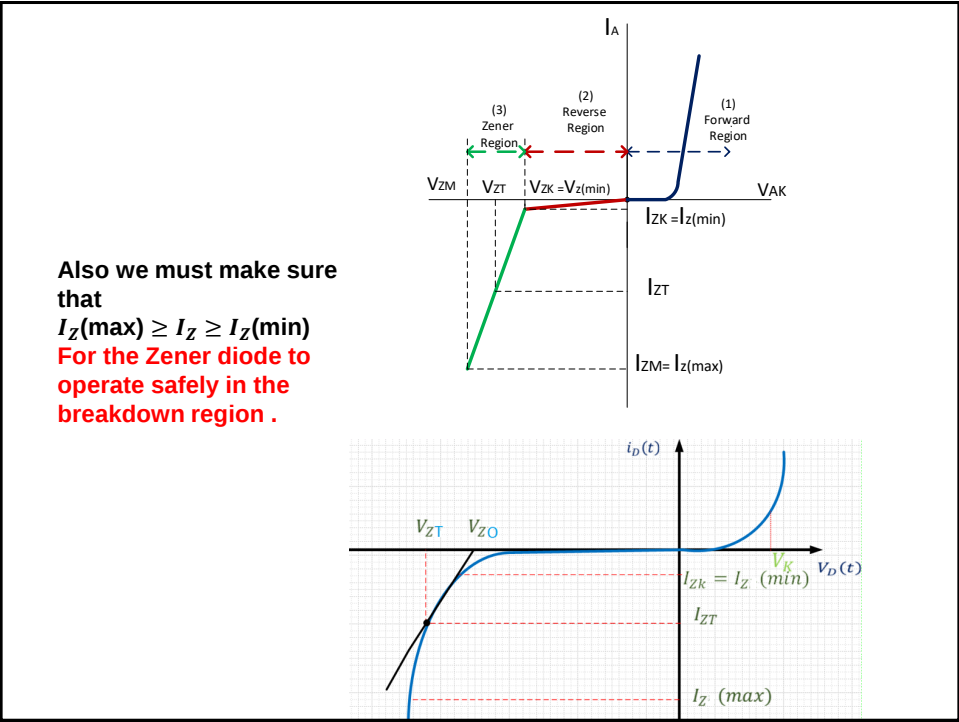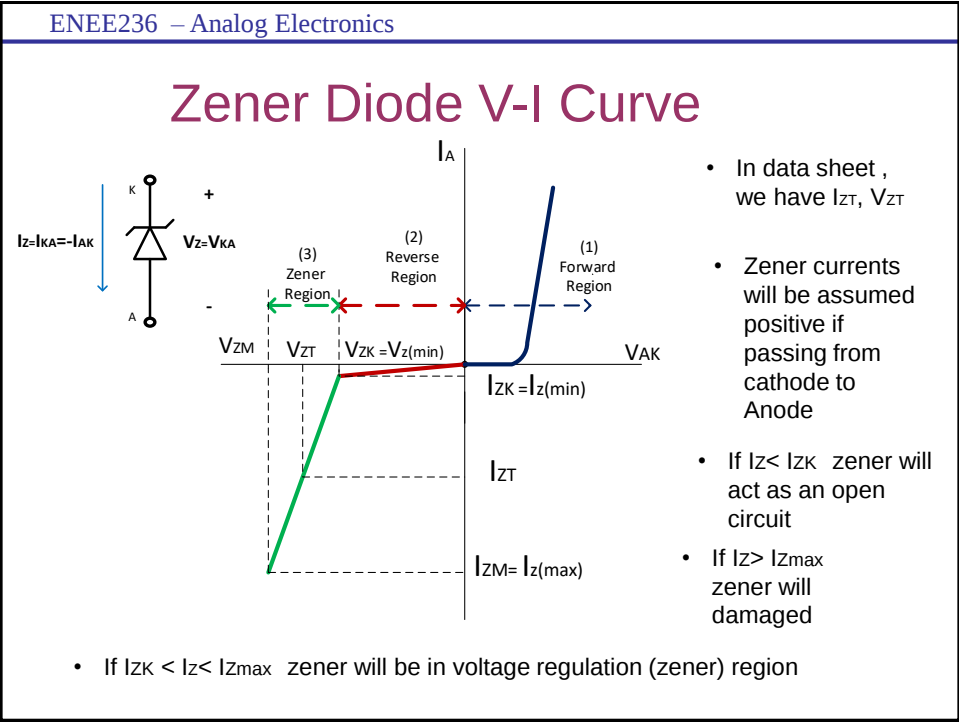

ENEE236 – Analog Electronics

Zener Diode Operation Regions

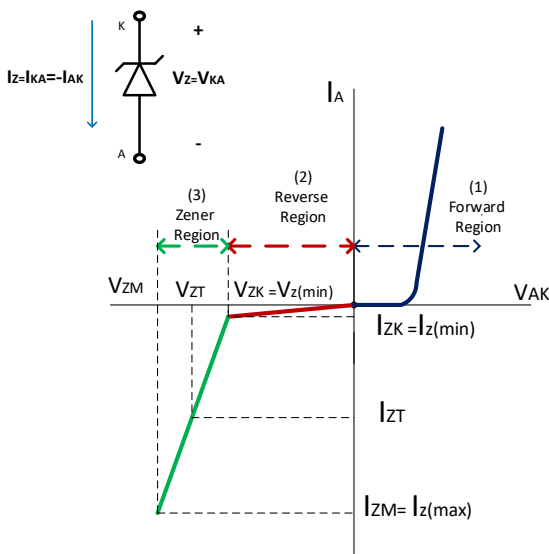

Region (1)

➤ When $V_{AK} > 0$, zener acts as regular diode ON

➤ Region (2)

When $0 < V_{AK} < V_{ZK}$, zener acts as regular diode OFF

➤ Region (3)

When $V_{KA} > V_{ZK}$, This is the intended operating region, and the zener acts as a voltage regulator

ENEE236 – Analog Electronics

Zener Diode Operation & Models


The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_Z).

Conditions for zener diode to operate in the breakdown (Zener/ON) region When

1. Cathode is more positive than anode
2. $V_{th} \geq V_Z$
3. $I_Z > I_{Z(min)}$
4. $I_Z < I_{Z(max)}$

==> Voltage across the Zener is V_Z

- Zener current: $I_Z = I_S - I_L$
- The Zener Power: $P_Z = V_Z I_Z$

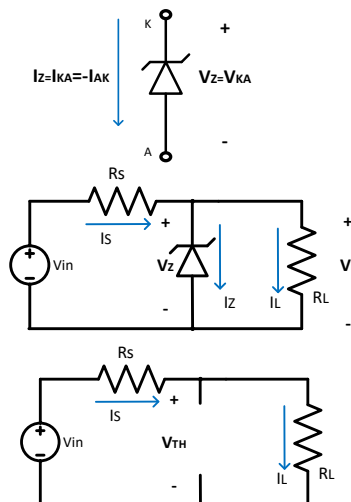

ENEE236 – Analog Electronics

Zener Diode Models

1. Ideal Model

"on" "off" ($V_Z > V > 0\text{ V}$)

2. Simplified Model *(will not be used in this course)*

$I_Z = I_{KA} = -I_{AK}$ $V_Z = V_{KA}$ r_Z

Zener Diode

$V_{ZT} = X @ I_{ZT} = Y$
 $r_Z = \frac{\Delta V_Z}{\Delta I_Z}$


Also we must make sure that
 $I_Z(\text{max}) \geq I_Z \geq I_Z(\text{min})$
For the Zener diode to operate safely in the breakdown region .

V-I Characteristic curve

First2022-2023
STUDENTS-HUB.com
Instructor: Nasser Ismail

Uploaded By: anonymous
6

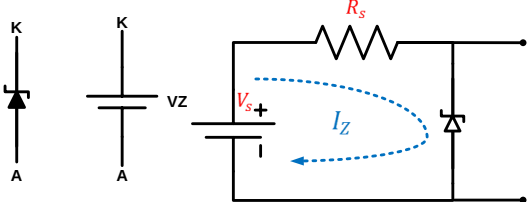
Ideal model of Zener in the breakdown region .




- If $V_S > V_Z$, the Zener diode is in the breakdown region .
- If $V_S < V_Z$, the Zener diode is open circuit.

Also we must make sure that

▶ $I_Z(\max) \geq I_Z \geq I_Z(\min)$

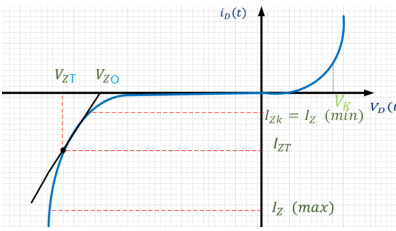

Zener Diode I-V Characteristics

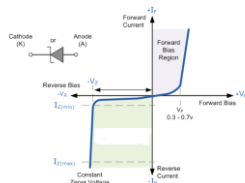

Fixed V_{in} , Variable R_L


- ▶ Due to the value of V_Z , there is specific values of R_L (I_L) that ensure the zener is in the ON (regulation) state
- ▶ Too small values of R_L can result in zener being OFF

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_{in}$$

$$R_{L(\min)} = \frac{R_S \cdot V_Z}{V_{in} - V_Z}$$

$$R_L \geq R_{L(\min)} \Rightarrow I_{L(\max)} = \frac{V_L}{R_L} = \frac{V_L}{R_{L(\min)}}$$

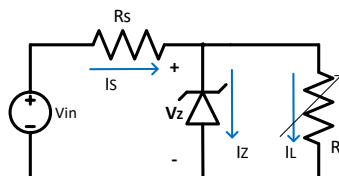Also, values of $R_L \geq R_{L(\max)}$ can result in $\Rightarrow I_Z > I_{Z(\max)}$



$$I_{L(\min)} = I_S - I_{Z(\max)}$$

↓

$$R_{L(\max)} = \frac{V_Z}{I_{L(\min)}}$$

ENEE236 – Analog Electronics

Example

Given the following values of R_L ,
find the mode of operation of the
zener and the voltage V_L

- a) $R_L = 0.1 \text{ k}\Omega$
- b) $R_L = 0.5 \text{ k}\Omega$
- c) $R_L = 5 \text{ k}\Omega$
- d) $R_L = \infty$

SOLUTION


- a) $R_L = 0.1 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{0.1}{0.1 + 1} 35 \text{ V} = 3.18 \text{ V}$$

Zener works in region 2, it acts
as open circuit

$$V_L = 3.18 \text{ V (it is not regulated)}$$

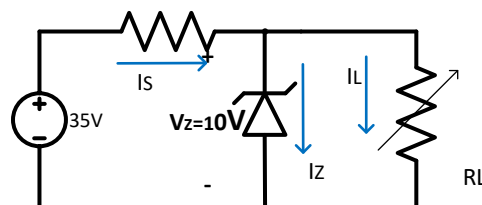

ENEE236 – Analog Electronics

Example

- b) $R_L = 0.5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{0.5}{0.5 + 1} 35 \text{ V} = 11.67 \text{ V}$$

$$V_{th} > V_Z$$


Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$

$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$


$$I_L = \frac{V_L}{R_L} = \frac{10}{0.5 \text{ k}\Omega} = 20 \text{ mA}$$

$$I_Z = I_S - I_L = 5 \text{ mA}$$

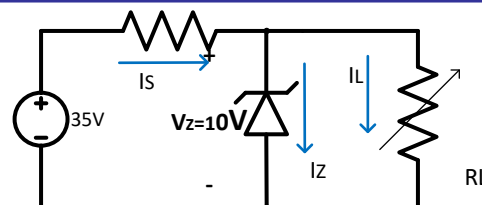

ENEE236 – Analog Electronics

Example

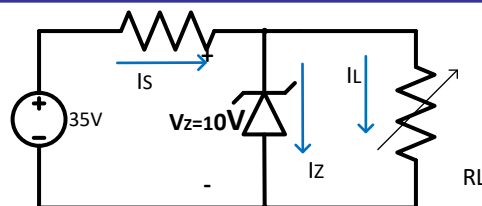

c) $R_L = 5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{5}{5+1} 35 \text{ V} = 29.17 \text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$


$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{5 \text{ k}\Omega} = 2 \text{ mA}$$

$$I_Z = I_S - I_L = 23 \text{ mA}$$

ENEE236 – Analog Electronics

Example

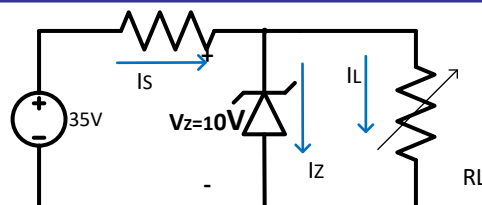

d) $R_L = 5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{\infty}{\infty + R_S} V_{in} = 35 \text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$

$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$


$$I_L = \frac{V_L}{R_L} = \frac{10}{\infty} = 0$$

$$I_Z = I_S - I_L = 25 \text{ mA}$$

ENEE236 – Analog Electronics

Example

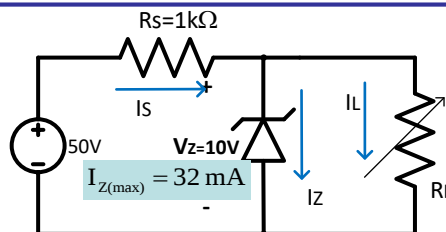- 1) Determine Range of R_L & I_L that will result in V_L being maintained at 10V
- 2) Determine the power rating of the zener diode



SOLUTION

- 1) To find $R_{L(min)}$ that will turn the zener diode ON :

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_i \Rightarrow$$

$$R_L = \frac{R_S}{V_i - V_Z} V_Z$$

$$R_{L(min)} = \frac{1 \text{ k}\Omega}{50 - 10} 10 = 250 \Omega$$

$$250 \Omega \leq R_L \leq 1.25 \text{ k}\Omega$$

- 2) To find $R_{L(max)} \Rightarrow$ we need $I_{L(min)}$

$$I_{L(min)} = I_S - I_{Z(max)}$$

$$I_S = \frac{V_i - V_Z}{R_S} = \frac{50 - 10}{1 \text{ k}\Omega} = 40 \text{ mA}$$

$$I_{L(min)} = 40 - 32 = 8 \text{ mA}$$

$\Downarrow$

$$R_{L(max)} = \frac{V_L}{I_{L(min)}} = \frac{10 \text{ V}}{8 \text{ mA}} = 1.25 \text{ k}\Omega$$

$$3) P_{Z(max)} = V_Z \cdot I_{Z(max)} = 10 \text{ V} \cdot 32 \text{ mA} = 320 \text{ mW}$$

The zener diode is chosen with power rating $\geq P_{Z(max)}$

ENEE236 – Analog Electronics

Fixed R_L , Variable V_{in}

For Fixed R_L , the voltage V_{in} must be large enough to turn the zener diode on (regulation region (3))

$$V_{in} = V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$V_{in(max)}$ is limited by maximum zener current $I_{Z(max)}$


$$I_S = I_Z + I_L$$

$$I_{S(max)} = I_{Z(max)} + I_L$$

$$V_{i(max)} = I_{S(max)} \cdot R_S + V_Z$$

$\Downarrow$

$$V_{in(min)} \leq V_{in} \leq V_{in(max)}$$

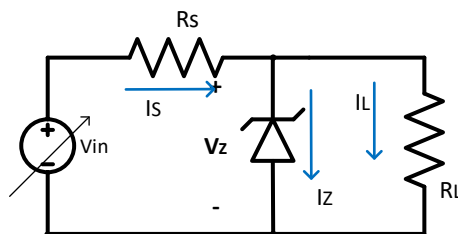

ENEE236 – Analog Electronics

Example

Find the range of values of V_i that will maintain the zener in the ON (regulation) State

$$V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$$= \frac{1200 + 220}{1200} 20 = 23.07 \text{ V}$$


$$I_S = I_Z + I_L$$

$$I_{S(max)} = I_{Z(max)} + I_L$$

$$I_L = \frac{V_L}{R_L} = \frac{20 \text{ V}}{1200 \Omega} = 16.67 \text{ mA}$$

$$I_{S(max)} = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$
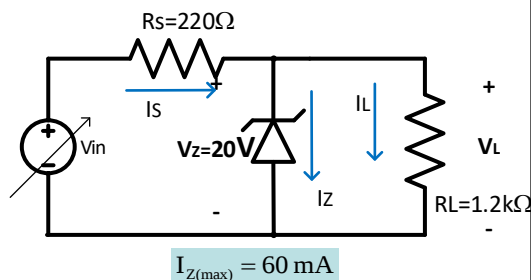
$$V_{i(max)} = (76.67 \text{ mA}) \cdot (220 \Omega) + 20 \text{ V} = 36.87 \text{ V}$$



$$\therefore 23.07 \text{ V} \leq V_{in} \leq 36.87 \text{ V}$$

ENEE236 – Analog Electronics

Design of R_S (Current limiting Resistor)

Given : $V_Z, I_{Z(min)}, I_{Z(max)}, V_{in(min)}, V_{in(max)}, R_{L(min)}, R_{L(max)}$

Find range of acceptable R_S in the voltage regulator

$$1) I_Z = I_S - I_L \geq I_{Z(min)}$$

Worst Case : the smallest value of

$$(I_S - I_L)$$


must be always higher than $> I_{Z(min)}$

$$I_{S(min)} - I_{L(max)} \geq I_{Z(min)}$$

$$\frac{V_{S(min)} - V_Z}{R_S} - I_{L(max)} \geq I_{Z(min)}$$

$$I_{Z(min)} + I_{L(max)} \leq \frac{V_{S(min)} - V_Z}{R_S}$$

$$R_S \leq \frac{V_{S(min)} - V_Z}{I_{Z(min)} + I_{L(max)}}$$

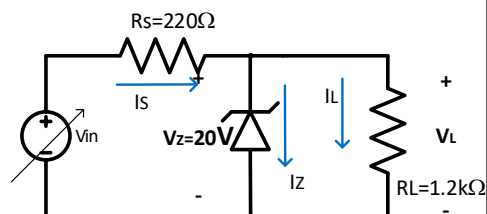

ENEE236 – Analog Electronics

Design of Rs (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$

Find range of acceptable Rs in the voltage regulator

$$2) I_Z \leq I_{Z(\max)}$$

Worst Case : the largest value of $(I_S - I_L)$ must be always smaller than $I_{Z(\max)}$

$$I_{S(\max)} - I_{L(\min)} \leq I_{Z(\max)}$$

$$\frac{V_{S(\max)} - V_Z}{R_S} - I_{L(\min)} \leq I_{Z(\max)}$$

$$I_{Z(\max)} + I_{L(\min)} \geq \frac{V_{S(\max)} - V_Z}{R_S}$$

$$R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Note That

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}}$$

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

ENEE236 – Analog Electronics

Design of Rs (Current limiting Resistor)

Given :

$$V_Z = 10 \text{ V},$$

$$I_{Z(\min)} = 5 \text{ mA}, I_{Z(\max)} = 200 \text{ mA},$$

$$V_{in(\min)} = 15 \text{ V}, V_{in(\max)} = 20 \text{ V},$$

$$R_{L(\min)} = 500, R_{L(\max)} = \infty$$

Find R_S ?

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}} = 10/500 = 20 \text{ mA}$$

$$200 \Omega \geq R_S \geq 50 \Omega$$

$$\text{let } R_S = 100 \Omega$$

$$\text{and}$$

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}} = 10/\text{infinity} = 0$$

ENEE236 – Analog Electronics

Clipper circuits using Zeners

a) When $V_i(t) < -0.7 \text{ V}$, Zener works in region (1) as regular diode ON

$$0.7 + i_D(t) \cdot R + V_i(t) = 0$$

$$i_D(t) = \frac{-V_i(t) - 0.7}{R} > 0$$

$$V_i(t) < -0.7$$

$$\therefore V_o(t) = -0.7$$

b) When $V_z > V_i(t) > -0.7 \text{ V}$, Zener works in region (2) as regular diode OFF $\therefore V_o(t) = V_i(t)$

c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator $\therefore V_o(t) = V_z$

ENEE236 – Analog Electronics

Clipper circuits using Zeners



c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator $\therefore V_o(t) = V_z$

Clipper circuits using Zeners

Find and sketch $V_o(t)$


- a) When $0.7V < V_i(t) < V_{Z2}$,
D1- regular diode ON
D2- regular diode OFF

$$\therefore V_o(t) = V_i(t)$$

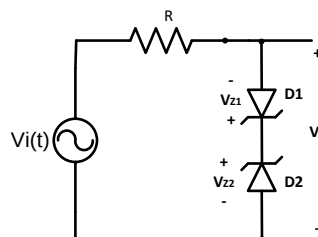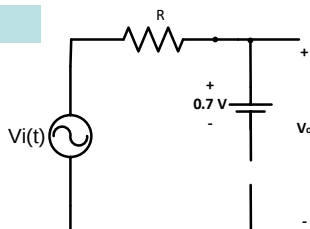

- b) When $V_i(t) > V_{Z2}$
D1 – ON (region 1)
D2- Zener ON (region 3)



$$\therefore V_o(t) = V_{Z2} + 0.7$$

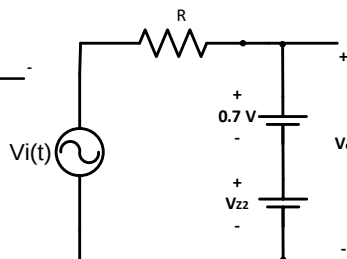

Clipper circuits using Zeners

- c) When $-0.7V > V_i(t) > -V_{Z1}$,
D1- regular diode OFF
D2- regular diode ON

$$\therefore V_o(t) = V_i(t)$$

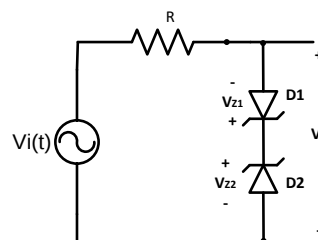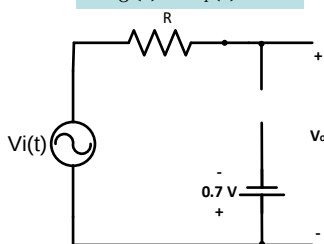

- d) When $V_i(t) < -V_{Z1}$
D2 – ON (region 1)
D1- Zener ON (region 3)

$$\therefore V_o(t) = -V_{Z1} - 0.7$$

