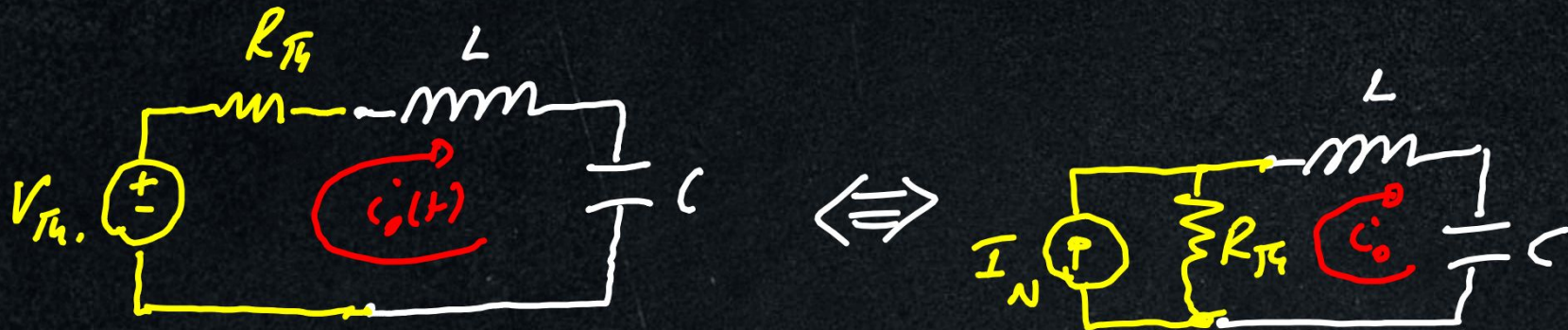


CH 8 :- Second order RLC Circuits


parallel RLC circuit



series RLC circuit



① Parallel RLC circuit

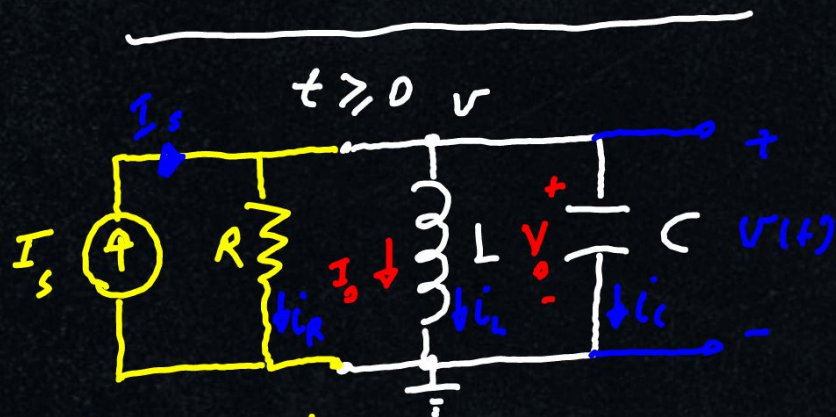

Norton
Equiv.
Circuit

KCL at v

$$-I_s + i_R + i_L + i_C = 0$$

$$i_R = \frac{v}{R}$$

$$i_C = C \frac{dv}{dt}$$

$$i_L = \frac{1}{L} \int v dt + I_0 ; v = L \frac{di_L}{dt}$$

I_0 initial inductive current ($\frac{1}{2} L I_0^2$)
 V_0 initial capacitive voltage ($\frac{1}{2} C V_0^2$)

$$I_s = \frac{v}{R} + C \frac{dv}{dt} + \frac{1}{L} \int v dt + I_0$$

$$0 = \frac{1}{R} \frac{dv}{dt} + C \frac{d^2 v}{dt^2} + \frac{1}{L} v$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0 \Rightarrow 2^{\text{nd}} \text{ order differential equation}$$

$$f^2 + \frac{1}{RC} f + \frac{1}{LC} = 0 \Rightarrow \text{chara. equation (*)}$$

Roots of equation (*) :-

$$f_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad ; \quad \alpha = \frac{1}{2RC} \quad , \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$\downarrow$
daper
Frequency


$\downarrow$
resonant
frequency

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Three possible outcomes


a) $\alpha^2 > \omega_0^2 \Rightarrow s_1 + s_2$ are real + unequal roots

"Over-damped response"

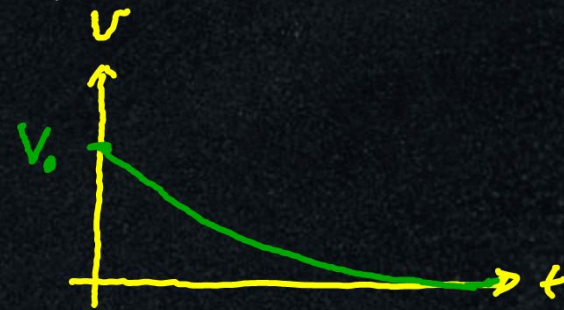


b) $\alpha^2 < \omega_0^2 \Rightarrow s_1 + s_2$ are complex roots

"Under-damped response"

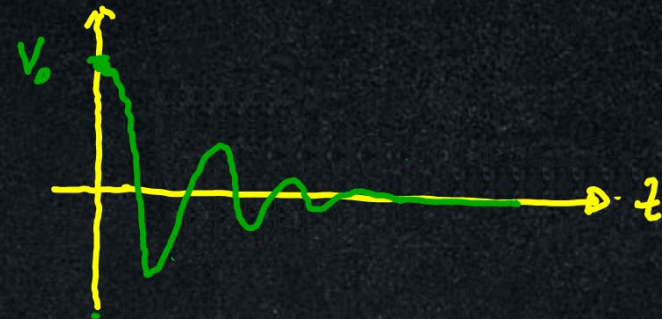

c) $\alpha^2 = \omega_0^2 \Rightarrow$ real + equal roots

critically damped response

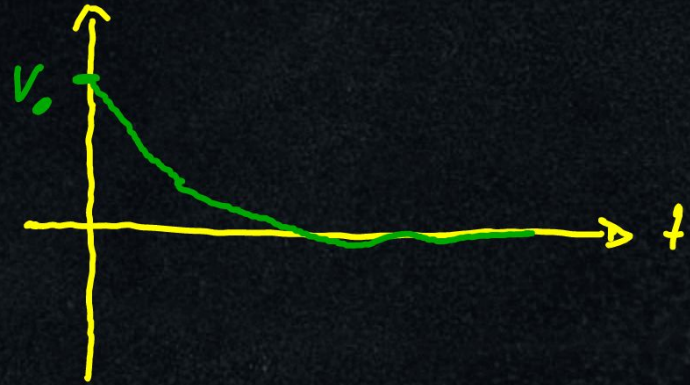

① Over-damped response ($\alpha^2 > \omega_0^2$)

The solution is given by

$$v(t) = \underline{A_1} e^{\underline{s_1}t} + \underline{A_2} e^{\underline{s_2}t} \quad t \geq 0$$


$$\underline{s_{1,2}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad , \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$v(0^+) \quad , \quad \frac{dv(0^+)}{dt}$$

$$v(0^+) = v(0^-) = v(0) = V_0$$
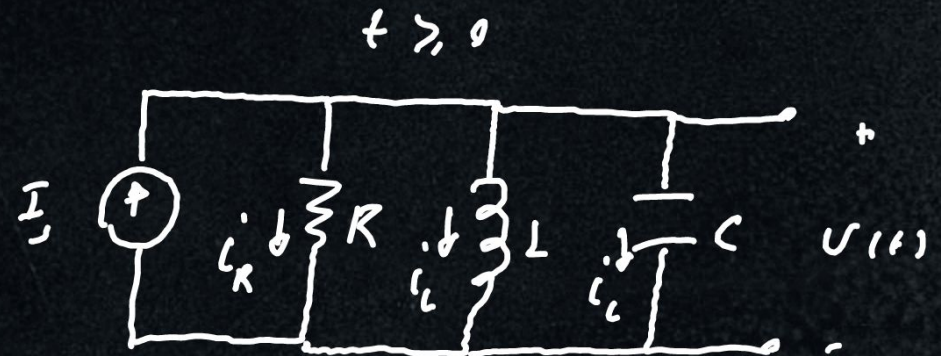
$$\frac{dv(0^+)}{dt} = \frac{C_C(0^+)}{C} = \frac{1}{C} \left[\underline{I_s} - \frac{V_0}{R} - \underline{I_0} \right]$$



$$\underline{V_0}, \underline{I_0}$$


$$\underline{I_s} = \dot{C_R}(0^+) + \dot{C_L}(0^+) + \dot{C_C}(0^+)$$

$$\dot{C_C}(0^+) = \underline{I_s} - \dot{C_R}(0^+) - \dot{C_L}(0^+)$$

$$\dot{C_C}(0^+) = \underline{I_s} - \frac{V_0}{R} - \underline{I_0}$$

$$\left. \begin{aligned} v(0^+) &= A_1 + A_2 \\ \frac{dv(0^+)}{dt} &= s_1 A_1 + s_2 A_2 \end{aligned} \right\} \Rightarrow \text{Solve for } A_1 \text{ and } A_2$$

Ex:-

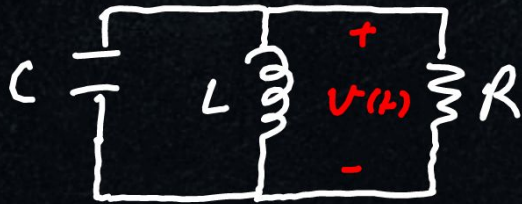

$$V_0 = 12 \text{ V}$$

$$I_0 = 30 \text{ mA}$$

$$C = 0.2 \mu\text{F}, L = 50 \text{ mH}, R = 200 \Omega$$

Find $V(t)$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(200)(0.2 \times 10^{-6})} = 1.25 \times 10^4 \text{ r/f}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50 \times 10^{-3} \times 0.2 \times 10^{-6}}} = 1 \times 10^4 \text{ r/sec}$$

$$\alpha > \omega_0 \Rightarrow \text{over-damped} \quad V(t) = \underline{A_1} e^{\underline{s_1} t} + \underline{A_2} e^{\underline{s_2} t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = \left[-1.25 \pm \sqrt{(1.25)^2 - (1)^2} \right] \times 10^4 = \begin{cases} -5000 \text{ r/sec} \\ -201000 \text{ r/sec} \end{cases}$$

$$V(0^+) = V_0 = 12 \text{ V}$$

$$\frac{dV(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{1}{C} \left(\cancel{I_s} - \frac{V_0}{R} - \bar{I}_L \right)$$



$$\frac{dV(0^+)}{dt} = \frac{1}{0.2 \times 10^{-6}} \left[\frac{-12}{200} - 30 \times 10^{-3} \right] = -450 \text{ kV/sec}$$

$$12 = A_1 + A_2 \quad \dots \textcircled{1}$$

$$\underbrace{-450,000}_{f_1} = \underbrace{-5,000}_{f_1} A_1 - \underbrace{20,000}_{f_2} A_2 \quad \dots \textcircled{2} \quad \left. \vphantom{\begin{matrix} 12 = A_1 + A_2 \\ -450,000 = -5,000 A_1 - 20,000 A_2 \end{matrix}} \right\} \Rightarrow \begin{matrix} A_1 = -14 \\ A_2 = 26 \end{matrix}$$

$$V(t) = -14 e^{-5000t} + 26 e^{-20,000t}, \quad t \geq 0$$

(b) Under-damped response ($\alpha < \omega_0$)

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm \sqrt{-1(\omega_0^2 - \alpha^2)}$$

$$s_{1,2} = -\alpha \pm j\omega_d ; \omega_d = \sqrt{\omega_0^2 - \alpha^2} + j = \sqrt{-1}$$

↓
damped

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}$$

$$v(t) = A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t} = e^{-\alpha t} \left[A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t} \right]$$

$$v(t) = e^{-\alpha t} \left[A_1 \cos(\omega_d t) + jA_1 \sin(\omega_d t) + A_2 \cos(\omega_d t) - jA_2 \sin(\omega_d t) \right]$$


$$v(t) = e^{-\alpha t} \left[\underbrace{(A_1 + A_2)}_{\beta_1} \cos \omega_d t + j \underbrace{(A_1 - A_2)}_{\beta_2} \sin \omega_d t \right]$$

$$v(t) = e^{-\alpha t} \left[\beta_1 \cos(\omega_d t) + \beta_2 \sin(\omega_d t) \right]$$

$$v(0^+) = \beta_1 = V_0$$

$$\frac{dv(0^+)}{dt} = \omega_d \beta_2 - \alpha \beta_1 = \frac{1}{C} \left[I_0 - \frac{V_0}{R} - I_0 \right]$$

EX

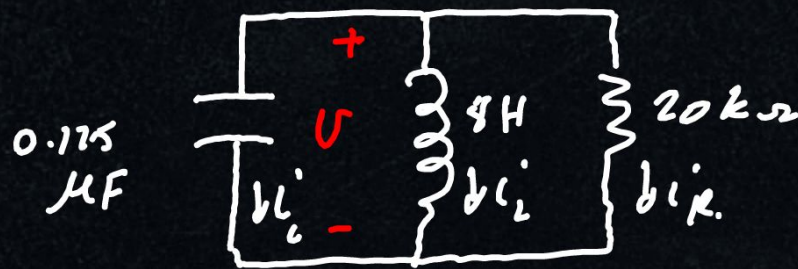

$$V_o = 0$$

$$I_o = -12.25 \text{ mA}$$

Find V , i_R , i_L + i_C

$$\alpha = \frac{1}{2RC} = \frac{1}{2(20 \times 10^3) \times (0.175 \times 10^{-6})} = 200 \text{ r/s}$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{8 \times 0.175 \times 10^{-6}}} = 1000 \text{ r/sec}$$

$\alpha < \omega_o \Rightarrow$ under-damped

$$V(t) = e^{-\alpha t} [\beta_1 \cos(\omega_d t) + \beta_2 \sin(\omega_d t)]$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{(1000)^2 - (200)^2} = 980 \text{ r/sec}$$

$$V(0^+) = V_0 = 0$$

$$\frac{dV(0^+)}{dt} = \frac{1}{C} \left(\cancel{I_s} - \cancel{\frac{V}{R}} - \cancel{I_L} \right) = 98,000 \text{ V/sec}$$


$\downarrow$ $\downarrow$ $\downarrow$
 0.125×10^{-6} 0 -12.75×10^{-3}

$$V(0^+) = \beta_1 = 0$$

$$\frac{dV(0^+)}{dt} = -\cancel{\alpha} \beta_1 + \omega_d \beta_2 = 98,000 \Rightarrow \beta_2 = \frac{98000}{980} = 100$$

$$V(t) = e^{-200t} [100 \sin(980t)]$$
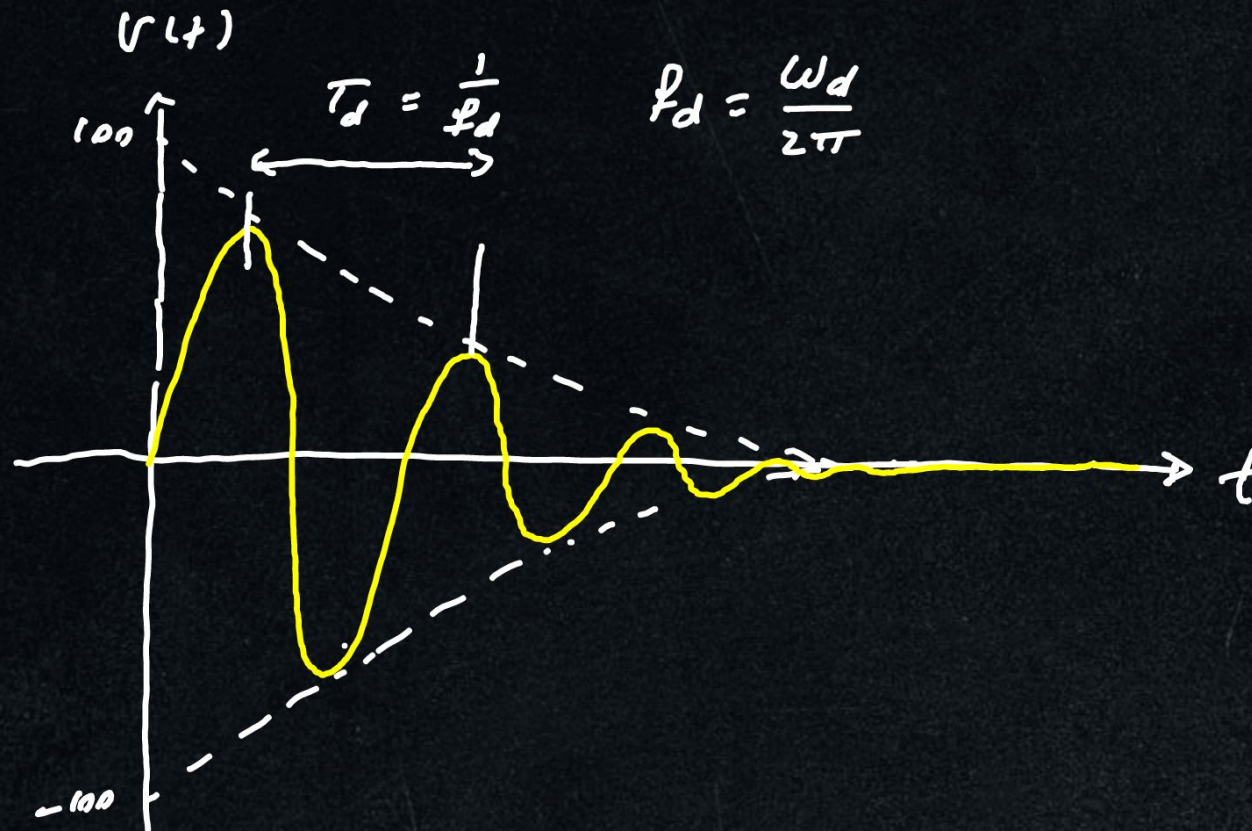
$$V(t) = 100 e^{-200t} \sin(980t) \quad \text{✓}, \quad t \geq 0$$




$$v(t) = 100 e^{j980t} \quad \text{V}, t \geq 0$$

$$i'_C = C \frac{dv}{dt}$$

$$i'_R = \frac{v}{R}$$

$$i'_L = \frac{1}{L} \int v dt + I_0$$
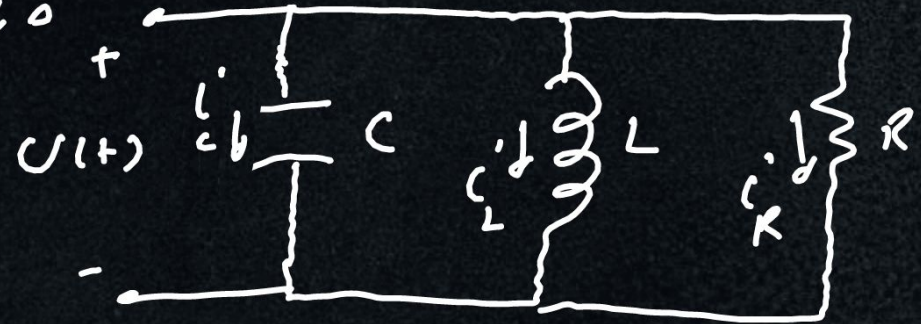
$$= -i'_R - i'_C = -\frac{v}{R} - C \frac{dv}{dt}$$



$$i'_R + i'_C + i'_L = 0$$

$$i'_L = -i'_R - i'_C$$

$$\int e^{ix} \sin x \, dx = \int \frac{e^{ix} e^{ix} - e^{ix} e^{-ix}}{2i} \, dx$$

$$\sin x = \frac{e^{ix} - e^{-ix}}{2i}$$

$$= \int \frac{e^{(1+i)x} - e^{(1-i)x}}{2i} \, dx$$

$$= \frac{1}{2i} \int e^{(1+i)x} \, dx - \frac{1}{2i} \int e^{(1-i)x} \, dx$$

parallel connected RLC



$$\begin{aligned} i_R &= \frac{v}{R} \\ i_C &= C \frac{dv}{dt} \\ i_L &= I_s - i_R - i_C \end{aligned}$$

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\left. \begin{aligned} v(0^+) &= V_0 \\ \frac{dv(0^+)}{dt} &= \frac{1}{C} \left(I_s - \frac{V_0}{R} - \frac{I_s}{\omega_0} \right) \end{aligned} \right\}$$

Overdamped

$$\alpha > \omega_0$$

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$v(0^+) = A_1 + A_2$$

$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2$$

Underdamped

$$\alpha < \omega_0$$

$$v = e^{-\alpha t} [\beta_1 \cos \omega_d t + \beta_2 \sin(\omega_d t)]$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$v(0^+) = \beta_1$$

$$\frac{dv(0^+)}{dt} = \omega_d \beta_2 - \alpha \beta_1$$

Critically-damp.

$$\alpha = \omega_0$$

$$v = (D_1 t + D_2) e^{-\alpha t}$$

$$v(0^+) = D_2$$

$$\frac{dv(0^+)}{dt} = D_1 - \alpha D_2$$

Series connected RLC circuit



V_0 : initial capacitive voltage ($\frac{1}{2} C V_0^2$)

I_0 : initial inductive current ($\frac{1}{2} L I_0^2$)

KVL in the loop

$$V_s = V_R + V_L + V_C$$

$$V_R = R i$$

$$V_L = L \frac{di}{dt}$$

$$V_C = \frac{1}{C} \int i dt + V_0$$

$$V_s = R i + L \frac{di}{dt} + \frac{1}{C} \int i dt + V_0$$

$$0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i \Rightarrow$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Charach. equation $s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha > \omega_0 \Rightarrow \text{overdamped} \Rightarrow i = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha < \omega_0 \Rightarrow \text{Under damped} \Rightarrow i = e^{-\alpha t} [\beta_1 \cos(\omega_d t) + \beta_2 \sin(\omega_d t)]$$

$$\alpha = \omega_0 \Rightarrow \text{critically-damped} \Rightarrow i = e^{-\alpha t} [D_1 t + D_2]$$

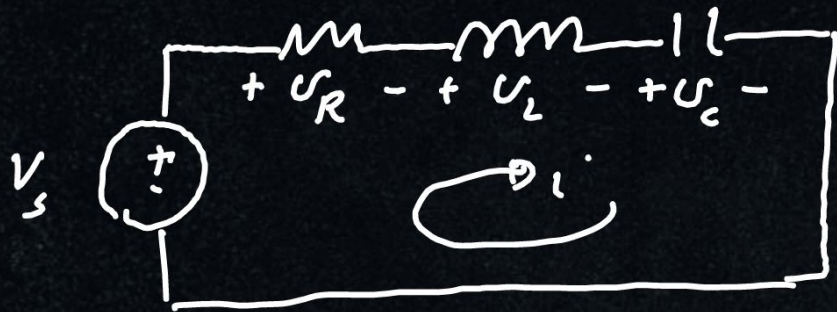To find (A_1, A_2) , (B_1, B_2) , or (D_1, D_2) , calculate $i(0^+) + \frac{di(0^+)}{dt}$



$$i(0^+) = i(0^-) = i(0) = I_0$$

$$V_L = L \frac{di}{dt}$$


$$V_s = V_R + V_L + V_C$$

$$V_L = V_s - V_R - V_C$$


$$V_L(0^+) = L \frac{di(0^+)}{dt} = V_s - V_R(0^+) - V_C(0^+)$$

$$\frac{di(0^+)}{dt} = \frac{1}{L} [V_s - R I_0 - V_0]$$

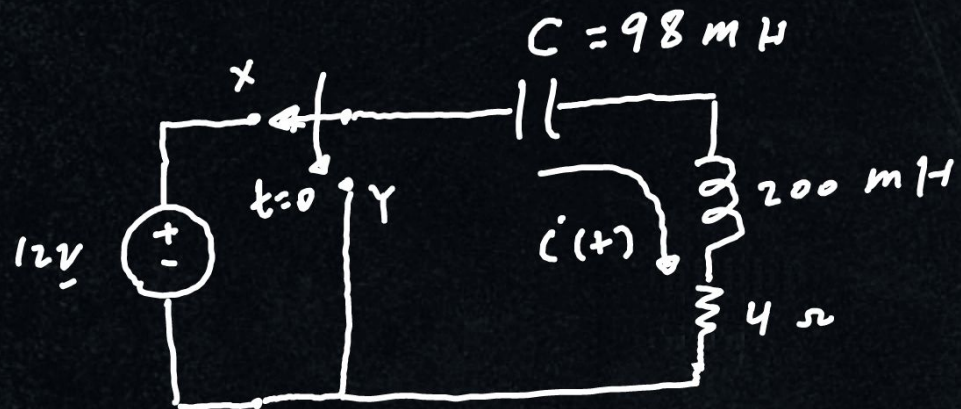EX:- The switch has been in position x for a long time. At $t=0$, the switch moves to position y . Calculate $i(t)$ $t \geq 0$




$t = 0^-$ (C is o/c + L is s/c)

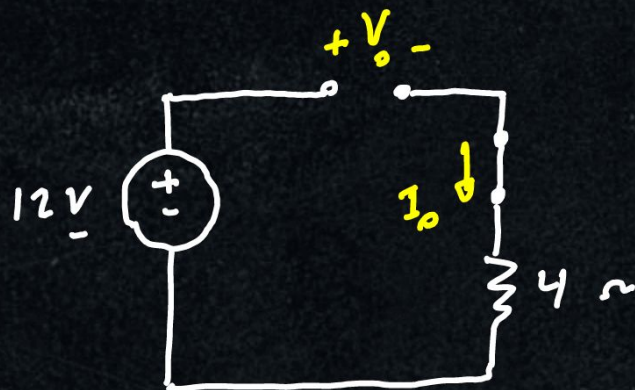

$$I_0 = 0$$

$$V_0 = 12 \text{ V}$$

$t \geq 0$

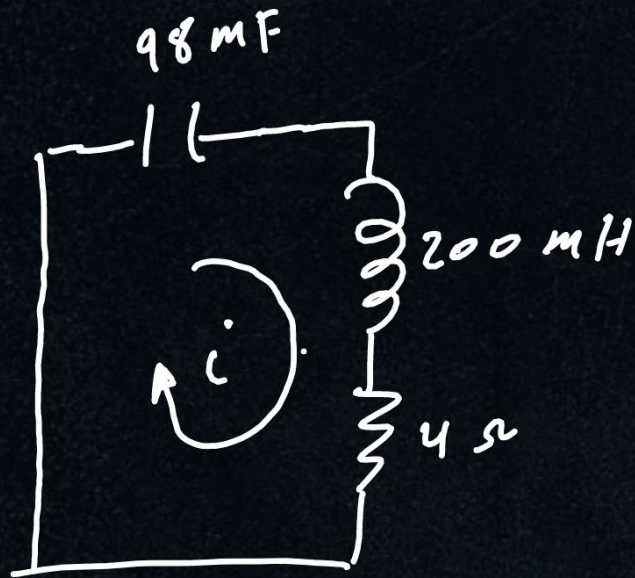

$$\alpha = \frac{R}{2L} = \frac{4}{2(0.2)} = 10 \text{ r/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(200)(98) \times 10^{-6}}} = 7.143 \text{ r/sec}$$

$\alpha > \omega_0 \Rightarrow \text{overdamped}$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = \begin{cases} -3 \text{ r/s} \\ -17 \text{ r/s} \end{cases}$$

$$i = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$i(0^+) = A_1 + A_2 = 0$$

$$A_1 = -A_2 \quad \text{--- (1)}$$


$$\frac{di(0^+)}{dt} = s_1 A_1 + s_2 A_2$$

$$-3A_1 - 17A_2 = -60 \quad \text{--- (2)} \Rightarrow A_1 = -4.29, A_2 = 4.29$$

$$i(0^+) = I_0 = 0$$

$$\frac{di(0^+)}{dt} = \frac{1}{L} [V_s - R I_0 - V_0] = \frac{-12}{0.2} = -60 \text{ A/s}$$
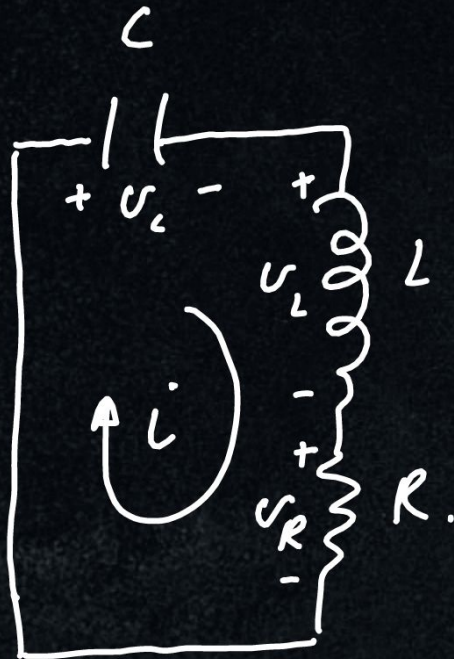
$$i(t) = 4.29 e^{-3t} + 4.29 e^{-17t} \text{ A} \quad t \geq 0$$




$$V_R = Ri$$

$$V_L = L \frac{di}{dt}$$

$$V_c = -V_R - V_L$$

EX :-

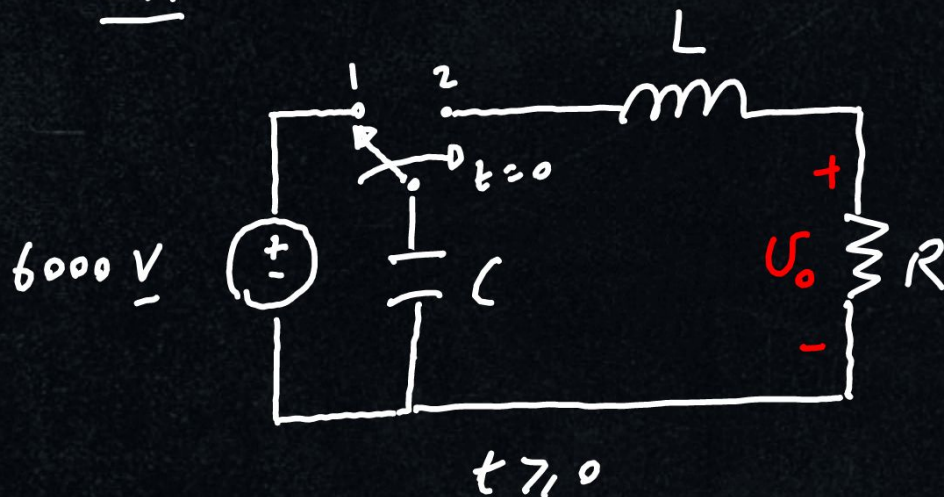


$$C = 31 \mu F$$

$$R = 50 \Omega$$

$$L = 50.3 \text{ mH}$$


The switch has been in position '1' for a long time. At $t=0$, the switch moves to position '2'. Find $V_o(t)$ $t > 0$.

$t = 0^-$ (C is o/c + L is s/c)

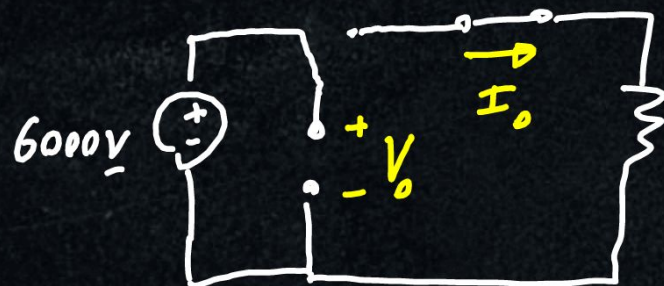

$$V_o = 6000 \text{ V}$$

$$I_o = 0$$

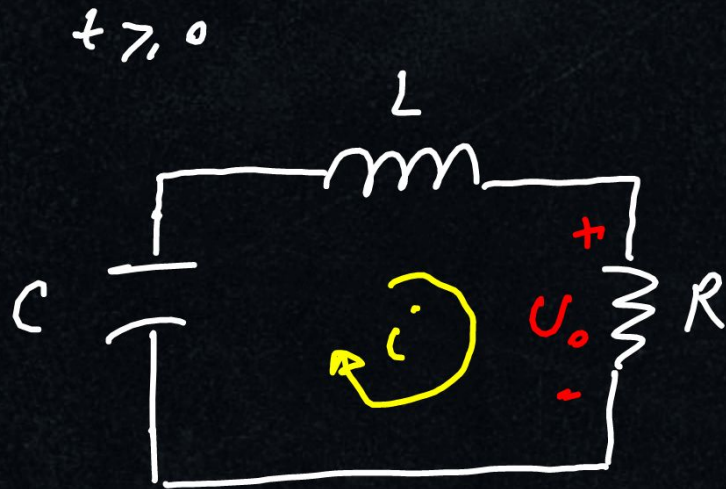

$$R = 50 \, \Omega$$

$$L = 50.3 \, \text{mH}$$

$$C = 31 \, \mu\text{F}$$

$$\alpha = \frac{R}{2L} = \frac{50}{2(50.3 \times 10^{-3})} = 497 \, \text{r/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50.3 \times 31 \times 10^{-9}}} = 800.82$$

$$\alpha < \omega_0 \Rightarrow \text{Underdamped}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 627 \, \text{r/sec}$$

$$i = e^{-\alpha t} [\beta_1 \cos(\omega_d t) + \beta_2 \sin(\omega_d t)]$$

$$i(0^+) = I_0 = 0 = \beta_1$$

$$\frac{di(0^+)}{dt} = \frac{1}{L} [\cancel{V_0} - R \cancel{I_0} - V_0] = \frac{-6000}{50.3 \times 10^{-3}} = -119.28 \times 10^3 \, \text{A/s}$$

$$\beta_2 = \frac{-119.28 \times 10^3}{627} = -190$$

$$\oint = \omega_d \beta_2 - \alpha \beta_1 = \omega_d \beta_2$$