

LS
26/7/2021

ENEE2360

Analog Electronics

T5:

Zener Diode

INSTRUCTOR: NASSER ISMAIL


ENEE236 – Analog Electronics

Zener Diode Simple Voltage Regulator ?


*


- The Zener is used as a voltage regulator to maintain a constant dc output under variations in load current and ac line voltage ^{keep}
- It can also be used as protection device against overvoltage
- Analysis starts by defining state of diode followed by using appropriate model, then find unknown quantities

Voltage Regulator

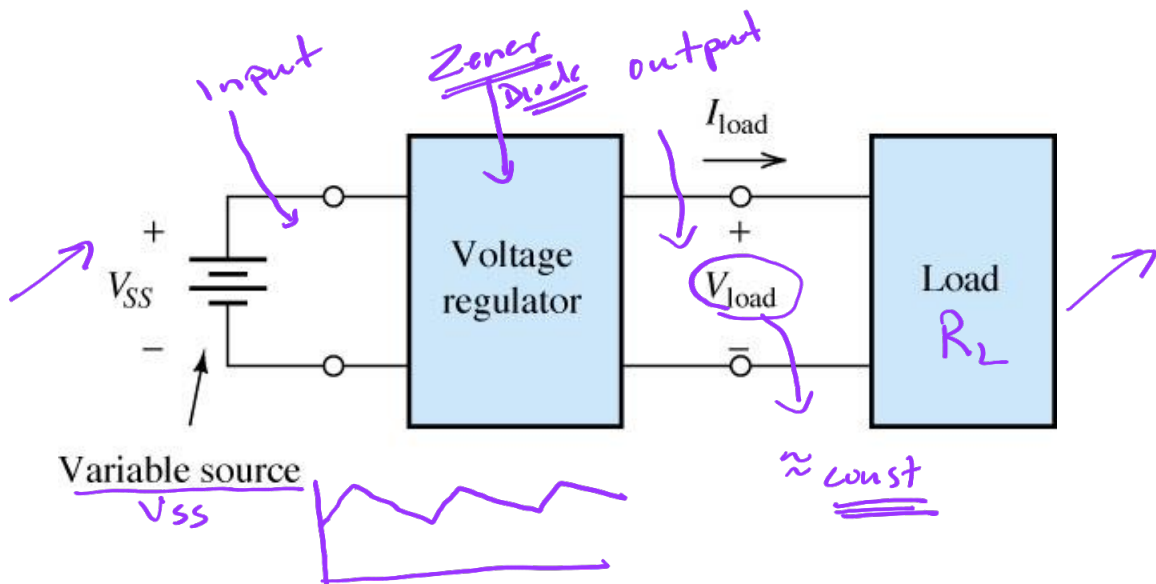


A voltage regulator supplies constant voltage to a load.

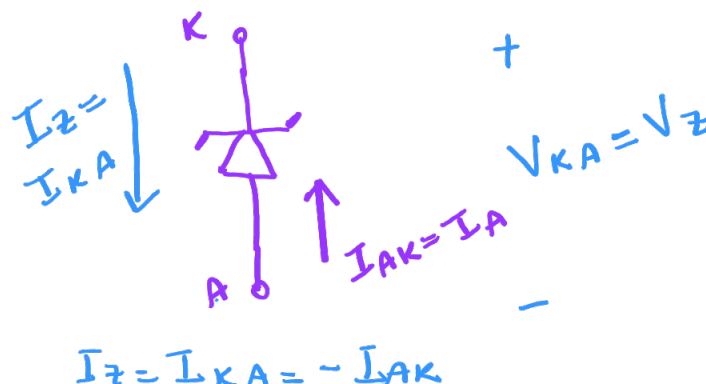

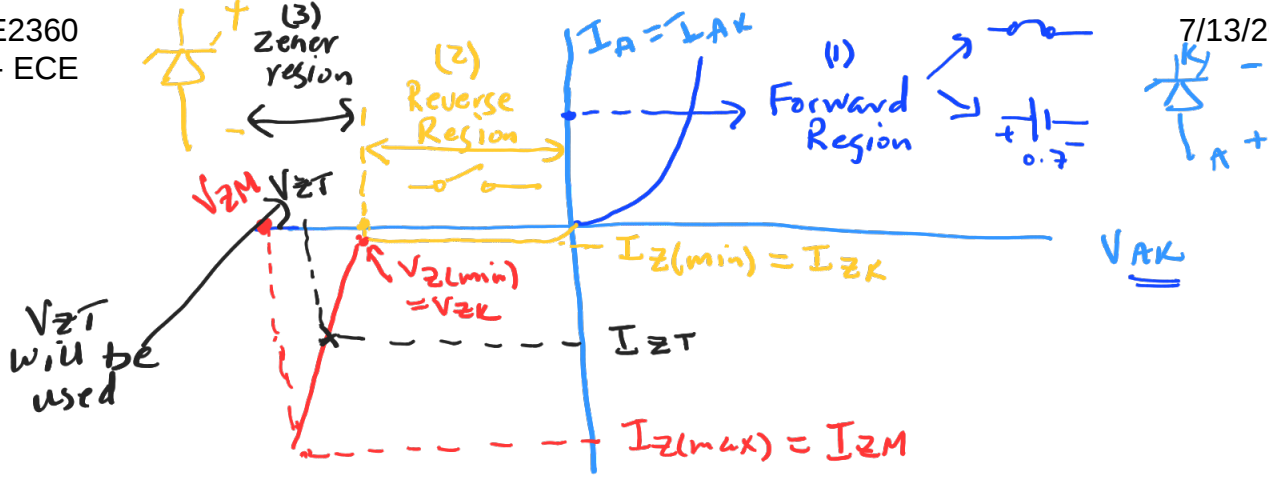

ENEE236 – Analog Electronics

Zener Diode V-I Curve

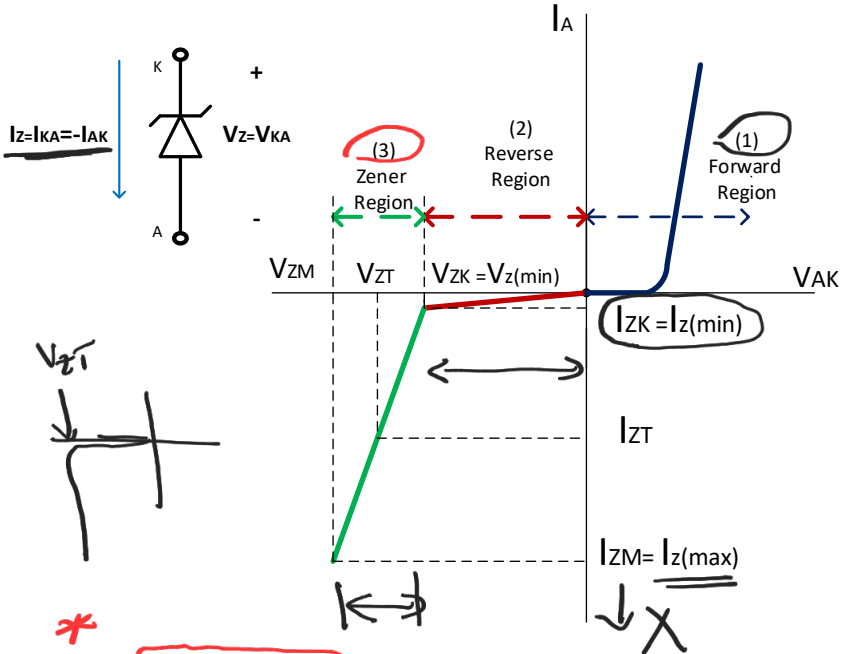


- In data sheet , we have I_{ZT} , V_{ZT}
 - Zener currents will be assumed positive if passing from cathode to Anode
 - If $I_Z < I_{ZK}$ zener will act as an open circuit
 - If $I_Z > I_{Zmax}$ zener will damaged
- region (2)*

* If $I_{ZK} < I_Z < I_{Zmax}$ zener will be in voltage regulation (zener) region

ENEE236 – Analog Electronics

Zener Diode Operation Regions

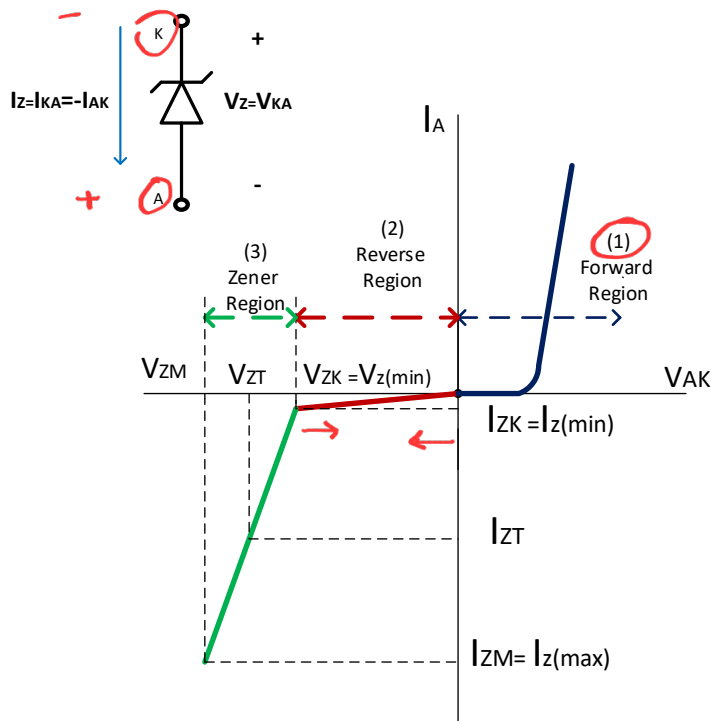

Region (1)

➤ When $V_{AK} > 0$, zener acts as regular diode ON

Region (2)

When $0 < V_{KA} < V_{ZK}$, zener acts as regular diode OFF

Region (3)

When $V_{KA} > V_{ZK}$, This is the intended operating region, and the zener acts as a voltage regulator

? Model

ENEE236 – Analog Electronics

Zener Diode Operation & Models

The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_Z).

Conditions for zener diode to operate in the breakdown (Zener/ON) region When


1. Cathode is more positive than anode
2. $V_{th} \geq V_Z$ ← *data sheet*
3. $I_Z > I_Z(\min)$
4. $I_Z < I_Z(\max)$

==> Voltage across the Zener is V_Z

• Zener current: $I_Z = I_S - I_L$


• The Zener Power: $P_Z = V_Z I_Z$

$$I_S = I_Z + I_L$$

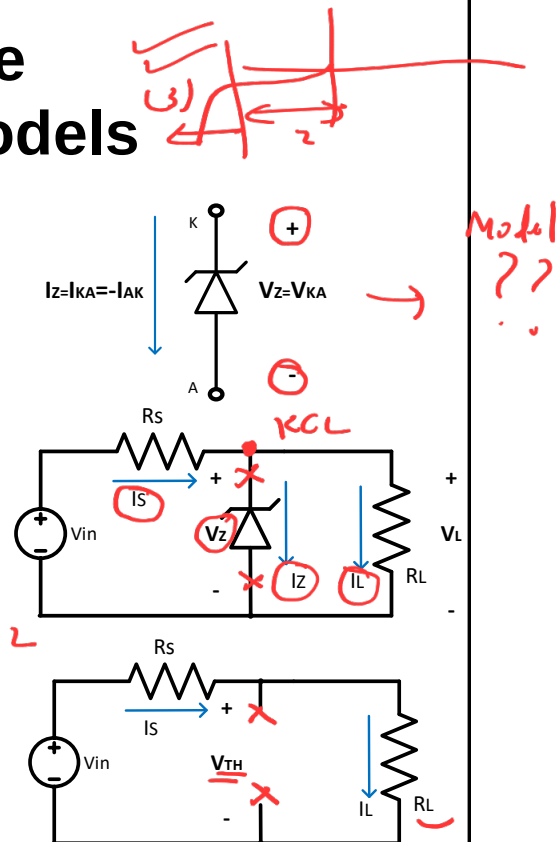

Zener Diode Models

1. Ideal Model *** ✓

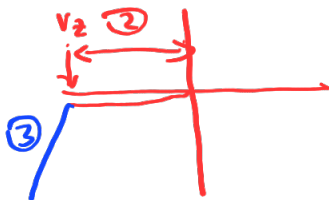




2. Simplified Model ✖


Handwritten red equation: $\Delta V_Z = \Delta I_Z \cdot r_Z$

$I_Z = I_{KA} = -I_{AK}$



$V_Z = V_{KA}$

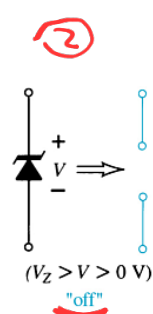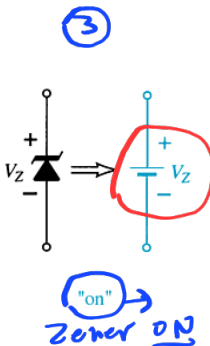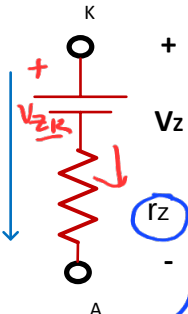

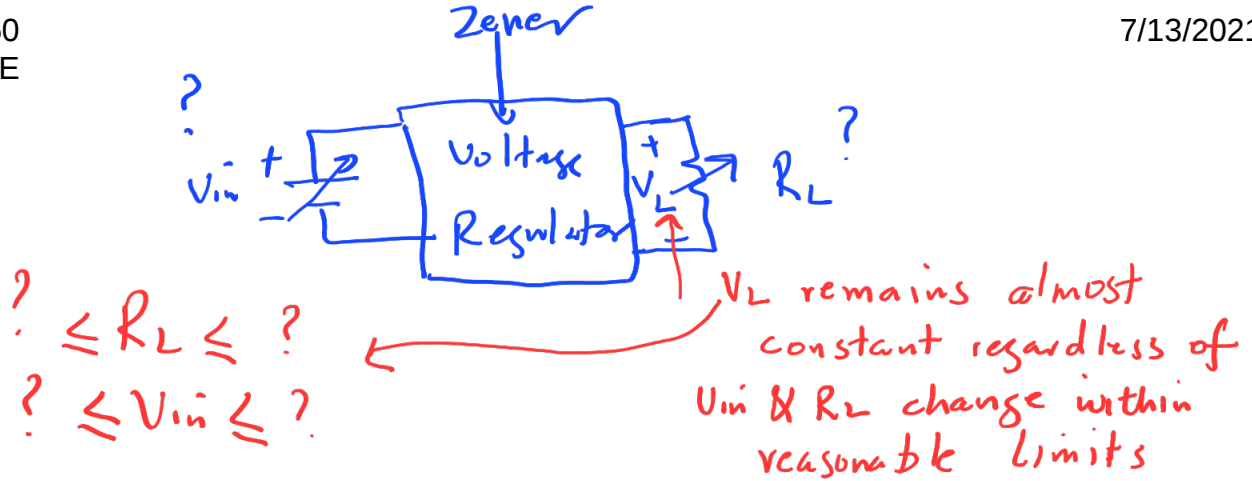

ENEE236 – Analog Electronics

Fixed V_{in} , Variable R_L

- Due to the value of V_Z , there is specific values of R_L (I_L) that ensure the zener is in the ON (regulation) state
- Too small values of R_L can result in zener being OFF

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_{in}$$

$$R_{L(min)} = \frac{R_S \cdot V_Z}{V_{in} - V_Z}$$


$$R_L \geq R_{L(min)} \Rightarrow I_{L(max)} = \frac{V_L}{R_L} = \frac{V_L}{R_{L(min)}}$$

Also, values of $R_L \geq R_{L(max)}$ can result in $\Rightarrow I_Z > I_{Z(max)}$

$$I_S = I_Z + I_L$$

$$I_L = I_S - I_Z$$

$$I_{L(min)} = I_{S(min)} - I_{Z(max)}$$

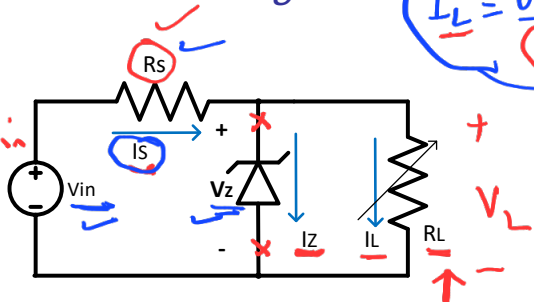

$$I_{L(min)} = I_S - I_{Z(max)}$$

$$R_{L(max)} = \frac{V_Z}{I_{L(min)}}$$

ENEE236 – Analog Electronics

Example

Given the following values of R_L , find the mode of operation of the zener and the voltage V_L , I_L , I_Z

- a) $R_L = 0.1 \text{ k}\Omega$ ✓
- b) $R_L = 0.5 \text{ k}\Omega$ ✓
- c) $R_L = 5 \text{ k}\Omega$ ✓
- d) $R_L = \infty$ ✓

SOLUTION


- a) $R_L = 0.1 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{0.1}{0.1 + 1} 35 \text{ V} = 3.18 \text{ V}$$

Zener works in region 2, it acts as open circuit
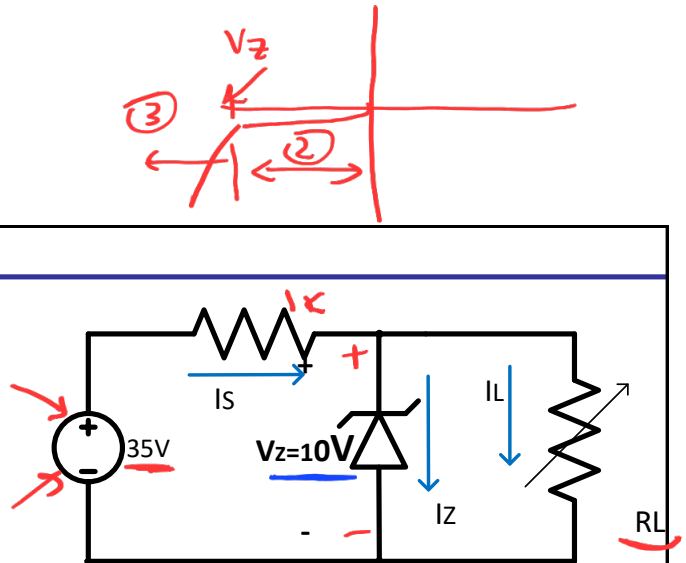
$$V_L = 3.18 \text{ V (it is not regulated)}$$



$$1) V_{th} = \frac{R_L}{R_L + R_S} \cdot V_{in}$$

$$V_{th} = \frac{0.1 \text{ k}}{0.1 \text{ k} + 1 \text{ k}} \cdot 35 = 3.18 < V_Z$$


region 2 → open circuit

$$\therefore V_L = V_{th} = 3.18 \text{ V}$$

$$I_Z = 0, I_L = \frac{3.18}{0.1 \text{ k}} = I_S$$

$$2) V_{th} = \frac{0.5 \text{ k}}{0.5 \text{ k} + 1 \text{ k}} \cdot 35$$

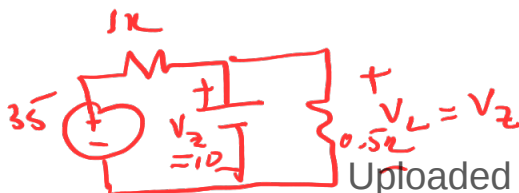
$$= 11.67 > V_Z = 10 \rightarrow \text{region 3}$$



✓

ENEE236 – Analog Electronics

Example

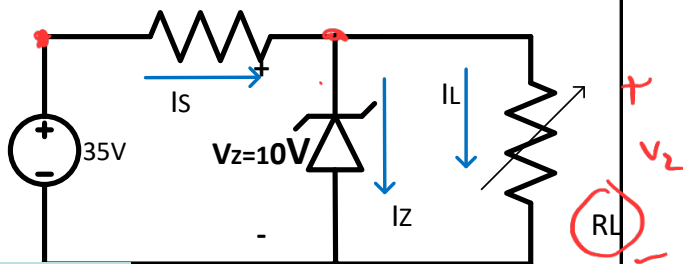

b) $R_L = 0.5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{0.5}{0.5 + 1} 35 \text{ V} = 11.67 \text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$


$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{0.5 \text{ k}\Omega} = 20 \text{ mA}$$

$$I_Z = I_S - I_L = 5 \text{ mA}$$

ENEE236 – Analog Electronics

Example

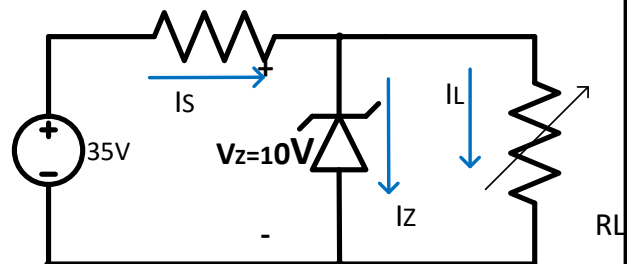

c) $R_L = 5\text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{5}{5+1} 35\text{ V} = 29.17\text{ V} > V_Z = 10$$

$V_{th} > V_Z$


Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10\text{ V}$$

$$I_S = \frac{35\text{ V} - 10\text{ V}}{1\text{ k}\Omega} = 25\text{ mA}$$


$$I_L = \frac{V_L}{R_L} = \frac{10}{5\text{ k}\Omega} = 2\text{ mA}$$

$$I_Z = I_S - I_L = 23\text{ mA}$$

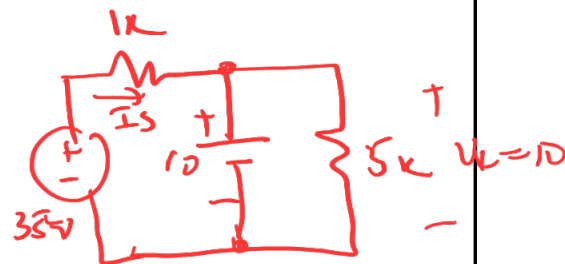

ENEE236 – Analog Electronics

Example

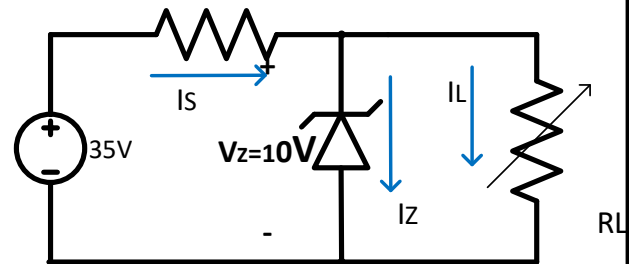

d) $R_L = \infty$

using ideal model

$$V_{th} = \frac{\infty}{\infty + R_s} V_{in} = \underline{35\text{ V}}$$

$$V_{th} > V_z$$


Zener works in region 3, it works as voltage regulator

$$V_L = V_z = \underline{10\text{ V}}$$

$$I_s = \frac{35\text{ V} - 10\text{ V}}{1\text{ k}\Omega} = \underline{25\text{ mA}}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{\infty} = \underline{0}$$


$$I_z = I_s - I_L = \underline{25\text{ mA}}$$

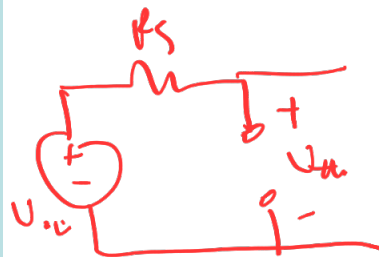

ENEE236 – Analog Electronics

Example

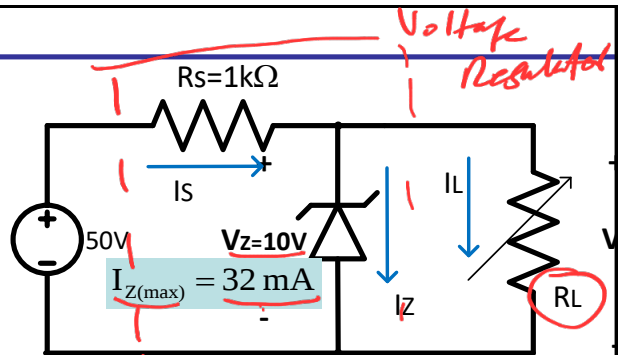- 1) Determine Range of R_L & I_L that will result in V_L being maintained at 10V
- 2) Determine the power rating of the zener diode $P_Z = V_Z \cdot I_Z$



SOLUTION

- 1) To find $R_{L(min)}$ that will turn the zener diode ON :

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_i \Rightarrow$$

$$R_L = \frac{R_S}{V_i - V_Z} V_Z$$

$$R_{L(min)} = \frac{1k\Omega}{50 - 10} 10 = 250 \Omega$$

$$250 \Omega \leq R_L \leq 1.25 k\Omega$$

- 2) To find $R_{L(max)} \Rightarrow$ we need $I_{L(min)}$

$$I_{L(min)} = I_S - I_{Z(max)}$$

$$I_S = \frac{V_i - V_Z}{R_S} = \frac{50 - 10}{1k\Omega} = 40 \text{ mA}$$

$$I_{L(min)} = 40 - 32 = 8 \text{ mA}$$

$\Downarrow$

$$R_{L(max)} = \frac{V_L}{I_{L(min)}} = \frac{10 \text{ V}}{8 \text{ mA}} = 1.25 k\Omega$$

$$3) P_{Z(max)} = V_Z \cdot I_{Z(max)} = 10 \text{ V} \cdot 32 \text{ mA} = 320 \text{ mW}$$

The zener diode is chosen with power rating $\geq P_{Z(max)}$

$$40 \text{ mA} \geq I_L \geq 8 \text{ mA}$$


$$\frac{10 \text{ V}}{250}$$

$$\frac{10 \text{ V}}{1.25 \text{ k}}$$

End of L8

1183336

29
27/7/2021

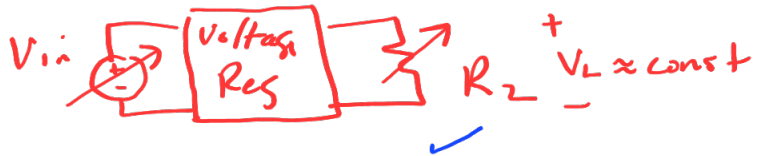

ENEE236 – Analog Electronics

Fixed R_L , Variable V_{in}

For Fixed R_L , the voltage V_{in} must be large enough to turn the zener diode on (regulation region (3))


$$V_{in} = V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$V_{in(max)}$ is limited by maximum zener current $I_{Z(max)}$

$$\begin{aligned} I_S &= I_Z + I_L \\ I_{S(max)} &= I_{Z(max)} + I_L \\ V_{i(max)} &= I_{S(max)} \cdot R_S + V_Z \end{aligned}$$

$$\Downarrow$$
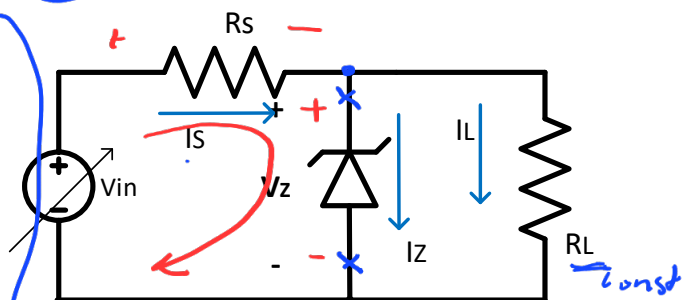
$$V_{in(min)} \leq V_{in} \leq V_{in(max)}$$



$$V_{th} = \frac{R_L}{R_L + R_S} \cdot V_{in} \geq V_Z$$

$$V_{in} \geq V_Z \frac{(R_L + R_S)}{R_L}$$

ENEE236 – Analog Electronics

Example

Find the range of values of V_i that will maintain the zener in the ON (regulation) State

$$\begin{aligned} V_{in(min)} &= \frac{R_L + R_S}{R_L} V_Z \\ &= \frac{1200 + 220}{1200} 20 = 23.07 \text{ V} \end{aligned}$$

$$I_S = I_Z + I_L$$


$$I_{S(max)} = I_{Z(max)} + I_L$$

$$I_L = \frac{V_L}{R_L} = \frac{20 \text{ V}}{1200 \Omega} = 16.67 \text{ mA}$$

$$I_{S(max)} = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$


$$V_{i(max)} = (76.67 \text{ mA}) \cdot (220 \Omega) + 20 \text{ V} = 36.87 \text{ V}$$

$$= I_{S(max)} \cdot R_S + V_Z$$

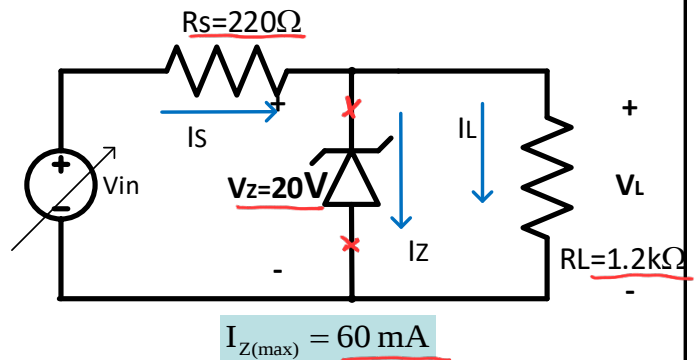

$$I_{Z(max)} = 60 \text{ mA}$$

$$\therefore 23.07 \text{ V} \leq V_{in} \leq 36.87 \text{ V}$$

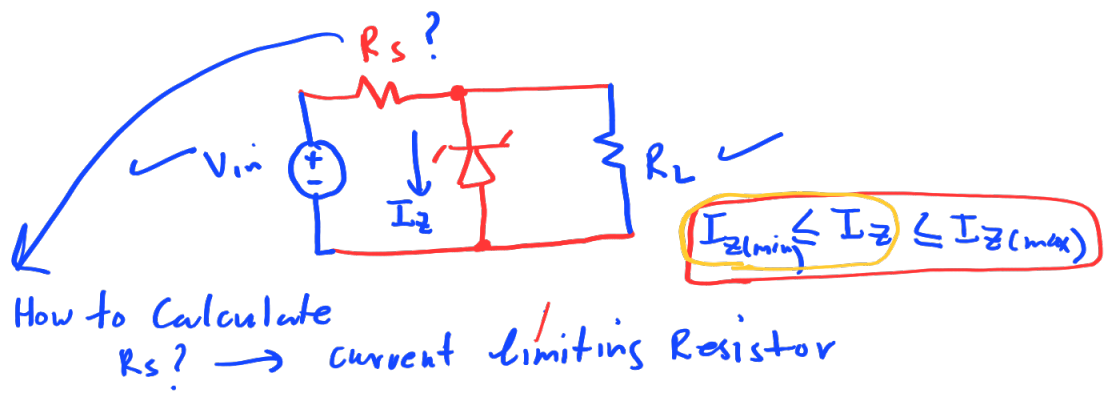

ENEE236 – Analog Electronics

Design of R_s (Current limiting Resistor)

Given : $V_Z, I_{Z(min)}, I_{Z(max)}, V_{in(min)}, V_{in(max)}, R_{L(min)}, R_{L(max)}$

Find range of acceptable R_s in the voltage regulator

$$1) I_Z = I_S - I_L \geq I_{Z(min)}$$

Worst Case : the smallest value of

$$(I_S - I_L)$$


must be always higher than $> I_{Z(min)}$

$$I_{S(min)} - I_{L(max)} \geq I_{Z(min)}$$

$$\frac{V_{S(min)} - V_Z}{R_S} - I_{L(max)} \geq I_{Z(min)}$$

$$I_{Z(min)} + I_{L(max)} \leq \frac{V_{S(min)} - V_Z}{R_S}$$

$$R_S \leq \frac{V_{S(min)} - V_Z}{I_{Z(min)} + I_{L(max)}}$$

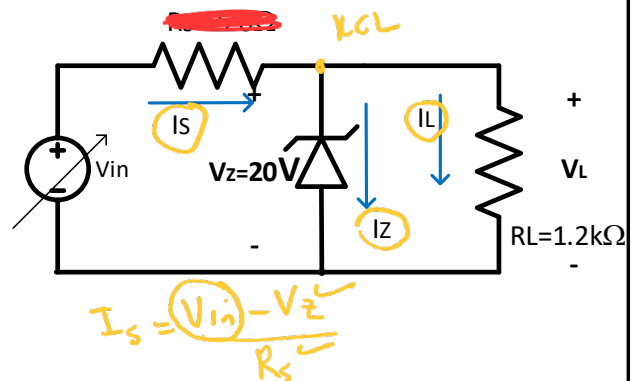

ENEE236 – Analog Electronics

Design of Rs (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$

Find range of acceptable Rs in the voltage regulator

2) $I_Z \leq I_{Z(\max)}$

Worst Case : the largest value of $(I_S - I_L)$ must be always smaller than $I_{Z(\max)}$

$$I_{S(\max)} - I_{L(\min)} \leq I_{Z(\max)}$$

$$\frac{V_{S(\max)} - V_Z}{R_S} - I_{L(\min)} \leq I_{Z(\max)}$$

$$I_{Z(\max)} + I_{L(\min)} \geq \frac{V_{S(\max)} - V_Z}{R_S}$$

$$R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Note That

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}}$$

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

ENEE236 – Analog Electronics

Design of R_s (Current limiting Resistor)

Given :

$$V_Z = 10 \text{ V},$$

$$I_{Z(\min)} = 5 \text{ mA}, I_{Z(\max)} = 200 \text{ mA},$$

$$V_{in(\min)} = 15 \text{ V}, V_{in(\max)} = 20 \text{ V},$$

$$R_{L(\min)} = 500 \Omega, R_{L(\max)} = \infty$$

Find R_s ?

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Solution

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}} = \frac{10 \text{ V}}{500 \Omega} = 20 \text{ mA}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}} = \frac{10 \text{ V}}{500 \Omega} = 0$$

$$200 \Omega \geq R_s \geq 50 \Omega$$

$$\text{let } R_s = 100 \Omega$$

ENEE236 – Analog Electronics

Variation of V_Z (using simplified model)


للعلم فقط

$$r_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

If V_{ZT} , I_{ZT} & r_Z are known

$$\begin{aligned} V_{Z(max)} = V_{ZM} &= V_{ZT} + \Delta I_Z \cdot r_Z \\ &= V_{ZT} + (I_{Z(max)} - I_{ZT}) \cdot r_Z \end{aligned}$$

$$\begin{aligned} V_{Z(min)} = V_{ZK} &= V_{ZT} - \Delta I_Z \cdot r_Z \\ &= V_{ZT} - (I_{ZT} - I_{Z(min)}) \cdot r_Z \end{aligned}$$

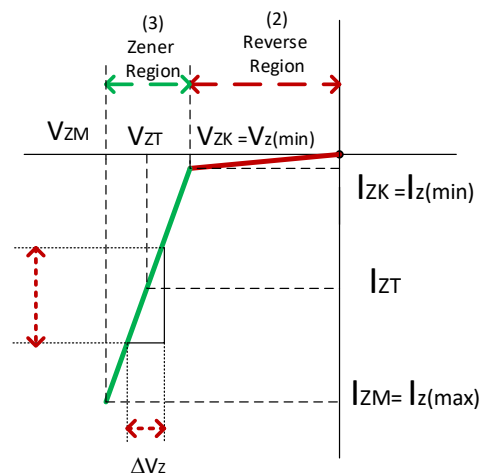

ENEE236 – Analog Electronics

Example

If $V_{ZT} = 15V$ at $I_{ZT} = 17mA$

& $r_{ZT} = 14\Omega$

$I_{ZK} = 0.25mA$

$P_{Zmax} = 1Watt$

Find :

1) Minimum and Maximum Values of V_Z



2) Value of R_S

3) Value of $R_{L(min)}$

$$1) I_{Z(max)} \cong \frac{P_{Z(max)}}{V_Z} = \frac{1Watt}{15} = 66.7mA$$

$$\begin{aligned} V_{Z(max)} = V_{ZM} &= V_{ZT} + \Delta I_Z \cdot r_Z \\ &= V_{ZT} + (I_{Z(max)} - I_{ZT}) \cdot r_Z \\ &= 15 + (66.7 - 17)mA (14\Omega) = 15.7V \end{aligned}$$
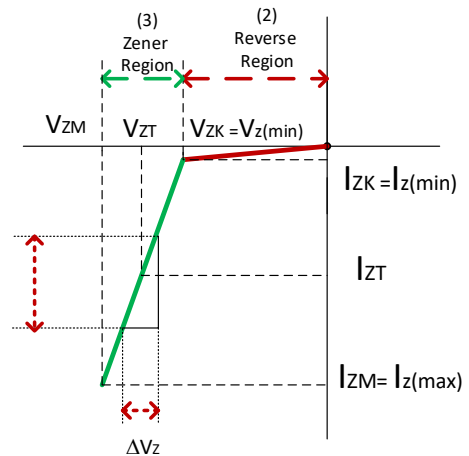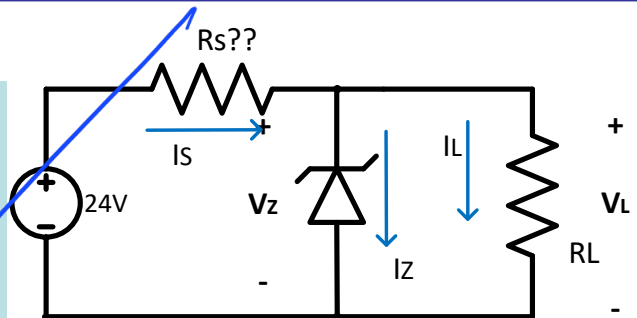
$$\begin{aligned} V_{Z(min)} = V_{ZK} &= V_{ZT} - \Delta I_Z \cdot r_Z \\ &= V_{ZT} - (I_{ZT} - I_{Z(min)}) \cdot r_Z \end{aligned}$$



Example

The diagram shows a DC circuit for Zener diode regulation. A 24V DC voltage source is connected in series with a resistor R_S . This series combination is connected to a Zener diode (labeled V_Z) in parallel with a load resistor R_L . The Zener diode is oriented with its cathode to the positive terminal. The current through the resistor R_S is labeled I_S . The current through the Zener diode is labeled I_Z , and the current through the load resistor R_L is labeled I_L . The output voltage across the load resistor is labeled V_L .

Figure 1 illustrates the Zener diode characteristic curve, plotting current I_Z against voltage V_Z . The curve shows a sharp increase in current at the breakdown voltage V_{ZT} . The region to the left of V_{ZT} is labeled (3) Zener Region, and the region to the right is labeled (2) Reverse Region. Key voltage points are V_{ZM} , V_{ZT} , and $V_{ZK} = V_{Z(min)}$. Key current points are I_{ZT} and $I_{ZM} = I_{Z(max)}$. The voltage difference between V_{ZM} and V_{ZT} is labeled ΔV_Z .

ENEE236 – Analog Electronics



Example


$$3) R_{L(\min)} \Rightarrow I_{L(\max)}$$

$$I_{L(\max)} = I_S - I_{L(\min)}$$

$$= 66.7 \text{ mA} - 0.25 \text{ mA} = 66.45 \text{ mA}$$

$$\therefore R_{L(\min)} = \frac{V_{Z(\min)}}{I_{L(\max)}} = \frac{14.76 \text{ V}}{66.45 \text{ mA}} \cong 222 \Omega$$

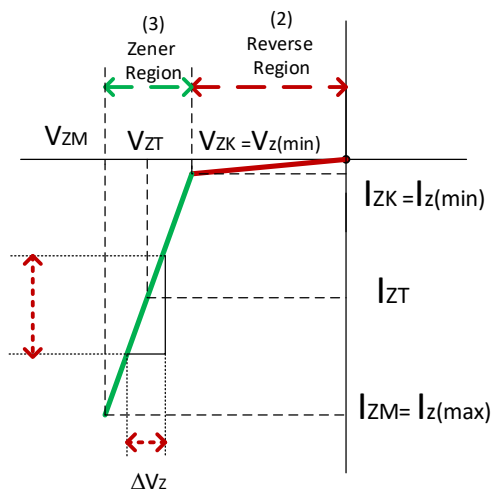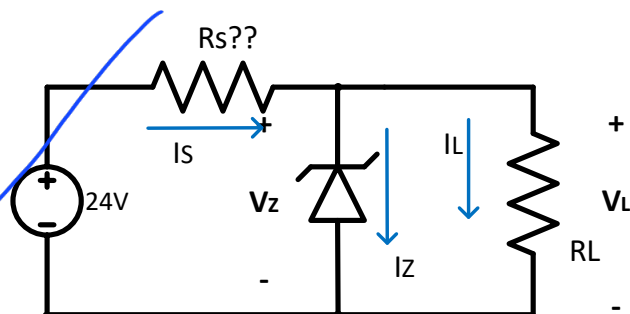

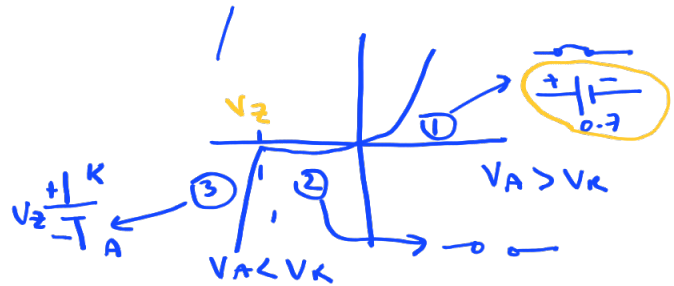

ENEE236 – Analog Electronics

Clipper circuits using Zeners

- a) When $V_i(t) < -0.7$ V, Zener works in region (1) as regular diode ON

$$0.7 + i_D(t) \cdot R + V_i(t) = 0$$

$$i_D(t) = \frac{-V_i(t) - 0.7}{R} > 0$$

$$V_i(t) < -0.7$$




$$\therefore V_O(t) = -0.7$$

- b) When $V_Z > V_i(t) > -0.7$ V, Zener works in region (2) as regular diode OFF

$$\therefore V_O(t) = V_i(t) \quad \checkmark$$

- c) When $V_i(t) > V_Z$, Zener works in region (3) as voltage regulator

$$\therefore V_O(t) = V_Z$$

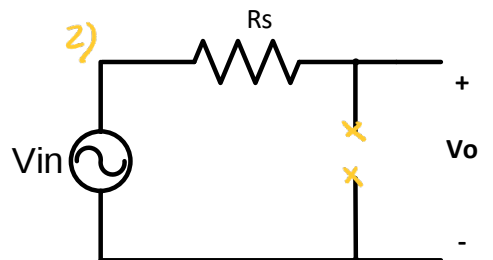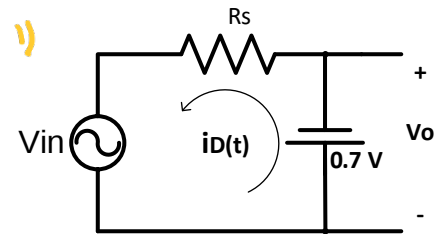
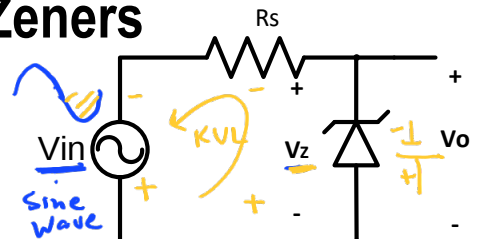



ENEE236 – Analog Electronics

Clipper circuits using Zeners

c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator

$$\therefore V_o(t) = V_z$$

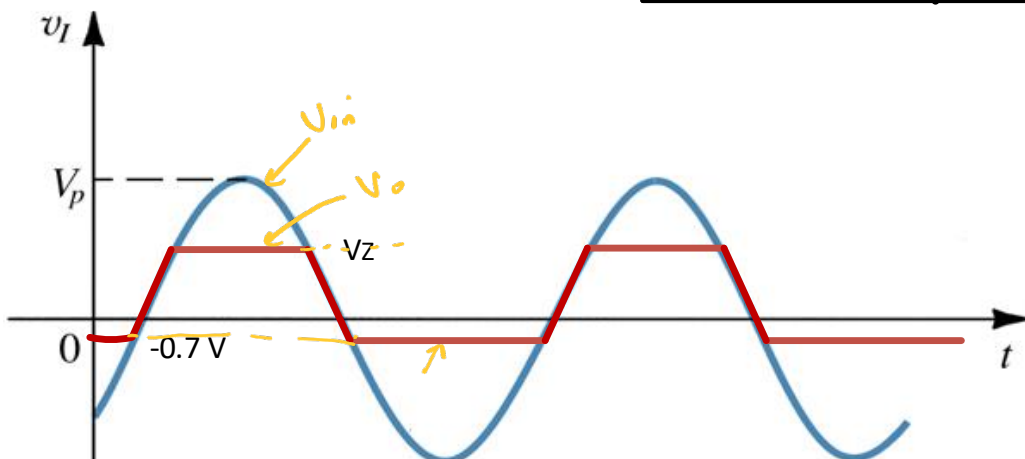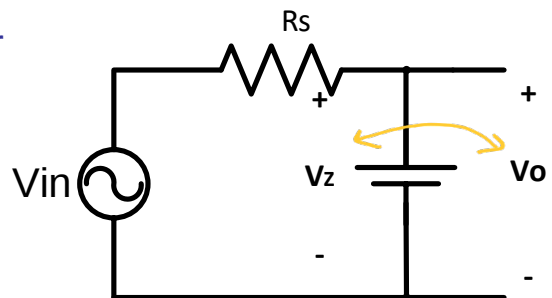

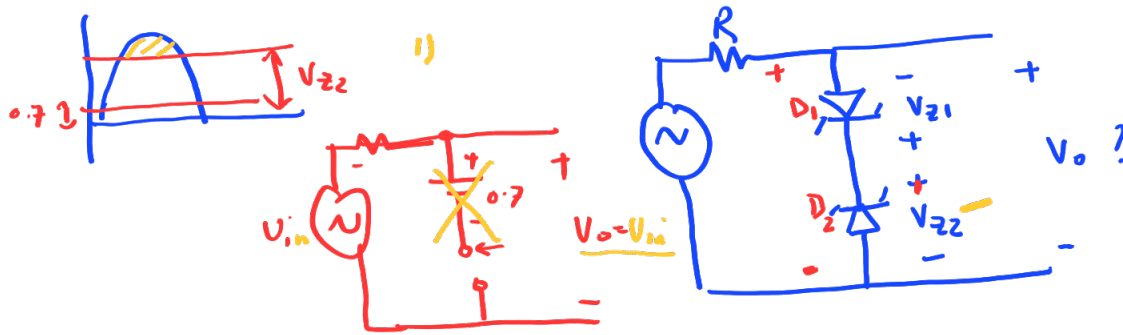



ENEE236 – Analog Electronics

Clipper circuits using Zeners

Find and sketch $V_o(t)$


- a) When $0.7V < V_i(t) < V_{Z2}$,
 D1- regular diode ON ✓ (1)
 D2- regular diode OFF ✓ (2)

$$\therefore V_o(t) = V_i(t)$$

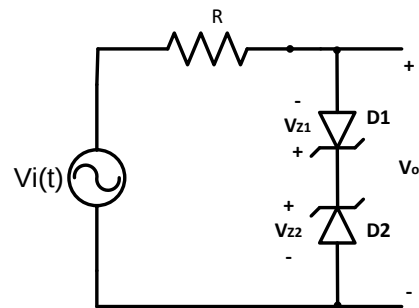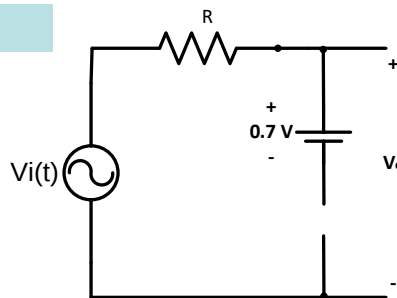

- b) When $V_i(t) > V_{Z2}$
 D1 – ON (region 1) ✓
 D2- Zener ON (region 3) ✓



$$\therefore V_o(t) = V_{Z2} + 0.7$$

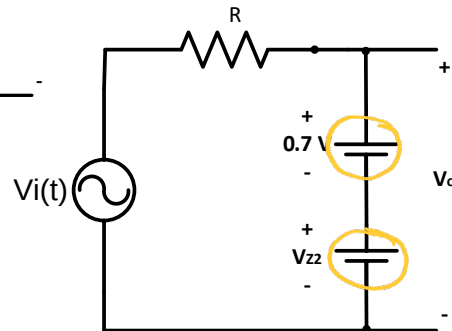




Clipper circuits using Zeners

c) When $-0.7V > V_i(t) > -V_{Z1}$,
D1- regular diode OFF
D2- regular diode ON

$\therefore V_o(t) = V_i(t)$

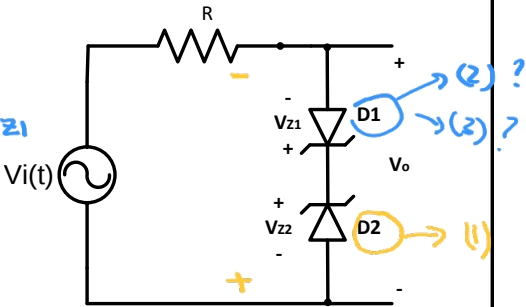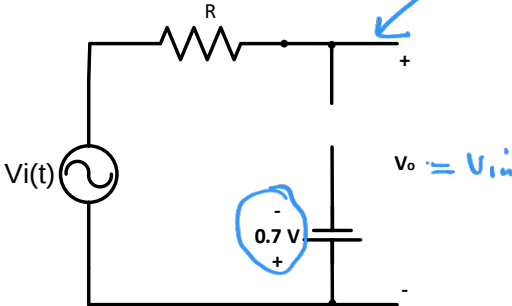

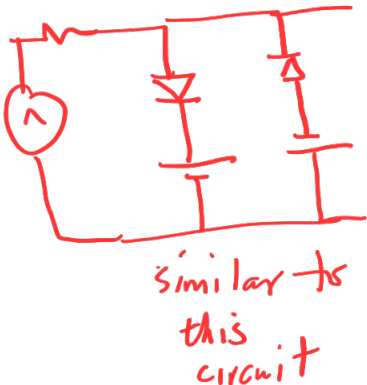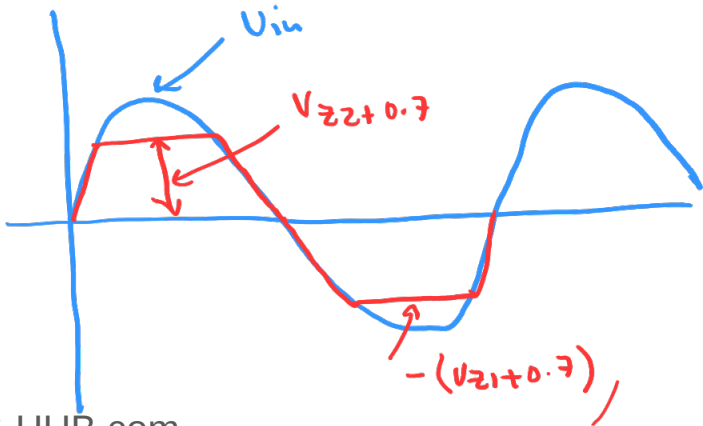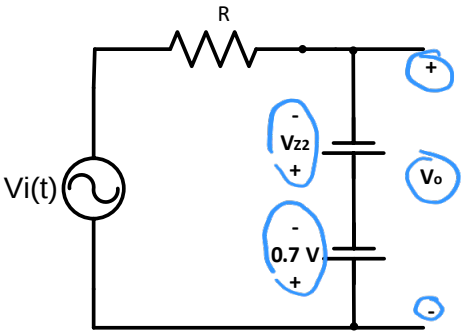d) When $V_i(t) < -V_{Z1}$
D2 – ON (region 1)
D1- Zener ON (region 3)
 $\therefore V_o(t) = -V_{Z1} - 0.7$




Voltage-Multiplier Circuits

Voltage multiplier circuits use a combination of diodes and capacitors to step up the output voltage of rectifier circuits. Three common voltage multipliers are the:

Voltage Doubler → $\times 2$



Voltage Tripler → $\times 3$

Voltage Quadripler → $\times 4$

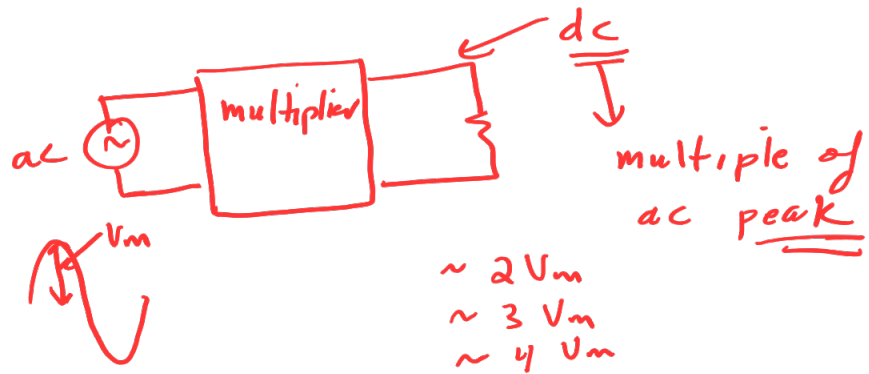

ENEE236 – Analog Electronics

Voltage Doubler

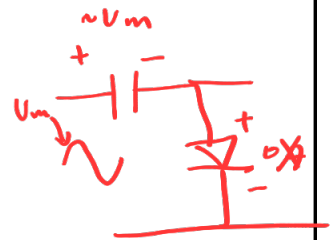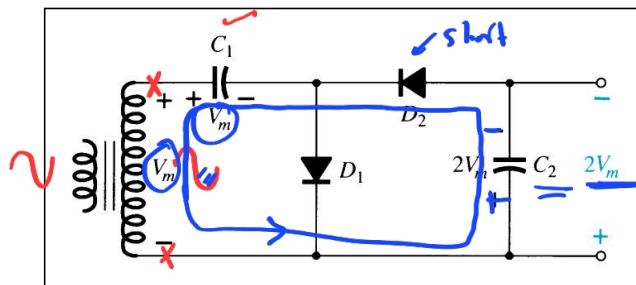

This half-wave voltage doubler's output can be calculated using:

$$V_{out} = V_{C2} = 2V_m$$

where V_m = peak secondary voltage of the transformer

ENEE236 – Analog Electronics

Voltage Doubler

similar to clamper circuit


Positive Half-Cycle

D_1 conducts
 D_2 is switched off
Capacitor C_1 charges to V_m

Negative Half-Cycle

D_1 is switched off
 D_2 conducts
Capacitor C_2 charges to V_m


$$V_{out} = V_{C2} = 2V_m$$

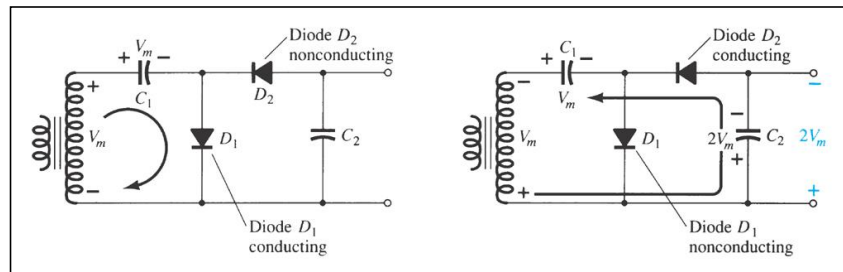

Test in the Lab

ENEE2103

Voltage Tripler and Quadrupler

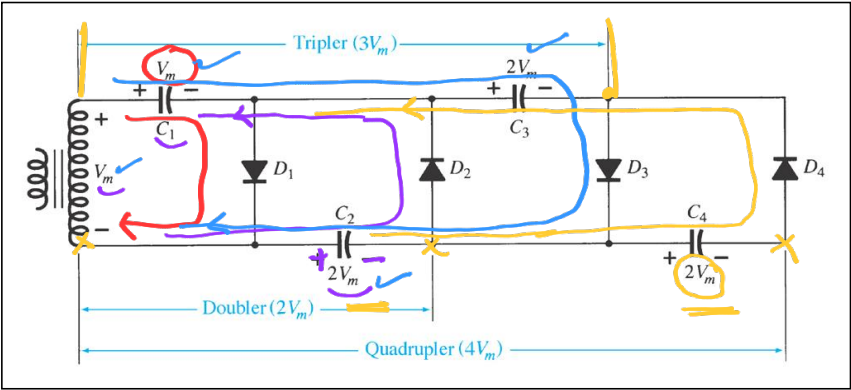

End of Diodes