



DEPARTMENT OF COMPUTER SYSTEM ENGINEERING

Digital Integrated Circuits - ENCS333

Dr. Khader Mohammad


Lecture #10 Dynamic and Sequential circuit

Integrated-Circuit Devices and Modeling

nMOS Logic Gates

- We will look at nMOS logic first, simpler than CMOS
- nMOS Logic (no pMOS transistors)
 - assume a resistive load to VDD
 - nMOS switches pull output low based on inputs


nMOS Inverter

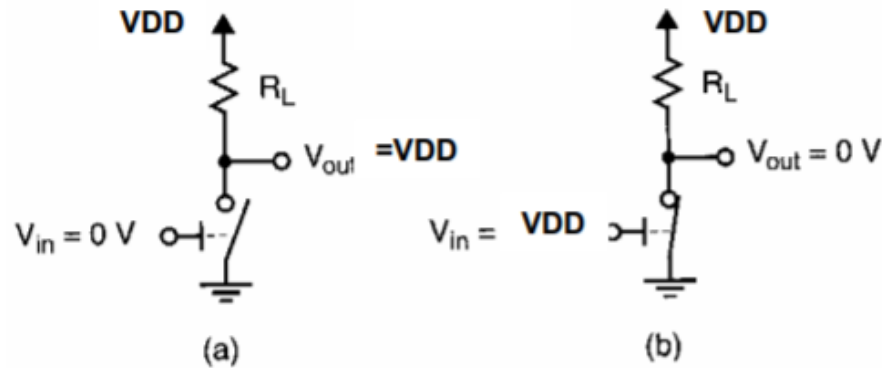

(a) nMOS is **off**
 → output is high (1)



(b) nMOS is **on**
 → output is low (0)

nMOS NOR

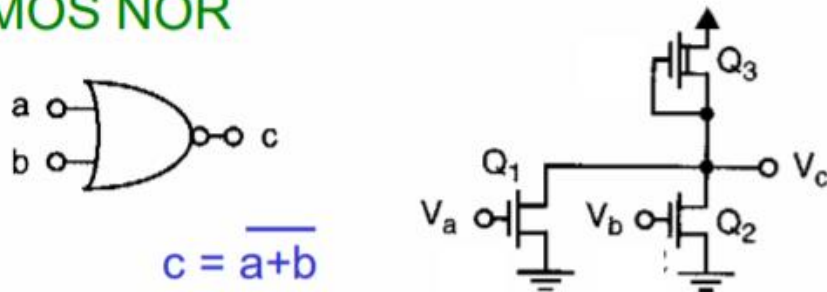

- parallel switches = OR function
- nMOS pulls low (NOTs the output)

nMOS NAND

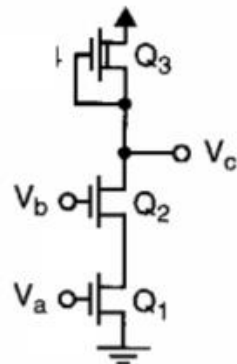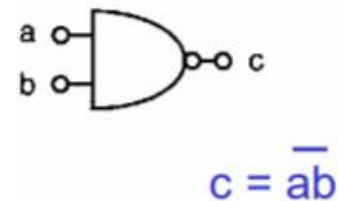

- series switches = AND function
- nMOS pulls low (NOTs the output)




DEPARTMENT OF COMPUTER SYSTEM ENGINEERING

Digital Integrated Circuits - ENCS333

Dynamic Gate

Complementary Design

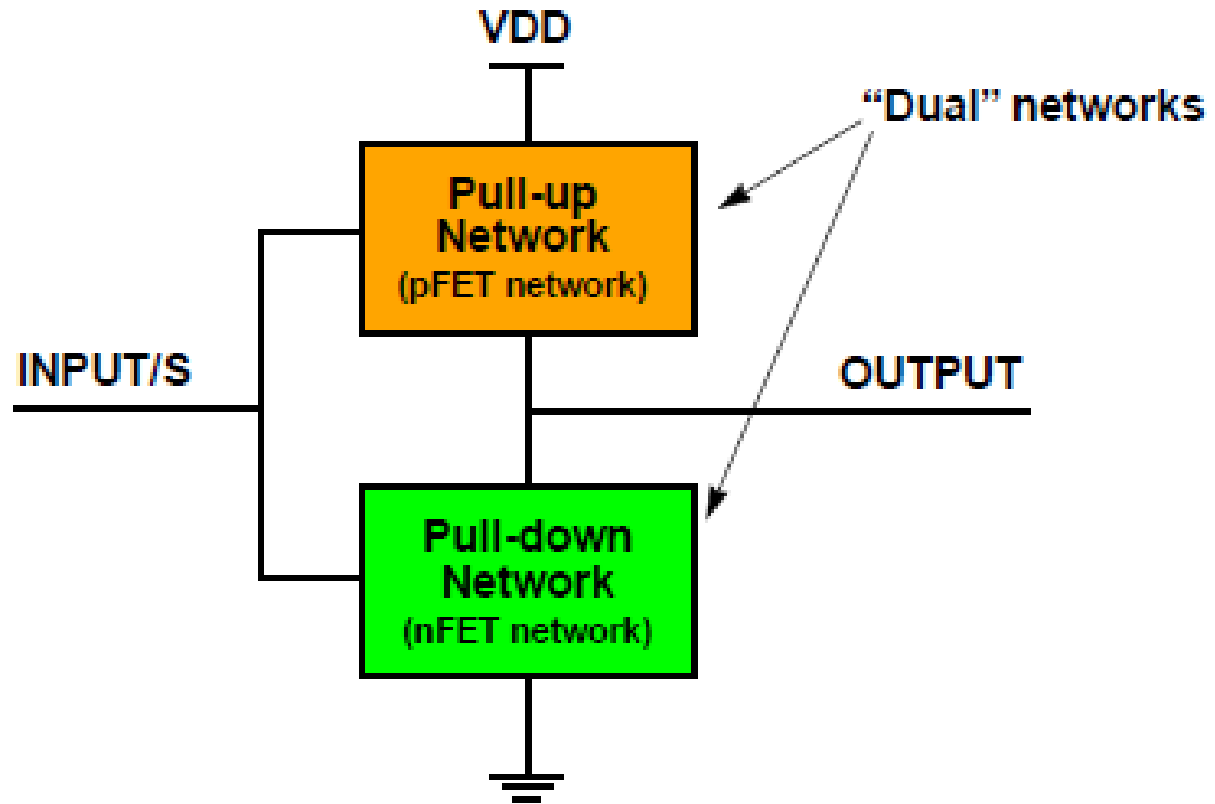



- PMOS “Pull-Up” Network (PUN)
- NMOS “Pull-Down” Network (PDN)

Dynamic Gate

Two phase operation

Precharge (CLK = 0)

Evaluate (CLK = 1)

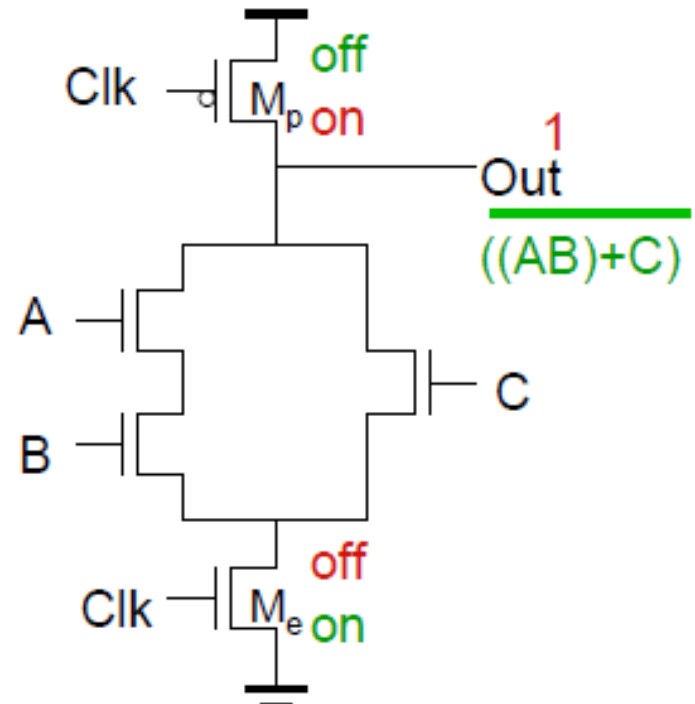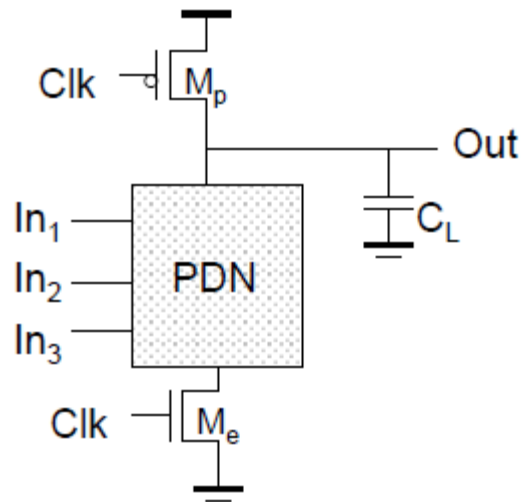

Conditions on Output

- ❑ Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- ❑ Inputs to the gate can make **at most** one transition during evaluation.
- ❑ Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L


Properties of Dynamic Gates

- Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
- Full swing outputs ($V_{OL} = \text{GND}$ and $V_{OH} = V_{DD}$)
- Non-ratioed - sizing of the devices does not affect the logic levels
- Faster switching speeds
 - reduced load capacitance due to **lower input** capacitance (C_{in})
 - reduced load capacitance due to smaller output loading (C_{out})
 - no I_{sc} , so all the current provided by PDN goes into discharging C_L

Properties of Dynamic Gates

- ❑ Overall power dissipation usually **higher** than static CMOS
 - no static current path ever exists between V_{DD} and GND (including P_{sc})
 - no glitching
 - **higher transition probabilities**
 - **extra load on Clk**
- ❑ PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}
 - low noise margin (NM_L)
- ❑ Needs a precharge/evaluate clock

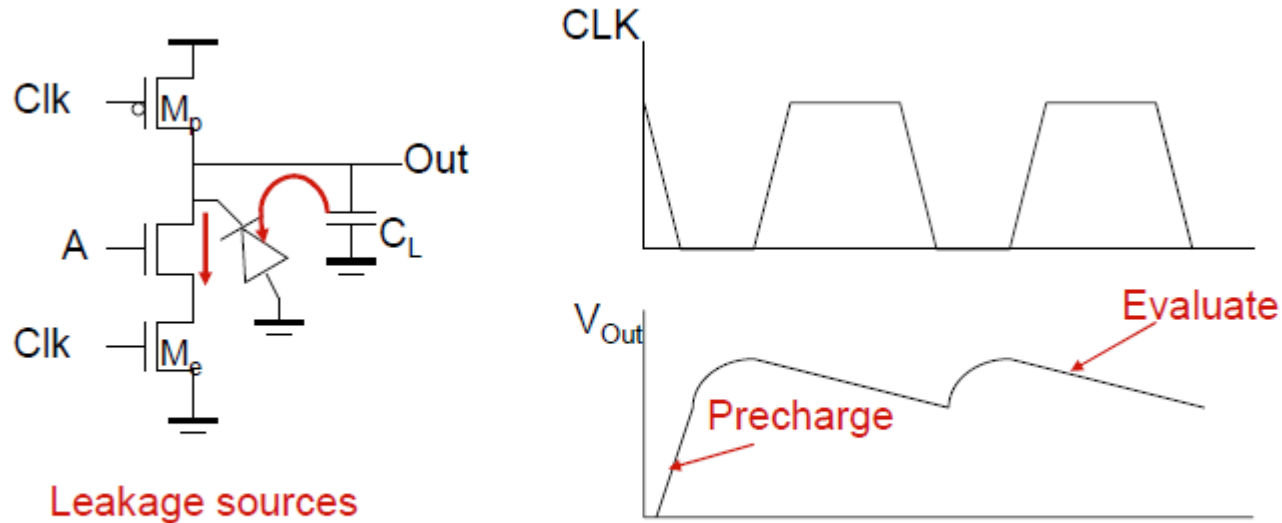
Issues in Dynamic Design 1: Charge Leakage



Leakage sources


Dominant component is subthreshold current

Solution to Charge Leakage

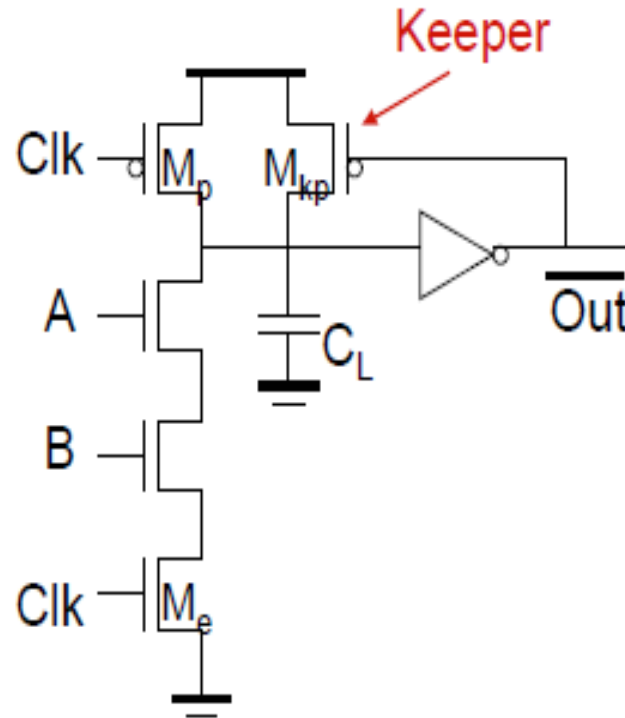


Same approach as level restorer for pass-transistor logic

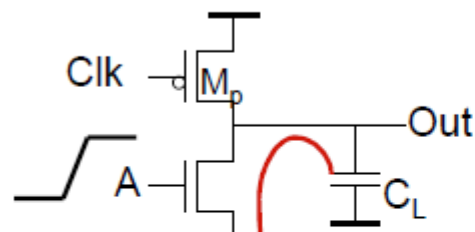
Issues in Dynamic Design 2: Charge Sharing



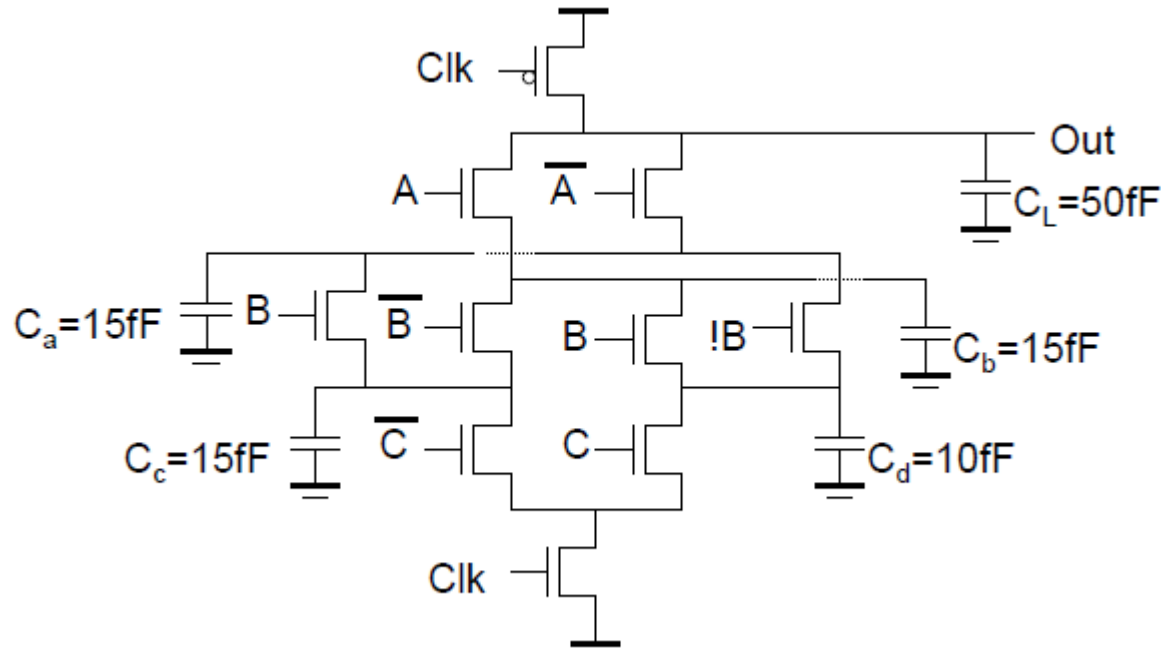
Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to reduced robustness



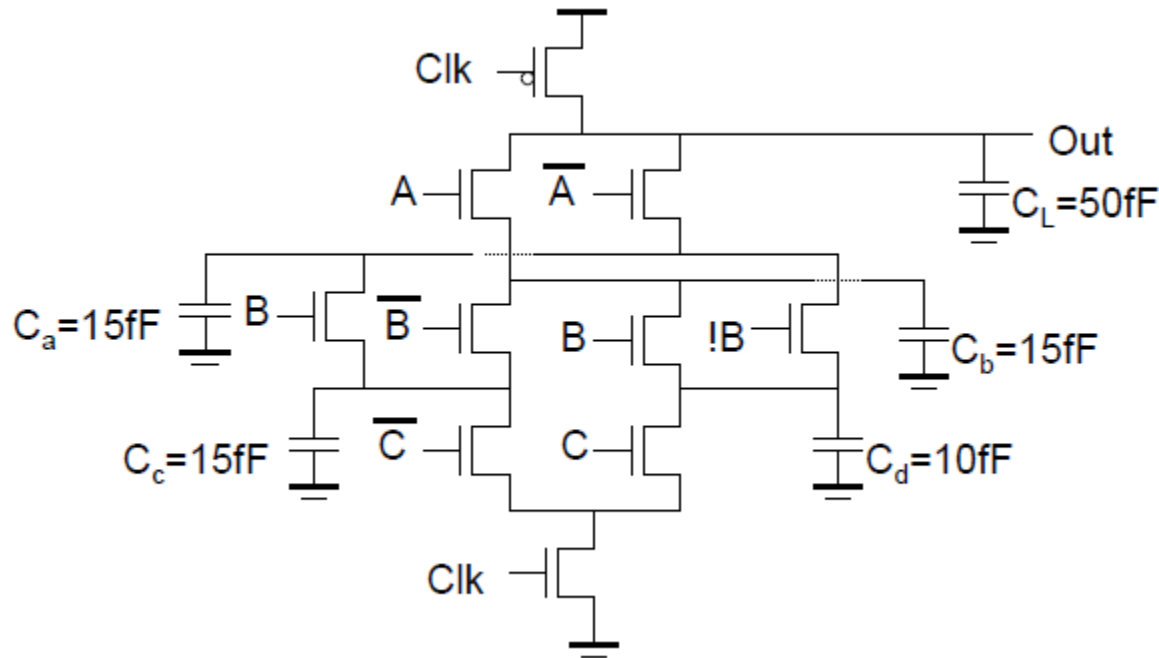Issues in Dynamic Design 2: Charge Sharing



Charge Sharing

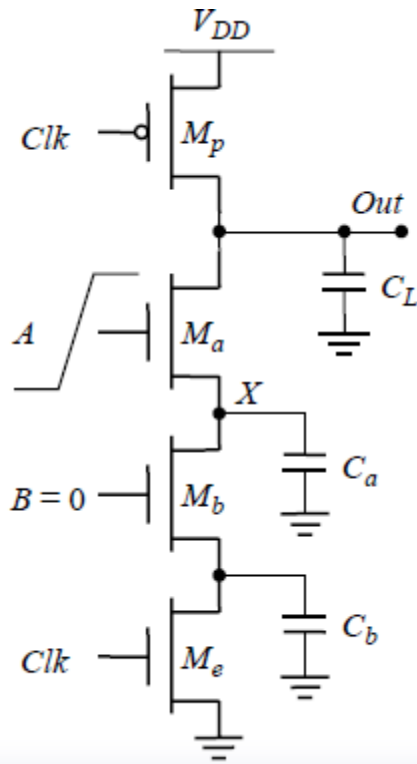

case 1) if $\Delta V_{out} < V_{Tn}$

$$C_L V_{DD} = C_L V_{out}(t) + C_a (V_{DD} - V_{Tn}(V_X))$$

or


$$\Delta V_{out} = V_{out}(t) - V_{DD} = -\frac{C_a}{C_L} (V_{DD} - V_{Tn}(V_X))$$

case 2) if $\Delta V_{out} > V_{Tn}$

$$\Delta V_{out} = -V_{DD} \left(\frac{C_a}{C_a + C_L} \right)$$

Solution to Charge Redistribution

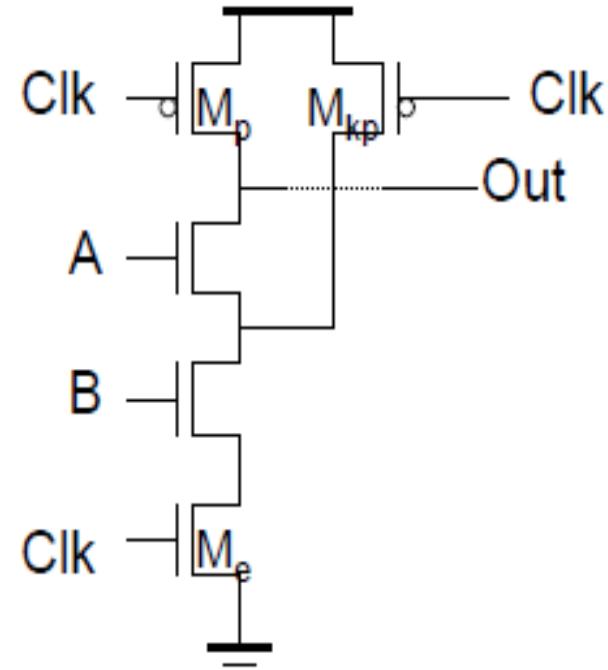Precharge internal nodes using a clock-driven transistor
(at the cost of increased area and power)





Sequential logic gates; Latches and Flip-Flops

- Basics of sequentials
- Latch and flop details
- Flop based design
- Other types of sequentials
- Understanding the power implications of flops


Sequential Gates



- Several Uses
 - Used to store state of the machine (Like a register)
 - Used in finite state machine to represent different states of the machine
 - Also used in pipelined machine to designate pipestages
- Always accept clock as an input to synchronize pipestages
- Types:
 - Latch (Phase 1/Phase 2)
 - Flip-flop (Rising/Falling edge)
- Flavors
 - Enabled
 - Synchronous Set/Reset
 - Asynchronous Set/Reset

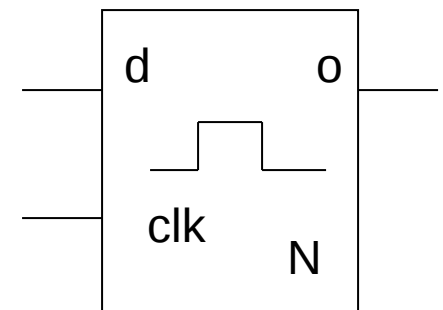
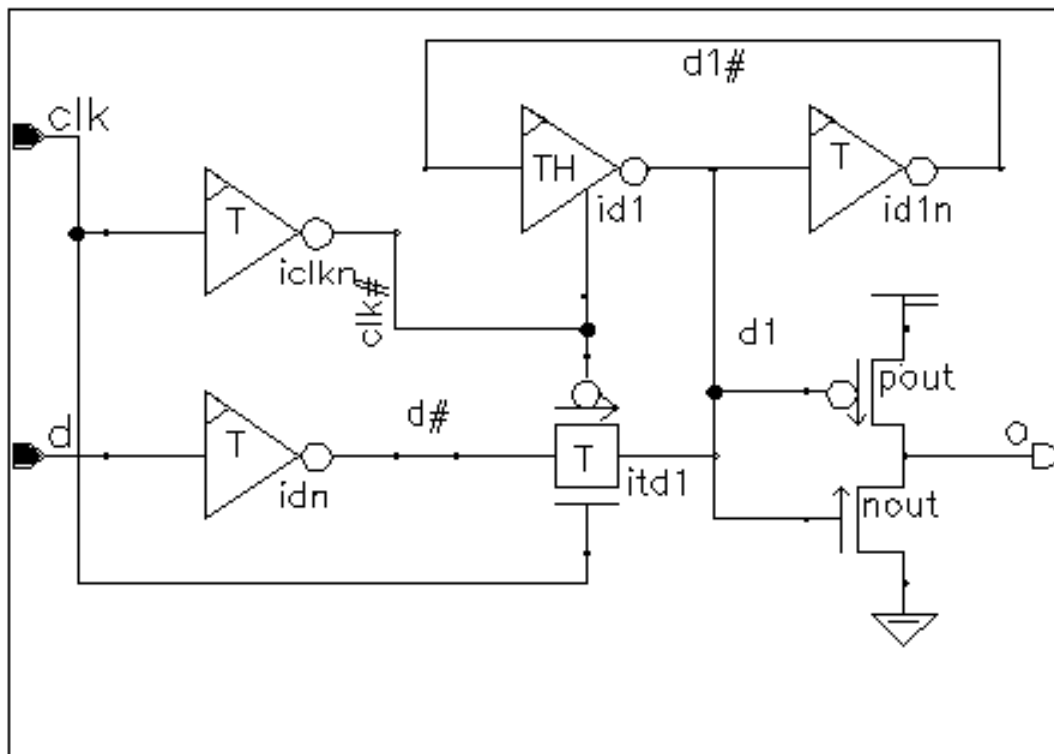


Traditional N-Latch

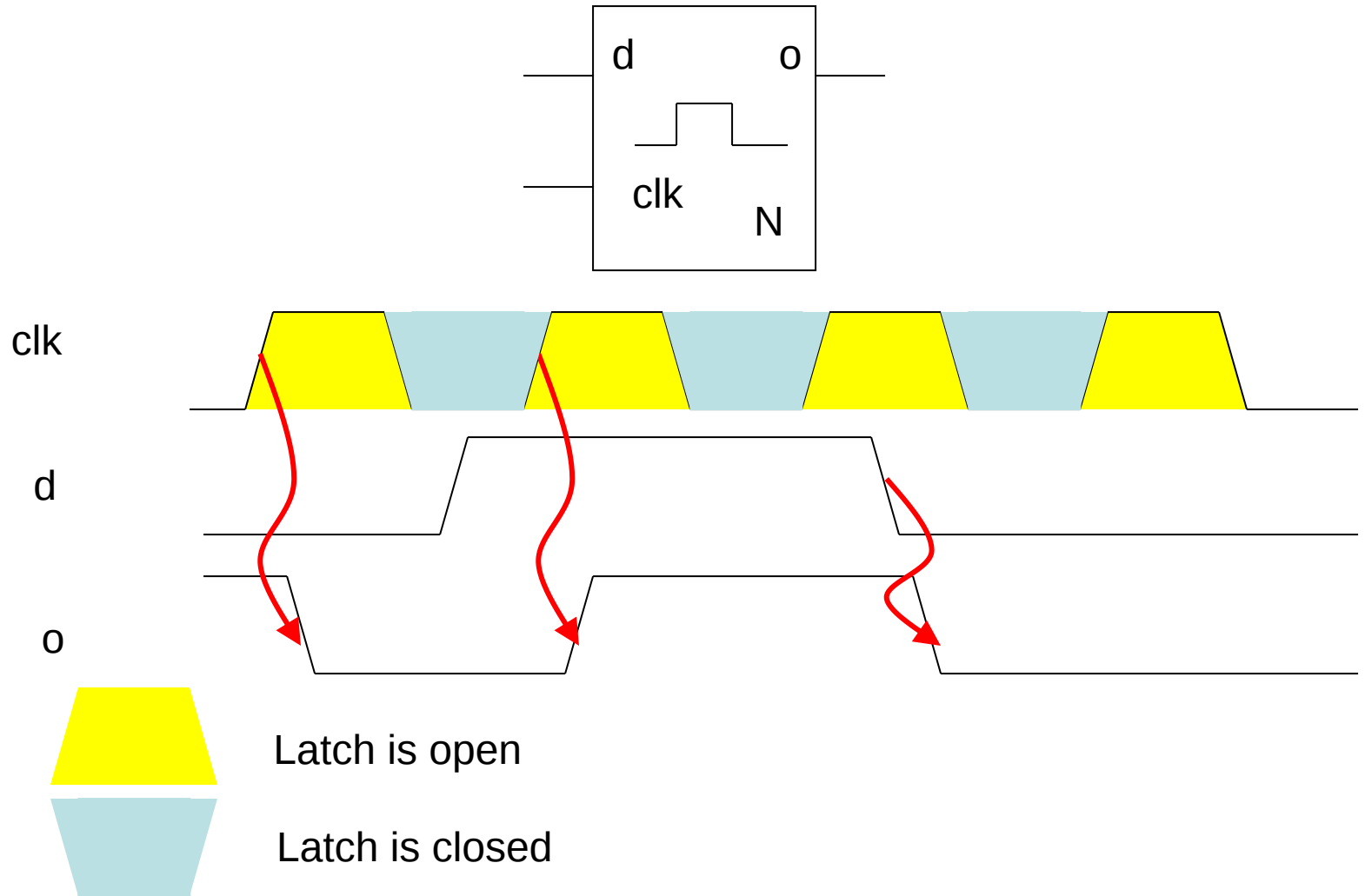


Traditional P-Latch

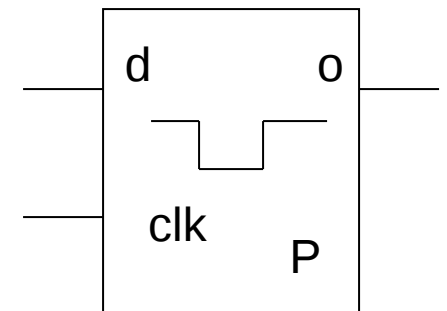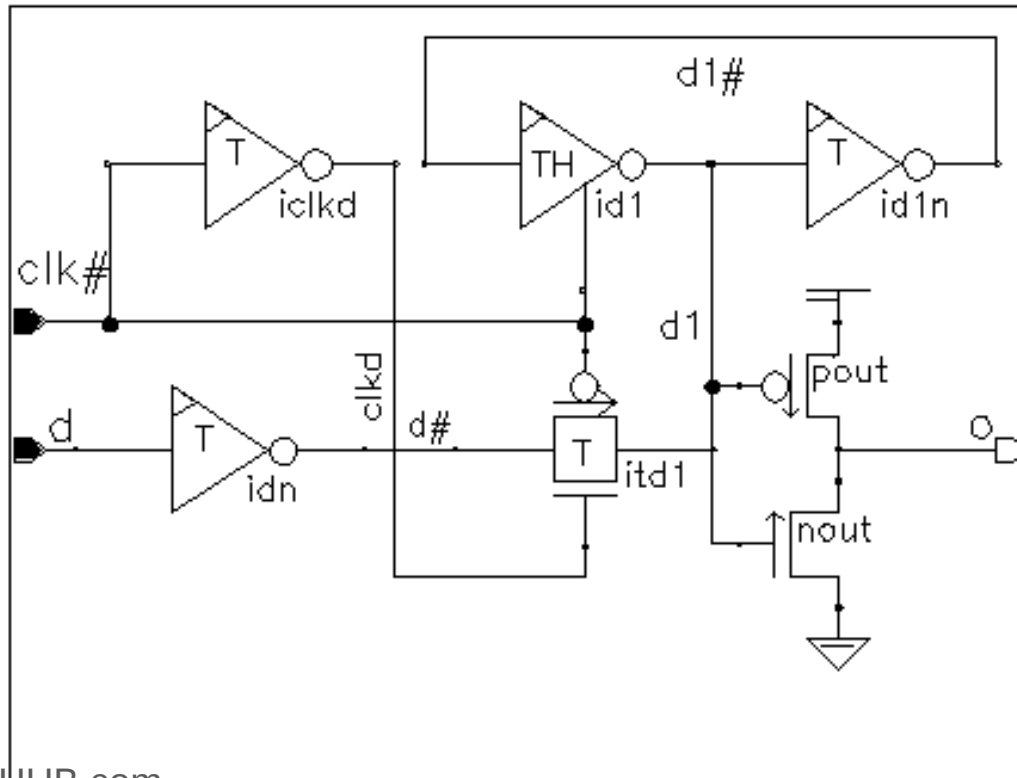- Level sensitive (Phase 2 open when clk is low)
- Also called P first or Phase 2 Latch





Traditional P-Latch

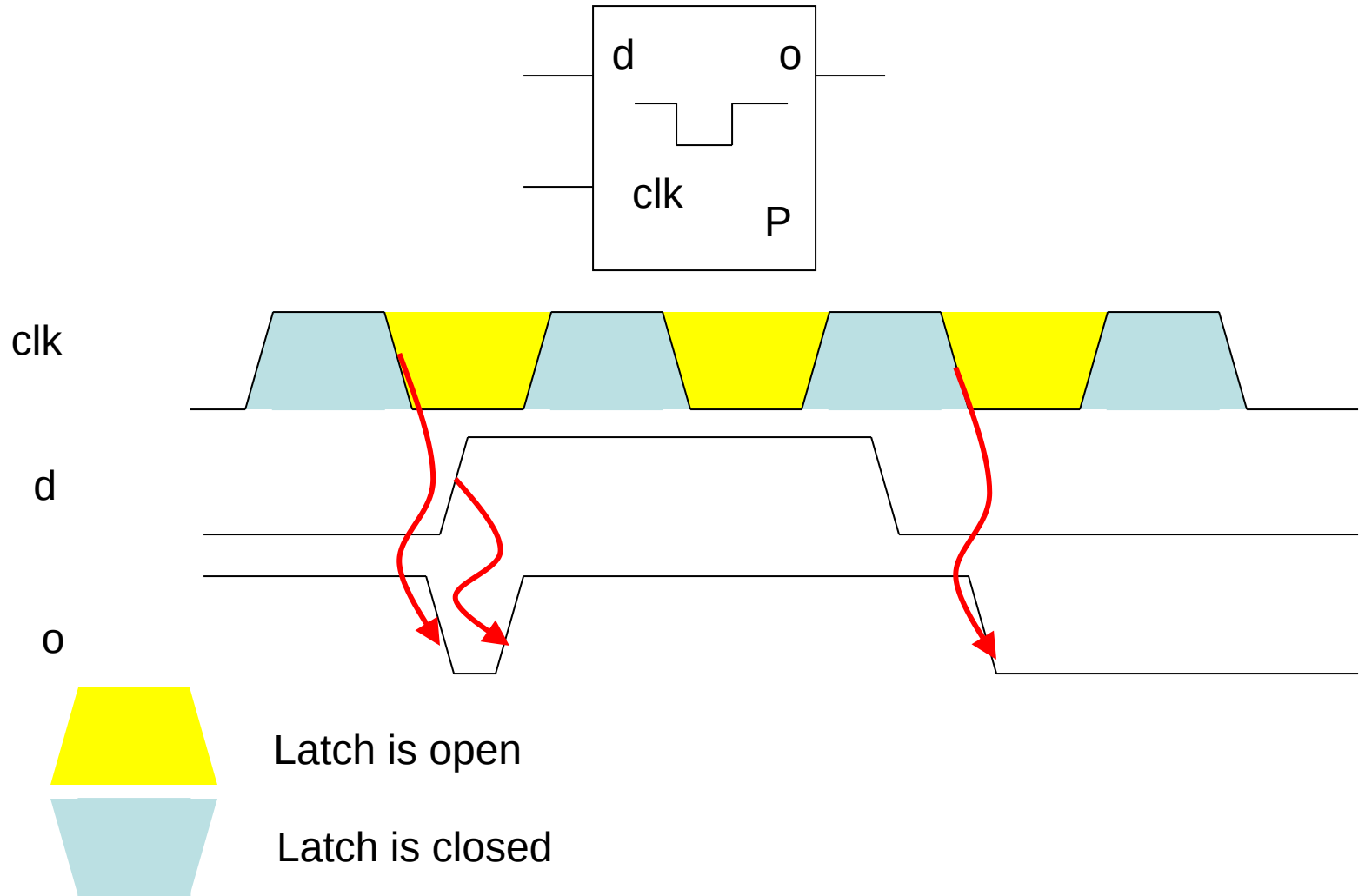


Positive Edge Flip-flop

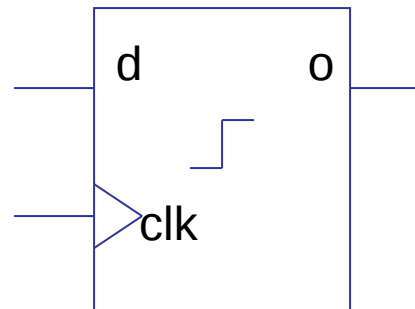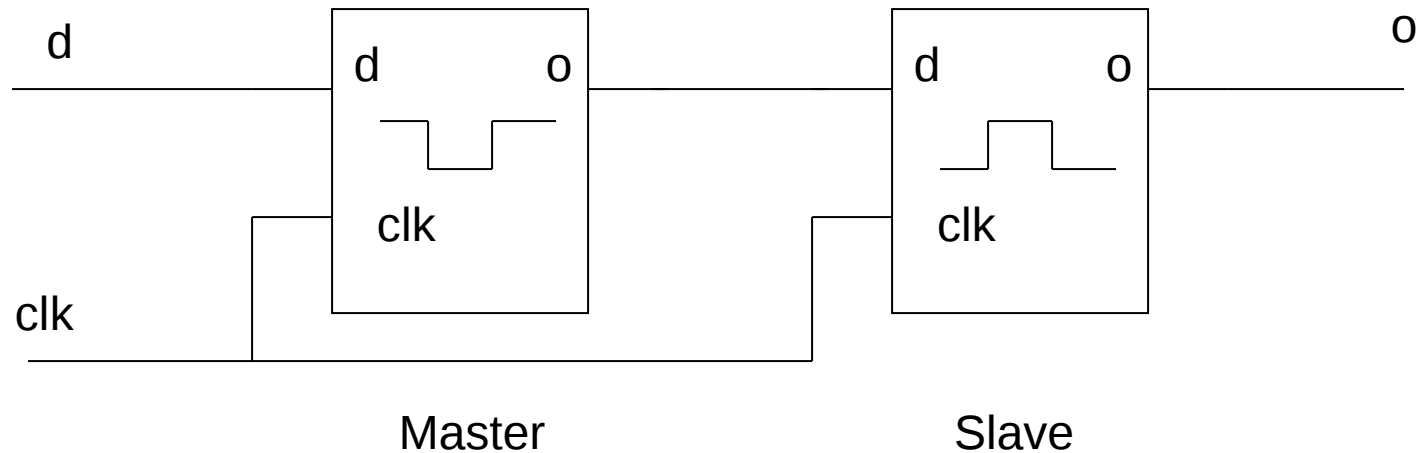- Edge sensitive
 - FF captures and drives data on rising edge of clk.
 - When clk rises, P latch shuts off, N latch turns on





Positive Edge Flip-flop

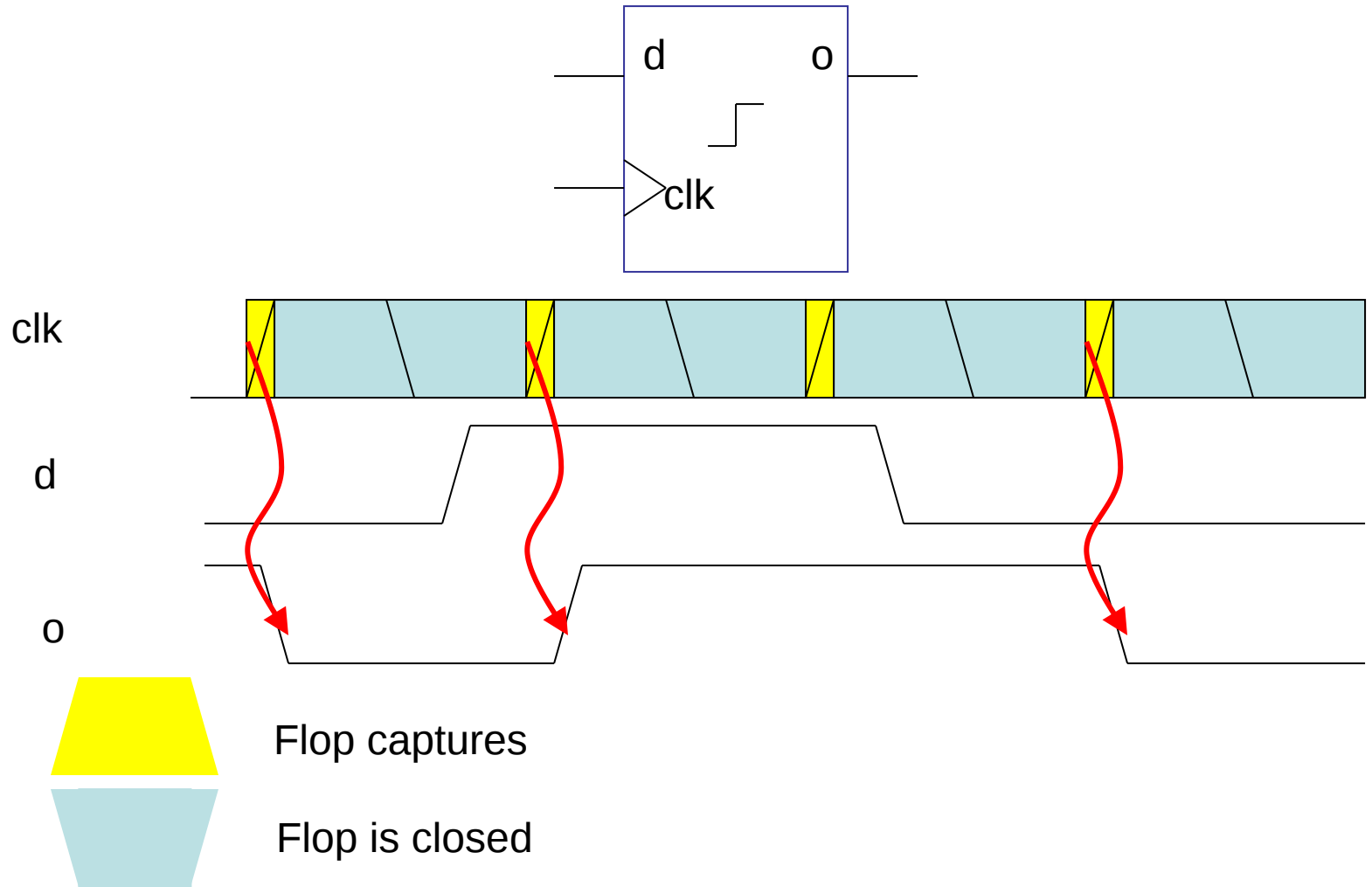


Negative Edge Flip-flop

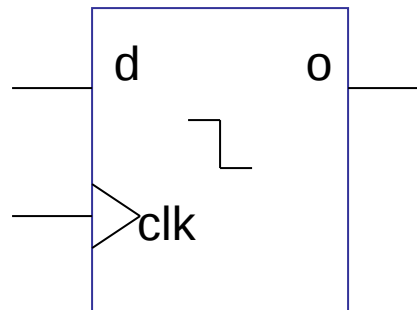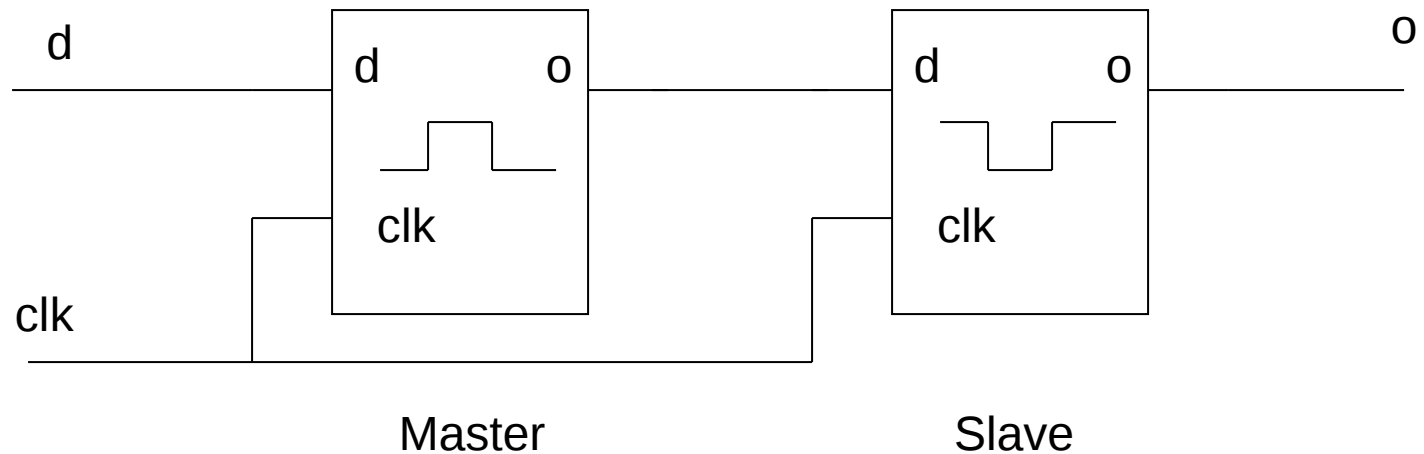- Edge sensitive (FF captures and drives data on falling edge of clk)




Latch parameters

- Setup time
 - Time, before the latch closes, that the data must arrive to guarantee the data is captured correctly after the latch closes
- Hold time
 - Time, after the latch closes, that the data can not switch to guarantee the data is captured correctly when the latch closes
- Clk to out delay
 - Delay from clk to out when the data is setup before the clk
- Data to out delay
 - Delay from data to out when the data arrives after the clk

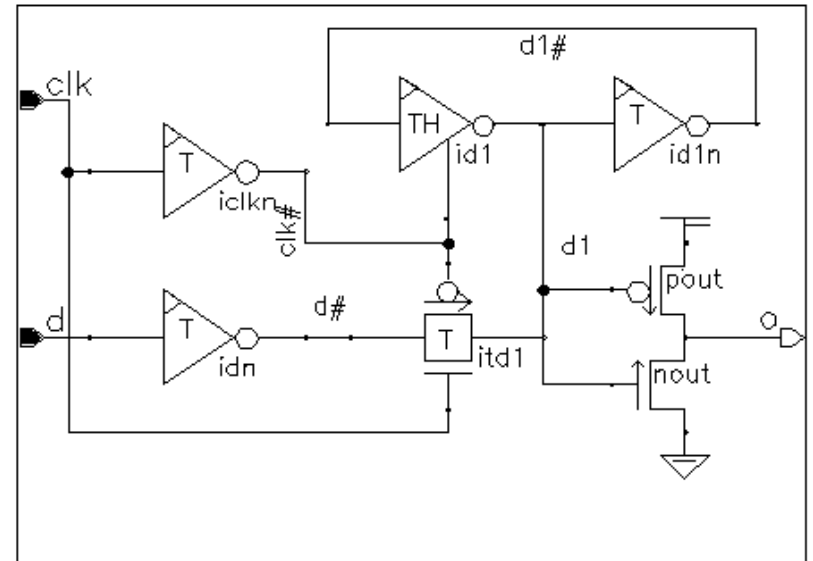

Traditional N-Latch

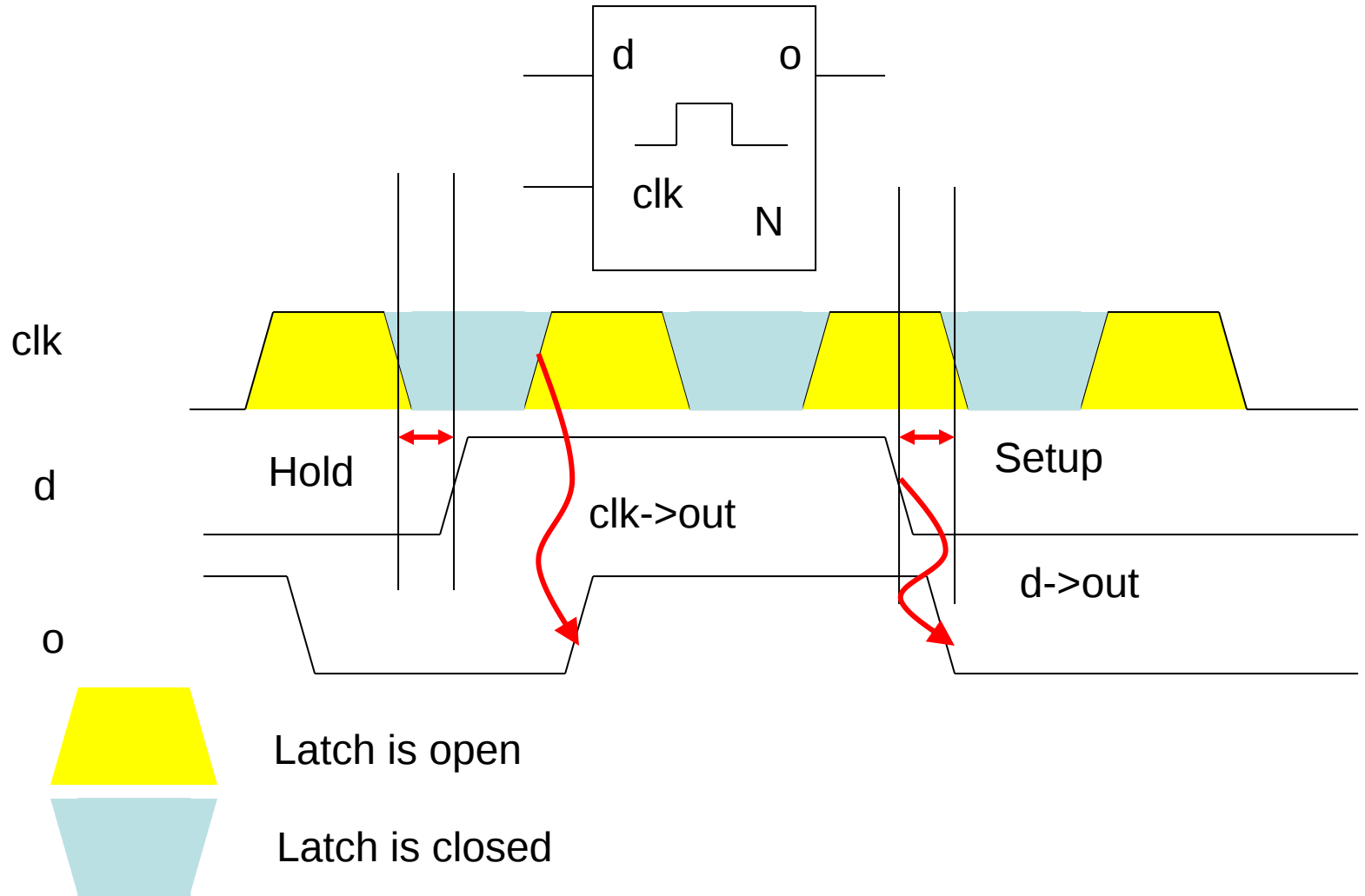


Flip-flop parameters

- Setup time
 - Time, before the opening clk edge, that the data must arrive to guarantee the data is captured correctly
- Hold time
 - Time, after the clk edge, that the data can not switch to guarantee the data is captured correctly
- Clk to out delay
 - Delay from clk to out when the data is setup before the clk.
- Note that there is no data to out delay since flops must have data setup to the edge.



Full keeper

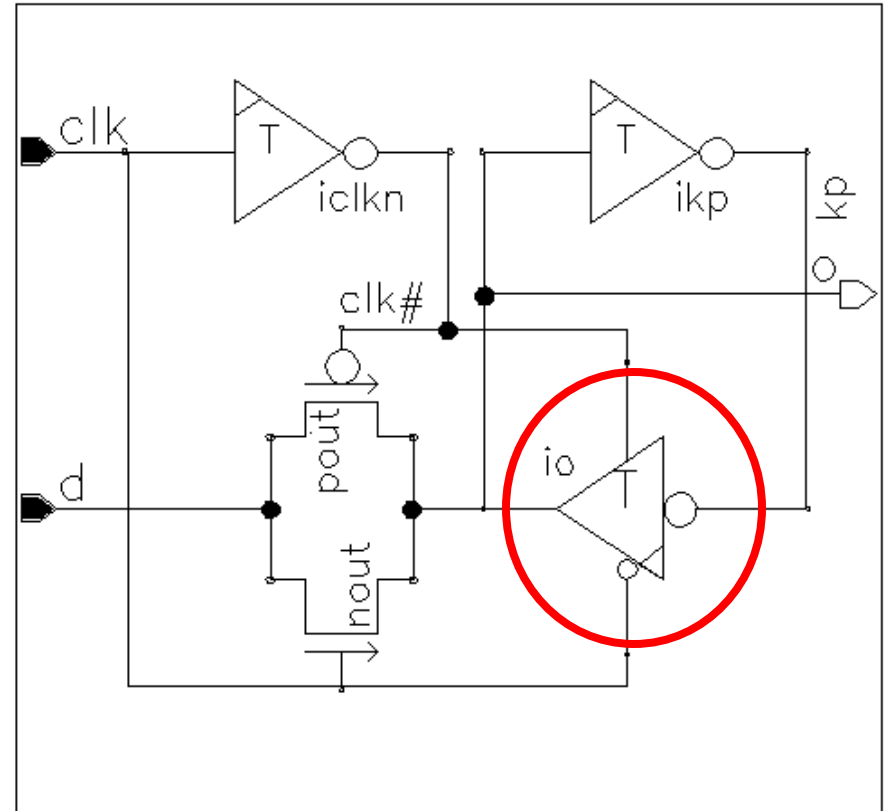- Feedback device has tristated both N and P.
- Writing of output through passgate has no opposition




Pipelining Sequence

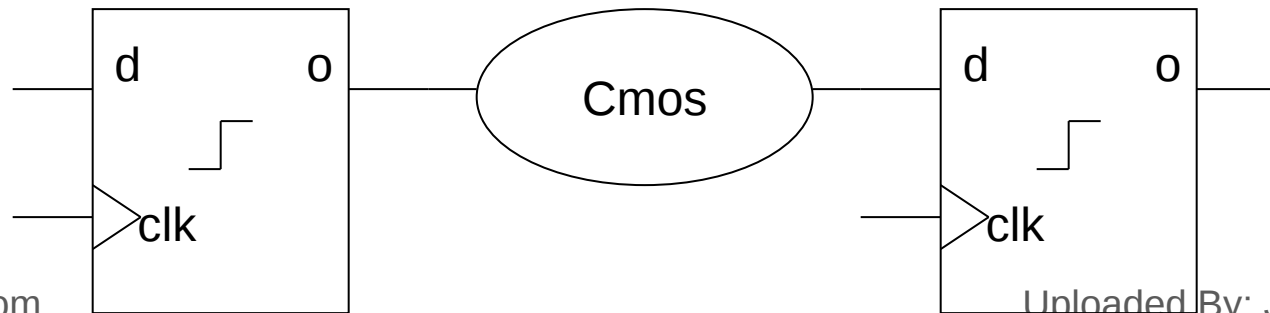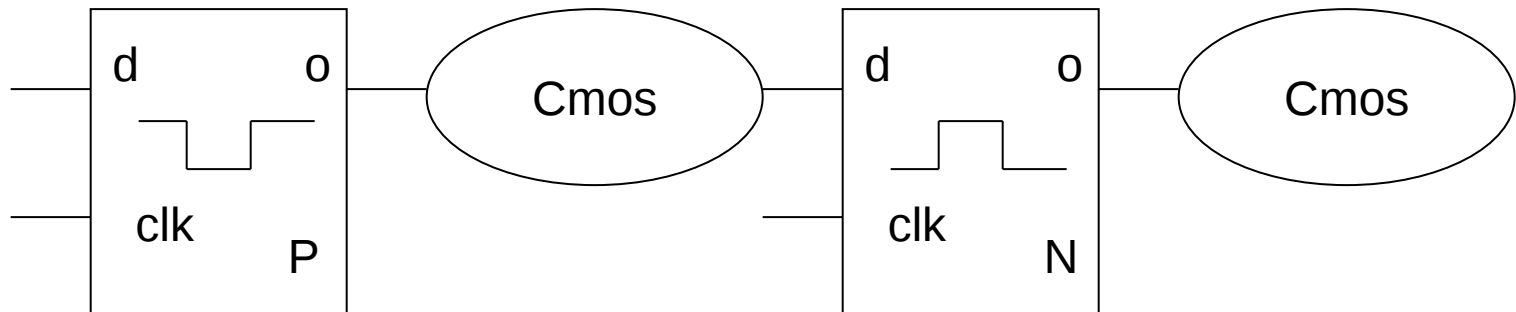- For proper pipelining, must always alternate N-latch and P-latch.
- Flops must be consecutive rising edge flops




What about Latch/Flop boundary?

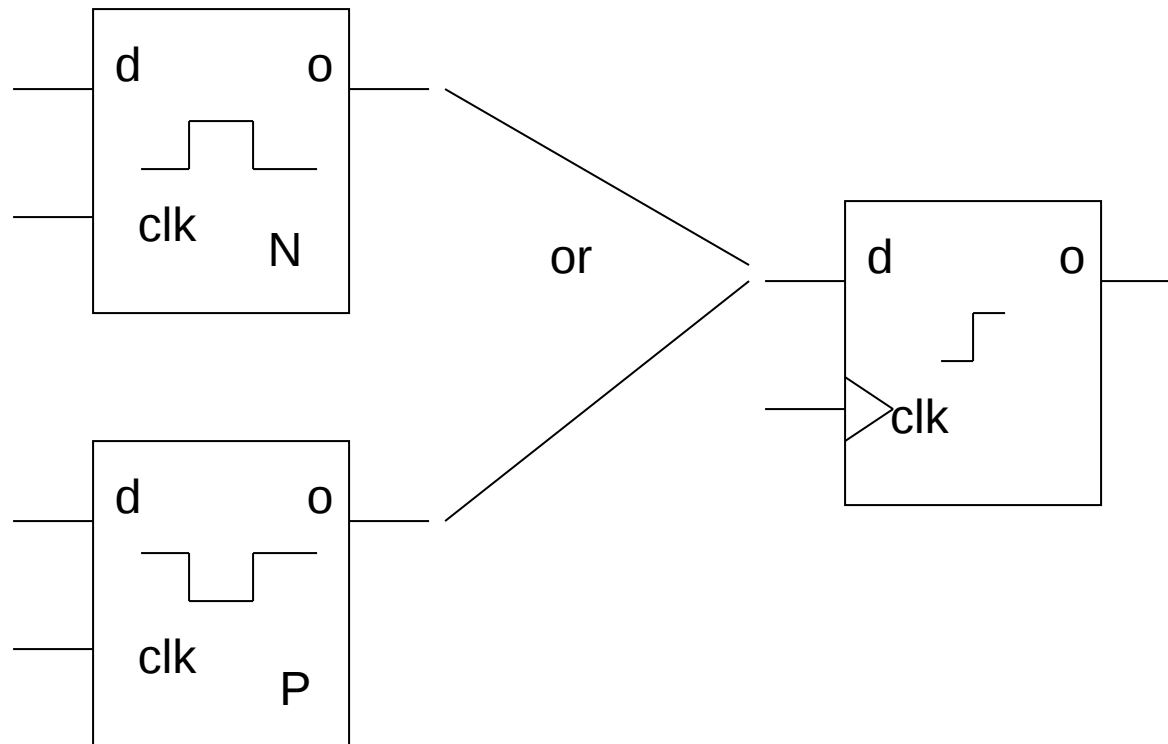- What type of latch should be in front of a rising edge flop?



What about Latch/Flop boundary?

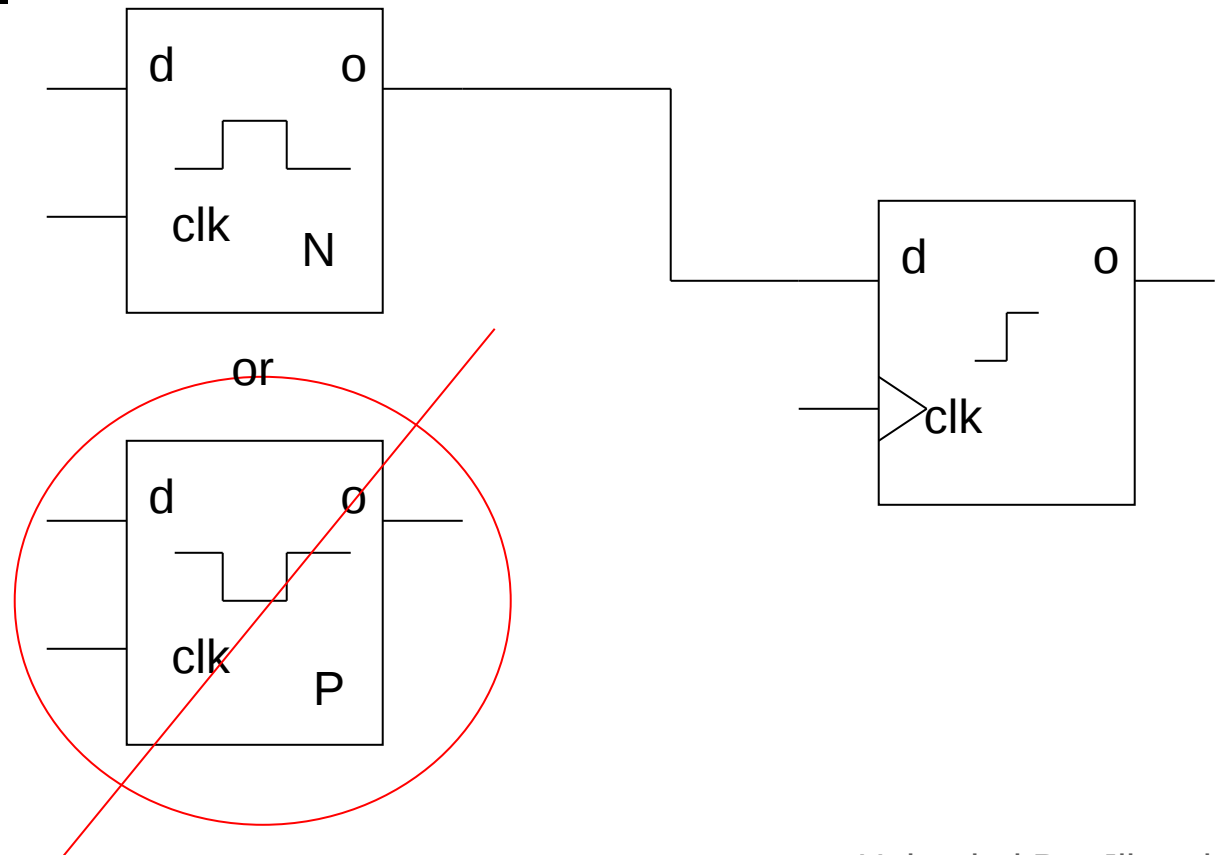- Since in a flop, the master is a P-latch, we **MUST** have a N-latch in front of a rising edge flop.




Likewise, Flop must drive to a P-latch

- On the other hand, since the slave is an n-latch, a rising edge flop must be followed by a p-latch




Flop issues

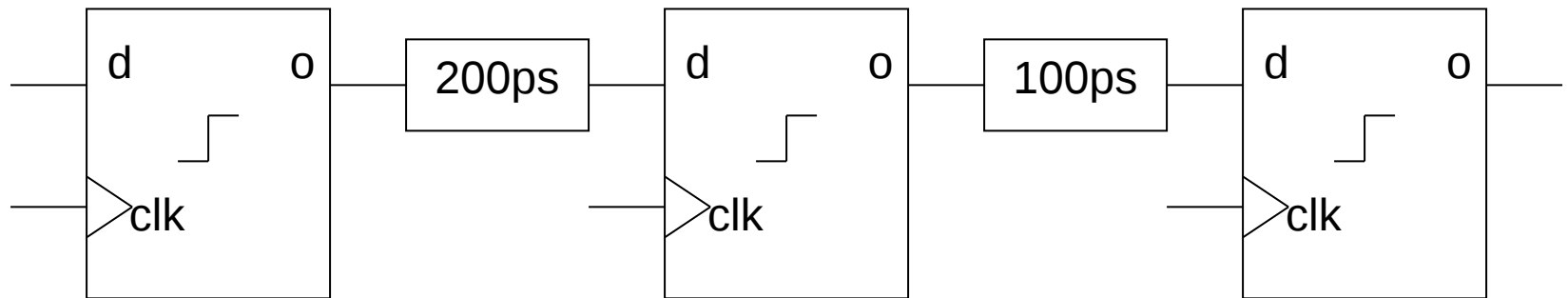- Assuming 100ps setup time, skew and clk-out delay
- How many paths are there and how many cycles?
- What is max frequency this circuit could run?




Flop Answers

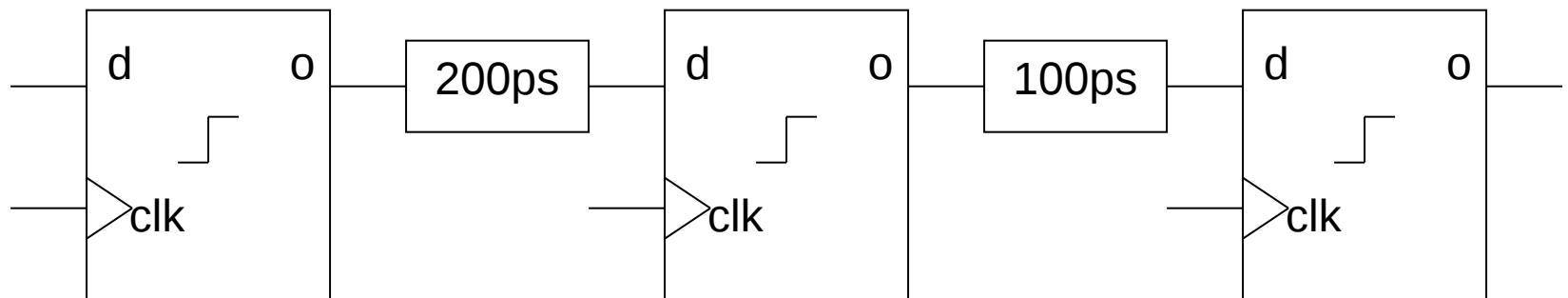- 2 paths (A->B and B->C) each 1 cycle
- $200\text{ps} + 100\text{ps} = 300\text{ps}$. $1/300\text{ps} = 3.33\text{GHz}$
- $100\text{ps} + 100\text{ps} = 200\text{ps}$. $1/200\text{ps} = 5.0\text{GHz}$
- Max frequency = 3.33GHz




Time borrowing

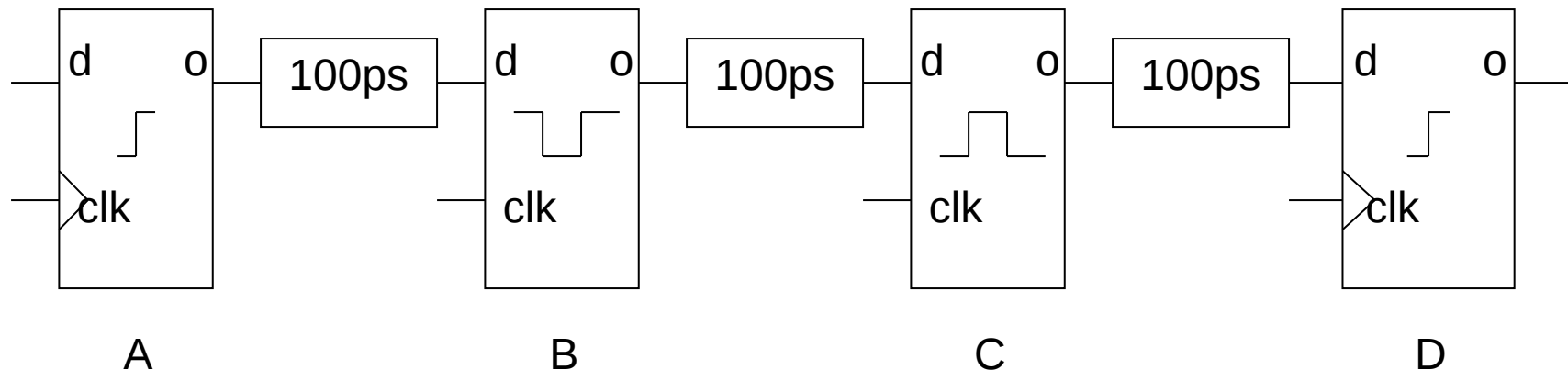- Time borrowing is a technique to increase frequency by converting flops to latches.
 - Allows amortizing skew, jitter, clk to out and data delays across more than 1 cycle
- How many paths are there and how many cycles?
- What is the new frequency assuming data-out delay is 50ps?




6 paths

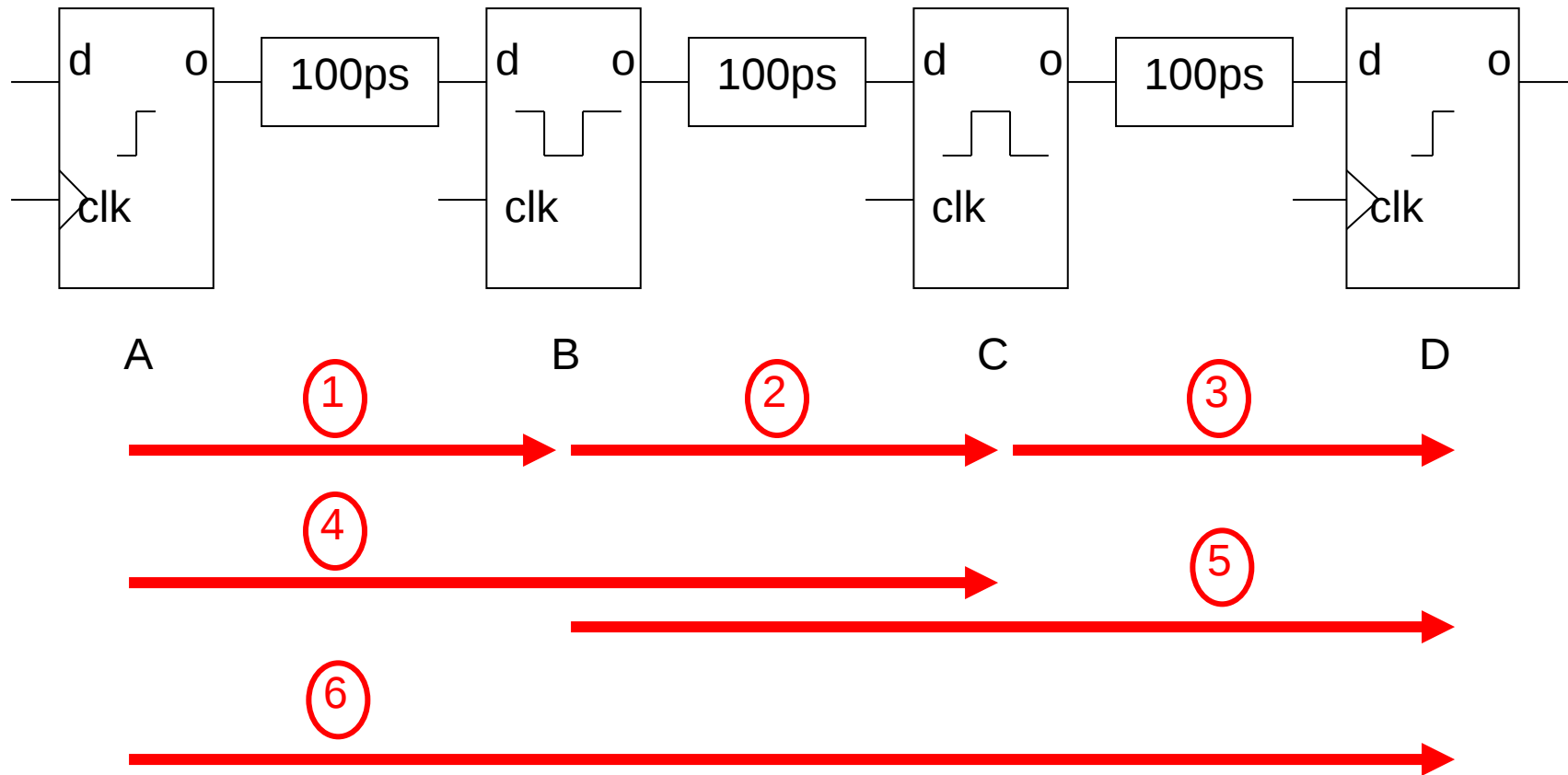- 6 paths (A-B, A-C, A-D, B-C, B-D, C-D).




6 paths

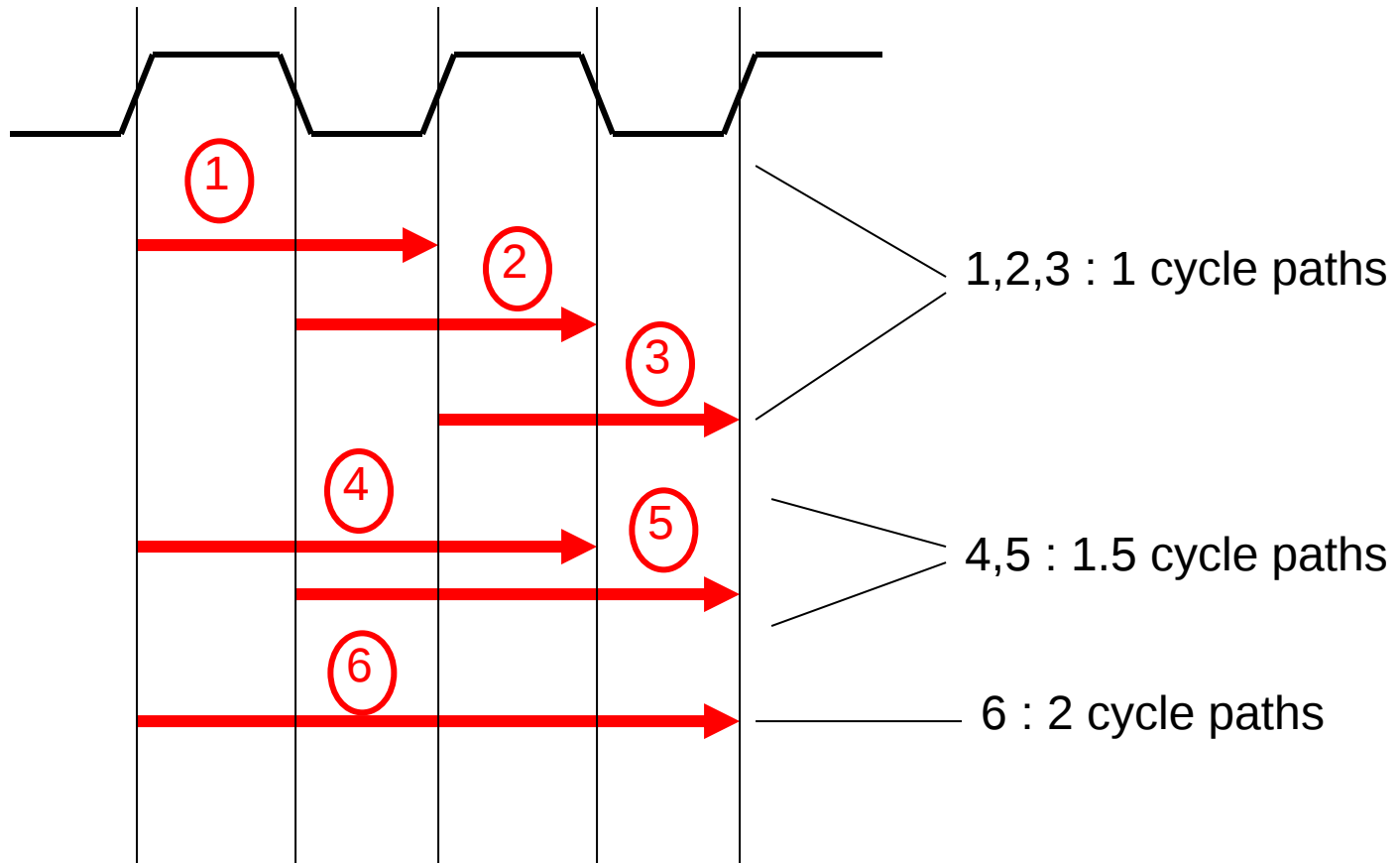- 6 paths (A-B, A-C, A-D, B-C, B-D, C-D).




Time borrowing Frequency calculations

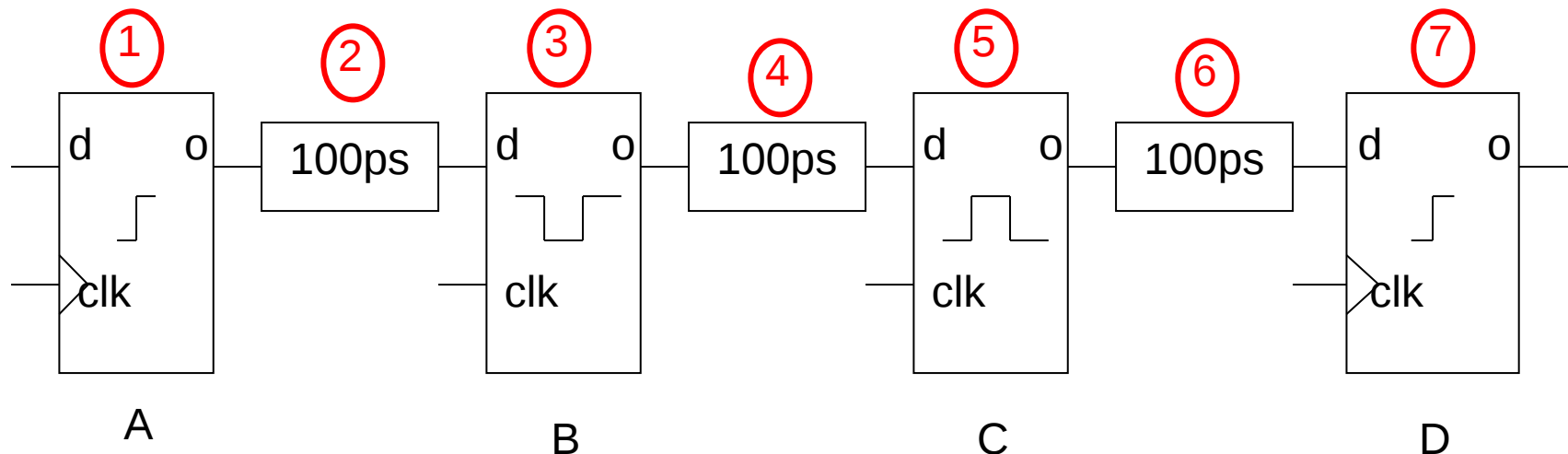- 2 paths -> 6 paths (A-B, A-C, A-D, B-C, B-D, C-D).
- A-B, B-C, C-D: 1 cycle path ($100\text{ps} + 100\text{ps}$) = 200ps = 5GHz
- A-C, B-D: 1.5 cycle path ($100 + 50 + 100 + 100$) = 350ps :
 $1.5/350\text{ps} = 4.28\text{GHz}$
- A-D: 2 cycle path ($100 + 50 + 100 + 50 + 100 + 100$) = 500ps :
 $2/500\text{ps} = 4\text{GHz}$
- New frequency = 4GHz



A-D path explained

- Assume 50ps clk-out and 50ps setup

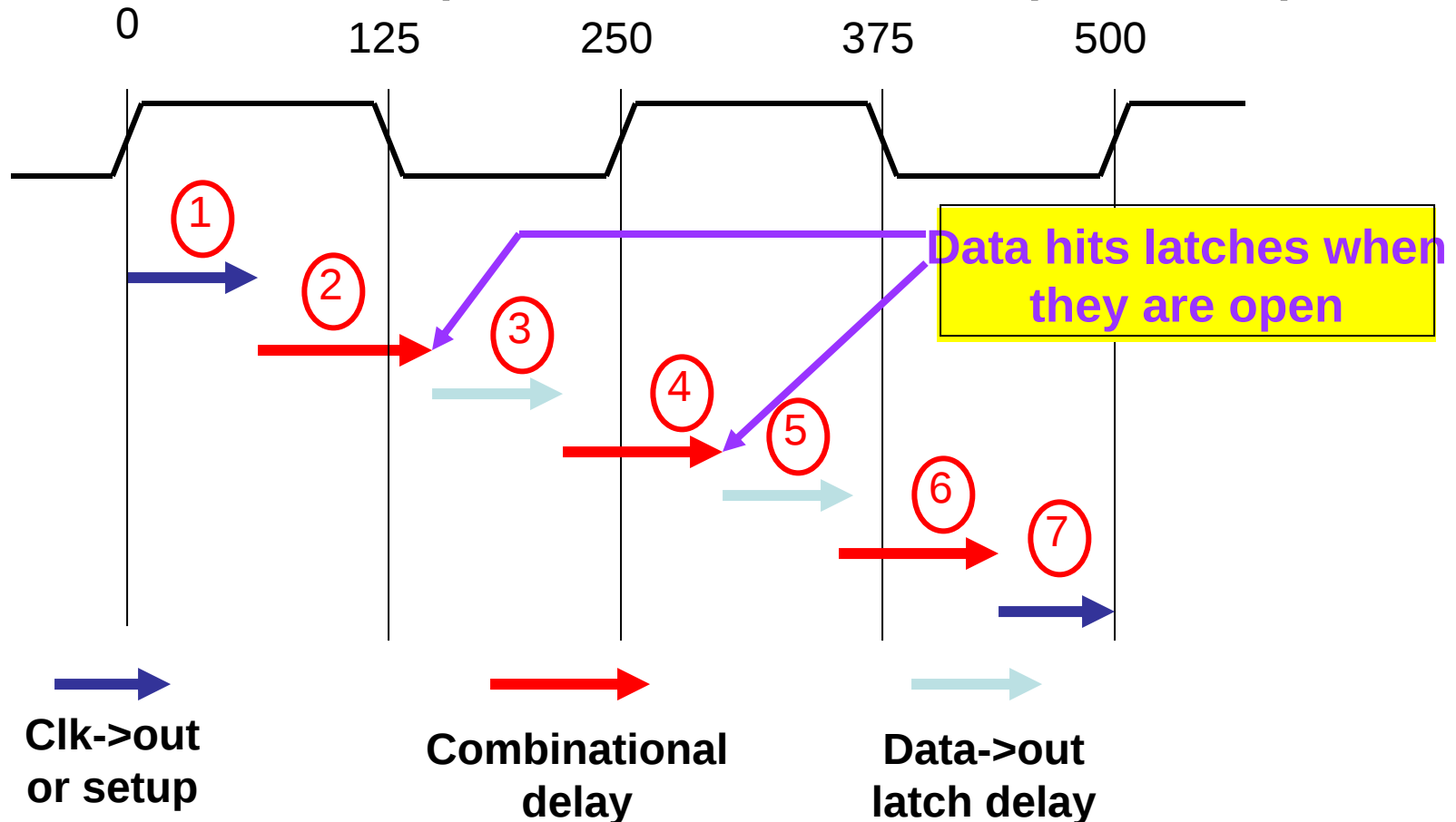

When/Why time borrowing works

- 2 advantages of time borrowing
 - Allows “borrowing” time from a cycle that has extra margin to a cycle that doesn’t
 - In our example, the cycle that ran at 3.33GHz borrows time from the cycle that had 5GHz
 - Allows amortization of setup time and skew over several cycles
 - In our example, the 100ps overhead penalty is now over 2 cycles so the per cycle penalty is 50ps


Time borrowing

- Positives:
 - Allows some amount of time borrowing without some of the negative of time borrowing
 - Very little extra clock load
 - No latch explosion
 - No RTL change
- Negatives:
 - Only allows only a buffer delay of borrowing
 - Min delay of the first path has been worsened by 1 buffer delay.

Skew has increased


Enabled latches

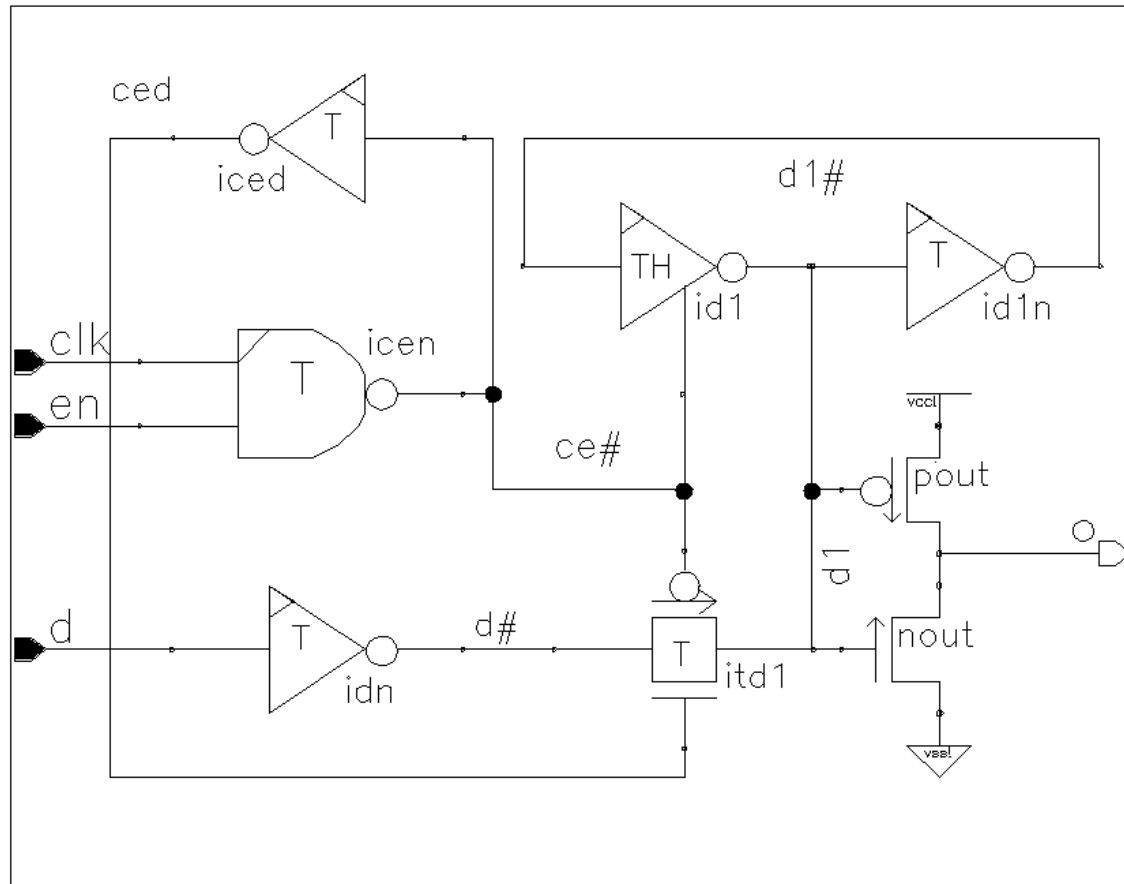- When enable is a 0, latch does keeps passgate closed




Synchronous Set latches

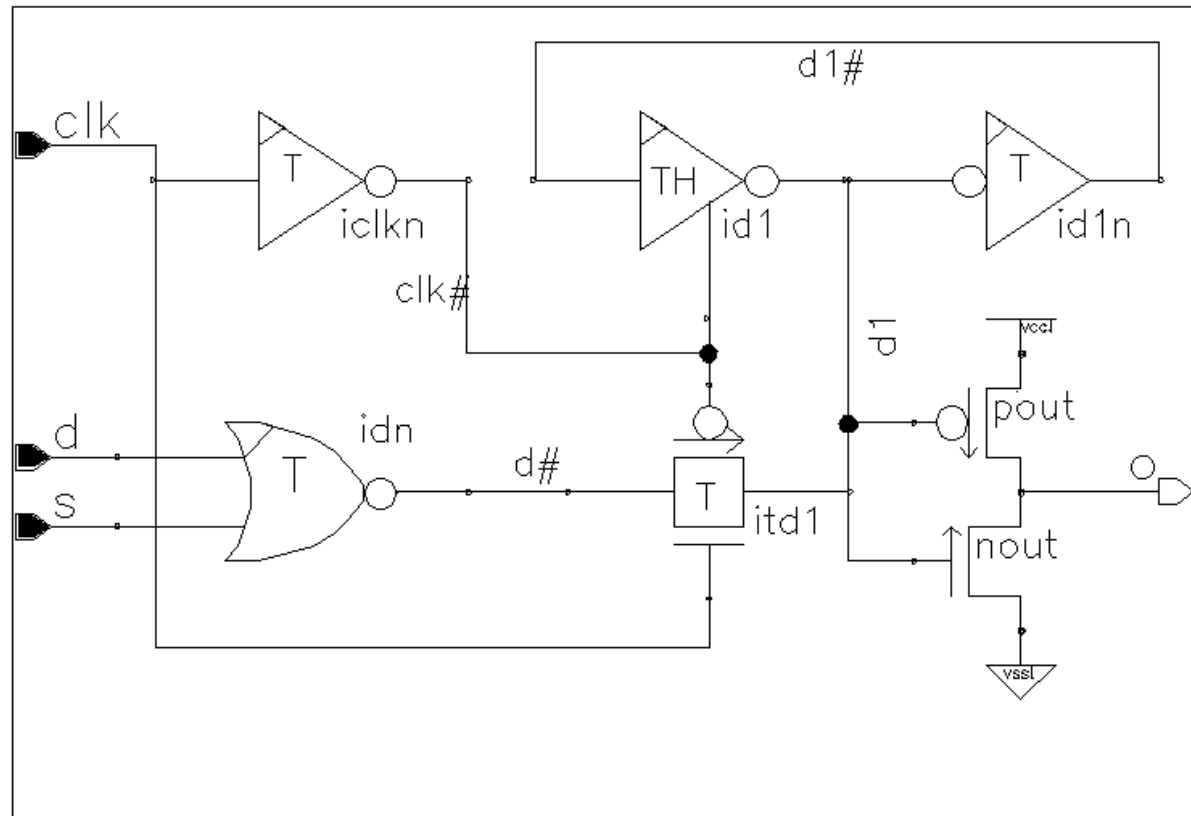- When set is a 1, when clk is open, latch stores a 1




Synchronous Reset latches

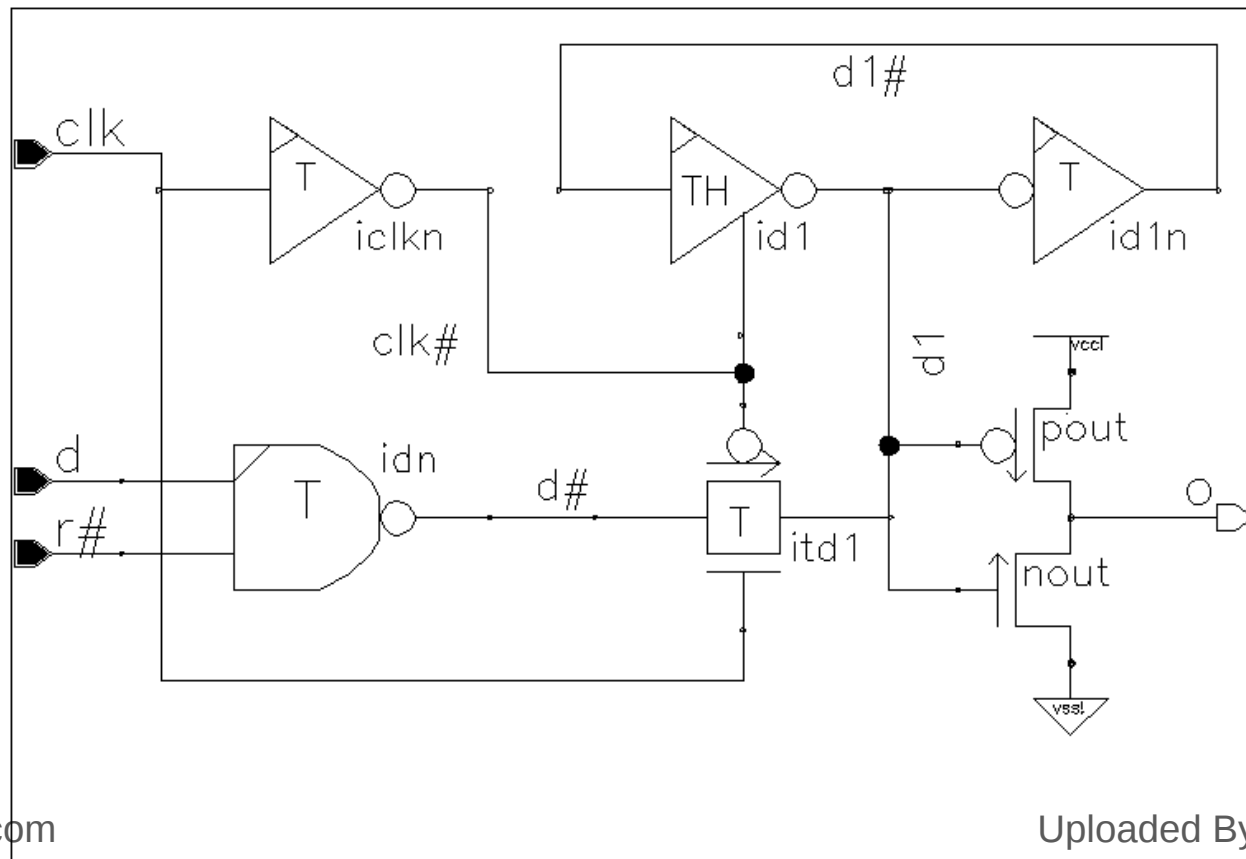- When $r\#$ is a 0, when clk is open, latch stores a 0




Asynchronous Set Flops

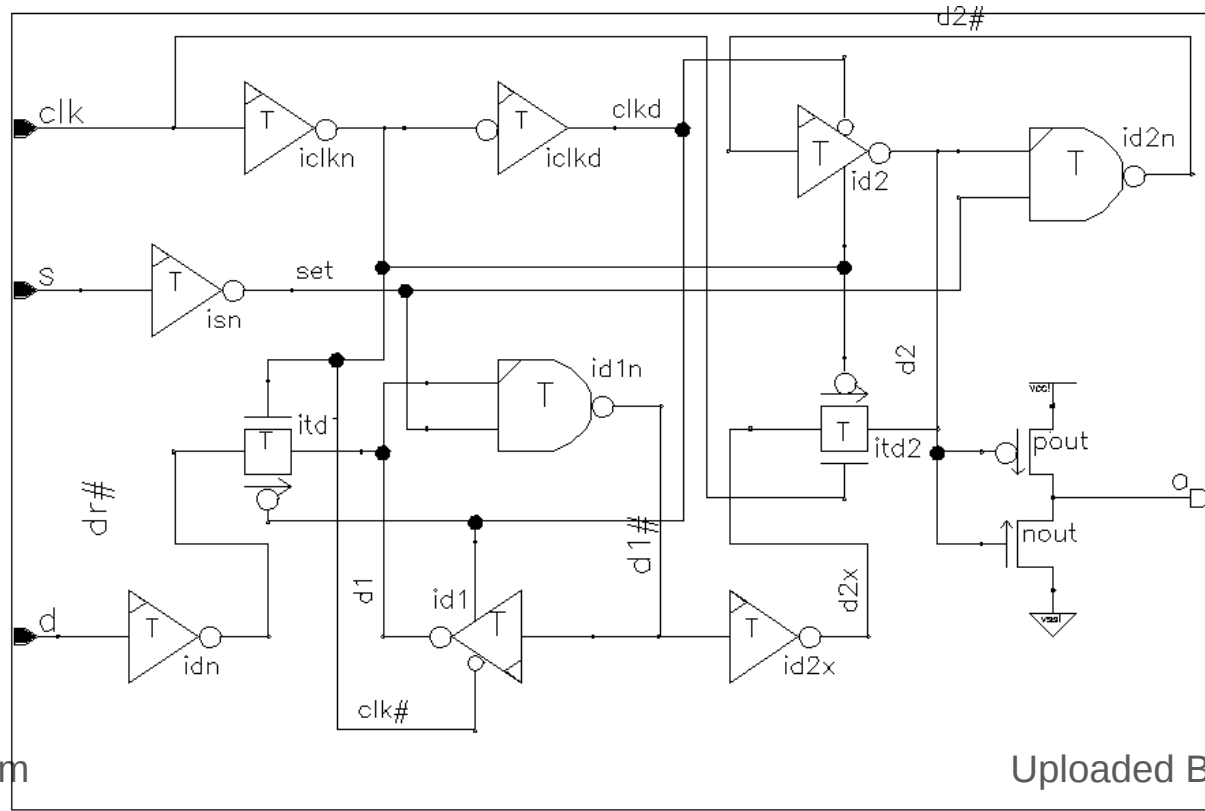- When set is a 1, output immediately changes to a 1
- Does not wait for rising edge of a clock




Mux latches

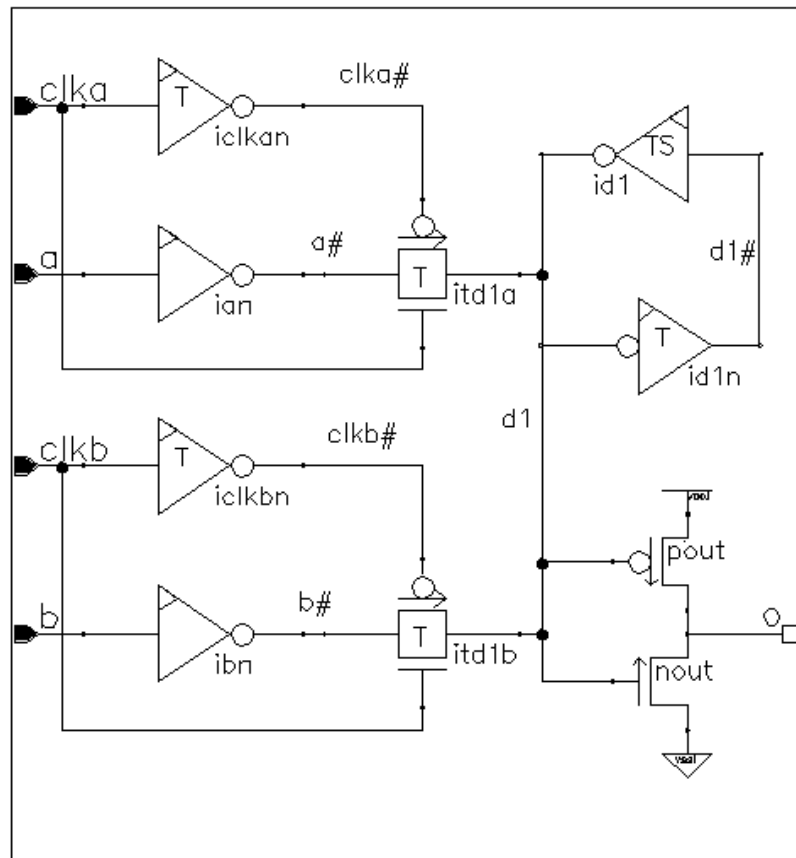- Note selects are muxed qualified clocks




Unprotected latches

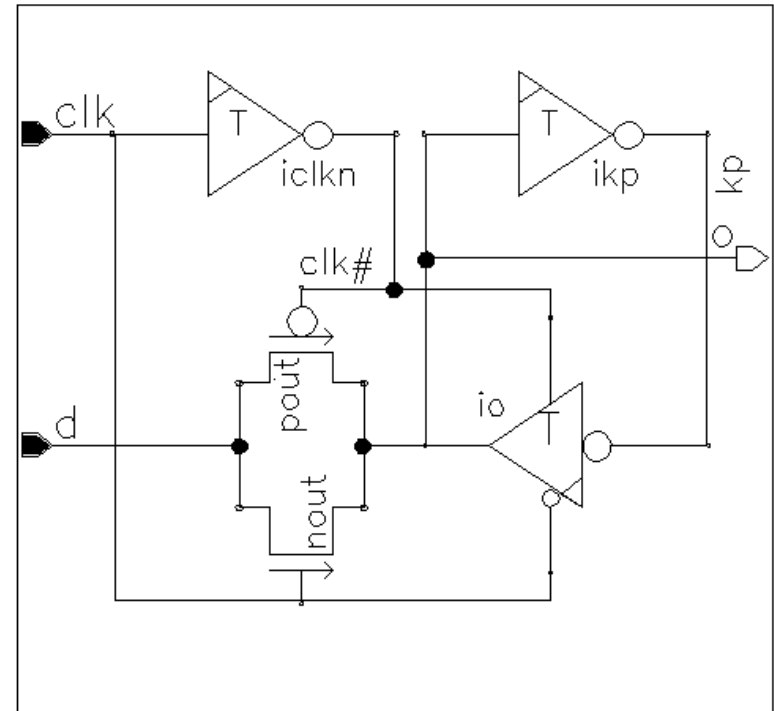- Either no input protection, output protection or both
- Allows converting the inverter to logic gates or customize the inverters normally in a latch
- Loss of output protection require extra caution not to disturb latch node
- To guarantee latch writability, should use a full keeper




Using the Enabled/Set/Reset sequentials

- Problem: How can we improve this?

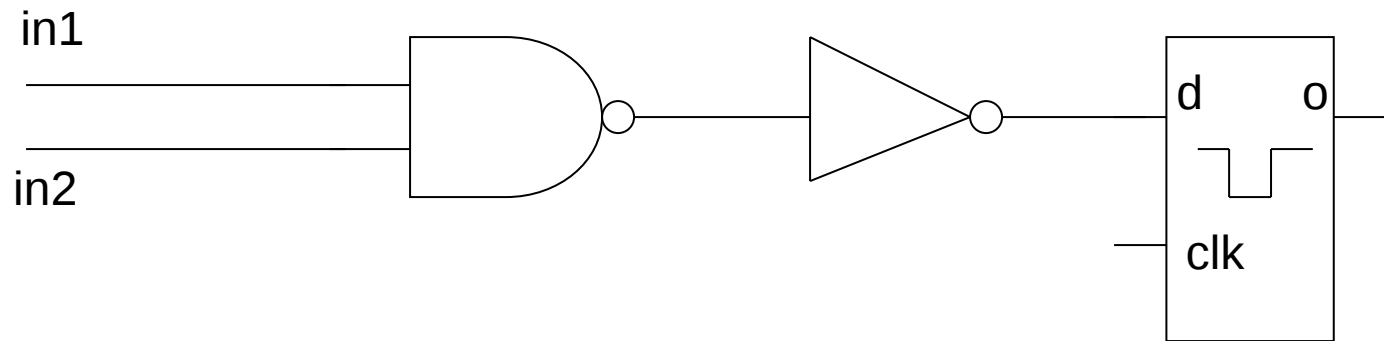


Use a Reset Latch to reduce logic

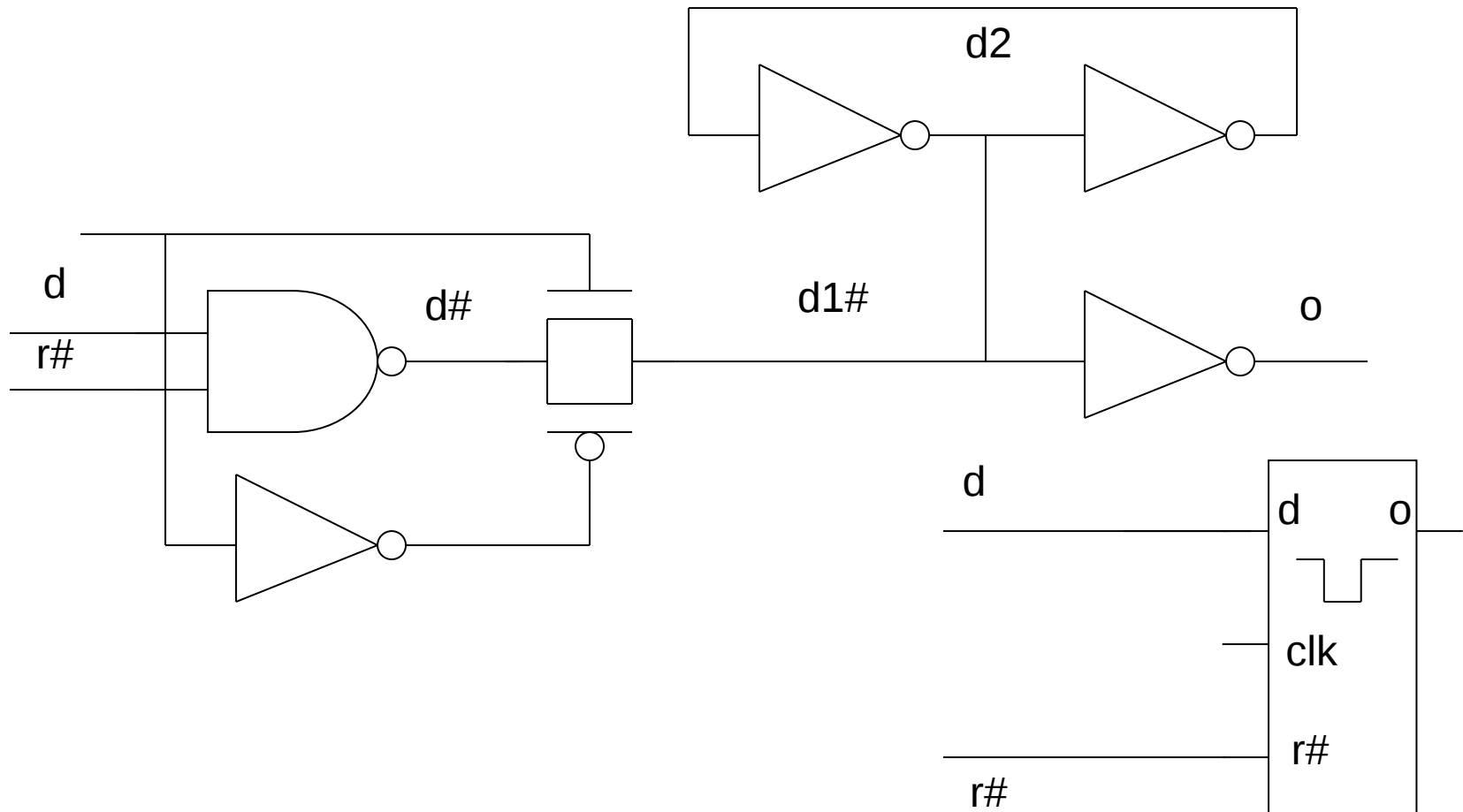- Converts the first inverter in a latch to a nand gate to eliminate 2 gates



Power issues

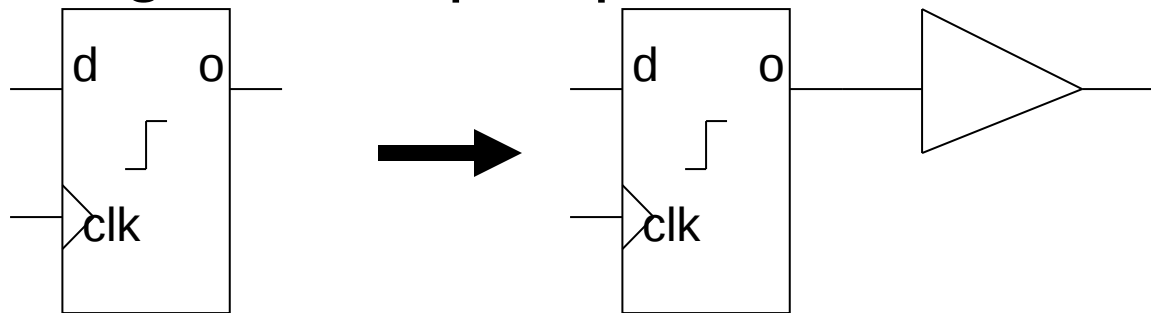
- Sequentials mean clock power!
 - Keep sequentials as small as possible by buffering outputs when timing allows to keep the sizing of the flip-flop small.



- Avoid duplicating/unnecessary flops (Look for opportunities for flop reduction)

Power issues




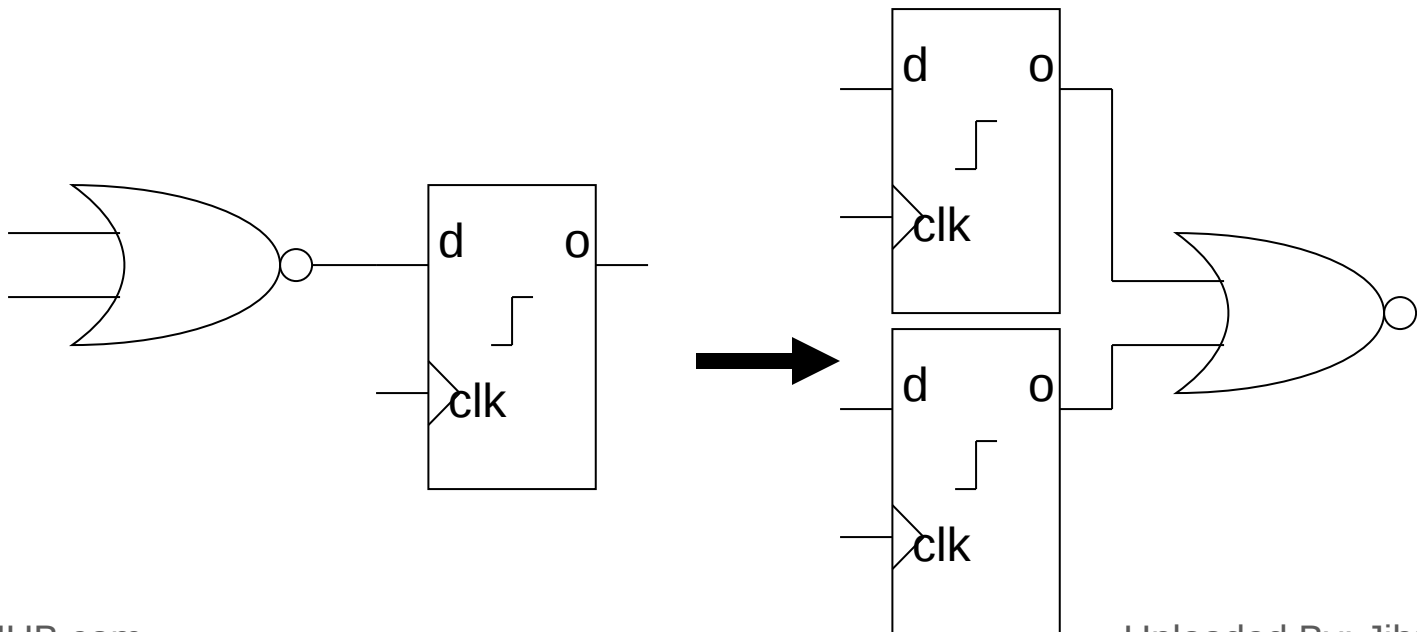
- Be careful where to select flops
 - When fixing speed paths by moving logic from 1 stage to another, watch for flop explosion
 - Same issue with flop->latch conversion



Summary


- Know the different types of sequential and the order they need to be used.
- Understanding time borrowing can help solve speed paths in a path at the expense of complexity, clock power
 - Select flop to latch conversion or time borrowing flop where appropriate
- ALWAYS think about power. Keep sequential count as low as possible and keep sequential sizes small by buffering outputs.

Basic LATCH Operation

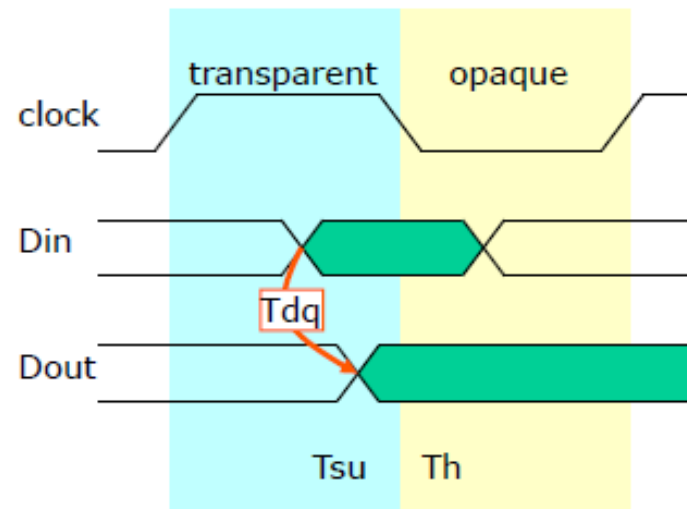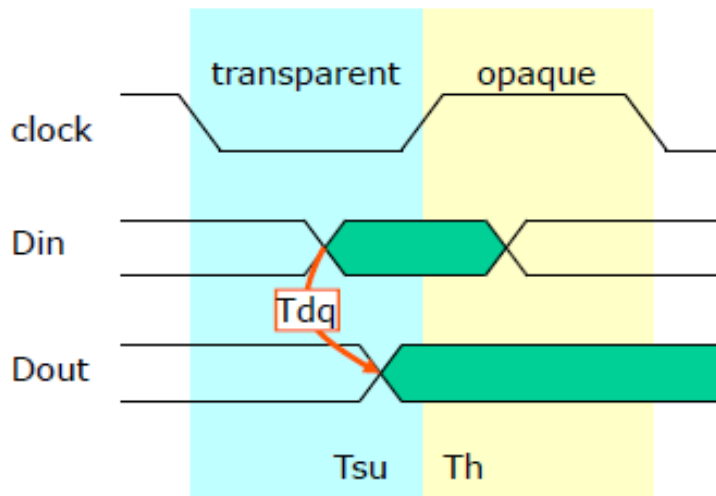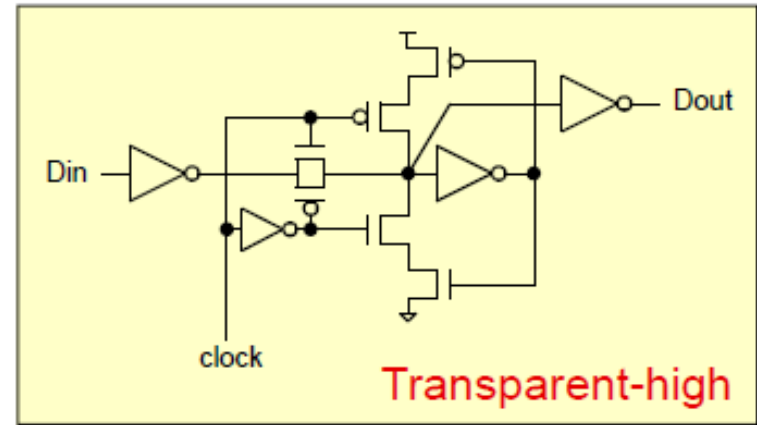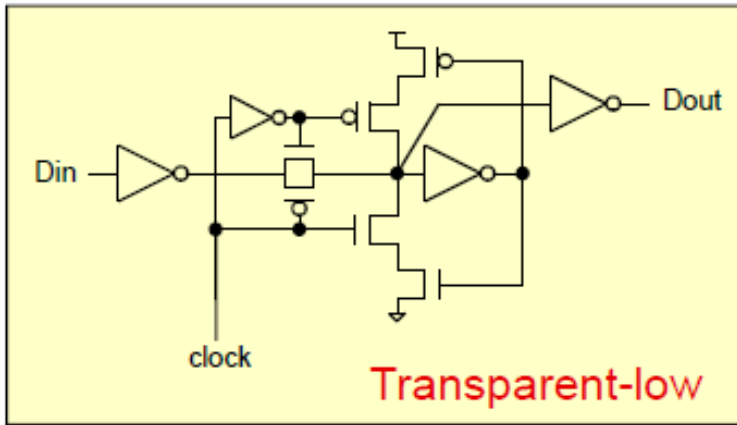


FLOP Delay

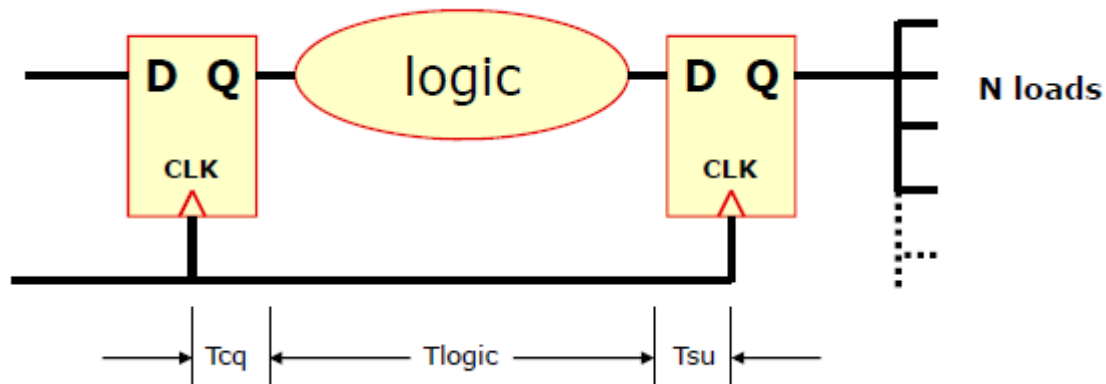
- Sum of setup time and Clk-output delay is the only true measure of the performance with respect to the system speed (MAXDELAY)
- $T_{cycle} = T_{cq} + T_{logic} + T_{su} + T_{skew}$
- T_{logic} contains interconnect delay



Building a FLOP with Two Latches

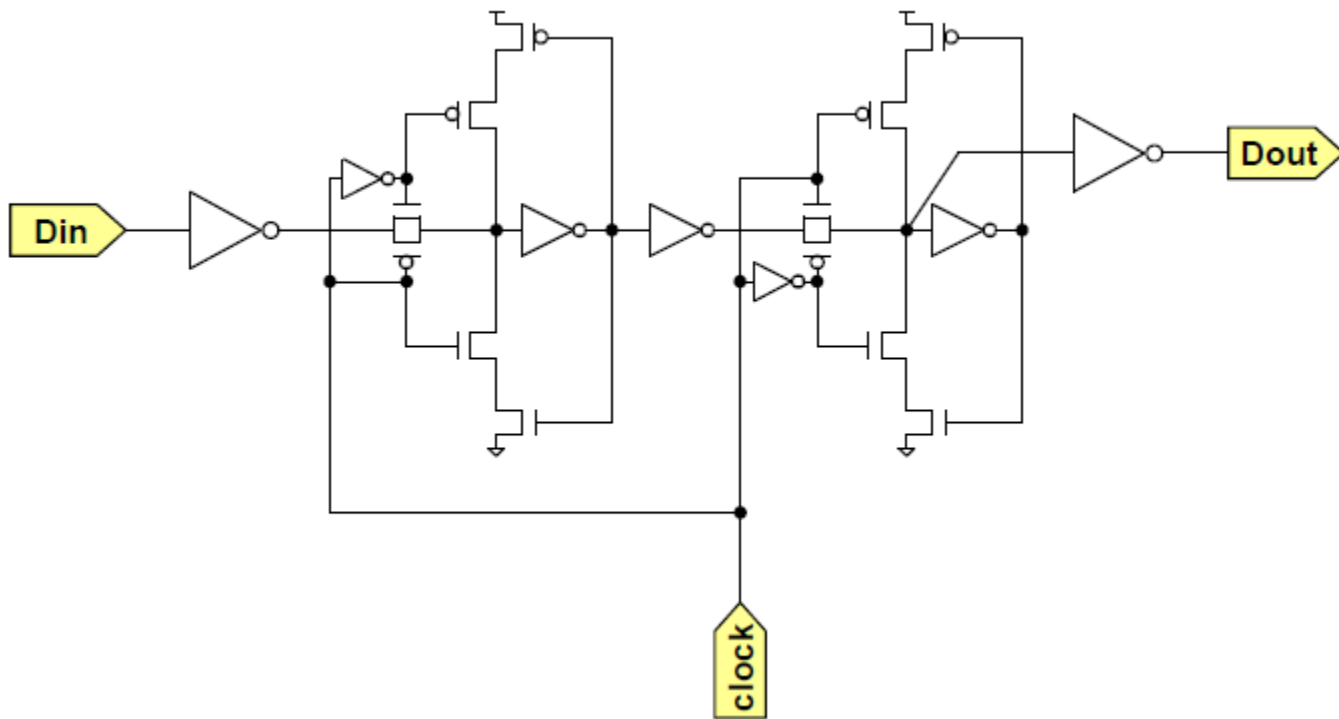

FLOP Timing Diagrams

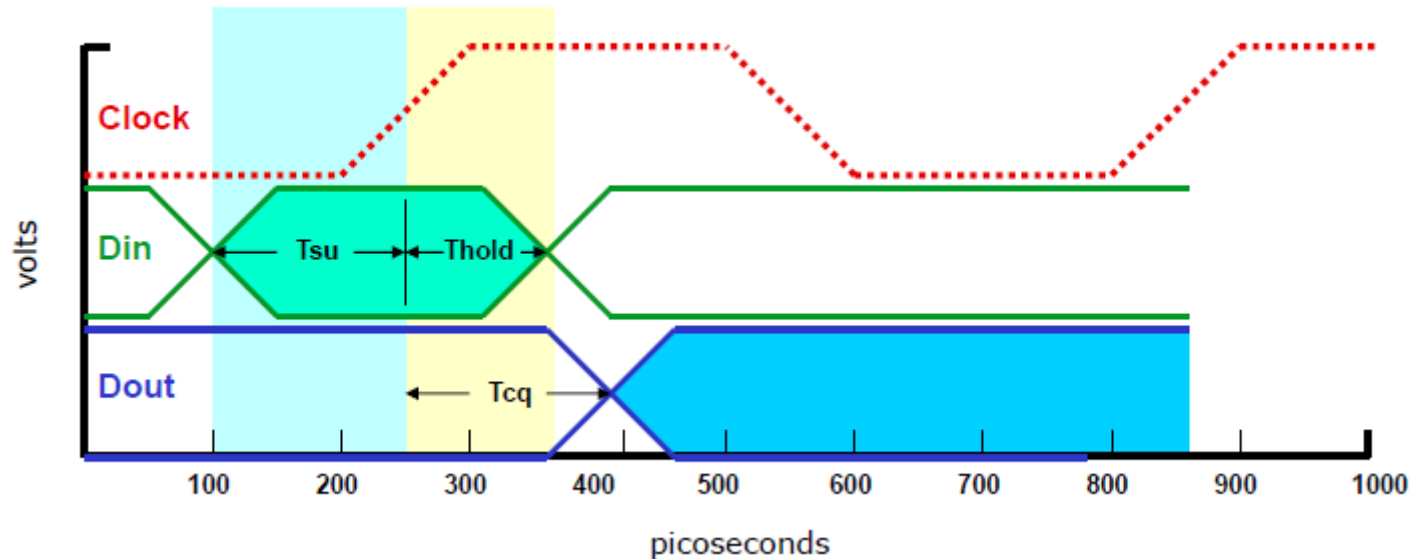



Tsu : input setup time

Thold : input hold time

Tcq : clock to out

Tdata to out = Tsu + Tcq

MAXDELAY

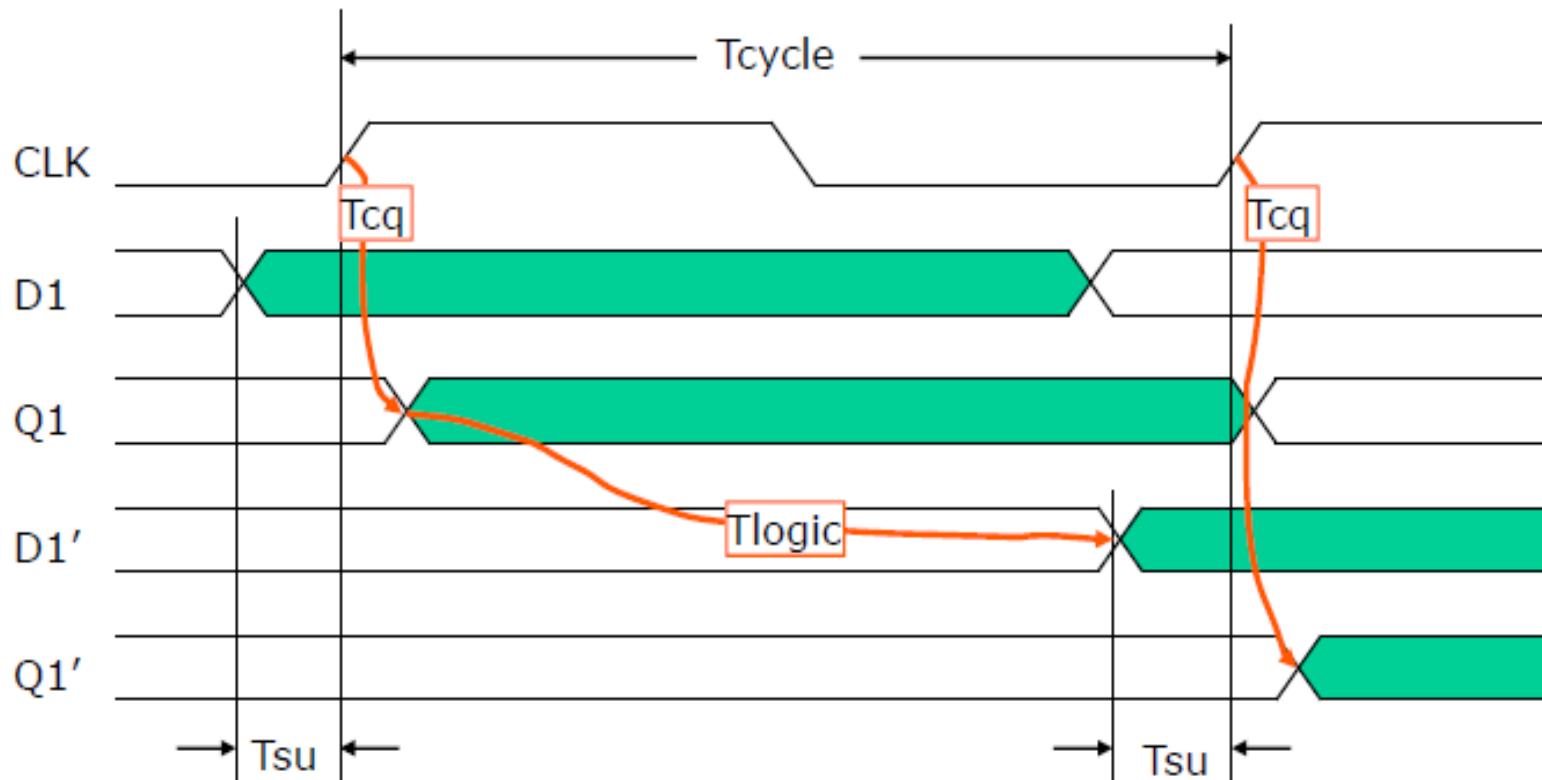
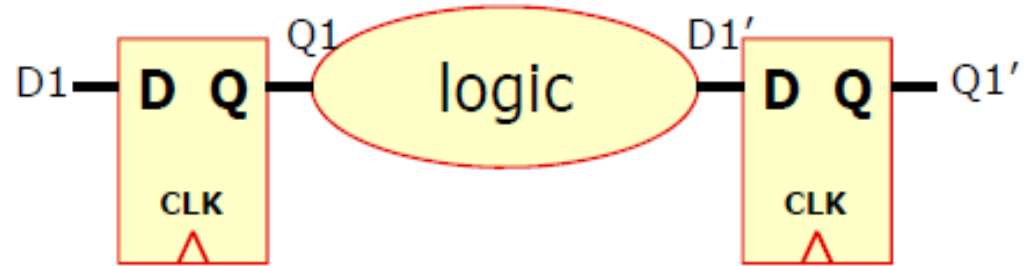


$$T_{logic} < T_{cycle} - (T_{cq} + T_{su})$$

or

$$T_{cycle} \leq T_{logic} + T_{cq} + T_{su}$$

MINDELAY

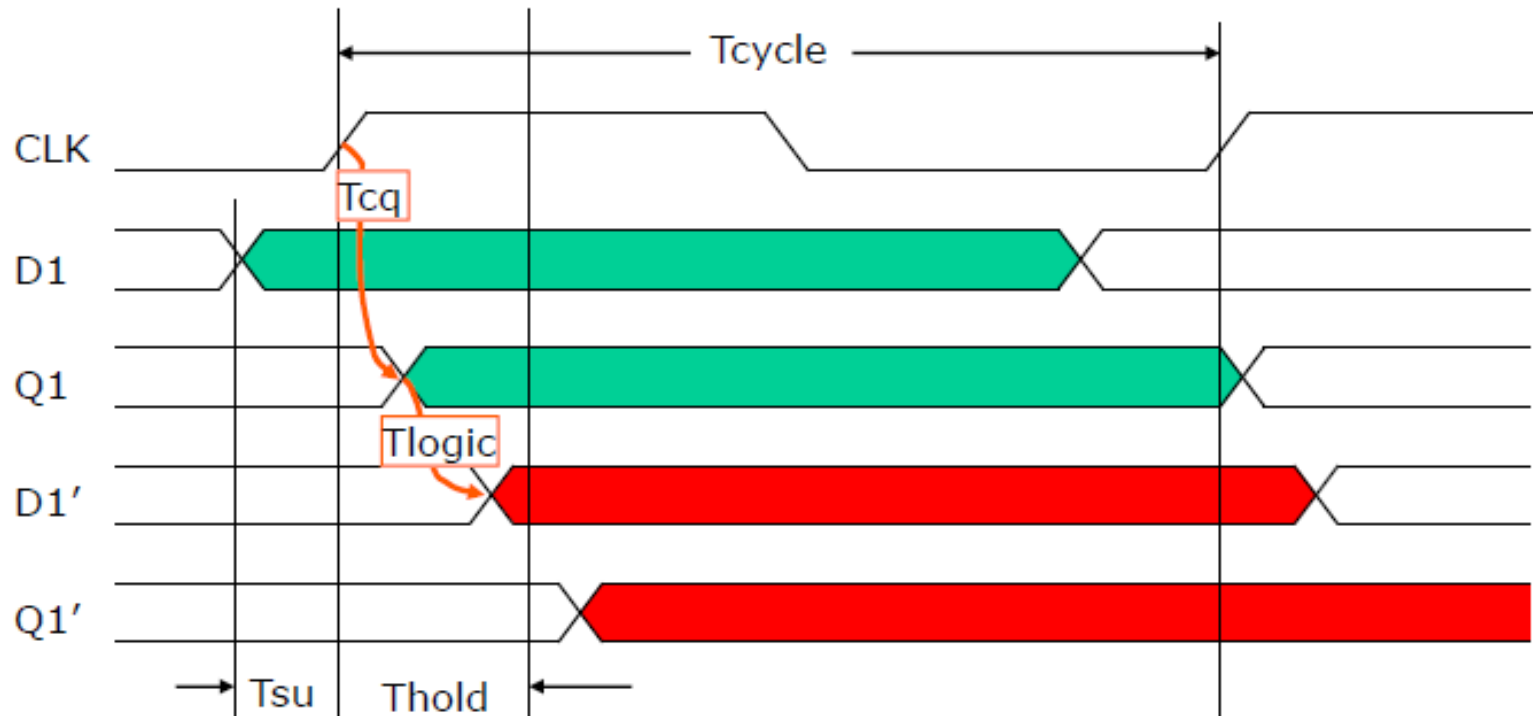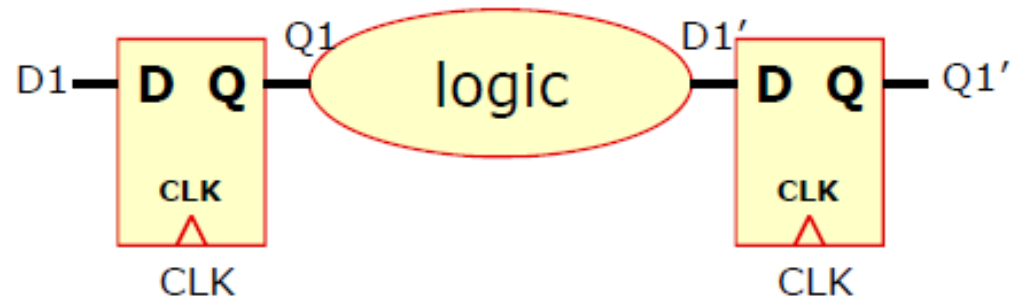

$$T_{logic} > T_{hold} - T_{cq} + T_{skew}$$

QZ

- What is this circuit ?

