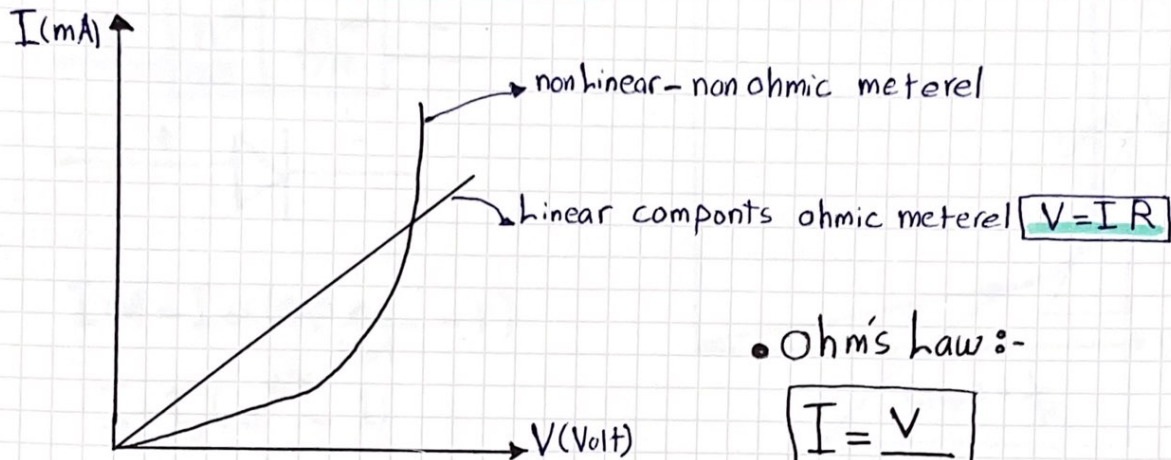


Experiment # 1

linear and nonlinear circuit components


IV-characteristic curve



• Ohm's Law:-

$$I = \frac{V}{R}$$



Carbon Resistor:-

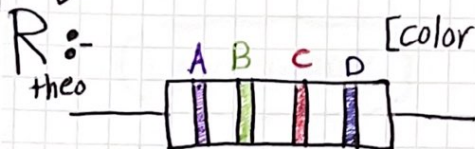

كيف نحسب قيمة المقاومة عن طريق [color code]

$$[(AB * 10^C) \pm (D * AB * 10^C)]$$

Exp circuit

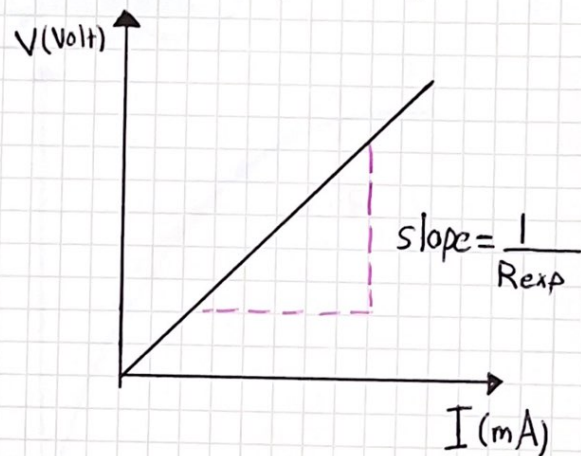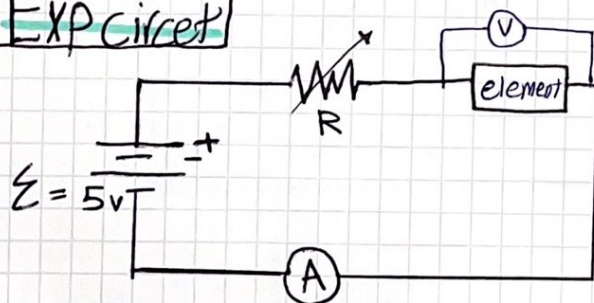


→ Keep changing the value of R to become (0.1, 0.4, ...) and measure I then draw I vs V by Excel or by hand.

V) Volt	0.1	0.4	0.8	1.2	1.5
(I) mA

linear and nonlinear circuit components


2 Diode:-

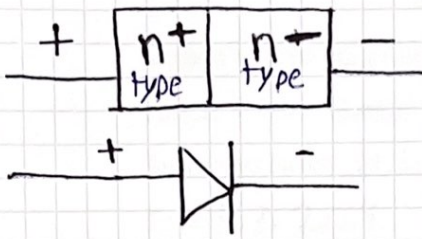Allow current to pass through in one Direction




$$I(V) = I_0 \left(\exp \frac{eV}{kT} - 1 \right)$$

$$I = I_0 (e^{V/K} - 1)$$

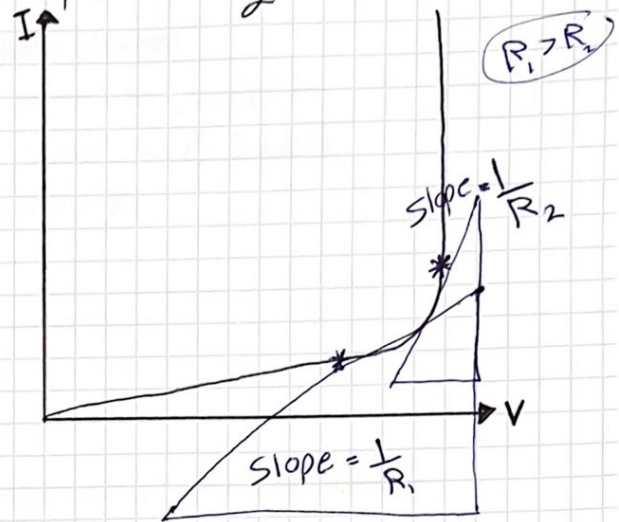


3 Light bulb - tungsten wire

Low current

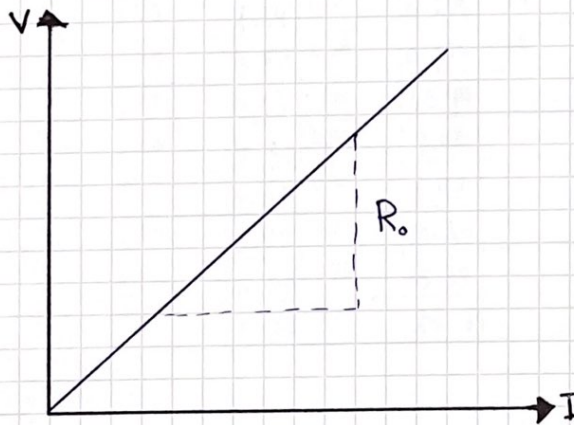

Linear

High current


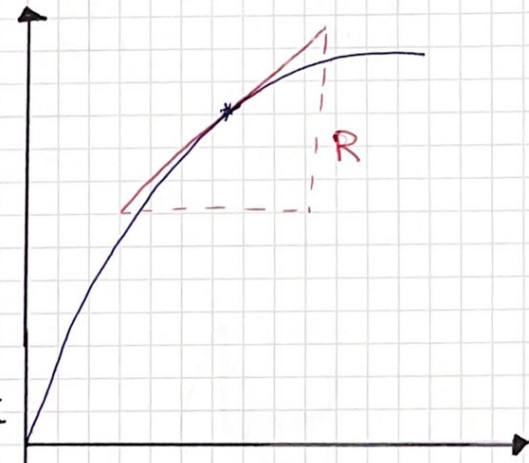


Non-Linear

$$R = R_0 [1 + \alpha (T - T_0)]$$

$T_0 = \text{room Temp}$
 $\alpha = (4.5 \times 10^{-3}) \text{ K}^{-1}$ (Tungsten)
 $\alpha = \text{Temp coefficient of resistivity}$
 $R_0 = \text{the resistance at } T_0$

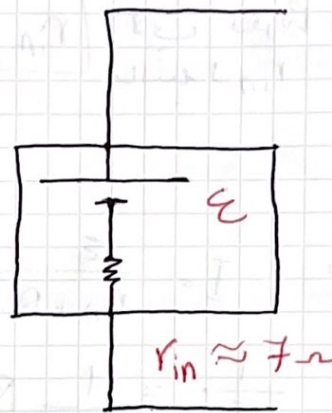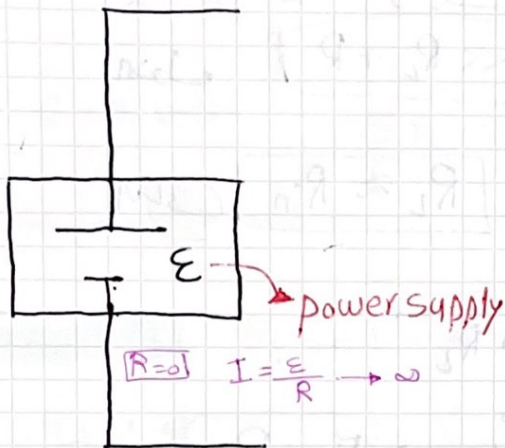Exp#2: Source Internal Resistance, Loading Problem and circuit Impedance Matching




Source internal Resistance.

$$V_{ab} \approx \epsilon$$

Ideal power supply Ideal Battery Real power supply Real Battery

Loading Problem:
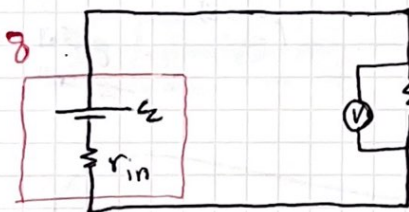
$$R_L \geq 10 r_{in} \quad \text{to avoid loading Source}$$



$R_L \rightarrow$ Load: load Resistance

كل أحمال يمكن أن يكون
مقاومة يمكن أن يكون

$$R_L V = IR$$

$$V_L = \frac{R_L}{r_{in} + R_L} \epsilon$$

$$I = \frac{\epsilon}{r_{in} + R_L}$$

$$V_L = \frac{1}{\frac{r_{in}}{R_L} + 1} \epsilon$$

$$r_{in} \approx R_L \rightarrow \frac{V_L}{\epsilon} \approx \frac{1}{2}$$

$$V_L \approx \frac{\epsilon}{2}$$

Power:-

$$P = I^2 R_L$$

$$* P = \left(\frac{\epsilon}{r_{in} + R_L} \right)^2 R_L$$

$$* P = \frac{V^2}{R_L} \quad V(R_L)$$

Maximum power

$$\frac{dP}{dR_L} = 0 \rightarrow R_L = r_{in}$$

Power (Max) $R_L = r_{in}$

Voltage (Full) $R_L \geq 10 r_{in}$


impedance matching

Impedance matching:

لكي تكون الشحنة تساري في
يحول على اقل قيمة Power
نطلع على $R_L = r_{in}$


من عشان انتظف من مشكلة التحول من قوة يكون على $R_L \geq 10 r_{in}$
صفت R واكثرها موجودة من ضمن البطارية
بغني دكاي يبي $R_L = R + r_{in}$

Exp #2

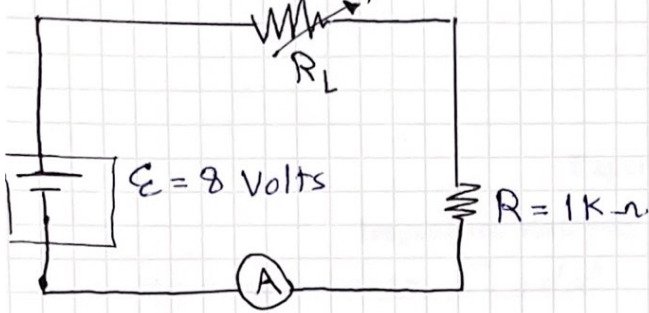

$$\Sigma_{exp} = \frac{1}{\text{slope}}$$
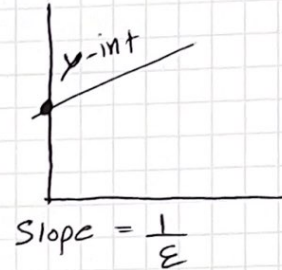
$$R_{in} = y\text{-int} \times \Sigma_{exp}$$



Graph [1] $R_L = 0.1 \rightarrow 1K\Omega$ فقط مدونات نأخذ

$$I = \frac{E}{R + r_{in} + R_L} = \frac{E}{R_{in} + R_L}$$

$$\frac{1}{I} = \frac{1}{\Sigma_{exp}} R_L + \frac{R_{in}}{\Sigma_{exp}}$$


$\xrightarrow{R + r_{in}}$

Graph [1] $\frac{1}{I} \text{ vs } R_L$ \square slope = $\frac{1}{\Sigma_{exp}}$ Straight line with slope = $\frac{1}{E}$

$$\square y\text{-intercept} = \frac{R_{in}}{\Sigma_{exp}}$$

$$y\text{-intercept} = \frac{R + r_{in}}{E}$$

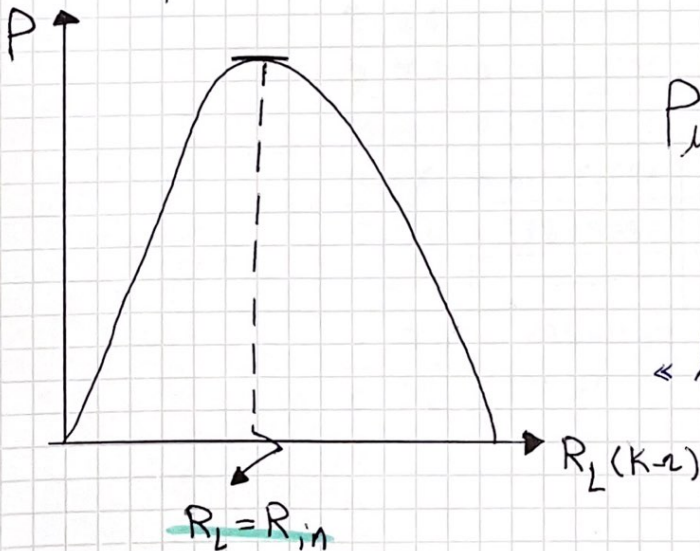Graph [2] $P \text{ vs } R_L$ (0.1 \rightarrow 60 K Ω) \hookrightarrow ∞ \rightarrow ∞




$$P_{max} \text{ at } R_L = R_{in}$$

$$R_{in} = \dots\dots\dots$$

« log axis »

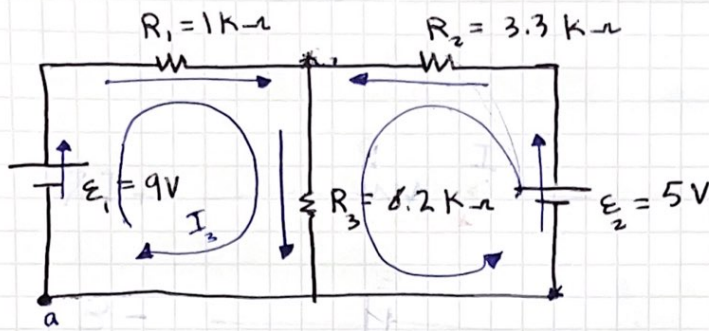Exp #3: Kirchhoffs Laws and Superposition Principle



1st Law: $\sum I_{(junction)} = 0$

$$\sum I_{in} = \sum I_{out}$$

$$I_1 + I_2 = I_3 \rightarrow ①$$

اتجاه التيار صلي لا يوجد
من E_1

Kirchheffs
2nd Law $\sum_{j=1}^N V_j = 0$

① ② ③ →

$I_1 = \dots \dots \dots$ mA
 $I_2 = \dots \dots \dots$ mA
 $I_3 = \dots \dots \dots$ mA

Loop 1


$$E_1 - I_1 R_1 - I_3 R_3 = 0 \rightarrow ②$$

Loop 2


$$E_2 - I_2 R_2 - I_3 R_3 = 0 \rightarrow ③$$

SPP

تجزئة
التيار
بجزيئين

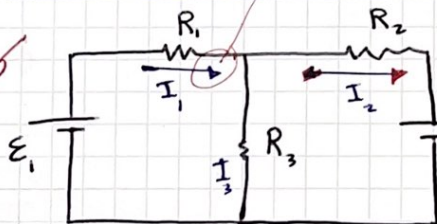

اتجاه التيار صلي
لا يوجد من E_2

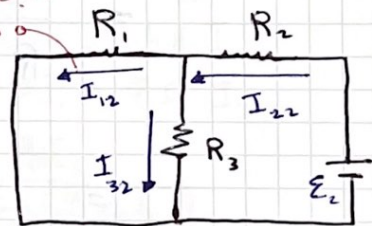

تيار E_2 يؤثر
على المقاومات

نفس الاتجاه
جميع
عكس الاتجاه
طرح

$$I_{11} - I_{12} = I_1$$

$$I_{22} - I_{21} = I_2$$


$$I_{31} + I_{32} = I_3$$

التيار
جاء من E_1 على
 I_1

التيار
جاء من E_2 على
 I_2

التيار
جاء من E_1 على
 I_3

تيار E_2 يؤثر
على المقاومات

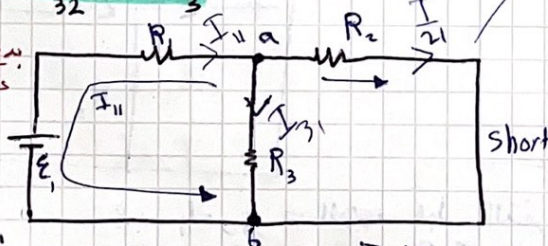

Short

$$I_{11} = \frac{E_1}{R_1 + \left(\frac{R_2 R_3}{R_2 + R_3} \right)}$$

$$V_{ab} = I_{21} R_2 = I_{31} R_3 = E_1 I_{11} R_1$$

$$I_{21} = \frac{V_{ab}}{R_2}$$

$$I_{31} = \frac{V_{ab}}{R_3}$$

انتهت المقارنة
الحكاية

للتأثير من القيم



$$I_1 = 1.77 \text{ mA}$$

$$I_2 = 0.66 \text{ mA}$$

$$I_3 = 1.20 \text{ mA}$$

بعض القواعد لاجار التيار

Some Rules:

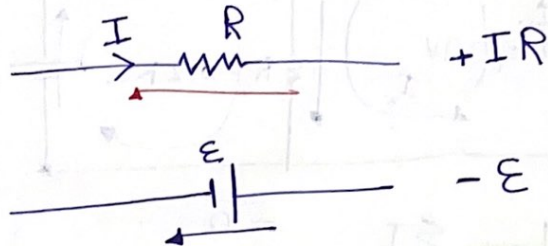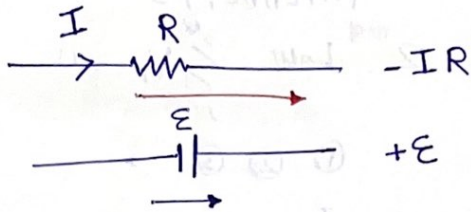

finding I_1 & -


$$R_2 \parallel R_3$$

$$I_1 = \frac{\epsilon_1}{R_1 + R_2 \parallel R_3}$$


$$= \frac{\epsilon_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

$$= \frac{12}{1 + \frac{3.3 \times 6.2}{3.3 + 6.3}}$$


$$= 3.8 \text{ mA } (\rightarrow)$$

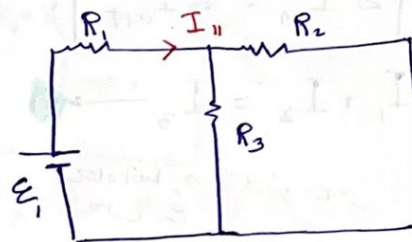
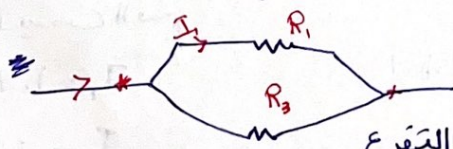
$$I = \frac{\epsilon_2}{R_2 + R_1 \parallel R_3}$$



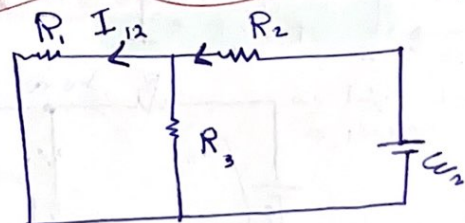جهد الفرع = الجهد قبل التقعر
 $I_1 R_1 = I (R_1 \parallel R_3)$



R_{eq}

EXP 3:-

Kirchhoff's laws and superposition principle


1) Kirchhoff's laws:

First Law:

$$\sum I_{\text{junction}} = 0$$

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$
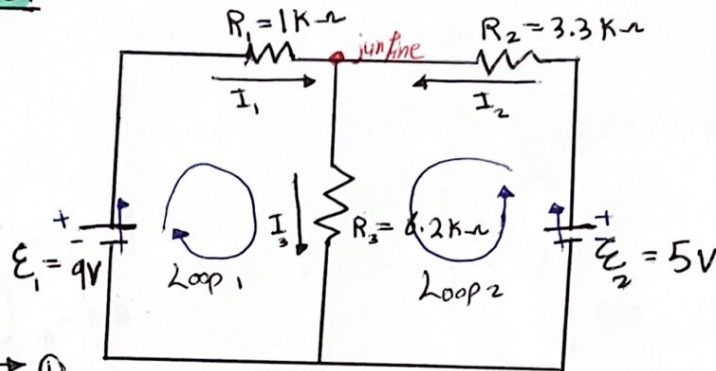
$$I_1 + I_2 = I_3 \rightarrow \textcircled{1}$$



Second Law:

$$\sum_{j=0}^n V_j = 0$$

From Loop 1

$$E_1 - I_1 R_1 - I_3 R_3 = 0$$

$$E_1 = I_1 R_1 + I_3 R_3 \rightarrow \textcircled{2}$$

$$9 = I_1 + 6.2 I_3$$

From Loop 2

$$E_2 - I_2 R_2 - I_3 R_3 = 0 \rightarrow \textcircled{3}$$

$$E_2 = I_2 R_2 + I_3 R_3$$

من المعادلة الأولى

$$E_2 = (I_3 - I_1) R_2 + I_3 R_3$$

$$= I_3 R_2 - I_1 R_2 + I_3 R_3$$

$$E_2 = I_3 (R_2 + R_3) - I_1 R_2$$

$$5 = I_3 (3.3 + 6.2) - 3.3 I_1$$

$$\text{eq 3} + \text{eq 2}$$

$$[9 = I_1 + 6.2 I_3] \times 3.3$$

$$29.7 = 3.3 I_1 + 20.46 I_3$$

$$+ 5 = -3.3 I_1 + 9.5 I_3$$

$$34.7 = 29.96 I_3$$

$$I_3 = 1.158 \text{ mA}$$

$$9 = I_1 + 6.2 (1.158)$$

$$I_1 = 1.819 \text{ mA}$$

$$I_1 + I_2 = I_3$$


$$I_2 = I_3 - I_1$$

$$= 1.158 - 1.819$$

$$I_2 = -0.661 \text{ mA}$$

2) Superposition principle

A) connect the circuit shown

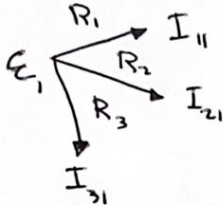

$$I_{11} = \frac{E_1}{R_1 + \left(\frac{R_2 R_3}{R_2 + R_3} \right)}$$

$$= \frac{9}{1 + \left(\frac{3.3 \times 6.2}{3.3 + 6.2} \right)} \quad 2.153$$

$$= \frac{9}{3.15}$$


$$I_{11} = 2.8571 \text{ mA}$$

$$\rightarrow I_{21} R_2 = I_{31} R_3 = I_{11} R_{23}$$

$$3.3 I_{21} = 6.2 I_{31} = 2.85 \times 2.153$$

$$I_{21} = \frac{6.136}{3.3} = 1.859 \text{ mA}$$
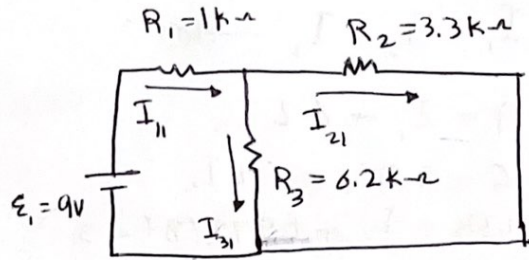
$$I_{31} = \frac{6.136}{6.2} = 0.9896 \text{ mA}$$



$$V = I_{11} R_1 = I_{31} R_3 = I_{21} R_2$$

$$V = 2.85 \text{ V}$$

$$V = 2.85$$

$$V = I_{31} R_3$$


$$I_{31} = \frac{V}{R_3}$$

$$V = I_{21} R_2$$

$$I_{21} = \frac{V}{R_2}$$

2) Superposition principle

B) connect the circuit shown

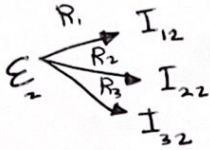

$$I_{22} = \frac{E_2}{R_2 + \left(\frac{R_1 R_3}{R_1 + R_3}\right)}$$

$$= \frac{5}{3.3 + \left(\frac{1 \times 6.2}{1 + 6.2}\right)}$$

$$= \frac{5}{4.16} \rightarrow 0.86$$

$$I_{22} = 1.20 \text{ mA}$$



$$I_{22} R_{13} = I_{32} R_3 = I_{12} R_1$$

$$1.20 \times 0.86 = I_{32} \times 6.2 = I_{12} \times 1$$

$$I_{32} = \frac{1.032}{6.2}$$

$$I_{32} = 0.1664 \text{ mA}$$

$$I_{12} = 1.032 \text{ mA}$$

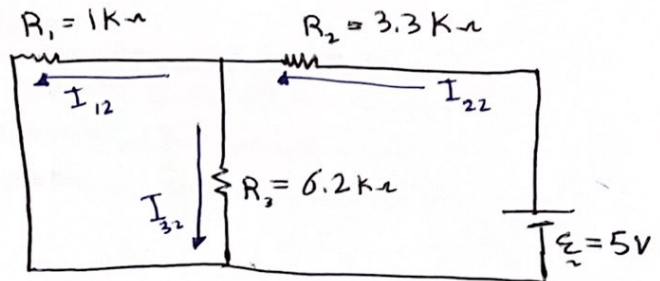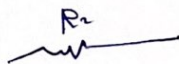

Final step

Find the current using SPP

$$* I_1 = I_{11} - I_{12}$$

$$= 2.853 - 1.032$$

$$I_1 = 1.821 \text{ mA}$$

$$* I_2 = I_{22} - I_{21}$$

$$= 1.20 - 1.859$$

$$I_2 = -0.659 \text{ mA}$$

$$* I_3 = I_{31} + I_{32}$$

$$= 0.9896 + 0.1664$$

$$I_3 = 1.156 \text{ mA}$$

EXP#4

Thevenin and Norton technique

① when $I_1 = I_2$


* $R_1 = 1k\Omega$

* $R_2 = 3.3k\Omega$

* $R_3 = 6.2k\Omega$


* $\mathcal{E}_1 = 9V$

* $\mathcal{E}_2 = 5V$

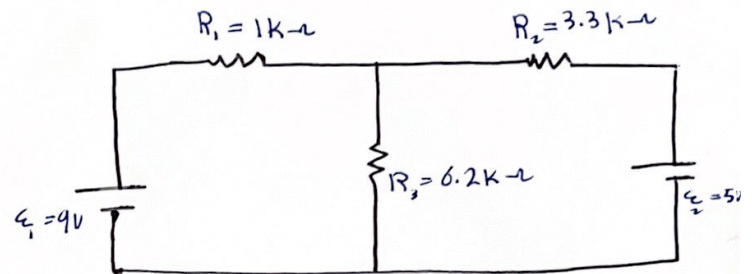

→ Kill our V sources to find R_{th}

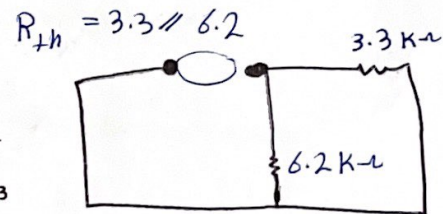Req $\rightarrow R_{eq} = \frac{R_2 * R_3}{R_2 + R_3}$



$$= \frac{3.3 * 6.2}{3.3 + 6.2}$$

$$= 2.153 k\Omega$$

to find V_{th} , Remove R_1 and return \mathcal{E}_1 and \mathcal{E}_2 to the circuit


2 $\mathcal{E}_{th} =$

By Kirchhoff:-

$$\mathcal{E}_1 - \mathcal{E}_{eq} - I_{eq} R_3 = 0$$

$$9 - \mathcal{E}_{eq} - 0.52(6.2) = 0$$

$$\mathcal{E}_{eq} = 5.736 V$$

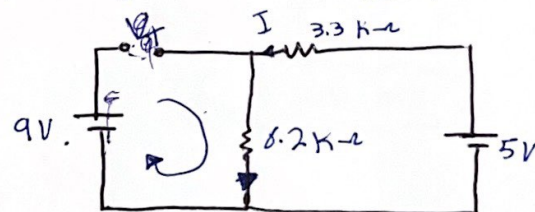

3 $I_{eq} = \frac{\mathcal{E}_2}{R_2 + R_3} = \frac{5}{3.3 + 6.2}$


$$= 0.52 mA$$

construct Thevenin circuit:-

$$I_1 = \frac{\epsilon_{eq}}{R_{eq} + R_L}$$

$$= \frac{5.776}{2.153 + 1}$$

$$I_1 = 1.83 \text{ mA}$$

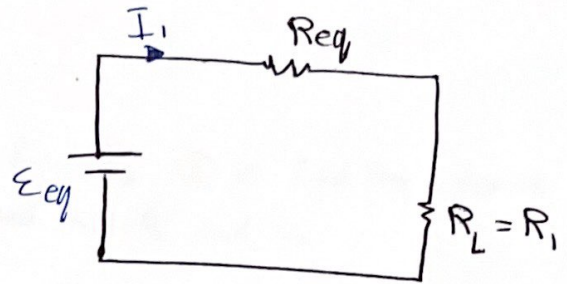

Construct Norton circuit:

$$R_{eq} = 2.153 \text{ K}\Omega \rightarrow$$


Thevenin \(\epsilon_{eq}\) و \(R_{eq}\)

$$I_{eq} \quad I_1 = I_2 + I_3$$

$$9 - 6.2 I_3 = 0$$

$$I_3 = 1.4516 \text{ mA}$$
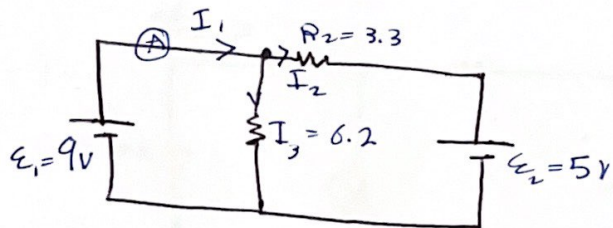
$$I_1 = I_{eq} = I_3 + I_2 = 2.8816 \text{ mA}$$



$$9 - 3.3 I_2 - 5 = 0$$

$$\frac{4}{3.3} = I_2$$


$$I_2 = 1.21 \text{ mA}$$

I جهد الفرع = جهد الفرع كامل

$$I_{eq} (R_{eq} \parallel R_L) = I R_L$$



$$2.8816 \left(\frac{2.153}{3.153} \right) = I \cdot 1 \text{ K}\Omega$$

$$I = 1.8174 \text{ mA}$$

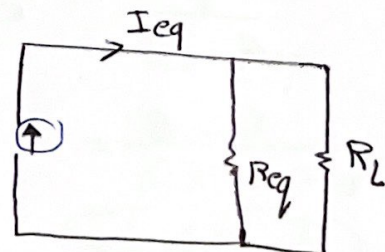

when $I_3 = I_L$

Thevenin $R_L = R_3$

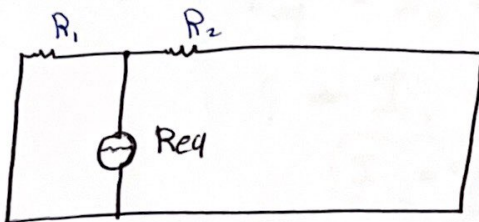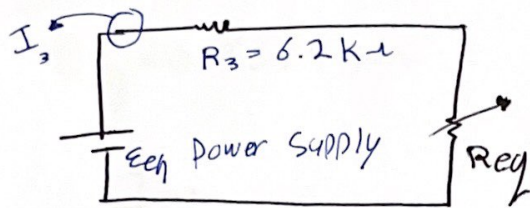

- to find I_3 (A) to find R_{eq} , Remove R_L and kill ϵ_1 and ϵ_2

$$R_{eq} = \frac{R_1 * R_2}{R_1 + R_2}$$

$$= \frac{1 * 3.3}{1 + 3.3}$$

$$R_{eq} = 0.7674 \text{ k}\Omega$$



- to find ϵ , Remove R_L and return ϵ_1 and ϵ_2

$$I' = \frac{\epsilon_1 - \epsilon_2}{R_1 + R_2} = \frac{9 - 5}{1 + 3.3} = 0.930 \text{ mA}$$

$$\epsilon_{eq} = \epsilon_1 - I' R_1$$

$$= 9 - (0.930) \times 1$$

$$= 8.07 \text{ Volt}$$

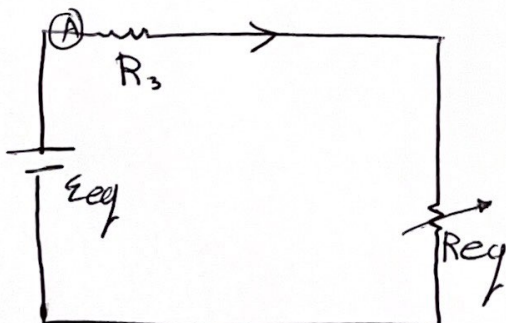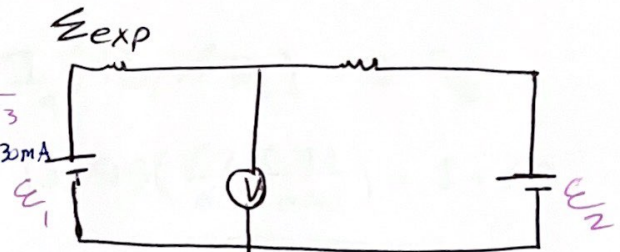


$$I_3 = \frac{\epsilon_{eq}}{R_3 + R_{eq}}$$

$$= \frac{8.07}{6.2 + 0.767}$$

$$= 1.1582 \text{ mA}$$

at Norton

$$R_{eq} = 0.7874 \text{ k}\Omega$$

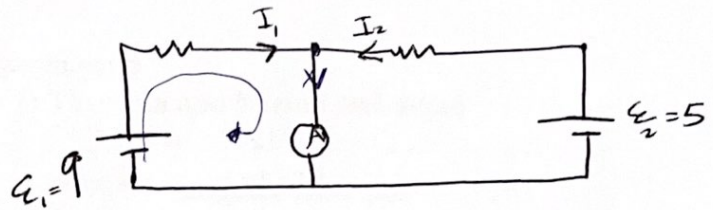

I_{eq}

$$I_{eq} = I_3 + I_2$$


$$9 = I_1 = 0$$

$$I_1 = 9 \text{ mA}$$

$$5 + 3.3I_2 = 0$$

$$I_2 = -1.515 \text{ mA}$$

$$I_{eq} = I_3 = 10.515 \text{ mA}$$

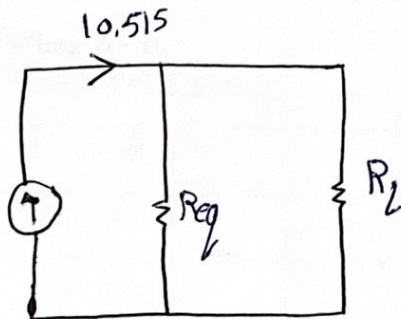

$$I_q (R_{eq} \parallel R_L) = I R_L$$

$$10.515 \left(\frac{6.2 \times 0.76}{6.2 + 0.76} \right) = I \times 6.2$$



$$I = 1.158 \text{ mA}$$

Experiment 5+6

Capacitor and Inductor

4 5-10

RC-circuit

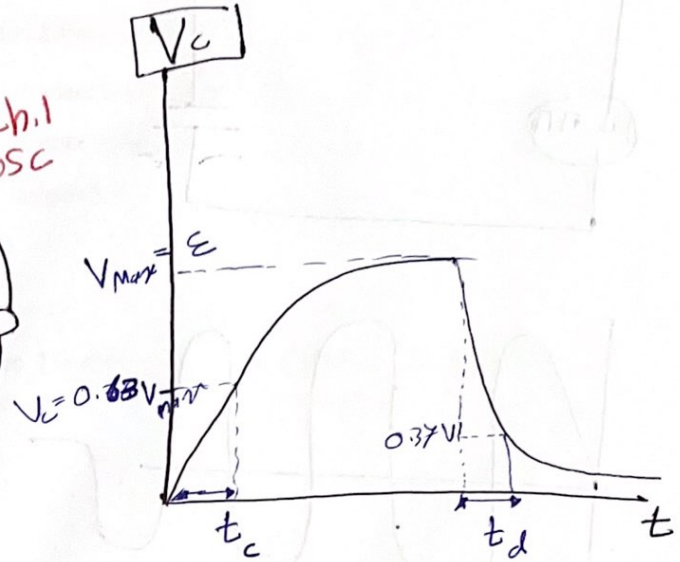
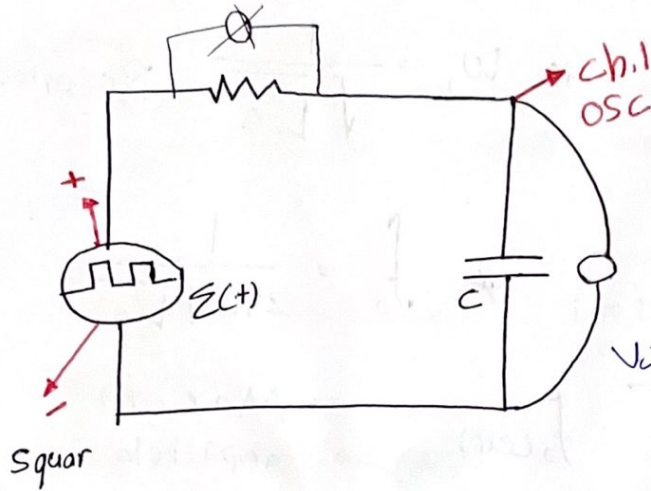


$t \rightarrow$ time constant

$$t_{theo} = RC = \text{Seconds}$$

$$t_{exp} = \frac{t_c + t_d}{2}$$


VR

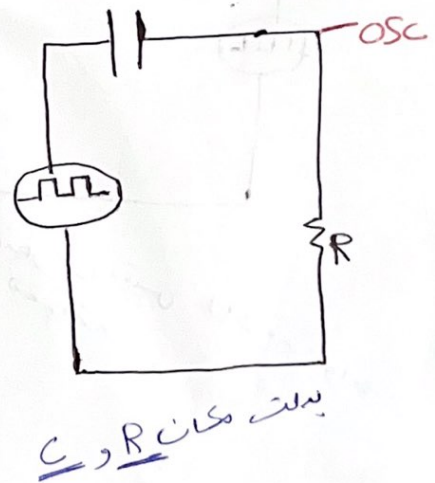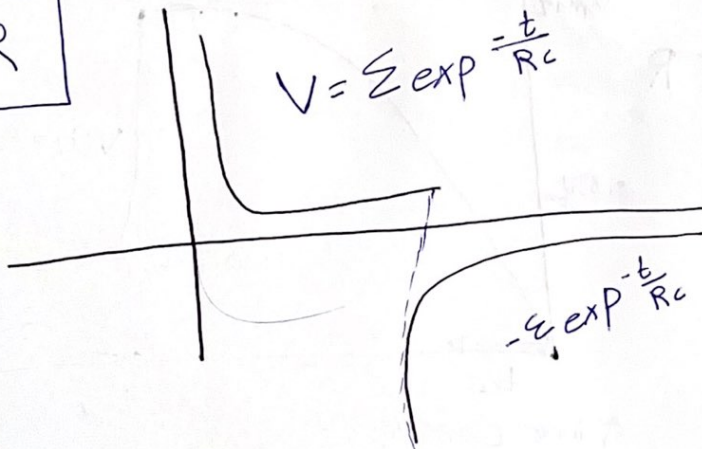

پسند من RC و C

LC-circuit

LC-circuit (L & C)

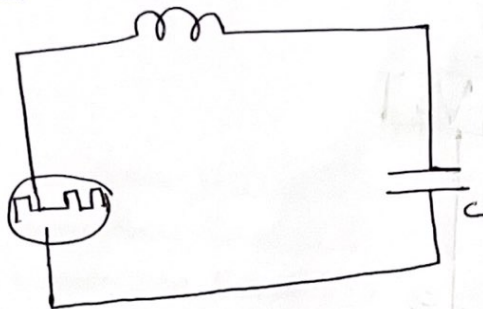


$$* V_c = V_c \cos(\omega t + \phi)$$

$$* V_c = \text{Amplitude}$$


$$* \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{Resonance}$$

$$* f_0 = \frac{1}{2\pi \sqrt{LC}}$$

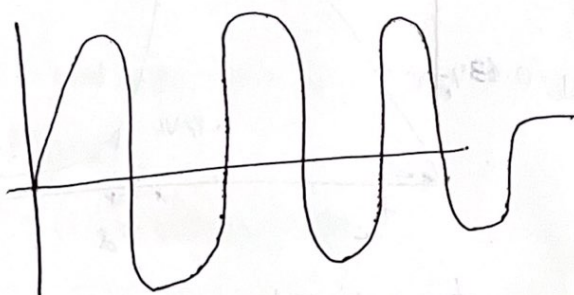

$f_0(\text{exp}) \rightarrow$ Maximum amplitude


RL-circuit

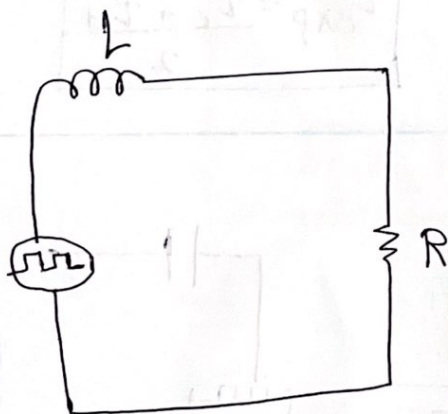

العمران يقيس في الجارة صوانة
للقولبة

V_R
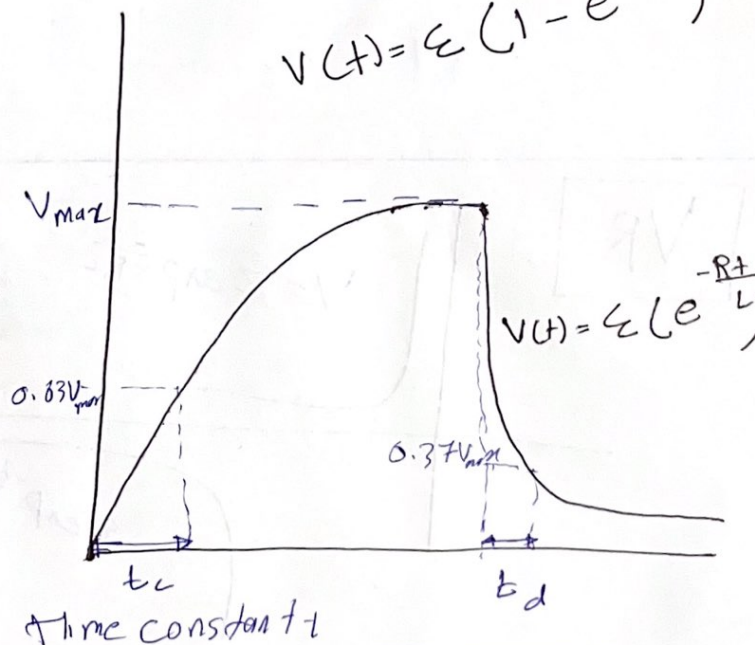
$$\text{charging } V(t) = \mathcal{E} (1 - e^{-\frac{Rt}{L}})$$




Time constant τ

$$\tau_{\text{thec}} = \frac{L}{R}$$

Experiment 7 Damped Oscillations

RLC-circuit DC-pr...

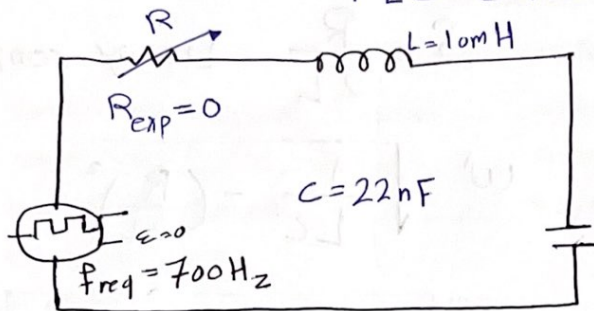

There cases:

$$\boxed{1} \left(\frac{R}{2L} \right)^2 < \frac{1}{LC} \Rightarrow \sqrt{-} \rightarrow \text{underdamping}$$

$$\boxed{2} \left(\frac{R}{2L} \right)^2 = \frac{1}{LC} \Rightarrow \sqrt{0} \rightarrow \text{critical damping}$$

$$\boxed{3} \left(\frac{R}{2L} \right)^2 > \frac{1}{LC} \Rightarrow \sqrt{+} \rightarrow \text{overdamping}$$

$$\mathcal{E} = V_R + V_L + V_C$$

$$\mathcal{E} = IR + L \frac{dI}{dt} + \frac{Q}{C}$$

$$\mathcal{E} = R \frac{dQ}{dt} + L \frac{d^2Q}{dt^2} + \frac{Q}{C}$$



2nd order linear diff equation

$$Q(t) = A_1 e^{\lambda_+ t} + A_2 e^{\lambda_- t}$$

$$\lambda_{\pm} = -\left(\frac{R}{2L} \right) \pm \sqrt{\left(\frac{R}{2L} \right)^2 - \frac{1}{LC}}$$

A_1, A_2 constant

1 under damping

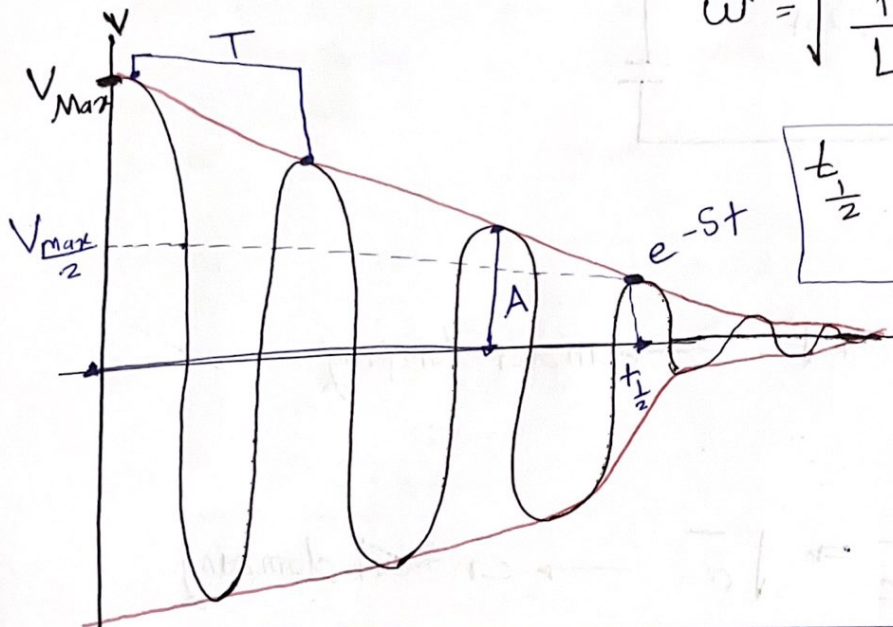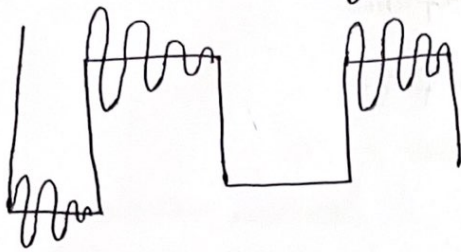


$$Q(t) = Q_0 e^{-st} \cos(\omega' t + \phi)$$

$$S = \frac{R}{2L} \quad \text{Decay constant}$$

$$\omega' = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$t_{\frac{1}{2}} = \frac{2L \ln 2}{R}$$


2 critical damping

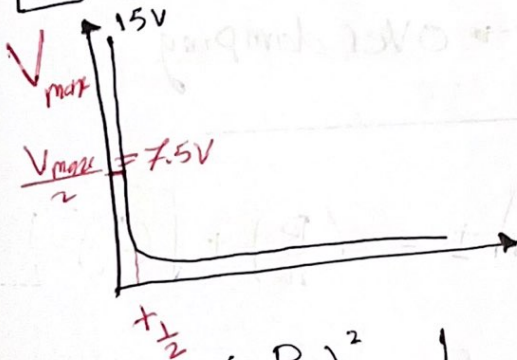

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$

$$S = \frac{\ln 2}{t_{\frac{1}{2}}}$$


3 over damping

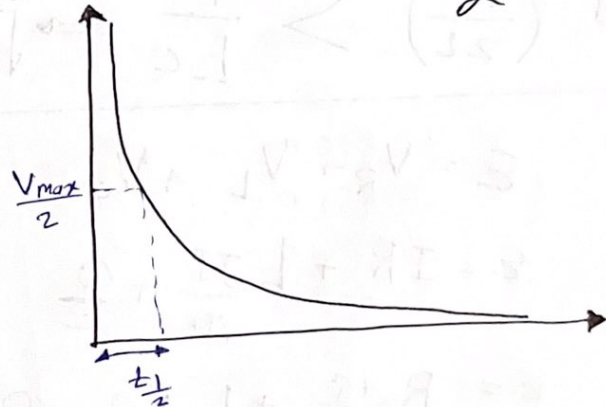

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

$$S = \frac{\ln 2}{t_{\frac{1}{2}}}$$

Exp # 8 Impedance and Reactance

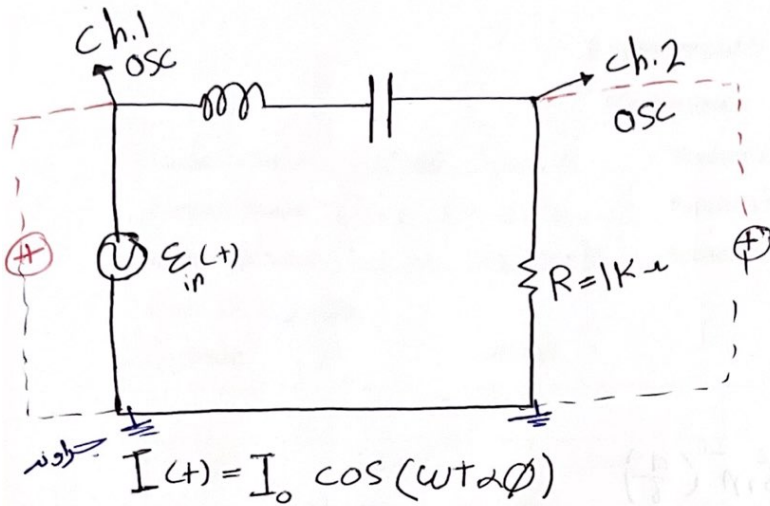


$$I_0 = \frac{\epsilon_0}{\sqrt{R + \left(\omega L + \frac{1}{\omega C}\right)^2}} \rightarrow \text{exp 9}$$

$$\phi = \tan^{-1} \left(\frac{-\omega L + \frac{1}{\omega C}}{R} \right) \rightarrow \text{exp 9}$$

phase shift angle

V_{Rin}

$$\omega = 2\pi f$$



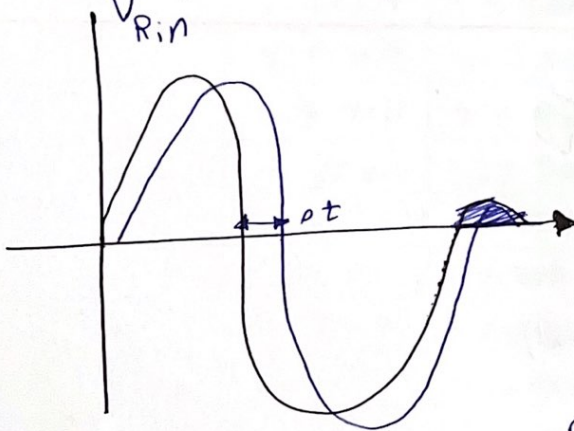


$$\phi (\text{phase shift}) = \omega \Delta t = 2\pi f \Delta t$$

internal mode

أي دائرة هـ ا حفر
أي دائرة هـ ا زرق
2P
او قطعهم عبر الشات
بجيب cursor

extending mode

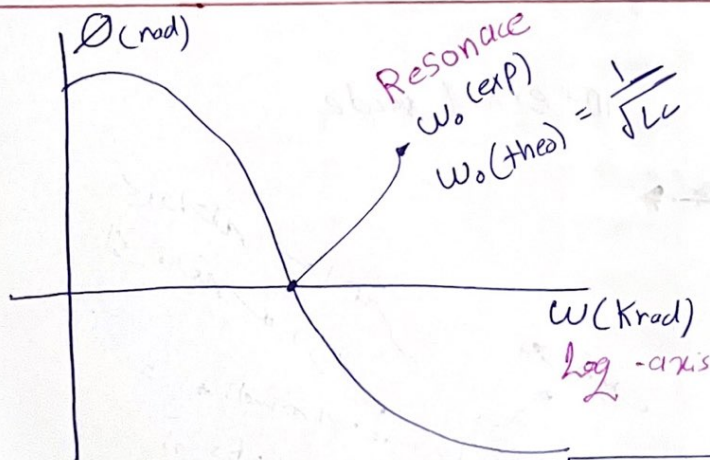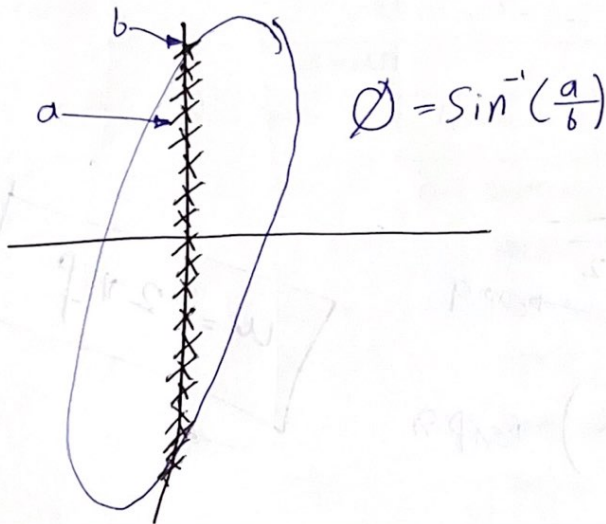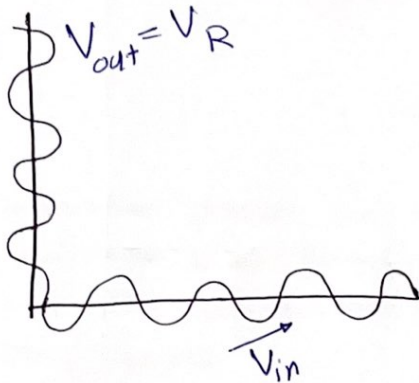


$$I(t) \propto \cos(\omega t + \phi) \quad \boxed{V_R = IR}$$

$$Q(t) = \int I(t) dt \propto \sin(\omega t + \phi) \quad \boxed{V_L = \frac{R}{\omega C}}$$

$$\frac{dI}{dt} \propto -\sin(\omega t + \phi) \quad \boxed{V_L = L \frac{dI}{dt}}$$

Exp # 9

Resonance

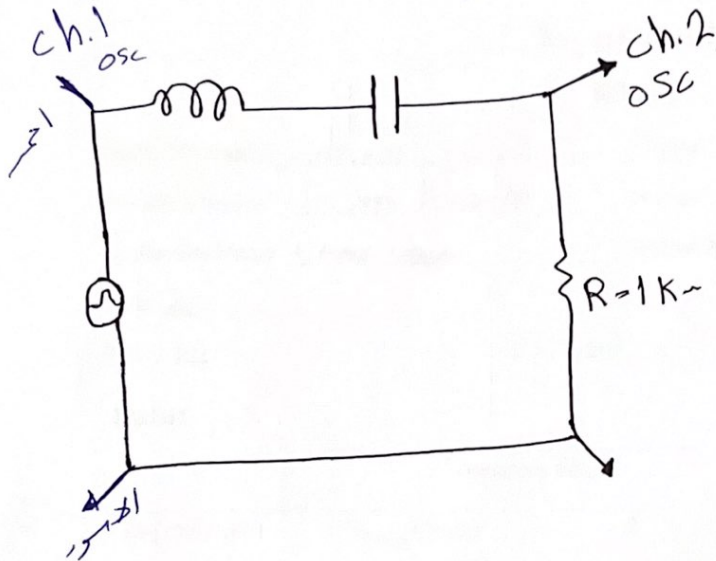

$$I(t) = I_0 \cos(\omega t + \phi)$$

$$I_0 = \frac{V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

of Resonance

$$(\omega_0 - \frac{1}{\omega C})^2 = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\omega L}{R}$$

$$= \frac{1}{R} \sqrt{\frac{L}{C}}$$


$$Q = \frac{\omega_0}{|\Delta \omega|}$$

$|\Delta \omega|$: band width

$$\omega_2 - \omega_1 = |\Delta \omega|$$


$$Q = \frac{\omega_0}{|\Delta \omega|}$$

$$I_0 = \frac{V_0}{R}$$

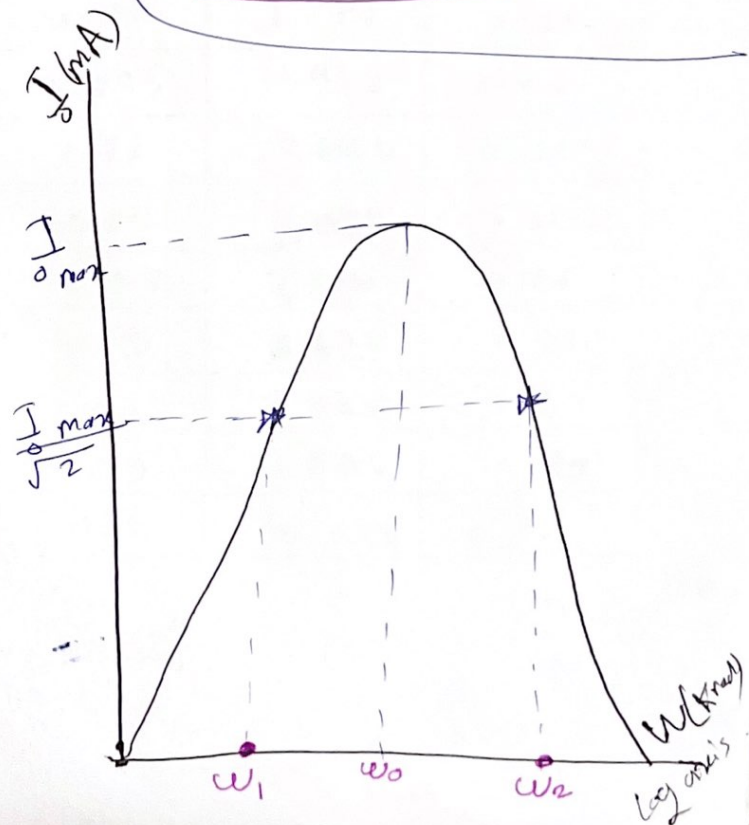

Exp #10 Filters

Low-pass filter

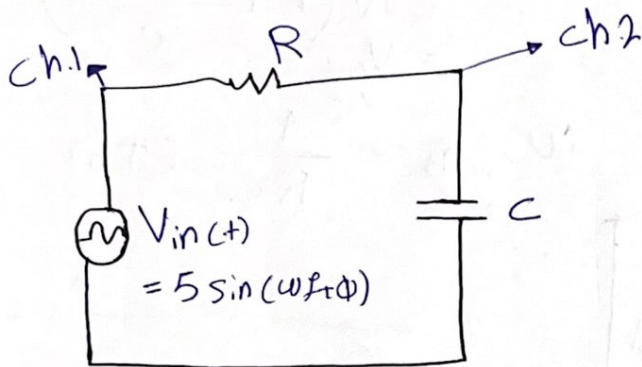

$$V(t) = V_c(t) = \frac{V_{in}(t)}{1 + j\omega RC}$$

$$\omega = 2\pi f$$

$$j = \sqrt{-1} \rightarrow \text{complex number}$$


Amplitude

$$V_{co}(t) = \frac{V_{ino}}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\frac{1}{RC} = \omega_{-3dB}$$


A: A Heruof ein factor
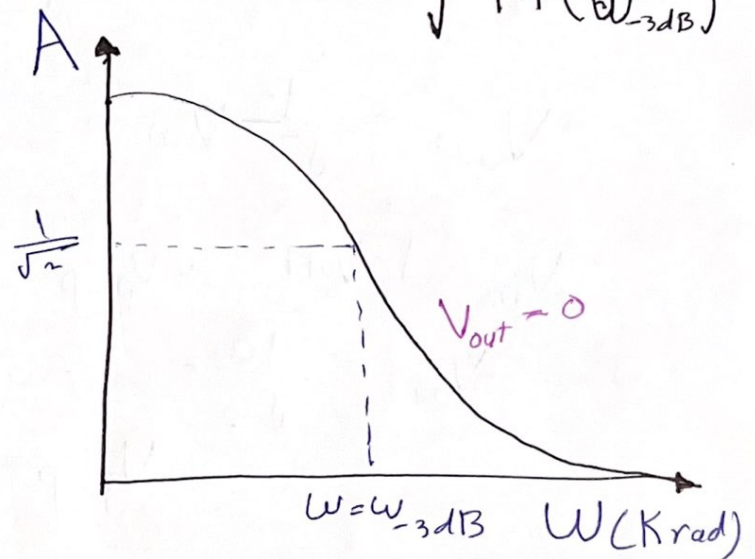
$$A = \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_{-3dB}}\right)^2}}$$



$$\omega \ll \omega_{-3dB} \quad \boxed{V_{out} = V_{in}}$$


High-pass filters

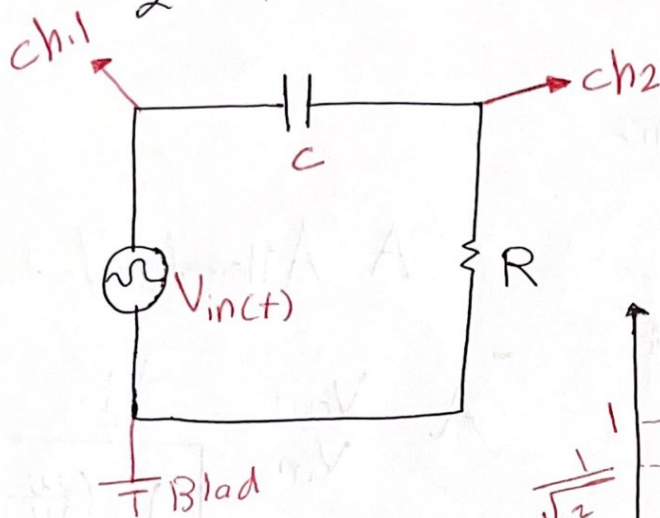

$$A = \frac{1}{\sqrt{\left(1 + \frac{\omega_{-3dB}}{\omega}\right)^2}}$$

$$= \frac{V_{out}}{V_{in}}$$
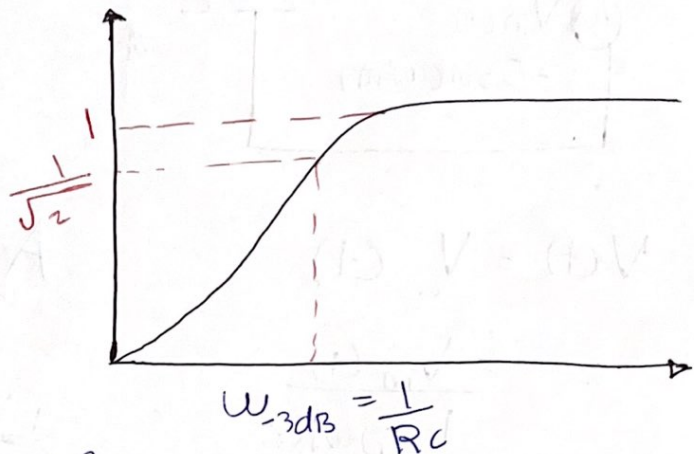
$$\omega_{-3dB} = \frac{1}{RC} \text{ (Th)}$$




$$V_{out} = \frac{1}{\sqrt{2}} V_{in}$$

$$V_{in} = 10 \text{ Volt} \rightarrow V_{p-p} = 20$$

$$V_{out} = \frac{10}{\sqrt{2}} = 7.07 \text{ Volt}$$

$$V_{p-p} = 14$$

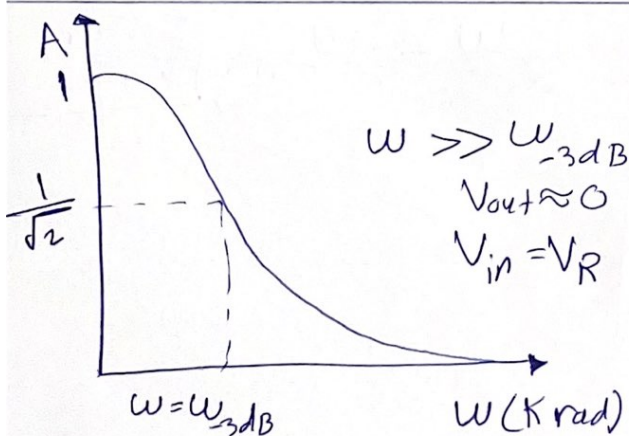
$$f_{-3dB} = \omega_{-3dB} = 2\pi f_{-3dB}$$



$$\omega \gg \omega_{-3dB}$$

$$V_{out} \approx 0$$

$$V_{in} = V_R$$

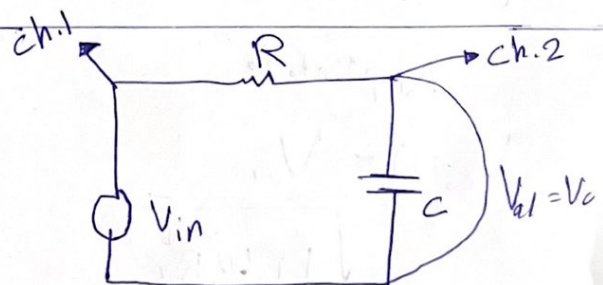

$$V_{out} = V_c = \frac{Q}{C}$$

$$I(t) = \frac{dQ}{dt}$$

$$Q(t) = \int I(t) dt$$

$$V_{out} = V_c = \frac{Q}{C}$$

$$= \frac{1}{C} \int I(t) dt \times \frac{R}{R}$$

$$\frac{1}{RC} \int \frac{RI(t) dt}{VR}$$