

• Testing of digital circuits :

→ 2 approaches for testing

a. Functional testing " exhaustive testing "

b. Structural testing " non-exhaustive testing "

* In exhaustive testing with " 1 GHz " speed of testing cpu,

→ For example

if the circuit has 32 inputs :

$2^{32} = 4 \times 10^9$, then we need "4 sec".

↳ Combination, or test vector, or test patterns.

** IF the circuit has 64 input

→ 2^{64} test vector \approx 585 year, using 1 GHz speed

(1 GHz = 10^9)


* Basic testing procedure :

- Apply test input to the input of the circuit

- Observe the output as compare then with expected values

Ex: Half Adder

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

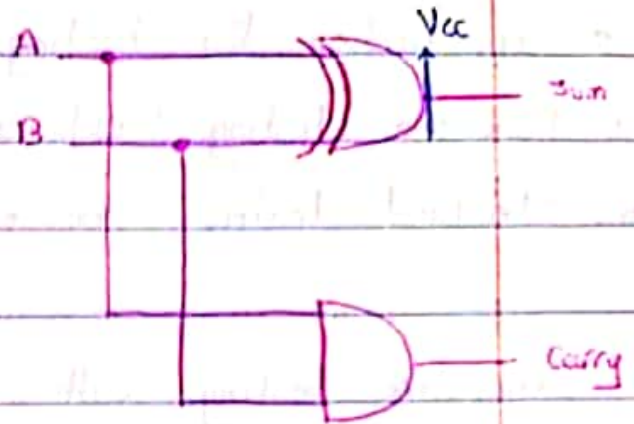

⇒ Assume the sum is short circuited with Vcc


A	B	Sum	Carry
0	0	1	0
0	1	1	0
1	0	1	0
1	1	1	1

⇒

IF A & B : 01 or 10 , has no effect , we should use 11 or 00

∴

Sum/Vcc →	A	B	Carry/Vcc →	A	B
	0	0		0	0
	1	1		0	1
				1	0

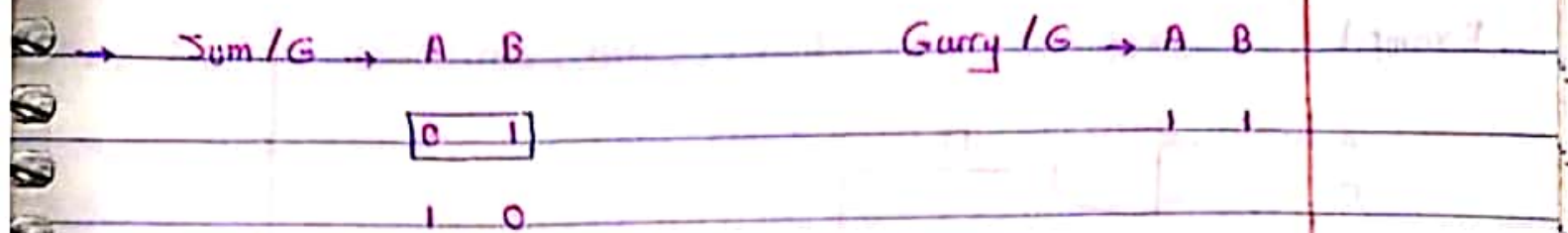

We should choose:

1. 11, "Sum/Vcc, Carry/G"
2. 01, "Sum/G, Carry/Vcc"

Fault modeling:

most common is the signal stuck at faults

1. Node is short circuited with Vcc \rightarrow "s-a-1, S₀₁"
2. Node is short circuited with ground \rightarrow "s-a-0, S₀₀"


Path Sensitization method (2. Value logic):

procedure \Rightarrow

For each node in the circuits

- a. Backtrace phase: drive the node to the non-fault condition
- b. Propagation phase: Steave the constant of the node to an output where we can compare.

Example:

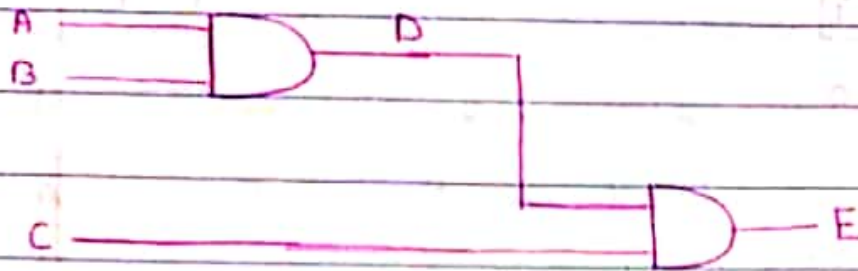

→ To test mod D:

* Assume D is 3-a-0

a. Backtrace: put 1 on mod D

→ $\overline{AB} = 11$, 1: Fault

0: not Fault

b. Propagation: C = 1

$\overline{ABC} = 111$, if E = 0 → Faulty

if E = 1 → not Faulty

* Assume D is 3-a-1

a. Backtrace: put 0 on mod D

→ $\overline{AB} = 00, 01, 10$

b. Propagation: C = 1


AI QUAD CAMERA

$\overline{ABC} = 001, 011, 101$ if $E = 1 \rightarrow$ Faulty
 if $E = 0 \rightarrow$ Fault-Free

Fault	Test Vector \overline{ABC}	Fault Free	Faulty
A-Stuck	011	0	1
B-Stuck	101	0	1
C-Stuck	110	0	1
D-Stuck	001, 011, 101	0	1
E-Stuck	000, 001, 100, 011, 101, 110, 010	0	1
A-Stuck0	111	1	0
B-Stuck0	111	1	0
C-Stuck0	111	1	0
D-Stuck0	111	1	0
E-Stuck0	111	1	0

* 4. Test Vector $\rightarrow 111, 011, 101, 110$ (100%).

* Example :

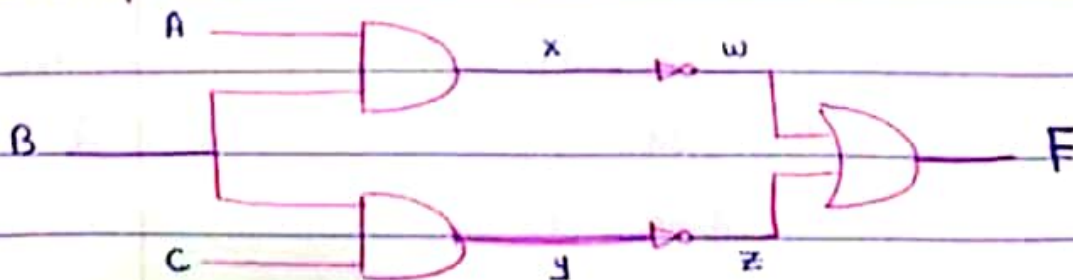

a. Backtrace : Assume B = 1

→ put 0 on B → 0 : if no fault

1 : if faulty

$A = 1, z = 0 \Rightarrow y = 1, \overline{BC} = 1$

$B = 1$

∴ Contradiction

b. Propagate : nod w to output F




REDMI NOTE 9S
AI QUAD CAMERA

* D-Algorithm (5-value logic)

→ 5-Values

- 1). 1 : Normal logic 1
- 2). 0 : Normal logic 0
- 3). X : Unknown
- 4). D : represent "1" under fault "3" condition, and "0" under faulty condition.
- 5). \bar{D} : represent logic "0" under fault "3" condition, and "1" under faulty condition.

* Example :

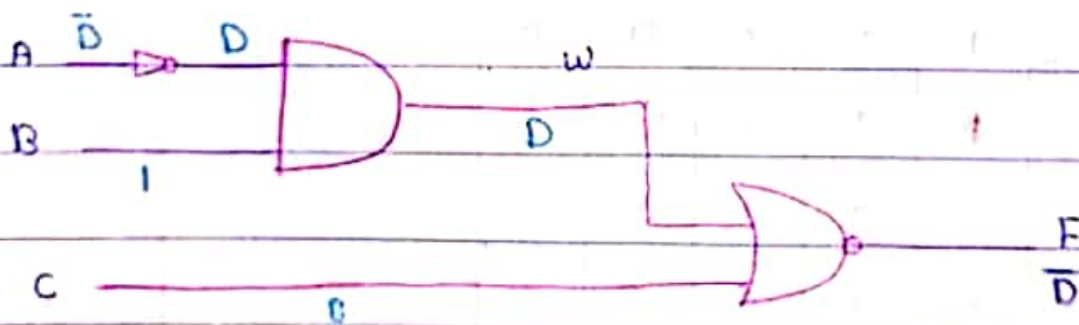

Test A fail ⇒

put 0 in A ($A = \bar{D}$)

A B C → if $F = 0$ No fault

0 1 0 $F = 1$ Fault

** Operation on 5-Value-logic:

1. Invert (Not) $\rightarrow Z = \bar{A}$

A	Z
0	1
1	0
D	\bar{D}
X	X
\bar{D}	D


2. AND $\rightarrow Z = A \cdot B$

A \ B	1	0	X	D	\bar{D}
1	1	0	X	D	\bar{D}
0	0	0	0	0	0
X	X	0	X	X	X
D	D	0	X	D	0
\bar{D}	\bar{D}	0	X	0	\bar{D}

3. OR $\rightarrow Z = A + B$

$B \backslash A$	0	1	x	D	\bar{D}
0	0	1	x	D	\bar{D}
1	1	1	1	1	1
x	x	1	x	x	x
D	D	1	x	D	1
\bar{D}	\bar{D}	1	x	1	D

* Example :

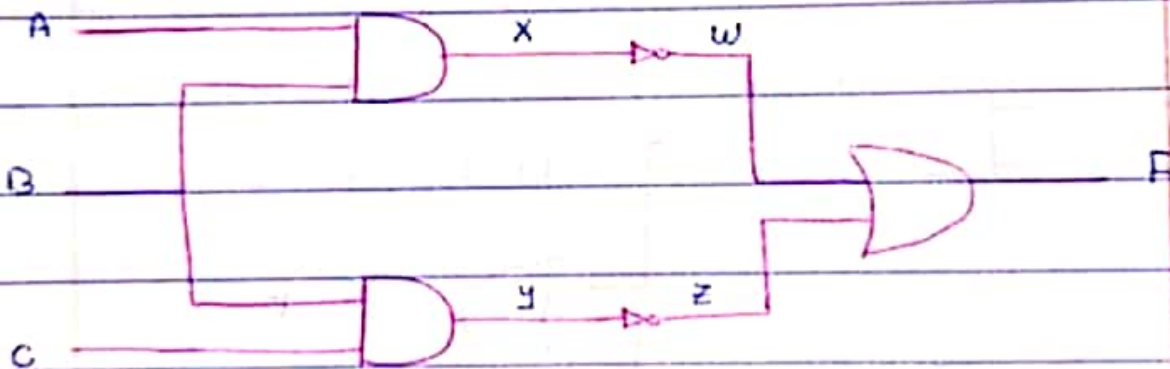

To test B s.a.1:

put 0 on B $\rightarrow B = \bar{D}$

Use both (BXWF)

$A=1 \rightarrow X=\bar{D} \rightarrow W=D$

propagate from w to F $\rightarrow Z=0 \rightarrow y=1$

then $\overline{BC} = 11$

Change the value of B.

• Use path $ByzF$: will fail (symmetry)

• Try path $BxwF$ and $ByzF$ together

put 0 on B $\rightarrow B = \bar{D}$


$A = 1 \rightarrow x = \bar{D} \rightarrow w = D \rightarrow F = D$

$C = 1 \rightarrow y = \bar{D} \rightarrow w = D$

• Test vector $ABC = 101$: if $F = 1 \rightarrow$ no fault

$F = 0 \rightarrow$ fault

* Example :

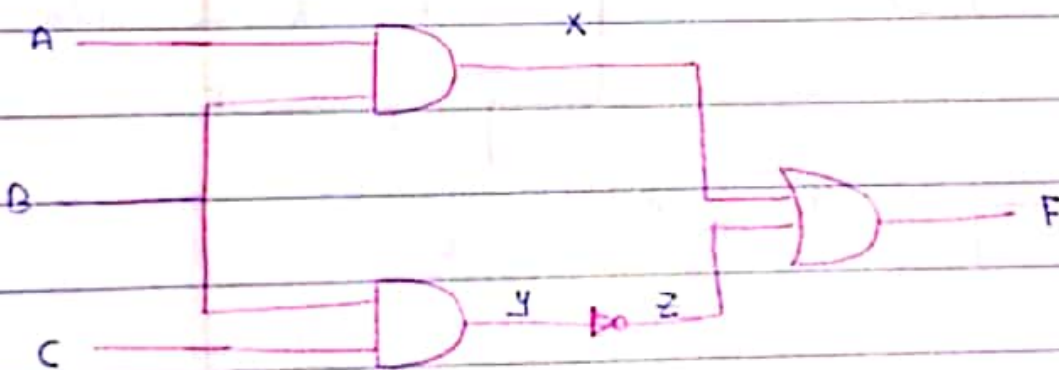

* Test B = 0

• path BxF and $ByzF$ together

put 1 on B $\rightarrow B = D$

$A = 1 \rightarrow x = D \rightarrow F = D \cdot 1 = D$, "False"

$C = 1 \rightarrow y = D \rightarrow z = \bar{D}$

• Try path Bx F :

put 1 on B $\rightarrow B = D$

$A = 1 \rightarrow x = D$

to propagate from nod x to output F

$\rightarrow Z = 0 \rightarrow y = 1 \rightarrow \overline{BC} = 11$

\therefore Contradiction . path fail

• Try path Byz F :

put 1 on B $\rightarrow B = D$

$C = 1 \rightarrow y = D \rightarrow \overline{Z} = \overline{D} \rightarrow \boxed{F = \overline{D}}$

propagate from nod Z to output F $x = 0$

$AB = 00, 01, 10 \rightarrow AB = 01$

Test vector ABC = 011




REDACTED = 50

Arabic

* Fault Collapsing :

2- Concept :

1). Fault equivalence

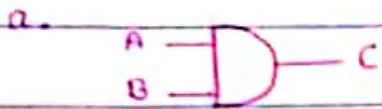

$$A \text{ } \overline{0}a0 \equiv B \text{ } \overline{0}a0 \equiv C \text{ } \overline{0}a0$$

$$AB = 11 \quad AB = 11 \quad AB = 11$$



$$A \text{ } \overline{0}a0 \equiv B \text{ } \overline{0}a0 \equiv C \text{ } \overline{0}a1$$

$$11 \quad 11 \quad 00$$



$$A \text{ } \overline{0}a1 \equiv B \text{ } \overline{0}a1 \equiv C \text{ } \overline{0}a1$$

$$00 \quad 00 \quad 00$$



$$A \text{ } \overline{0}a1 \equiv B \text{ } \overline{0}a1 \equiv C \text{ } \overline{0}a0$$

c. $A \rightarrow B$

$$A \supseteq 0 \equiv B \supseteq 1$$

$$A \supseteq 1 \equiv B \supseteq 0$$

2). Fault dominance

F_1 is said to dominate F_2 if the test vector for F_2 are subset of the test vector of F_1 .



A sat

B sat

C sat

A B

A B

~~A B~~

0 1

1 0

~~0 0~~

~~0 1~~

~~1 0~~

\therefore C sat dominates A sat

dominates B sat



A sat

B sat

~~C sat~~

A B

A B


~~A B~~

1 0

0 1

~~0 1, 1 0, 1 1~~

* Example :

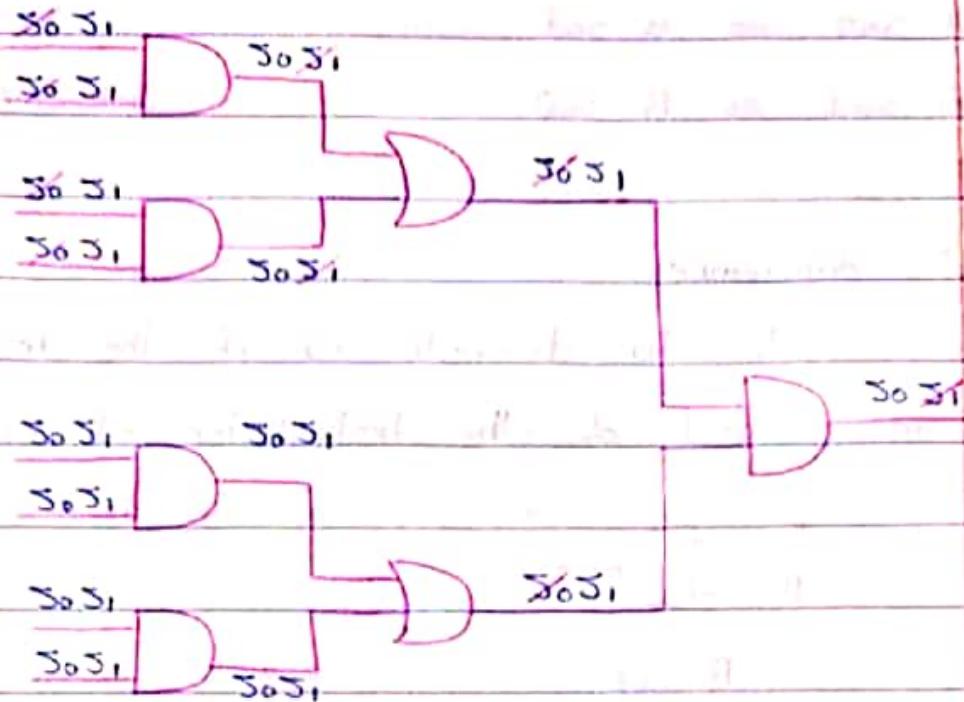

1). Exclusive test


8 input $\rightarrow 2^8 = 256$ test vector

2). Using fault model $\rightarrow 15 \text{ nodes} \times 2 = 30$

max 30 test vector


3). Use fault collapsing \rightarrow max 15

* Boolean Difference

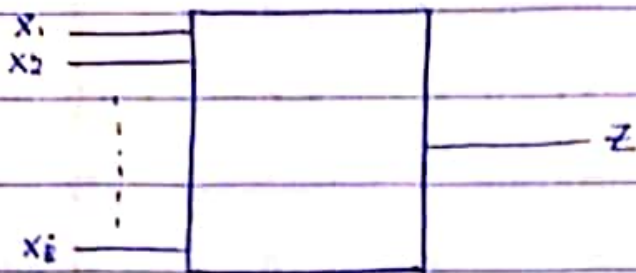

$$\frac{dz}{dx_i} = F(x_i=0) \oplus F(x_i=1)$$

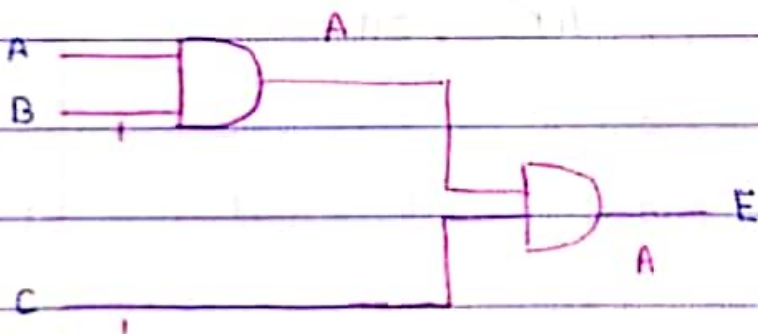z is sensitive to x_i when $\frac{dz}{dx_i} = 1$



When E is sensitive to A

$$E = F(A, B, C) = A.B.C$$

$$\frac{\partial E}{\partial A} = F(A=0) \oplus F(A=1)$$

$$= 0 \oplus B.C$$

$$= B.C$$

$\rightarrow E$ is sensitive to A when $\frac{\partial E}{\partial A} = 1$ ($BC=1$)

$$\overline{BC} = 0$$



REDNOTE4S
AI QUAD CAMERA

• To test x_i $\rightarrow 0$

$$x_i \cdot \frac{\partial z}{\partial x_i} = 1$$

• To test x_i $\rightarrow 1$

$$(x_i)' \cdot \frac{\partial z}{\partial x_i} = 1$$

$\therefore A \rightarrow 0$

$$A \cdot \frac{\partial E}{\partial A} = 1$$

$$A \cdot (BC) = 1$$

$$\overline{ABC} = 111$$


$(A) \rightarrow 1$

$$(A') \cdot \frac{\partial E}{\partial A} = 1$$

$$(A') \cdot (BC) = 1$$

$$\overline{ABC} = 011$$

* Example :

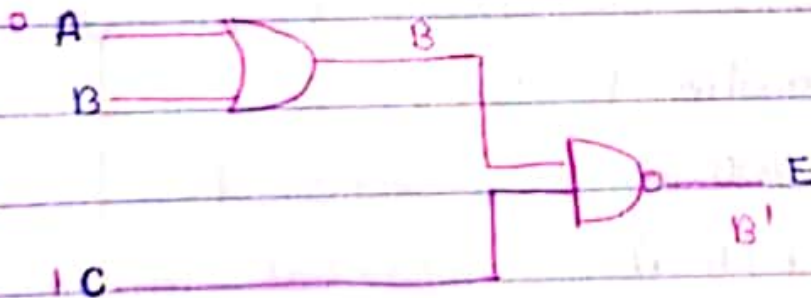

→ To test node B

E sensitive to B when $AC = 01$

$$\rightarrow E = [(A+B) \cdot C]'$$

$$\frac{\partial E}{\partial B} = F(B=0) \oplus F(B=1)$$

$$= (A \cdot C)' \oplus (C)'$$

A	B	$(A.C)'$	C'	$\frac{\partial E}{\partial B}$
0	0	1	1	0
0	1	1	0	1
1	0	1	1	0
1	1	0	0	0



E sensitive to B where $\frac{\partial E}{\partial B} = 1 \rightarrow AC = 01$

A	C	$(A.C)'$	C'	$(A.C)' \oplus C'$
0	0	1	1	0
0	1	1	0	1
1	0	1	1	0
1	1	1	0	0

E sensitive to B when $\frac{\partial E}{\partial B} = 1$
 → $AC = 01$

$$\begin{aligned}
 (A.C)' \oplus C' &= (A.C)' \cdot C + \cancel{(A.C)'} \cdot \cancel{C'}^0 \\
 &= (A.C)' \cdot C \\
 &= (A' + C') \cdot C \\
 &= A'C + \cancel{C'C}^0 \\
 &= A'C \stackrel{?}{=} 1 \quad "AC = 01" \rightarrow
 \end{aligned}$$

• Test B = 0

$$B \cdot \frac{dF}{dB} = 1$$

$$B \cdot A'C = 1$$


$$\overline{ABC} = 011$$

• Test B = 1

$$B' \cdot A'C = 1$$

$$\overline{ABC} = 001$$

* Example

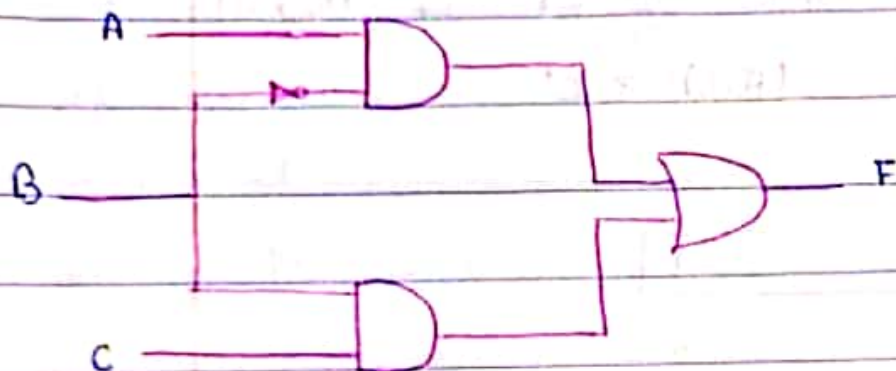

* To test node B

$$F = AB' + BC$$

$$\frac{dF}{dB} = F(B=0) \oplus F(B=1)$$

$$= A \oplus C$$

F is sensitive to B where $\frac{dF}{dB} = 1 \Rightarrow A \oplus C = 1$

$$\therefore AC$$

$$01$$

$$10$$

B 3a.0

$$B \cdot (A \oplus C) = 1$$

A B C

0 1 1

1 1 0

B 3a.1

$$B' \cdot (A \oplus C) = 1$$

A B C

0 0 1

1 0 0

* To test mod x

$$F = x \cdot B \cdot C$$

$$\frac{dF}{dx} = F(x,0) \oplus F(x,1)$$

$$B \cdot C \oplus 1$$

$$(BC)'$$

F is sensitive to x when $(BC)' = 1$

BC = 00, 01, 10

$$(AB') \cdot (BC)' = 1$$

A	B	C	AB'	$(BC)'$	$(AB') \cdot (BC)'$
0	0	0	0	1	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	0	0

$$\overline{ABC} = 100, 101$$

$$QB : (AB') \cdot (BC)' = 1$$

$$= AB' \cdot (B' + C')$$

$$= AB' + AB'C'$$

$$= AB' (1 + C')$$

$$= AB' = 1$$

$$\rightarrow AB = 10, \therefore C = X \text{ "Don't care"}$$

$$ABC = 100 \rightarrow ABC = 101 \rightarrow$$

* Example :



$$\rightarrow \frac{\partial F}{\partial X} = F(X=0) \oplus F(X=1)$$

$$= 1 \oplus 0 = 1$$

* Example :



$$F = X \cdot X' = 0$$


$$\frac{\partial F}{\partial X} = F(X=0) \oplus F(X=1)$$

$$= 0 \oplus 0 = 0, \text{ impossible}$$

Untestable Faults

- Completely untestable nodes
- Partially untestable nodes

A). Completely untestable faults

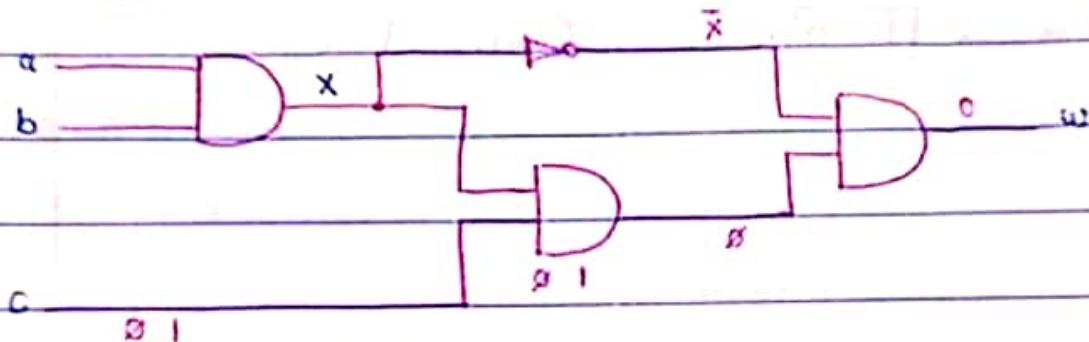

→ node x is completely untestable


1). $x = 0$ untestable x

2). $x = 1$ untestable x

$$w = x \cdot c \cdot \bar{x} = 0$$

$$\frac{dw}{dx} = 0 \rightarrow \text{not sensitive}$$

B). Partially untestable faults

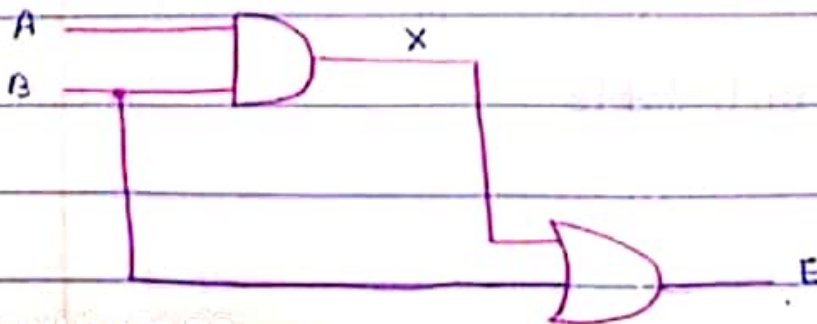

$$E = AB + B$$

$$X = a - 1$$

$$a. \text{ Backtrace} \rightarrow AB = X = \bar{D}$$

$$0 \ 0$$

$$\boxed{0 \ 1}$$

$$1 \ 0$$

$$b. \text{ Propagation} \rightarrow \boxed{B = 0} \quad \text{Contradiction}$$

→ test vector :

$$A \ B$$

$$0 \ 0$$

$$1 \ 0$$

$$X = a - D$$

$$A \ B, \quad X = D \rightarrow \text{"Backtrace"}$$

$$1 \quad \boxed{1}$$

Contradiction

$$B = \boxed{0} \rightarrow \text{"Propagation"}$$

∴ No test vector ∴ untestable



** Example : " Boolean difference "

$$E = AB + B$$

$$E = X + B$$

$$\frac{\partial E}{\partial x} = f(x=0) \oplus f(x=1)$$
$$= B \oplus 1 = B'$$

E is sensitive to x when

$$B' = 1 \rightarrow B = 0$$

X=0

$$x \cdot \frac{\partial E}{\partial x} \stackrel{?}{=} 1$$

$$A \cdot B \cdot B' \stackrel{?}{=} 1$$

$$0 \cdot ? \cdot 1$$

\therefore untestable

X=1

$$x' \cdot \frac{\partial E}{\partial x} \stackrel{?}{=} 1$$

$$(A \cdot B)' \cdot B' \stackrel{?}{=} 1$$

$$(A' + B') \cdot B' \stackrel{?}{=} 1$$

$$A' B' + B' = B' (1 + A')$$
$$= B'$$

Test vector $\rightarrow B' = 1$

$$B = 0$$

A B

(X) 0 \rightarrow 00

\downarrow
Don't Care \rightarrow 10