

Diode large signal application

Example

► Find the Q point



Using thevenin's theorem , the circuit is simplified to

$$R_{th} = 10k + 10k \parallel 20k = 16.7k$$


$$V_{th} = \frac{20k}{20k+10k} * 6 = 4V$$

since $V_{th} \geq V_k$, the diode is on

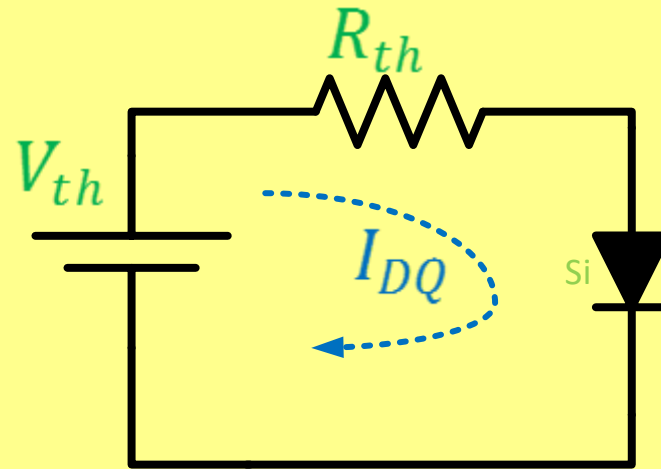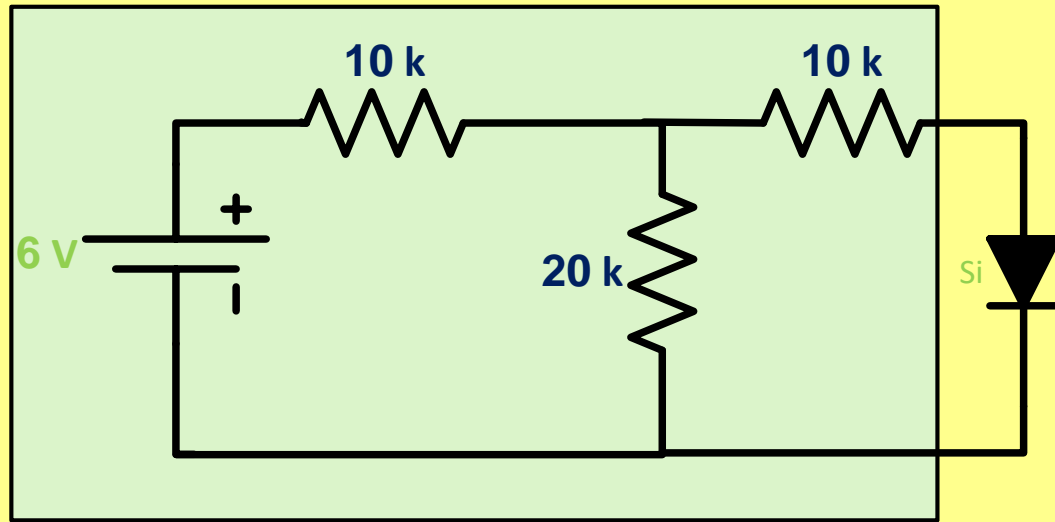since $V_{th} < 10 V_k$, we must use the knee voltage model




Knee voltage model

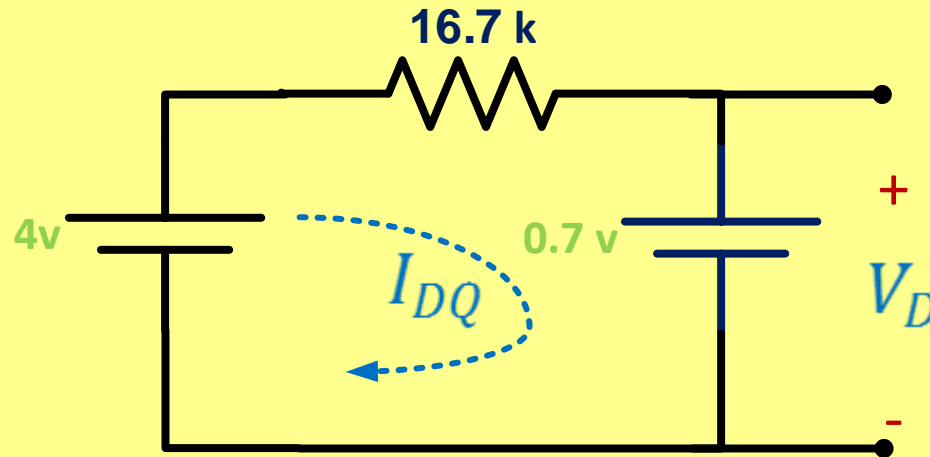

$$I_{DQ} = \frac{4 - 0.7}{16.7K} = 0.198 \text{ mA}$$

$$V_{DQ} = V_K = 0.7 \text{ V}$$

Second method

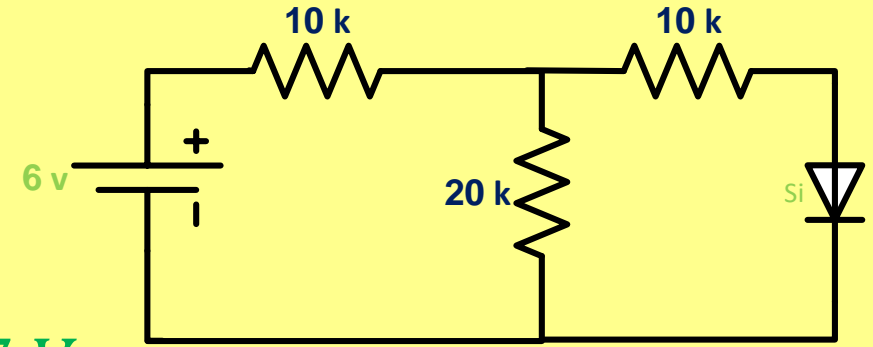

assume the diode is on , replace it with $V_K = 0.7 V$



KVL:


$$6 = 30 I_1 - 20 I_2$$

$$-0.7 = -20 I_1 + 30 I_2$$

Solve for:

$$I_2 = 0.198 \text{ mA}$$
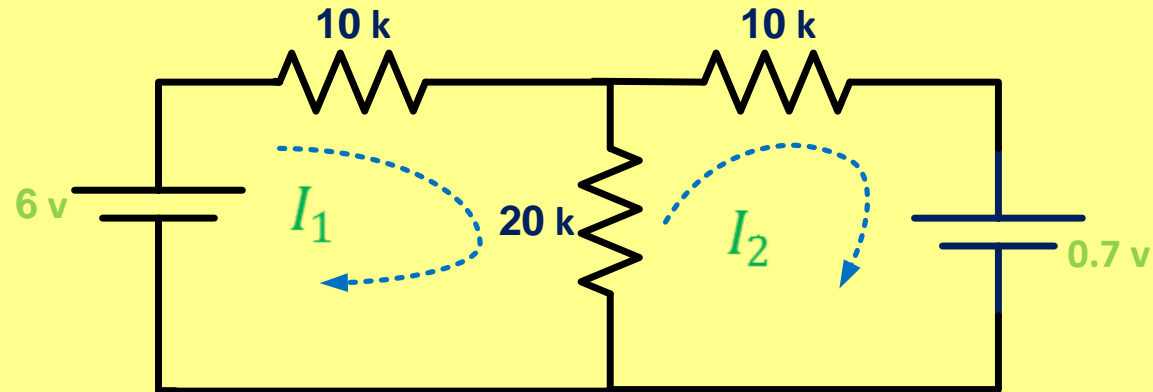
$$\therefore I_D = I_2 = 0.198 \text{ mA}$$



STUDENTS HUB.COM Since $I_D > 0$, \therefore our assumption is ok




Uploaded By: anonymous

Diode large - signal application

1) Diode clipper circuit

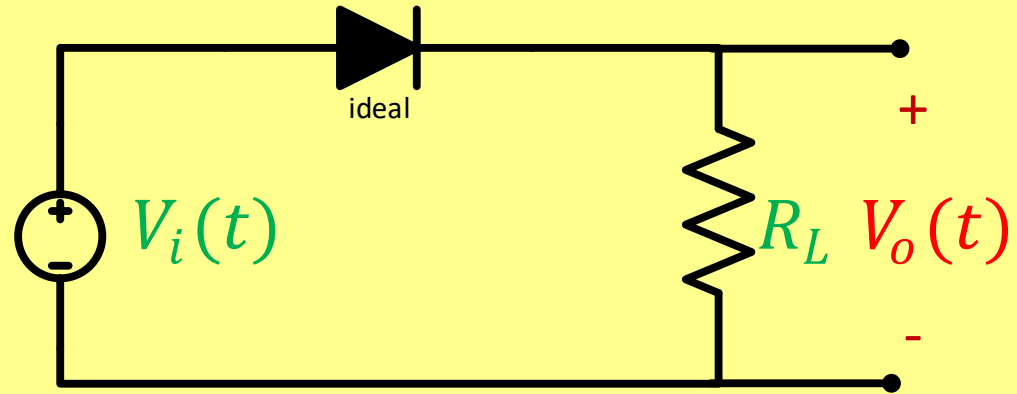
a) assume the diode is on
replace it with short circuit



$$i_D(t) > 0$$

$$i_D(t) = \frac{V_i(t)}{R_L} > 0$$

$$\therefore V_i(t) > 0$$

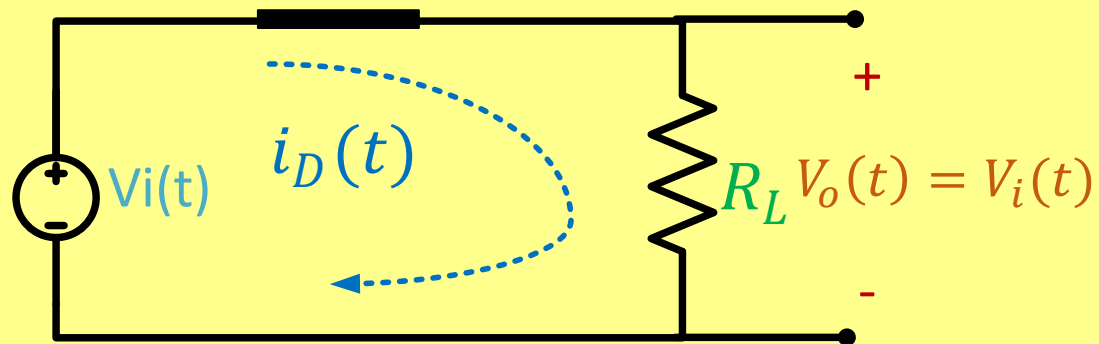


\therefore when $V_i(t) > 0$, the diode is on and $V_o(t) = V_i(t)$

\therefore when $V_i(t) < 0$, the diode is off and $V_o(t) = ?$.

\therefore when $V_i(t) < 0$, the diode is off

$$V_o(t) = 0.$$

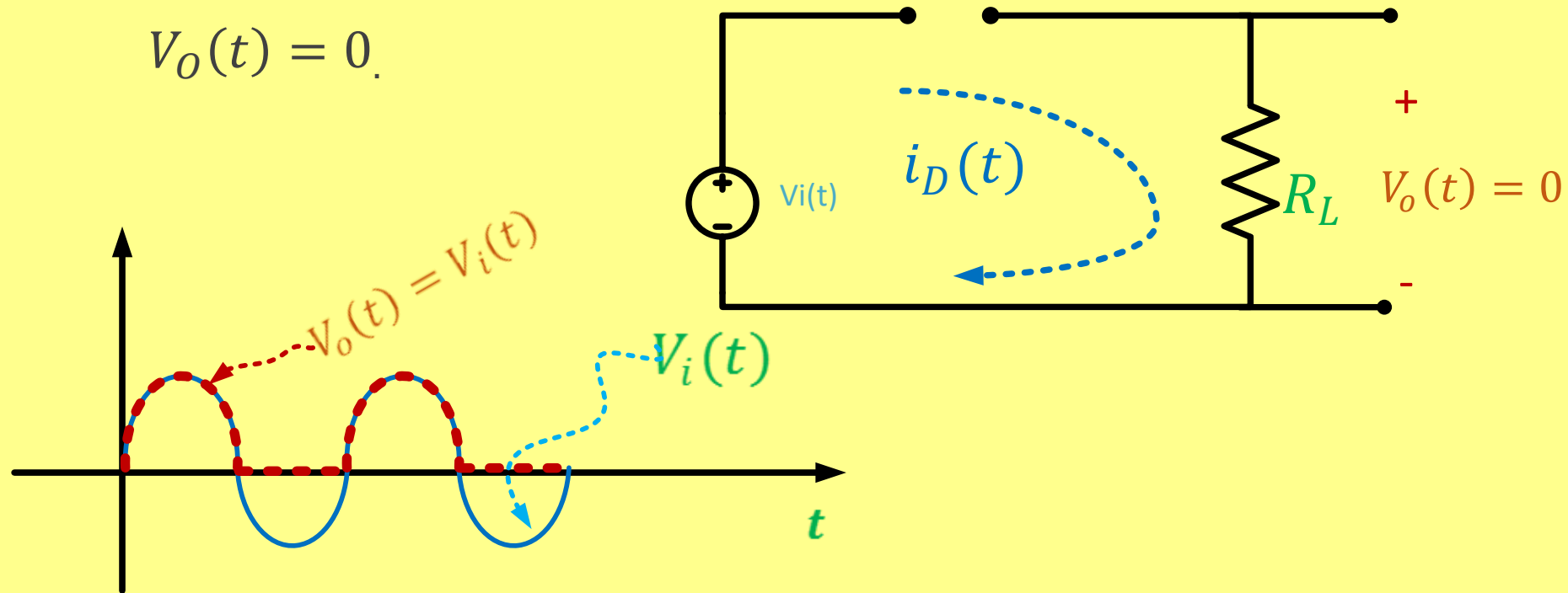

\therefore the clipper circuit used to eliminate portion of the input signal .




Example



- a) assume that the diode is on
- b) replace it with short circuit

$$V_o(t) = V_i - 10$$

c) $i_D(t) > 0$

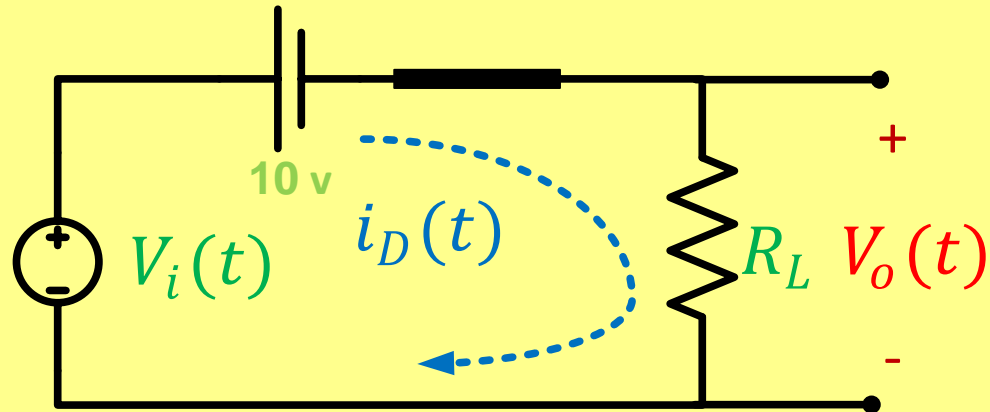

$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$

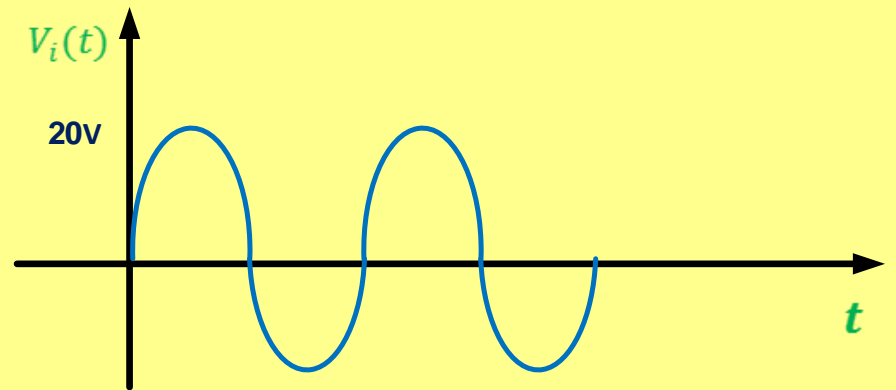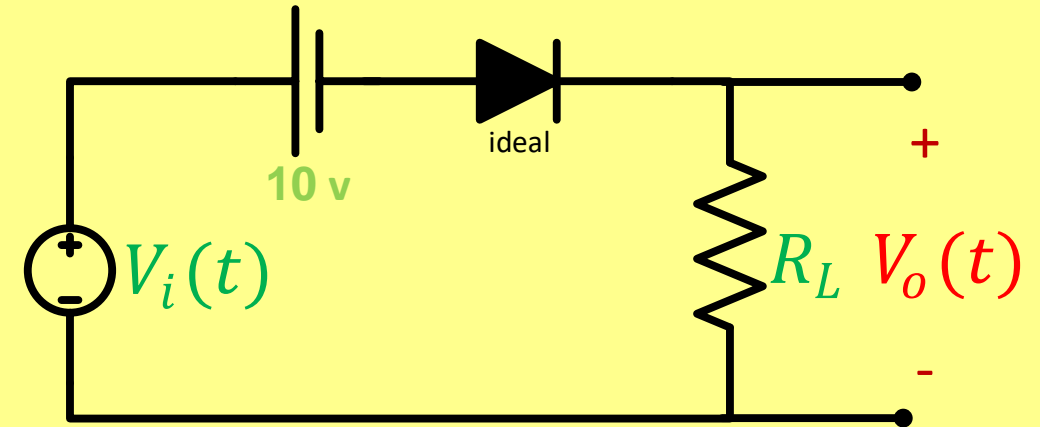

$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$


$$\therefore V_i(t) - 10 > 0$$

$$\therefore V_i(t) > 10$$


$$V_o(t) = V_i - 10$$


\therefore when $V_i(t) > 10 \text{ V}$, the diode is on and $V_o(t) = V_i - 10$

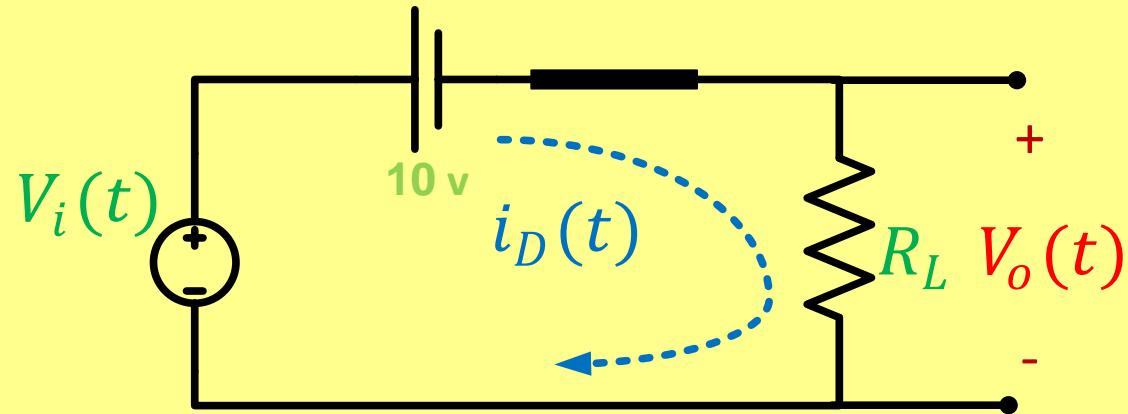and also we can prove that when $V_i(t) < 10 \text{ V}$, the diode is off





$$\therefore V_o(t) = 0$$

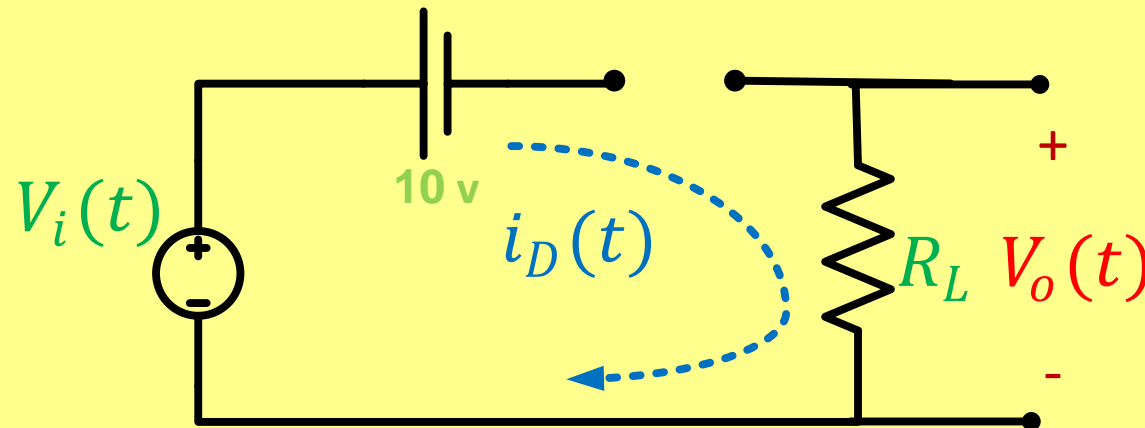

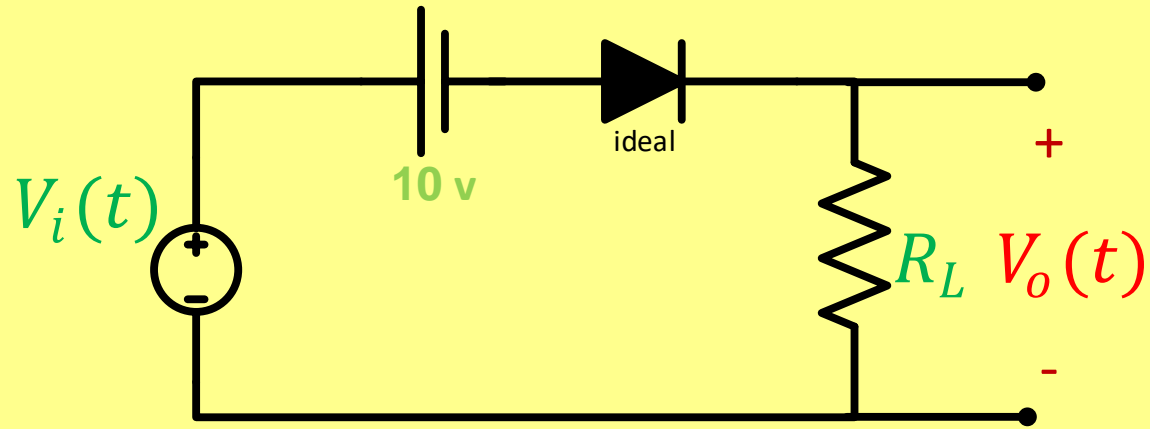



\therefore when $V_i(t) > 10 \text{ V}$, the diode is on and $V_o(t) = V_i - 10$

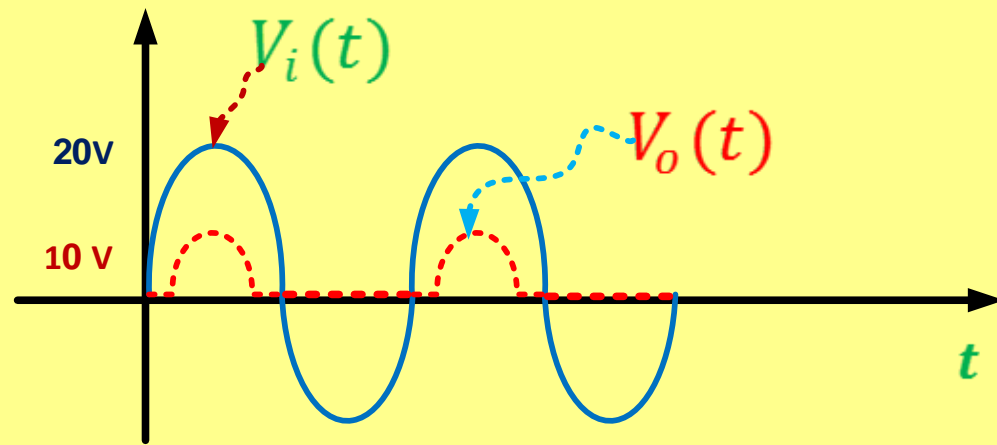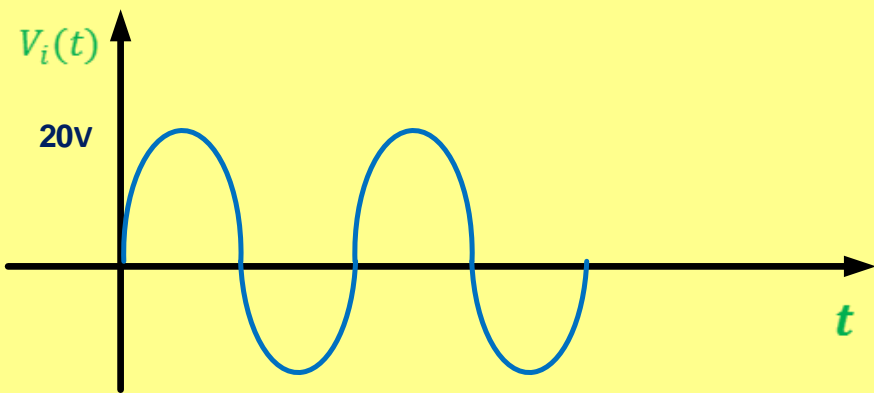\therefore when $V_i(t) < 10 \text{ V}$, the diode is off and $V_o(t) = 0$



Second method

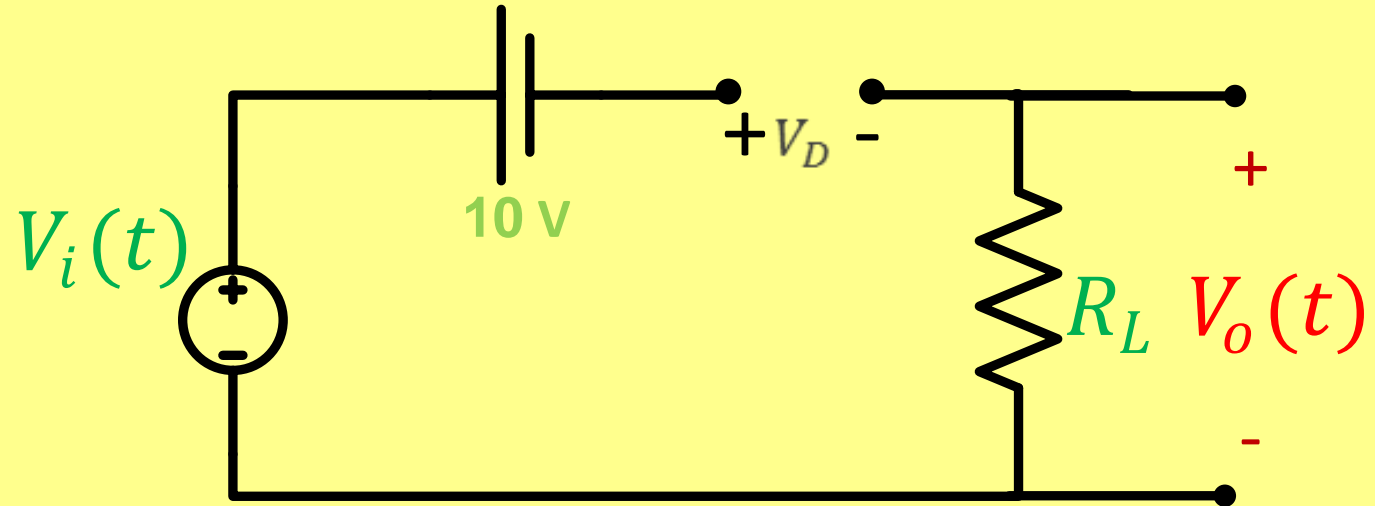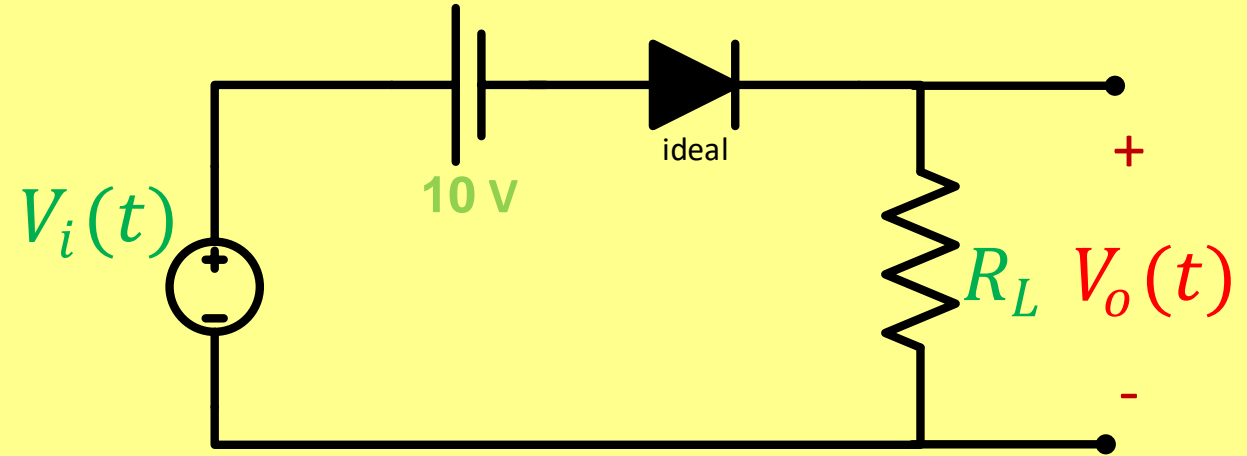- a) assume that the diode is off
- b) replace it with open circuit
- c) $V_D(t) < 0$.



$$V_D(t) = -10 + V_i$$

$$V_i(t) < 10 \text{ V}$$

\therefore when $V_i(t) < 10 \text{ V}$, the diode is off and $V_o(t) = 0$

