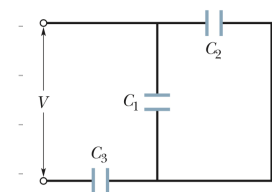


Q2



$$q_{12} = \frac{q_1}{C_1} + \frac{q_2}{C_2}$$

$$V = 75V, C_1 = 10\mu F, C_2 = 5\mu F, C_3 = 15\mu F$$

a) $q_3 = ?$ b) $V_3 = ?$ c) $U_3 = ?$ d) $q_1 = ?$ e) $V_1 = ?$ f) $U_1 = ?$ g) $q_2 = ?$ h) $V_2 = ?$ i) $U_2 = ?$

C_1 & C_3 are in parallel $\Rightarrow C_{12} \Rightarrow$

$$C_{12} = C_1 + C_3 = 10 + 5 = 15\mu F$$

C_{12} & C_2 are in series: $\Rightarrow q = q_{12} = q_3, V = V_{12} + V_3$

$$V_3 = \frac{q_3}{C_3} + \frac{q_3}{C_2} = \frac{q_3}{C_3} + \frac{q_3}{C_2} \Rightarrow V = q \left(\frac{1}{C_{12}} + \frac{1}{C_2} \right) \Rightarrow 75 = q \left(\frac{1}{15\mu F} + \frac{1}{5\mu F} \right) \Rightarrow 75 = \frac{2q}{15\mu F} \Rightarrow q_3 = 5.625 \times 10^{-4} C = q_{12} = q_1$$

Now find $U_3 \Rightarrow U_3 = \frac{q_3}{C_3} = \frac{5.625 \times 10^{-4}}{15 \times 10^{-6}} \Rightarrow U_3 = 37.5V \Rightarrow$ and $V = V_{12} + V_3$ so $75 = V_{12} + 37.5 \Rightarrow U_{12} = 37.5 \Rightarrow$ and $U_{12} = V_1 = V_2 = 37.5$

$U_3 \Rightarrow U_3 = \frac{1}{2} C_3 V_3^2 = \frac{1}{2} \times 15 \times 10^{-6} \times (37.5)^2 \Rightarrow U_3 \approx 0.01059 J$

Now find q_1 & $q_2 \Rightarrow V_{12} = V_1 = V_2 \Rightarrow \frac{q_{12}}{C_{12}} = \frac{q_1}{C_1} \Rightarrow \frac{5.625 \times 10^{-4}}{15 \times 10^{-6}} = \frac{q_1}{10 \times 10^{-6}} \Rightarrow q_1 = 3.75 \times 10^{-4} C$

$U_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} (10 \times 10^{-6}) (37.5)^2 \Rightarrow U_1 = 7.03125 \times 10^{-3} J$

$U_2 = \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (5 \times 10^{-6}) (37.5)^2 \Rightarrow U_2 = 3.515625 \times 10^{-3} J$

Q10

$A = 90 \text{ cm}^2, d = 1 \text{ mm}, V = 500 \text{ V}$

$\epsilon_r = 10^{-12}$

$\epsilon_r = 10^{-12} \text{ m}^2 \text{ إلى } \text{Cm}^2$

a) $C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12}) (90 \times 10^{-4})}{1 \times 10^{-3}} = 3.5 \times 10^{-4} F = 35 \mu F$

b) $q = CV = (35 \times 10^{-4}) (500) = 1.75 \times 10^{-2} C$

c) $U = \frac{1}{2} CV^2 = \frac{1}{2} (35 \times 10^{-4}) (500)^2 = 4.375 \times 10^{-2} J$

d) $V = Ed \Rightarrow E = \frac{V}{d} = \frac{500}{1 \times 10^{-3}} = 500,000 = 5 \times 10^5 \text{ V/m}$

e) $U = \frac{1}{2} \epsilon_0 E^2 = \frac{1}{2} (8.85 \times 10^{-12}) (5 \times 10^5)^2 = 1.10625 \text{ J/m}^3$

Q11

$C_0 = 8 \mu F, U = 3.2 \mu F, V = 350.8 \text{ V}$

$C = \frac{\epsilon_0 A}{d} \Rightarrow C = \frac{K \epsilon_0 A}{d} \Rightarrow \frac{C}{C_0} = K \Rightarrow$ so now we should find C before we find K

$U = \frac{1}{2} CV^2 \Rightarrow 3.2 \times 10^{-6} = \frac{1}{2} C (350.8)^2 \Rightarrow C = 62 \mu F$

$K = \frac{C}{C_0} = \frac{62 \times 10^{-6}}{8 \times 10^{-6}} = 7.75$

Q12

$C_0 = 21 \mu F = 21 \times 10^{-6} F, d_1 = 2d_2, C_1 = 2.6 \mu F = 2.6 \times 10^{-6} F$

$C = \frac{\epsilon_0 A}{d} \Rightarrow C = \frac{K \epsilon_0 A}{d}$

$\frac{C_0}{C} = \frac{\epsilon_0 A}{d} \div \frac{K \epsilon_0 A}{2d} \Rightarrow \frac{C_0}{C} = \frac{2}{K} \Rightarrow K = \frac{2C}{C_0} = \frac{2(2.6 \times 10^{-6})}{(21 \times 10^{-6})} = 2.476$

Q17

$A = 85 \text{ cm}^2, d = 8 \text{ mm}, V_i = 16 \text{ V}, d_2 = 3 \text{ mm}$

a) $E_i = E_f \Rightarrow \frac{V_i}{d_i} = \frac{V_f}{d_f} \Rightarrow V_f = \frac{V_i d_i}{d_f} = \frac{16(8 \times 10^{-3})}{3 \times 10^{-3}} = 64 \text{ V}$

b) $U_i = \frac{1}{2} CV_i^2$ so we have to find C :

$C = \frac{\epsilon_0 A}{d_i} = \frac{(8.85 \times 10^{-12}) (85 \times 10^{-4})}{8 \times 10^{-3}} = 9.403125 \times 10^{-13}$

$U_i = \frac{1}{2} CV_i^2 = \frac{1}{2} (9.403125 \times 10^{-13}) (16)^2 = 1.2036 \times 10^{-10} J$

c) $U_f = \frac{1}{2} CV_f^2$ so we have to find C :

$C = \frac{\epsilon_0 A}{d_f} = \frac{(8.85 \times 10^{-12}) (85 \times 10^{-4})}{3 \times 10^{-3}} = 2.5075 \times 10^{-12}$

$U_f = \frac{1}{2} CV_f^2 = \frac{1}{2} (2.5075 \times 10^{-12}) (64)^2 = 4.5135 \times 10^{-10} J$

d) $W = U_f - U_i = (4.5135 \times 10^{-4}) - (1.2036 \times 10^{-4}) = 3.3099 \times 10^{-4}$

Q18 $A = 5.56 \text{ cm}^2$, $d = 5.56 \text{ mm}$, $K_1 = 7$, $K_2 = 10$

من هنا يبقى الكا بتر متغيره هـ 2 كابتير متغيره على التوالي

Figure 25-23 Problem 18.

$$C_1 = \frac{K_1 \epsilon_0 A/2}{d} = \frac{K_1 \epsilon_0 A}{2d} = \frac{7(8.85 \times 10^{-12})(5.56 \times 10^{-4})}{2(5.56 \times 10^{-3})} = 3.0975 \times 10^{-12} \text{ F}$$

$$C_2 = \frac{K_2 \epsilon_0 A/2}{d} = \frac{K_2 \epsilon_0 A}{2d} = \frac{10(8.85 \times 10^{-12})(5.56 \times 10^{-4})}{2(5.56 \times 10^{-3})} = 4.425 \times 10^{-12} \text{ F}$$

وازي

$$C = C_1 + C_2 = 3.0975 \times 10^{-12} + 4.425 \times 10^{-12} = 7.5225 \times 10^{-12} \text{ F}$$

Q22 $A = 12.5 \text{ cm}^2$, $d = 7.12 \text{ mm}$, $K_1 = 21$, $K_2 = 42$, $K_3 = 58$

$$C_1 = \frac{K_1 \epsilon_0 A/2}{d} = \frac{K_1 \epsilon_0 A}{2d} = \frac{21(8.85 \times 10^{-12})(12.5 \times 10^{-4})}{2(7.12 \times 10^{-3})} = 1.63141 \times 10^{-11} \text{ F}$$

$$C_2 = \frac{K_2 \epsilon_0 A/2}{d} = \frac{K_2 \epsilon_0 A}{2d} = \frac{42(8.85 \times 10^{-12})(12.5 \times 10^{-4})}{2(7.12 \times 10^{-3})} = 6.52563 \times 10^{-11} \text{ F}$$


$$C_3 = \frac{K_3 \epsilon_0 A/2}{d} = \frac{K_3 \epsilon_0 A}{2d} = \frac{58(8.85 \times 10^{-12})(12.5 \times 10^{-4})}{2(7.12 \times 10^{-3})} = 9.01189 \times 10^{-11} \text{ F}$$

C_2 & C_3 in series:

$$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3} \Rightarrow \frac{1}{C_{23}} = \frac{C_2 + C_3}{C_2 C_3} \Rightarrow C_{23} = \frac{C_2 C_3}{C_2 + C_3} = \frac{(6.52563 \times 10^{-11})(9.01189 \times 10^{-11})}{(9.01189 \times 10^{-11}) + (6.52563 \times 10^{-11})} \approx 3.78487 \times 10^{-11} \text{ F}$$

C_{23} & C_1 are in parallel:
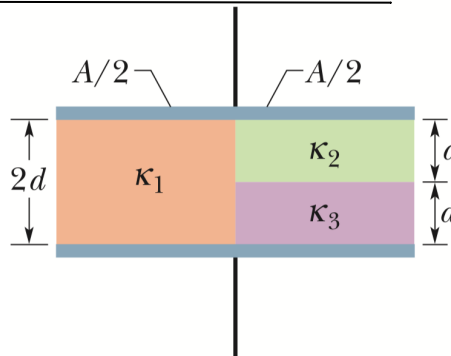
$$C_{\text{tot}} = C_{23} + C_1 = 3.78487 \times 10^{-11} + 1.63141 \times 10^{-11} \approx 5.41628 \times 10^{-11} \text{ F}$$



Q28 $C = 50 \text{ pF}$, $A = 0.3 \text{ m}^2$

a) $C = \frac{\epsilon_0 A}{d} \Rightarrow d = \frac{\epsilon_0 A}{C} = \frac{(8.85 \times 10^{-12})(0.3)}{(50 \times 10^{-12})} = 5.31 \times 10^{-2} \text{ m}$

b) $C = \frac{K \epsilon_0 A}{d} = \frac{(5.6)(8.85 \times 10^{-12})(0.3)}{(5.31 \times 10^{-2})} \approx 2.8 \times 10^{-10} \text{ F}$

Q39 $C_1 = 1 \text{ } \mu\text{F}$, $C_2 = 3 \text{ } \mu\text{F}$, for both $(C, C_1) \Rightarrow V = 200 \text{ V}$ (التي متساوية بالفولتية كما بالبرقية)

When switches S_1 and S_2 are closed, the potential differences across the capacitor are the same and the two capacitor are in parallel

a) $V_{ab} = \frac{q_{\text{net}}}{C_{\text{eq}}} \Rightarrow q = C V$ but we have to find C

$$C_{\text{eq}} = C_1 + C_2 = 1 + 3 = 4 \text{ } \mu\text{F} = 4 \times 10^{-6} \text{ F}$$

before the switch was closed

$$q_1 = C_1 V = (1 \times 10^{-6})(200) = 2 \times 10^{-4} \text{ C}$$

$$q_2 = C_2 V = (3 \times 10^{-6})(200) = 6 \times 10^{-4} \text{ C}$$

$$\text{So } q_{\text{net}} = q_1 + q_2 = (2 + 6) \times 10^{-4} = 8 \times 10^{-4} \text{ C}$$

$$V = \frac{q_{\text{net}}}{C_{\text{eq}}} = \frac{8 \times 10^{-4}}{4 \times 10^{-6}} = 200 \text{ V}$$

b) the charge on capacitor 1 is now $q_1 = C_1 V_{ab} = (1 \times 10^{-6})(100) = 1 \times 10^{-4} \text{ C}$

c) the charge on capacitor 2 is now $q_2 = C_2 V_{ab} = (3 \times 10^{-6})(100) = 3 \times 10^{-4} \text{ C}$

Q53 $C = 100 \text{ pF}$, $V_f = 80 \text{ V}$, $U_f = 35$

ومن ثم تم تحويله على الفولتية كما بالبرقية (التي متساوية بالفولتية كما بالبرقية) حيث انخفضت فوه الجهد عبر الكابيتور الى 35 V فما هي الطاقة؟

هـ الشحنة ينبغي مصغرة (يعني بهن بيلد بالناهي) الشحنة الكليته هلت من قبل

$$C \Rightarrow \text{الصنع قبل العملية هـ } q = C \cdot V_f = (100 \times 10^{-12})(80) = 8 \times 10^{-9} \text{ C}$$

$$C_1 \text{ في نفس فوه الجهد الكا باجل الثاني } q_1 = C_1 V_f = (100 \times 10^{-12})(35) = 3.5 \times 10^{-9}$$

$$\text{م 5} \Rightarrow C_2 = 12 \text{ pF} \Rightarrow C_1 V_f = (C_1 + C_2) V \Rightarrow (100 \times 10^{-12})(80) = ((100 \times 10^{-12}) + C_2)(35) \Rightarrow C_2 = 12 \text{ pF}$$