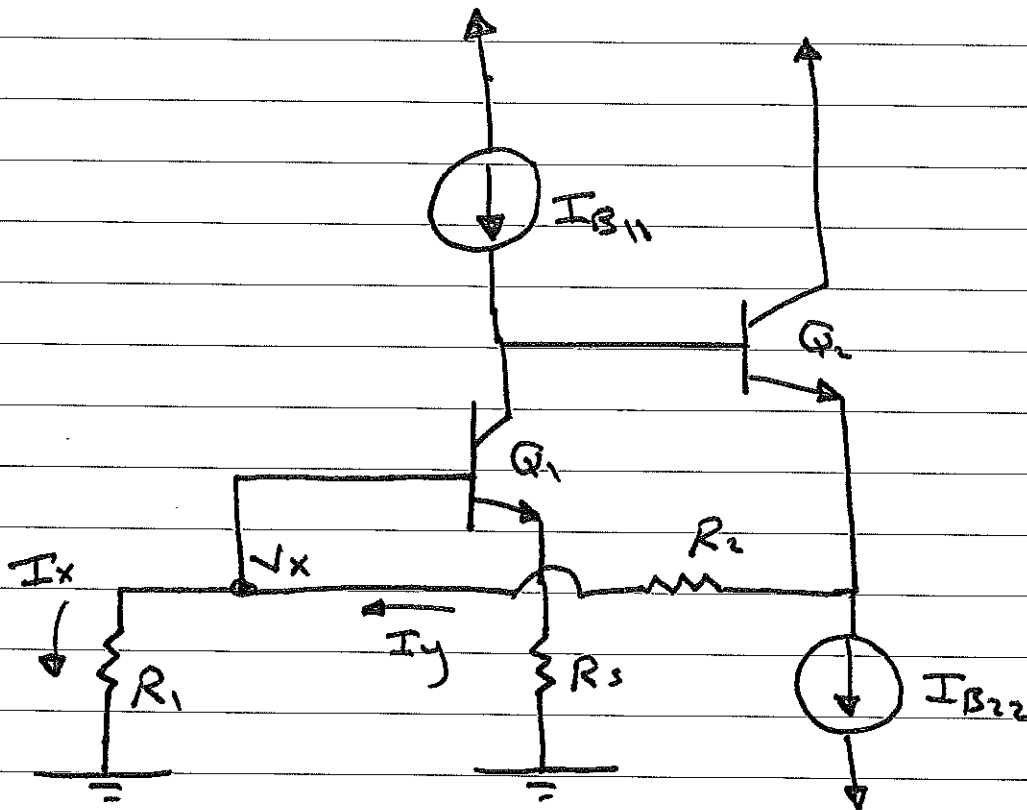


8.32

Dc Analysis :



$$I_{B11} = I_{C1} + I_{B2}$$

$$I_y = I_x + I_{B1} = I_{E2} - I_{B22}$$


$$I_x = \frac{V_x}{R_1}$$

$$V_x = V_{BE1} + R_s I_{E1}$$

$$\therefore I_{E2} = 1.708 \text{ mA}$$


$$I_{E1} = 83.08 \mu\text{A}$$

Ac small Signal Equivalent CKT

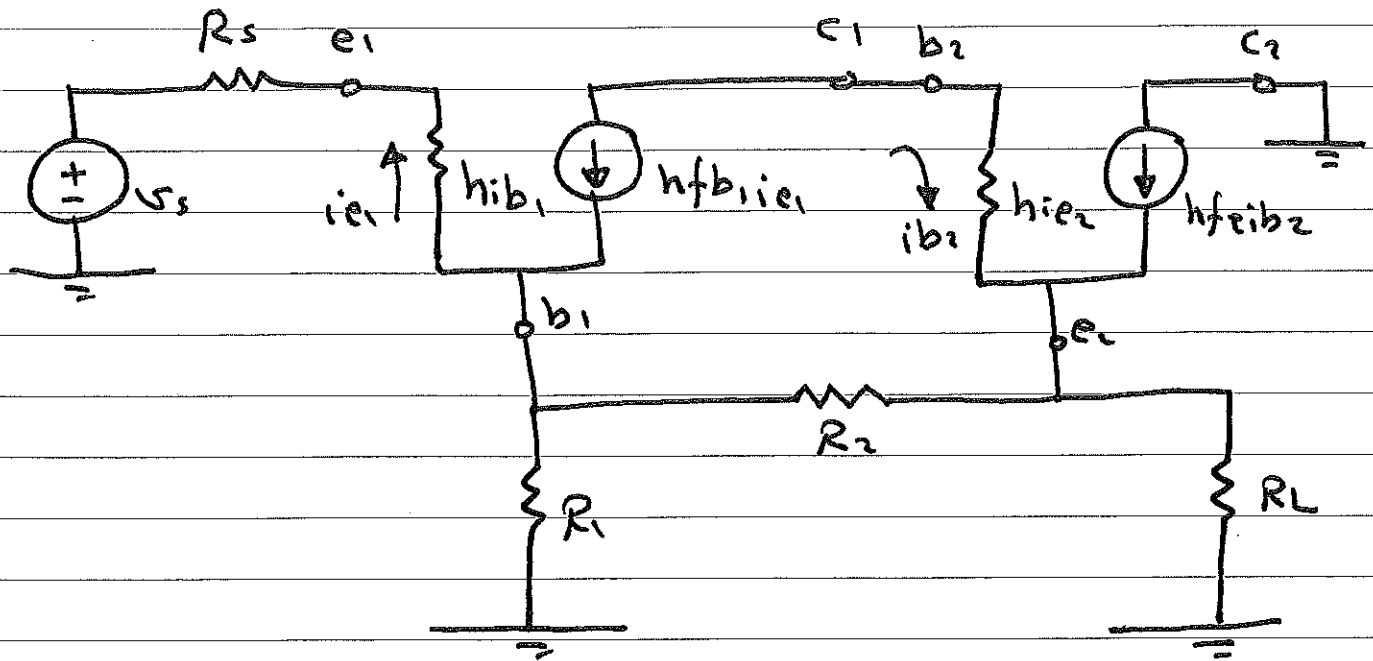

Series-shunt feedback

The feedback network :

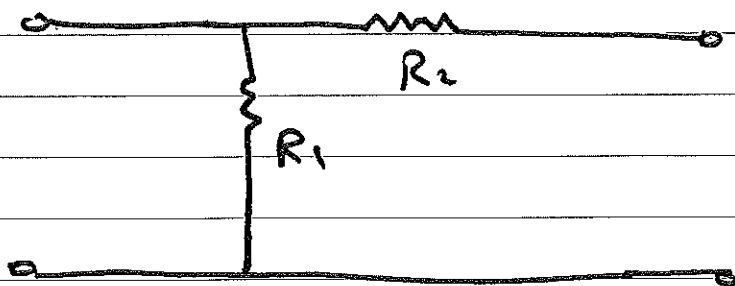


$$h_{if} = R_1 \parallel R_2 = 0.91 \text{ k}\Omega$$

$$h_{22f} = \frac{1}{R_1 + R_2} = 0.091 \text{ mS}$$

$$h_{12f} = \frac{R_1}{R_1 + R_2} = 0.091$$

$$\therefore \beta = 0.091$$

The new basic amplifier

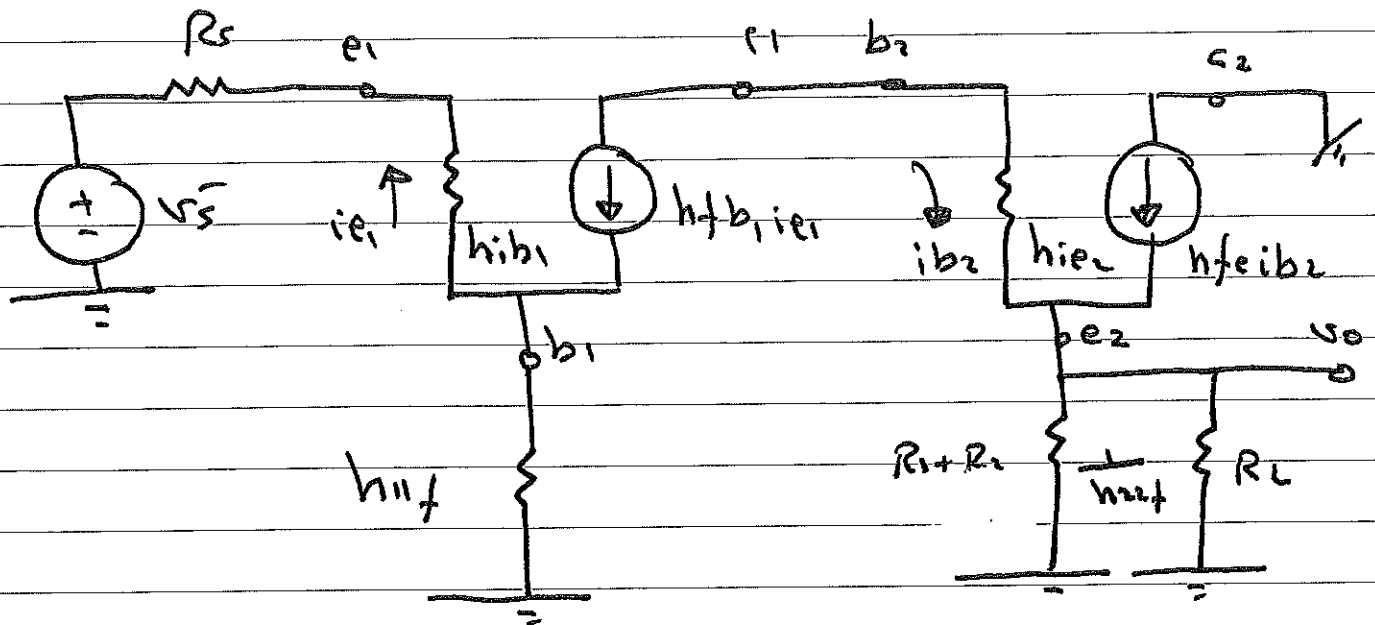

$$h_{ib1} = \frac{\sqrt{I}}{I_{E1}} = 309.2 \Omega$$

$$A = \frac{V_o}{V_s}$$

$$V_o = (1k \parallel 11k) i_{e2}$$

$$i_{e2} = (h_{fe} + 1) i_{b2}$$

$$i_{b2} = -h_{fb} i_{e1}$$

$$i_{e1} = \frac{-V_s}{R_s + h_{ib1} + \frac{h_{uf}}{h_{fe} + 1}}$$

$$\therefore A = 219.57$$

$$AB = 19.98$$

$$A_f = \frac{A}{1 + AB} = 10.46 ; \frac{1}{\beta} = 11$$

$$Z_{if} = R_i (1 + AB)$$

$$R_i = h_{ib1} + R_s + \frac{h_{mf}}{h_{fe} + 1} = 418 \Omega$$

$$\therefore Z_{if} = 8.77 \text{ K} \Omega$$

$$Z_{if} = R_s + R_{in}$$

$$\therefore R_{in} = 8.67 \text{ K} \Omega$$

$$Z_{of} = \frac{R_o}{1 + AB}$$

$$R_o = R_L \parallel \frac{1}{h_{mf}} = 0.9167 \text{ K} \Omega$$


$$Z_{of} = 43.69 \Omega$$

$$Z_{of} = R_L \parallel R_{ov}$$

$$\therefore R_{ov} = 45.69 \Omega$$


$$R_o = R_L \parallel \frac{1}{h_{mf}} = 0.9167 \text{ K} \Omega$$

8.42

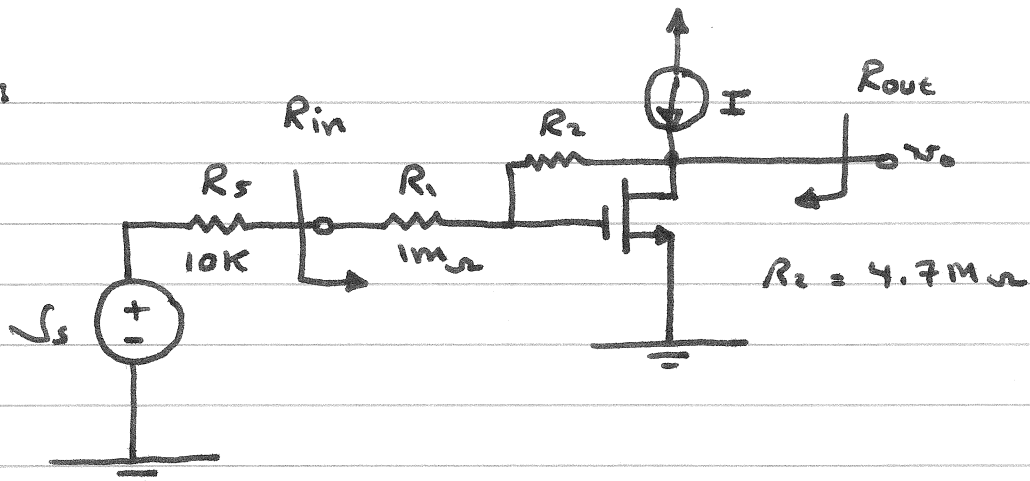


$$I = 1\text{mA}, V_{GS} = 0.8\text{V}, V_T = 0.6\text{V}, V_A = 30\text{V}$$

Shunt-shunt feedback

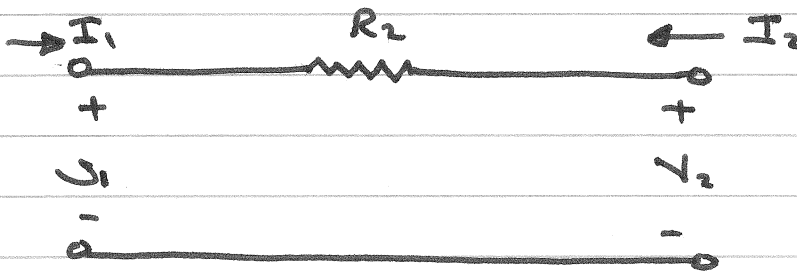

$$y_{11} = \frac{1}{R_2}; y_{22} = \frac{1}{R_2}; y_{12} = \beta = -\frac{1}{R_2}$$

To find A

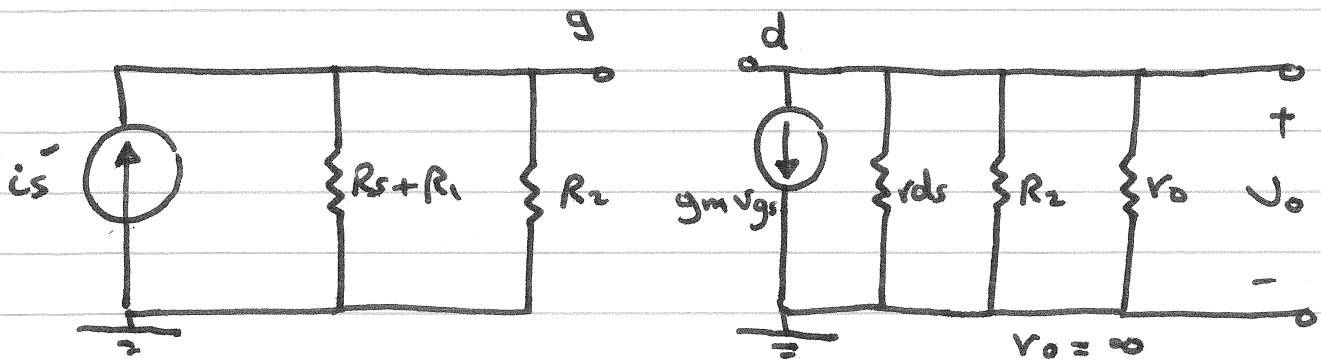

$$V_o = -g_m V_{GS} (r_{ds} \parallel r_o \parallel R_2) = -g_m V_{GS} (r_{ds} \parallel R_2)$$

$$V_{GS} = V_G = i_s (R_2 \parallel (R_s + R_1))$$

$$g_m = \frac{2I_{DQ}}{V_{GS} - V_T} = 10\text{mS}, r_{ds} = \frac{V_A}{I_{DQ}} = 30\text{K}$$

$$A = \frac{V_o}{i_s} = -24100\text{K}\Omega$$

$$A_f = \frac{A}{1+AB} = -3931 \text{ K}\Omega$$

$$A_v = \frac{V_o}{V_s} = \frac{V_o}{i_s} \cdot \frac{i_s}{V_s} = (A_f) \cdot \left(\frac{1}{R_s + R_i} \right)$$

$$\therefore A_v = -3.9$$

$$Z_{of} = \frac{R_o}{1+AB}$$

$$R_o = R_2 \parallel r_{ds} = 4.7 \text{ M} \parallel 30 \text{ K} = 29.8 \text{ K}$$

$$\therefore Z_{of} = 4.86 \text{ K}\Omega = R_{out}$$

$$Z_{if} = \frac{R_i}{1+AB}$$

$$R_i = (R_s + R_1) \parallel R_2 = 0.83 \text{ M}\Omega$$

$$\therefore Z_{if} = 136 \text{ K}$$