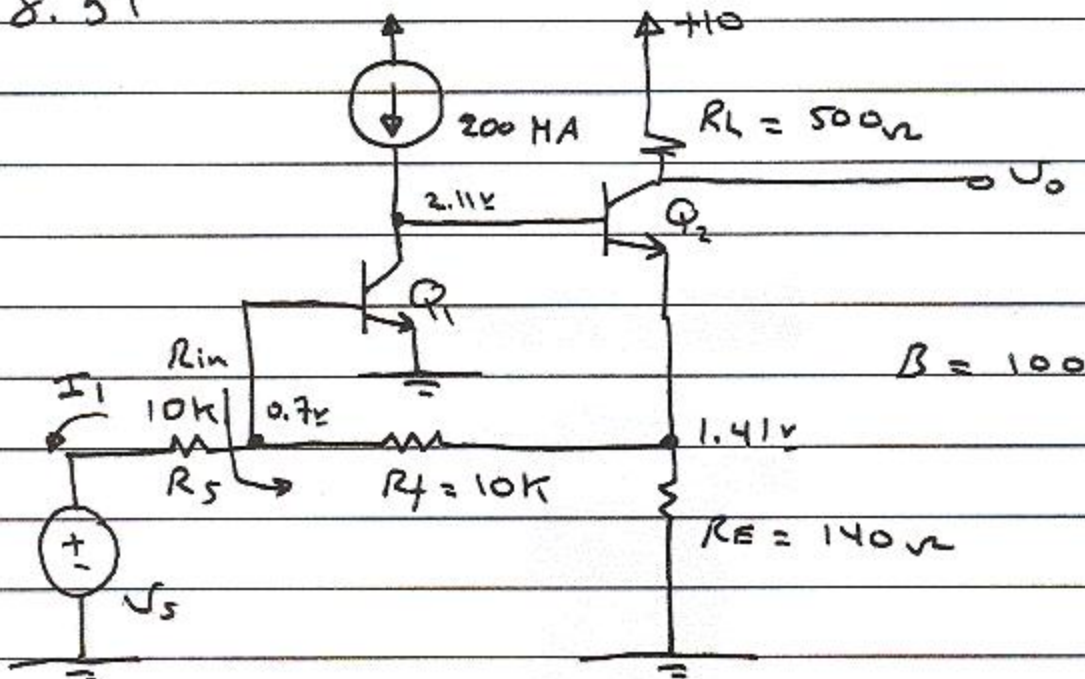


8.51



DC Analysis

$$I_{B2} + I_{C1} = 200 \mu A \quad ; \quad I_1 = \frac{0.7}{10K}$$

$$-0.14K (I_{E2} - I_{B1} - I_1) + 10K (I_{B1} + I_1) + 0.7 = 0$$


$$I_{B2} = 0.1 mA \quad ; \quad I_{C2} = 10 mA$$

$$I_{C1} = 0.1 mA$$

$$V_{B1} = 0.7V, \quad V_{E2} = 1.41V, \quad V_{B2} = V_{C1} = 2.11V$$

ac analysis

shunt-series feedback

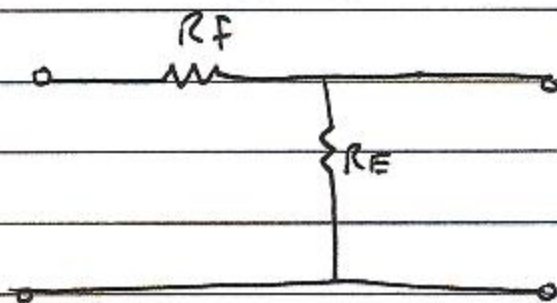


$$g_{11} = \frac{1}{R_E + R_F}$$

$$g_{22} = R_E || R_F$$

$$g_{12} = \beta = \frac{-R_E}{R_E + R_F} = -0.0138$$

To find $A = \frac{i_o}{i_s}$

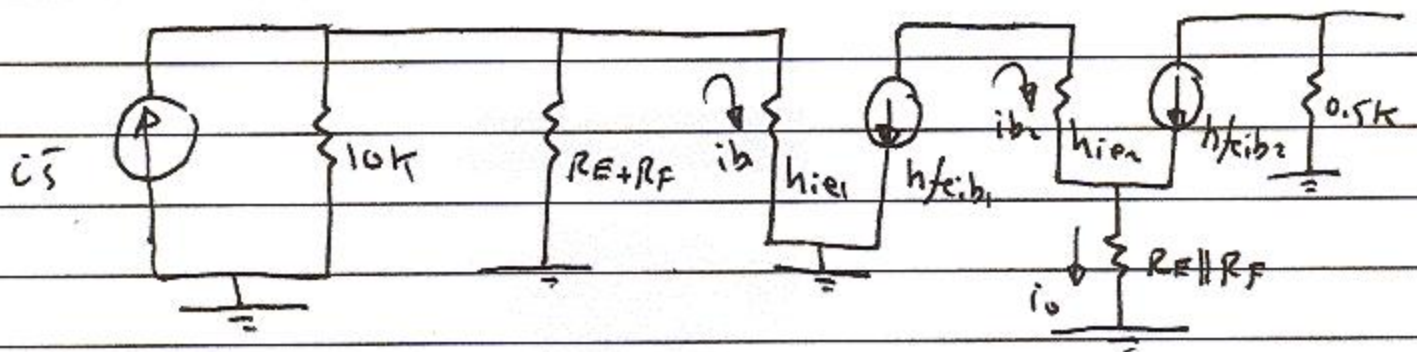

$$i_o = i_{e2} = (1 + h_{fe}) i_{b2} = (1 + h_{fe}) (-h_{fe} i_{b1})$$

$$i_{b1} = i_s \frac{10k \parallel 10.14k}{10k \parallel 10.14k + h_{ie1}} i_s$$

$$h_{ie1} = h_{fe} \frac{V_T}{I_{E1}} = 25.69k$$

$$A = \frac{i_o}{i_s} = -1629.2, \quad A_B = 22.49$$

$$A_f = \frac{i_o}{i_s} = -69.4$$

$$A_{VS} = \frac{v_o}{v_s} = \left(\frac{i_o}{i_s} \right) \left(\frac{v_o}{i_o} \right) \left(\frac{v_s}{i_s} \right)$$

$$= (A_f) (-0.5k) \left(\frac{1}{10k} \right)$$

$$A_{VS} = +3.47$$

$$Z_{if} = \frac{R_i}{1 + A_B}; \quad R_i = (10k \parallel 10.14k \parallel 25.69k) = 4.2k$$