



**Faculty of Engineering and Technology**  
**Electrical and Computer Engineering Department**  
**Circuits LAB (ENEE2102)**  
**Pre-LAB of Experiment #4**  
**Network Theorems**

---

Prepared by:

Name: Sara Totah

Number: 1181779

Instructor:

Jaser Sa'Ed

Date:

20/9/2020

Section: #1

## Part A: Proportionality:


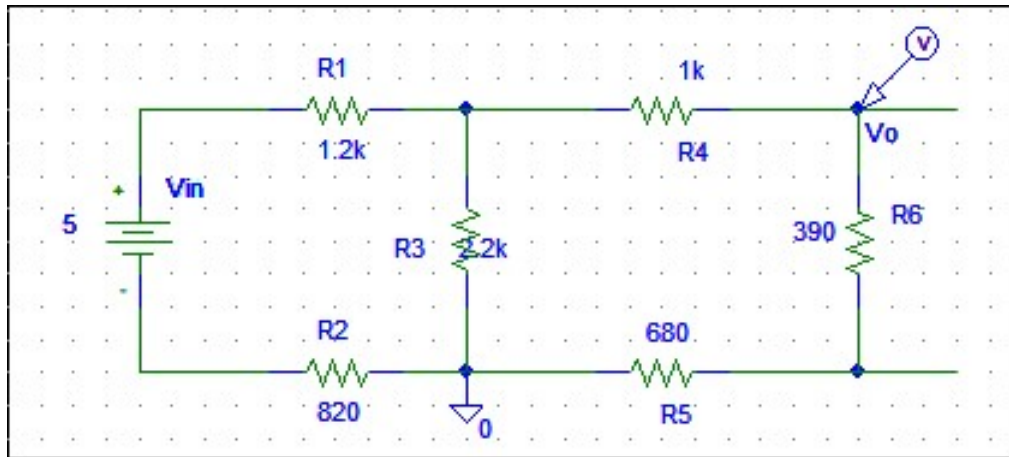


Fig (4-1)

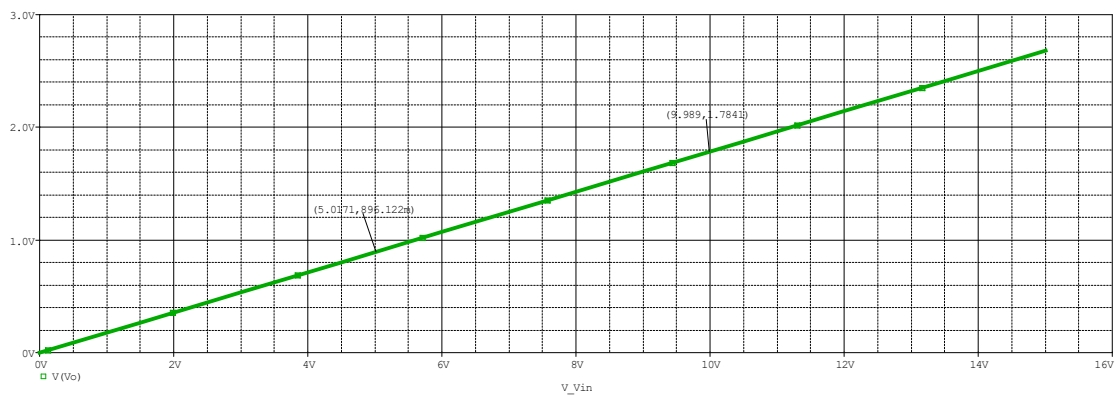

Plot (4-1)

- When  $V_{in} = 5$ :  
 $V_o = 896.122\text{mV}$ .
- When  $V_{in} = 10$ :  
 $V_o = 1.7841\text{V}$ .

## Part B: Superposition:

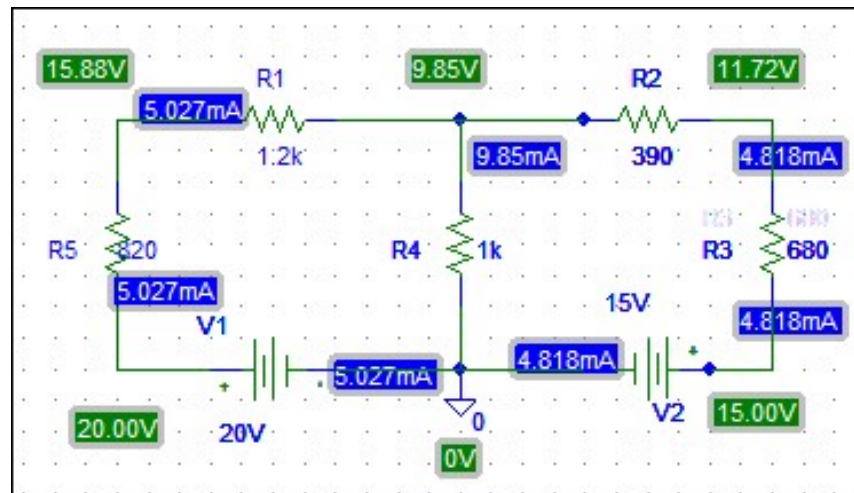


Fig (4-2)

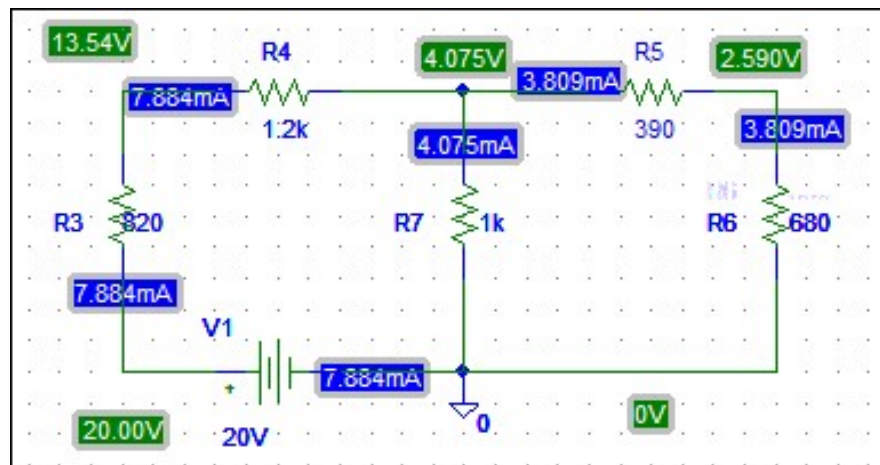


Fig (4-3)

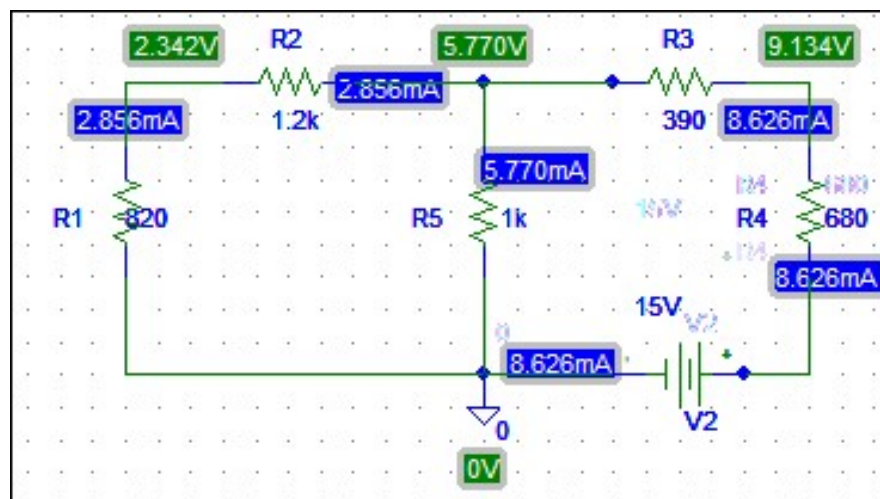


Fig (4-4)

## Part C: Thevenin's Theorem:

A.

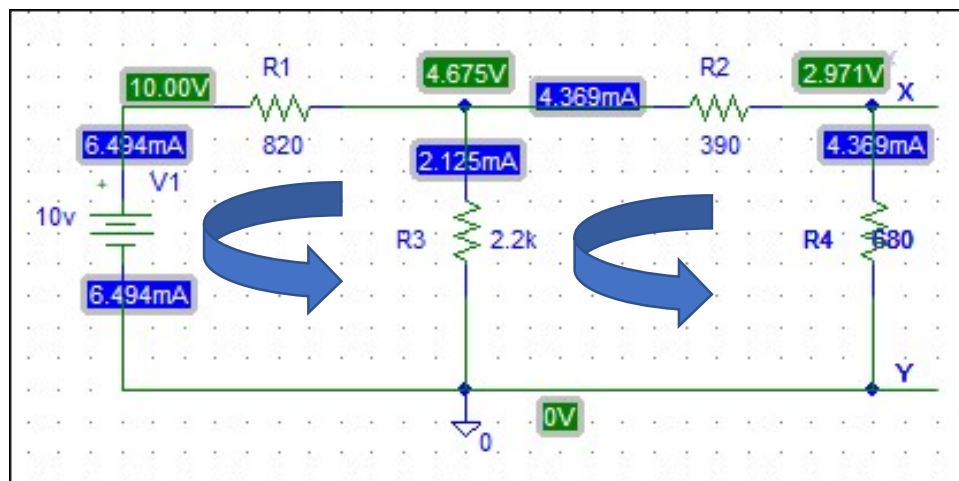


Fig (4-5) a

To find  $R_{th}$  remove  $R_4$  and replace it with open circuit, and replace  $V_1$  with short circuit:

$$R_{th} = (2.2k \parallel 820) + 390 = 987.35 \Omega$$

To find  $V_{th}$  replace  $R_4$  with short circuit, with KCL:

$$V_{th} = 7.2v$$

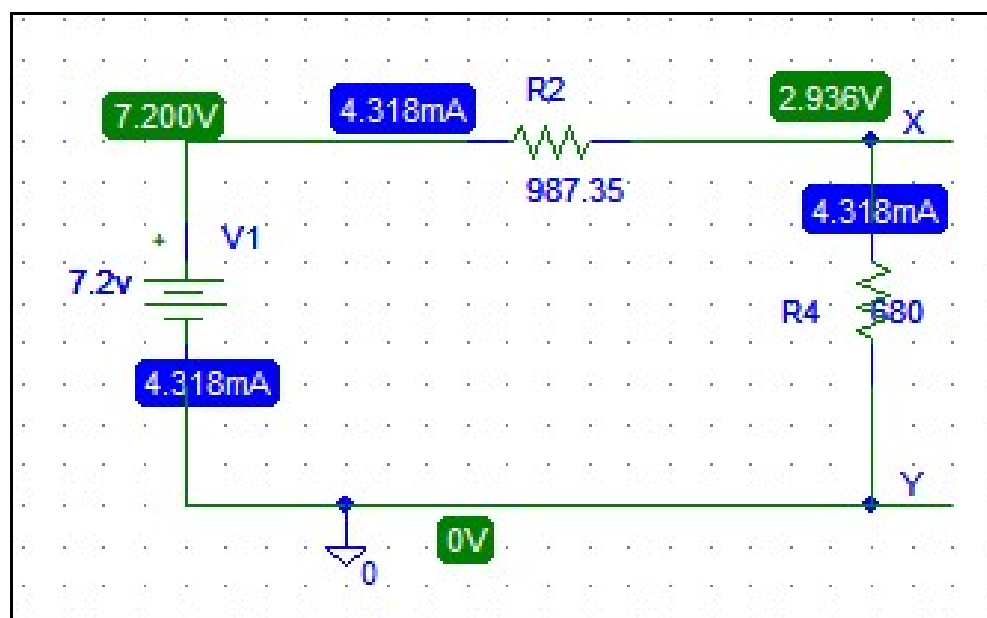


Fig (4-5) b

## Part D: Δ-Y Transformation:


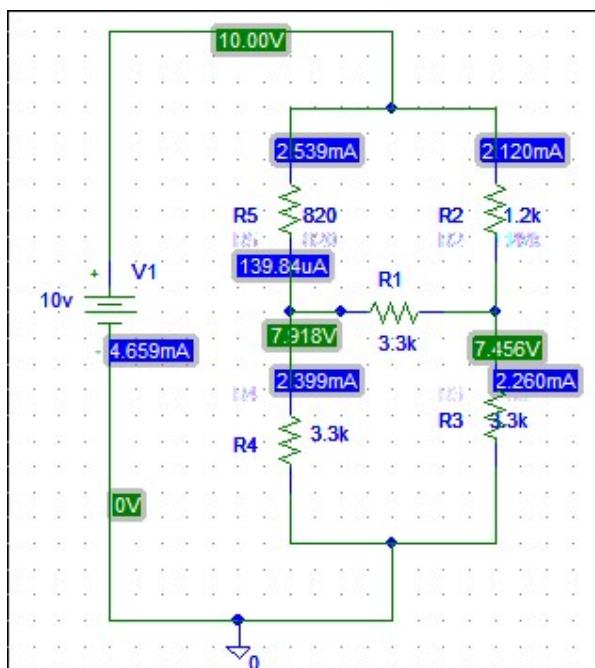


Fig (4-8) a

Y-Delta Transformation:
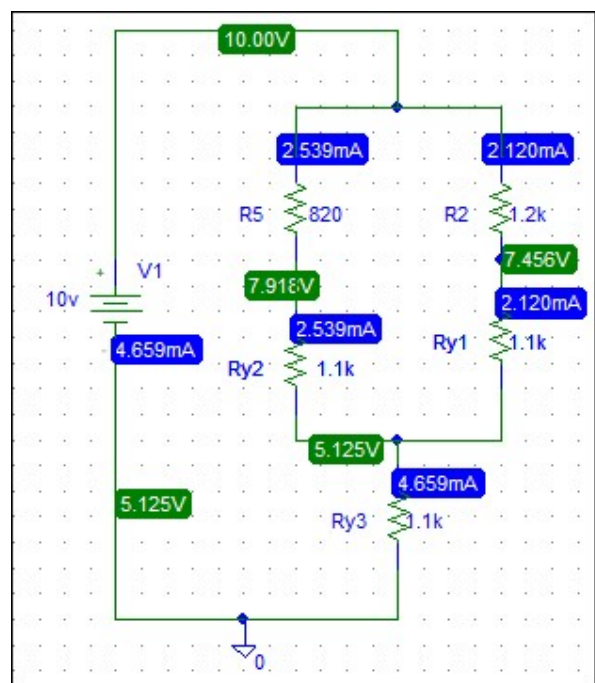
$$R_{Y1} = R_{Y2} = R_{Y3} = \frac{3.3k}{3.3k * 3} = 1100 \Omega$$



Y Transformation

Fig (4-8) b

## Part E: The Reciprocity Theorem:

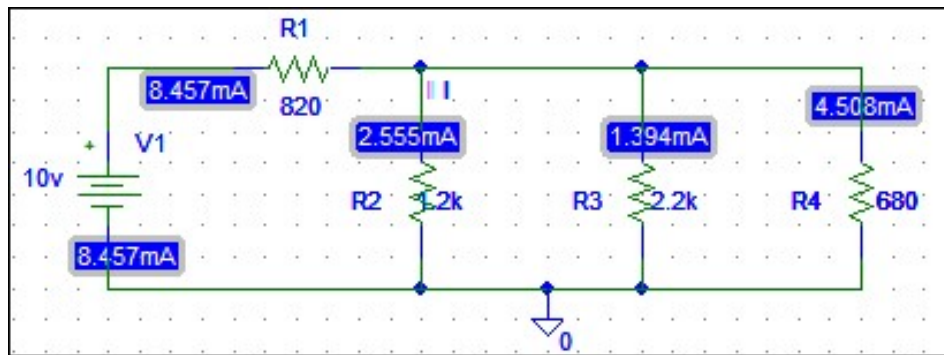


Fig (4-9)

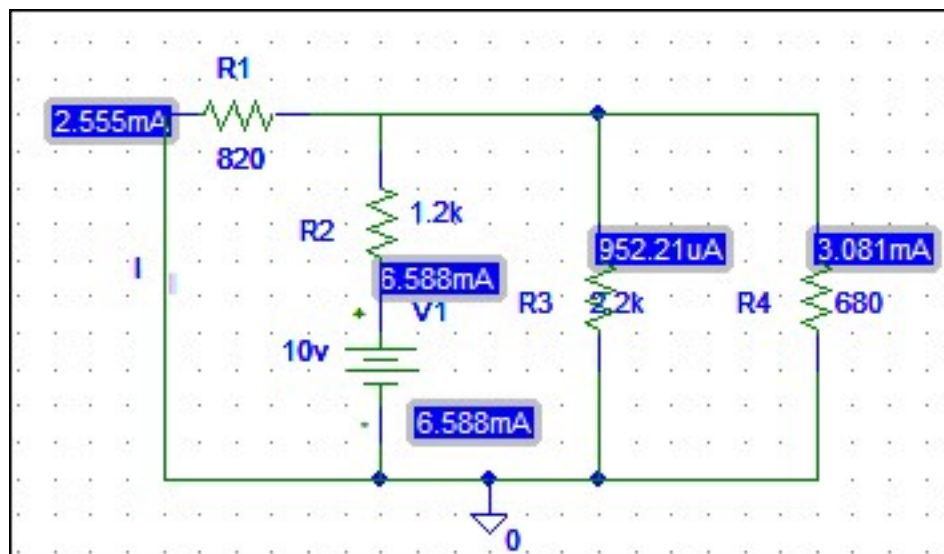


Fig (4-10)