

Chapter 3:

Resistors in Series and ~~Parallel~~ Parallel


VDR

CDR

$\Delta - Y$

$Y - \Delta$

* Resistors in Series

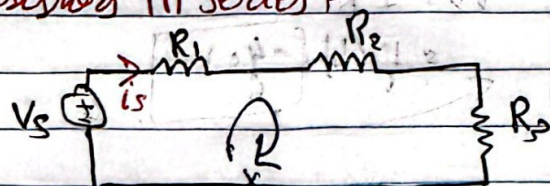


series elements have the same current.

$$\hookrightarrow \text{KVL} \rightarrow -V_s + R_1 i_s + R_2 i_s + R_3 i_s = 0$$

$$(R_1 + R_2 + R_3) i_s = V_s$$

$$R_{eq} = \sum_{i=1}^N R_i = R_1 + R_2 + R_3 + \dots + R_N$$

* Resistors in Parallel:

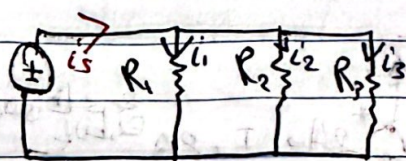

Parallel

~~Series~~ elements have the same voltage.



$$i_1 = \frac{V_s}{R_1}, \quad i_2 = \frac{V_s}{R_2}, \quad i_3 = \frac{V_s}{R_3}$$

$$\text{KCL} \rightarrow I_s = i_1 + i_2 + i_3$$

$$= \frac{V_s}{R_1} + \frac{V_s}{R_2} + \frac{V_s}{R_3}$$

$$I_s = V_s \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$
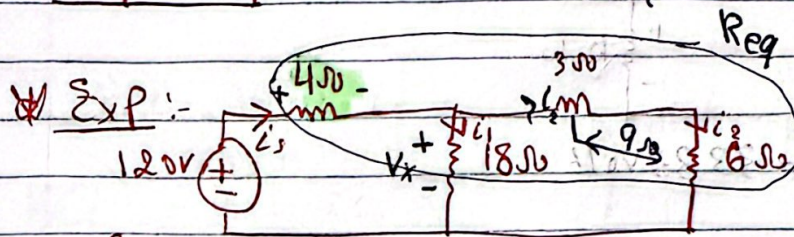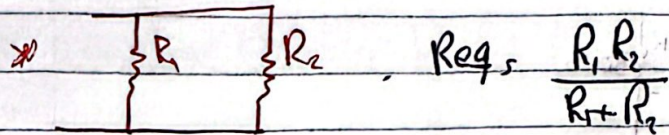
$$\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$



Find i_s, i_1, i_2 :

$$R_{eq} = \left[\frac{(6+3) \parallel 18}{\text{Parallel}} \right] + 4 \quad \text{series}$$

$6+3=9$
 $9 \parallel 18 = \frac{9 \cdot 18}{9+18} = 6$
 $6+4=10$

$$= 10 \Omega$$

$$\therefore V_s = R_{eq} \cdot I_s$$

$$120 = 10 I_s \rightarrow \boxed{I_s = 12 \text{ A}}$$

$$\hookrightarrow V_x = 120 - 4(12)$$

$$= 120 - 48 = 72 \text{ Volt}$$

$$\text{or } V_x = i_s \times (18 \parallel 9)$$

$$= 12 \times 6 = 72 \text{ volt}$$

$$\therefore i_1 = \frac{V_x}{18} = \frac{72}{18} = \boxed{4 \text{ A}}$$

$$i_2 = \frac{V_x}{9} = \frac{72}{9} = \boxed{8 \text{ A}}$$

* Voltage Divider Rule: (VDR)

$$V_1 \rightarrow V_s$$

$$V_2 \rightarrow V_s$$

$$1) R_{eq} = R_1 + R_2$$


$$2) I_s = \frac{V_s}{R_{eq}} = \frac{V_s}{R_1 + R_2}$$

$$3) V_1 = I_s R_1$$


$$V_2 = I_s R_2$$

$$V_1 = V_s \cdot \frac{R_1}{R_1 + R_2}$$
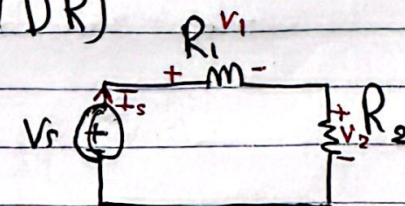
$$V_2 = V_s \cdot \frac{R_2}{R_1 + R_2}$$




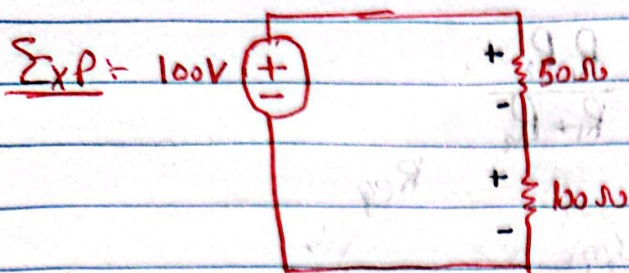طريقة تقسيم الجهد (Voltage Divider Rule) تستخدم لحساب الجهد على أحد المقاومات في دارة المقاومات المتسلسلة.




$$V_{50\Omega} = \left(\frac{50}{50+100} \right) 100 = 33.33 \text{ Volt}$$
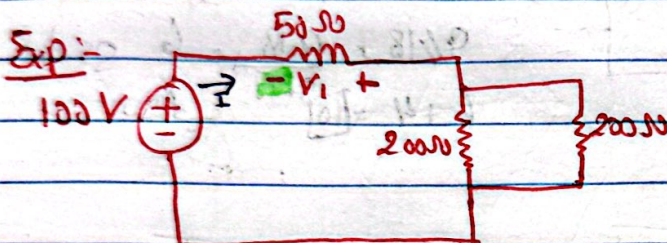
$$V_{100\Omega} = \left(\frac{100}{100+50} \right) 100 = 66.66 \text{ Volt}$$



Exp:-
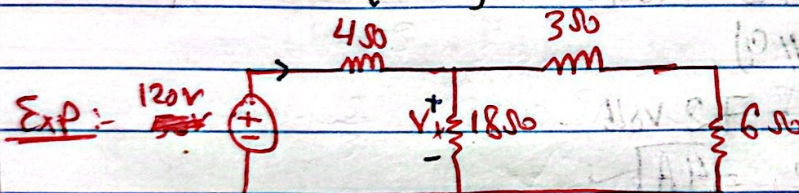
$$V_1 = \frac{50}{50 + (200 \parallel 200)} \times 100$$



$$V_x = \frac{(18 \parallel 6)}{(18 \parallel 6) + 4} \times 120 = \frac{4.5}{4.5 + 4} \times 120 = \frac{4.5}{8.5} \times 120 = 72 \text{ Volt}$$

* Current Divider Rule: (C DR)


$$V_s, R_1, i_1, V_2, R_2, i_2$$

$$V_s, i_s, R_{eq}$$

$$V = i_s \cdot R_1 R_2 / (R_1 + R_2)$$

BCI

$$i_s = i_1 + i_2$$

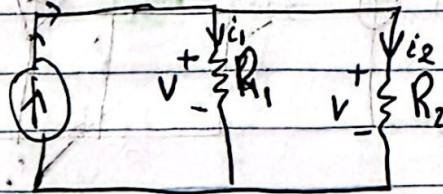


the same voltage

$$R_1 i_1 = \frac{R_1 R_2}{R_1 + R_2} i_s$$

$$i_1 = \frac{R_2}{R_2 + R_1} * i_s$$

$$i_2 = \frac{R_1}{R_1 + R_2} * i_s$$

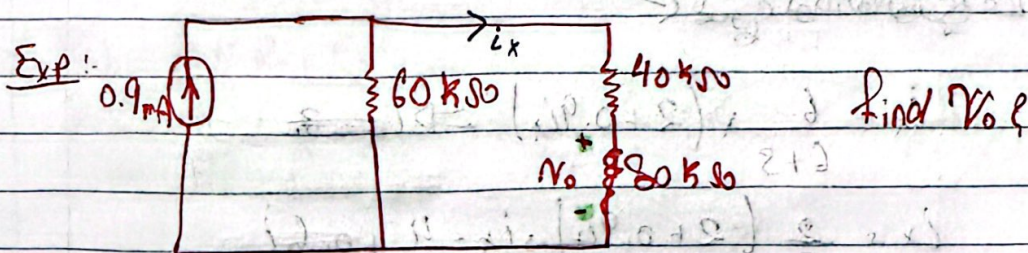


$$V_0 = (80k) i_x$$

$$A_{eq} = (80k) \left(\frac{60k}{60k + (80+40)k} * 0.9m \right)$$

$$= 24 \text{ Volt}$$

~~Find V0 by solving~~

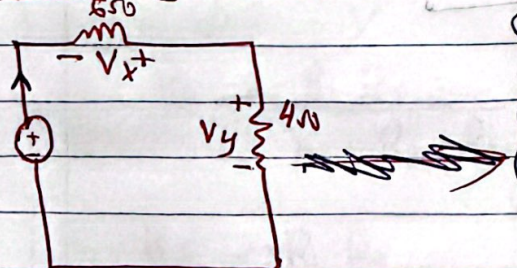


$$(KVL) \Rightarrow -V_x + V_y - 10 = 0$$

$$-10 - (-6I) + 4I = 0$$

$$-10 + 6I + 4I = 0$$

$$I = 1A$$


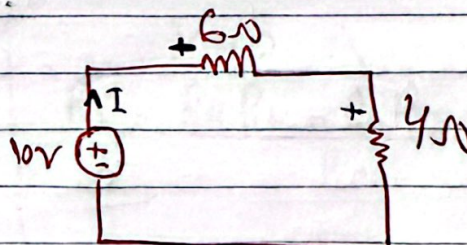


KVL

$$-10 + 6I + 4I = 0$$

$$I = 1A$$

Expt-

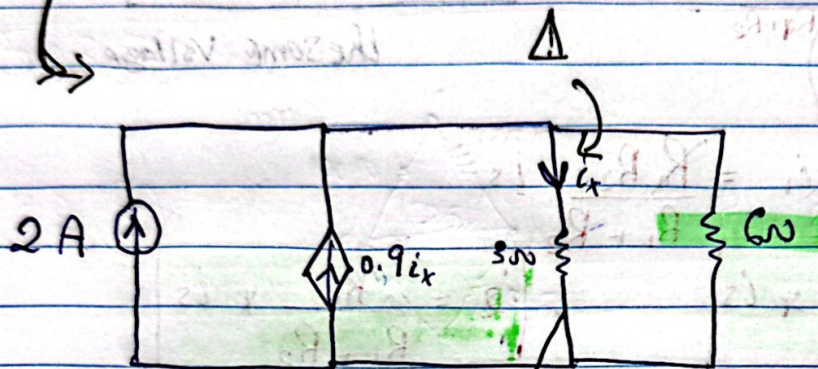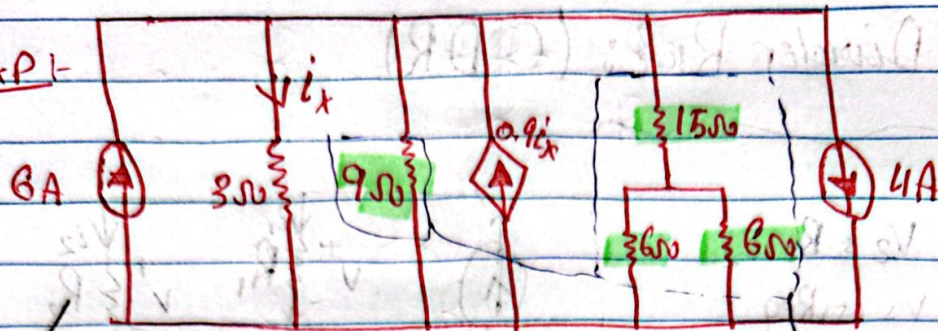

i_x ← i_x is the current through the 3Ω resistor

$$6 \parallel 6 = \frac{6 \times 6}{6+6} = 3$$

$$3 + 15 = 18 \Omega$$

$$18 \parallel 9 = \frac{18 \times 9}{18+9} = 6 \Omega$$

$$i_x = \frac{6}{6+9} (2 + 0.9i_x) \Rightarrow i_x = \frac{4}{3} + 0.6i_x$$




$$i_x = \frac{4}{3} + 0.6i_x \Rightarrow 0.4i_x = \frac{4}{3} \Rightarrow i_x = 3.33 A$$

$$0.4i_x = \frac{4}{3} \Rightarrow i_x = 3.33 A$$

$$V = i_x R = 10 V$$

$$P_x = -V(0.9i_x) = -10(0.9 \times 3.33) = -30 W$$

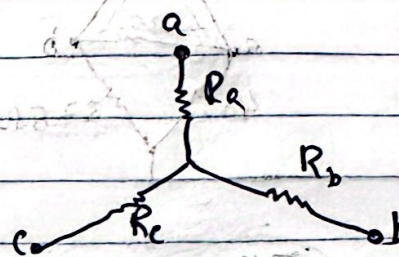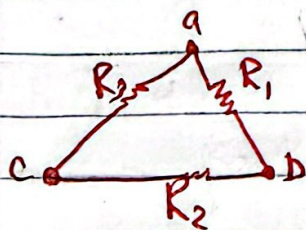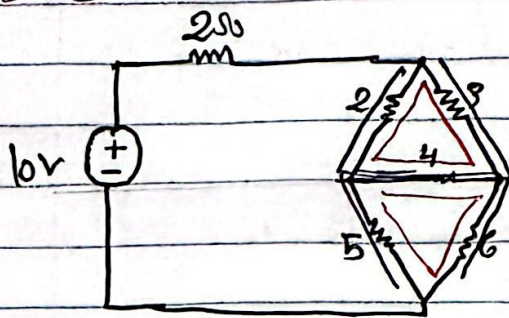$\Delta \rightarrow Y$
 $Y \rightarrow \Delta$ } transformation



$$R_{ab} = R_1 \parallel (R_2 + R_3)$$

$$R_{ab} = \frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} = R_a + R_b \quad \text{--- (1)}$$

$$R_{bc} = \frac{R_2 (R_1 + R_3)}{R_1 + R_2 + R_3} = R_b + R_c \quad \text{--- (2)}$$

$$R_{ca} = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_3} = R_c + R_a \quad \text{--- (3)}$$

$\Delta \rightarrow Y$

$$R_a = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$Y \rightarrow \Delta$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$


$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

Note + if $R_1 = R_2 = R_3 = R_0$
 if $R_a = R_b = R_c = R_x$

$$\therefore R_0 = 3 R_x$$


$$R_x = \frac{1}{3} R_0$$

Ex 3.7

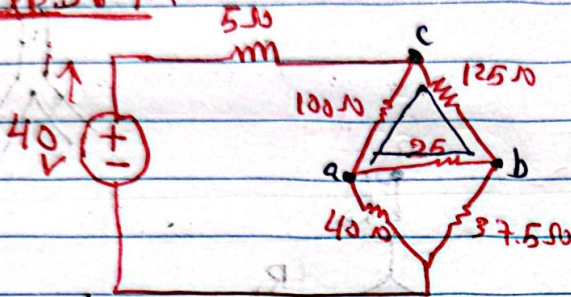

$P_{40V}?$

$\Delta \rightarrow Y$

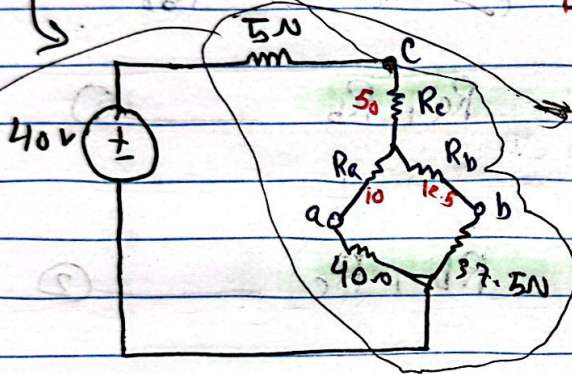

$$5 + 50 = 55$$

$$55 \parallel (10 + 40) = 55 \parallel 50$$

$$55 \times 50 / (55 + 50) = 25$$

$$R_a = \frac{25 \times 100}{100 + 25 + 125} = \frac{2500}{250} = 10 \Omega$$

$$R_b = \frac{25 \times 125}{250} = 12.5 \Omega$$

$$R_c = \frac{100 \times 125}{250} = 50 \Omega$$

$$R_{eq} = 5 + 50 + \frac{(10 + 40) \parallel (12.5 + 37.5)}{25} = 80 \Omega$$

$$P_{80\Omega} = \frac{V^2}{R_{eq}} = \frac{40^2}{80} = 20 \text{ W}$$

$$P_{40V} = \frac{40^2}{80} = 20 \text{ W}$$