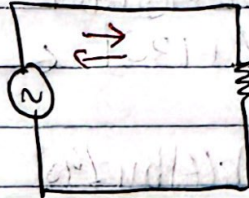


# Chapter 9: AC Sinosoidal steady-state analysis


التيار المتردد



$$v(t) = V_m \sin \omega t$$

$$f = \frac{1}{T} \text{ (Hz)}$$

$$\omega = 2\pi f \text{ (rad/s)}$$

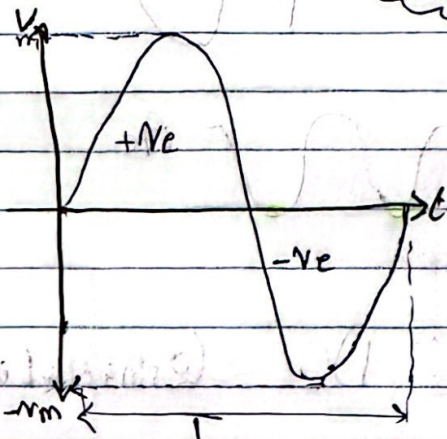


$$f = \frac{1}{T} \text{ (Hz)}$$

$$\omega = 2\pi f \text{ (rad/s)}$$

$$v_1(t) = V_m \sin \omega t$$

$$v_2(t) = V_m \sin(\omega t + \phi)$$

$\phi$  = phase, phase shift

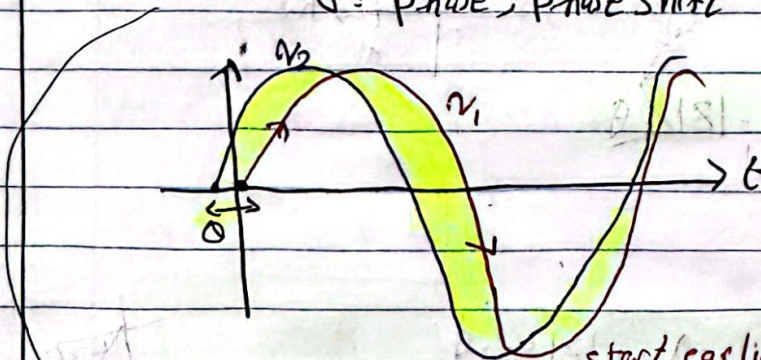

Lead / Lag

start earlier

$v_2(t)$  leads  $v_1(t)$  by  $\phi$

$v_1(t)$  lags  $v_2(t)$  by  $\phi$

start later






$$v_i(t) = V_m \sin(\omega t - 40^\circ)$$

$$i_i(t) = I_m \cos(\omega t + 40^\circ)$$

$$= I_m \sin(\omega t + 40^\circ + 90^\circ)$$

$$= I_m \sin(\omega t + 130^\circ)$$

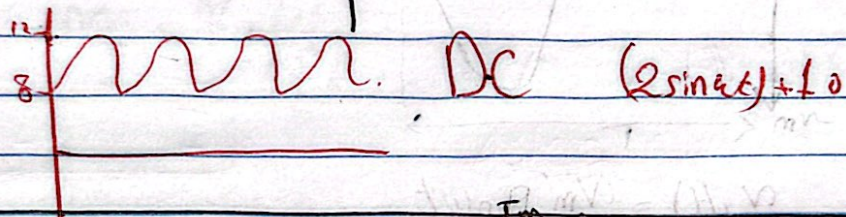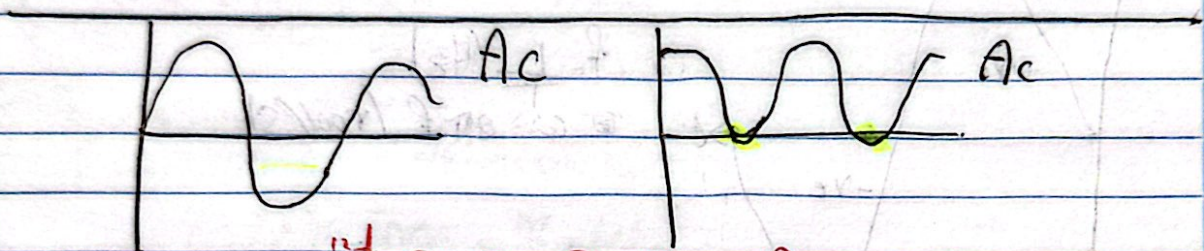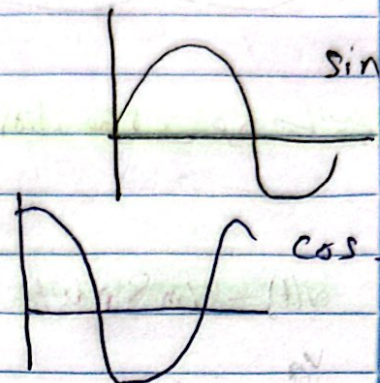$i_i(t)$  leads  $v_i(t)$  by  $140^\circ$




Complex numbers:

$$Z = X + jY$$

$$Z = |Z| \angle \theta$$

$$|Z| = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$

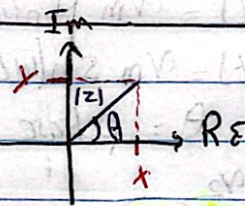

$$\rightarrow Z = x + jy = |Z| \cos \theta + j |Z| \sin \theta$$

$$Z = |Z| e^{j\theta}$$

$$\rightarrow e^{j\theta} = \cos \theta + j \sin \theta$$

$$Z_1 = 4 - j2 = 4.47 \angle -26.56^\circ$$

$$Z_2 = 2 + j2 = 2.82 \angle 45^\circ$$

بجمع او  
تفریق

$$Z_1 + Z_2$$

$$Z_1 - Z_2$$

بقسمة او  
تقسیم

$$Z_1 \times Z_2$$

$$\frac{Z_1}{Z_2}$$



## Phasor:


input  $\rightarrow$  [circuit]  $\rightarrow$  output

$$V_m \cos(\omega t + \theta_v)$$

$$\vec{V}_m \angle \theta_v$$

$$I_m \cos(\omega t + \theta_i)$$


$$\vec{I}_m \angle \theta_i$$

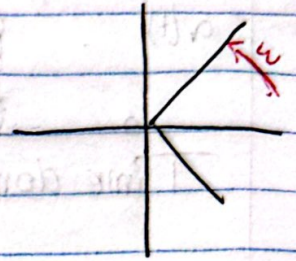


## \* Resistor

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

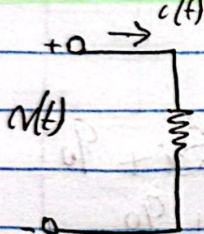

Time Domain

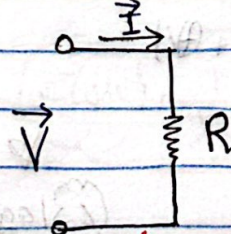


Phasor Domain

$$v(t) = Ri(t) \rightarrow \vec{V} = R\vec{I}$$

$$V_m e^{j\theta_v} = R I_m e^{j\theta_i}$$


$$\vec{V} = R \vec{I}$$

$\theta_v = \theta_i$  in phase

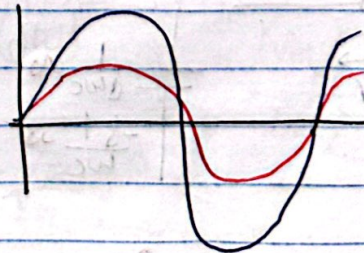




## \* Inductor:

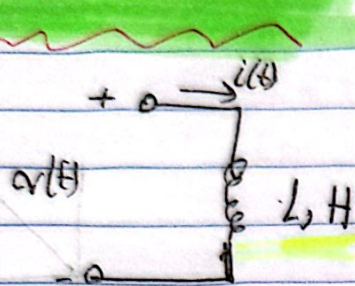

Time domain

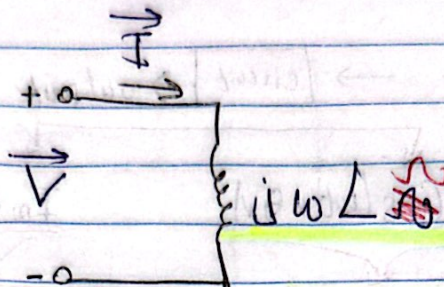

phasor domain

$$v(t) = L \frac{di(t)}{dt}$$


$$V_m e^{j(\omega t + \phi_v)} = L \frac{d}{dt} I_m e^{j(\omega t + \phi_i)}$$

$$V_m e^{j(\omega t + \phi_v)} = L I_m j \omega e^{j(\omega t + \phi_i)}$$

$$\vec{V} = (j\omega L) \vec{I}$$

\*  $\phi_v = \phi_i + 90^\circ$   
 I lags V by  $90^\circ$

## \* Capacitor:

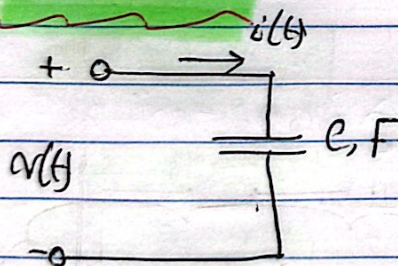


$$i(t) = C \frac{dv(t)}{dt}$$

$$I_m e^{j\omega t} = C j \omega V_m e^{j\omega t}$$

$$\vec{I} = (j\omega C) \vec{V}$$
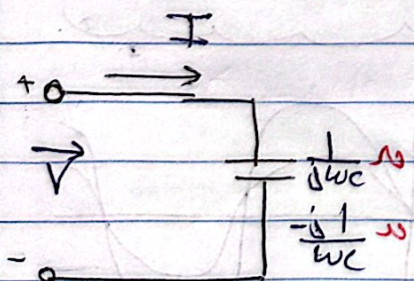
$$\vec{V} = \frac{1}{j\omega C} \vec{I}$$




$$\frac{V}{I} = \frac{1}{j\omega C}$$

\*  $\phi_i = \phi_v + 90^\circ$

I leads V by  $90^\circ$




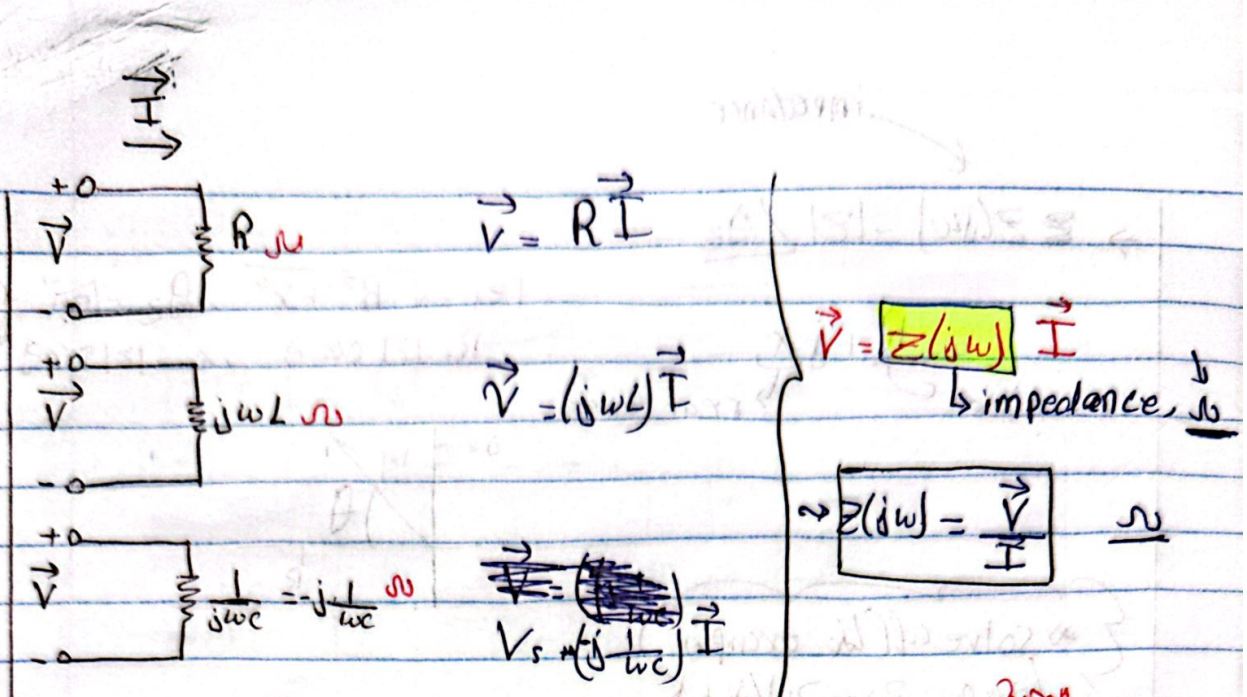

impedance  $\rightarrow \boxed{Y(j\omega) = \frac{\vec{I}}{\vec{V}}}$  admittance,  $\underline{Y}$   
 $\left\{ Y = \frac{1}{Z} \right\}$   
 $\therefore Z(j\omega) = \frac{1}{Y(j\omega)}$

Element	Impedance	admittance
R	$Z(j\omega) = R$	$Y(j\omega) = \frac{1}{R}$
C	$Z(j\omega) = \frac{1}{j\omega C}$	$Y(j\omega) = j\omega C$
L	$Z(j\omega) = j\omega L$	$Y(j\omega) = \frac{1}{j\omega L}$

Impedance:  $Z(j\omega)$

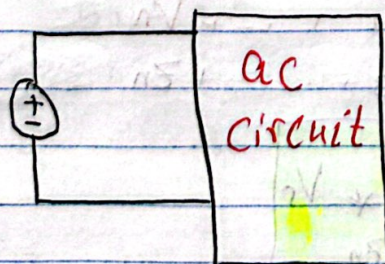

$$Z(j\omega) = \frac{\vec{V}}{\vec{I}} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i}$$

$$Z(j\omega) = \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

$$= |Z| \angle \theta_z$$

$Z(j\omega)$  is a complex number, But Not a phasor  
 sin/cos.  $\vec{Z}$  is a phasor




impedance

$$\rightarrow \underline{Z}(\omega) = |Z| \angle \theta_z$$

$$= \underbrace{R}_{\text{resistance}} + j \underbrace{x}_{\text{reactance}}$$

$$|Z| = \sqrt{R^2 + x^2}, \theta_z = \tan^{-1} \frac{x}{R}$$

$$R = |Z| \cos \theta, x = |Z| \sin \theta$$

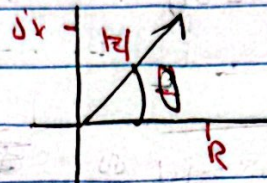


\* solve all the examples  
(page 30-71) (Notes)

Imag.


real

$$5 + j10 \rightarrow \text{conjugate} \rightarrow 5 - j10$$
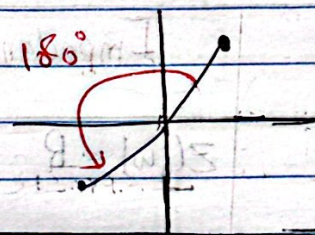
$$5 + j10 \rightarrow x(-1) \rightarrow -5 - j10$$



\* Application of KVL for phasor:

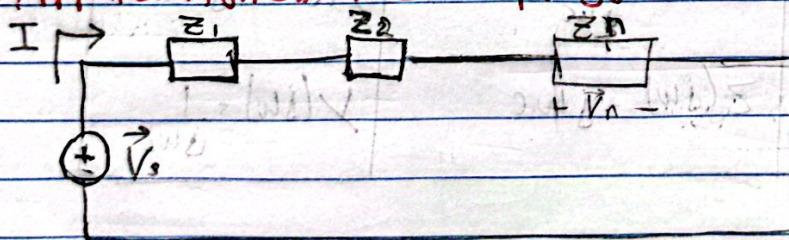

$$\text{KVL: } V_s(t) = V_1(t) + V_2(t) + \dots + V_n(t)$$


$$\vec{V}_s = \vec{V}_1 + \vec{V}_2 + \dots + \vec{V}_n$$

$$\vec{Z}_{eq} = \vec{Z}_1 + \vec{Z}_2 + \vec{Z}_3 + \dots + \vec{Z}_n$$


$$\vec{V}_n = \frac{\vec{Z}_n}{\vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_n} * \vec{V}_s$$



## \* Application of KCL for Phasor:

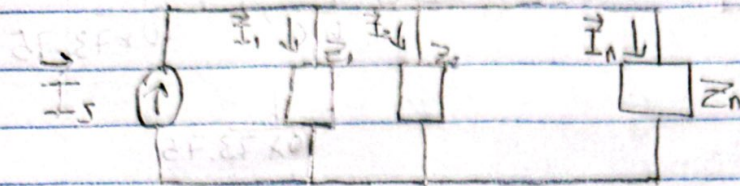

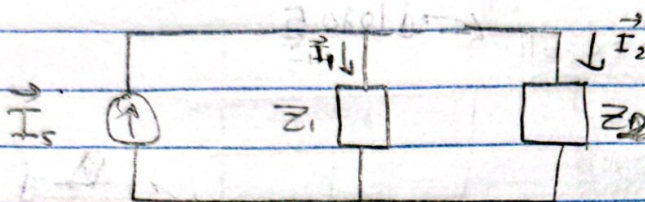
KCL  $\vec{I}_s = \vec{I}_1 + \vec{I}_2 + \dots + \vec{I}_n$



$$I_1 = \frac{Z_2}{Z_1 + Z_2} \times I_s$$

$$I_2 = \frac{Z_1}{Z_1 + Z_2} \times I_s$$

Find  $Z_{eq}$ :

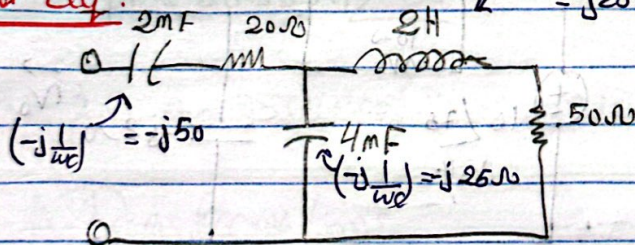

our reference is Cos  
(انجاب Sin) (انجاب Cos)

$$Z_{eq} = \left[ (50 + j20) \parallel (-j25) \right] + (20 - j50)$$

$$= \frac{(50 + j20)(-j25)}{50 - j5} + 20 - j50 = \frac{-j250 + (-j)(500)}{50 - j5} + 20 - j50$$

$$= \frac{1346.29 \angle -68.19^\circ}{50.25 \angle -5.71^\circ} + 20 - j50 = 26.79 \angle -62.48^\circ + 20 - j50$$

طرح الزوايا


$$= 32.37 - j73.75 \, \Omega$$








Calculate volt:

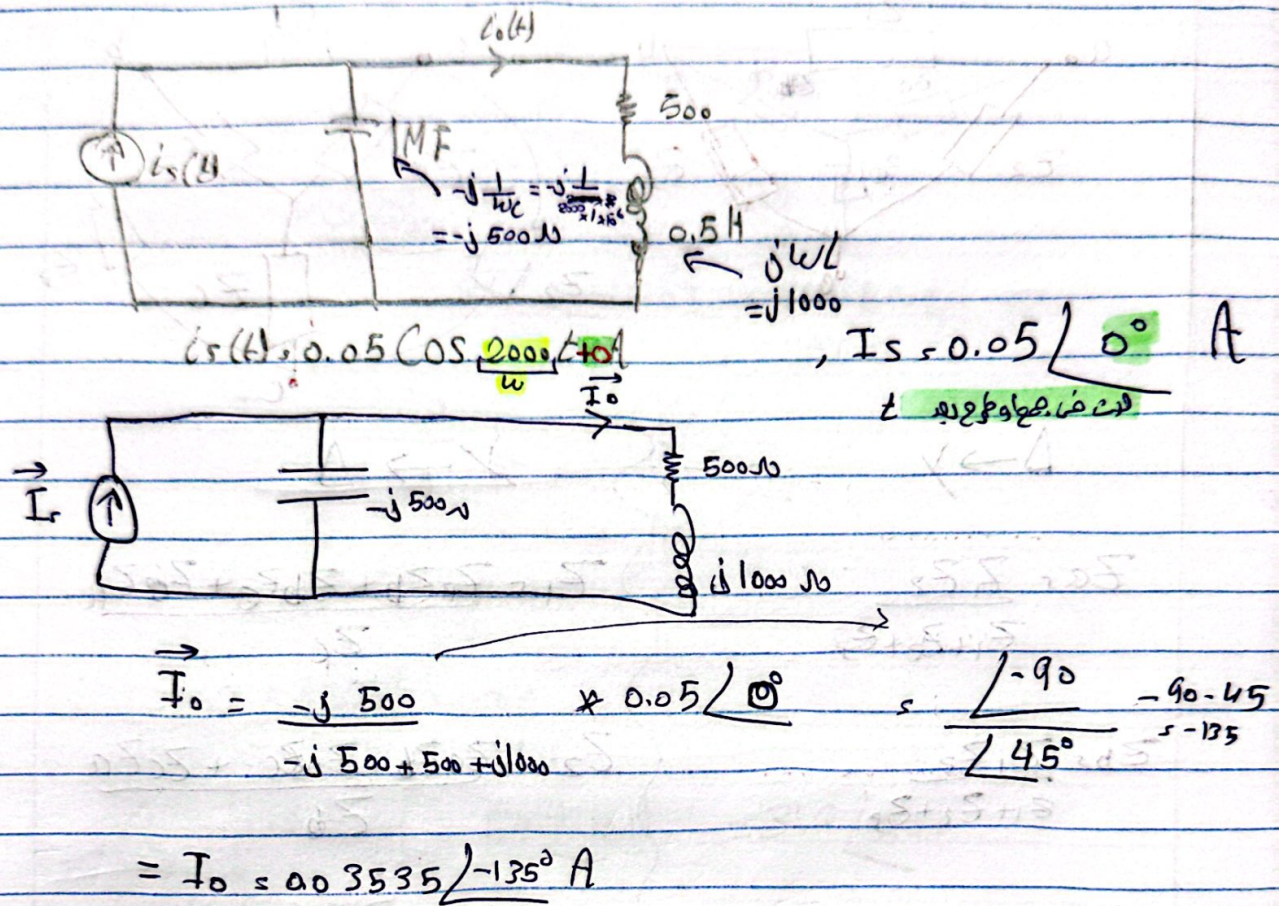



$\therefore v_o = 0.03535 \cos(2000t + -135^\circ)$

Y-Δ Transformation:

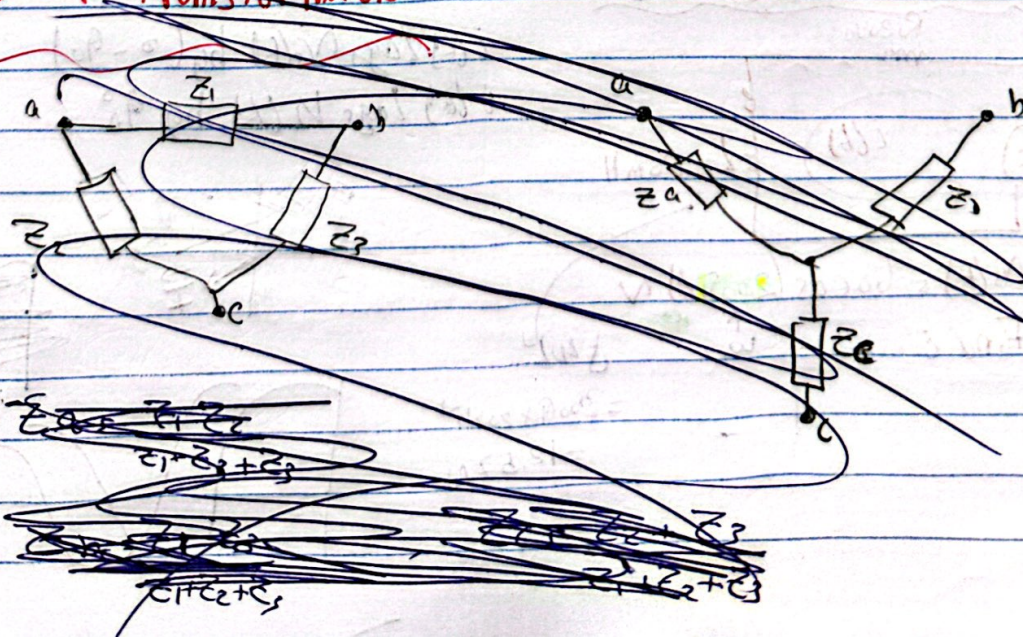



## Y-Δ Transformation:

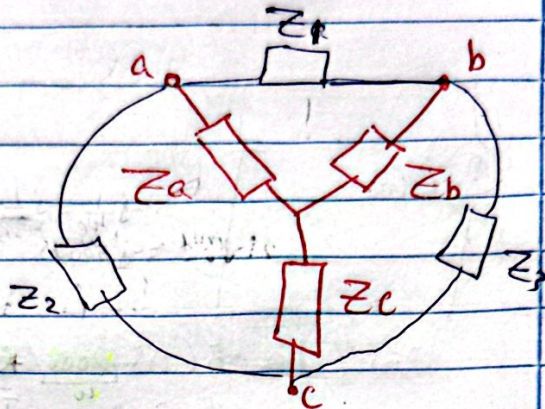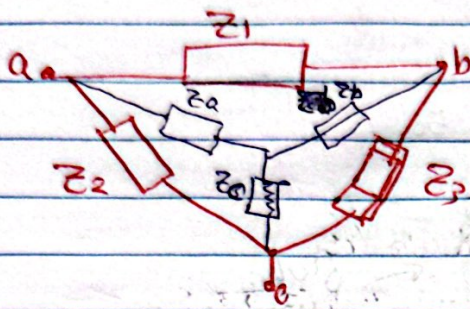

$\Delta \rightarrow Y$

$$Z_a = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_b = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_c = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$


$Y \rightarrow \Delta$

$$Z_1 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c}$$

$$Z_2 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_b}$$

$$Z_3 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_a}$$

## \* Series RL Circuit:

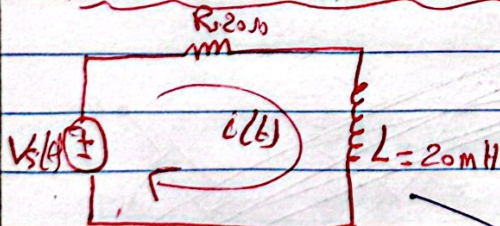


$$V_s(t) = 60 \cos(200\pi t) \text{ V}$$

Find  $i$


$$\begin{aligned} j\omega L &= 200\pi \times 20 \times 10^{-3} \\ &= 12.57 \Omega \end{aligned}$$

$i(t)$  lags  $V_s(t)$  by  $(\phi - \phi_0)$

$i(t)$  lags  $V_L(t)$  by  $90^\circ$

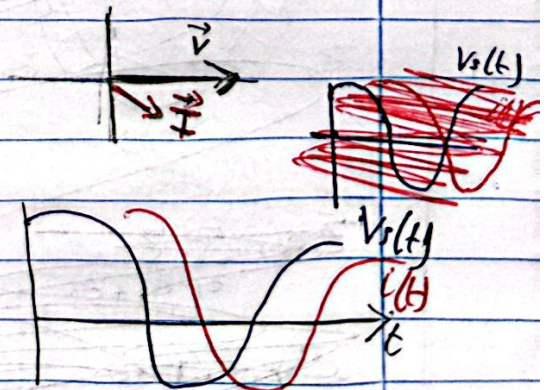



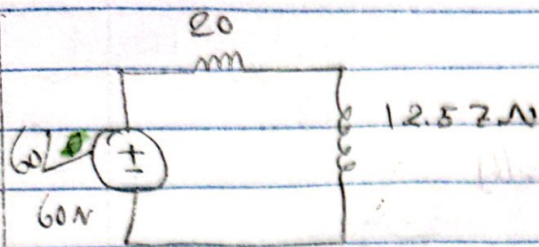

KVL:  $V_s = V_R + V_L$   
 $60 \angle 0 = 20\vec{I} + j12.57\vec{I}$

$$\rightarrow \vec{I} = \frac{60 \angle 0}{20 + j12.57} = \frac{60 \angle 0}{23.6 \angle 32.1}$$


$$\vec{I} = 2.54 \angle -32.1$$

$$i(t) = 2.54 \cos(200\pi t - 32.1) \text{ A}$$

$$\vec{V}_L = (j12.57)(2.54 \angle -32.1) = 31.9 \angle 53.9$$

$\vec{I}$  lags  $\vec{V}_L$  by  $90^\circ$


$\vec{I}$  lags  $\vec{V}_s$  by  $32.1$

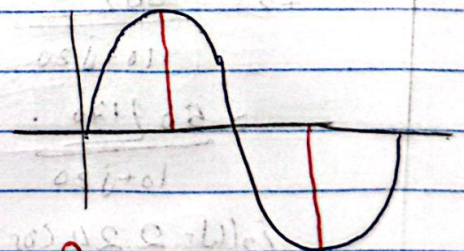

$$P = VI \cos(\theta_v - \theta_i)$$



Page 57:

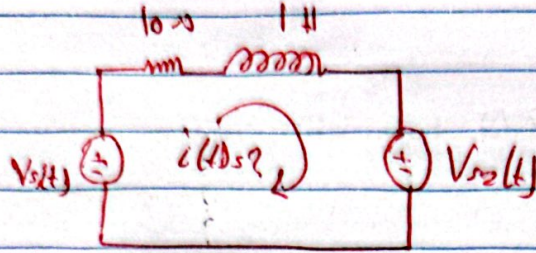


$V_s(t) = 100 \cos 10t$  Volt,  $\omega_s = 10 \text{ rad/s}$

$$V_s(t) = 50 \cos(20t - 10^\circ) \text{ Volt}, \quad \omega_2 = 20 \text{ rad/s}$$

→ superposition.


\*  $I_1$  due to  $\vec{V}_{s1}(t)$

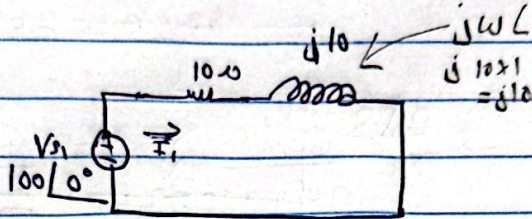

$$I_1 = \frac{100 \angle 0^\circ}{10 + j10} = 7.07 \angle -45^\circ$$

i.  $I_A = 2.07 \cos(102.45^\circ)$ .

\*  $I_2 \text{ due } V_{S2}(t)$

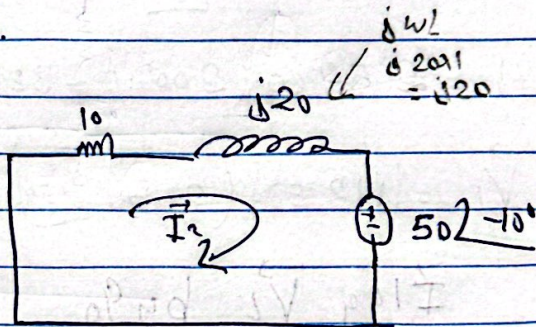

$$I_{25} = 50 \angle -10^\circ$$

$$= \frac{50 \angle 170}{10 + j20} = 2.24 \angle 106.57^\circ$$

$$i_2(t) = 2.24 \cos(20t + 106.57^\circ)$$


$$\rightarrow i(t) = i_1(t) + i_2(t)$$

$$= 7.07 \cos(10t + 45^\circ) \text{ A} + 2.24 \cos(20t + 106.57^\circ) \text{ A}$$

بمعنی کے حوالہ Time Domain, اور رابطہ کے لیے Polar  
 اور کل و امواج کے مختلف



## Nodal Analysis:

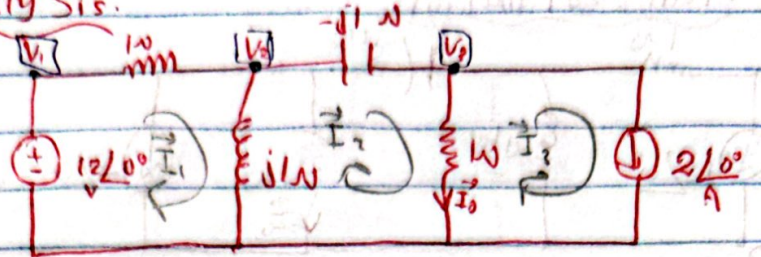

Using Nodal

$$-I_0 = \frac{V_3}{1}$$

$$\rightarrow V_1 = 12\angle 0^\circ \quad \text{--- (1)}$$

→ KCL at Node 2:

$$\frac{V_2 - V_1}{1} + \frac{V_2}{j1} + \frac{V_2 - V_3}{-j1} = 0 \rightarrow -V_1 + V_2 - jV_3 = 0 \quad \text{--- (2)}$$

KCL at Node 3:

$$\rightarrow -2\angle 0^\circ = \frac{1}{-j1} V_2 + \left(\frac{1}{-j1} + 1\right) V_3 \rightarrow -2\angle 0^\circ = -jV_2 + (1+j)V_3 \quad \text{--- (3)}$$

$$\text{Solving for } V_3 \rightarrow V_3 = \left(\frac{8}{5} + j\frac{26}{5}\right) V$$

$$\therefore I_0 = \frac{V_3}{1} = \left(\frac{8}{5} + j\frac{26}{5}\right) A$$

Using mesh Analysis.

Find  $I_0$  using mesh:

$$I_0 = I_2 - I_3 \quad \text{--- (1)}$$

→ KVL for mesh 1:

$$12\angle 0^\circ = (1+j1)\vec{I}_1 - j1\vec{I}_3 \quad \text{--- (2)}$$

→ KVL for mesh 2:

$$0 = -j1\vec{I}_1 + (1+j1-j1)\vec{I}_2 - \vec{I}_3 \rightarrow 0 = -j1 + I_2 - I_3 \quad \text{--- (3)}$$

$$I_3 = 2\angle 0^\circ A$$


$$\text{Solving for } \vec{I}_2 \text{ and } \vec{I}_3 \rightarrow I_2 = \left(\frac{18}{5} + j\frac{26}{5}\right) A$$

$$\rightarrow I_0 = 2\angle 0^\circ A$$


$$\therefore I_0 = \left(\frac{18}{5} + j\frac{26}{5}\right) A$$





## Source Transformation:

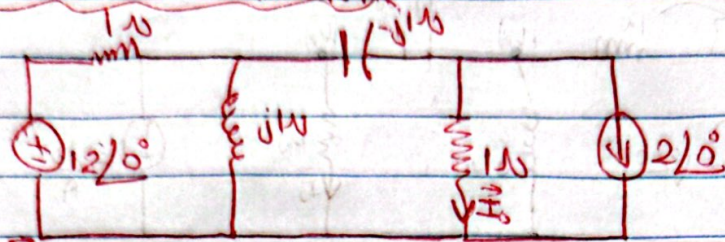


Find  $I_0$  using source transformation

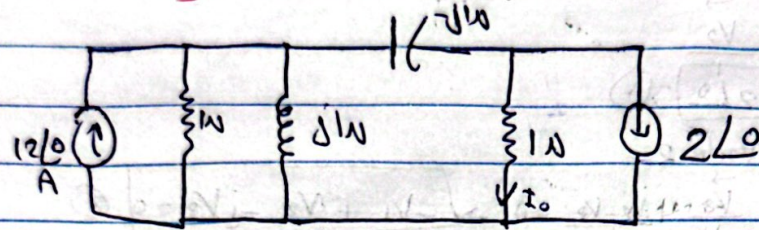
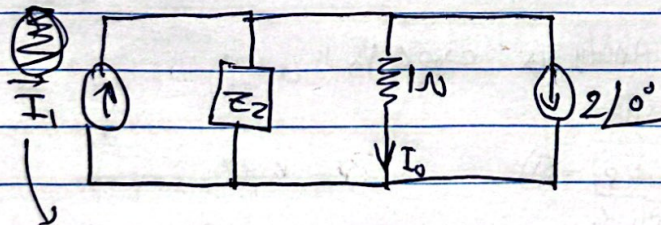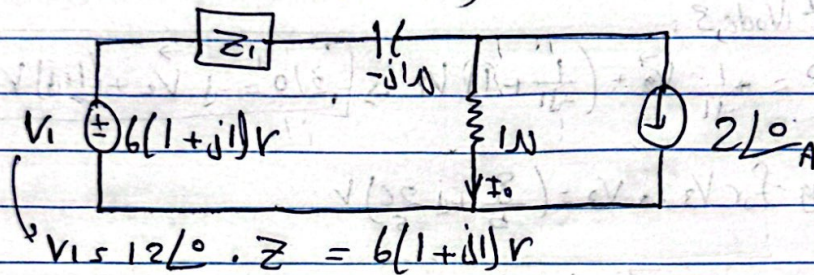
$$-Z_1 = 1\Omega \parallel j1\Omega = \left(\frac{1}{2} + j\frac{1}{2}\right)\Omega$$


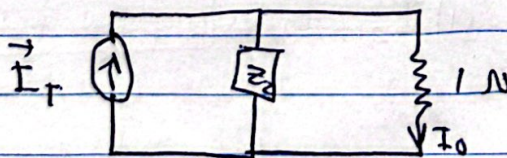
$$I_1 = \frac{V_1}{Z_1} = \frac{12(1+j1)}{1-j1}, \quad Z_2 = -j1 + Z_1 = \left(\frac{1}{2} - j\frac{1}{2}\right)\Omega$$




$$I_T = I_1 + 2\angle 0^\circ \rightarrow I_T = \left(\frac{10+j14}{1-j1}\right) A$$

$$I_0 = \frac{Z_T}{Z_T + 1} \quad \boxed{I_T = \left(\frac{8}{5} + j\frac{26}{5}\right) A}$$




## Superposition:

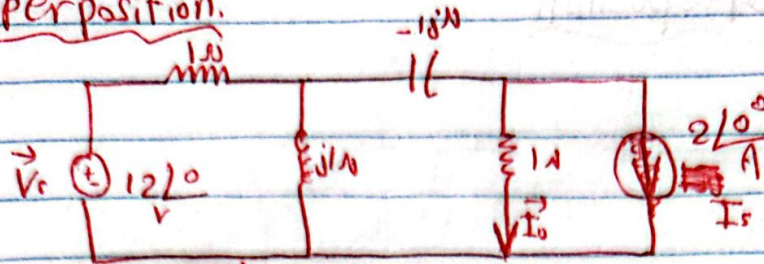

Find  $\vec{I}_0$  using Superposition:


1)  $\vec{I}_{01}$  due to  $\vec{V}_s$

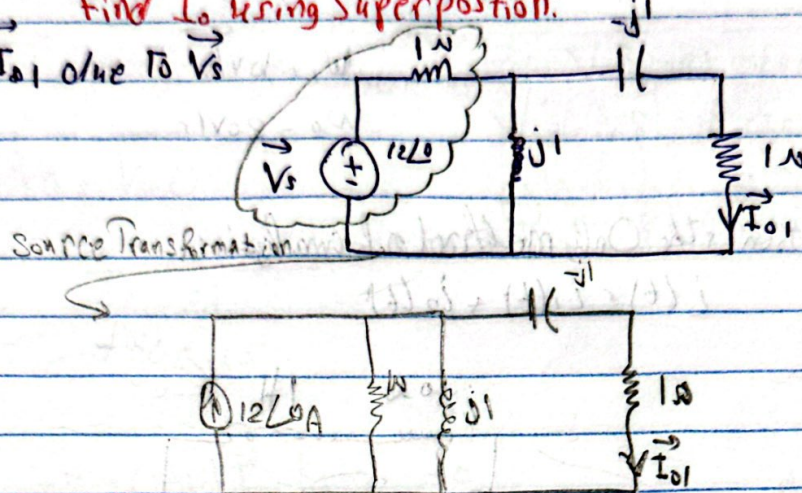

$$\vec{I}_{01} = \frac{(1/j1)}{(1/j1) + (1-1j)} \times 12\angle 0^\circ$$

$$= \frac{12}{1-j2} \text{ A}$$

2)  $\vec{I}_{02}$  due to  $\vec{I}_s$

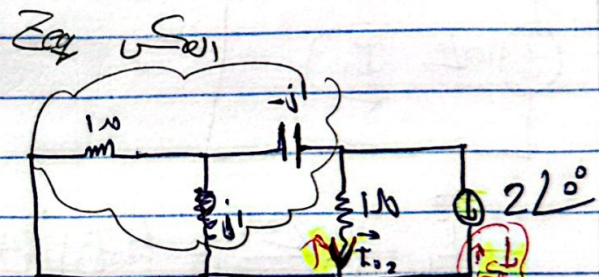

$$\vec{I}_{02} = \frac{\vec{Z}_{eq}}{\vec{Z}_{eq} + 1} \times 2$$

$$= \frac{\vec{Z}_{eq}}{\vec{Z}_{eq} + 1} \times 2\angle 180^\circ$$

$$= \frac{[j1/j1] - j1}{(1/j1) - j1 + 1} \times 2\angle 180^\circ$$

$$\vec{Z}_{eq} = \{ [1/j1] - j1 \}$$

لا السالب يعني لايهم اللفظ  
Polar  $180^\circ$  الزاوية بالأسفل


$$= \frac{2}{2+j1}$$

$$\therefore \vec{I}_0 = \vec{I}_{01} + \vec{I}_{02}$$

$$= \left( \frac{8}{5} + j\frac{26}{5} \right) \text{ A}$$



## \* The Power of Superposition

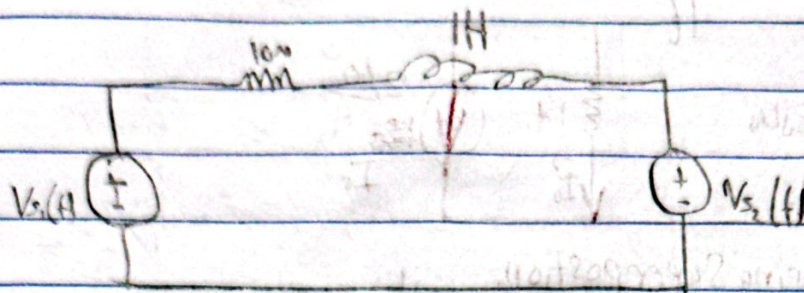

$$V_1(t) = 100 \cos 10t \text{ V}$$


$$W_1 = 10 \text{ V/s of } 10t$$

$$V_2(t) = 50 \cos(20t - 10^\circ) \text{ V}$$

$$W_2 = 20 \text{ V/s}$$

\* Superposition is the Only method of analysis:-


$$i(t) = i_1(t) + i_2(t)$$

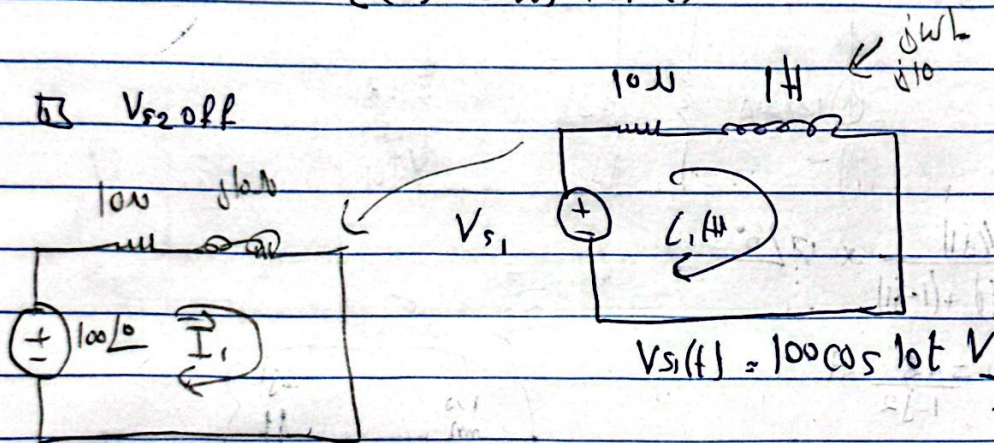

$$V_1(t) = 100 \cos 10t \text{ V}$$

$$\vec{I}_1 = \frac{100 \angle 0^\circ}{10 + j10} = 7.07 \angle -45^\circ \text{ A}$$
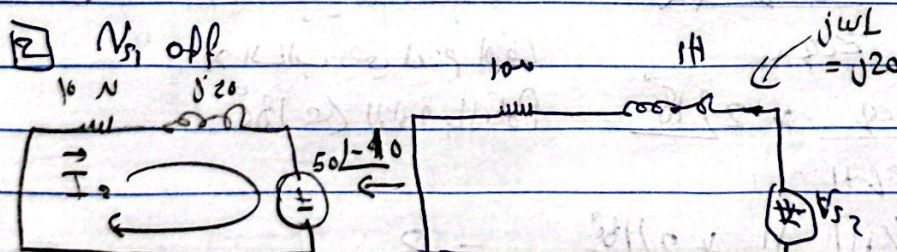
$$i_1(t) = 7.07 \cos(10t - 45^\circ) \text{ A}$$




$$\vec{I}_2 = \frac{-50 \angle -10^\circ}{10 + j20} = \frac{50 \angle 170^\circ}{10 + j20}$$

$$i_2(t) = 2.24 \cos(20t + 106.57^\circ) \text{ A}$$

$$\therefore i(t) = 7.07 \cos(10t - 45^\circ) + 2.24 \cos(20t + 106.57^\circ) \text{ A}$$




## Thévenin's and Norton's Theorems:

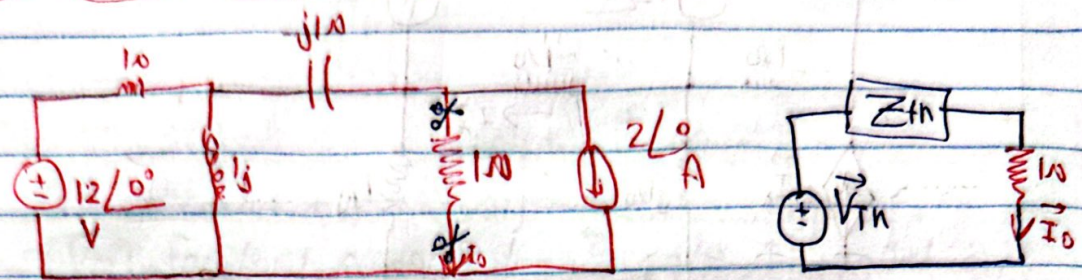

Find  $I_o$  using Ther.

$\vec{V}_{Th}, \vec{V}_o$

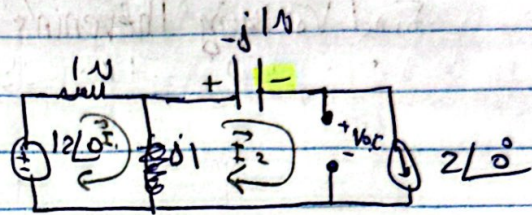

At  $I_2$   $\vec{I}_2 = 2A$

$$= 2 + j0$$

$$= 2 \angle 0^\circ$$

At  $I_1$   $-12 + (1 + j1)\vec{I}_1 - j1(2) = 0$

$$\rightarrow \vec{I}_1 = \frac{12 + j2}{1 + j1} = \boxed{7 - j5A}$$

$\vec{V}_{Th} = \vec{V}_{-j1} + \vec{V}_{j1}$

$$= -(-j1)(\vec{I}_2) + (j1)(\vec{I}_1 - \vec{I}_2)$$


$$= +j1 \times 2 + j1(7 - j5 - 2)$$

$$= j2 + j5 + 5$$

$$= \boxed{5 + j7V}$$

$\hookrightarrow \vec{Z}_{Th} = [1/j1] + -j1$

$$= \frac{1}{j} - j1$$

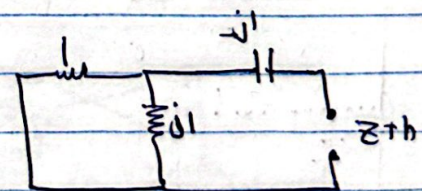

$$\vec{I}_o = \frac{\vec{V}_{Th}}{\vec{Z}_{Th} + 1} = \frac{5 + j7}{\frac{1}{j} - j1 + 1}$$

$$= \boxed{\frac{8}{5} + j\frac{26}{5}}$$

