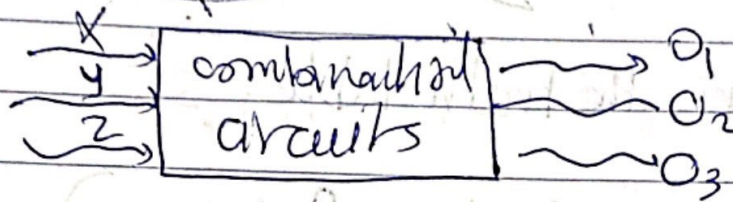



Ch 4 combinational circuits (Design)

Two types of digital circuits

① Combinational circuits (Ch 4): output only depends on input




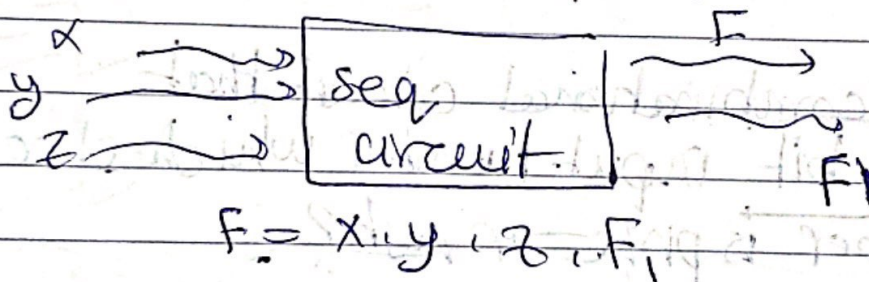② sequential circuit (Ch 5 & Ch 6): output depends on inputs and previous outputs.



$$F = x, y, z, F_1$$

combinational circuit

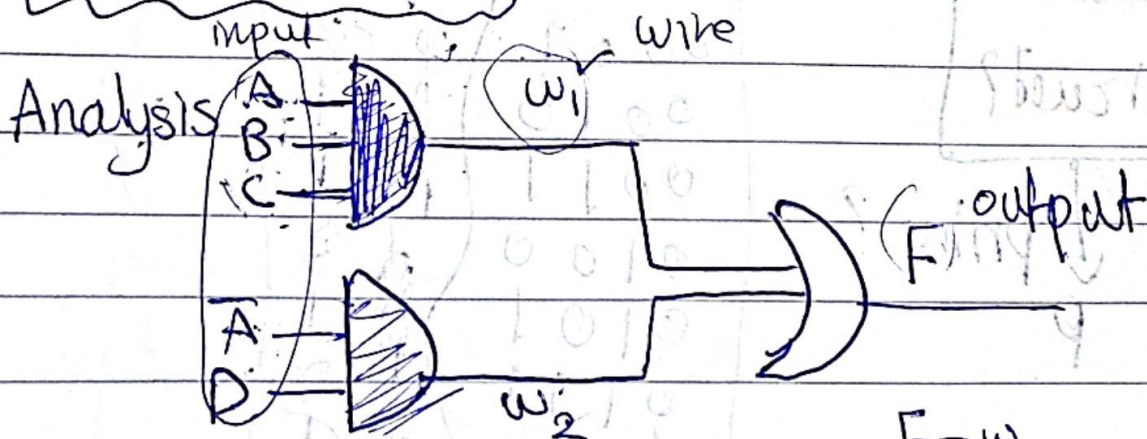

$$w_1 = A \cdot B \cdot C$$

$$w_2 = \bar{A} \cdot D$$


$$F = w_1 + w_2$$

$$F = \underbrace{A \cdot B \cdot C}_{\text{input}} + \underbrace{\bar{A} \cdot D}_{\text{input}}$$


Design procedure \Rightarrow

- ① you need to read the problem carefully.
- ② Determine the number of inputs & outputs.
- ③ Assigns letter symbols to inputs & outputs.
- ④ determine the truth table.
- ⑤ Simplify the boolean function.
- ⑥ Design the circuits.

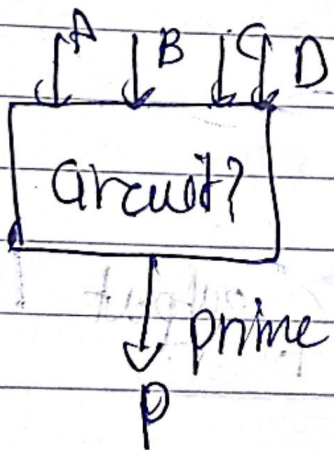
Ex. Design a combinational circuit that takes 4 bit input number which checks if the number is prime or not?




A	B	C	D	p
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1

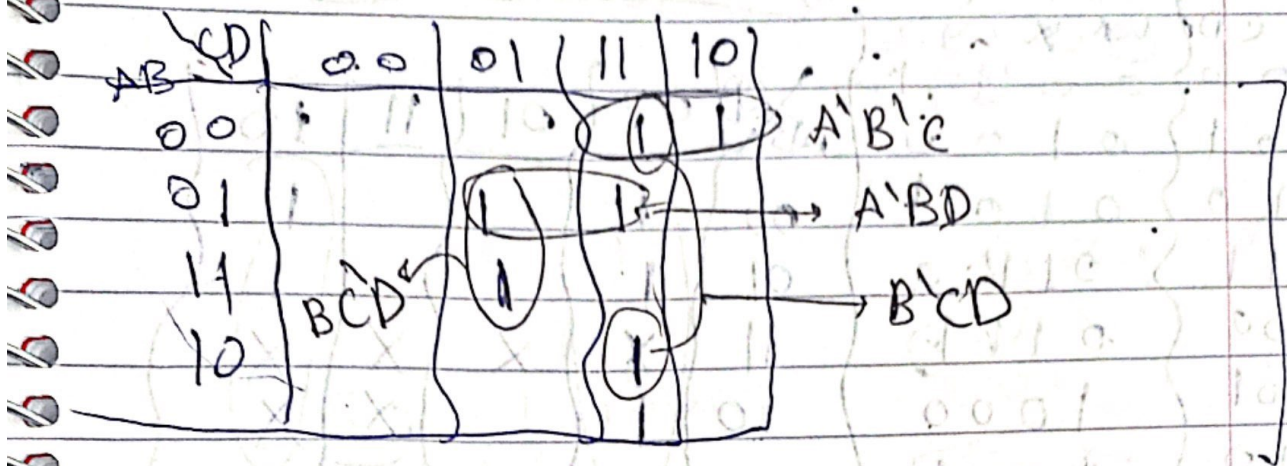

$$P = A'B'C + A'BD + B'C'D + B'CD$$

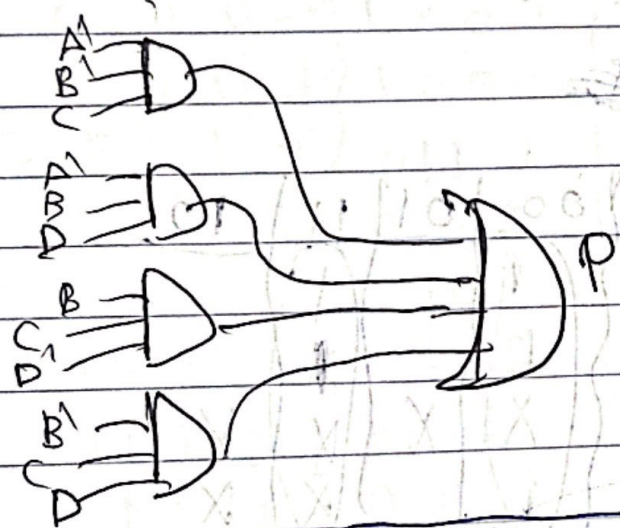

Design BCD to excess-3 code conversion?

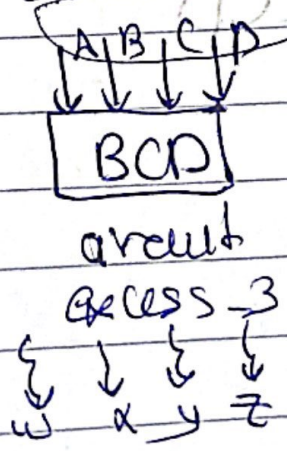

BCD	excess
0000	0011

input (BCD) output (excess 3)

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	1
1	0	1	1	1	1	1	0
x	x	x	x	x	x	x	x
x	x	x	x	x	x	x	x
x	x	x	x	x	x	x	x
x	x	x	x	x	x	x	x



AB	CD	00	01	11	10
00	00	1			1
01	00	1			1
11	00	X	X	X	X
10	00	1		X	X

$$z = D'$$


AB	CD	00	01	11	10
00	00	1			
01	00	1			
11	00	X	X	X	X
10	00	1		X	X

$$y = C'D' + CD$$

X is 1 & 0
w is 0

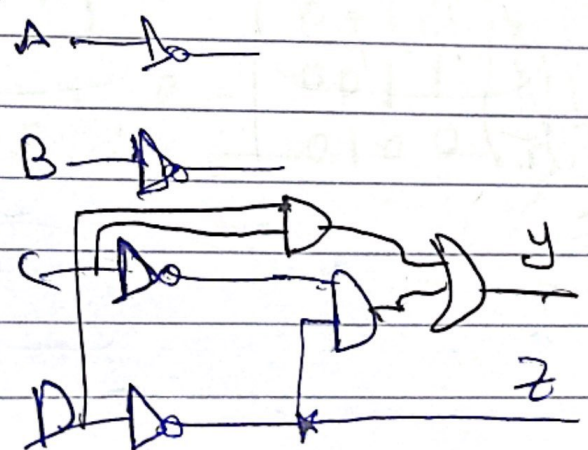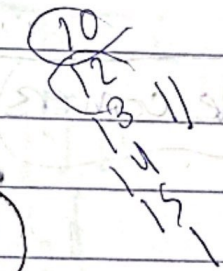

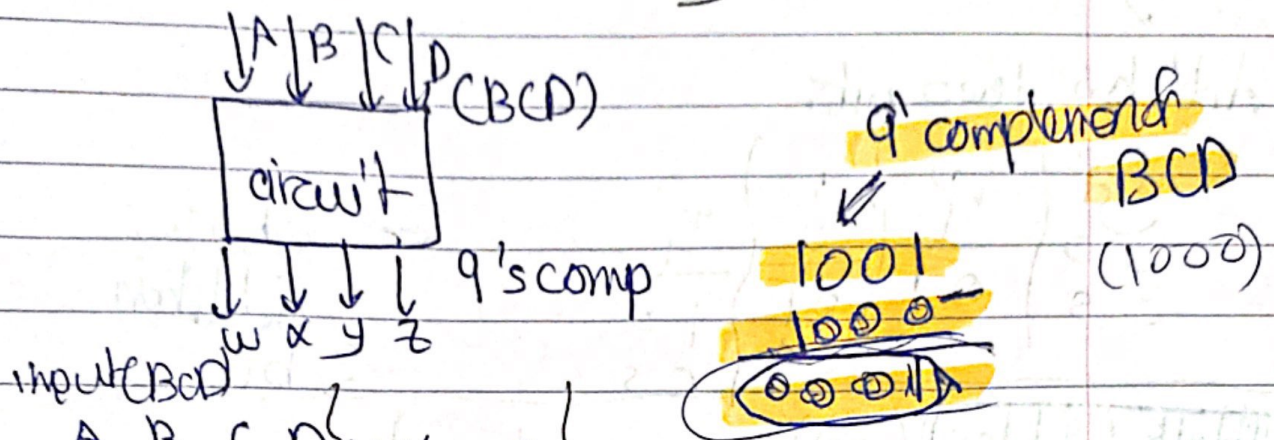design a combinational circuit that generate the 9's comp of a BCD digit?



input BCD

A	B	C	D	w	x	y	z
0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	0	0
0	1	1	0	0	0	1	1
0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0
x	x	x	x	x	x	x	x
x	x	x	x	x	x	x	x
x	x	x	x	x	x	x	x
x	x	x	x	x	x	x	x

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	x	x	x	x
10	1		x	x

$z = D'$

AB \ CD	00	01	11	10
00			1	1
01			1	1
11	x	x	x	x
10			x	x

$y = C$

$x, w \leftarrow 1001$


1) Half Adder

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \begin{array}{r}
 0 \\
 0 \\
 \hline
 0
 \end{array}
 \begin{array}{r}
 1 \\
 0 \\
 \hline
 1
 \end{array}
 \begin{array}{r}
 1 \\
 1 \\
 \hline
 10
 \end{array}$$

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = AB$$

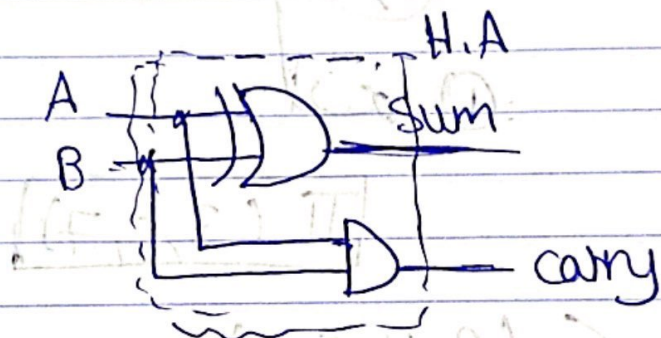

2) Full adder

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \begin{array}{r}
 0 \\
 1 \\
 1 \\
 \hline
 0
 \end{array}$$

A	B	C _{in}	C _{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


A \ B C _{in}	00	01	11	10
0	0	1	0	1
1	1	0	1	0

لوحه دالة
⊕


$$\begin{aligned}
 \text{Sum} &= A'BC + A'BC' + AB'C' + ABC \\
 &= A'(B'C + BC') + A(B'C' + BC) \\
 &= A'(B \oplus C) + A(B \odot C) \\
 &= A \oplus (B \oplus C)
 \end{aligned}$$

A \ B C _{in}	00	01	11	10
0	0	0	1	0
1	0	1	1	1
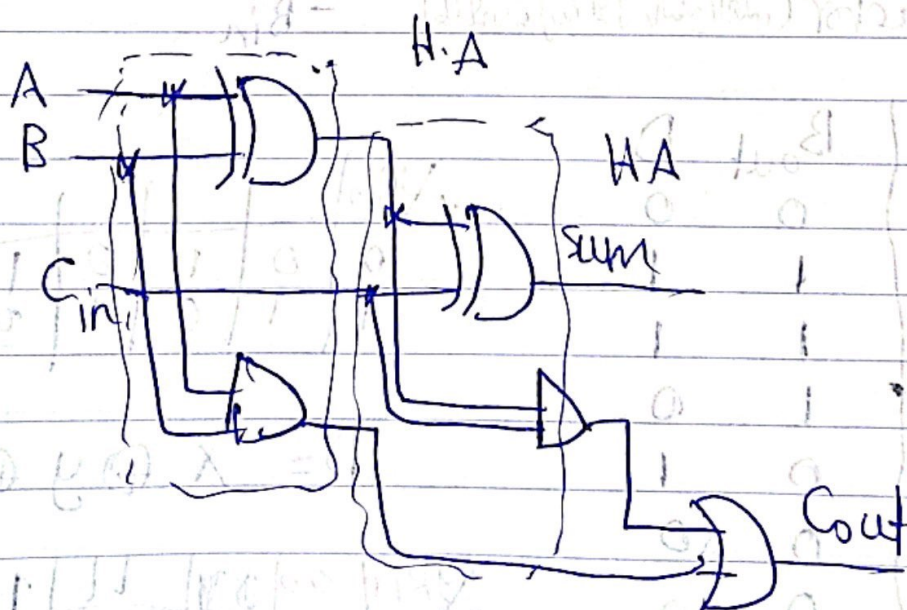
$$\begin{aligned}
 C_{out} &= AB + A'BC + AB'C \\
 &= AB + C(A'B + AB') \\
 &= AB + C(A \oplus B)
 \end{aligned}$$






$$\text{FA} = 2\text{HA} + \text{OR}$$

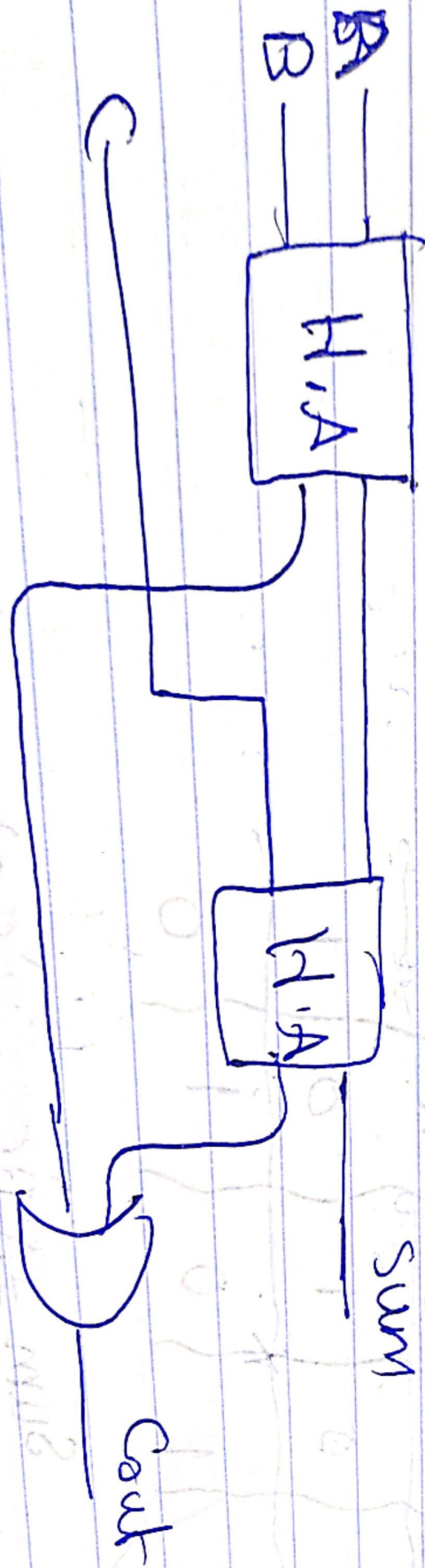


4 - Bit Adder
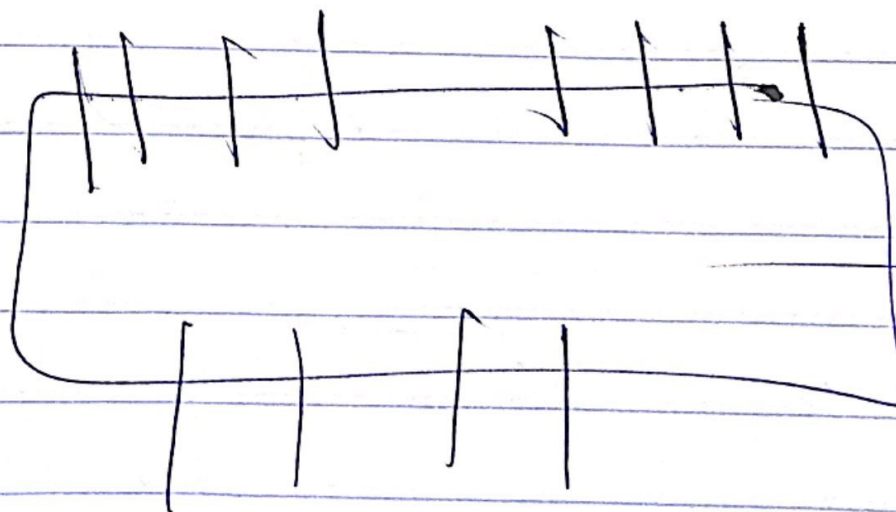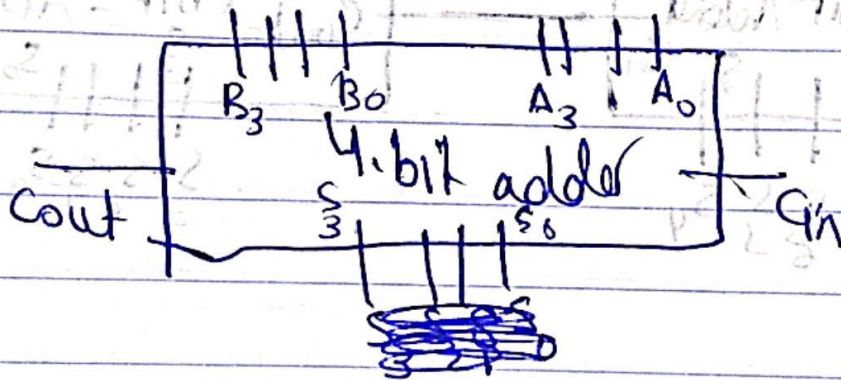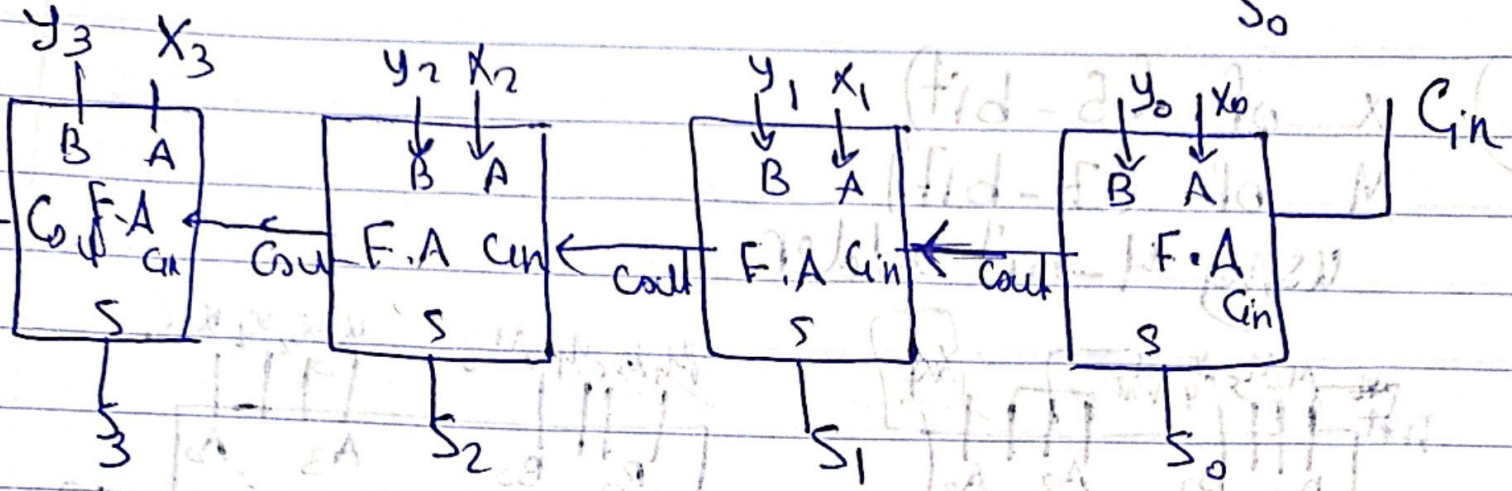
$$\begin{array}{r}
 \textcircled{1} \\
 \begin{array}{cccc}
 X & X_3 & X_2 & X_1 & X_0 \\
 + & Y & Y_3 & Y_2 & Y_1 & Y_0 \\
 \hline
 & & & & S_0
 \end{array}
 \end{array}$$




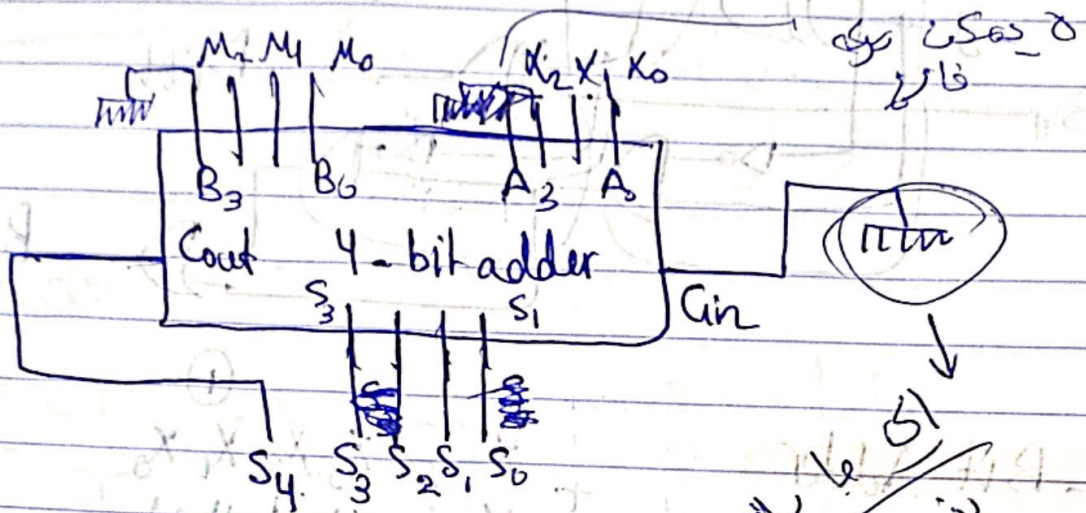
Design a logical circuit to add
 X of (2-bit) to M of (8 bit)
 using 4-bit adder in your design



المجموع 6 بت
 256 بت
 256 بت

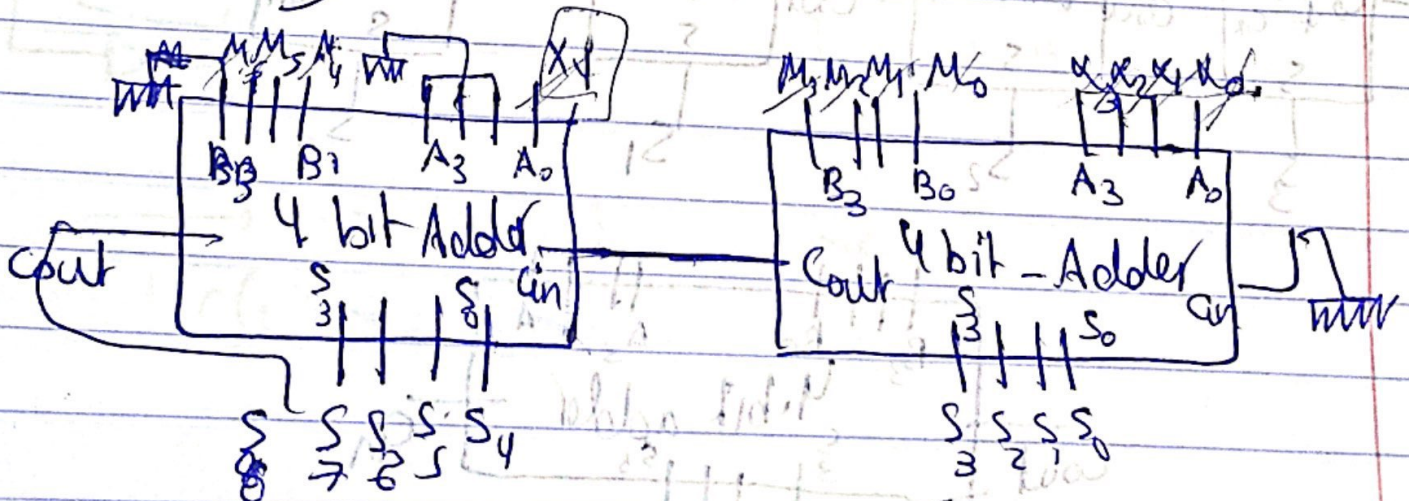Ex: X of (5-bit)
 M of (7-bit)
 using 4-bit adder



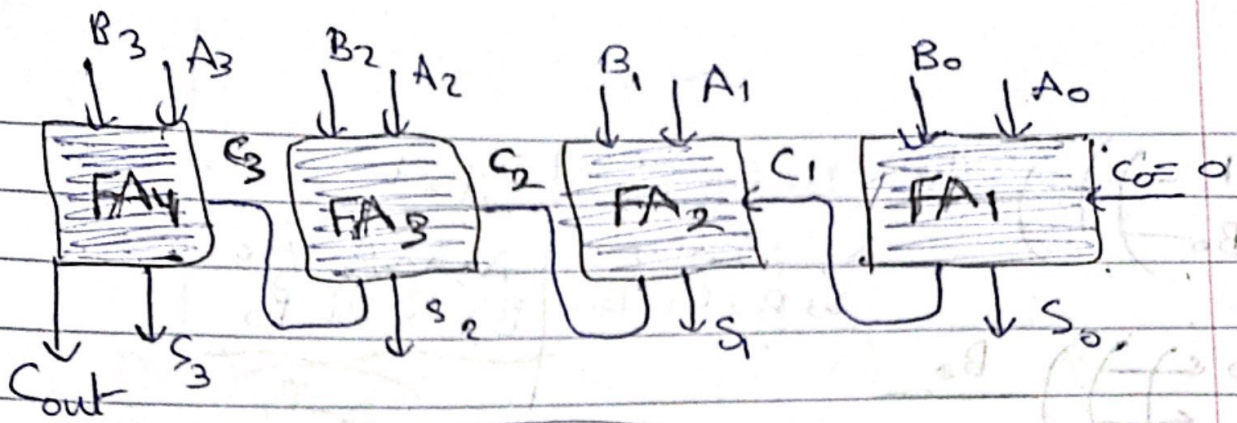

Binary Subtractor

$$A + 2^{\text{nd}} \text{ comp } B$$

$$A - B = A + 2^{\text{nd}} \text{ comp } B$$



$$A + 1^{\text{st}} \text{ comp } + 1(B)$$




$$A + B^- + 1$$

$$A = 1010$$

$$B = 0011$$


$$A - B$$

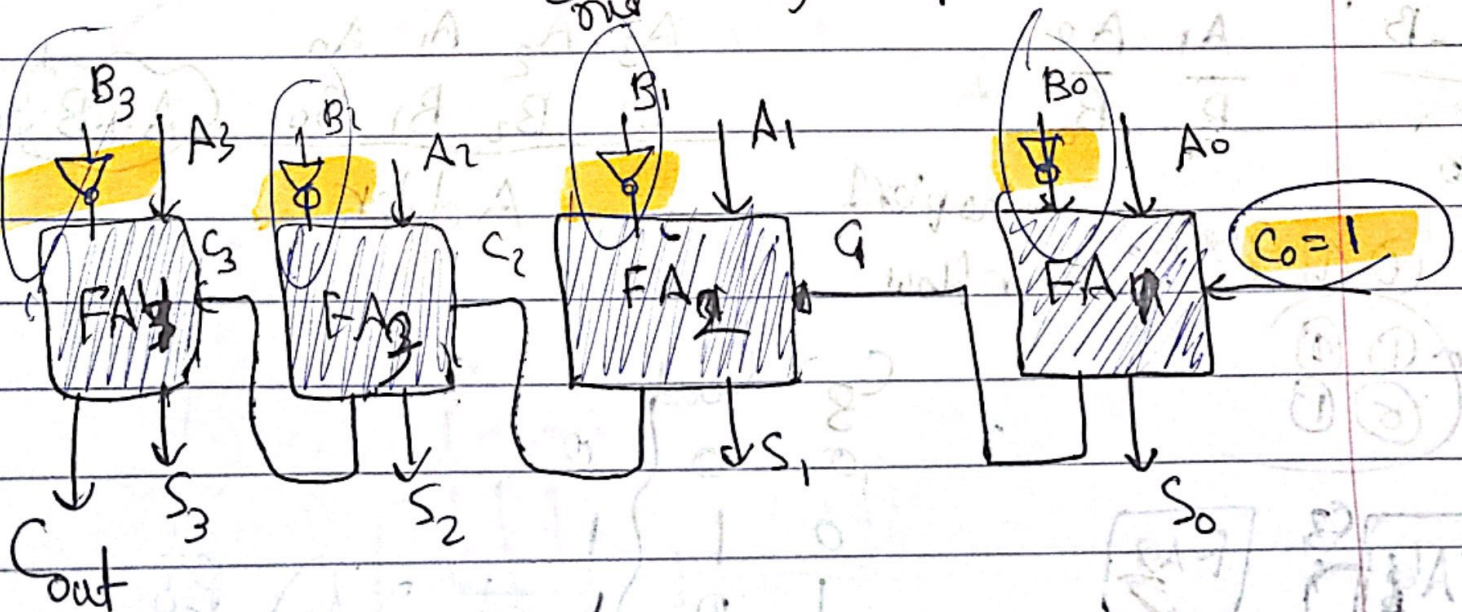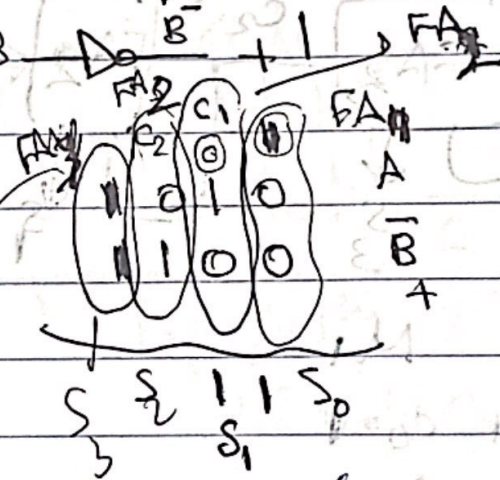

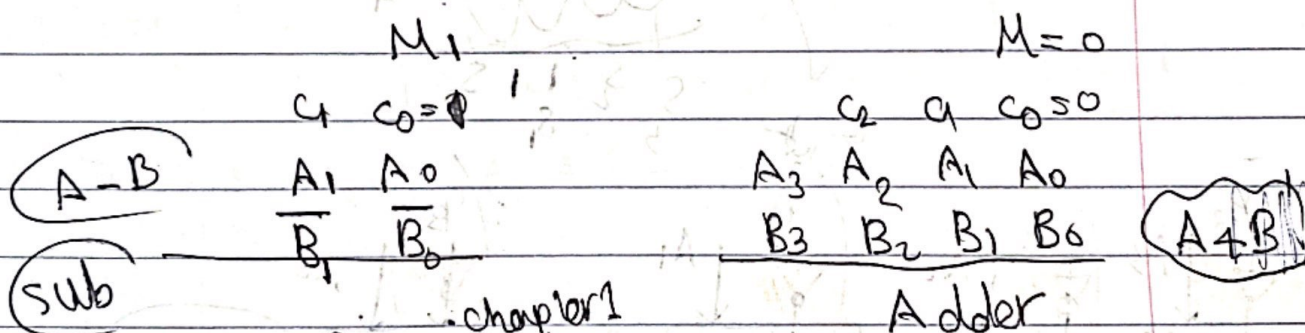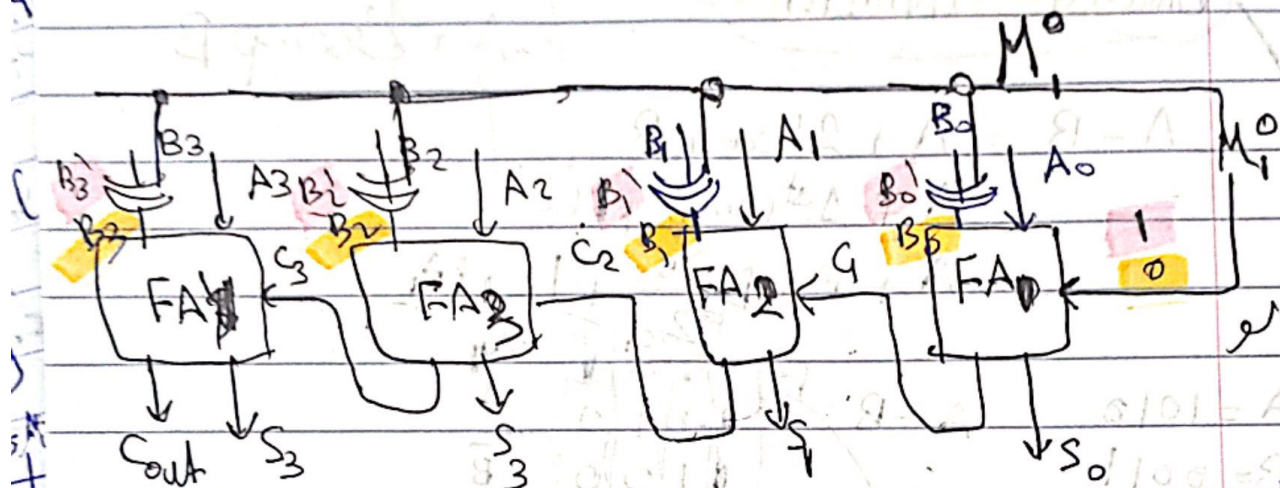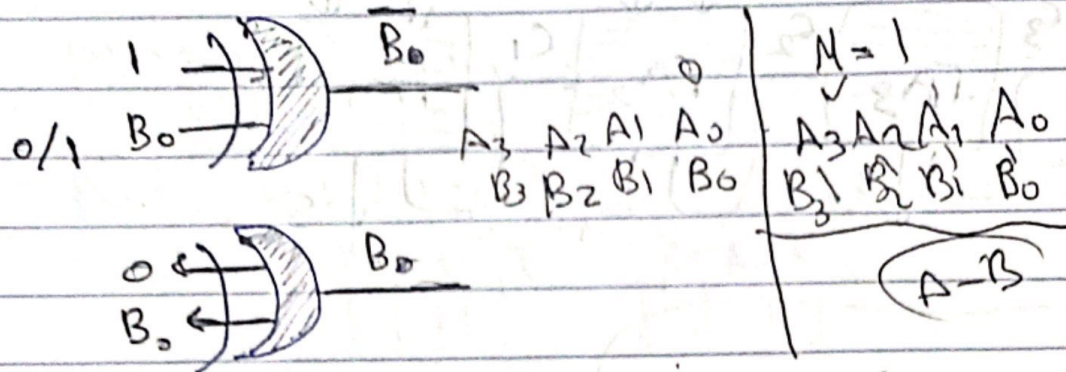


chapter 1
over flow

over flow

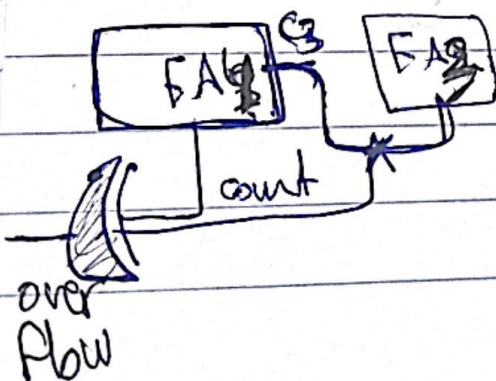

Count

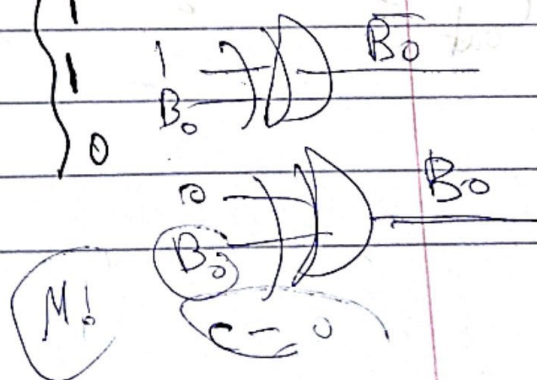

5 full adder

Design 5 bits binary adder?] X

BCD Adder (Decimal Adder)

8
+4
0 1 0 1
0 1 0 0

0 1 0 0 1 valid

yes


8
+5
0 1 0 1
0 1 0 1

0 1 0 1 0

0 1 1 0 2's

addition

Binary 4 bits. Cout

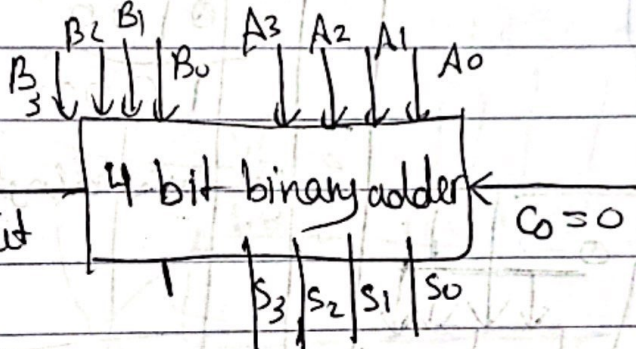

1 0 0 1
↑
اذا صار واحد

Ⓛ


او اذا صار واحد

8
+5
0 1 0 1
0 1 0 1
0 1 0 1 0

4 full adder * يوجد

8
+9
1 0 0 1
1 0 0 1
0 0 0 1 0
count = 1

0 8 6 4
9 6 3 0
9 6

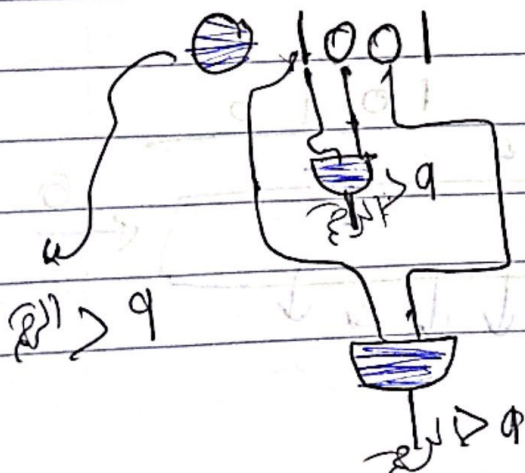

9 > 9

9 > 9


Binary Multiplier

$$\begin{array}{r} 42 \\ 16 \\ \hline 252 \\ 420 \\ \hline 672 \end{array}$$

$1 \times 0 = 0$
 $0 \times 1 = 0$
 $0 \times 0 = 0$
 $1 \times 1 = 1$

AND

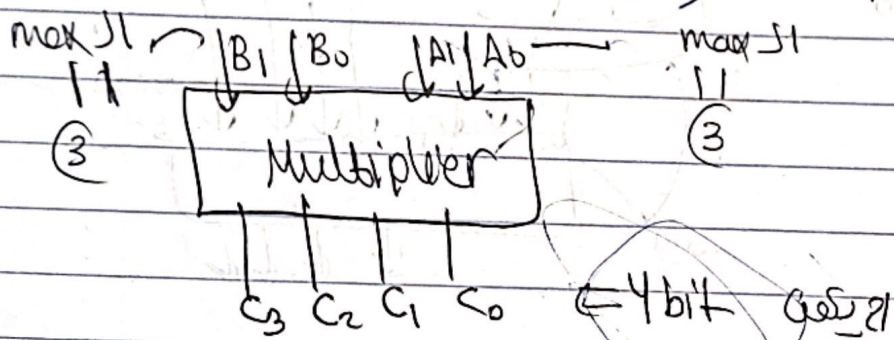Design a 2bit \times 2bit binary multiplier.



A ₁	A ₂	B ₁	B ₂	C ₁	C ₂	C ₃	C ₄
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	1	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0				
1	1	1	1	1	0	0	0

$$\begin{array}{r} 20 \\ 20 \times \\ \hline 40 \end{array}$$

00
X0

$$\begin{array}{r} 01 \\ \hline 10 \end{array}$$

$$\begin{array}{r} 100 \\ 100 \\ \hline 200 \end{array}$$


$A_1 A_0 \backslash B_1 B_0$	00	01	11	10
00				
01		1	1	
11			1	
10				

اربع مربعیات (4 squares)


co der

C_3
 C_2
 C_1
 C_0

2 bit x 2 bit binary multiplier ← truth

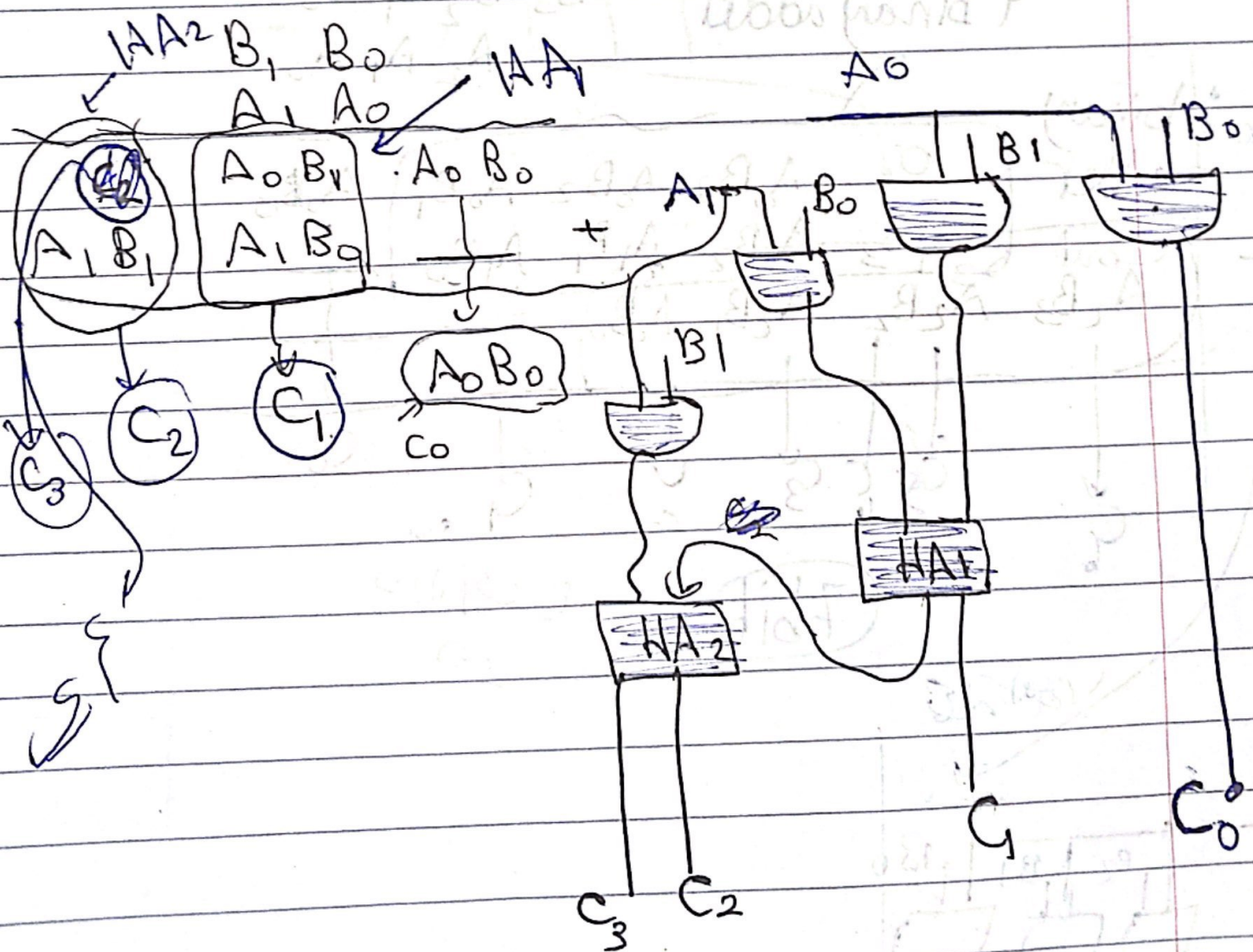


Design 4 bits x 3 bits multiplier

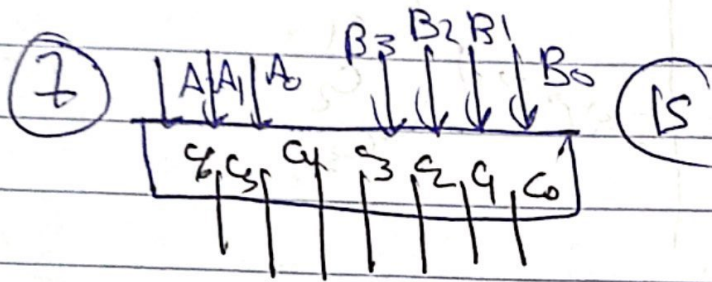


4 binary adder

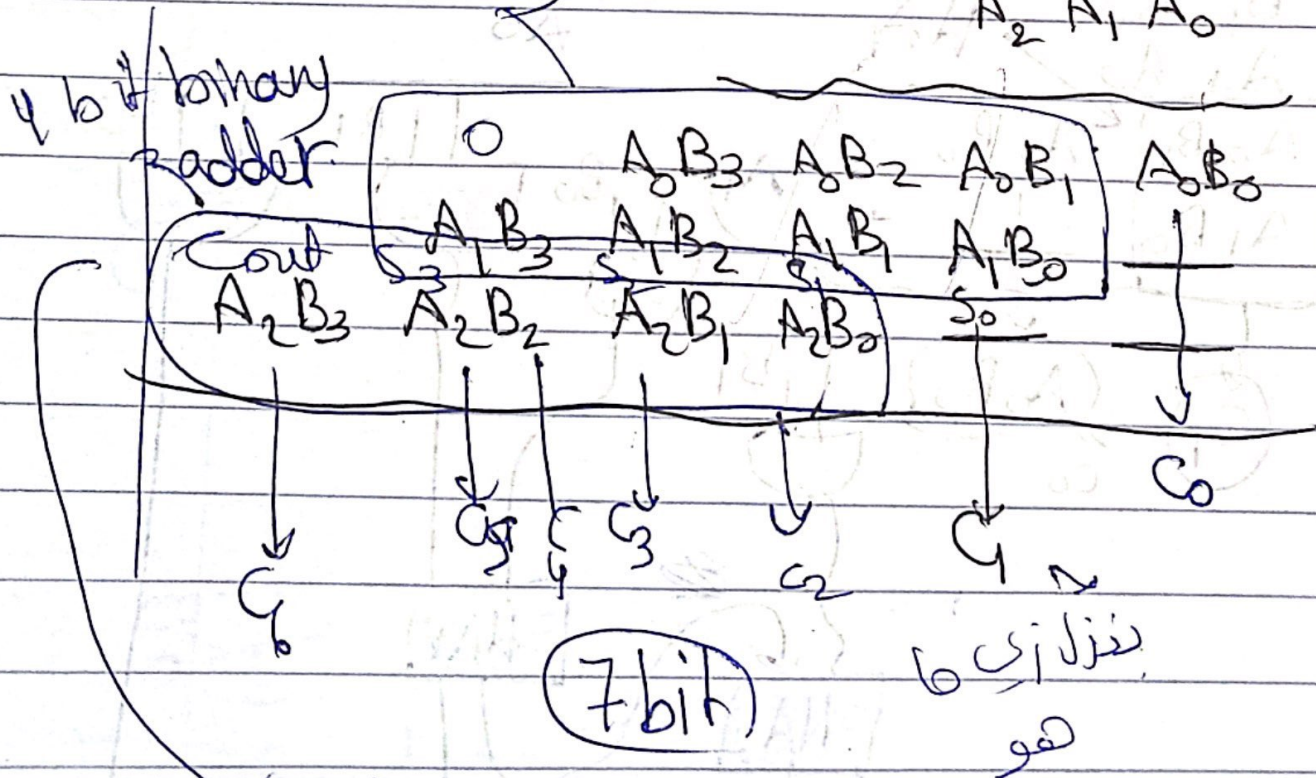$B_3 \ B_2 \ B_1 \ B_0$
 $A_2 \ A_1 \ A_0$




نتیجه

A₀

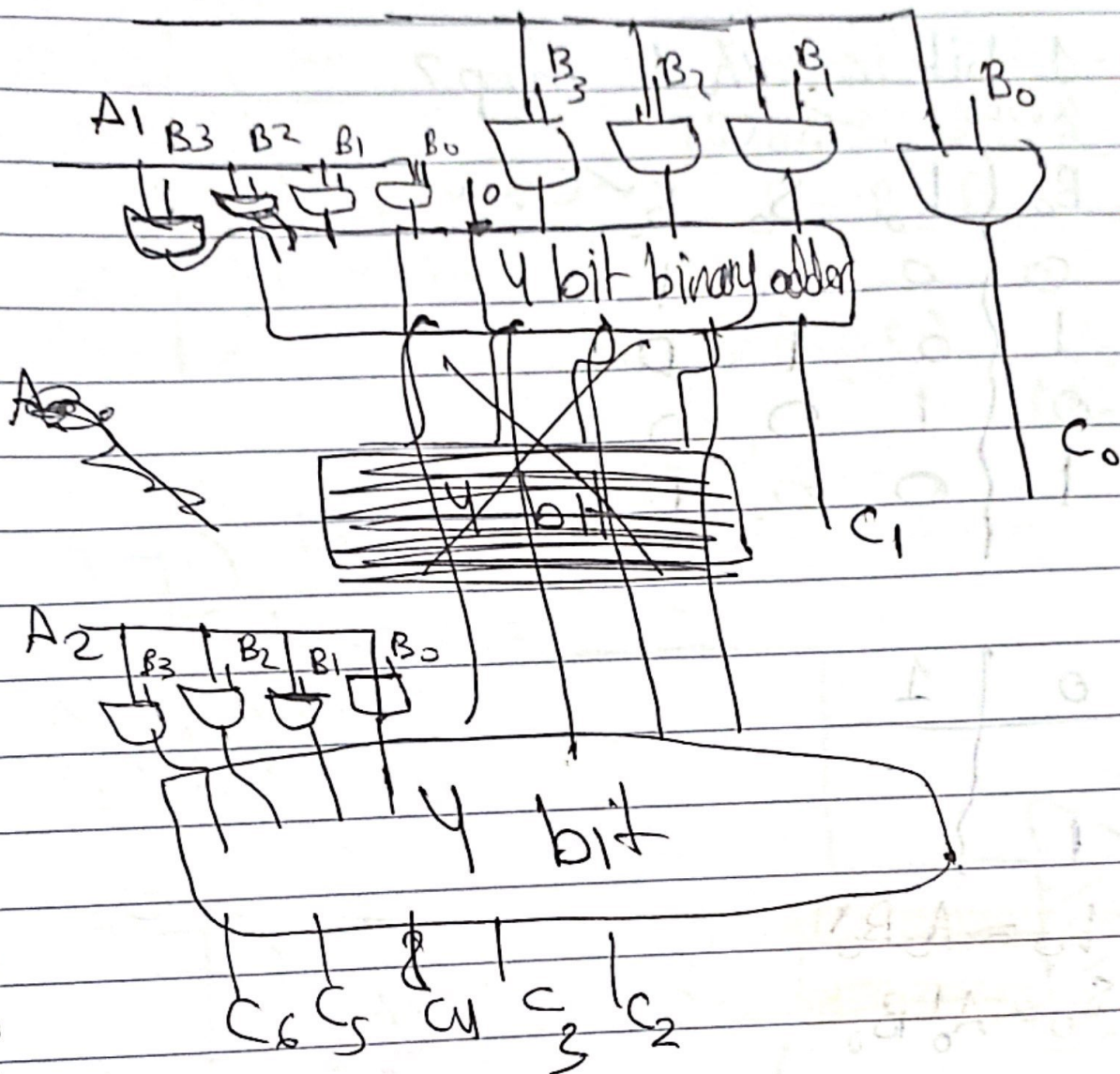

magnitude computer

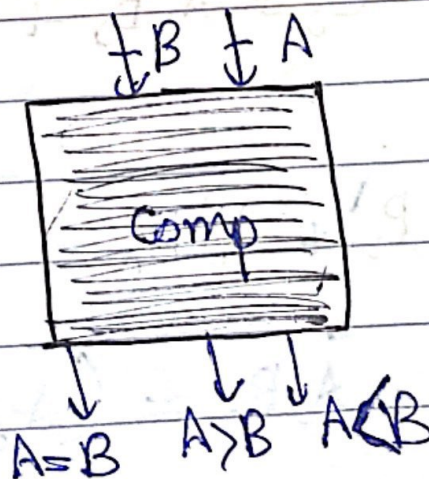

Design 1 bit magnitude comp?

		$A_0 > B_0$		$A_0 < B_0$		$A_0 = B_0$	
A_0	B_0	L_0	S_0	L_0	S_0	E_0	Equal
0	0	0	0	0	0	1	
0	1	0	1	1	0	0	
1	0	1	0	0	1	0	
1	1	0	0	0	0	1	

$A_0 \backslash B_0$	0	1
0	0	0
1	1	0

$$L_0 = A_0 B_0'$$

$$S_0 = A_0' B_0$$


$A_0 \backslash B_0$	0	1
0	1	0
1	0	1

$$E_0 = A_0' B_0' + A_0 B_0$$

$$L_0 + S_0 = A_0 B_0' + A_0' B_0 = A_0 \oplus B_0$$

$$E_0 = A_0' B_0' + A_0 B_0 = (A_0 + B_0)'$$

$$E_0 = (L_0 + S_0)'$$

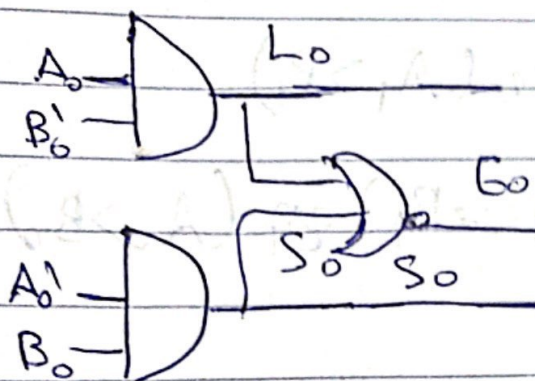





$$A = A_2 A_1 A_0$$

$$B = B_2 B_1 B_0$$

$$A=B \Rightarrow (A_2=B_2) \text{ and } (A_1=B_1) \text{ and } (A_0=B_0)$$

وإذا كانا متساويين


$$A=B$$

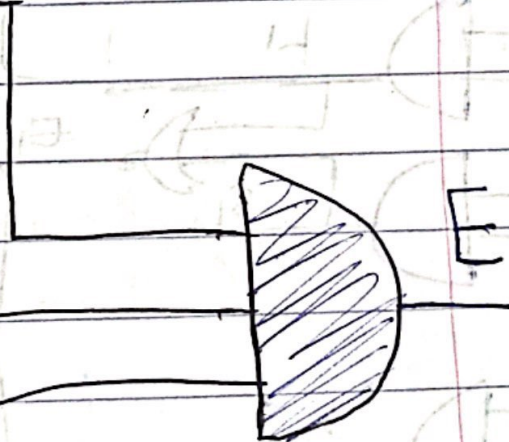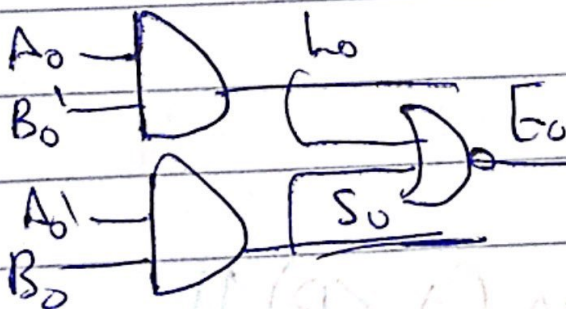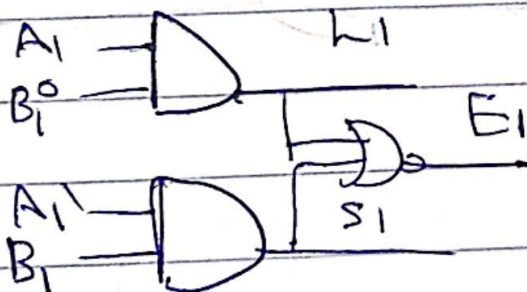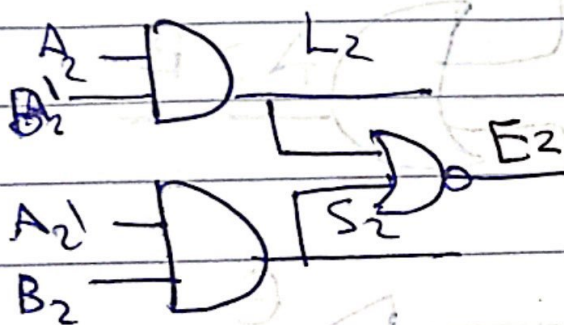

✓ 10000
01111

$$A > B = (A_2 > B_2) \parallel (A_2 == B_2) \wedge (A_1 > B_1)$$
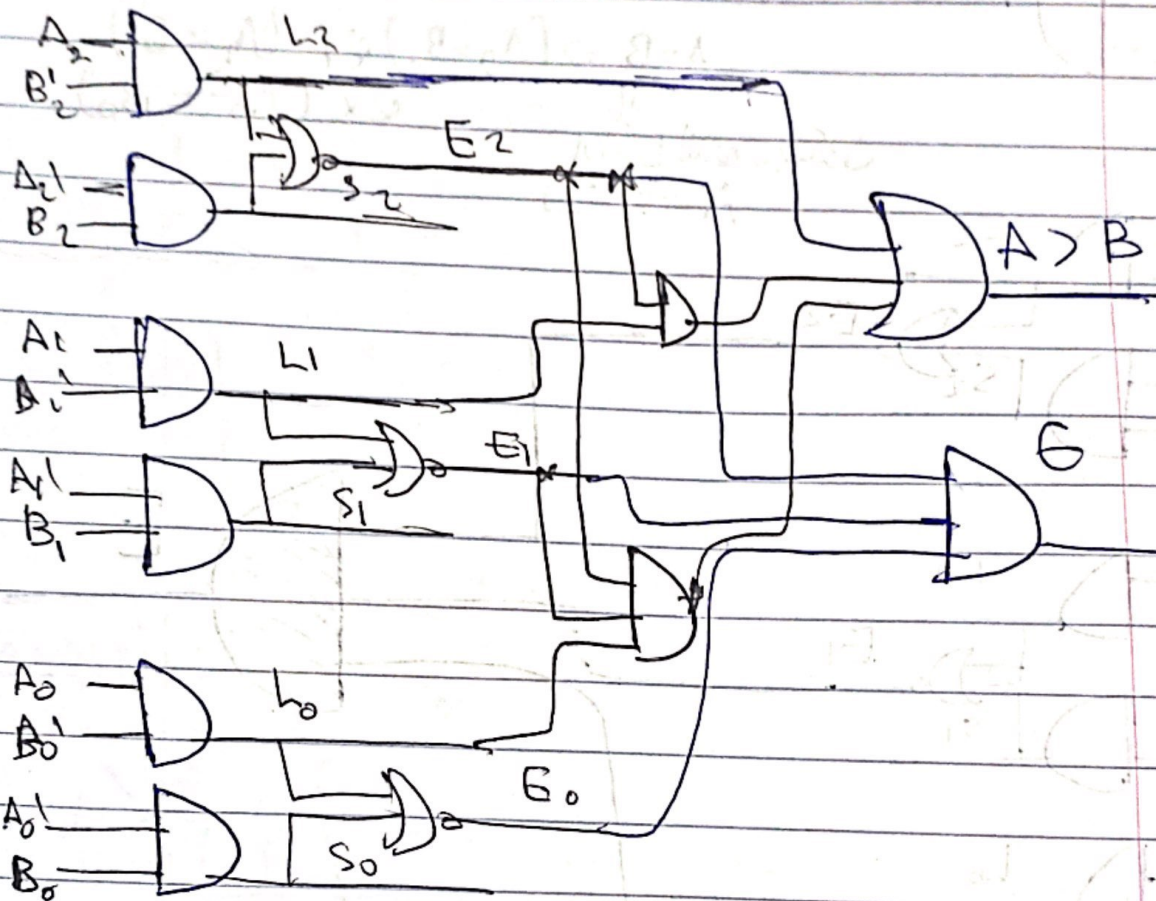
$$\parallel (A_2 == B_2) \wedge (A_1 == B_1) \wedge (A_0 > B_0)$$



$$A < B = (A_2 < B_2) \parallel (A_2 == B_2) \wedge (A_1 < B_1) \parallel$$

$$(A_2 == B_2) \wedge (A_1 == B_1) \wedge (A_0 < B_0)$$

Design 4 bit x 4 bit equality computer?


$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$


$A=B$

A	B	$(A \oplus B)$
0	0	0
0	1	1
1	0	1
1	1	0

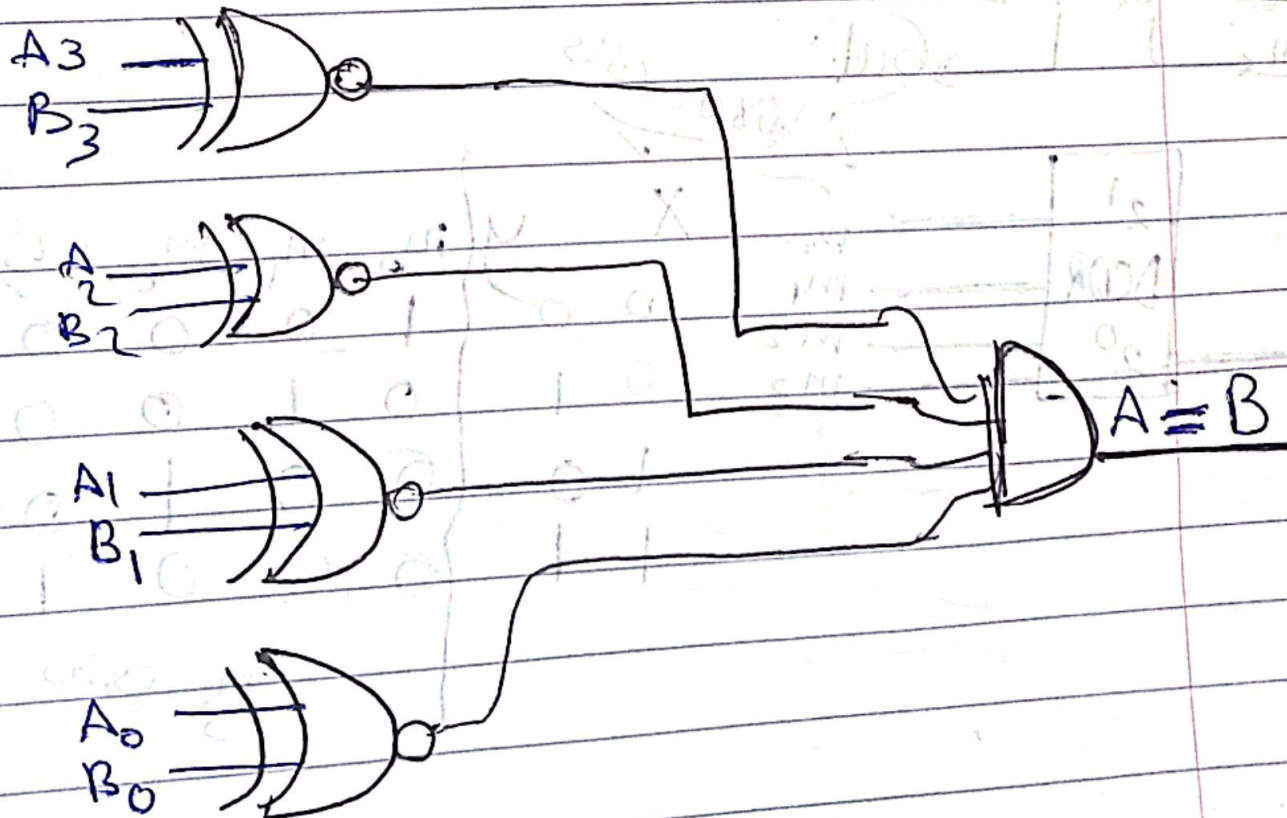
$A=B$ $(A_3=B_3) \text{ AND } (A_2=B_2) \text{ AND } (A_1=B_1) \text{ AND } (A_0=B_0)$



Decoders

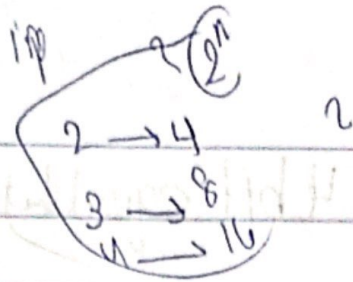


combinational circuit

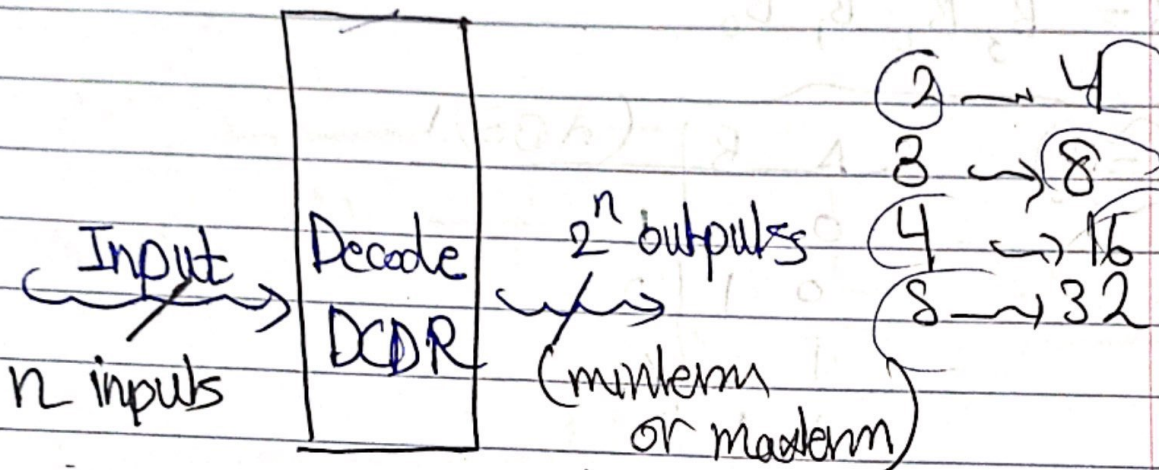

only one output is on other is off.

Ex 2x4 Decoder

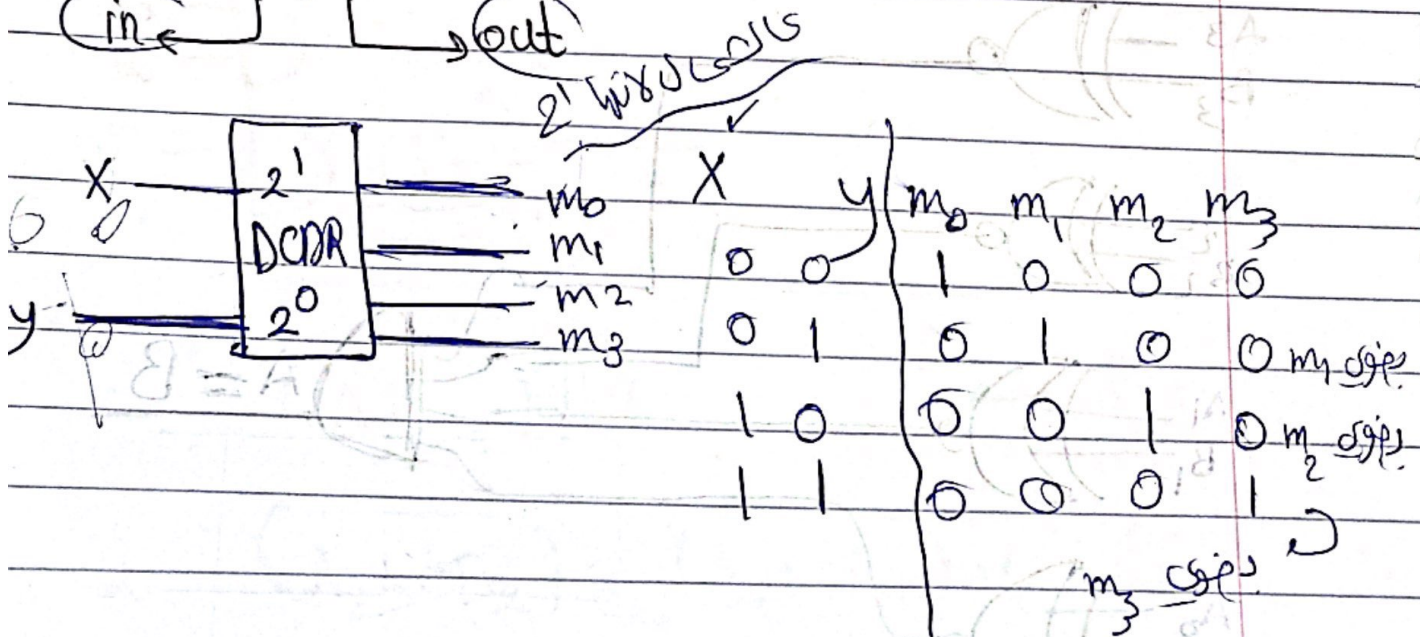


$x \backslash y$	0	1
0	0	1
1	1	0


$$m_0 = x' y'$$

Decoder
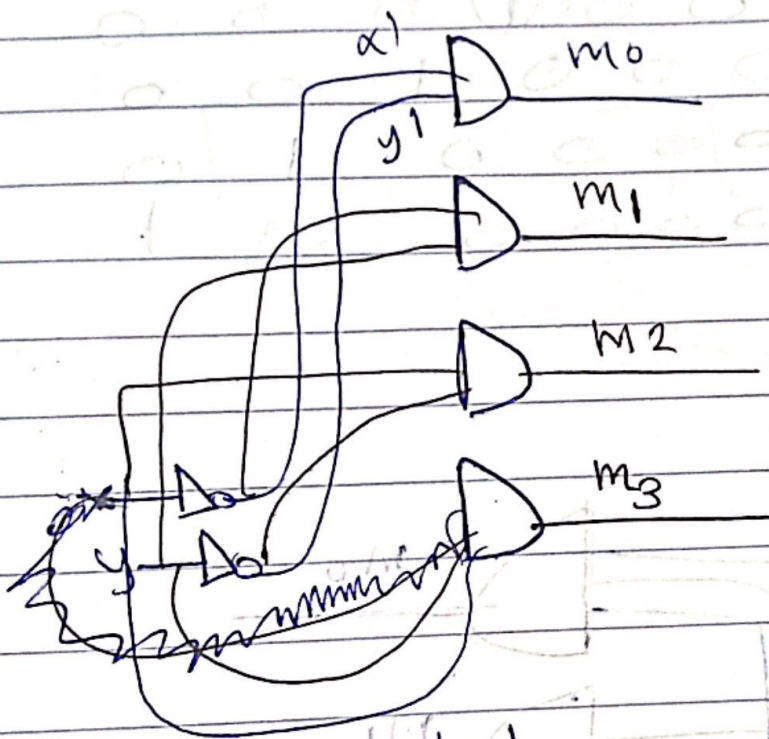
$$\begin{aligned} D_0 & \rightarrow m_0 = x' y' \\ D_1 & \rightarrow m_1 = x' y \\ D_2 & \rightarrow m_2 = x y' \\ D_3 & \rightarrow m_3 = x y \end{aligned}$$



input → output
Decoder 3 x 8

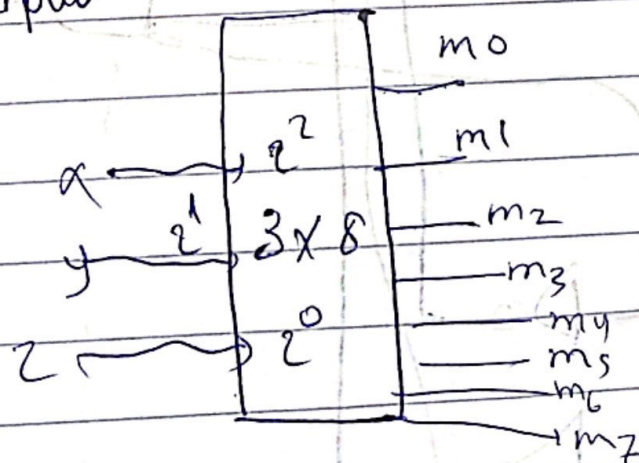

x	y	z	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$m_0 = x'y'z'$$


$$m_1 = x'y'z$$

$$m_2 = x'y z'$$

$$m_3 =$$

$$m_4$$


$$m_5$$

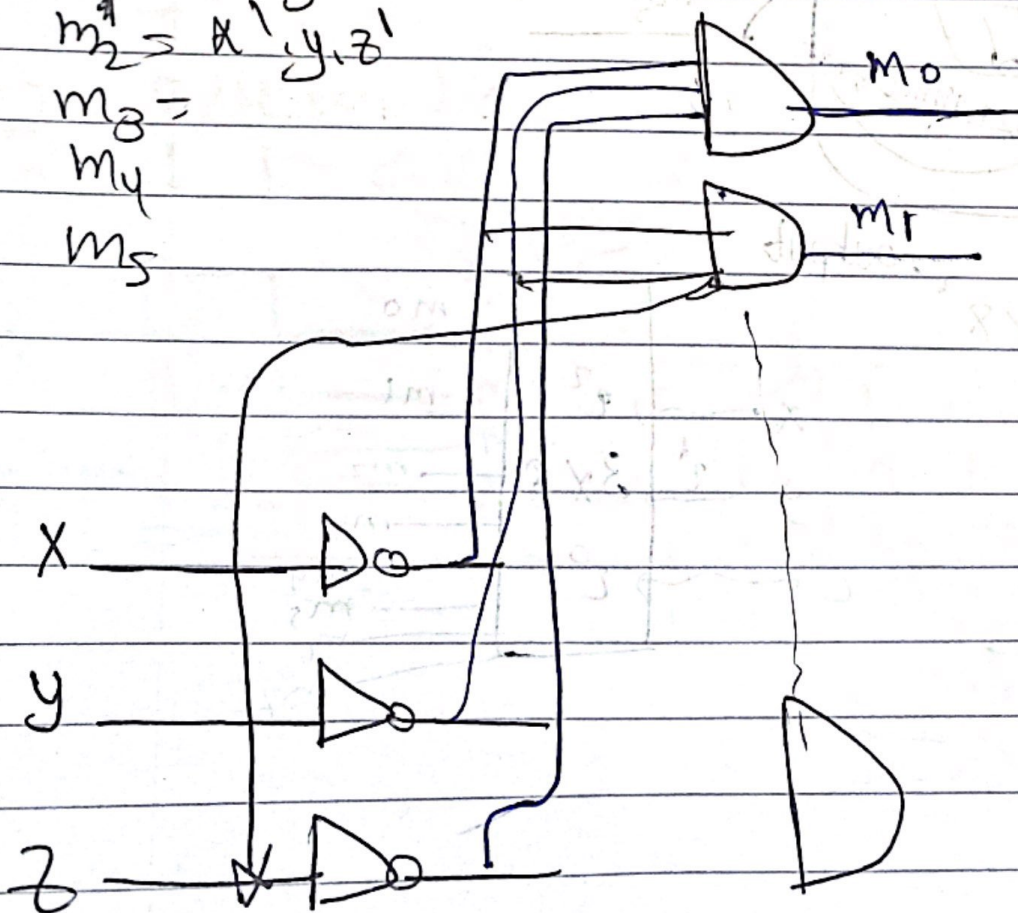

Implement the function, using decoder?

$$F_1(x, y) = \Sigma(0, 3) = m_0 + m_3$$
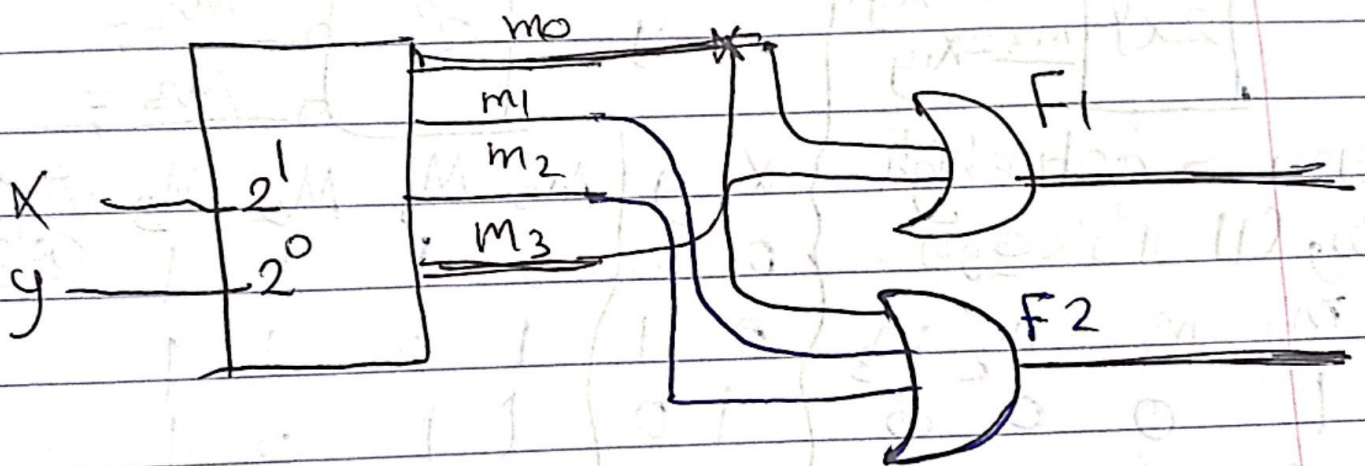
$$F_2(x, y) = \Sigma(0, 1, 2) = m_0 + m_1 + m_2$$




Inputs 11 MS bits by an arrow ←

نوعی دیگر

Active high decoder

2x4 active high decoder

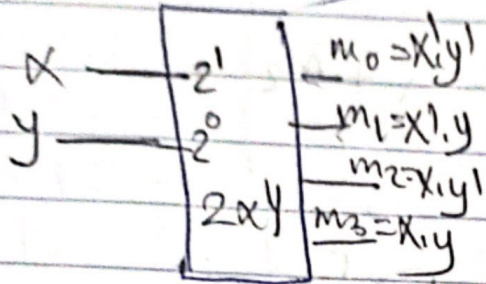

minterm = active high


نوعی دیگر (1) و (0) های

X	Y	m ₀	m ₁	m ₂	m ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

الگوی 0 و 1

Active low decoder

2x4 active low decoder

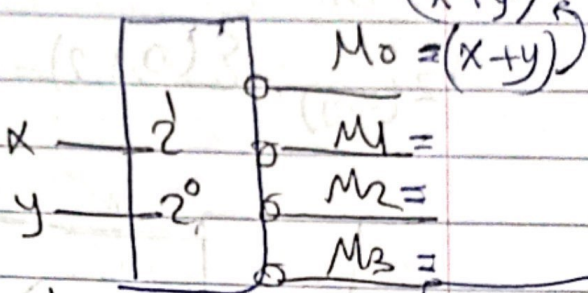

X	Y	M ₀	M ₁	M ₂	M ₃
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0


نوعی دیگر
نوعی دیگر

$$M_1 = X + Y' = (X'Y)'$$

$$M_2 = X' + Y = (XY)'$$


$$M_3 = X' + Y' = (XY)'$$

الگوی 0 و 1
(0) های

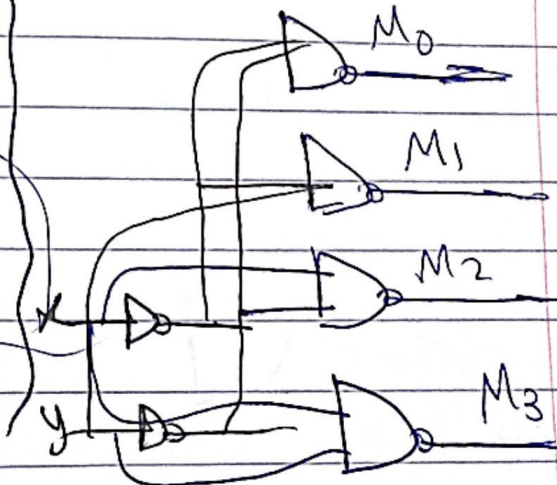

$$M_0 = (m_0)'$$

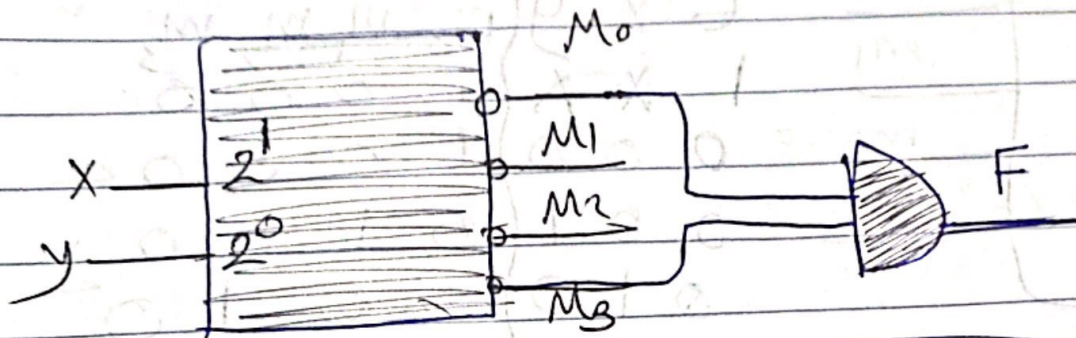
implement the following function using
 Decode $F(x, y) = \Pi(0, 3)$
 $= M_0 \cdot M_3$



خروج (1) مضروب
 خروج (0)


Ex: active high decoder 2 x 4 with
 input output control

high enable [E]

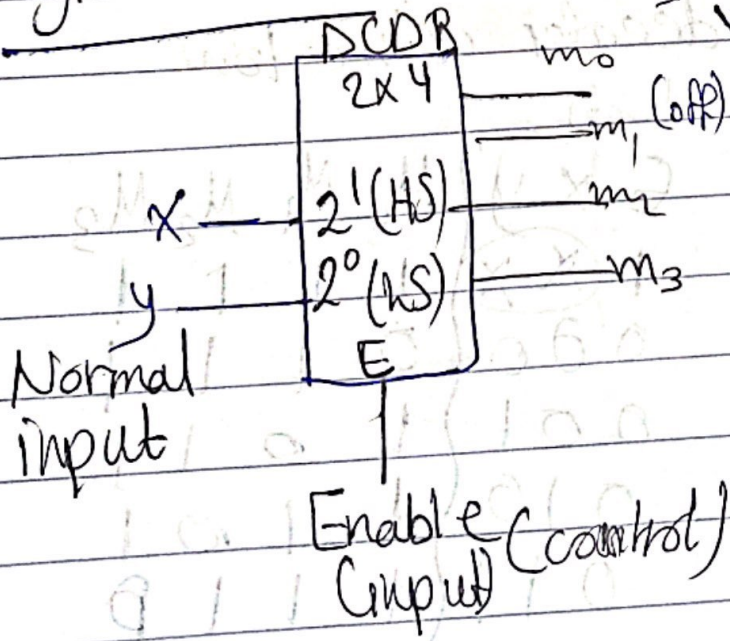


x	y	m_0	m_1	m_2	m_3
0	x	0	0	0	0
1	0	1	0	0	0
1	0	0	1	0	0
1	1	0	0	1	0
1	1	0	0	0	1

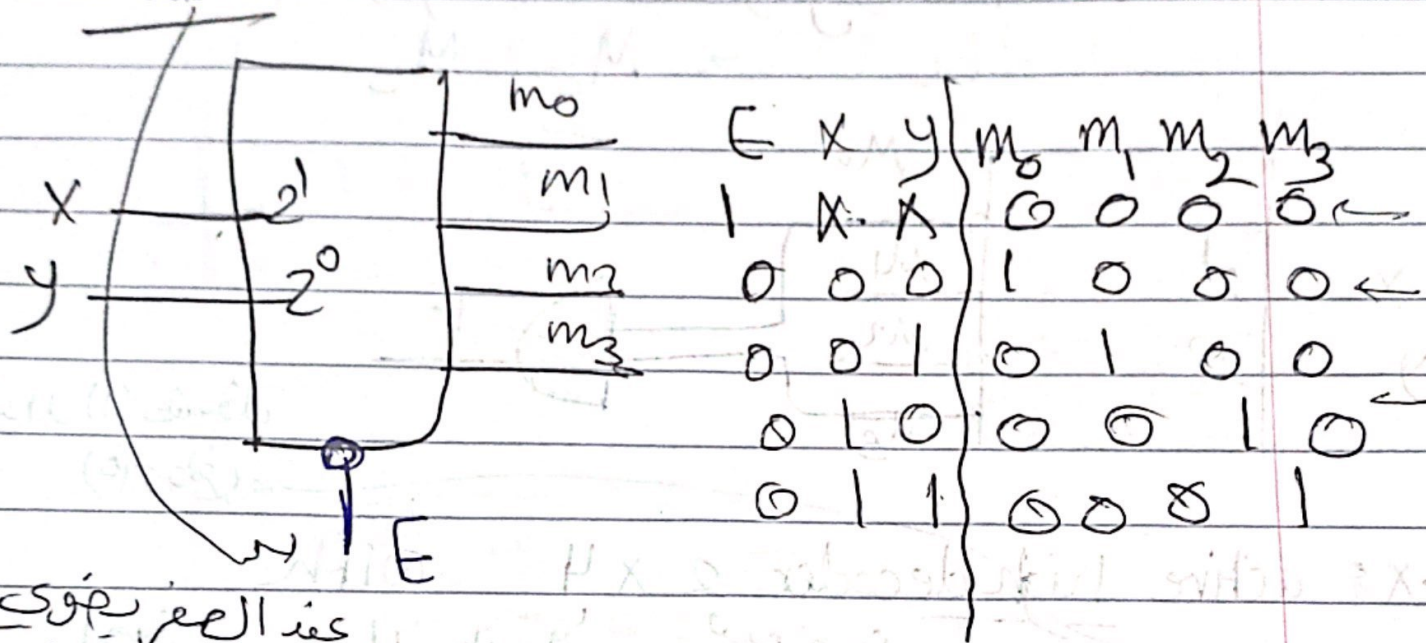
2x4 active high decoder with active low enable.



عند الصفر يفتوح
كيف القام يطفئ

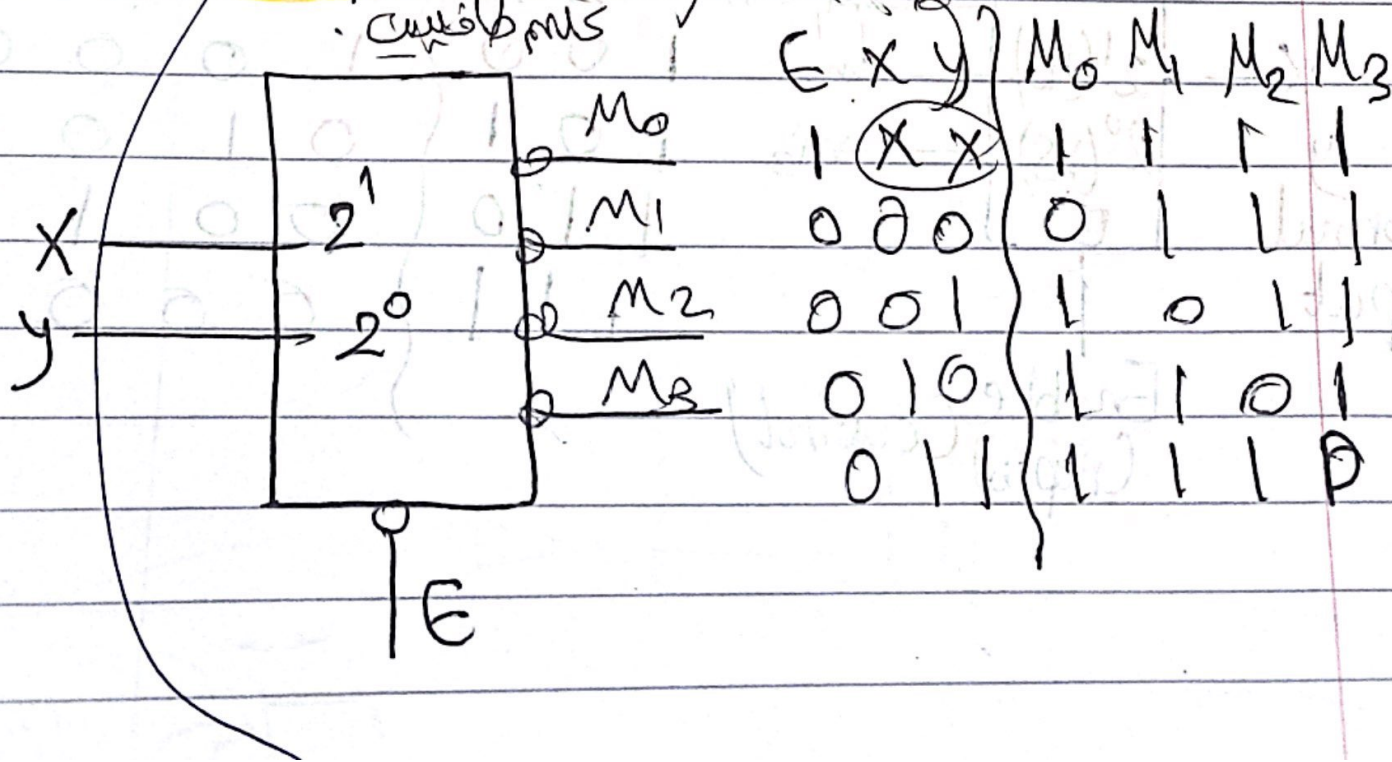2x4 active low decoder active low enable.



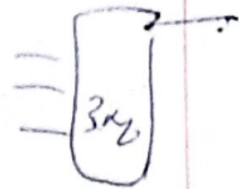


Implement Full adder using decoder
 (1) 3x8 (2) decoder 2x4.

x	y	z	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$m_1 + m_2 + m_4 + m_7$$

$$\text{sum}(x, y, z) = \sum(1, 2, 4, 7)$$
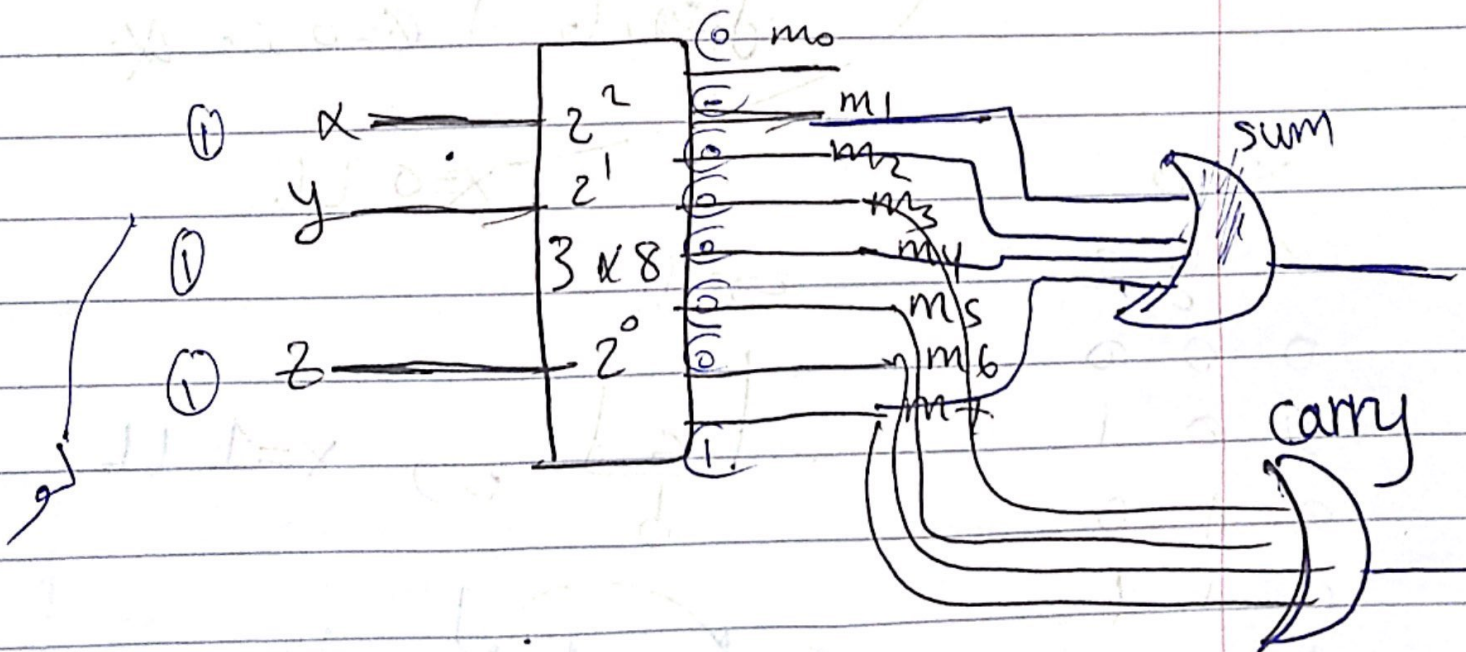
$$\text{carry}(x, y, z) = \sum(3, 5, 6, 7)$$



لما كان
في حال
بسيط

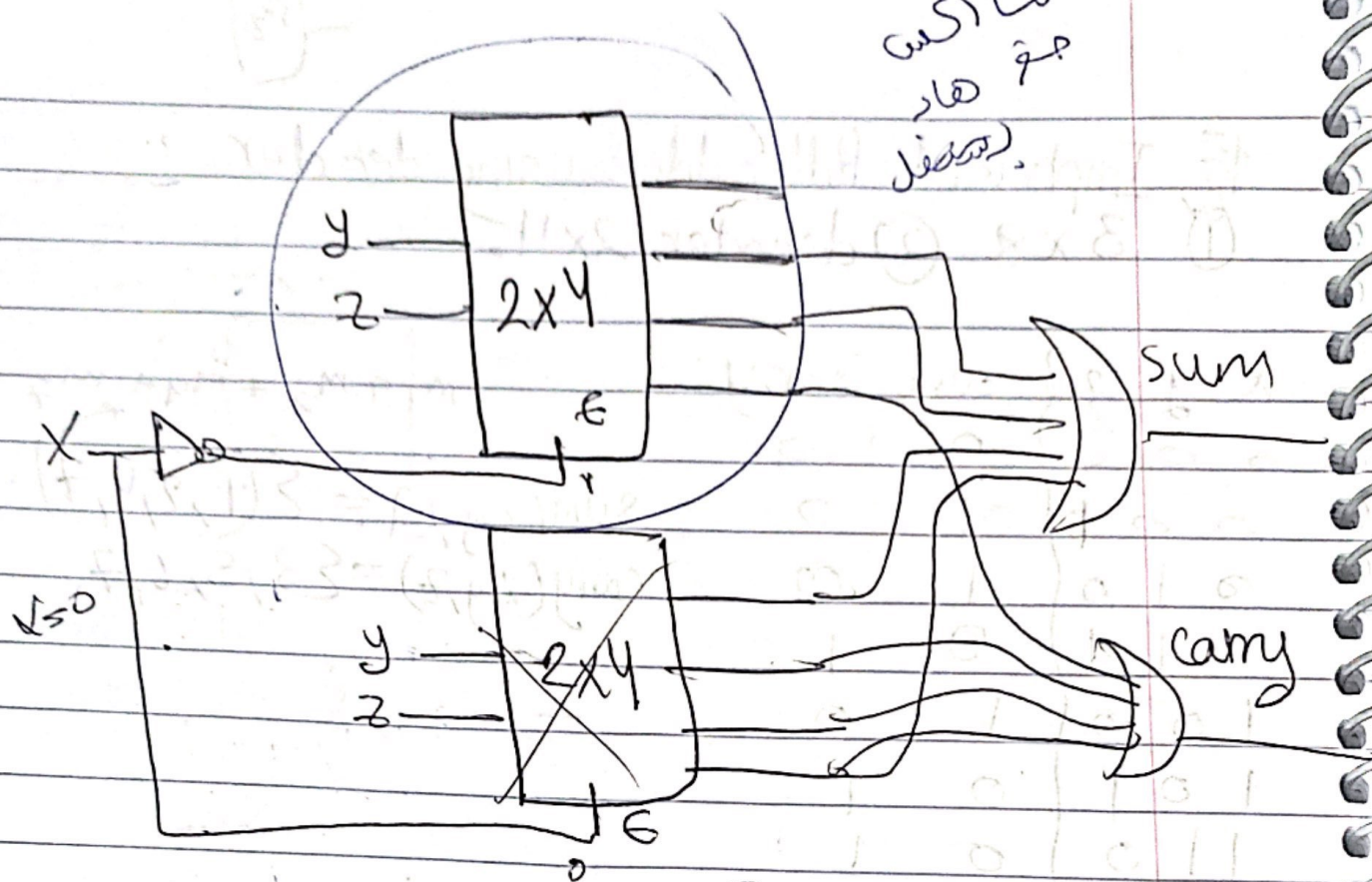

عند $E=0$ لا يعمل

$X=0$


$X=0$ لا

X	y	z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

القيمة




$X=1$ لا




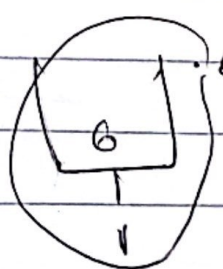


لما كان
بسيط


4 x 16 Decoder.

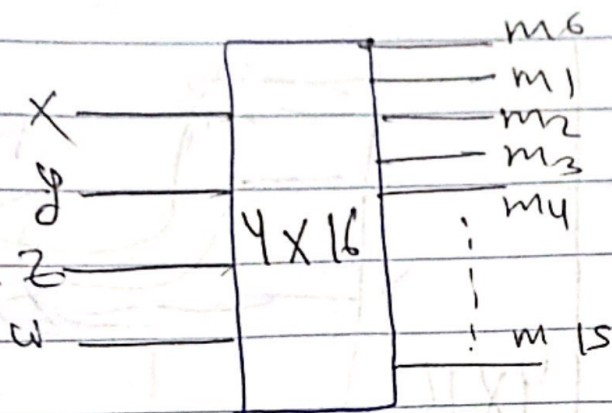

2x4 decoder

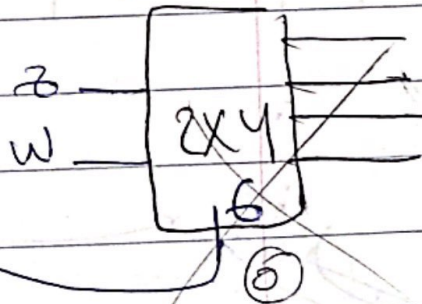
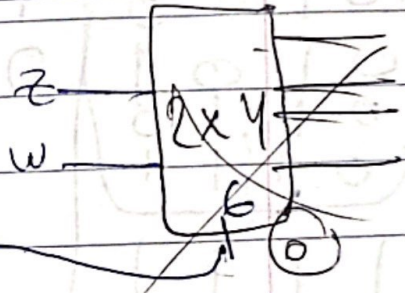
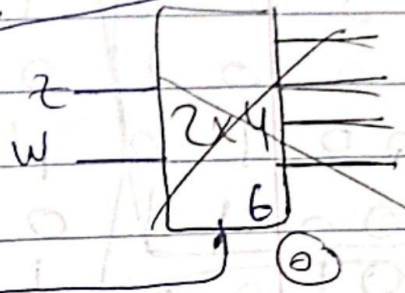
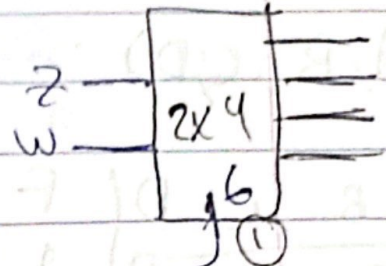


البيان
بشكل

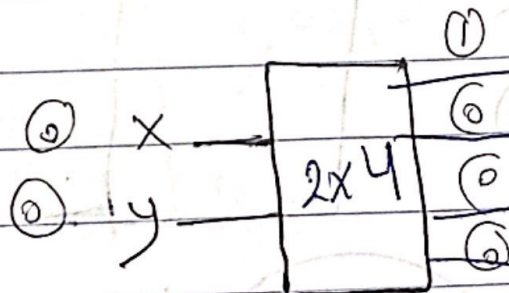


control decoder

البيان
بشكل

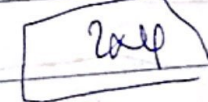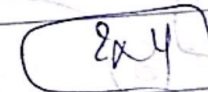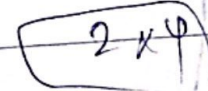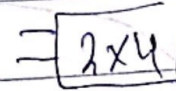


$$F(A, B, C, D) = \sum 0, 2, 4, 15$$

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

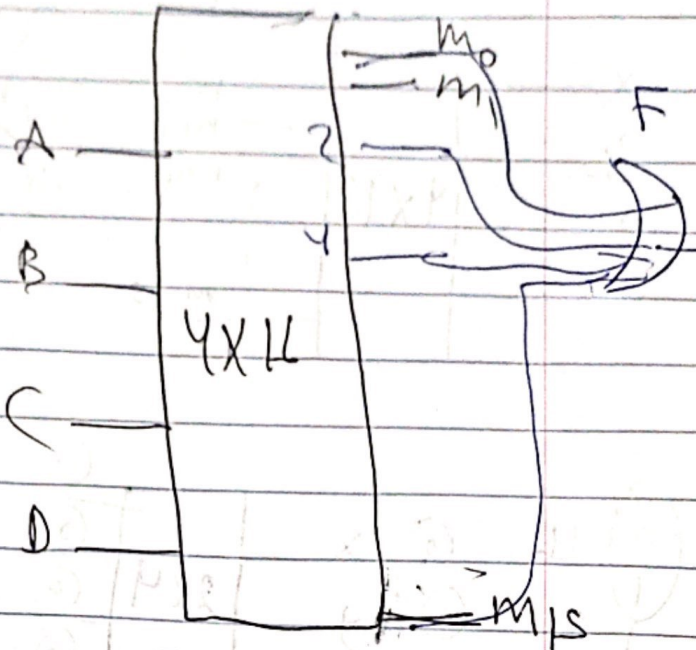

2x4

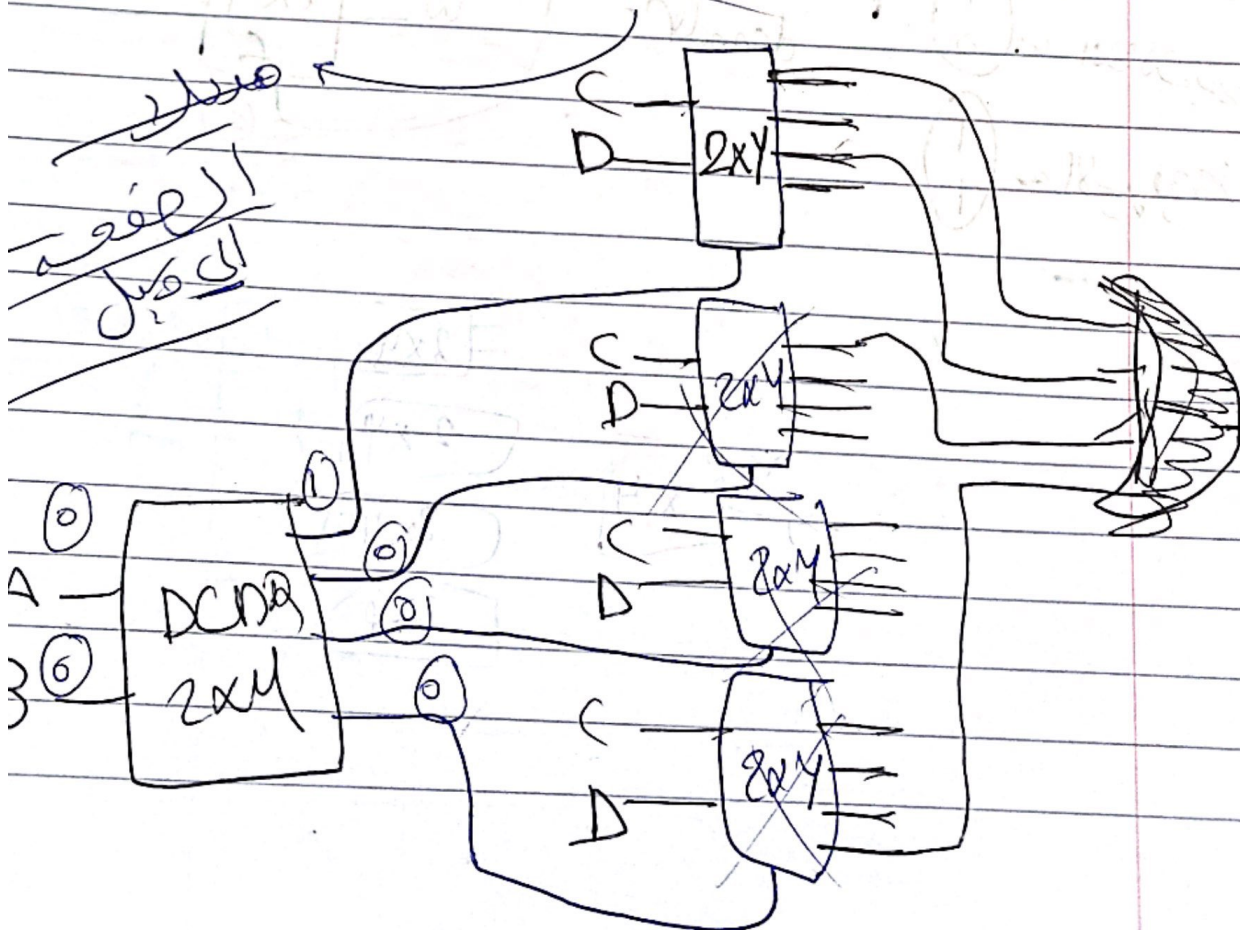


$$\begin{bmatrix} D_0 & D_1 & D_2 & D_3 \\ \hline 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \approx 4$$


$$\begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} \xrightarrow{\text{decoder}} \begin{bmatrix} A \\ B \end{bmatrix}$$

Encoder

Inverse operation Decoder

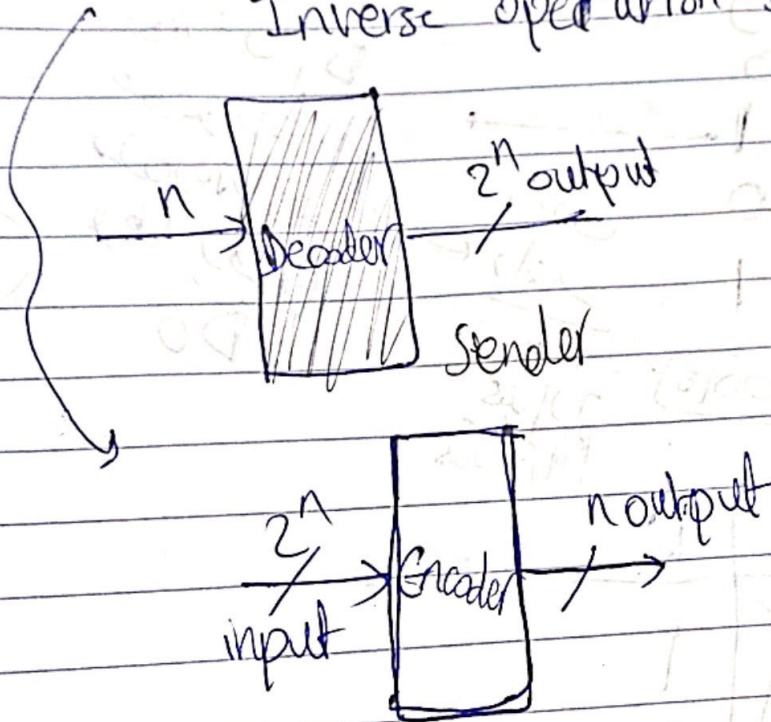

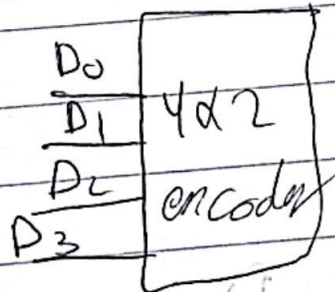input \rightarrow 4x2 encoder \rightarrow output



D_0	D_1	D_2	D_3	x	y
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$x = D_2 + D_3$$

$$y = D_1 + D_3$$

- اولی
- Priority encoder. (Input priority on other input).

مثال 4x2 priority encoder (D_3, D_2, D_1, D_0)


D_0	D_1	D_2	D_3	X	Y
0	0	0	0	0	0
X	1	0	0	0	1
X	X	1	0	1	0
X	X	X	1	1	1

D_1 has priority over D_0
 X means we ignore D_0
 برکتی و آخر
 کنترول کنترول کنترول

$D_3 D_2$	$D_1 D_0$	X	Y
00	00	0	0
01	01	0	1
11	11	1	0
10	10	1	1


$X = 0001$
 $Y = 1111$

$$X = D_2 + D_3$$

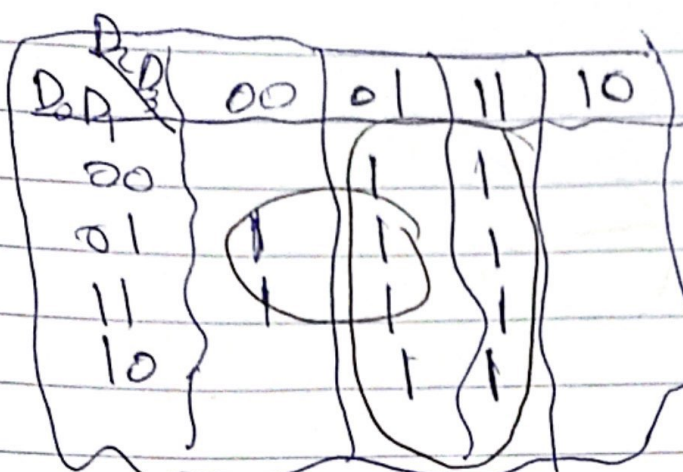

- 0001
- 0011
- 0101
- 0111
- 1001
- 1011
- 1101
- 1111

$$y = D_3 + D_1 D_2'$$

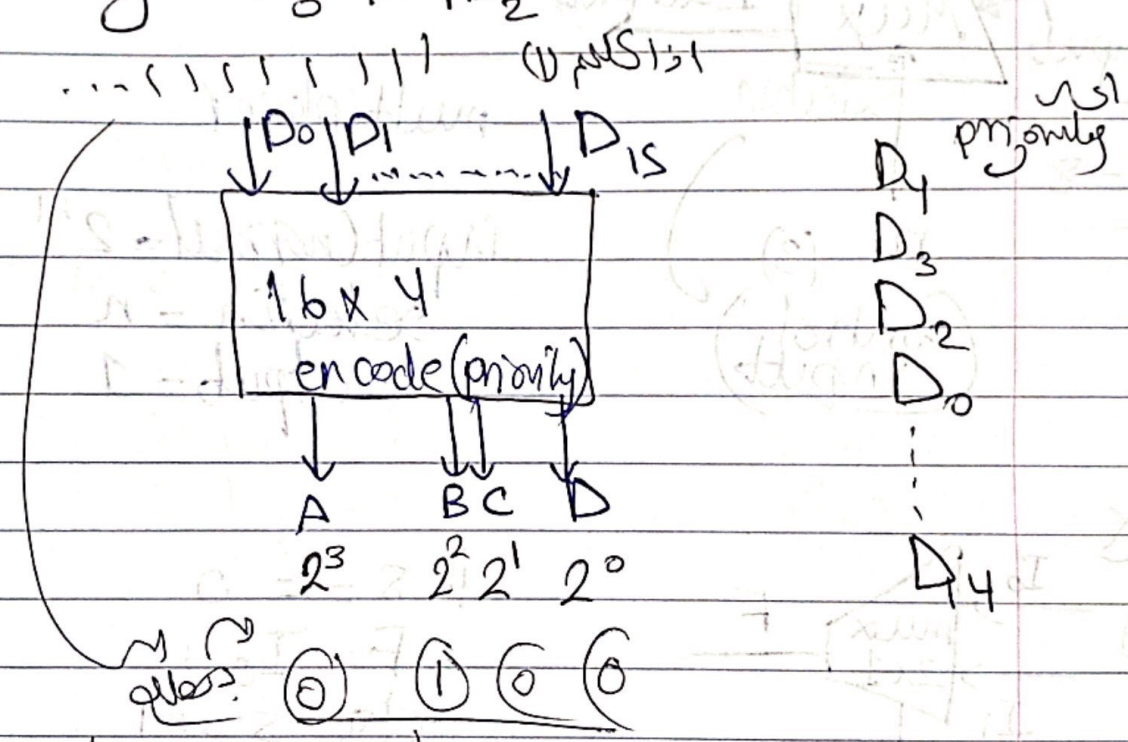

priority list
دولت اولویت

0 0 1 1 (0) $\leftarrow D_4$


1 1 1 1 1 1 1 1
D0 ————— D15

A B C D $\leftarrow 1 \leftarrow D_4$
0 1 0 0
0 0 1 1 $\leftarrow D_3$ (یعنی)

Multiplexer (Mux)

also
also (e.g., (kio))


Mux

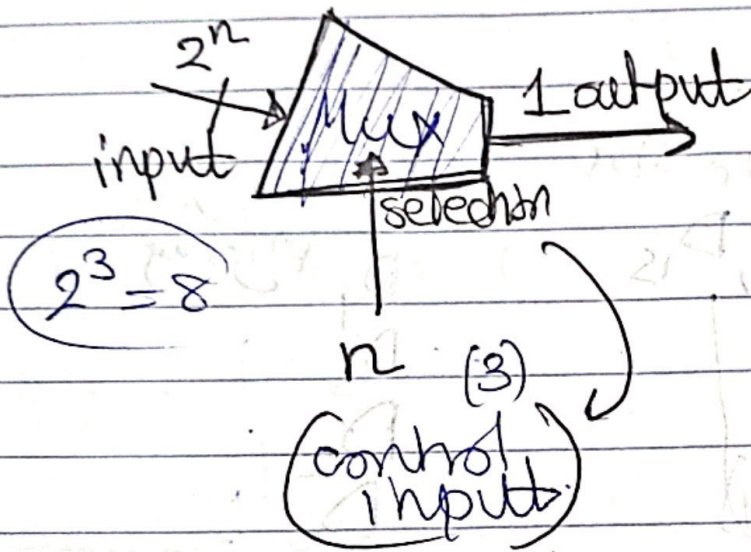

multiplexer

input (normal) = 2^n
selection = n
output = 1

Ex

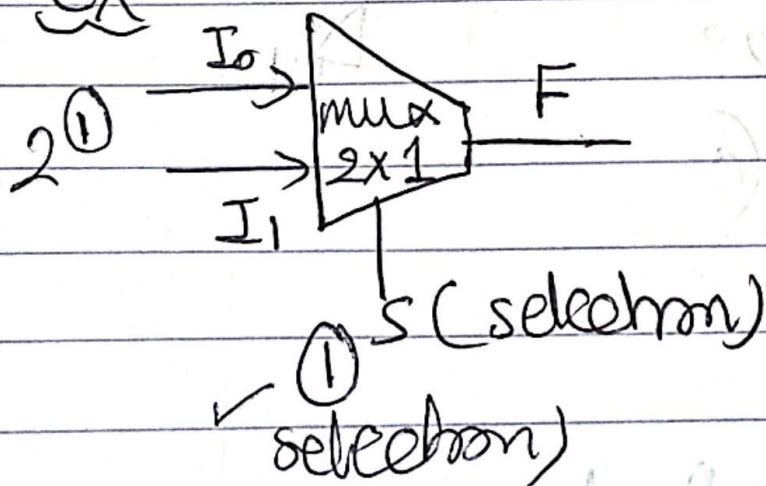


if $s \neq 0$

$F = I_0$


else $s = 1$

$F = I_1$

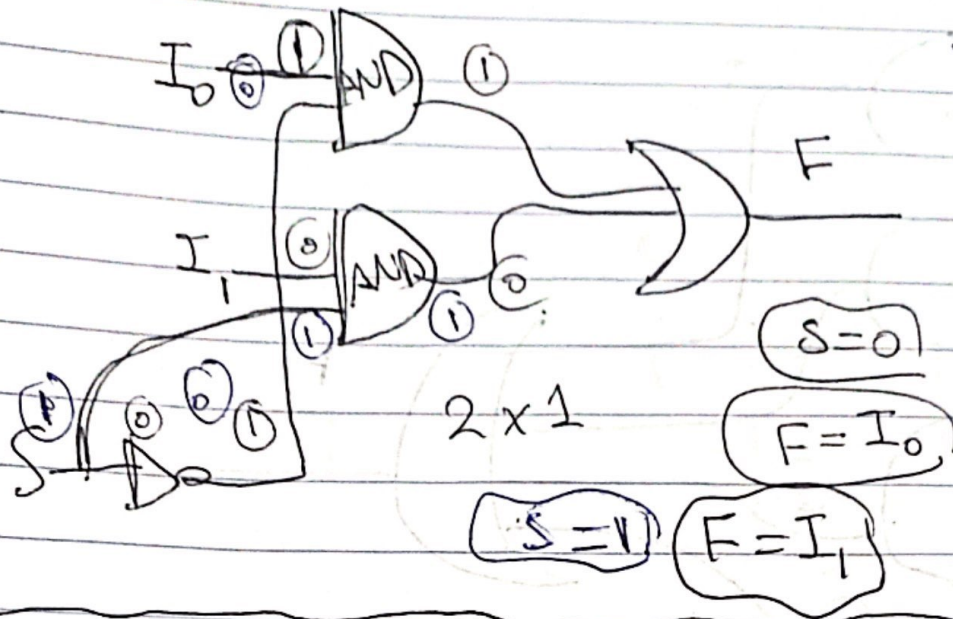



Mux 4x1

input output

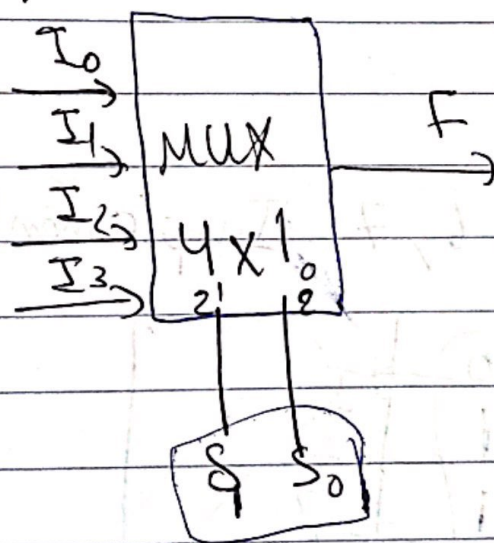


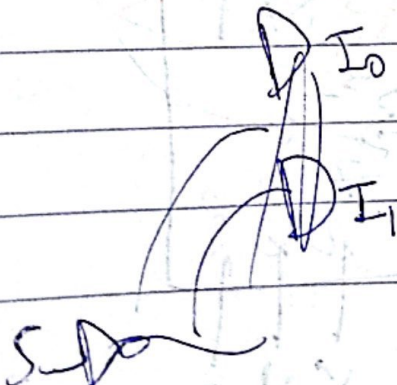if $S_1 S_0 = 00$
 $F = I_0$
 $S_1 S_0 = 01$
 $F = I_1$
 $S_1 S_0 = 10$
 $F = I_2$
 $S_1 S_0 = 11$
 $F = I_3$



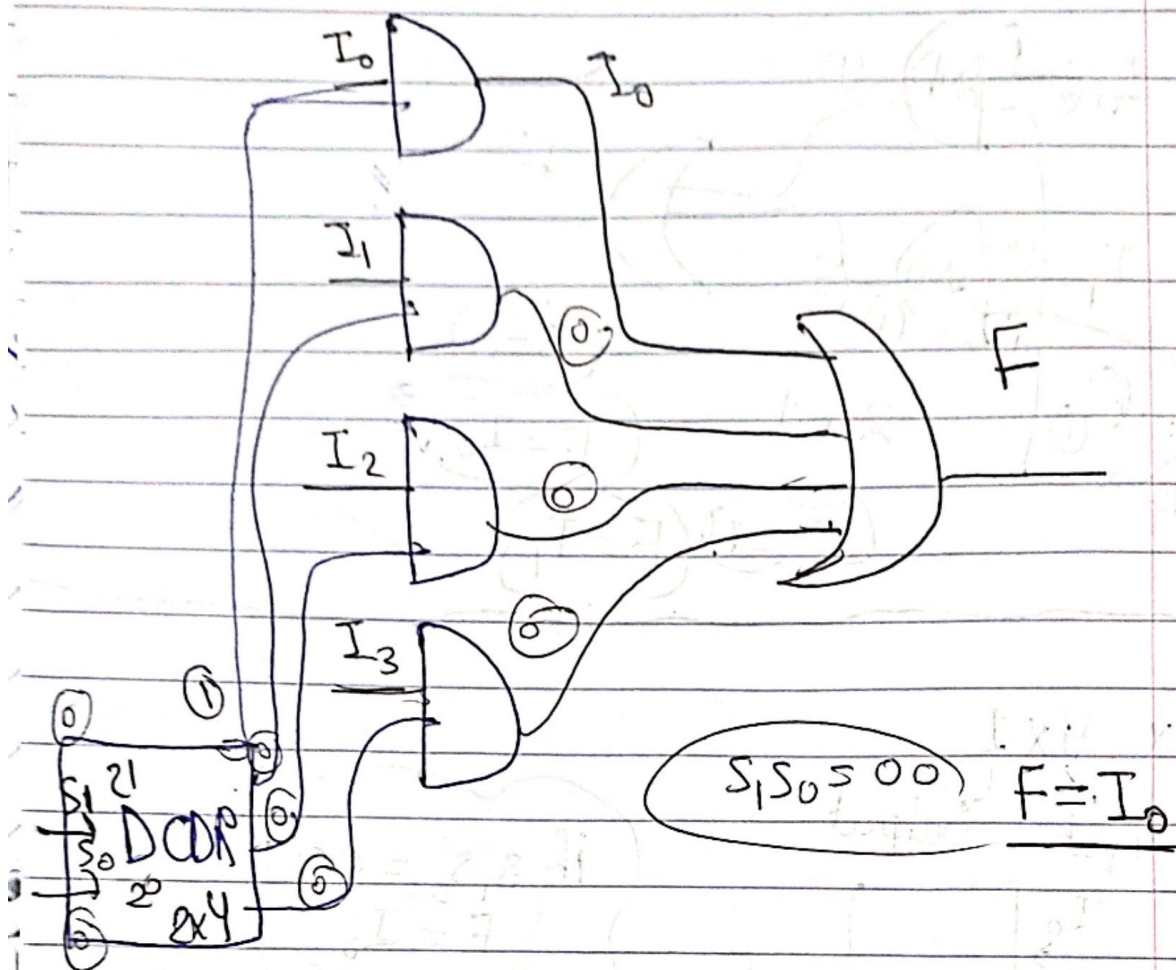

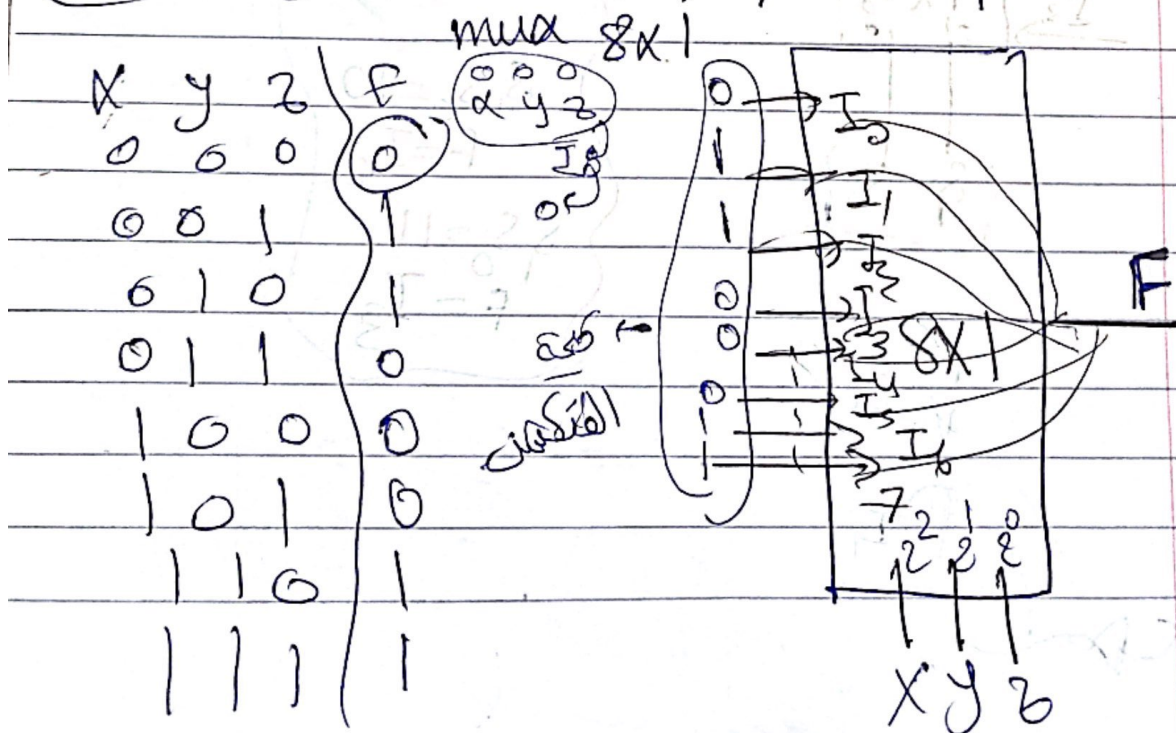
Q. $F(x, y, z) = \sum 1, 2, 6, 7$ Implementation



$$F(A, B, C) = \sum 0, 3, 6, 7$$

A	B	C	F		
0	0	0	1	1 →	I ₀
0	0	1	0	0 →	I ₁
0	1	0	0	0 →	I ₂
0	1	1	1	1 →	I ₃
1	0	0	0	0 →	I ₄
1	0	1	0	0 →	I ₅
1	1	0	1	1 →	I ₆
1	1	1	1	1 →	I ₇
					A B C

∴ A B C 0 0 0 ⇒ F ⇒ I₀ ⇒ 1

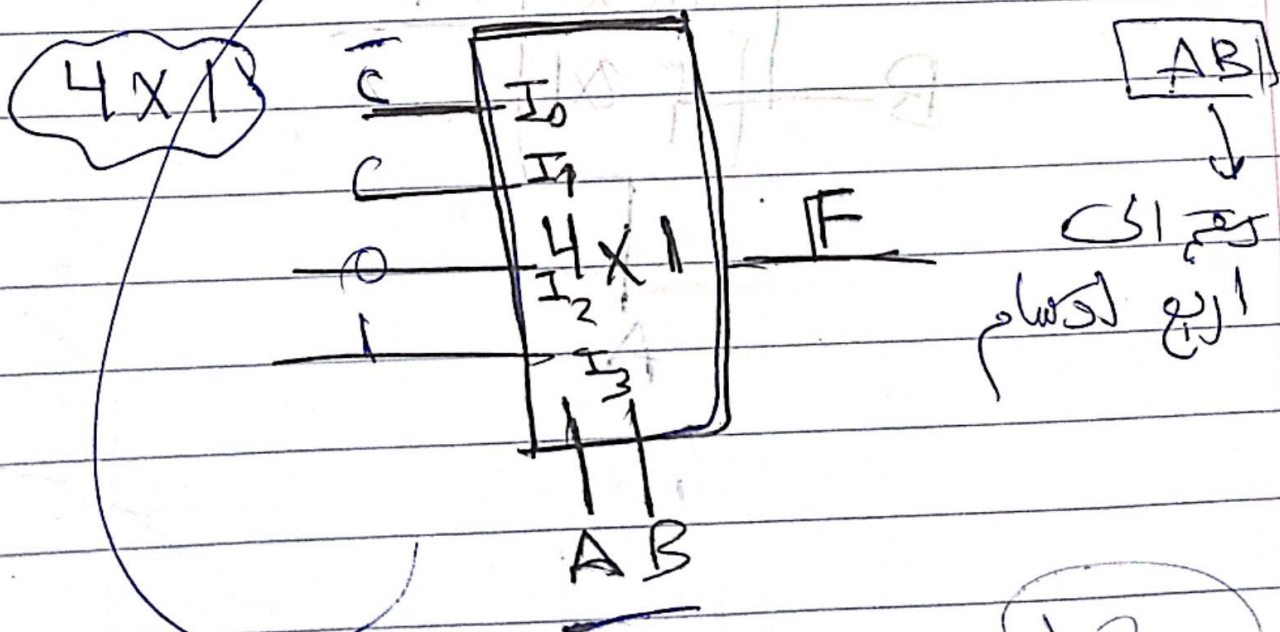

12

$$F_{(A,B,C)} = \sum 0, 3, 6, 7$$


(2x1)

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

B \ C	0	1
0	1	0
1	0	1

$$F = BC' + BC$$

$$(B \oplus C)'$$


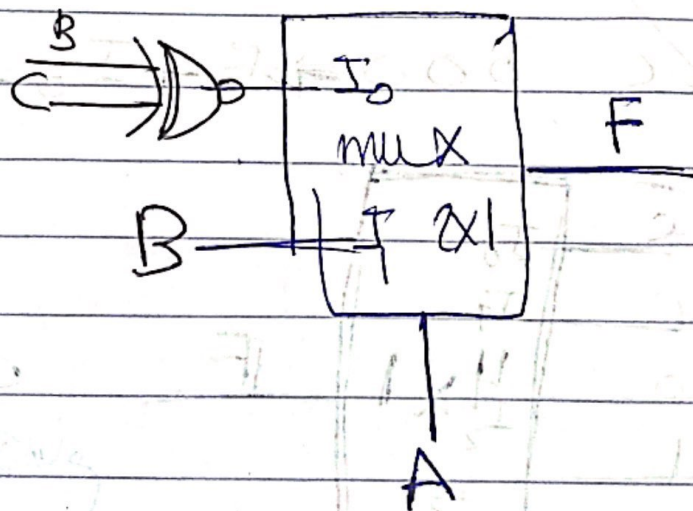


$$F(A, B, C, D) = \sum 0, 2, 4, 5, 6, 10, 14, 15$$



A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	1	1

~~4x1 Mux~~

16x1

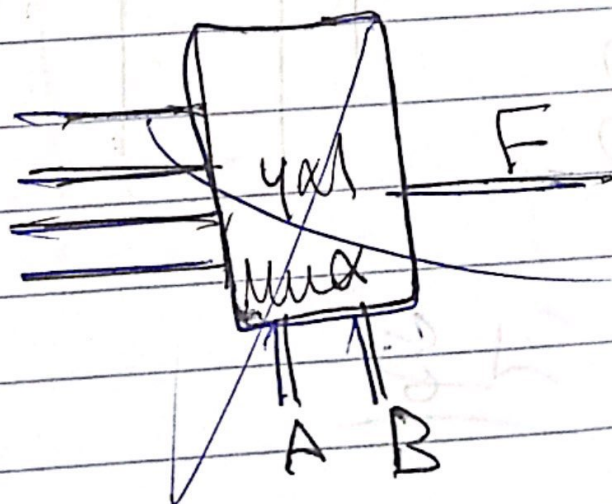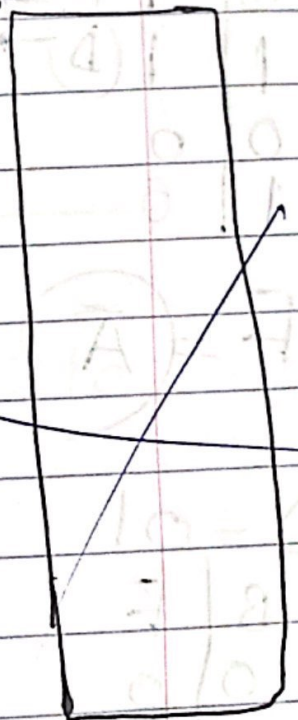


CD selection
(~ 5)/B, 1

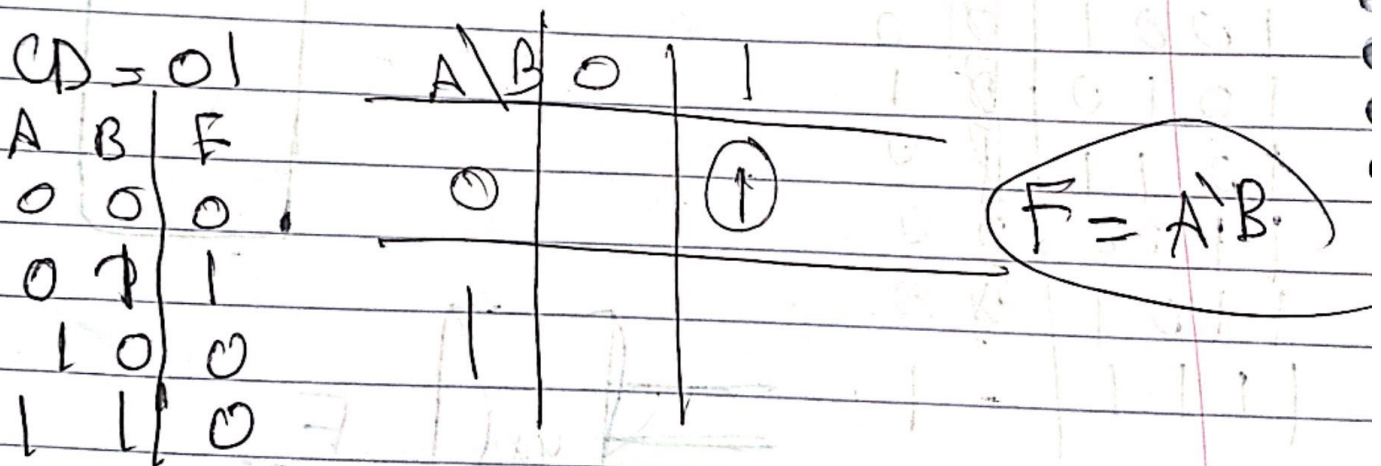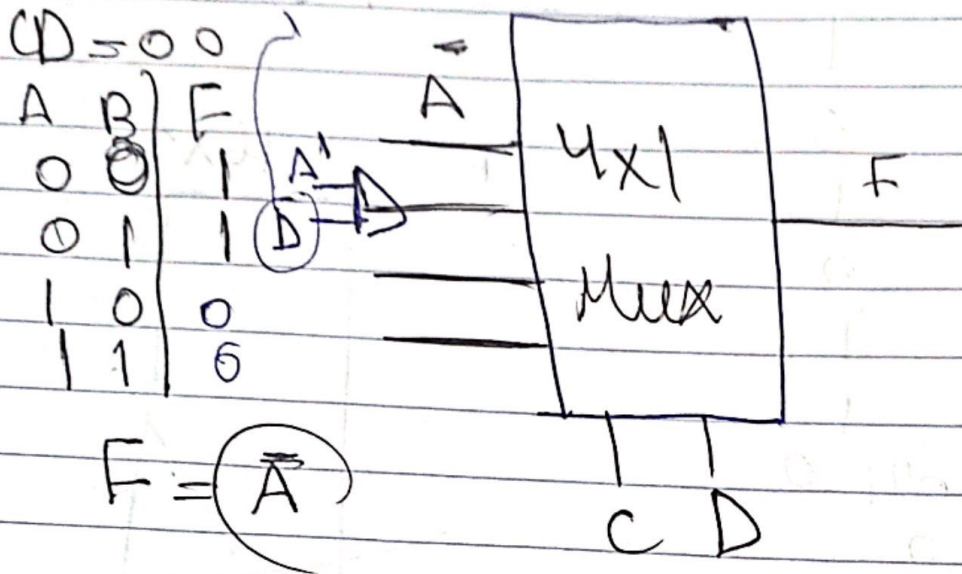


~ 5


Demultiplexer (De mux)

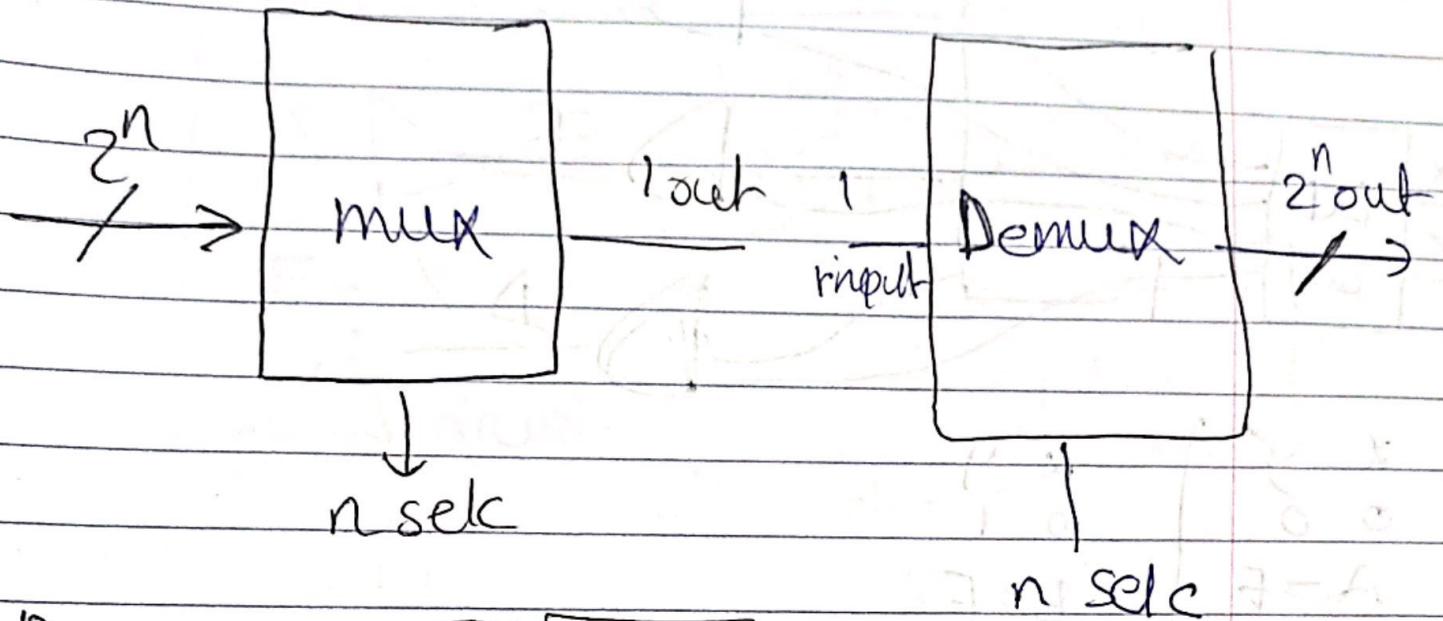

De mux ~~4x1~~ 1x4

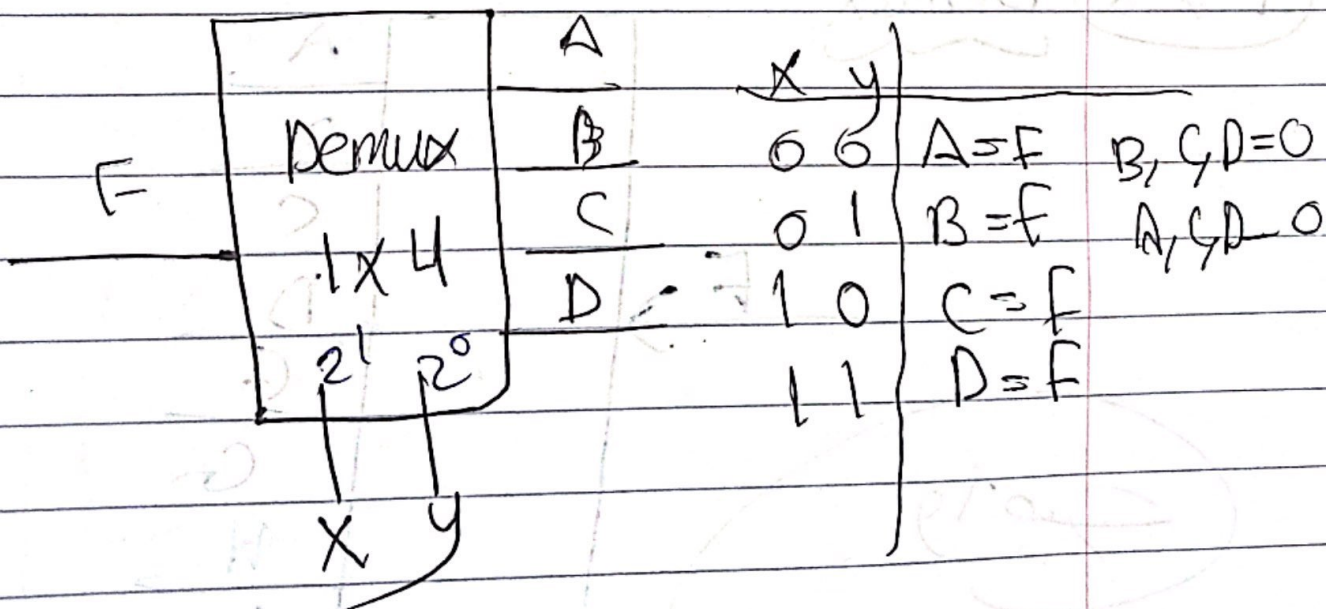

1x8

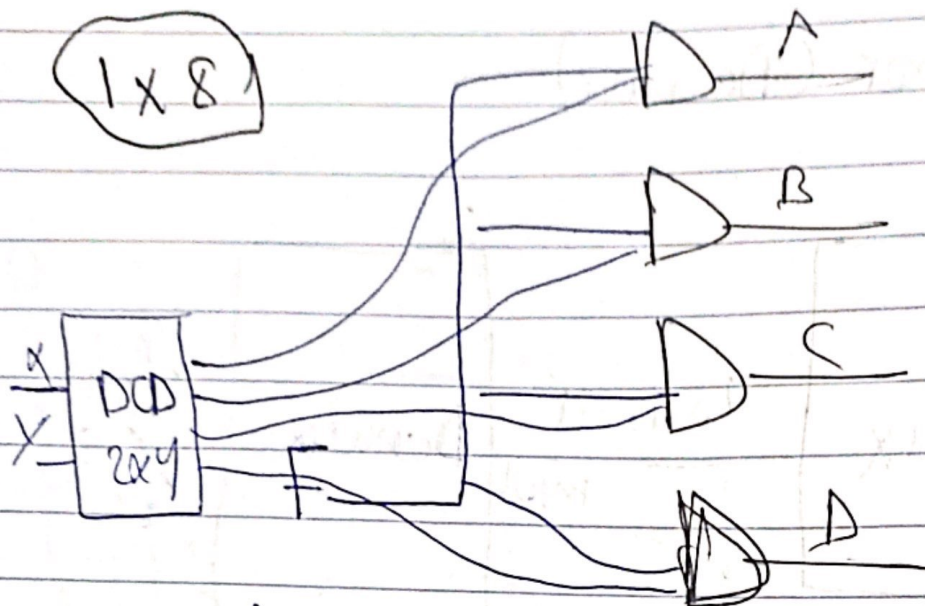

X	Y	X	Y
0	0	0	1
A = F		B = F	


mmms l'so,

1x8 Demux



Scanned with CamScanner

Three (Tri) state buffer

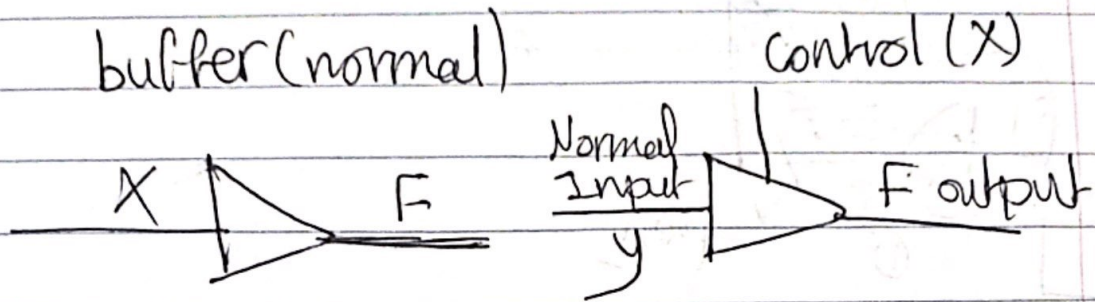

$$F = X$$

short circuit

$$\text{if } X = 1$$

$$F = y \text{ (normal buffer)}$$

else


$$X = 0$$

(open circuit)

high impedance

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

2x1 mux

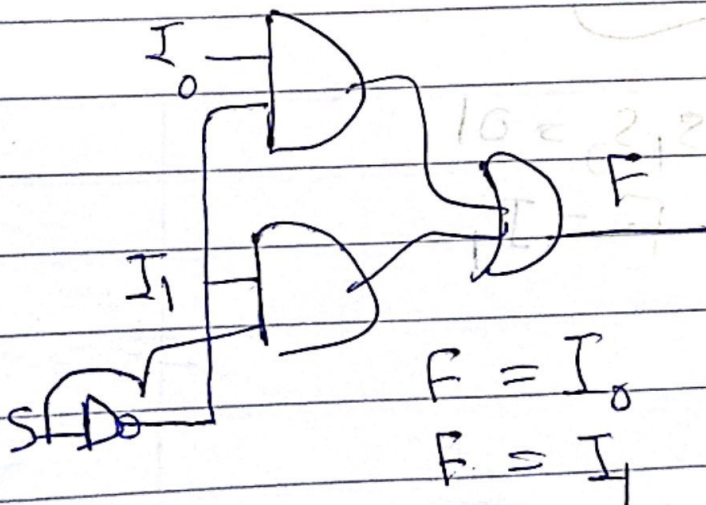


$$F = I_0 \quad S = 0$$

$$F = I_1 \quad S = 1$$



low sp.

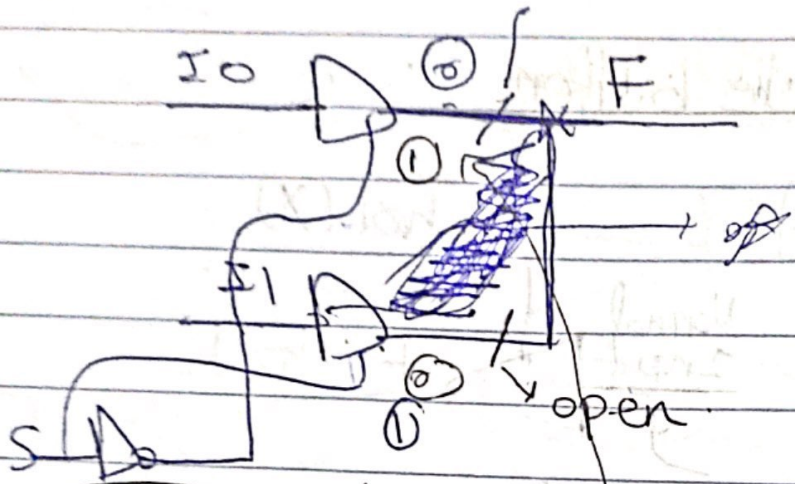


$S=0$

$F=I_0$

$S=1$

$F=I_1$

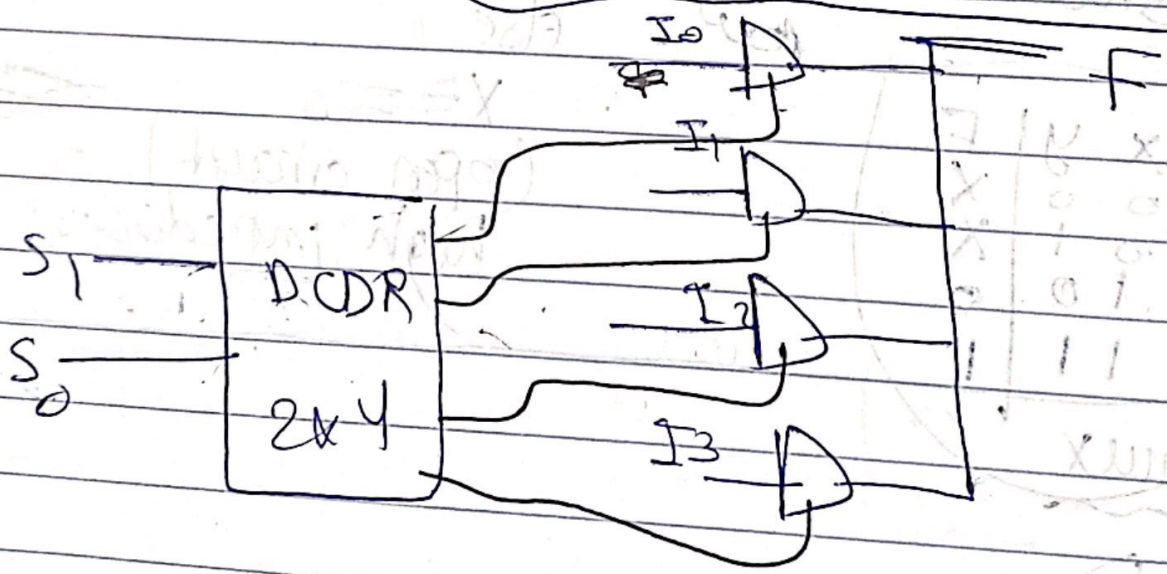

$S_1 S_0 = 00$

$F=I_0$

$S_1 S_0 = 01$

$F=I_1$