

L16 - part 2  
8/8/2021

## ENEE2360 Analog Electronics

### T9: Field Effect Transistor- FET

Instructor : Nasser Ismail

2

## FET Vs conventional Transistors (BJT)

### Advantages


- 1- High input impedance ; ~100 M !
- 2- Fewer steps in manufacturing process.
- 3- More devices can be packaged into smaller area for integrated circuit **IC**



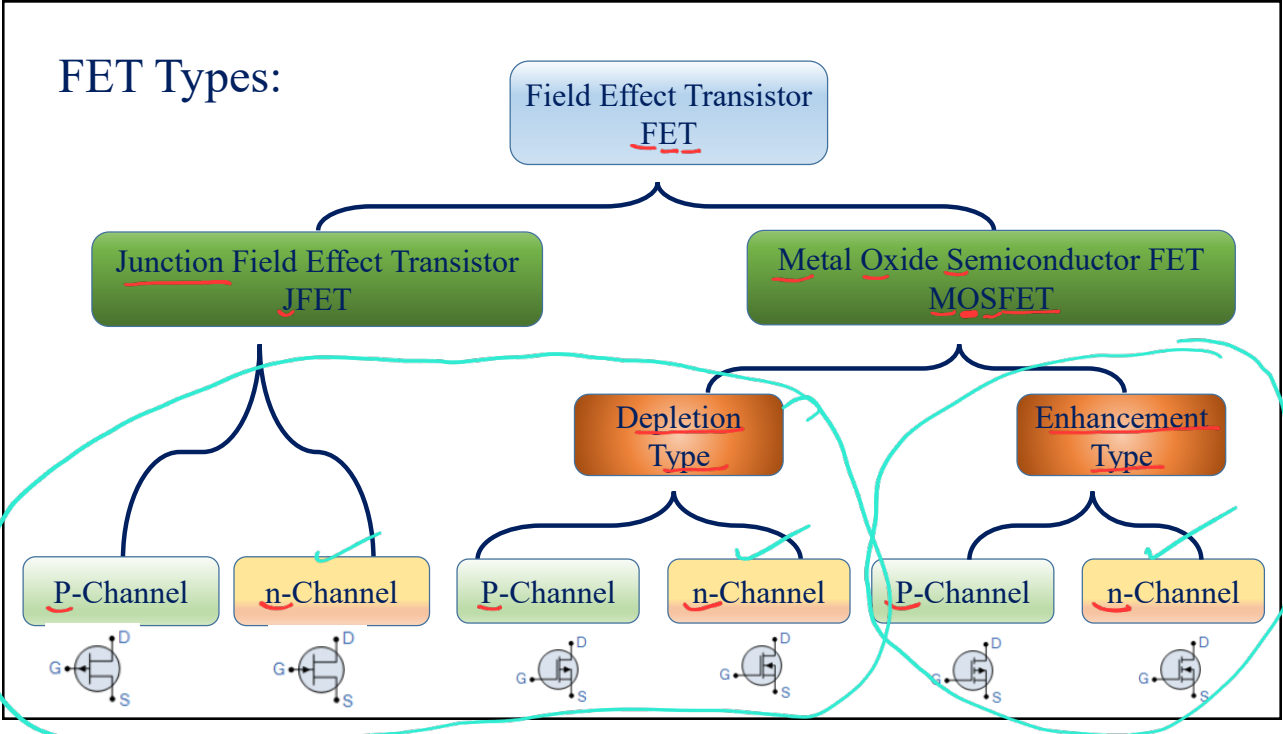
### Disadvantages

- 1- Low values of voltage gain.
- 2- Poor high frequency performance.
- 3- Sensitivity to Electro-static Discharge (ESD) and special handling is required.






 


## Junction Field Effect Transistor JFET
 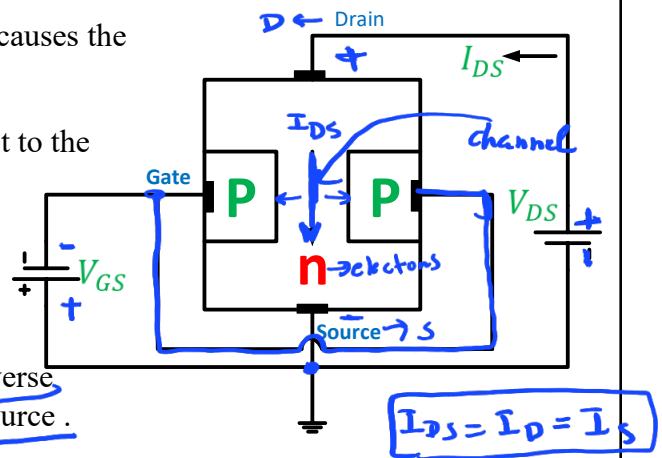
### JFET construction:


n-channel JFET

- ✓ Reverse biasing the gate to source junctions causes the formation of the depletion region
- ✓ The drain has the proper polarity with respect to the source to establish the drain current  $I_{DS}$
- ✓ The value of  $I_{DS}$  depends on the width of the channel.
- \* ✓ The width of the channel is controlled by reverse biasing the pn-junctions between gate and source.
- ✓ If the channel width increases  $I_{DS}$  increases.









Operation of a JFET

 

  [http://www.learnabout-electronics.org/fet\\_03.php](http://www.learnabout-electronics.org/fet_03.php)


  
## N-Channel JFET Operation → characteristic





- When  $V_{DD}$  is applied, electrons are drawn to the drain terminal establishing drain current  $I_D$
- Drain and source currents are equivalent ( $I_D = I_S$ )
- $I_D$  is limited by the resistance of the n-channel between the drain and source
- $I_G = 0$  ( due to the fact that the pn junction is reverse biased)
- As  $V_{DS}$  is increased ,  $I_D$  will also increase according to ohms law

ENEE236

7

  
## N-Channel JFET Operation

- As  $V_{DS}$  is increased towards a value  $V_P$  (pinch off voltage), the depletion region is widened and channel width is reduced increasing resistance to  $I_D$  and the two depletion regions will appear as touching each other
- These two effects result in  $I_D$  being kept almost constant




8


### N-Channel JFET Operation

 

 (a) Bias is zero and depletion layer is thin; low-resistance channel exists between the drain and the source



 (b) Moderate gate-to-channel reverse bias results in narrower channel




(c) Bias greater than pinch-off voltage; no conductive path from drain to source

The nonconductive depletion region becomes thicker with increased reverse bias.  
(Note: The two gate regions of each FET are connected to each other.)


JFET Circuit Symbol:

P-Channel

n-Channel


 


 $0 \leq V_{GS} \leq V_P$   
positive value



$V_P \leq V_{GS} \leq 0$   
negative

JFET output characteristic:

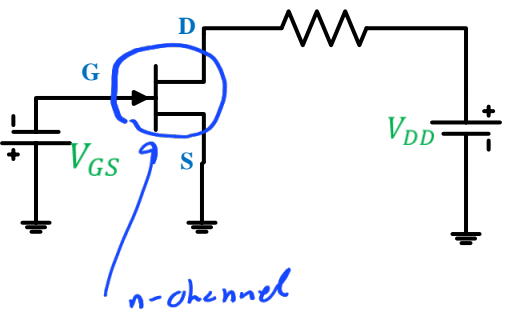 


### Pinch of voltage $V_P$ :

For  $V_{GS} = 0$ , the value of  $V_{DS}$  at which  $I_{DS}$  becomes essentially constant  
Is the absolute of the pinch of voltage  $V_{DS} = |V_P|$

Some literature refer to  $V_P$  as  $V_{GS(off)}$
 
$$V_P = \begin{cases} \text{negative value for } n\_channel \\ \text{positive value for } p\_channel \end{cases}$$



JFET Transfer characteristic curve:

$I_D = I_{DS}(t) = I_{DSS} \left( 1 - \frac{V_{GS}(t)}{V_P} \right)^2$


data sheet

In pinch off region:

$V_P < V_{GS} \leq 0$

$|V_{DS}| > |V_P| - |V_{GS}|$

for both  
n & p  
channel

 



P-channel JFET


$$I_{DS}(t) = I_{DSS} \left(1 - \frac{V_{GS}(t)}{V_P}\right)^2$$

In pinch off region:

$$|V_{DS}| > |V_P| - |V_{GS}|$$

$$V_P > V_{GS} \geq 0$$

موجب

 

## Summary: Pinch off voltage: $\equiv$ active region in BJT

✓ The voltage that causes the depletion region to touch and close the channel is called pinch off voltage

✓ For the **n-channel** JFET to be in the pinch off region:

سالبة  $\rightarrow$   $V_P < V_{GS} \leq 0$

$|V_{DS}| > |V_P| - |V_{GS}|$

✓ For the **p-channel** JFET to be in the pinch off region:

$|V_{DS}| > |V_P| - |V_{GS}|$

✗✗

موجبة  $\rightarrow$   $V_P > V_{GS} \geq 0$

/


End of L16

L17  
10-8-2021

Common JFET Biasing Circuits

- Fixed-Bias
- Self-Bias
- Voltage-Divider Bias

DC  
pinch-off mode  
↓  
active mode

 

## Basic Current Relationships


For all FETs:

$$I_G \cong 0 \text{ A}$$

$$I_D = I_S = I_{DS}$$

For JFETS
 
$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$



1)

## Fixed-Bias Configuration

KVL 2


$$V_{DS} = V_{DD} - I_D R_D$$

$$V_S = 0 \text{ V}$$

$$\therefore V_D = V_{DS}$$

$$\therefore V_{GS} = -V_{GG}$$

KVL 1

 

KVL 2

Find  $V_{GS}$  &  $I_D$  ?

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_G = 0 \rightarrow \text{KVL1}$$

$$1.5 + V_{GS} = 0 \Rightarrow V_{GS} = -1.5 \text{ V}$$


$$I_D = 10 \text{ mA} \left( 1 - \frac{-1.5}{-4} \right)^2$$

$$= 3.9 \text{ mA}$$

KVL2

$$16 = I_D R_D + V_{DS} \rightarrow V_{DS} = 16 - 3.9 \text{ mA} \times 2 \text{ k}\Omega$$

$$= 8.2 \text{ V}$$

 

## Example

$$V_{GS} = V_G - V_S = -1.5 - 0 = -1.5 \text{ V}$$

Assuming JFET is in pinch off region

$$1) I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$


$$= 10 \text{ mA} \left( 1 - \frac{-1.5}{-4} \right)^2$$

$$= 3.9 \text{ mA}$$

$$2) V_{DS} = V_{DD} - I_D R_D$$

$$= 16 - ((2 \text{ k}\Omega)(3.9 \text{ mA}))$$

$$= 8.2 \text{ V}$$

 


3) check for  $|V_{DS}| > |V_P| - |V_{GS}|$  ?

to make  
sure JFET  
is in pinch-off  
region


$$|8.2| > |-4| - |-1.5|$$

assumption is true

 
 
### Graphical method:

- $I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$  X
- $V_{GS} = -1.5 \text{ V}$  Fixed



$$V_S = I_D R_S$$

$$V_D = V_{DD} - I_D R_D$$


OR

$$V_{DS} = V_D - V_S$$

$$V_D = V_{DS} + V_S$$

never

$$V_D = I_D R_D \neq V_S$$

 

$$V_S = I_D \cdot R_S$$

## Self-Bias Configuration

KVL 1

$$V_{GS} = V_G - V_S = 0 - V_S = -V_S$$

$$V_S = I_D R_S$$

$$f(I_D) \leftarrow V_{GS} = -I_D R_S \quad (1)$$


KVL 2

$$V_D = V_{DD} - I_D R_D$$

$$V_{DS} = V_D - V_S$$

$$= V_{DD} - I_D R_D - I_D R_S$$

$$= V_{DD} - I_D (R_S + R_D)$$

 

$R_G$  is important to isolate the ~~low~~ ac signal from ground in amplifier circuits

$$V_G = 0$$

$$V_S = I_D \cdot R_S$$



### Solution


$$V_G = 0 \quad (I_G = 0)$$

$$V_s = I_D R_s$$

assume pinch-off region

$$I_D = \check{I}_{DSS} \left(1 - \frac{V_{GS}}{\check{V}_P}\right)^2$$

$$I_D = 10 \text{ mA} \left( 1 - \frac{-I_D R_s}{-4} \right)^2 \leftarrow \text{quadratic equation}$$

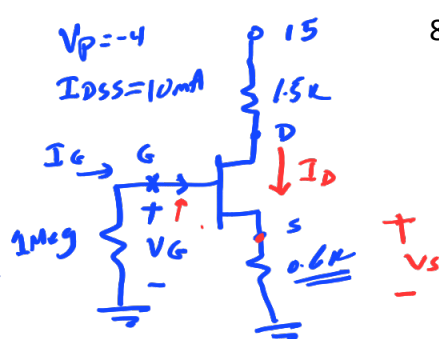
$$V_P = -4 \text{ V}$$

$$I_{DSS} = 10 \text{ mA}$$


$$V_{GS} = V_G - V_S = 0 - V_S = -V_S$$

$$V_s = I_D R_s = 600 I_D$$

$$V_{GS} = -600I_D$$

$$1) \quad I_D = 10 \text{ mA} \left( 1 - \frac{-600 I_D}{-4} \right)^2 \quad \leftarrow x = I_D$$
 
$$\underbrace{ax^2 + bx + c = 0}_{\text{Quadratic Equation}}$$




22

X  $I_{D1} = 14.7 \text{ mA}$  X  $> I_{DSS}$

$$I_{D2} = 3 \text{ mA}$$
 
$$\begin{aligned} V_{GS} &= -I_D \times R_S \\ &= -3 \text{ mA} \times 0.6 \text{ k}\Omega \\ V_{GS} &= -1.8 \text{ V} \end{aligned}$$



## Example-continued

solving for  $I_D$  :

$I_{D1} = 14.77 \text{ mA} > I_{DSS}$  and this solution is not possible

$I_{D2} = 3 \text{ mA} \leftarrow$  this is the correct solution

$$2) \therefore V_{GS} = -600I_D = -600 \times 3\text{mA} = -1.8\text{V}$$

$$V_D = V_{DD} - I_D R_D$$


$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$= 15 - 3\text{mA} (1\text{k} + 0.6\text{k}) = 10.2 \text{ V}$$

3) check for  $|V_{DS}| > |V_P| - |V_{GS}|$  ?

$$|10.2| > |-4| - |-1.8|$$

assumption is true

 

KVL


Graphical method

$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$  ✓ → curve

$V_{GS} = -(0.6K) I_{DS}$

when  $V_{GS}=0 \rightarrow I_{DS}= 0\text{mA}$

 when  $V_{GS}= -3\text{v} \rightarrow I_{DS}= 5\text{mA}$





L18  
11-8-2021

sec 1

Voltage-Divider Bias

 $I_G = 0\text{ A}$   
 $I_D$  responds to changes in  $V_{GS}$ .



 

## Voltage-Divider Bias Calculations

$$I_G = 0 \text{ A}$$

$V_G$  is equal to the voltage across divider resistor  $R_2$ :


$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2} = V_{th}$$

$$V_S = I_D R_S$$

Using Kirchhoff's Law:

$$V_{GS} = V_G - I_D R_S$$
 
$$V_{GS} = \frac{R_2 V_{DD}}{R_1 + R_2} - I_D R_S$$



The Q-point is established by plotting a line that intersects the transfer curve.

(1) ...

$$V_{GS} = V_G - V_S = V_G - I_D R_S = \frac{R_2}{R_1 + R_2} V_{DD} - I_D R_S$$

(2) ...

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

sub (1) in (2)

✓  $I_D = I_{DSS} \left( 1 - \frac{V_G - I_D R_S}{V_P} \right)^2$  ← معادله كيرشوف

$I_{D1} \rightarrow ?$   
 $I_{D2} \rightarrow ?$  → ? only one correct solution

✓  $V_{GS}$

### Example

$V_S$  must be more positive than  $V_G$

to keep the gate – source junction reverse biased

$$V_S = I_D R_S$$


$$V_{GS} = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = \frac{R_2 V_{DD}}{R_1 + R_2} - I_D R_S$$

$$V_D = V_{DD} - I_D R_D = 7 \text{ V}$$
 
$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{12 - 7}{3300} = 1.52 \text{ mA}$$



$$V_D = V_{DD} - I_D R_D$$

28

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

→ if  $V_{DS}$  was known instead of  $V_D$ ?

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S \rightarrow I_D = \frac{V_{DD} - V_{DS}}{R_D + R_S}$$

→ if  $V_S$  was known

$$V_S = I_D R_S \rightarrow I_D = \frac{V_S}{R_S}$$

## Example


$$V_s = I_D R_s = (1.52 \text{ mA}) (2.2 \text{ k}\Omega) = 3.34 \text{ V}$$

$$V_p \neq V_{gs} \leq 0 \Rightarrow$$

$$V_G = \frac{1 \text{ M}}{1 \text{ M} + 6 \text{ M}} 15 = 1.54 \text{ V}$$

$$V_{gs} = 1.54 - 3.34 = -1.8 \text{ V} < 0 \Rightarrow \text{OK}$$
 
$$\text{also } I_D = \frac{V_s}{R_s} = \frac{3.34}{2200} = 1.52 \text{ mA}$$



29

Example- $V_D$  unknown


For the same example, if  $V_D$  was not given, then we use the square law rule  $I_D = f(V_{GS})$  to find  $I_D$  and  $V_{GS}$  by substituting the expression

for  $V_{GS} = \frac{R_2 V_{DD}}{R_1 + R_2} - I_D R_S$  in it and solving for  $I_D$

$V_{GS} = 1.54 - I_D R_S$


$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$

 $= I_{DSS} \left( 1 - \frac{1.54 - I_D R_S}{V_P} \right)^2$



HW  
assume  
 $V_P = -4$   
 $I_{DSS} = 10 \text{ mA}$   
solve

Do not submit

 




## Voltage-Divider Q-Point

Plot the line that is defined  
by these two points:

$$V_{GS} = V_G, I_D = 0 \text{ A}$$

$$V_{GS} = 0 \text{ V}, I_D = V_G / R_S$$

 Plot the transfer curve by  
plotting  $I_{DSS}$ ,  $V_P$  and the  
calculated values of  $I_D$



The Q-point is located where the line intersects the transfer  
curve

Example p-channel


$$V_{GS} = \frac{R_2 \times (-20)}{R_1 + R_2} + I_D R_S$$

$$V_{GS} = -4 + I_D R_S$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= I_{DSS} \left( 1 - \frac{-4 + I_D R_S}{V_P} \right)^2$$

 $V_P = 5\text{ V}$  ← positive → P-channel JFET  
 $I_{DSS} = 18\text{ mA}$



$V_S = -I_D R_S$   
 $V_G = \frac{R_2 \times (-20)}{R_1 + R_2}$

معادلة تربيعية

$$I_D = 18 \text{ mA} \left( 1 - \frac{-4 + 1650 I_D}{5} \right)^2$$

- Solving the quadratic equation and finding its roots yields:

$$I_{D1} = 4.7 \text{ mA}$$

$$I_{D2} = 7.4 \text{ mA}$$

both values of  $I_D < I_{DSS}$  and are possible solutions

⇒ so we verify value of  $V_{GS}$ :

$$V_{GS1} = -4 + (4.7 \text{ mA})(1.65 \text{ k}\Omega) = 3.75 \text{ V} < V_p \angle \text{correct solution}$$

$$V_{GS2} = -4 + (7.4 \text{ mA})(1.65 \text{ k}\Omega) = 8.21 \text{ V} > V_p \times \text{wrong solution}$$

p-channel  
S  
D  
 $0 \leq V_{GS} \leq V_p$


Graphical method


•  $I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$

•  $V_{GS} = -4 + (1.65k) I_{DS}$

when  $V_{GS} = -4\text{V} \rightarrow I_{DS} = 0\text{mA}$

 when  $V_{GS} = 0\text{V} \rightarrow I_{DS} = 2.12\text{mA}$



 

## Midpoint Bias $\rightarrow$ FET

### For maximum Symmetrical Swing

- Place Q-point in the middle point of the transfer characteristic to allow for maximum swing between  $I_{DSS}$  and zero


1)  $I_D = 0.5I_{DSS}$

$$0.5I_{DSS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$0.5 = \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$\rightarrow$  2)  $V_D = 0.5V_{DD}$


$$\begin{aligned} \sqrt{\frac{1}{2}} &= 1 - \frac{V_{GS}}{V_P} \\ \frac{V_{GS}}{V_P} &= 1 - \sqrt{\frac{1}{2}} \\ V_{GS} &= V_P (1 - 0.707) \\ &= V_P (0.2928) \\ \therefore V_{GS} &\cong \frac{V_P}{3.41} \end{aligned}$$

 

ENEE236

36

## Example

 

$$V_P = V_{GS(off)} = -3 \text{ V}$$

$$I_{DSS} = 12 \text{ mA}$$

Choose  $R_D$  and  $R_S$  for mid point bias

$$I_D = 0.5 I_{DSS} = 6 \text{ mA}$$

$$V_D = 0.5 V_{DD} = 6 \text{ V}$$

$$V_{GS} = \frac{V_{GS(off)}}{3.4} = \frac{-3}{3.4} = -0.882 \text{ V}$$

$$R_S = \frac{V_S}{I_D} = \frac{0.882}{6 \text{ mA}} = 147 \Omega$$

$$V_{DD} - I_D R_D - V_D = 0$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = 1 \text{ k}\Omega$$


$$\begin{aligned} V_G &= 0 \\ \rightarrow V_S &= V_G - V_{GS} \\ &= 0 - (-0.882) \\ &= 0.882 \\ &= I_D R_S \end{aligned}$$

ENEE236

37

$R_G \rightarrow$  cannot be found from dc analysis  
must be high

# DMOSFET → n-channel

 

$V_P, I_{DSS}$

for  $V_{GS} = 0$   
if  $V_{DD} \uparrow > 0$   
for  $V_{GS} = -1$


$I_D$  becomes less

for  $V_{GS} = V_P$

$I_D \sim 0A$


for  $V_{GS} = +1V$

n-channel JFET

 

## Metal Oxide Semiconductor Field Effect Transistor MOSFET

 - 1) Depletion type MOSFET: DMOSFET
- 2) Enhancement type MOSFET: EMOSFET
- The MOSFET differs from the JFET in that it has no pn junction structure; instead, the gate of the MOSFET is insulated from the channel by a silicon dioxide ( $\text{SiO}_2$ ) layer.
- Due to this the input resistance of MOSFET is greater than JFET.



- Construction of n-channel DMOSFET:





## Operation , characteristic and parameters of DMOSFET

### ◆ n-channel DMOSFET

- On the application of  $V_{DS}$  and keeping  $V_{GS}=0$  electrons from the n-channel are attracted towards positive potential of the drain terminal .
- This establishes current through the channel to be denoted as  $I_{DSS}$  at  $V_{GS}=0$  .
- If we apply negative gate voltage ( $V_{GS} < 0$ ) the negative charge on the gate repel electrons from the channel . The number of repelled electrons depends on the magnitude of the negative voltage  $V_{GS}$ .
- The greater the negative voltage applied at the gate, the level of drain current will be reduced until it reaches zero ;  $V_{GS} = V_P$  .

 


Figure 5.24 n-Channel depletion-type MOSFET with  $V_{GS} = 0\text{ V}$  and an applied drain voltage  $V_{DD}$ .

 


Figure 5.26 Reduction in free carriers in channel due to a negative potential at the gate terminal.



 
 


Figure 5.25 Drain and transfer characteristics for an n-channel depletion-type MOSFET.

 
- For positive value of  $V_{GS}$ , the positive gate will draw additional electrons from the p-type substrate and the drain current increases .



 
Drain characteristics for an n-channel DMOSFET



 
Transfer characteristics for an n-channel DMOSFET



 Drain characteristics for an p-channel DMOSFET



 Transfer characteristics for an p-channel DMOSFET



In the pinch off region

$$i_{DS}(t) = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

◆ For the n- channel

$$V_{GS} > V_P (\text{negative})$$

$$V_{DS} > V_{GS} - V_P$$

◆ For the p- channel

$$V_{GS} < V_P (\text{positive})$$

$$V_{DS} < V_{GS} - V_P$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

→ Depletion mode

$$V_P \leq V_{GS} \leq 0, 0 < I_D \leq I_{DSS}$$

→ Enhancement mode

$$V_{GS} > 0$$

$$I_D > I_{DSS}$$

\*



### Example

Suppose that the DMOSFET is in the pinch off region

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \dots\dots\dots 1$$


$$V_{GS} = V_G - V_S = V_G$$

$$V_G = \frac{11M}{11M + 100M} (12) = 1.19 \text{ v} \dots\dots\dots 2$$

sub 2 into 1 , we obtain

→  $I_{DS} = 6.13 \text{ mA} > I_{DSS}$  !! **THIS IS POSSIBLE AND DMOSFET WILL OPERATE IN ENHANCEMENT MODE**

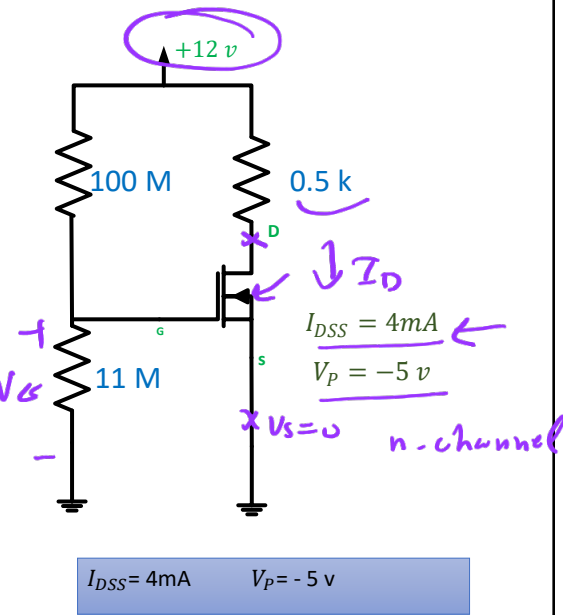→  $V_{DS} = V_{DD} - 0.5K I_{DS} = 8.93 \text{ v}$   
 $V_{DS} > V_{GS} - V_P = 6.19 \text{ v}$  ✓ pinch off region



### E MOSFET (n-channel)

→ no physical channel

→ we will have an induced channel due to  $V_{GS}$


$V_{GS} > V_{GS(th)} = V_T$

→ gate-to-source threshold voltage

→ This is the minimum required voltage to have an induced channel (carriers near the gate)

### Enhancement Type MOSFET


- Construction of n-channel EMOSFET:

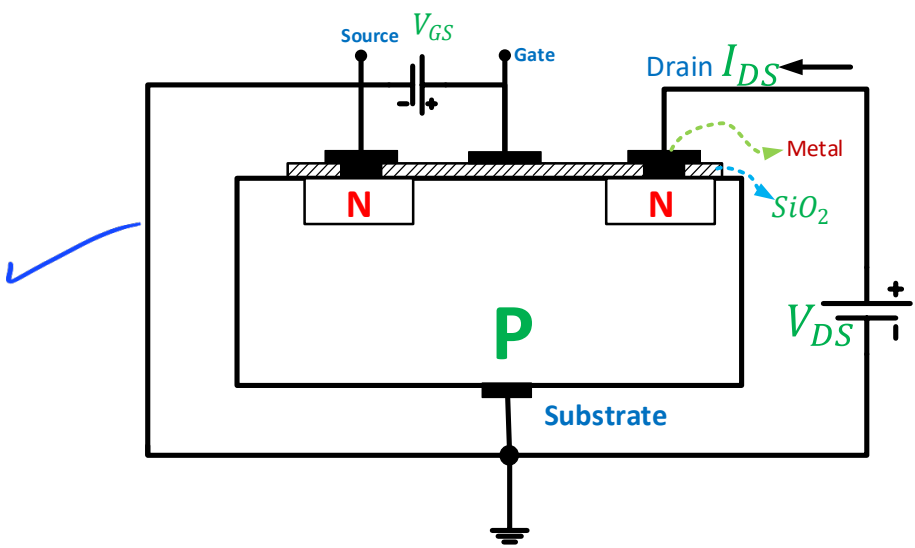

 
## Operation , characteristic and parameters of EMOSFET

- On the application of  $V_{DS}$  and keeping  $V_{GS}=0$  practically zero current flows .
- If we increase  $V_{GS}$  in the positive direction the concentration of electrons near the  $SiO_2$  surface increases ,
- At particular value of  $V_{GS}$  there is a measurable current flow between drain and source ;  $I_{DS}$  .
- This value of  $V_{GS}$  is called threshold voltage denoted by  $V_T$  or  $V_{GS(TH)}$  → not + 25.69 mV  
→ in volts
- A positive  $V_{GS}$  above  $V_T$  induce a channel and hence the drain current ( $I_{DS}$ ) by creating a thin layer of negative charges (electrons) in the substra<sup>it</sup> adjacent to the  $SiO_2$  large .

The conductivity of the channel is enhanced by increasing  $V_{GS}$  and thus pulling more electrons into the channel .




P-channel  
EMOSFET

 


n-channel  
EMOSFET


n-channel  
DMOSFET

 

 Drain characteristics for an n-channel EMOSFET



 Transfer characteristics for an n-channel EMOSFET





End of L18  
sec 11

L19  
12-8-2021


n-channel E MOSFET

  $V_{GS} > V_T$  (or  $V_{GS(th)}$ )  
↑  
Threshold voltage  
(data sheet)




Drain characteristics for an p-channel EMOSFET

**n-channel**

 

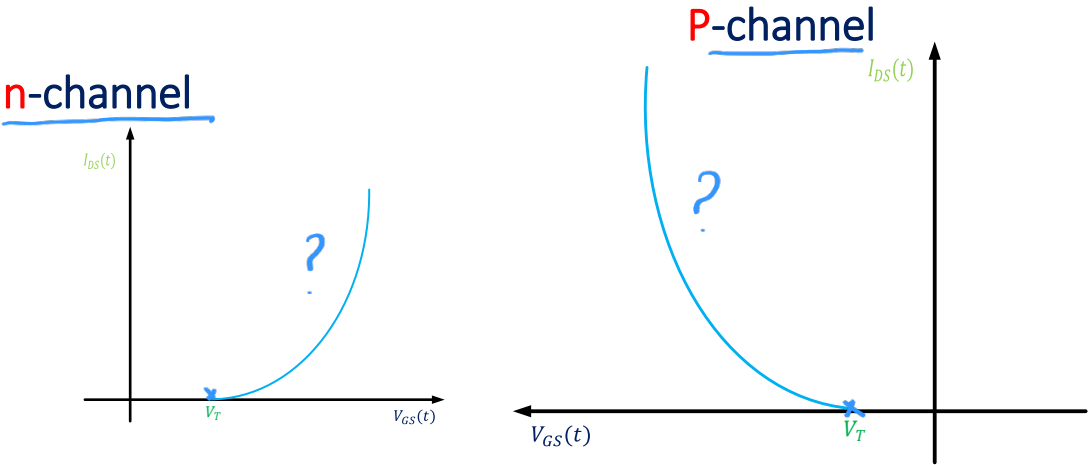Transfer characteristics for an p-channel EMOSFET




$I_D = f(V_{GS}) ?$

$$I_D = K_n (V_{GS} - V_T)^2 \Rightarrow \bar{I}_D = \bar{I}_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$\uparrow$   
EMOSFET

$\uparrow$   
JFET  
DMOSFET



 

In the pinch off region- EMOSFET

$$i_{DS}(t) = K_n (V_{GS}(t) - V_T)^2$$

$$|V_{DS}| > |V_{GS} - V_T|$$

both  
n-channel  
p-channel

$$\begin{array}{ll} V_{GS} > V_T & ; \text{ n-channel} \\ V_{GS} < V_T & ; \text{ p-channel} \end{array}$$




$I_{DS} = I_D = I_S$

Example → Find  $V_{GS}$ ,  $I_D$ ,  $V_{DS}$  ?

$I_D = I_{DS} = K_n(V_{GS} - V_T)^2 \dots\dots\dots 1$

$V_{GS} = V_G - V_S$

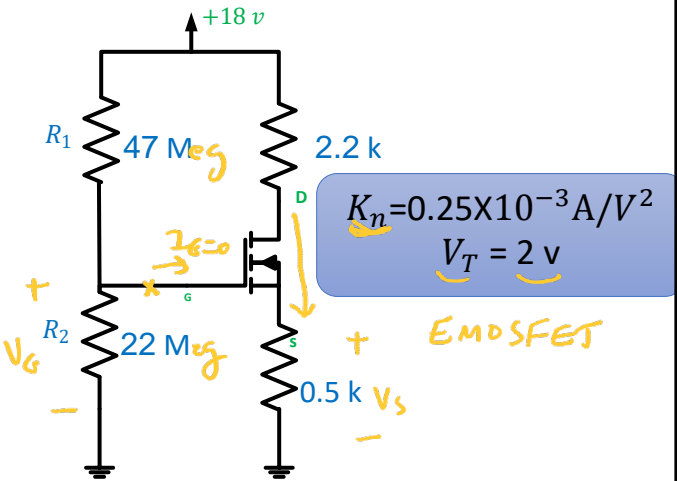$V_G = \frac{22M}{22M + 47M}(18) = 5.74V$



$$I_D = \frac{5.74 - V_{GS}}{500}$$

$$I_D = K_n (V_{GS} - V_T)^2$$

معادله  
کریمیه  
 $V_{GS}$

$$V_S = (0.5K) I_{DS}$$

$$V_{GS} = 5.74 - (0.5K) I_{DS} \dots\dots\dots 2$$

$V_G - V_S$


solving for  $V_{GS}$ :  $\rightarrow$

$$V_{GS} = 4.78\text{v} \quad \checkmark$$
$$= -8.78\text{v} \quad \times < V_T$$

$$I_{DS} = 1.92\text{mA} = I_D$$

$$V_{DS} = 12.82 > |V_{GS} - V_T|$$


$|4.78 - 2| = 2.78$

 

$$K_n = 0.25 \times 10^{-3} \text{ A/V}^2$$
$$V_T = 2\text{V}$$

$$V_{DS} = 18 - I_D (2.2\text{k} + 0.5\text{k})$$
$$= 18 - 1.92\text{m} (2.7\text{k})$$
$$= 12.82 \checkmark$$

$V_{GS} > V_T$

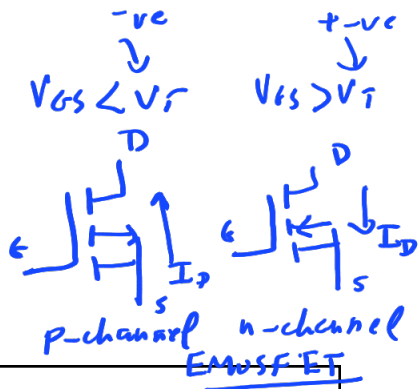

# Complementary MOS (cmos) inverter


$V_{GS1} = V_{G1} - V_{S1} = 10 - 0 = 10 \text{ v} > V_{T1}$  ✓ ON


1) Let  $V_S(t) = 10 \text{ v}$   $[0, t_1]$

$V_{GS2} = V_{G2} - V_{S2} = 10 - 10 = 0 \text{ v} < V_{T2}$  ✗ OFF

$Q_1$  is on , replaced with short circuit

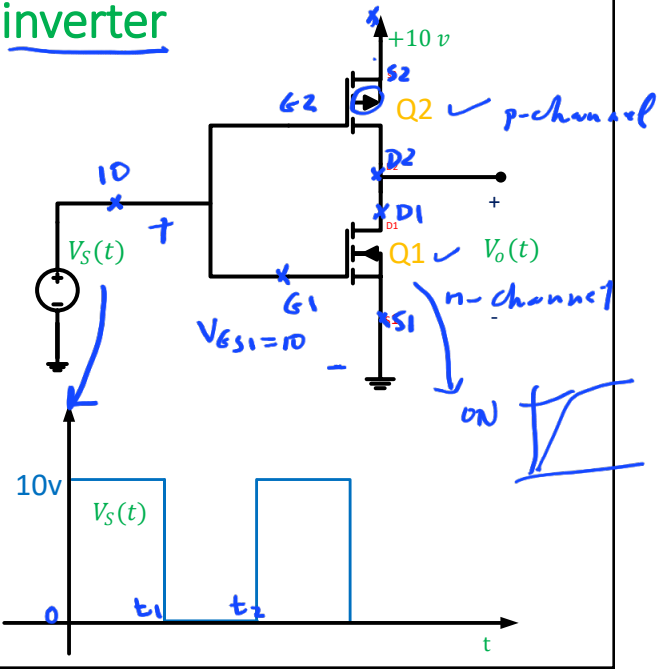$Q_2$  is off , replaced with open circuit



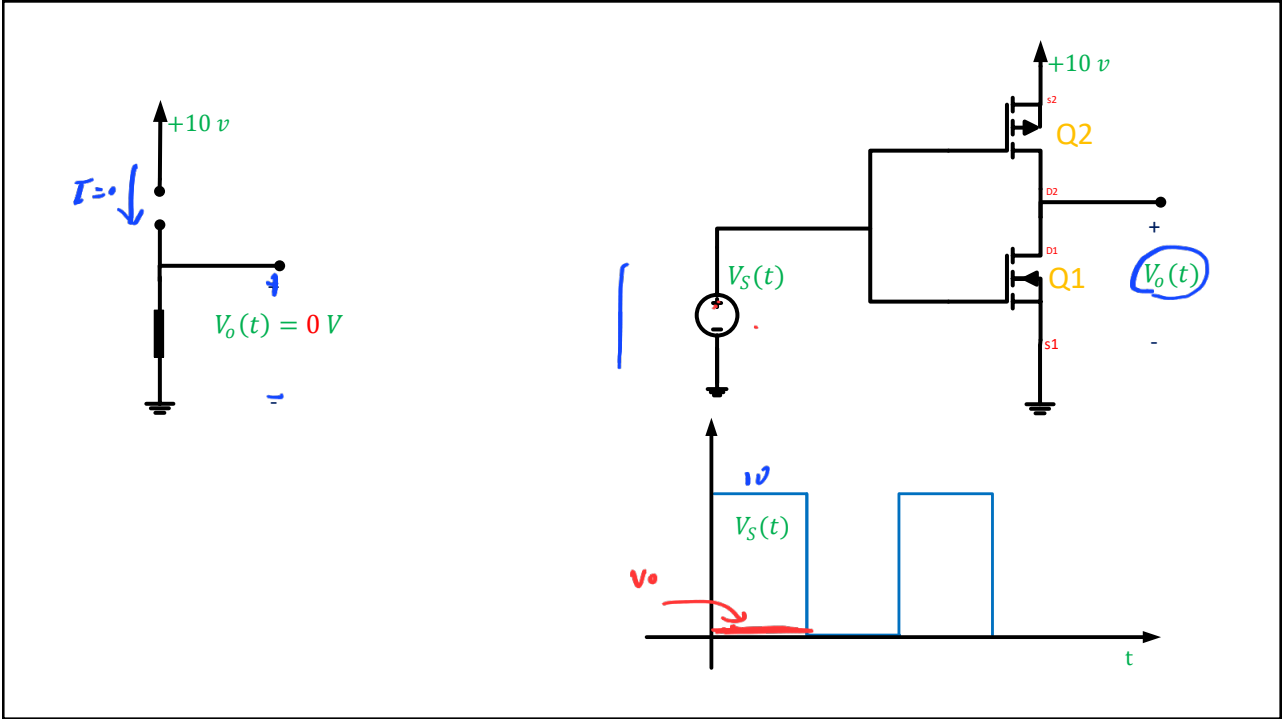

[t<sub>1</sub> - t<sub>2</sub>]


2) Let  $V_S(t) = 0\text{ v}$

$V_{GS1} = V_{G1} - V_{S1} = 0 = 0\text{ v} < V_{T1} \rightarrow \text{OFF}$


Q<sub>1</sub> is off , replaced with open circuit

$V_{GS2} = V_{G2} - V_{S2} = 0 - 10 = -10\text{ v} < V_{T2} \rightarrow \text{ON}$

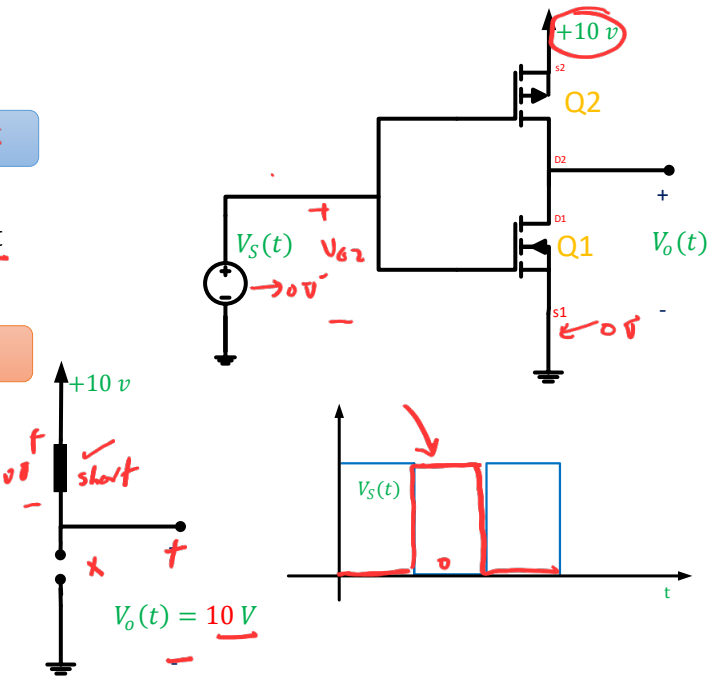Q<sub>2</sub> is off , replaced with short circuit



Inverter = NOT GATE

 

CMOS - inverter



