

Circuit Analysis

By

Jibreel Bornat

Chapter 8

Birzeit University

2025

Chapter 8

Natural and Step Response of RLC Circuits

It's when we have resistor, inductor and capacitor (RLC) in the same circuit, either they are connected in series or parallel, and this is called second order differential equation


1 - parallel RLC circuits

We have two cases

1.1 - natural response

to find the DE apply KCL

$$i_R + i_L + i_C = 0$$

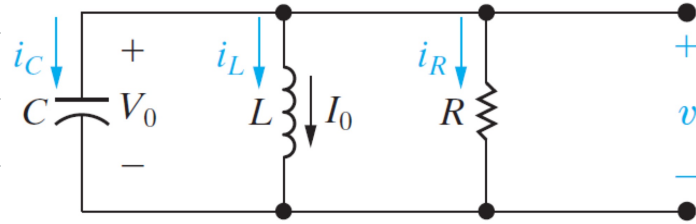

important to find the initial conditions

$$\frac{V(t)}{R} + \frac{1}{L} \int V(t) dt + C \frac{dV}{dt} = -i_L(0^-)$$

resonant frequency

$$\omega = \frac{1}{\sqrt{LC}}$$

Neper frequency

$$\alpha = \frac{1}{2RC}$$

$$s_1 = -\alpha - \sqrt{\alpha^2 - \omega^2}$$

$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega^2}$$

① if $\alpha^2 > \omega^2$, the solutions are real distinct

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \Rightarrow \text{Over Damped}$$

② if $\alpha^2 = \omega^2$, the solutions are real similar

$$V(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t} \Rightarrow \text{Critical Damped}$$

③ if $\alpha^2 < \omega^2$, the solutions are complex


$$\text{let } \omega_d = \sqrt{\omega^2 - \alpha^2}$$

$$V(t) = e^{-\alpha t} (\beta_1 \cos \omega_d t + \beta_2 \sin \omega_d t) \Rightarrow \text{Under Damped}$$

Example 1

$$V_C(0^+) = 12V, \quad i_L(0^+) = 30mA$$

Find $V(t)$?

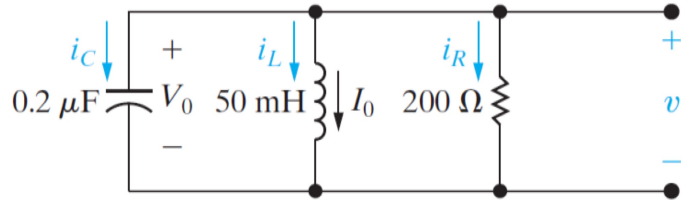

Step 1 - Find s_1 and s_2

$$\alpha = 1/2RC \Rightarrow \alpha = 1/2 \times 200 \times 0.2 \times 10^{-6} \Rightarrow \alpha = 1.25 \times 10^4$$
$$\omega = 1/\sqrt{LC} \Rightarrow \omega = 1/\sqrt{50 \times 0.2 \times 10^{-9}} \Rightarrow \omega = 10^4$$

$$s_1 = -\alpha - \sqrt{\alpha^2 - \omega^2} \Rightarrow s_1 = -1.25 \times 10^4 - 7500 \Rightarrow s_1 = -20,000$$
$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega^2} \Rightarrow s_2 = -1.25 \times 10^4 + 7500 \Rightarrow s_2 = -5,000$$

$$V(t) = A_1 e^{-20000t} + A_2 e^{-5000t} \quad \text{--- (1)}$$

Step 2 - find the initial conditions

i have $V(0^+)$, so i have to find $V'(0^+)$ first derivative

$$\frac{dV}{dt} = \frac{i_C(0^+)}{C}, \quad \text{by applying KCL to find } i_C(0^+)$$

$$i_C(0^+) = -i_L - i_R \Rightarrow i_C = 30 \times 10^{-3} - \frac{12}{200}$$
$$\Rightarrow i_C(0^+) = -90mA$$

$$\frac{dV}{dt} = \frac{-90 \times 10^{-3}}{0.2 \times 10^{-6}} \Rightarrow \frac{dV}{dt} = -450KV$$

Step 3 - Find the first derivative of eq. 1 then find A_1, A_2

$$V'(t) = -20000 A_1 e^{-20000t} - 5000 A_2 e^{-5000t} \quad \text{--- (2)}$$

apply the initial conditions to get 2 equations

$$12 = A_1 + A_2$$

$$-450K = -20000 A_1 - 5000 A_2$$

$$\left. \begin{array}{l} 12 = A_1 + A_2 \\ -450K = -20000 A_1 - 5000 A_2 \end{array} \right\} \text{Solve } \begin{array}{l} A_1 = -14 \\ A_2 = 26 \end{array}$$

$$\text{hence :- } V(t) = 26 e^{-20000t} - 14 e^{-5000t}$$

1.2 - step response

$$X(t) = X_n(t) + X_f(t)$$

• $X_n(t)$: natural response.

• $X_f(t)$: step response


* if(t) = current source , $V_f(t)$ = voltage source

Example 2

The initial stored energy = 0

$$R = 625 \Omega, I = 24 \text{ mA}$$

Find $i_L(t)$

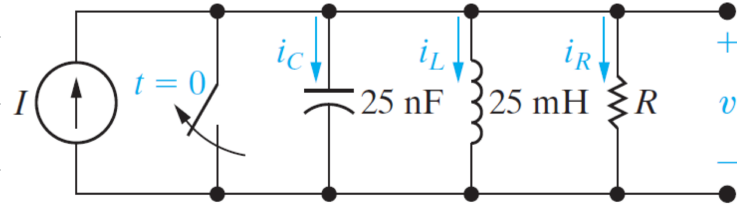

Step 1 - Solve normal as natural

$$\alpha = 1/2RC \Rightarrow \alpha = 1/3.125 \times 10^{-5} \Rightarrow \alpha = 32 \times 10^3$$

$$\omega = 1/\sqrt{LC} \Rightarrow \omega = 1/2.5 \times 10^{-5} \Rightarrow \omega = 40 \times 10^3$$

Since $\omega > \alpha$ we apply $\Rightarrow \omega_d = \sqrt{\omega^2 - \alpha^2}$

$$\omega_d = \sqrt{1.6 \times 10^9 - 1.024 \times 10^9} \Rightarrow \omega_d = 24 \times 10^3$$

$$\begin{aligned} i_n(t) &= e^{-\alpha t} (\beta_1 \cos \omega_d t + \beta_2 \sin \omega_d t) \\ &= e^{-32000t} (\beta_1 \cos 24000t + \beta_2 \sin 24000t) \end{aligned}$$

$$\therefore i(t) = 24 + e^{-32000t} (\beta_1 \cos 24000t + \beta_2 \sin 24000t)$$

* Note : initial conditions are found for the final equation

Since the initial stored energy = 0 $\Rightarrow i(0^+) = V(0^+) = 0$

$$V(0^+) = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{V(0^+)}{L} = \frac{0}{L} \Rightarrow \frac{di}{dt} = 0$$

Step 2 - get the first derivative of $i(t)$ then solve when $t=0$

$$\begin{aligned} 24 + \beta_1 &= 0 \Rightarrow \beta_1 = -24 \quad \text{--- (1)} \\ -32000\beta_1 + 24000\beta_2 &= 0 \quad \text{--- (2)} \end{aligned} \quad \left\{ \begin{array}{l} \beta_1 = -24 \\ \beta_2 = -32 \end{array} \right.$$

$$i(t) = 24 + e^{-32000t} (-24 \cos 24000t - 32 \sin 24000t)$$


2 - Series RLC circuits

We have two cases

2.1 - step response

to find the DE apply KVL

$$V_R + V_L + V_C = 0$$

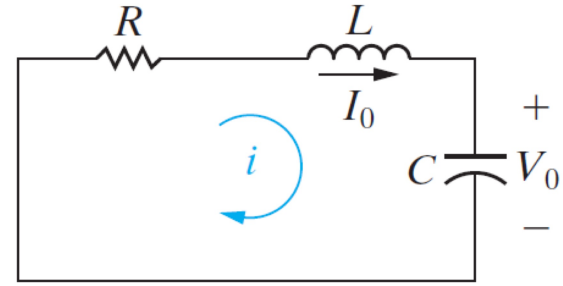

important to find the initial conditions

$$iR + \frac{1}{C} \int_0^t i(t) dt + L \frac{di}{dt} = -V_C(0^-)$$

Same as parallel

resonant frequency

$$\omega = \frac{1}{\sqrt{LC}}$$

Neper frequency

$$\alpha = \frac{R}{2L}$$

Same as parallel

$$s_1 = -\alpha - \sqrt{\alpha^2 - \omega^2}$$

$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega^2}$$

Same as parallel

① if $\alpha^2 > \omega^2$, the solutions are real distinct

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \Rightarrow \text{Over Damped}$$


② if $\alpha^2 = \omega^2$, the solutions are real similar

$$V(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t} \Rightarrow \text{Critical Damped}$$


③ if $\alpha^2 < \omega^2$, the solutions are Complex

$$\text{let } \omega_d = \sqrt{\omega^2 - \alpha^2}$$
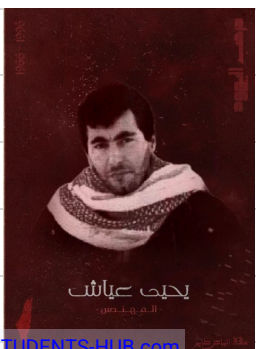
$$V(t) = e^{-\alpha t} (\beta_1 \cos \omega_d t + \beta_2 \sin \omega_d t) \Rightarrow \text{Under Damped}$$




وَمَنْ يَتَوَكَّلْ عَلَى اللَّهِ فَهُوَ مَكْبُ

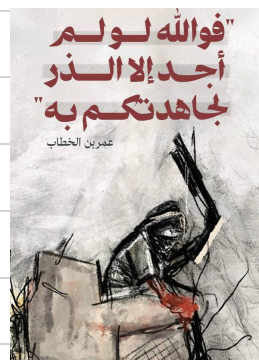

Example 1

$$V_C(0^-) = 100 \text{ V}$$

Find $i(t)$

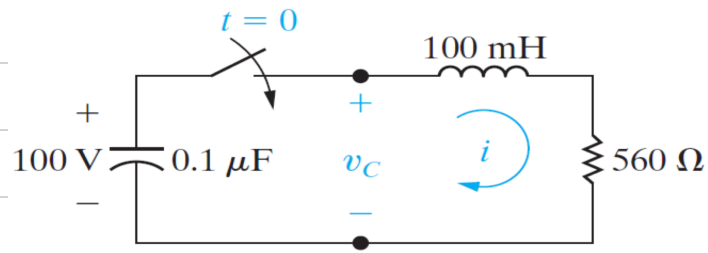

$$\alpha = R/2L \Rightarrow \alpha = 560 / 2 \times 100 \times 10^{-3} \Rightarrow \alpha = 2800$$

$$\omega = 1/\sqrt{LC} \Rightarrow \omega = 1/\sqrt{10^{-8}} \Rightarrow \omega = 10000$$

$$\omega_d = \sqrt{\omega^2 - \alpha^2} \Rightarrow \omega_d = \sqrt{92.16 \times 10^6} \Rightarrow \omega_d = 9600$$

$$i(t) = e^{-2800t} (\beta_1 \cos 9600t + \beta_2 \sin 9600t)$$

Initial Conditions :-

The circuit was opened $\Rightarrow i(0^-) = 0$

$$V_C = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{V_C(0^-)}{L} = \frac{100}{100 \times 10^{-3}} \Rightarrow \frac{di}{dt} = 1000 \text{ A}$$

differentiate $i(t)$:-

$$\begin{aligned} & \left((e^{-2800t} \times -9600 \beta_1 \sin 9600t) + (\beta_1 \cos 9600t \times -2800 e^{-2800t}) \right) \\ & \quad \text{First Part} \\ & + \left((e^{-2800t} \times 9600 \beta_2 \cos 9600t) + (\beta_2 \sin 9600t \times -2800 e^{-2800t}) \right) \\ & \quad \text{Second Part} \end{aligned}$$

Solve when $t = 0$:-

from the first equation $\Rightarrow \beta_1 = 0$

from the second equation :

$$(1 \times 0) + (\beta_1 \times -2800) + (1 \times 9600 \beta_2) + (0 \times 1) = 1000$$

$$-2800 \beta_1 + 9600 \beta_2 = 1000$$

$$-2800 \times 0 + 9600 \beta_2 = 1000$$

$$9600 \beta_2 = 1000 \Rightarrow \beta_2 = \frac{1000}{9600} \Rightarrow \beta_2 = 0.104$$

$$i(t) = e^{-2800t} \times 0.104 \sin 9600t$$

2.2 - step response


$$X(t) = X_n(t) + X_f(t)$$

- $X_n(t)$: natural response
- $X_f(t)$: step response

* $i_f(t)$ = current source , $V_f(t)$ = voltage source

Example 2

No energy is stored at C, L
Find $V(t)$

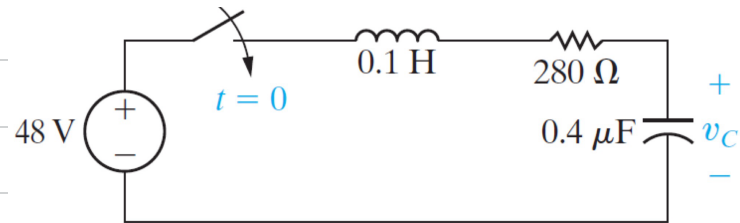

$$\alpha = R/2L \Rightarrow \alpha = 280/2 \times 0.1 \Rightarrow \alpha = 1400$$

$$\omega = 1/\sqrt{LC} \Rightarrow \omega = 1/\sqrt{4 \times 10^{-8}} \Rightarrow \omega = 5000$$

$$\omega_d = \sqrt{\omega^2 - \alpha^2} \Rightarrow \omega_d = \sqrt{23 \times 10^6} \Rightarrow \omega_d = 4800$$

$$V_n(t) = e^{-1400t} (\beta_1 \cos 4800t + \beta_2 \sin 4800t)$$

$V(0^-) = 0$ since the initial stored energy = 0

$$i(0^-) = 0 = C \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = 0$$

After getting the equations $\Rightarrow \beta_1 = -48$
 $\beta_2 = -14$

$$V(t) = V_f(t) + V_n(t)$$

$$V(t) = 48 + e^{-1400t} (-48 \cos 4800t - 14 \sin 4800t)$$